

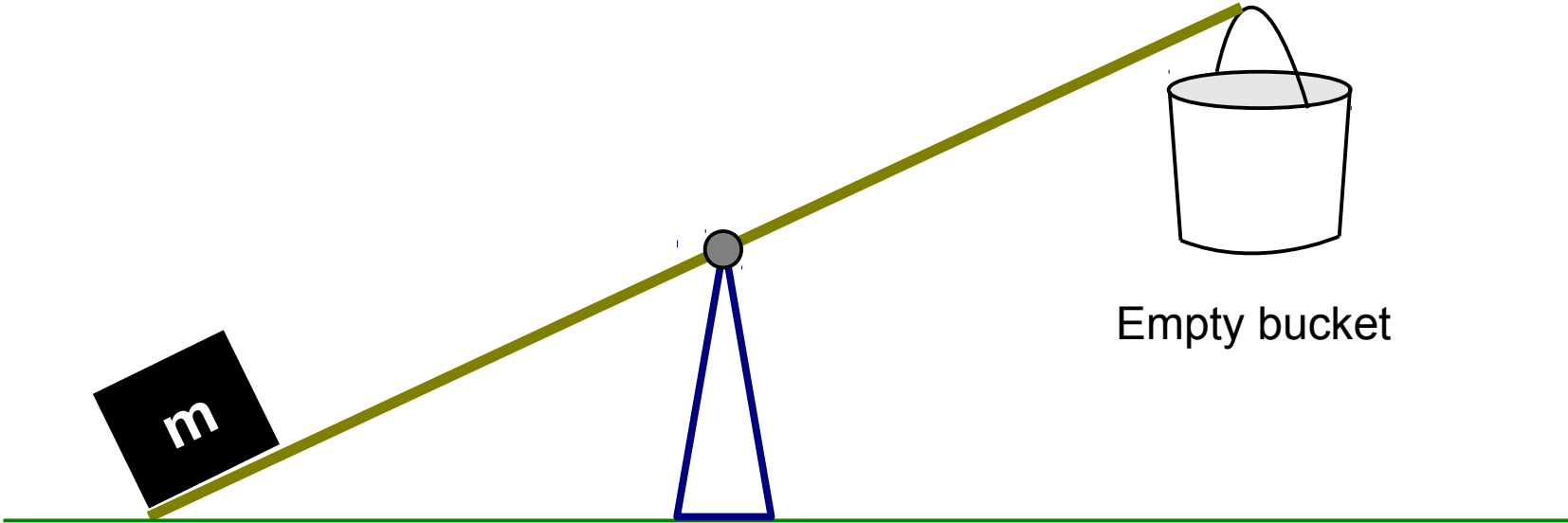



Lab 11: Relaxation oscillators

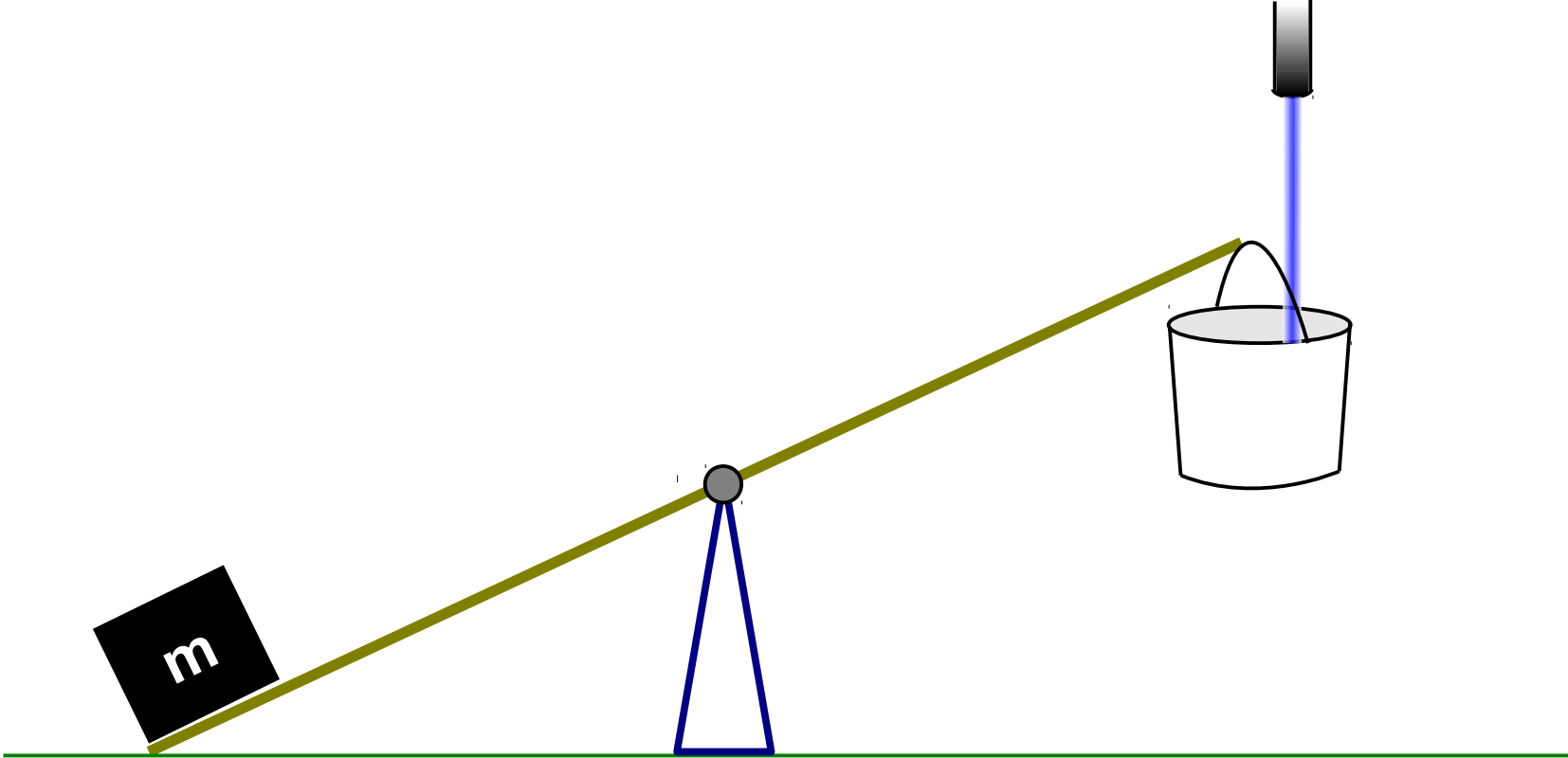



Empty bucket

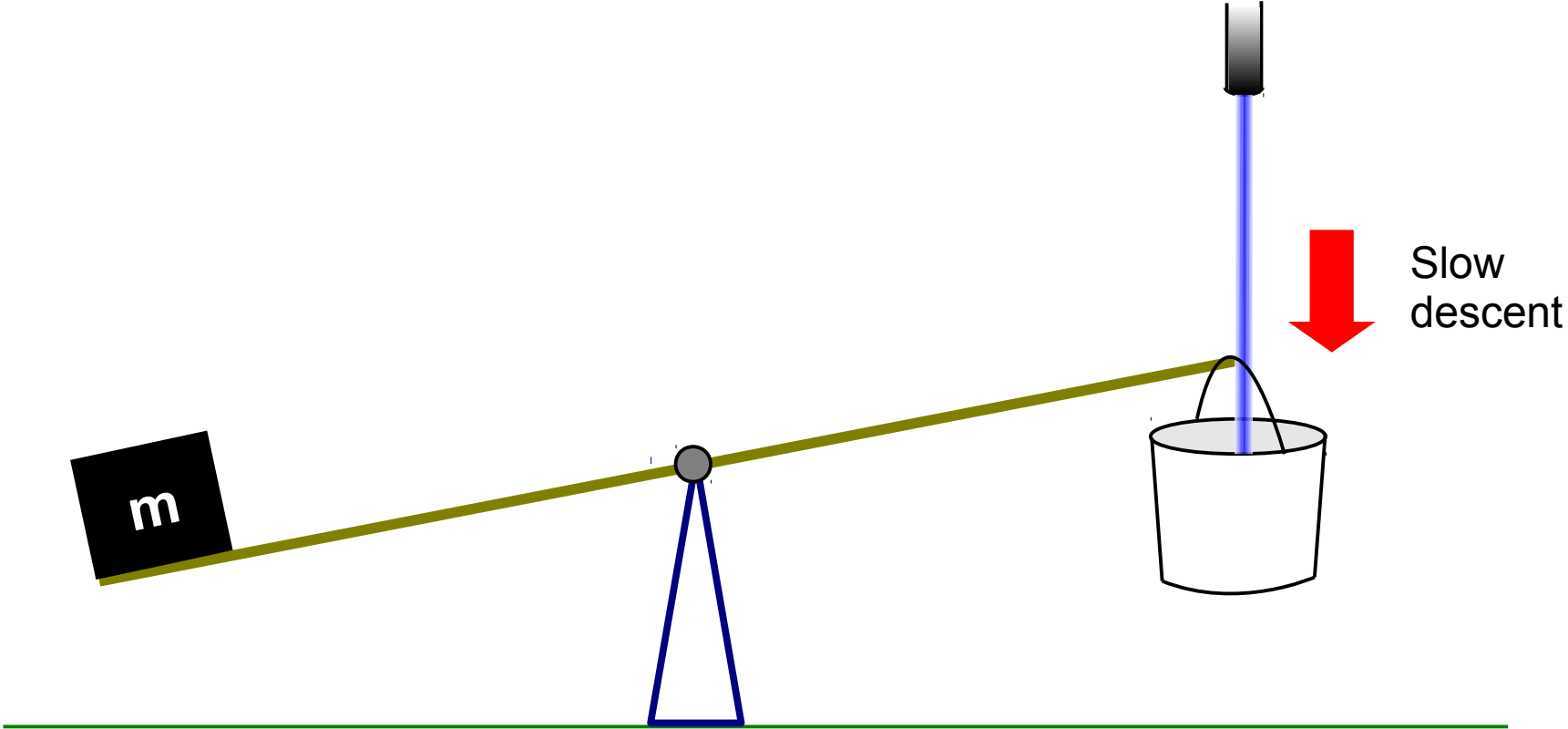



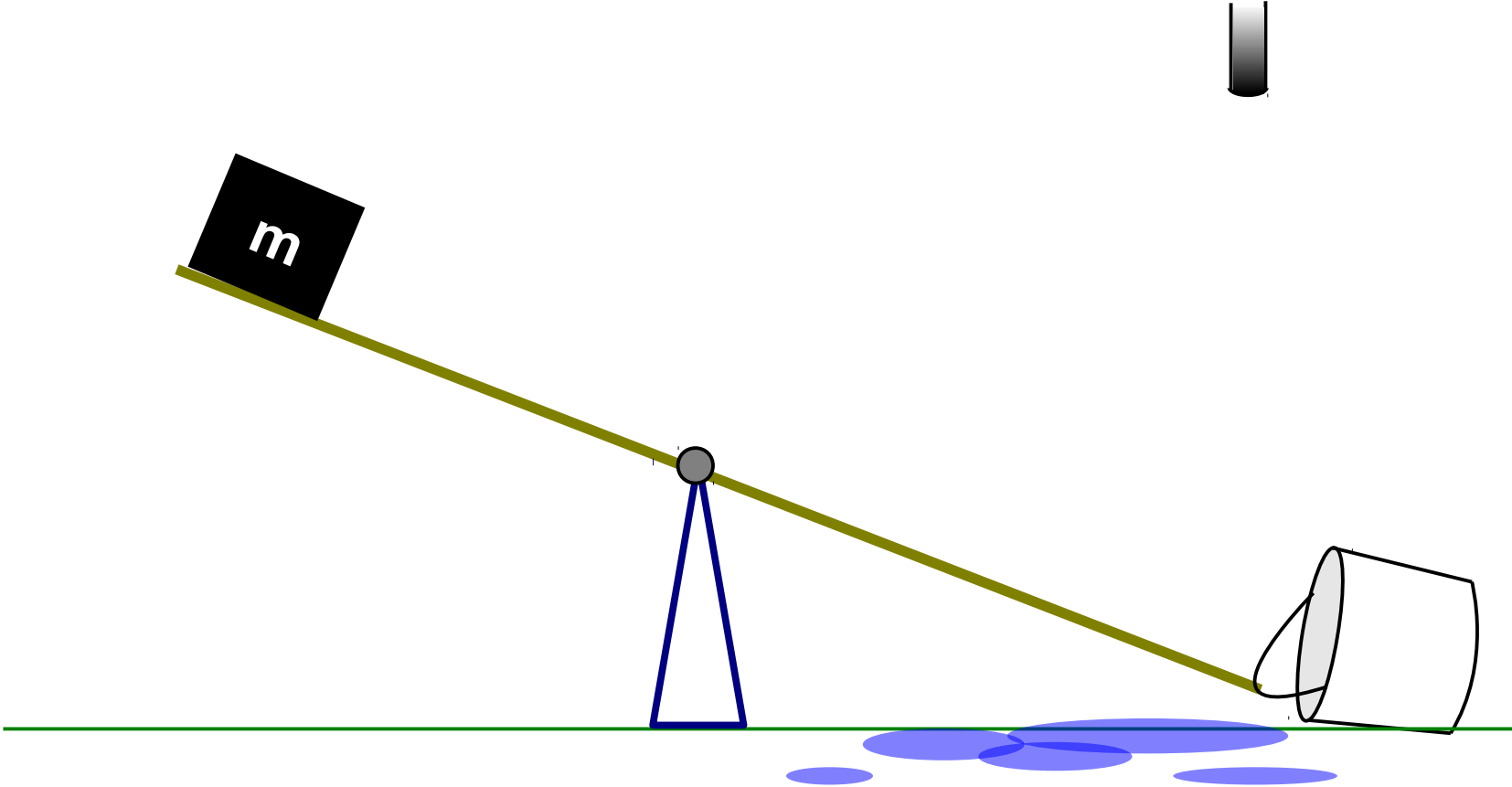

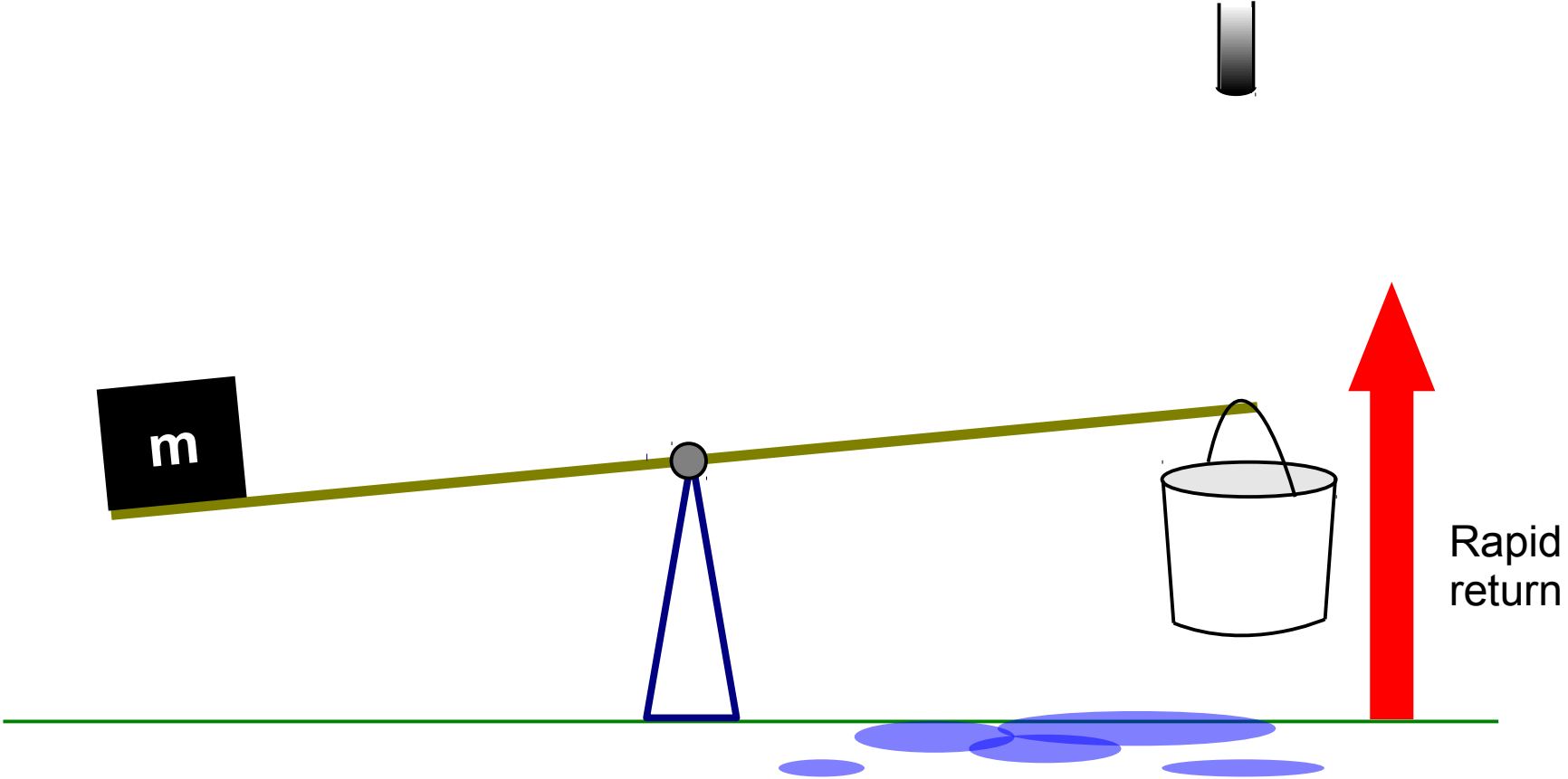

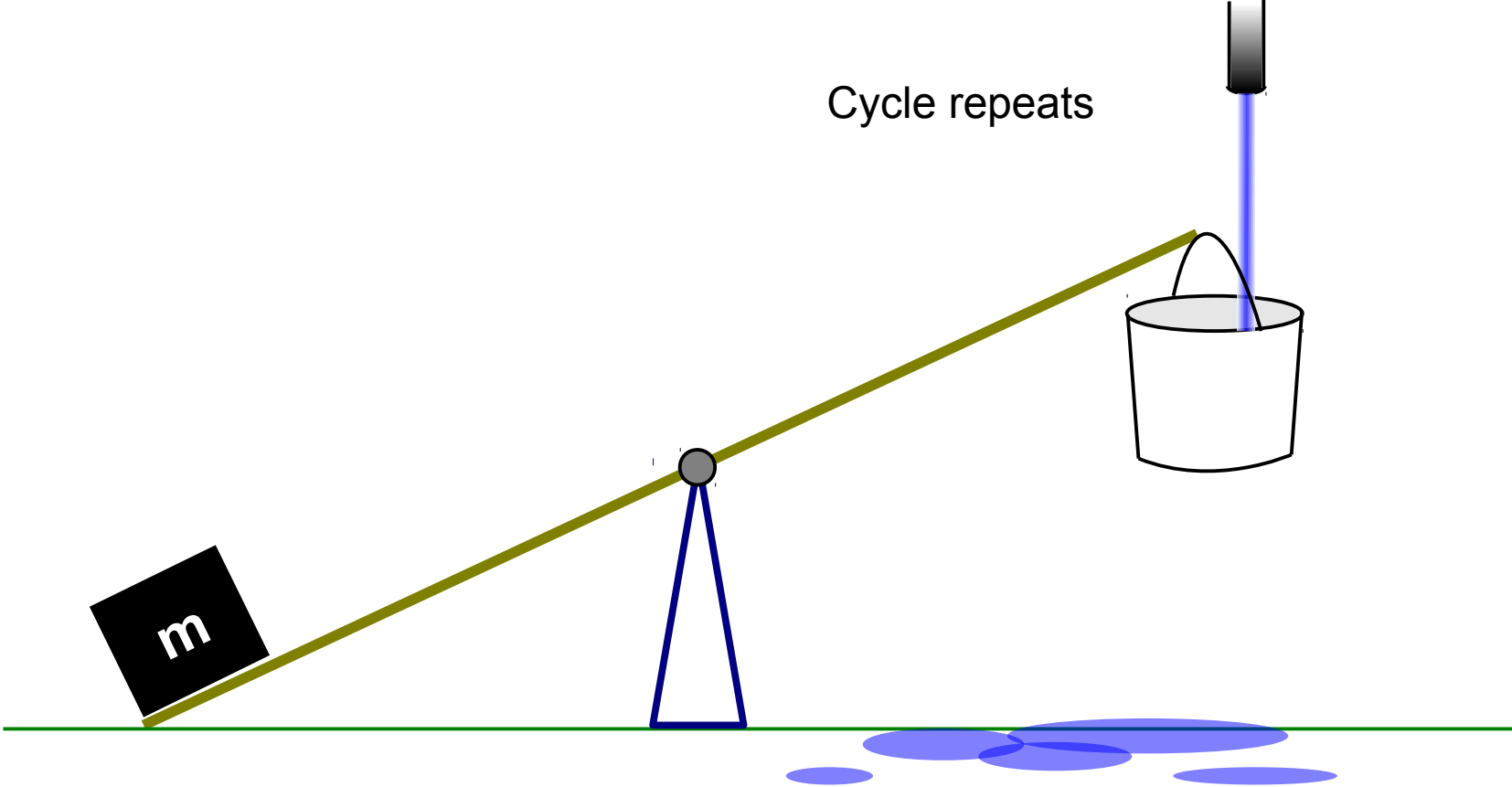

Relaxation oscillators:

Cycle of adding and dissipating energy

Asymmetric, non-sinusoidal time behavior


Examples:

- Laser physics
- Heart muscle
- Vocal cords
- Predator-prey population cycles



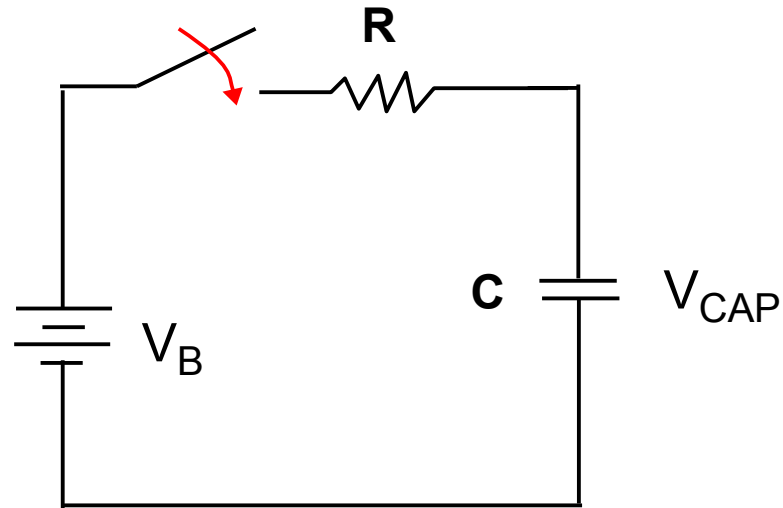B. van der Pol
(1889-1959)


Storing and releasing energy with a capacitor




Determine charging rate

Don't use impedance $Z = 1/j\omega C$


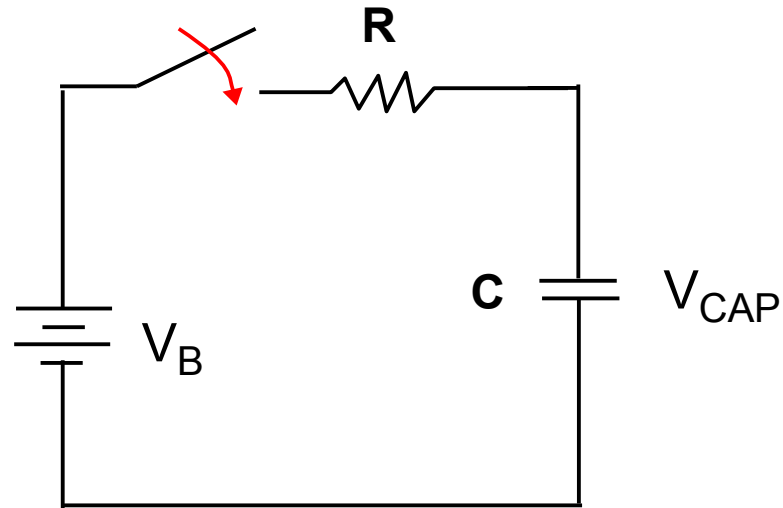
Storing and releasing energy with a capacitor




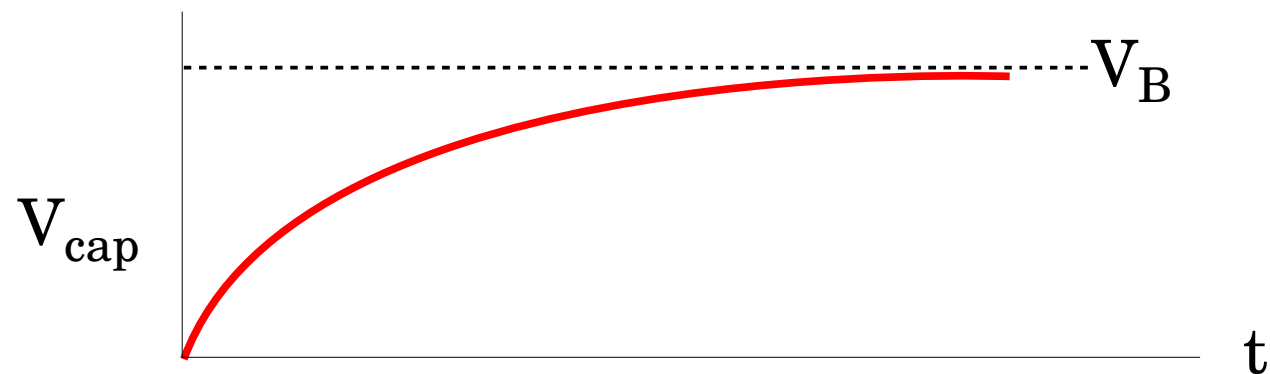
$$V_{\text{cap}} = V_B \left(1 - e^{-t/RC}\right) = V_B \left(1 - e^{-t/\tau}\right)$$



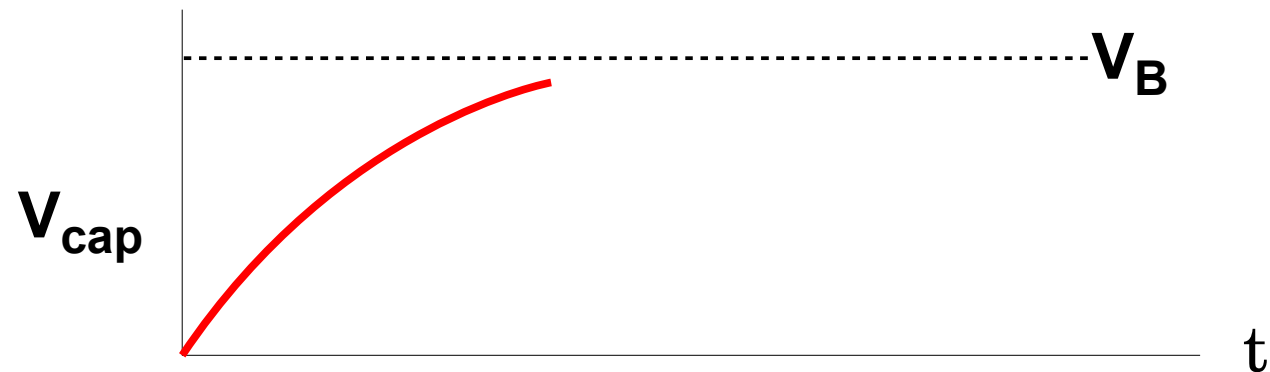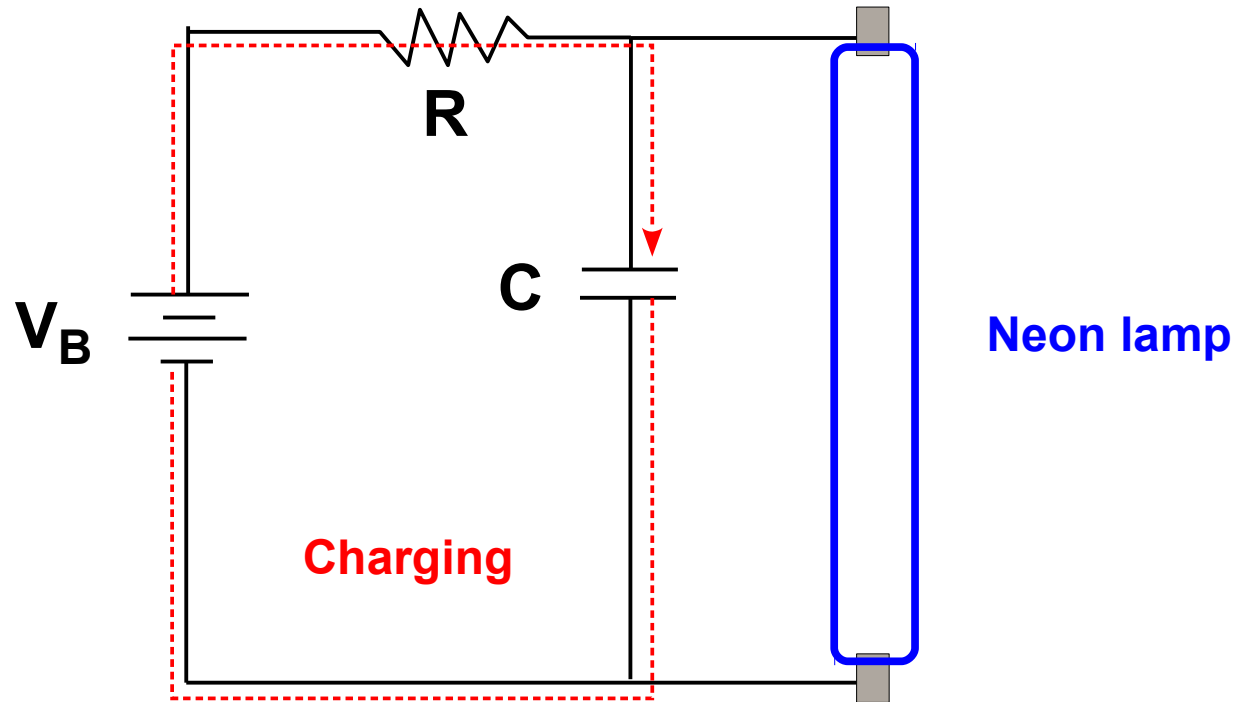Storing and releasing energy with a capacitor




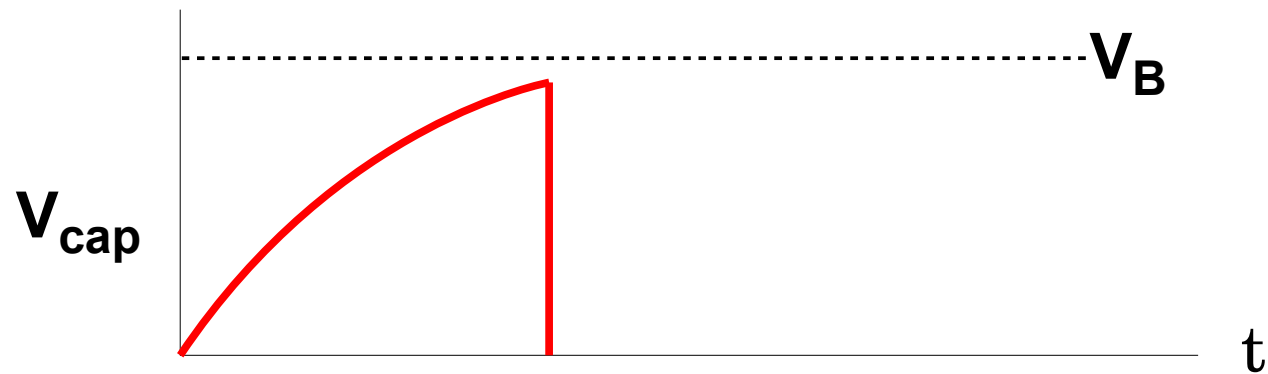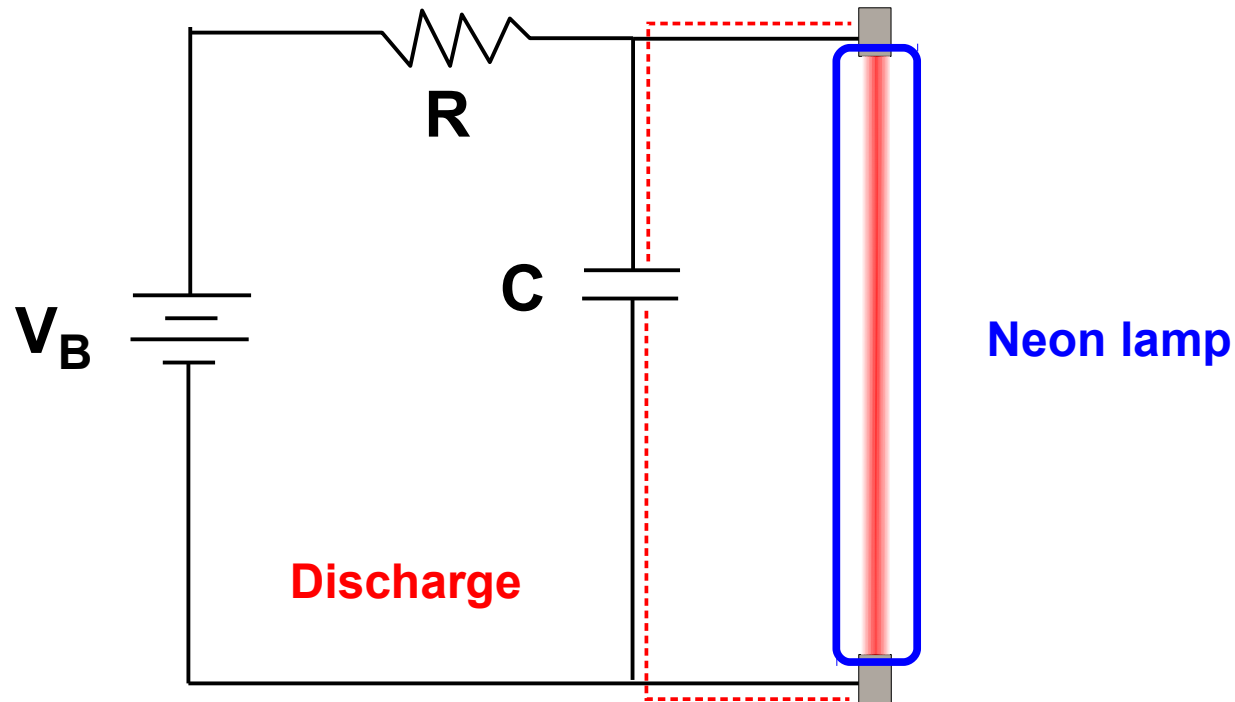Storing and releasing energy with a capacitor




Neon Lamp Relaxation Oscillator

Waveform Chart

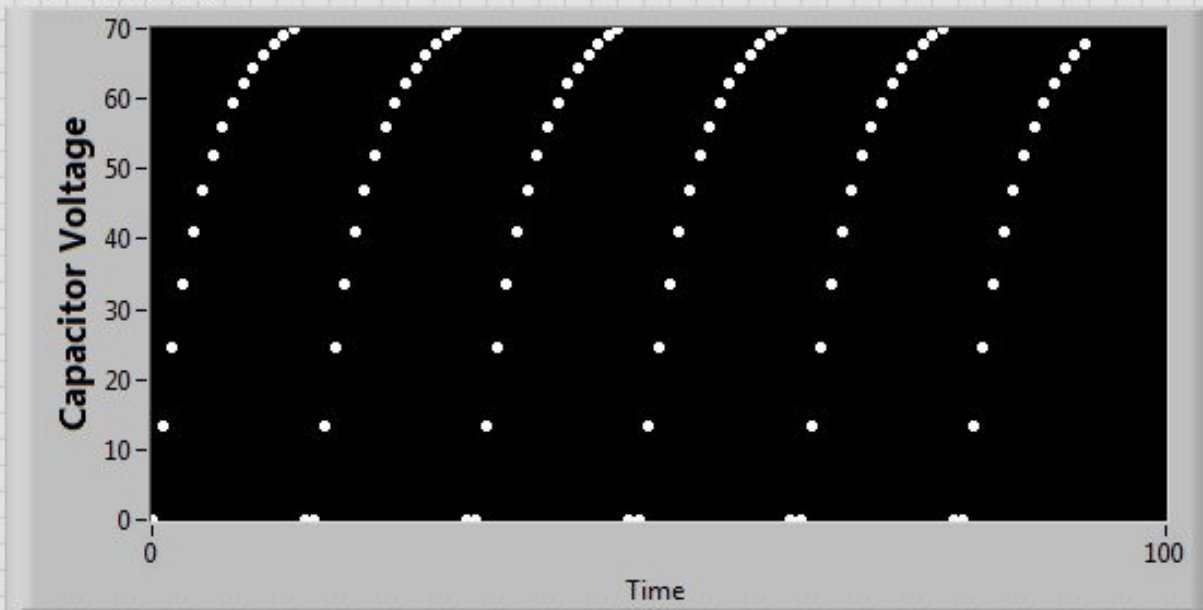


STOP

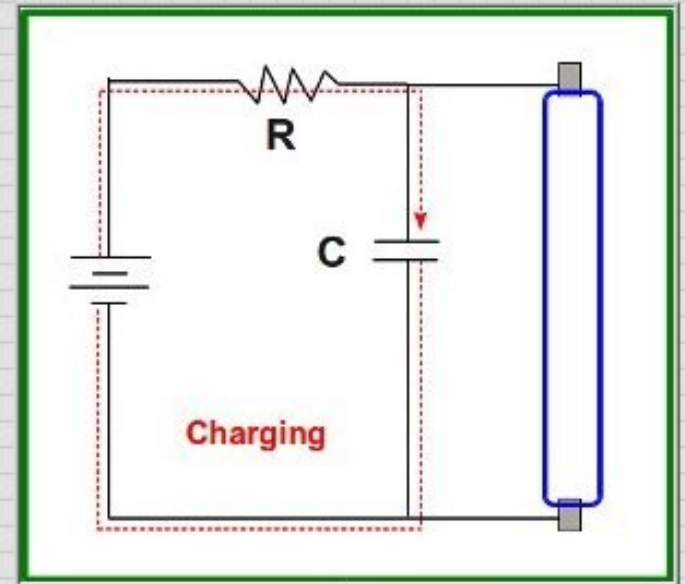


100- **DC voltage** R $1E+6$ C $1E-6$
75- **74.5** Time constant (sec) 1
50- dt 0.2
25-
0-

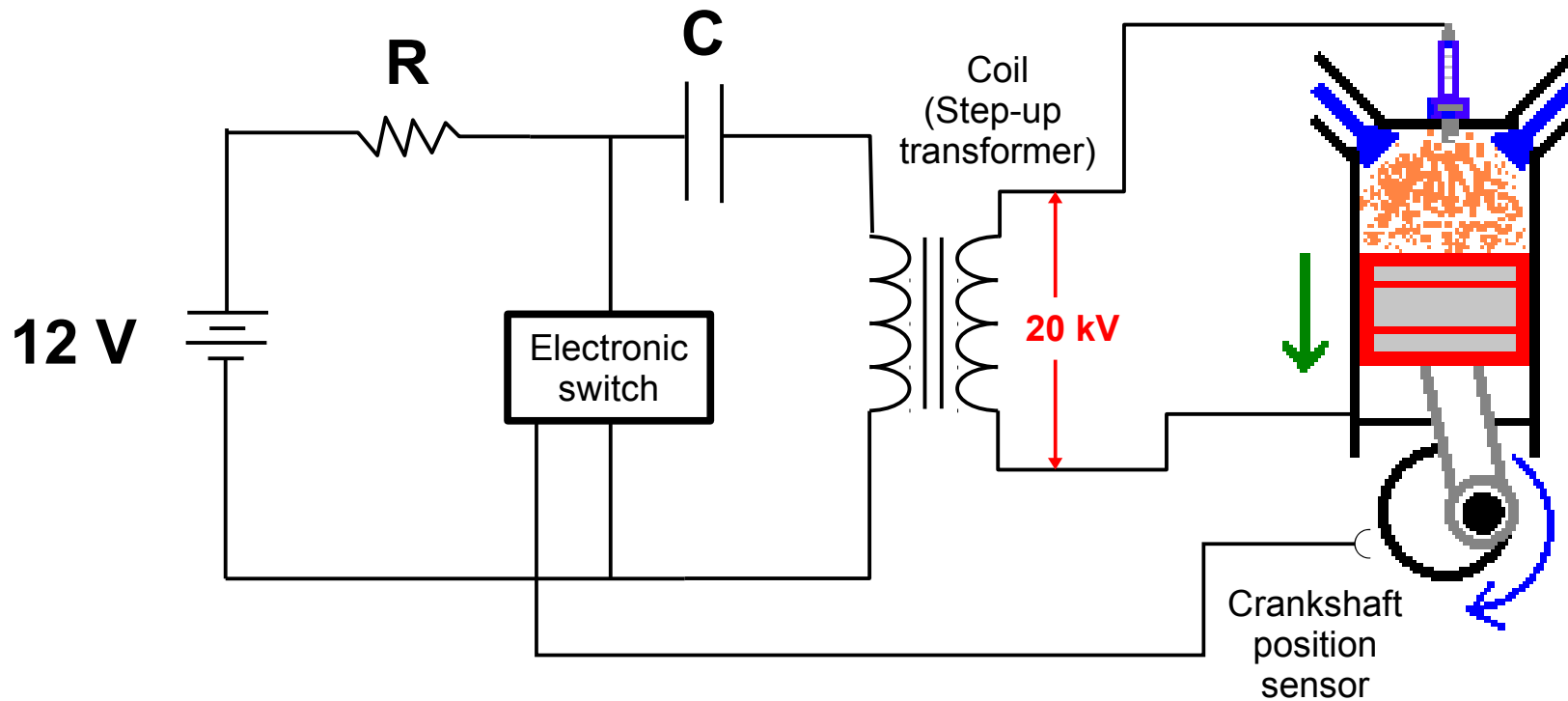Storing and releasing energy with a capacitor: Capacitive discharge ignition




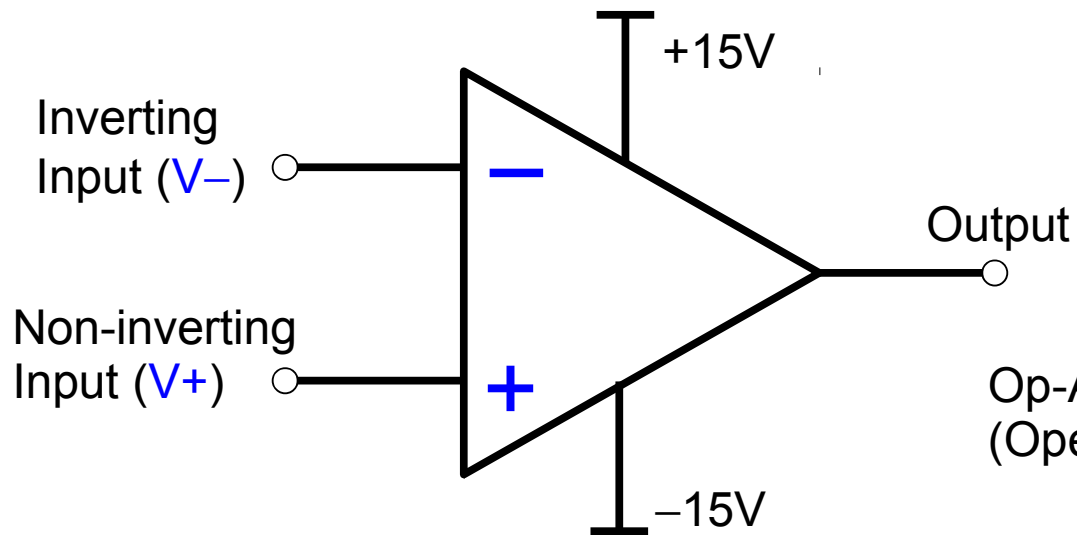Relaxation oscillator: Implementation with Op-Amp



Op-Amp without feedback: Infinite gain
(Open loop gain of ideal Op-Amp)

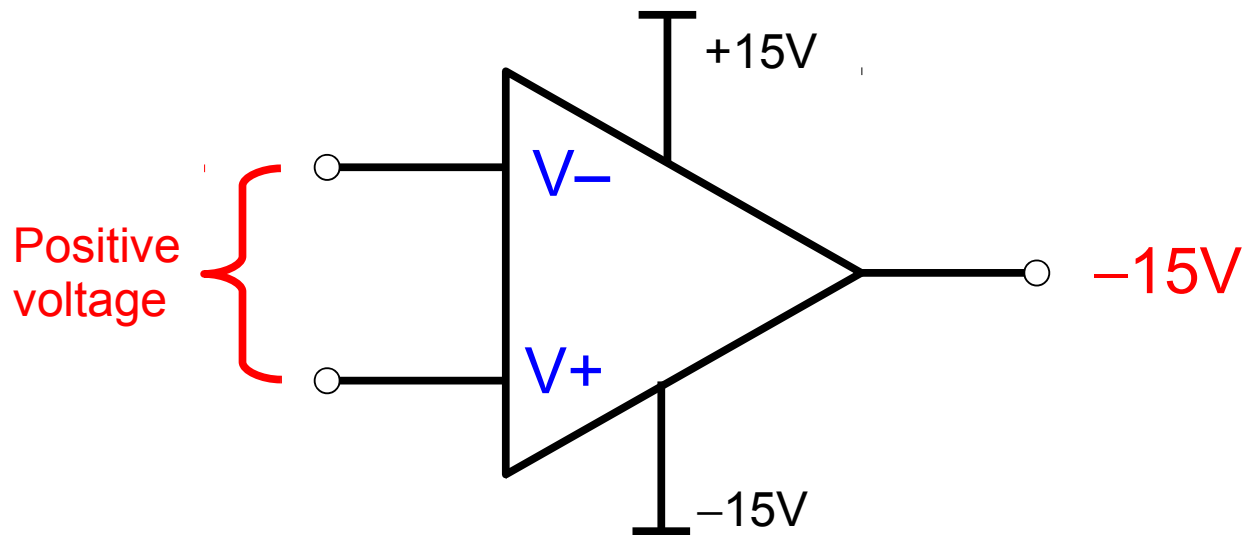Relaxation oscillator: Implementation with Op-Amp




$V-$ greater than $V+$

Output drives to negative ∞

Clamped at $-15V$ of power supply

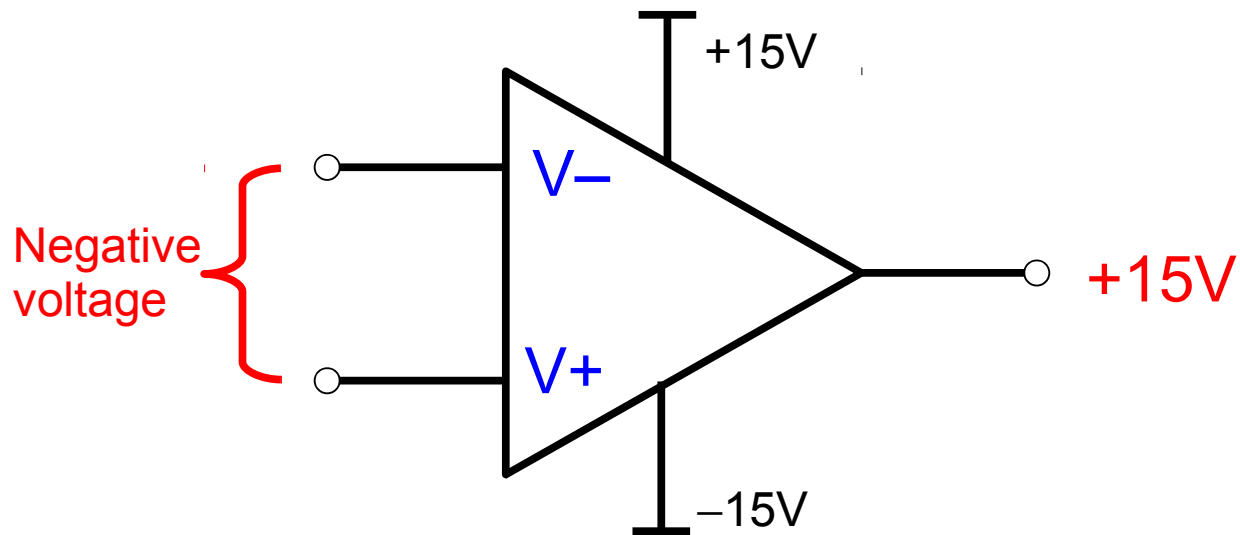Relaxation oscillator: Implementation with Op-Amp




$V+$ greater than $V-$

Output drives to positive ∞

Clamped at $+15V$ of power supply

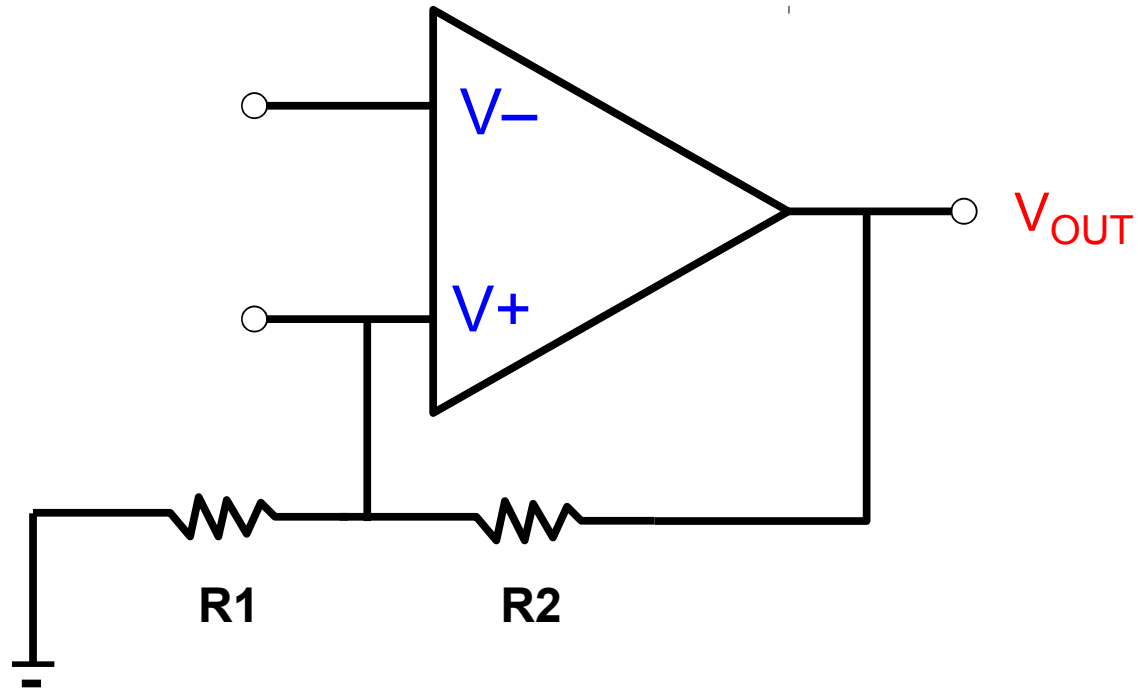Relaxation oscillator: Implementation with Op-Amp




Make V_+ a reference voltage

Voltage divider: $R_1 = R_2$

$$V_+ = \frac{1}{2} V_{OUT} = +7.5V \text{ or } -7.5V$$

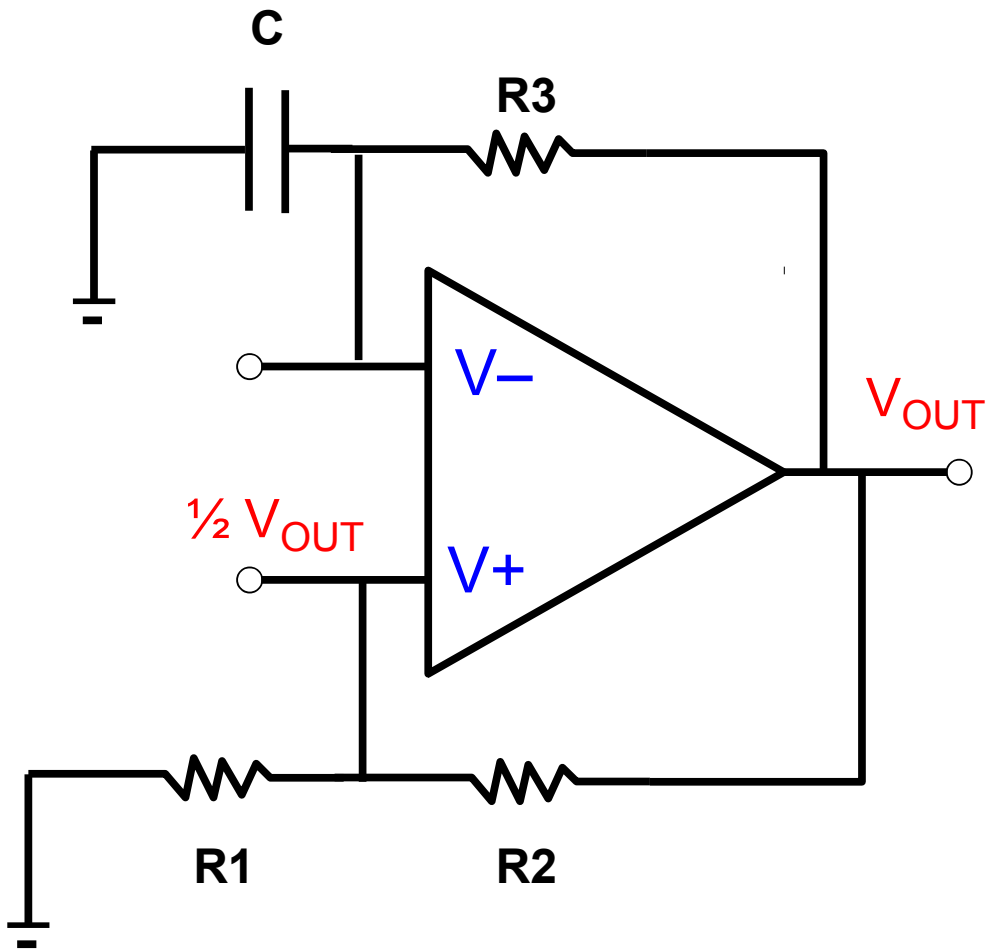
Relaxation oscillator: Implementation with Op-Amp




Add RC feedback to inverting input

V_- can't follow V_{OUT} instantly

Capacitor charges with $\tau = R_3C$

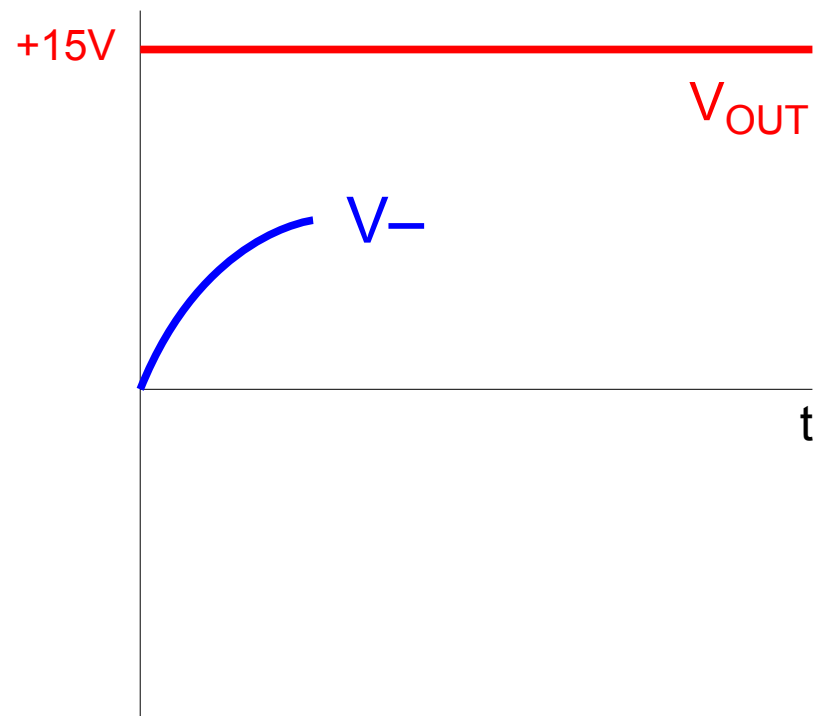

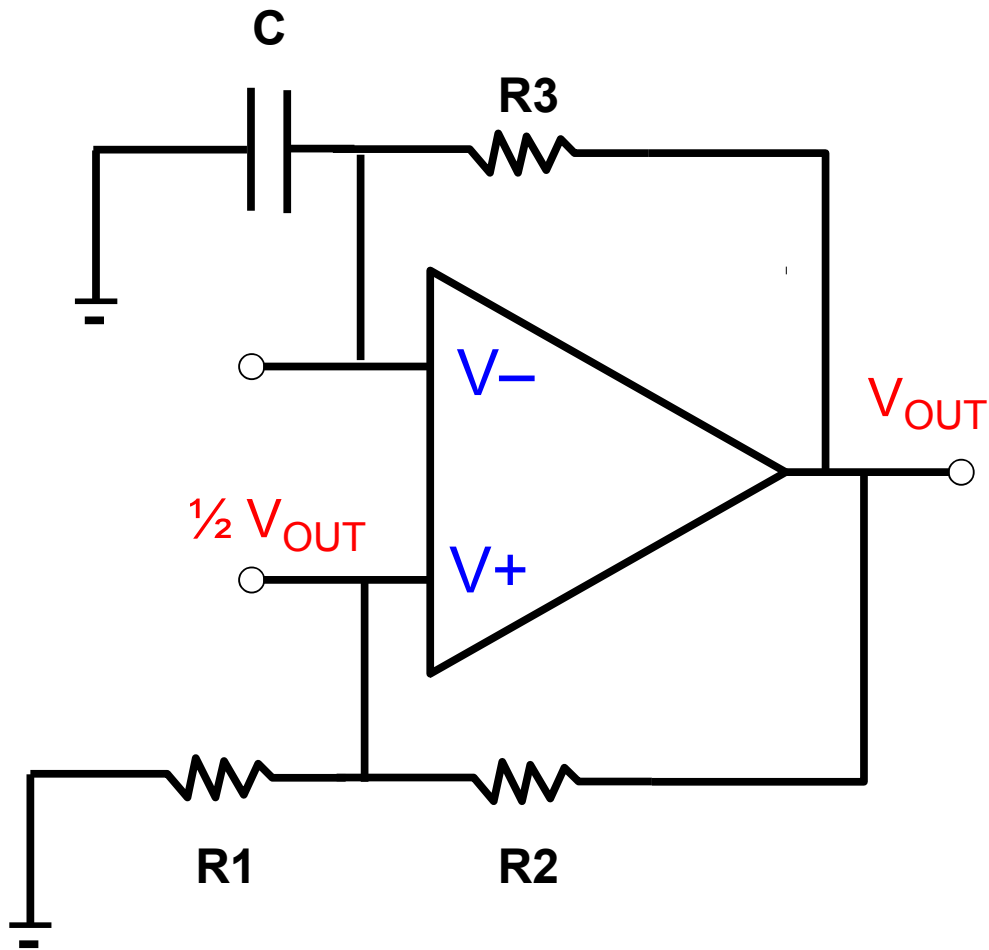
Relaxation oscillator: Implementation with Op-Amp




Add RC feedback to inverting input

V_- can't follow V_{OUT} instantly

Capacitor charges with $\tau = R_3C$

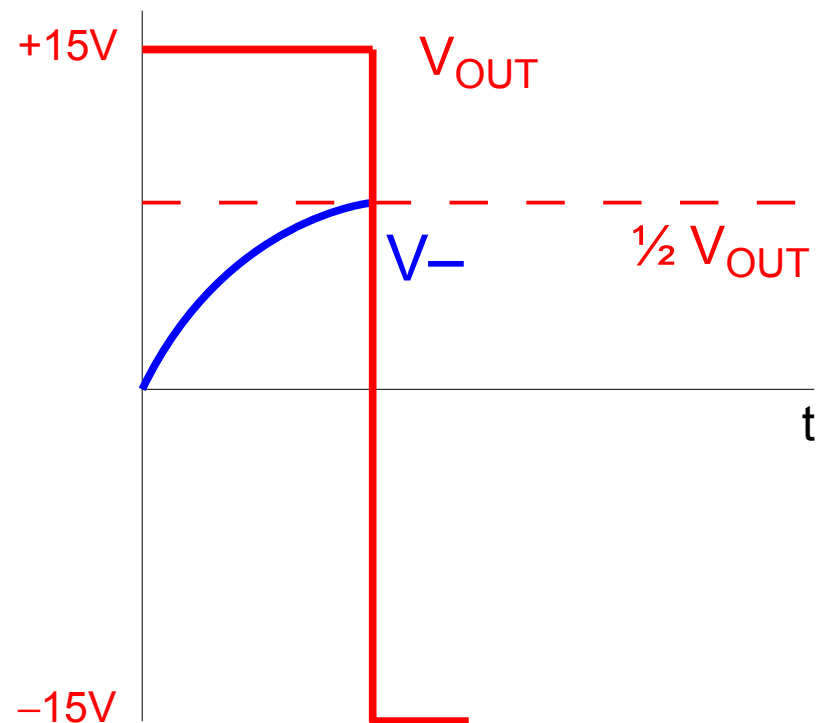

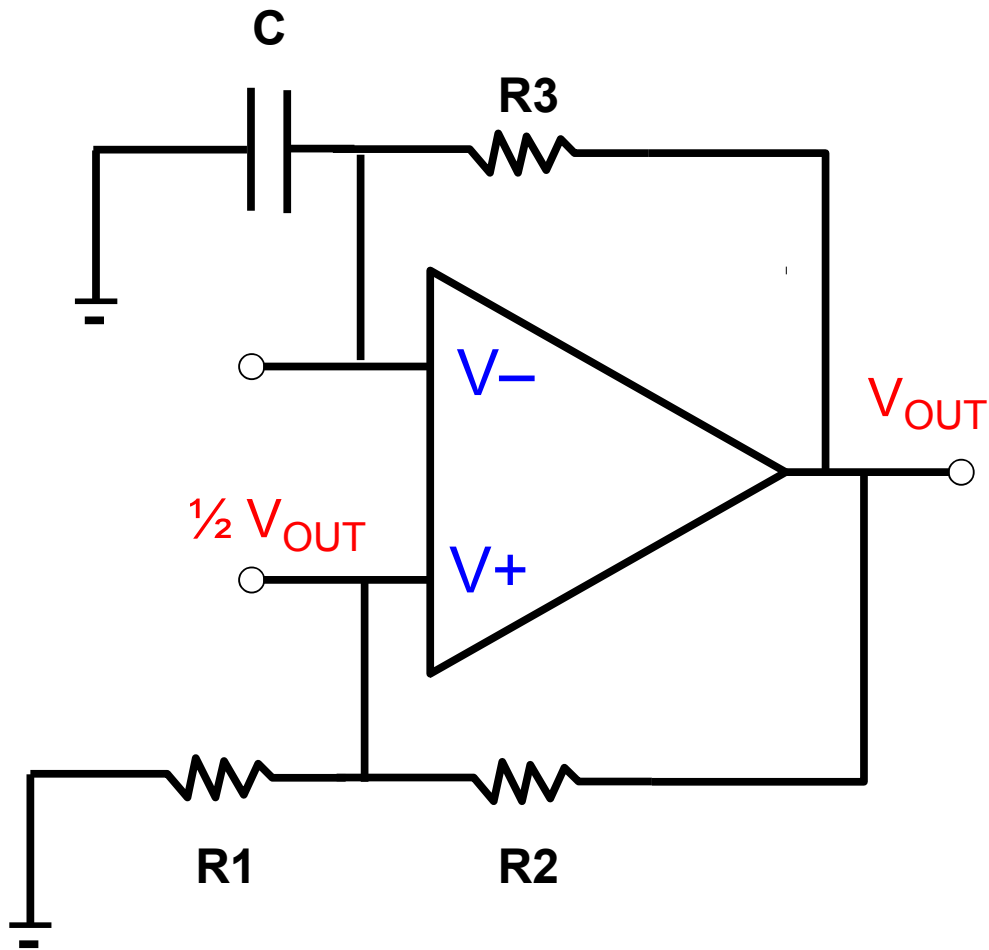
Relaxation oscillator: Implementation with Op-Amp




Add RC feedback to inverting input

V_- can't follow V_{OUT} instantly


Capacitor charges with $\tau = R_3C$

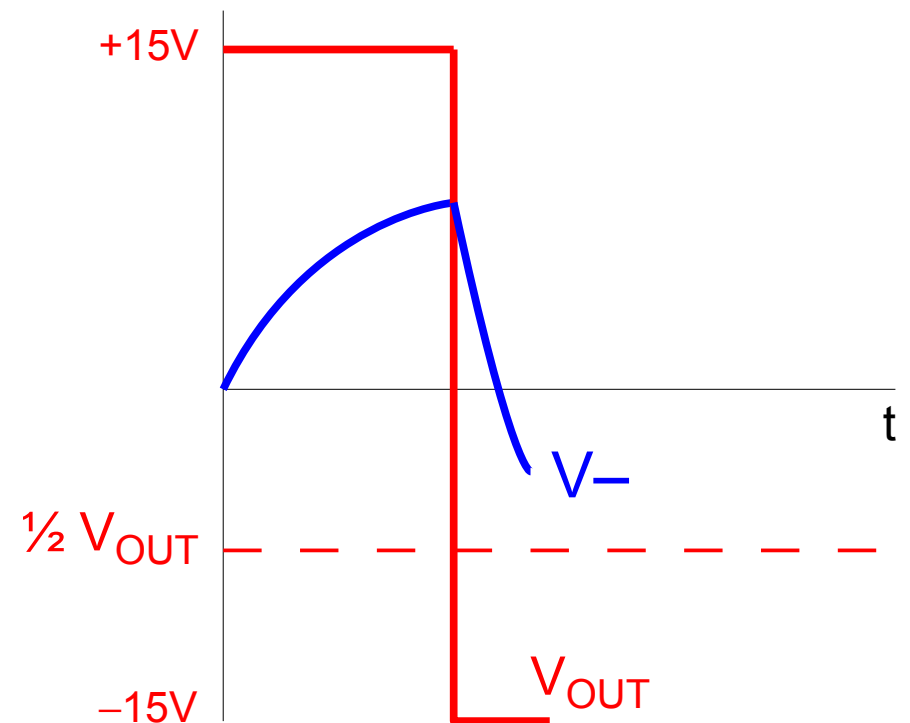

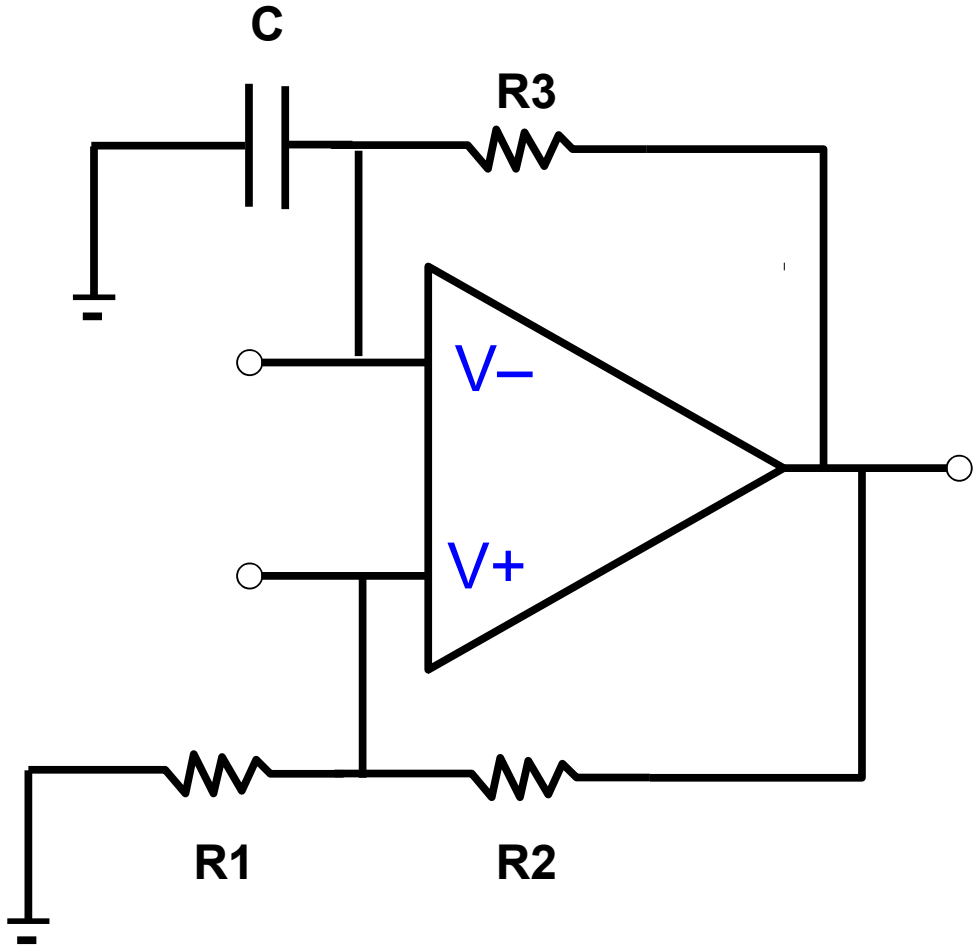Relaxation oscillator: Implementation with Op-Amp



If $R1 = R2$

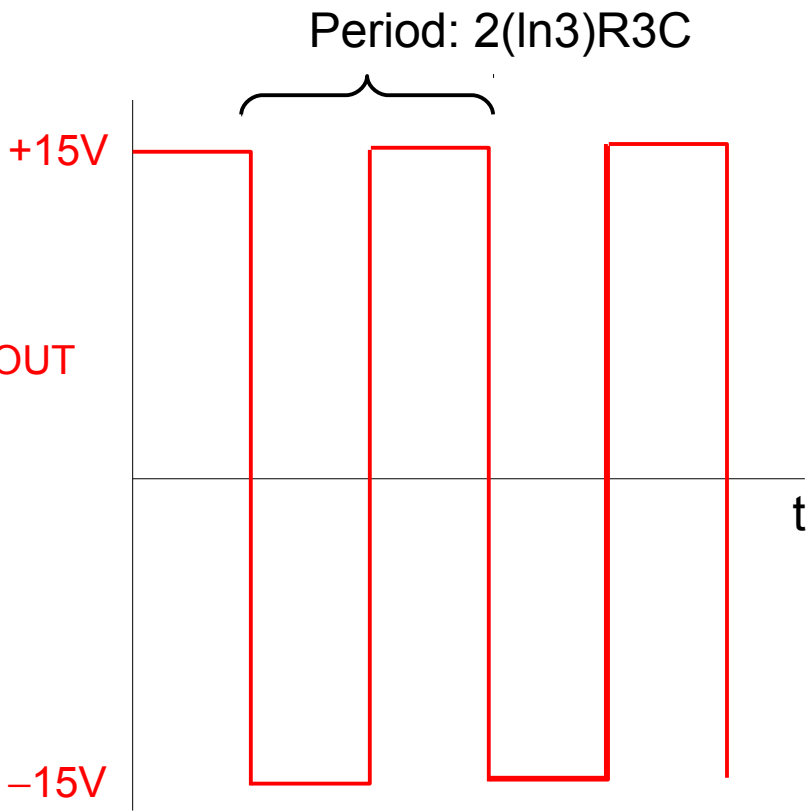


Slewing: Op-Amp cannot switch instantly

Limits the maximum oscillator frequency

Ideal




Slewing visible

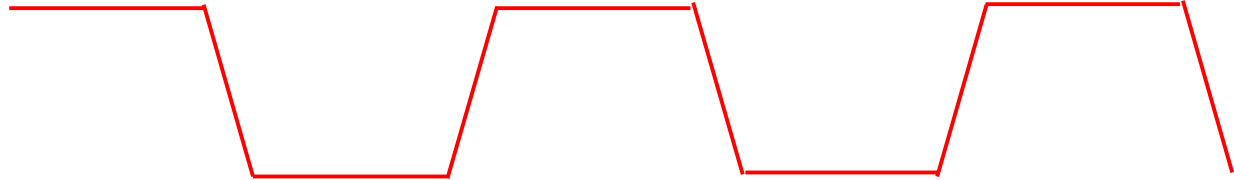

Slewing severe



555 Timer Chip

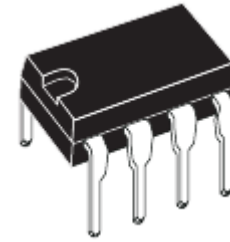


Make rectangular wave relaxation oscillator

Period adjustable with R and C


Set from microseconds to hours

Adjustable duty cycle: T_{ON} / Period


50% duty cycle

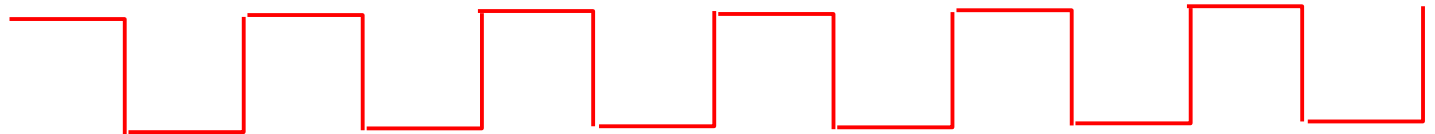

33% duty cycle

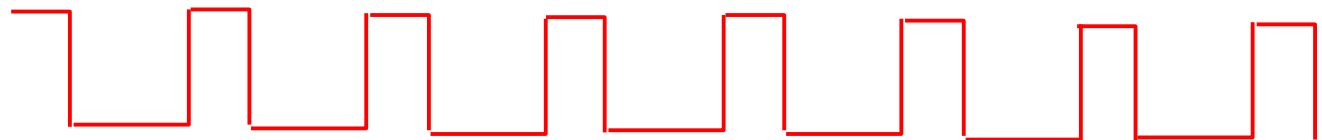

12.5% duty cycle

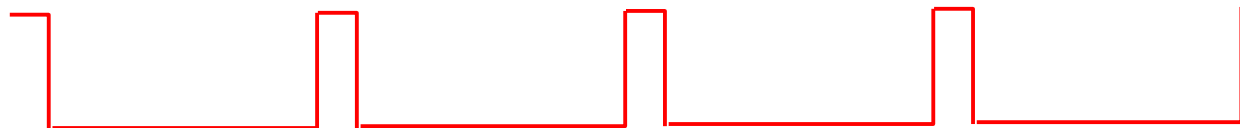

VI Server Architecture

- Programmatically control Front Panel objects
[These objects are in the Control Class]
- Programmatically edit properties of a running VI
[These objects are in the VI Class]

Objects have **PROPERTIES** and **METHODS**

PROPERTIES are attributes of an object (eg. color, size, visibility, etc)

METHODS are actions or operations of an object (eg. initializing a control)

PROPERTIES are changed programmatically with **PROPERTY NODES**

METHODS are changed programmatically with **INVOKE NODES**