

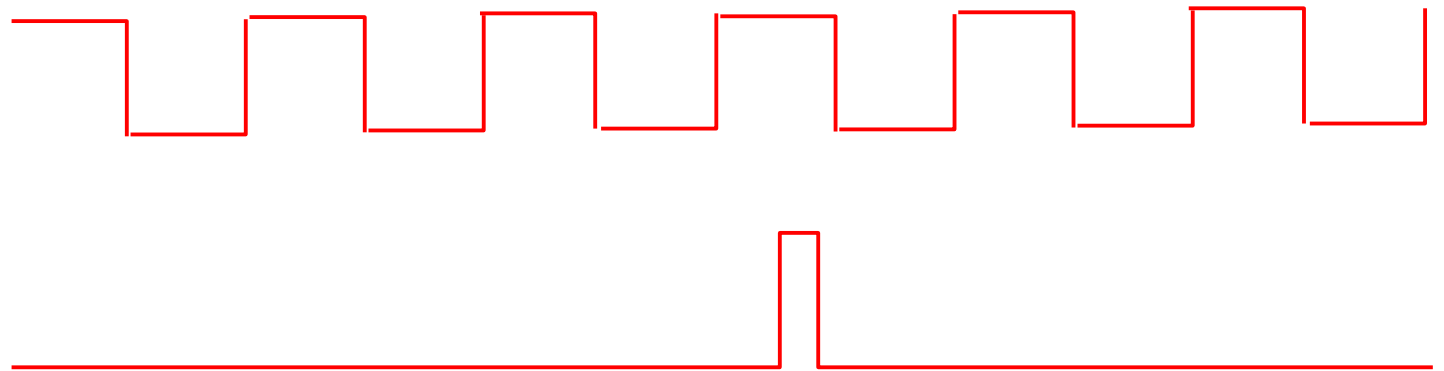


Lab 12: Timing and Control


Digital Timing: True or False; 1 or 0

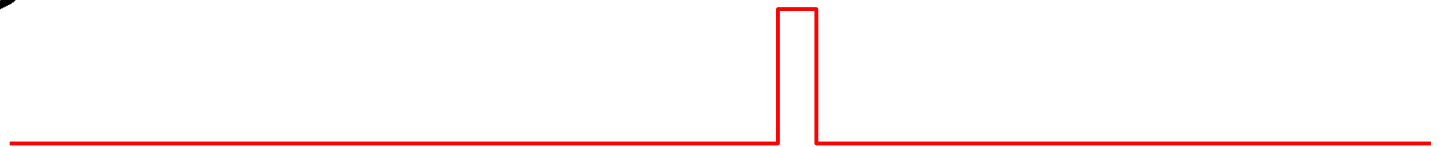


AND Gate

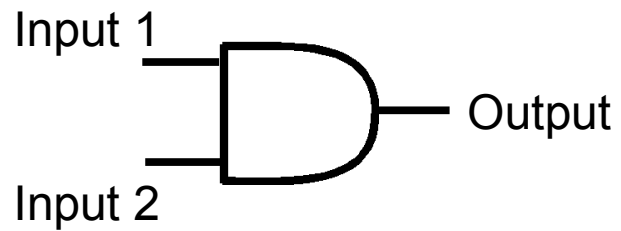


Digital Timing: True or False; 1 or 0

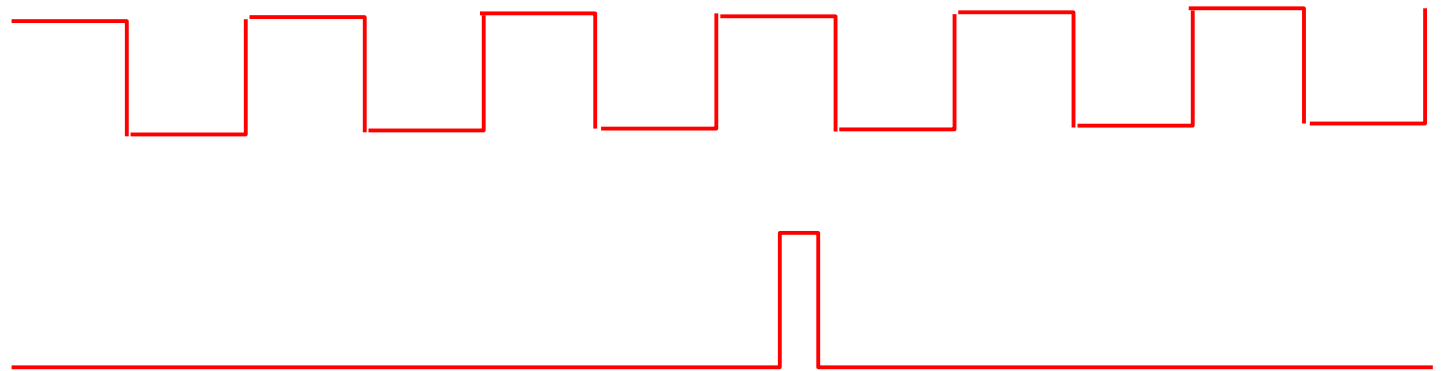



OR Gate

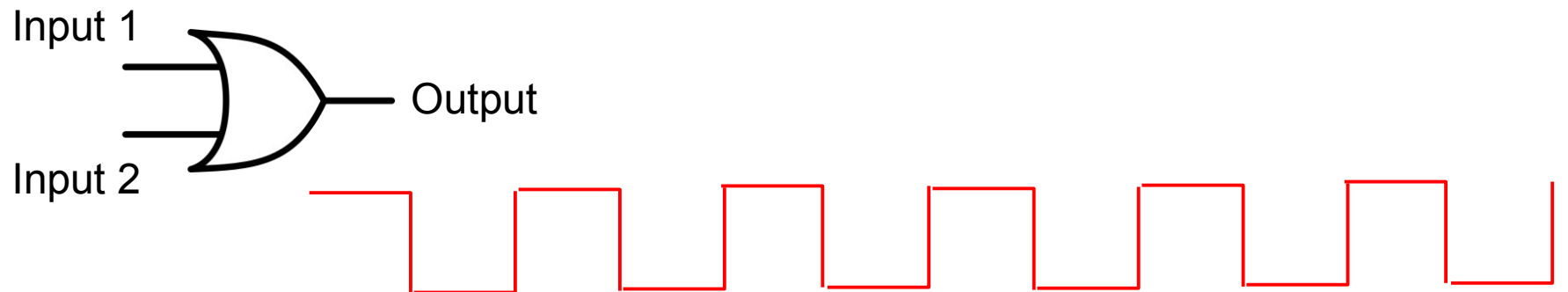


Digital Timing: True or False; 1 or 0

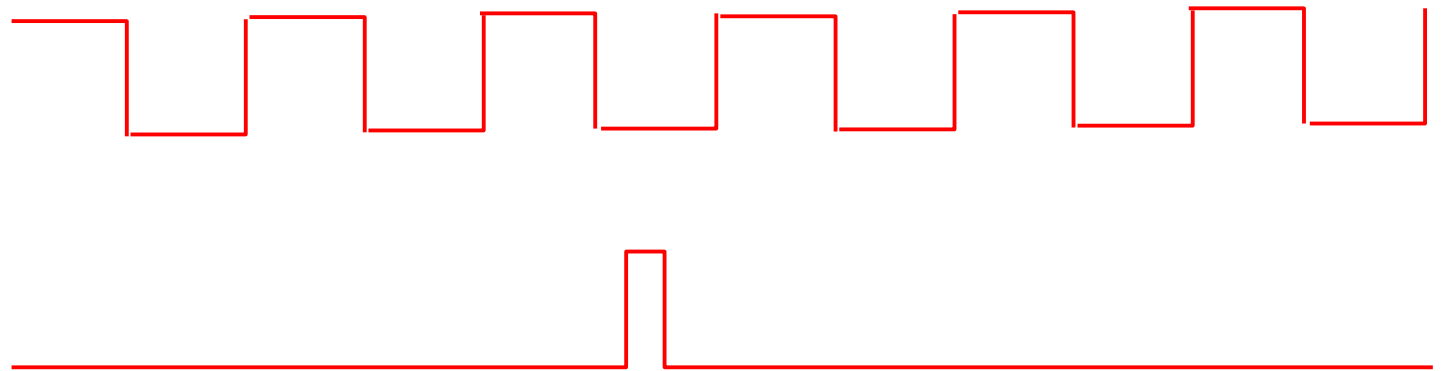


OR Gate

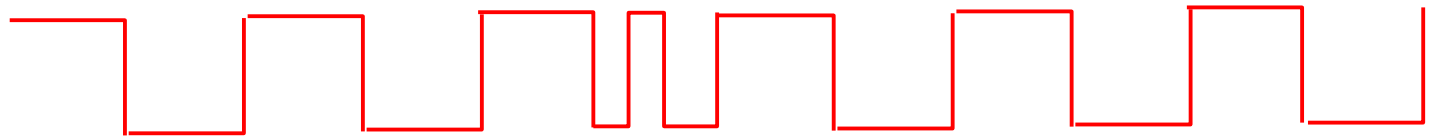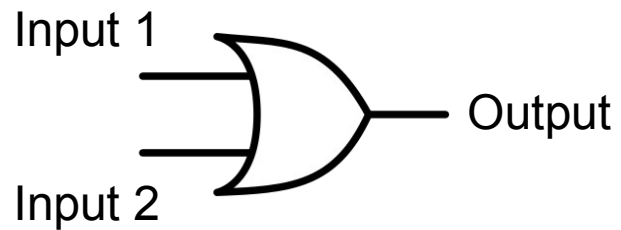



Digital Timing: True or False; 1 or 0

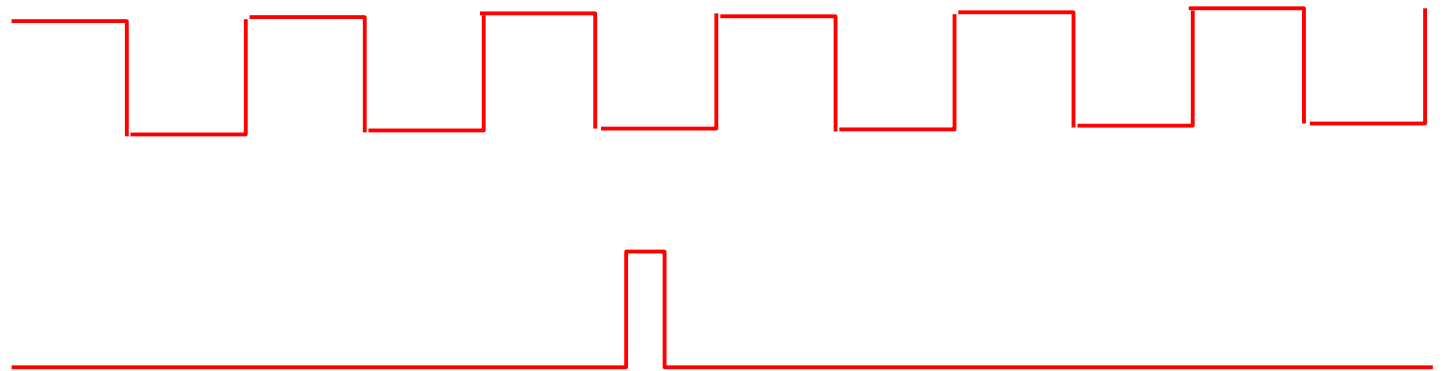


AND Gate

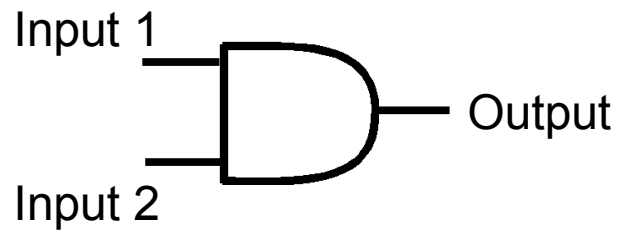

Relaxation Oscillator

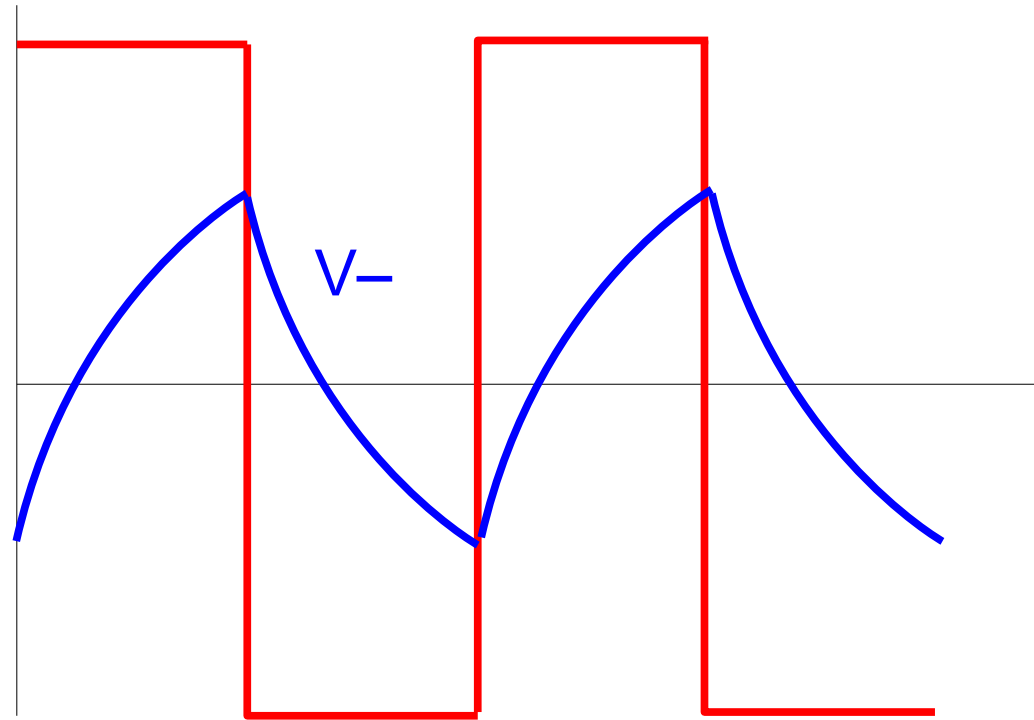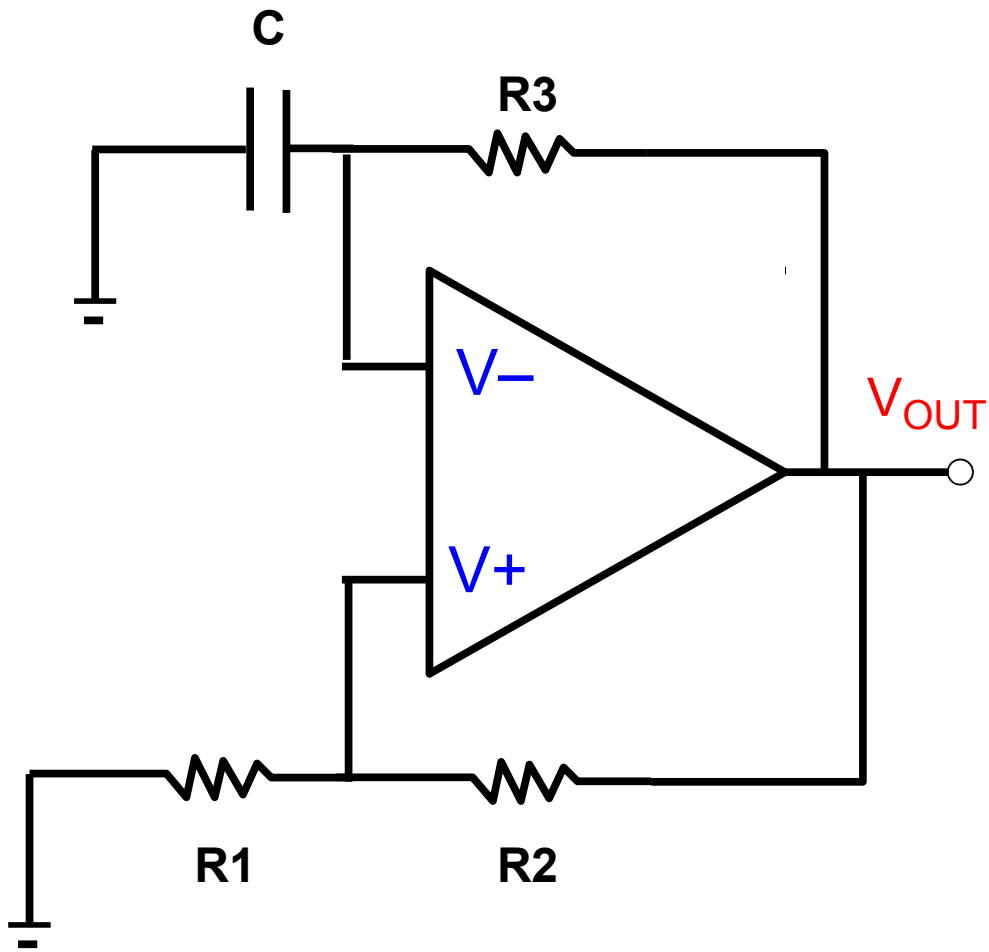

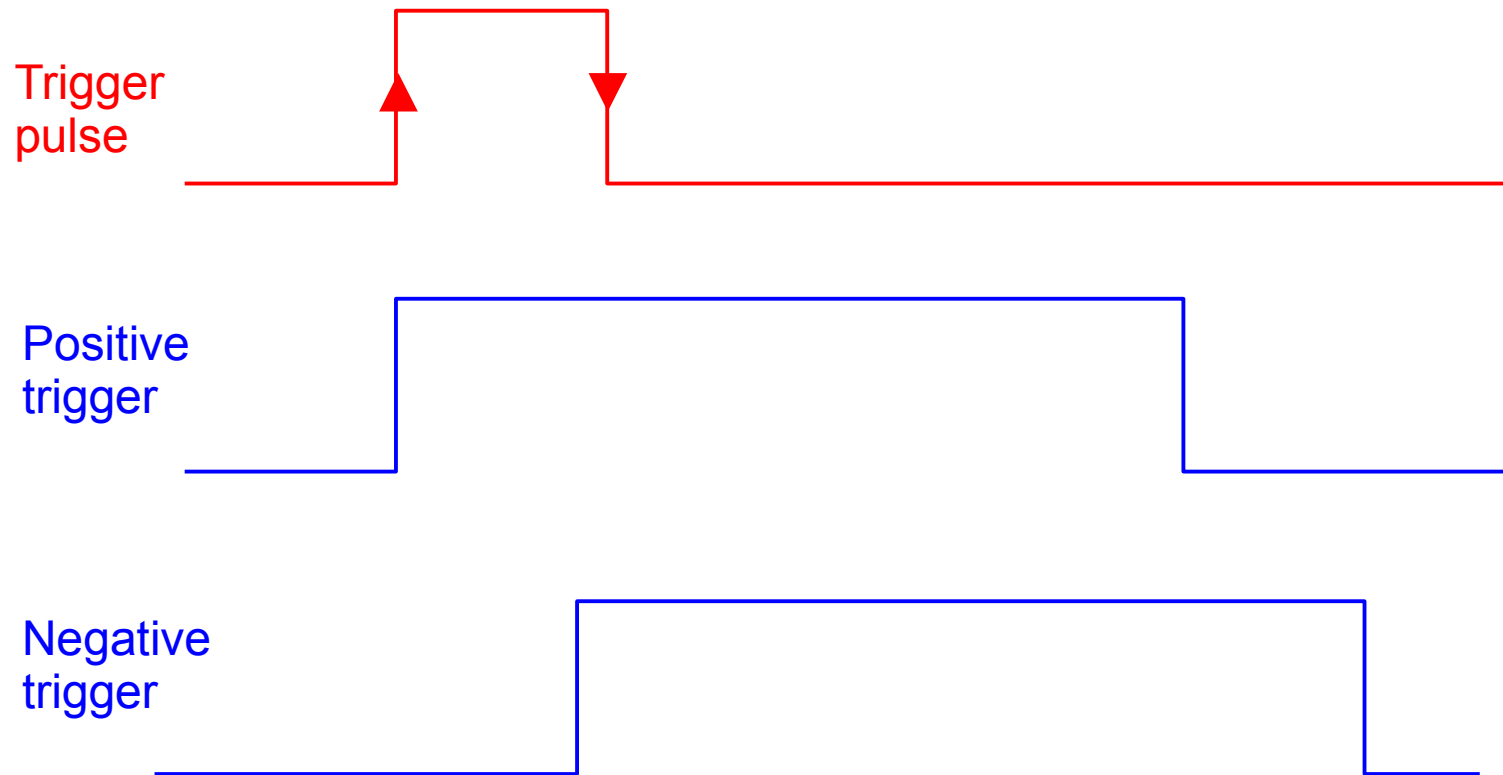Edge triggering of single-shot square pulse



Timing diagram: Traffic Light



Clock pulse



Green



Timing diagram: Traffic Light



Clock
pulse




Green

Yellow

Timing diagram: Traffic Light



Clock pulse

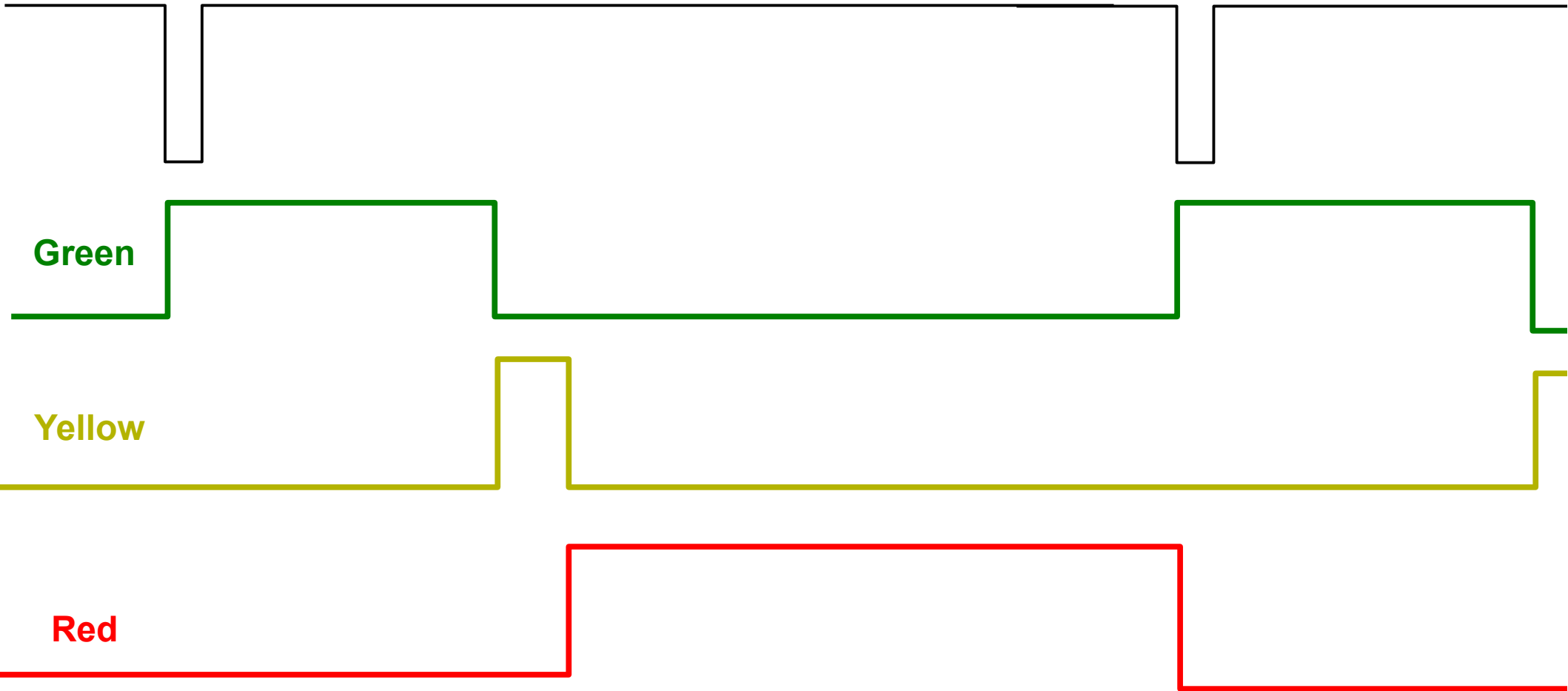

Green

Yellow

Red

Timing: Traffic Light (State 1)



North-South bound



East-West bound

Timing: Traffic Light (State 2)



North-South bound



East-West bound

Timing: Traffic Light (State 3)



North-South bound



East-West bound

Timing: Traffic Light (State 4)



North-South bound



East-West bound

Timing: Traffic Light (State 5)



North-South bound



East-West bound

Timing: Traffic Light (State 6)





North-South bound



East-West bound

Differentiating pulses with RC circuit

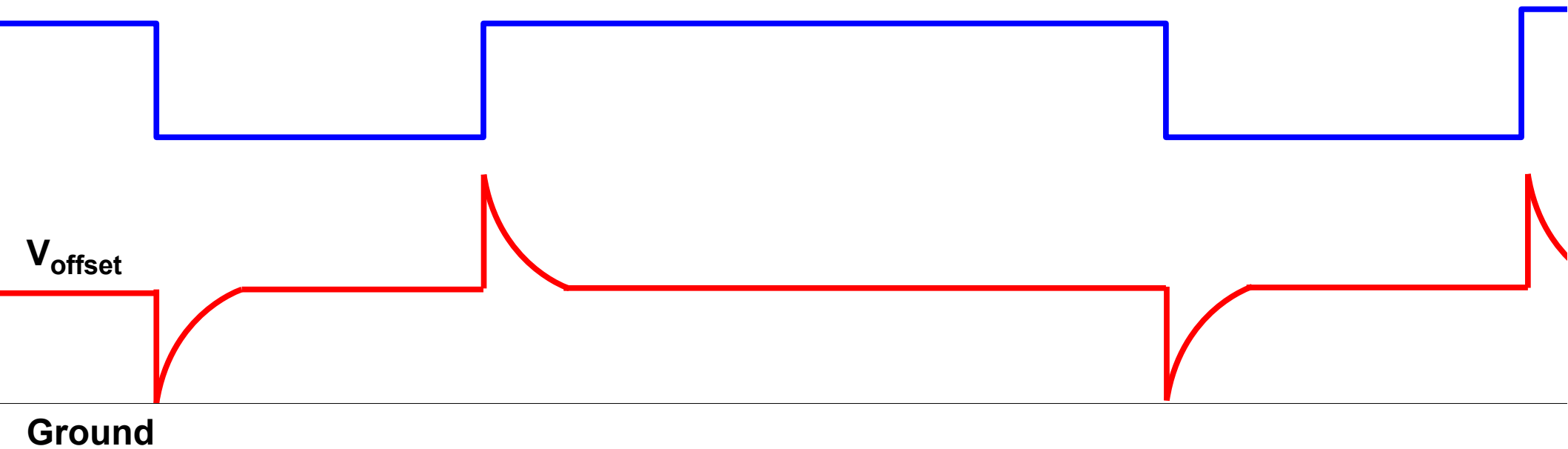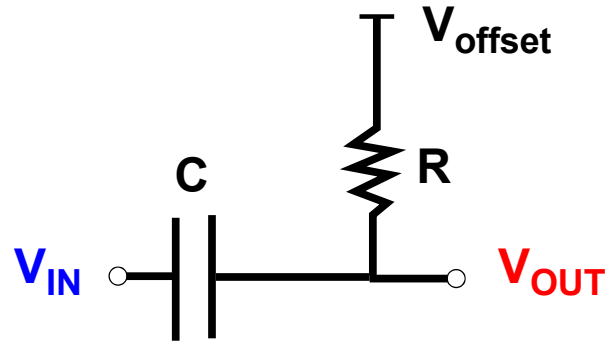

100% Hardware

Cheaper

No PC

No proprietary software/OS

More reliable

No PC to crash

More compact

Depends on complexity

Inherently faster

Interface I/O limits speed

Less power

LabView + Hardware

Easier to setup/troubleshoot

Easier to expand/adapt new versions

LabView code more transparent
than circuit schematic

Probably better approach
for research lab environment

EMBEDDED SYSTEMS

Dedicated computer hardware replaces the general purpose PC

Inexpensive, low-power micro-controllers (RAM, Flash, I/O, etc)

Optimized to solve a specific problem or task

Examples

- Digital watch
- Game console
- Cellphone
- MP3 player
- PDA
- GPS
- Smoke detector
- Digital camera
- Microwave oven

Two-direction traffic light implemented with state-machine on a \$1 TI micro-controller. Battery powered.

```
//Runs a 6 LEDs in sequence, simulating a two-direction traffic light.
//Implemented with timer interrupts using the 12 kHz VLO clock.
//MCU spends most of its time in LPM3.
//This is a state-machine with 6 states


#include <msp430g2253.h>
#ifndef TIMER0_A1_VECTOR
#define TIMER0_A1_VECTOR  TIMERA1_VECTOR
#define TIMER0_A0_VECTOR  TIMERA0_VECTOR
#endif

int main(void) {
    WDTCTL = WDTPW | WDTHOLD;          // Stop watchdog timer
    P1DIR |= BIT0 + BIT4 + BIT6; // Direction 1: Red, yellow, green on P1.0, 1.4, & 1.6
    P1DIR |= BIT1 + BIT2 + BIT3; // Direction 2: Red, yellow, green on P1.1, 1.2, & 1.3
    P1OUT |= BIT0 + BIT1 + BIT2 + BIT3 + BIT4 + BIT6; //Turn all LEDs on
    BCSCTL3 |= LFXT1S_2; //Set low frequency clock to the 12 kHz VLO
    //Divide the VLO (ACLK) as follows: DIVA_0,1,2,3 correspond to divide by 1,2,4,8
    //For DCO = 150 kHz, set RSELx = 1 and DCOx = 3
    BCSCTL1 = DIVA_2;
    TACCR0=6000; //12000 counts for 1 second at DIVA_0;
    //Maximum count is 65535 (unsigned 16-bit)
    TACCTL0 |= CCIE; //Enable timer interrupt
    //Configure TACTL last because it starts the timer
    TACTL |= TASSEL_1 + MC_1; //Set Timer A to ACLK; MC_1 to count up to TACCR0.
    _BIS_SR(GIE); //Enable global interrupts. Shouldn't be set until module is fully configured
    LPM3;
    P1OUT &= ~(BIT0 + BIT1 + BIT2 + BIT3 + BIT4 + BIT6); //Turn off all LEDs
```

```
for (;;) { // Endless loop
    //State 1
    P1OUT &= ~BIT2; //Yellow 2 off
    P1OUT |= BIT0 + BIT1; //Both red LEDs on
    TACCR0=12000; //2 second wait
    LPM3;
    //State 2
    P1OUT &= ~BIT0; //Red 1 off
    P1OUT |= BIT6; //Green 1 on
    TACCR0=30000; //5 second wait
    LPM3;
    //State 3
    P1OUT &= ~BIT6; //Green 1 off
    P1OUT |= BIT4; //Yellow 1 on
    TACCR0=12000; //2 second wait
    LPM3;
    //State 4
    P1OUT &= ~BIT4; //Yellow 1 off
    P1OUT |= BIT0 + BIT1; //Both red LEDs on
    TACCR0=12000; //2 second wait
    LPM3;
    //State 5
    P1OUT &= ~BIT1; //Red 2 off
    P1OUT |= BIT3; //Green 2 on
    TACCR0=24000; //4 second wait
    LPM3;
    //State 6
    P1OUT &= ~BIT3; //Green 2 off
    P1OUT |= BIT2; //Yellow 2 on
    TACCR0=12000; //2 second wait
    LPM3;
}

#pragma vector=TIMER0_A0_VECTOR
__interrupt void timerfoo (void)
{
    LPM3_EXIT;
}
```


CONTROL: OPEN LOOP

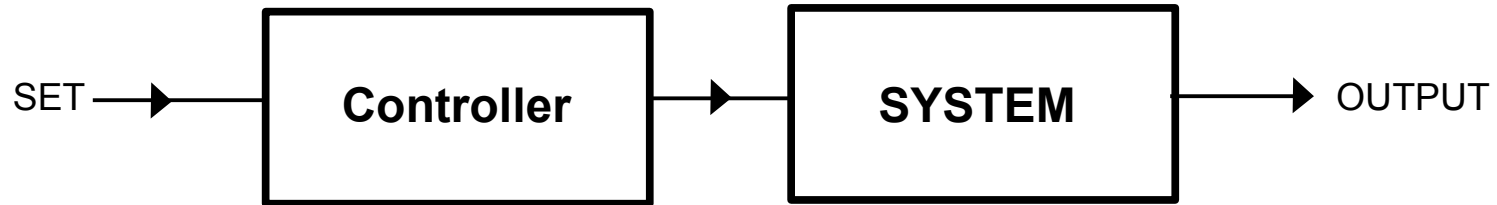


EXAMPLES:

- Washing machine
- Lawn sprinkler system


CONTROL: CLOSED LOOP

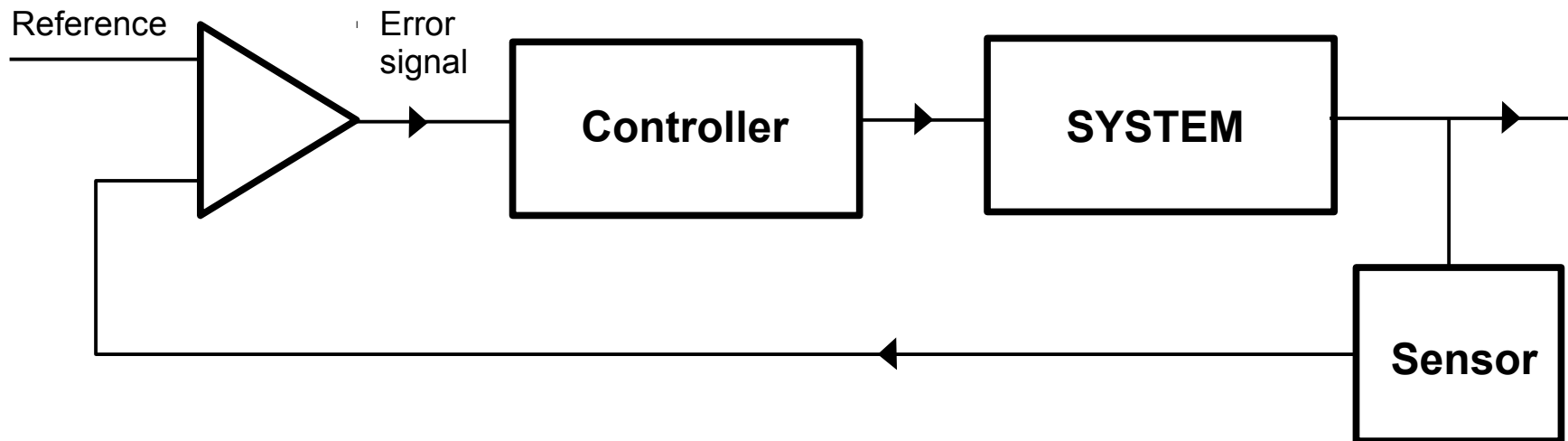


CLOSED LOOP

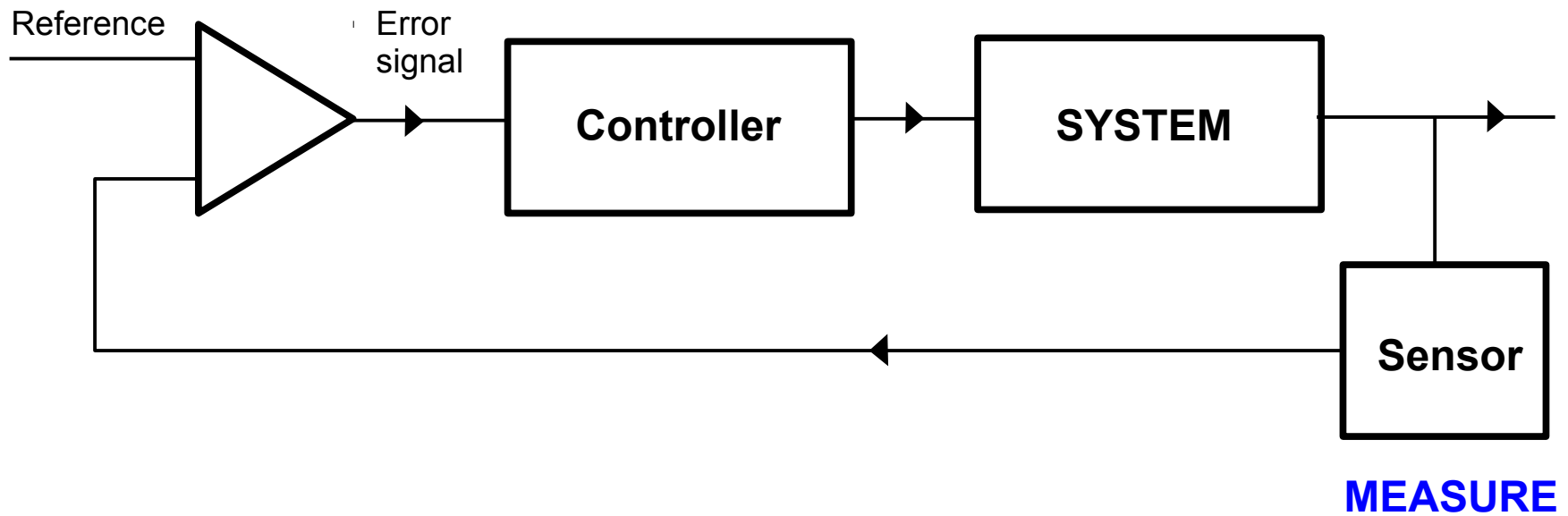

CLOSED LOOP

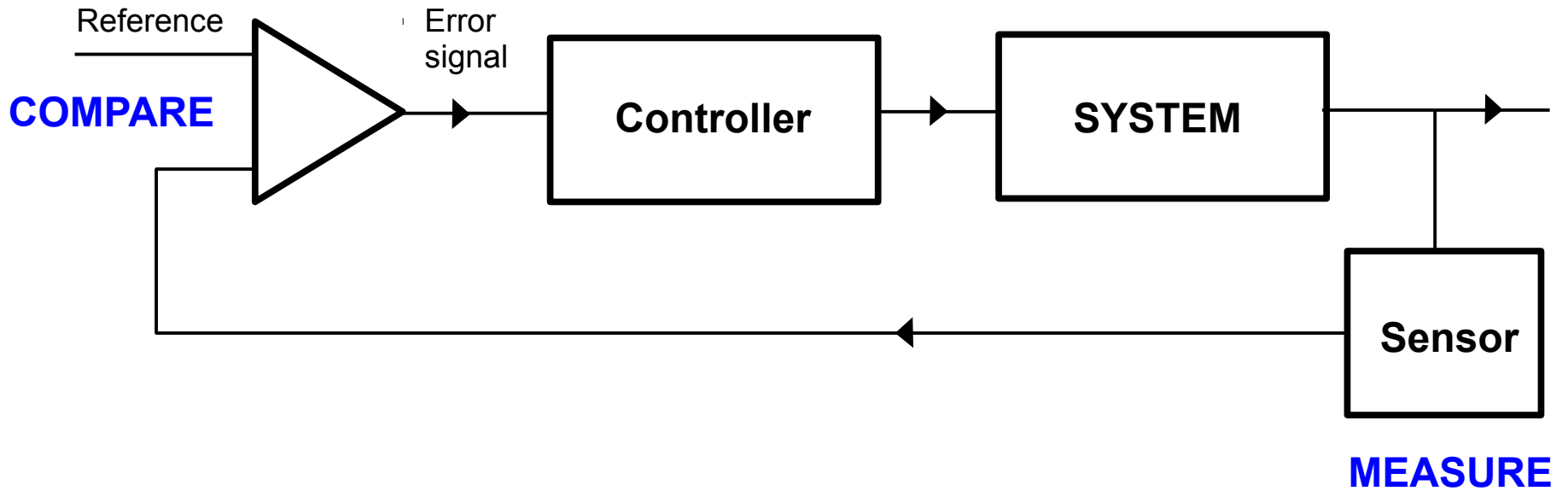

CLOSED LOOP

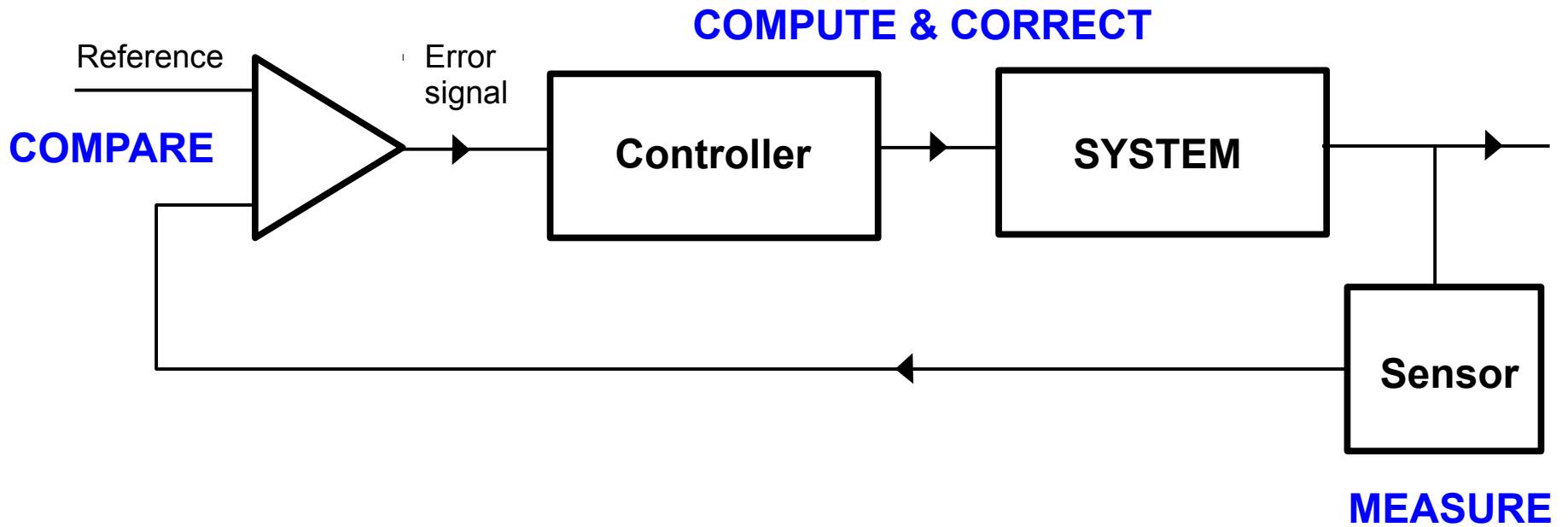

Examples of closed loop controllers

Cruise control on car

Thermostat on furnace


Water level in hot water heater or swamp cooler

Compact disk player


Cabin air pressure in passenger plane

Clock on a PC


HYSTERETIC CLOSED LOOP CONTROLLER

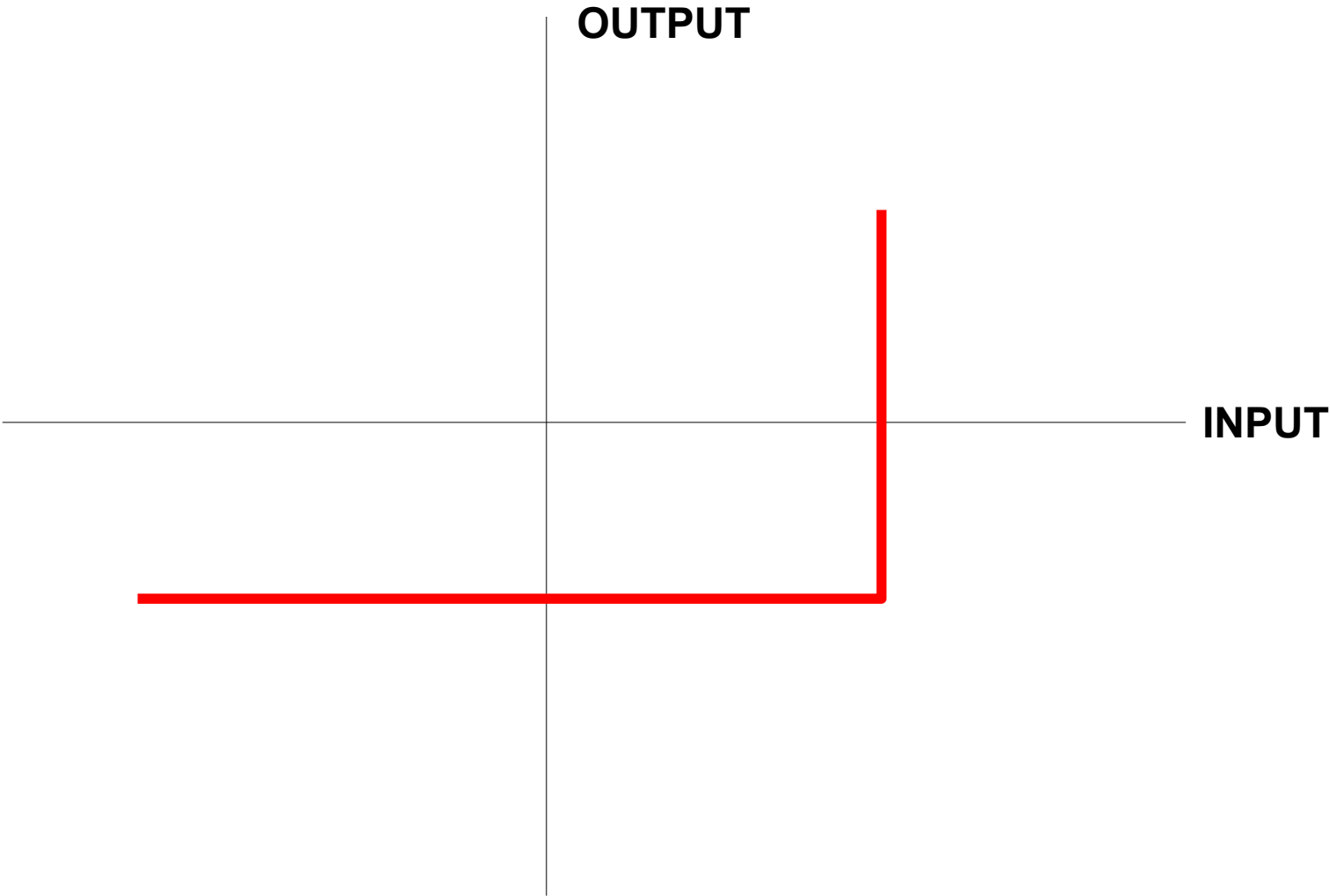


HYSTERETIC CLOSED LOOP CONTROLLER

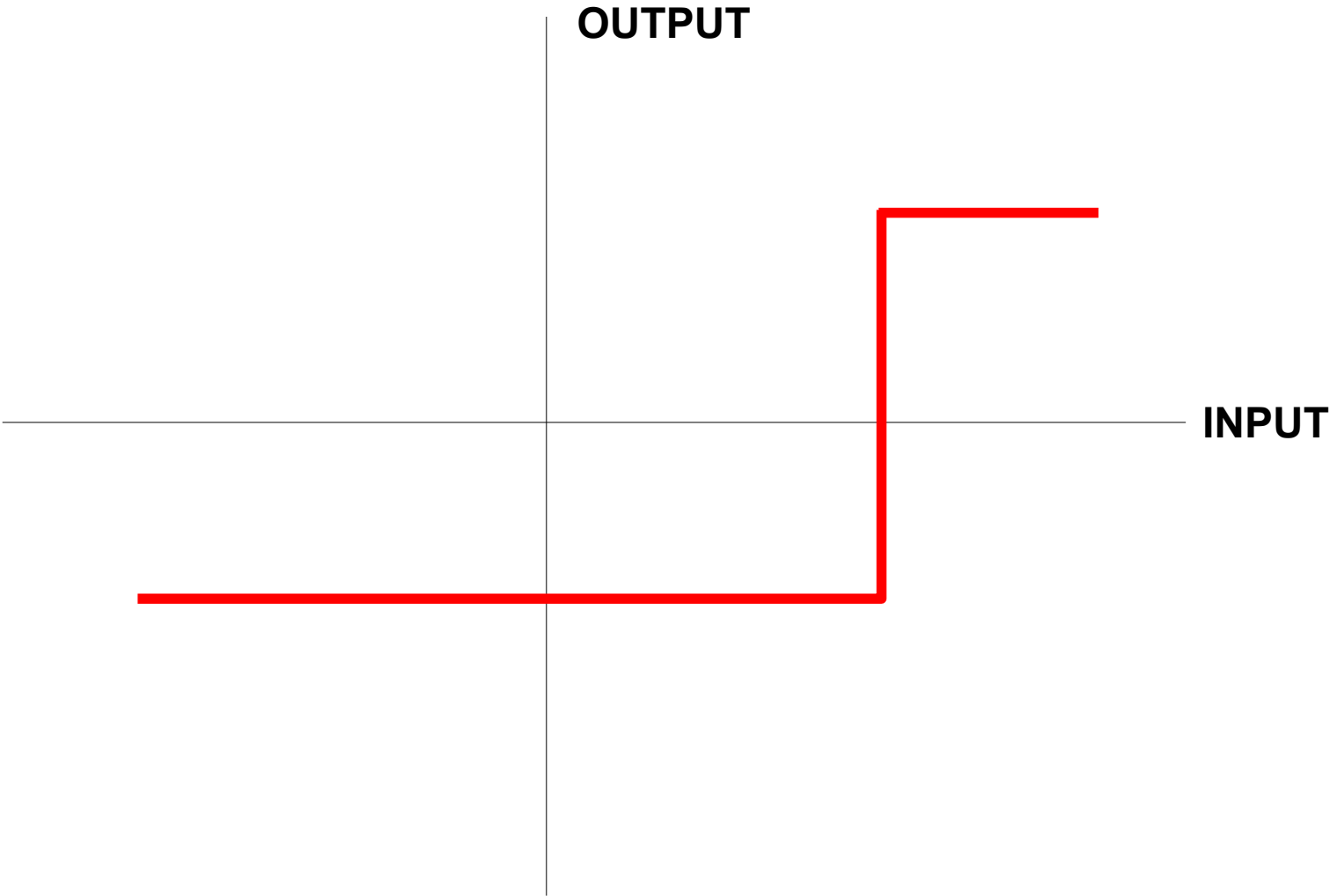


HYSTERETIC CLOSED LOOP CONTROLLER

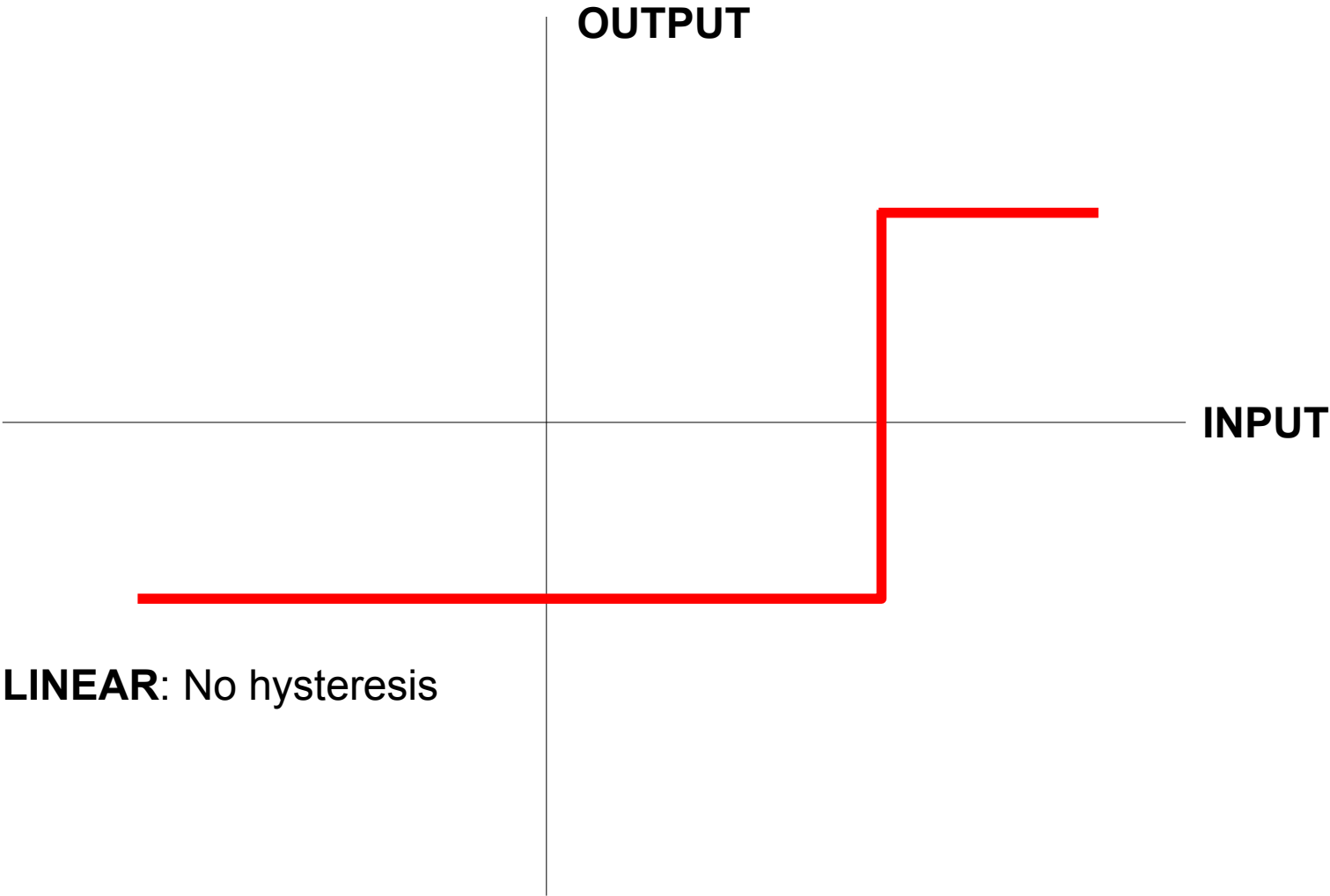

HYSTERETIC CLOSED LOOP CONTROLLER

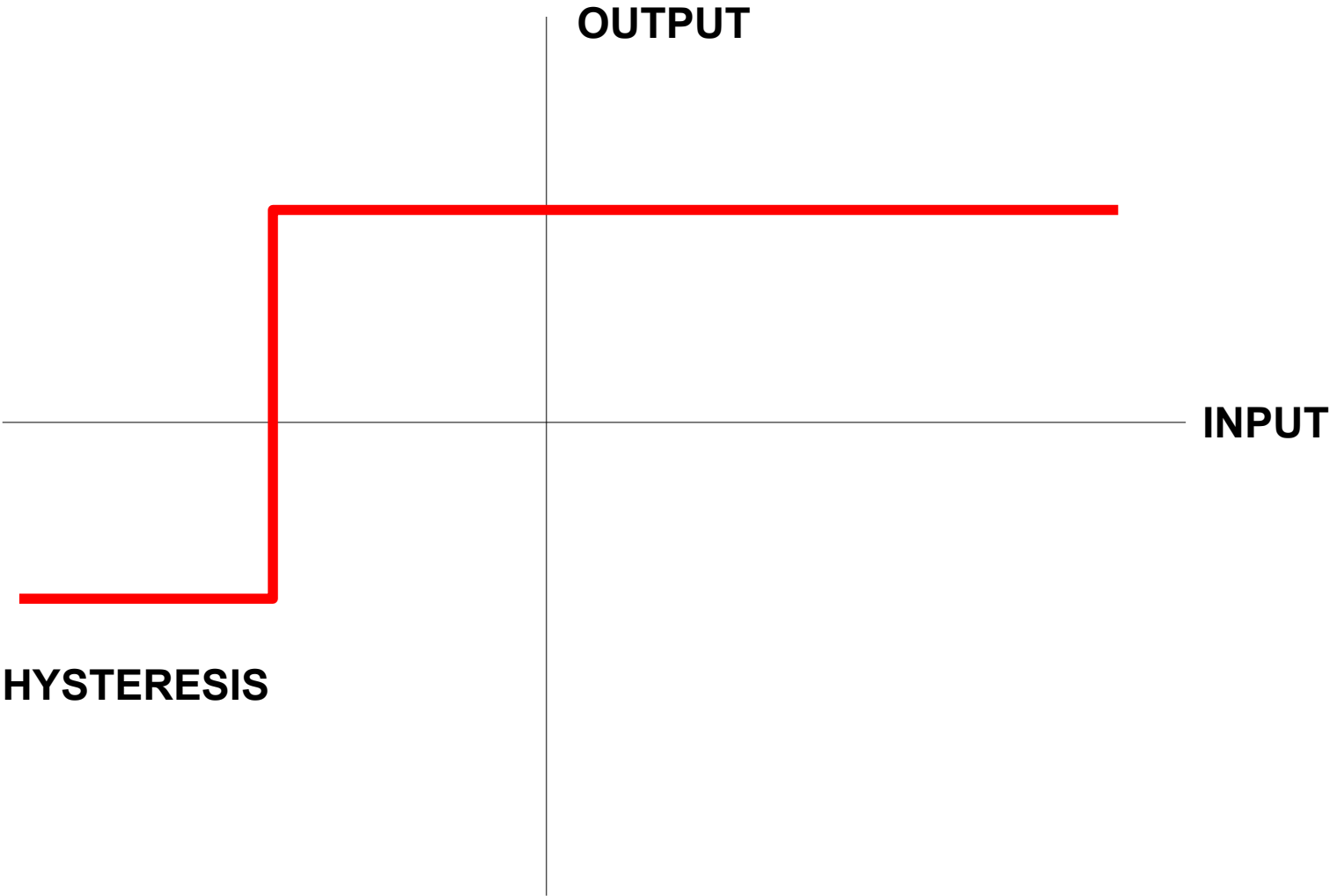


HYSTERETIC CLOSED LOOP CONTROLLER

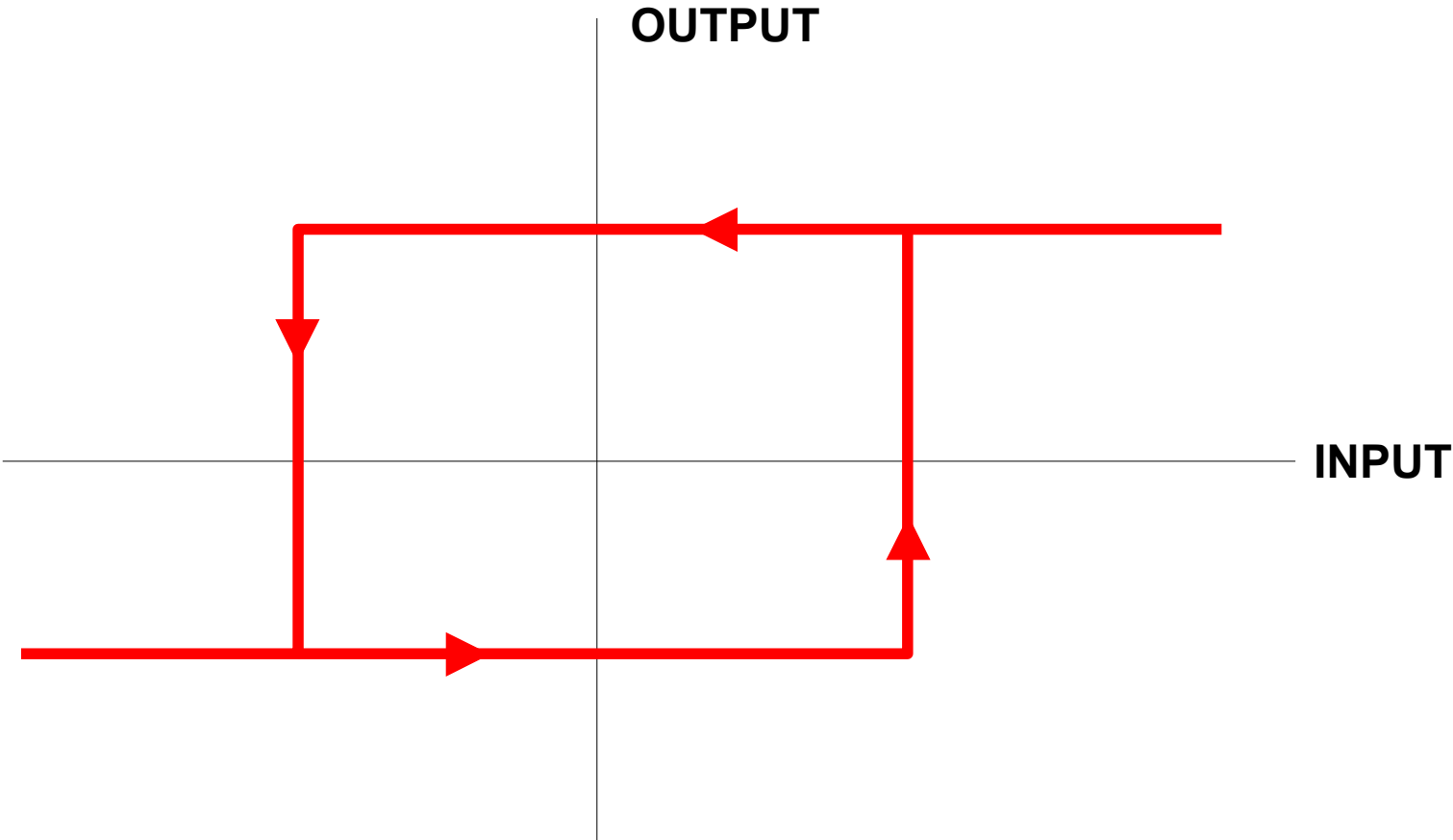


OUTPUT state depends on direction of INPUT state


HYSTERETIC CLOSED LOOP CONTROLLER

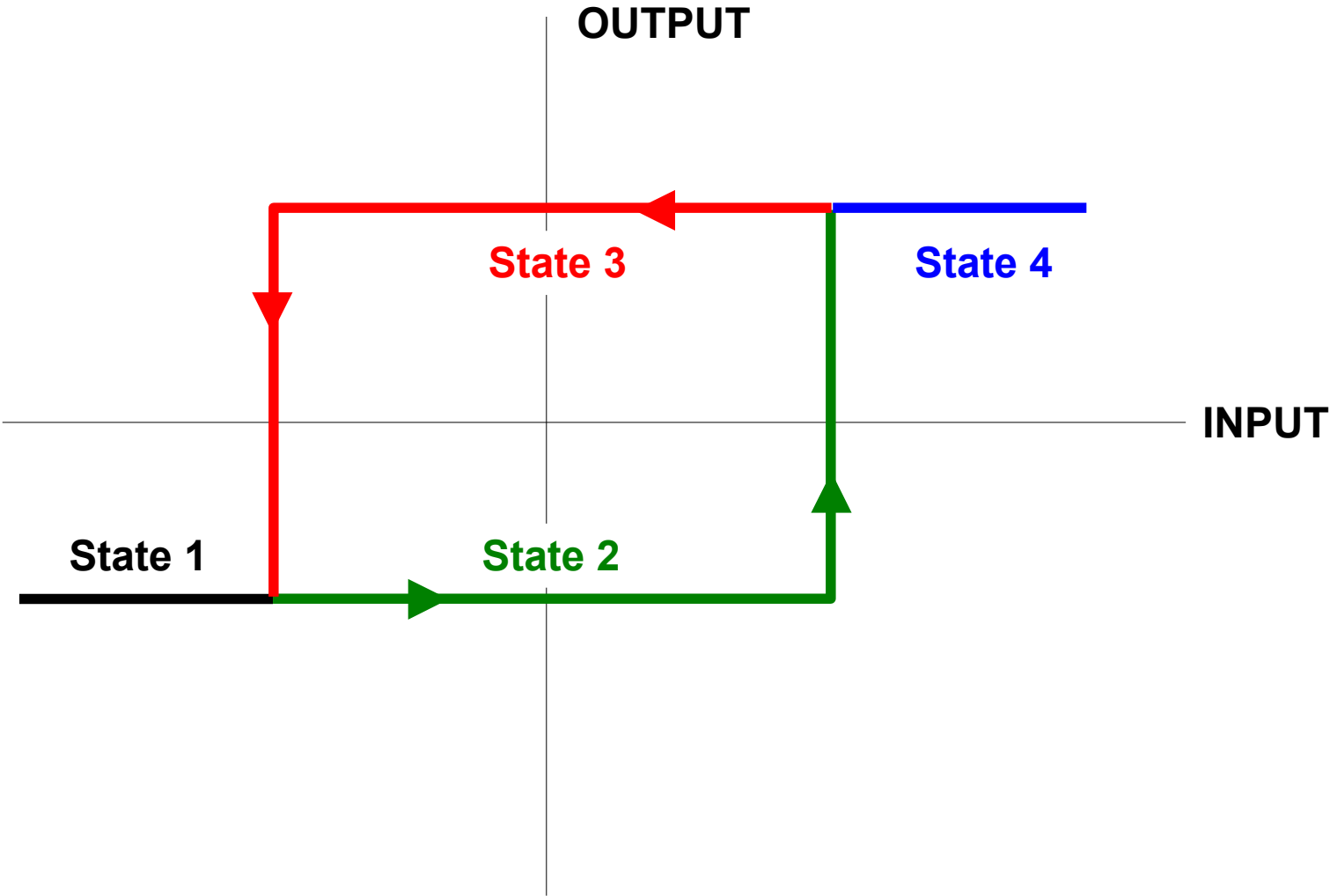

Cryostat Temperature Controller

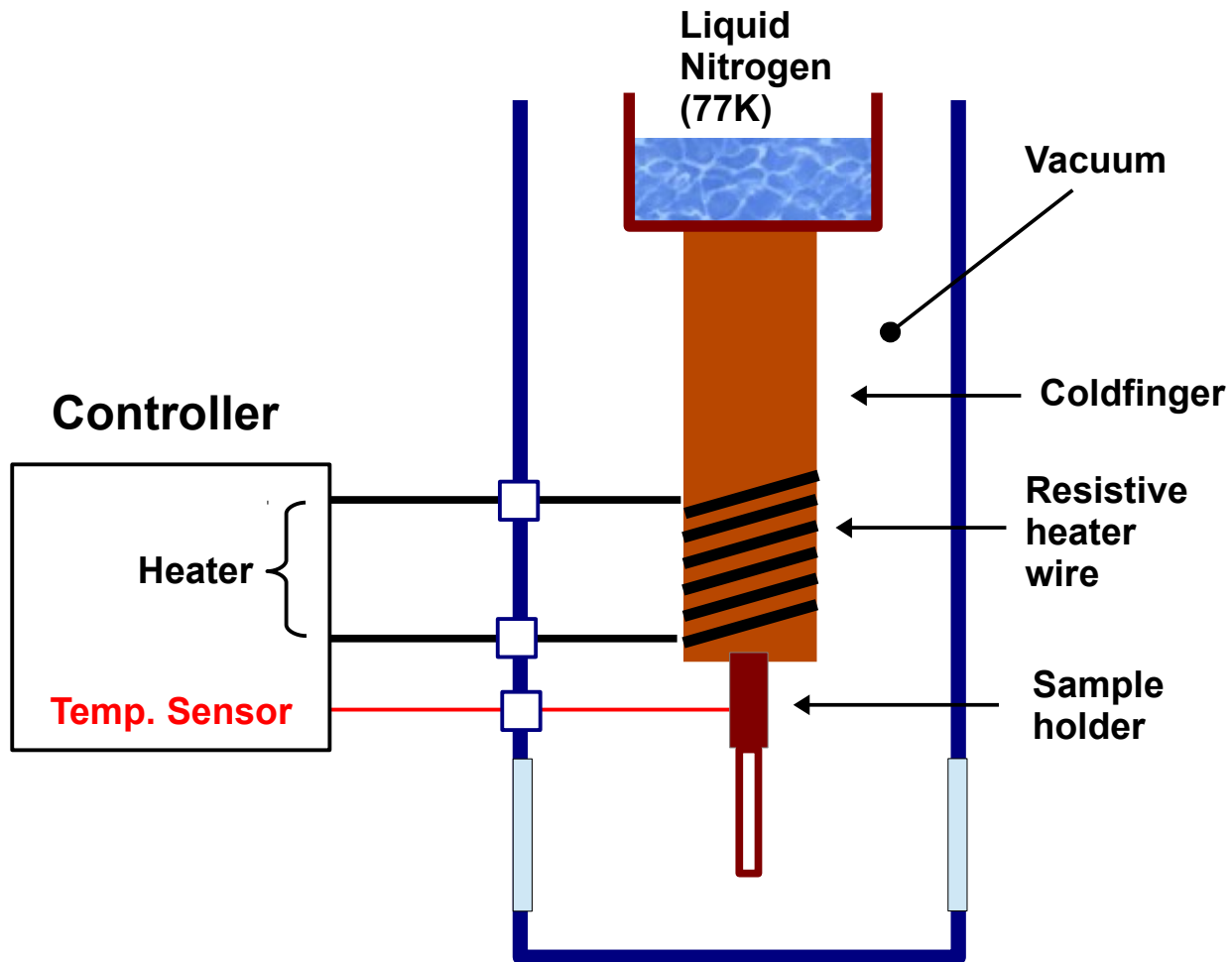

Cryostat Temperature Controller

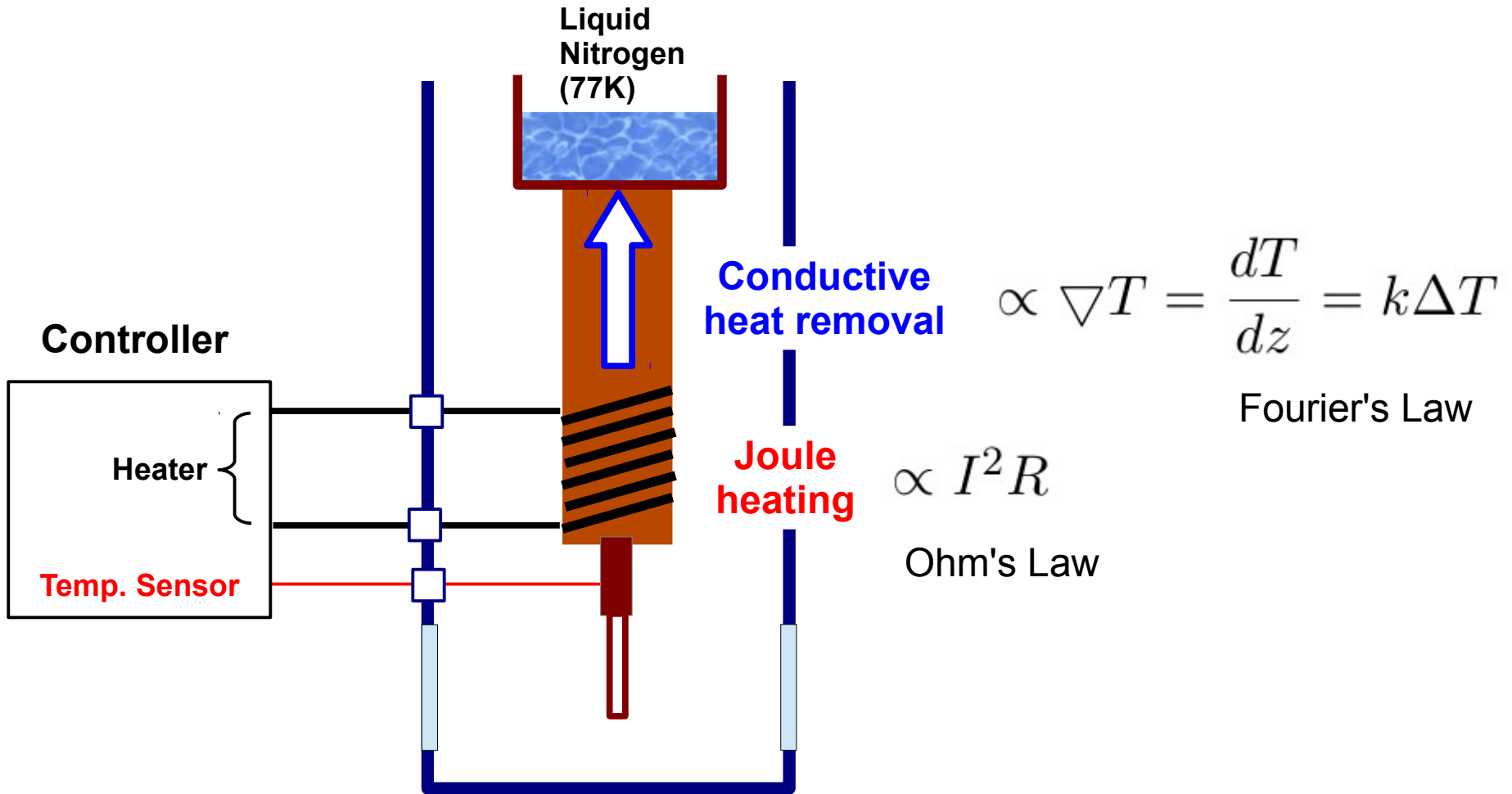


Heater current **High**


Hi Setpoint (K) **150**

Coldfinger Temperature (K) **77**

Low Setpoint (K) **145**

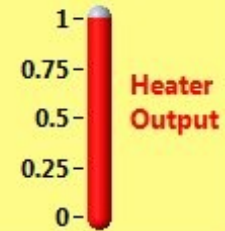

Waveform Chart

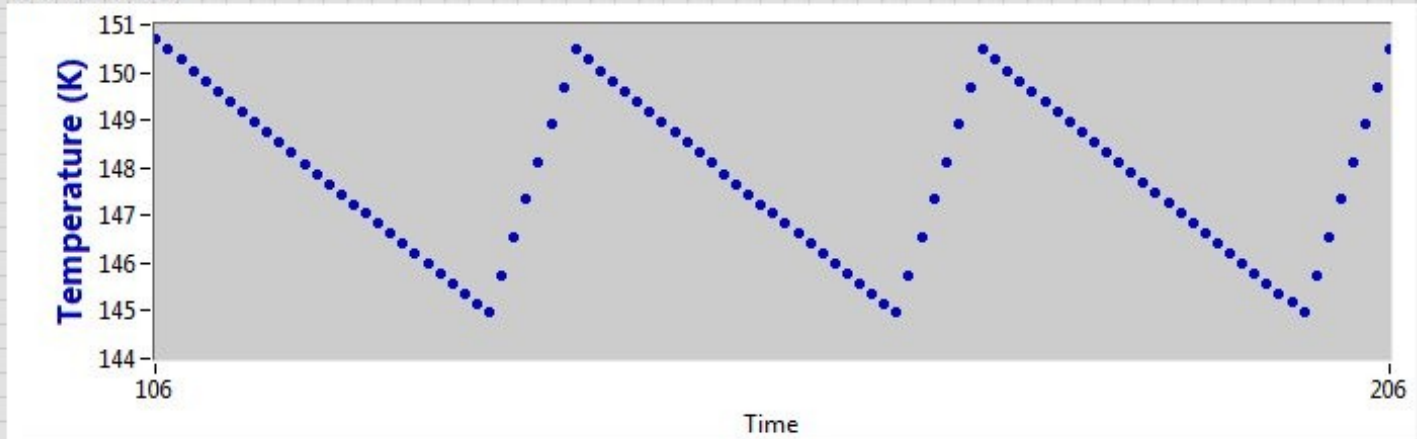

stop
STOP

dt (s) **0.5**

Sample temperature (K) **150.486**