


Lab 2: AC Circuits and Oscilloscope

Ideal meters

VOLTMETER:

$$I_{\text{meter}} \approx 0$$

EXAMPLE: 10X oscilloscope probe

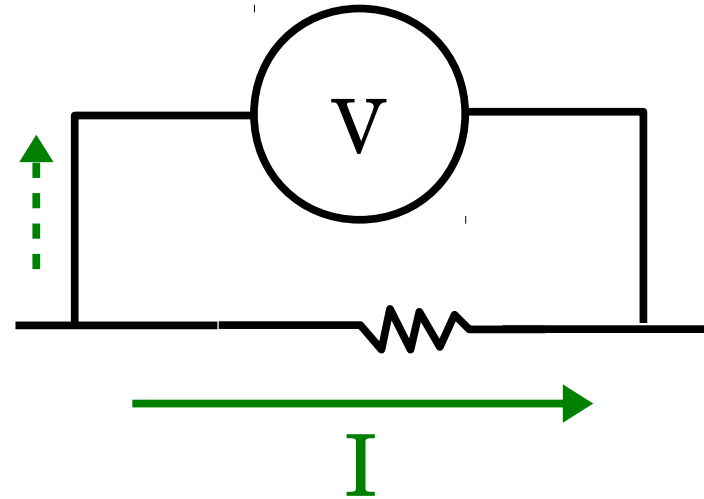


Ideal meters

VOLTMETER:


$$I_{\text{meter}} \approx 0$$

EXAMPLE: 10X oscilloscope probe

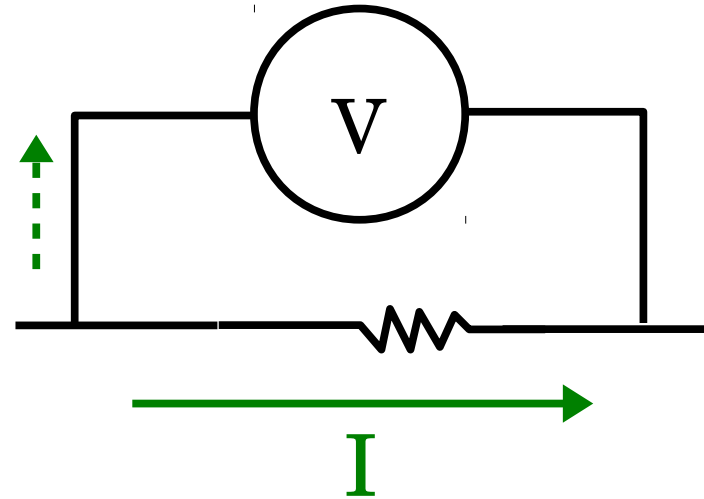


AMMETER:


$$V_{\text{meter}} \approx 0$$

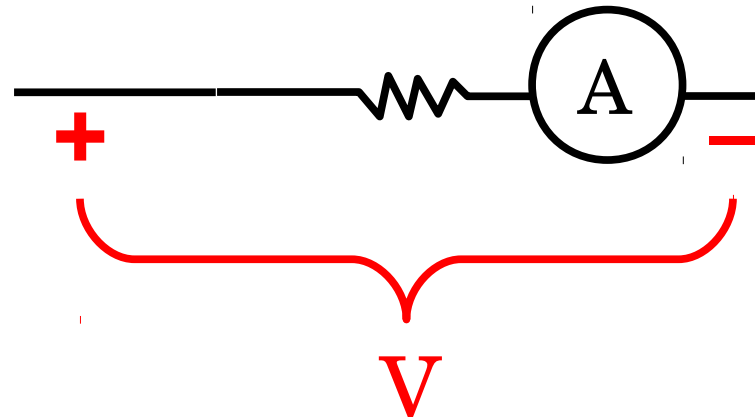

Power Dissipation

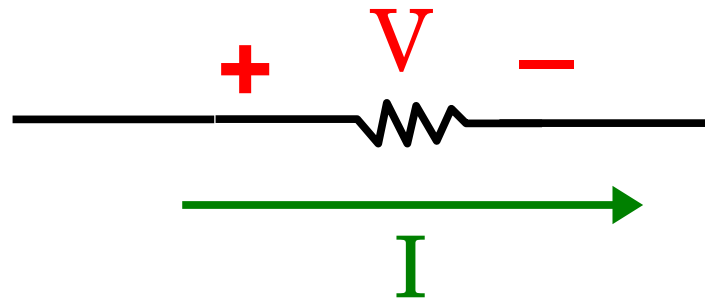

Power Dissipation

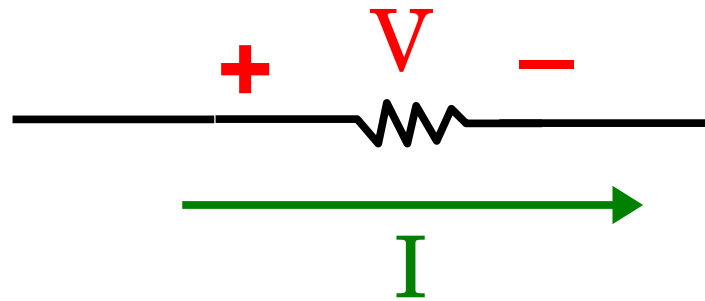


$$\text{Power dissipated} = \frac{V^2}{R} = I^2 R$$

AC (alternating current) circuits



AC (alternating current) circuits

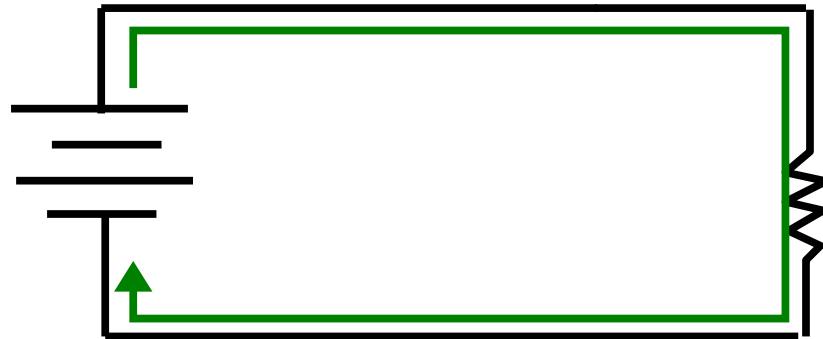


Current flow

AC (alternating current) circuits




AC (alternating current) circuits


Current flow

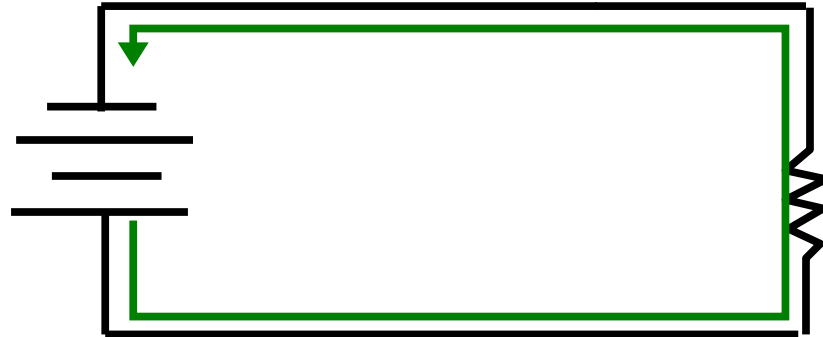



Square wave source

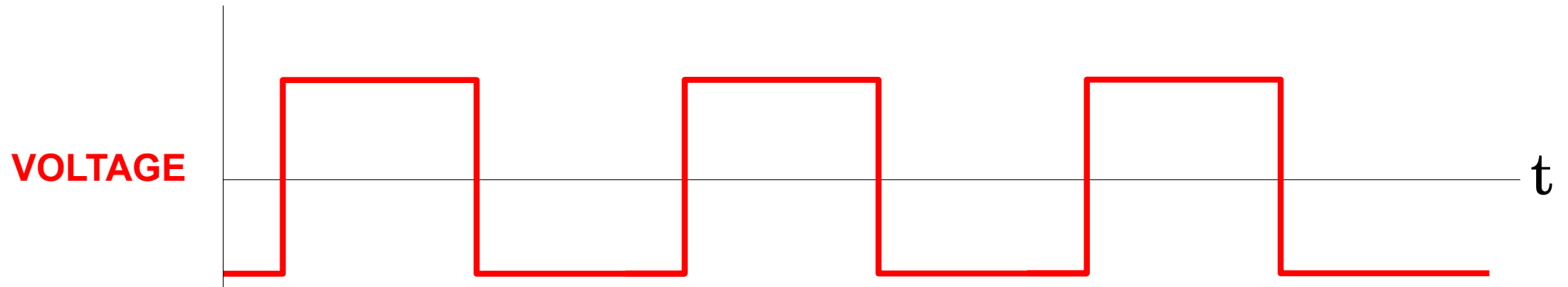



Square wave source

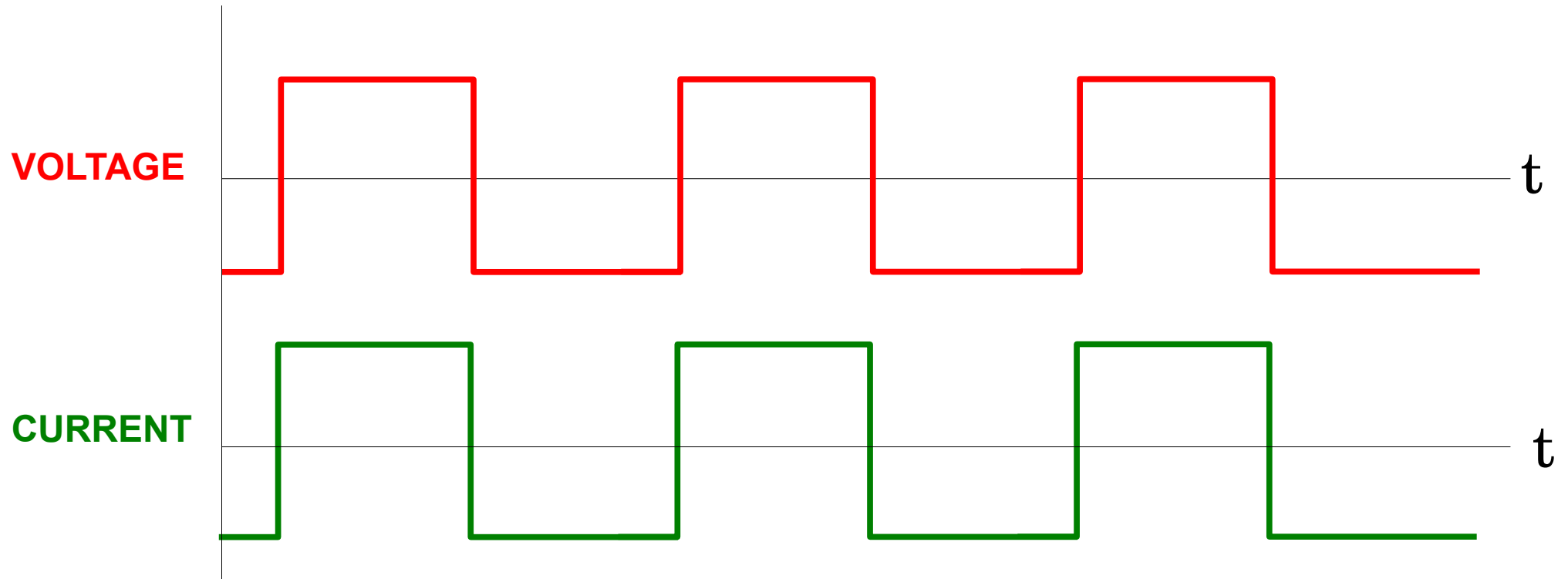



Square wave source +

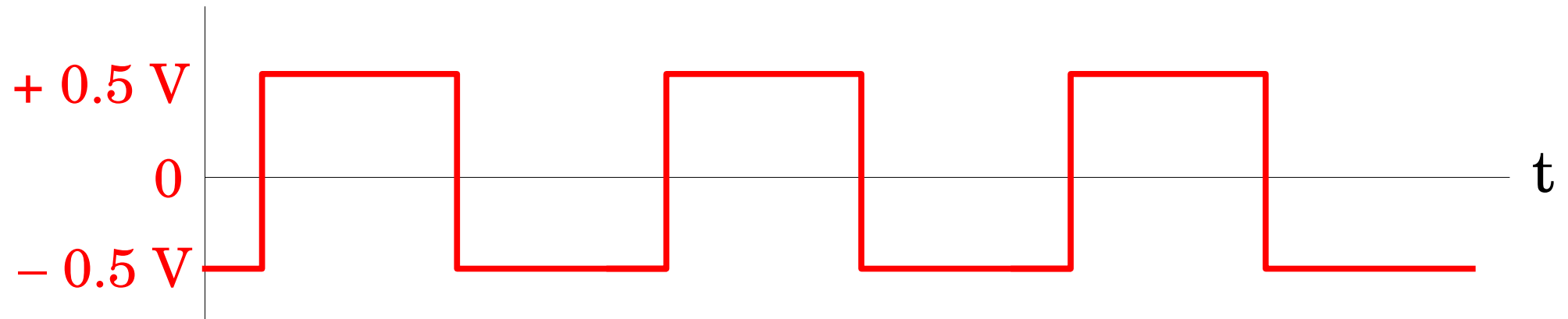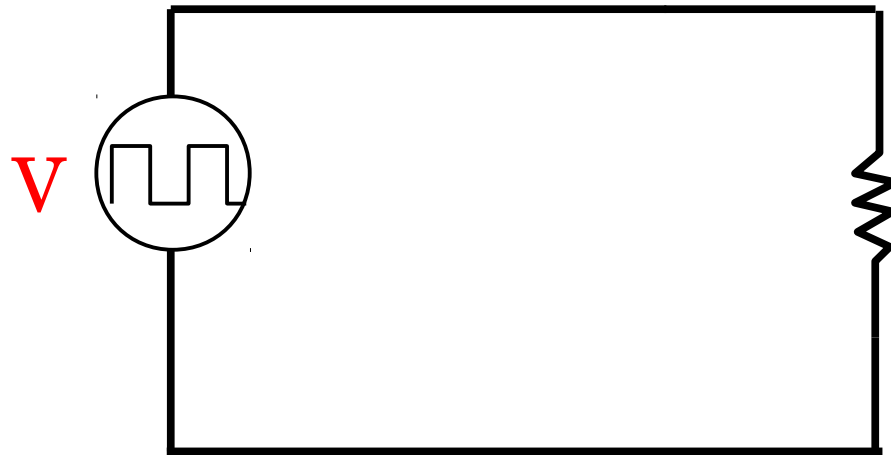



Square wave source + voltage offset

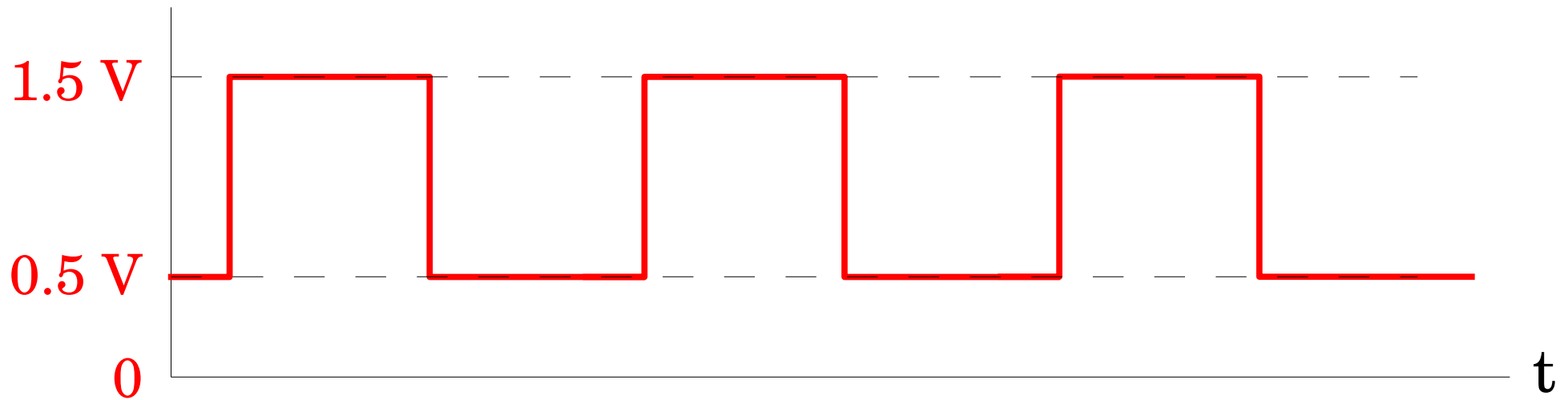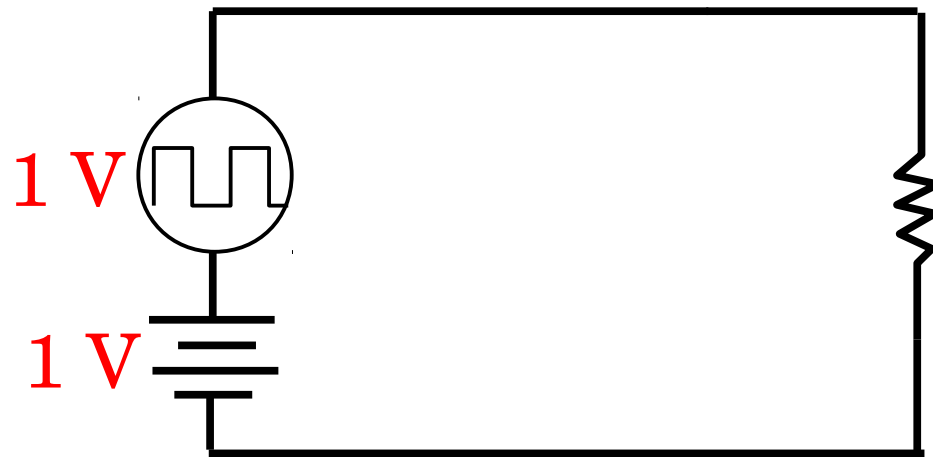


Square wave source + voltage offset

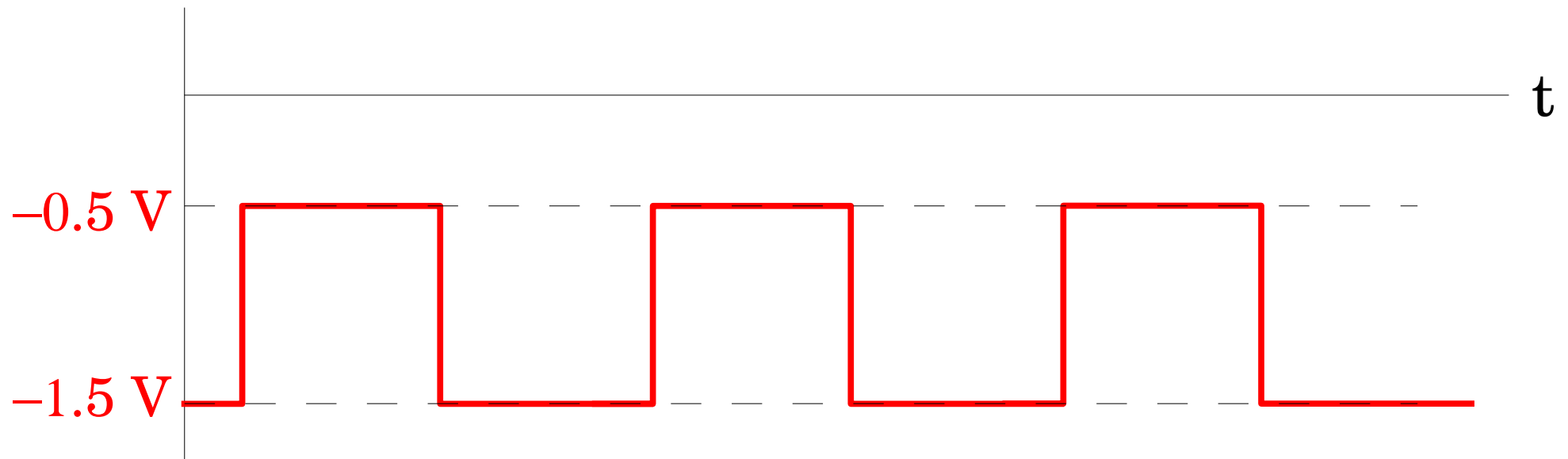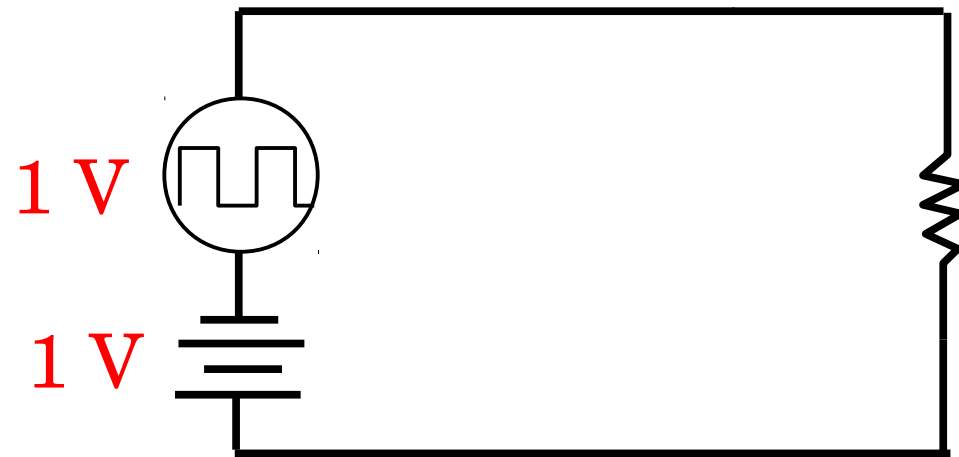


Square wave source + voltage offset

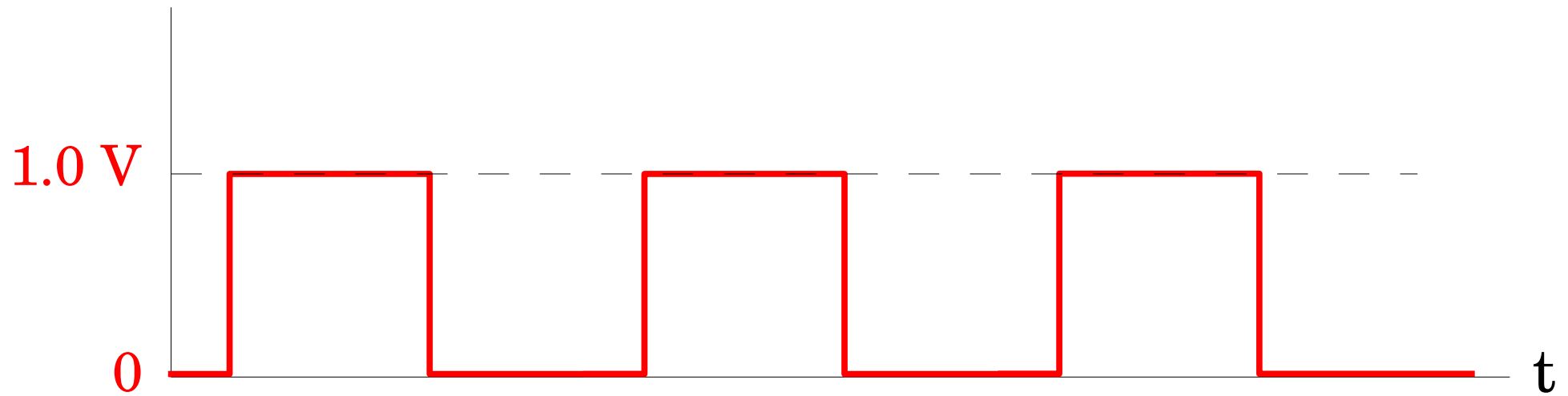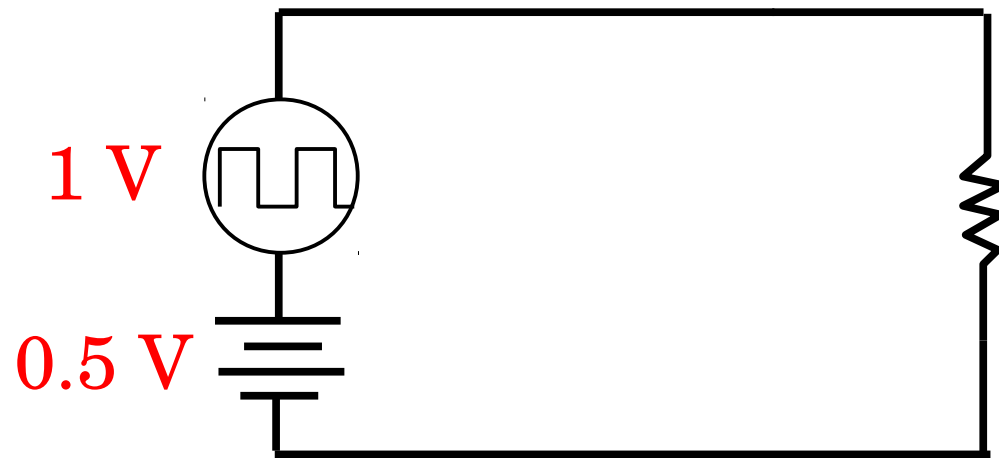


Triangle wave source

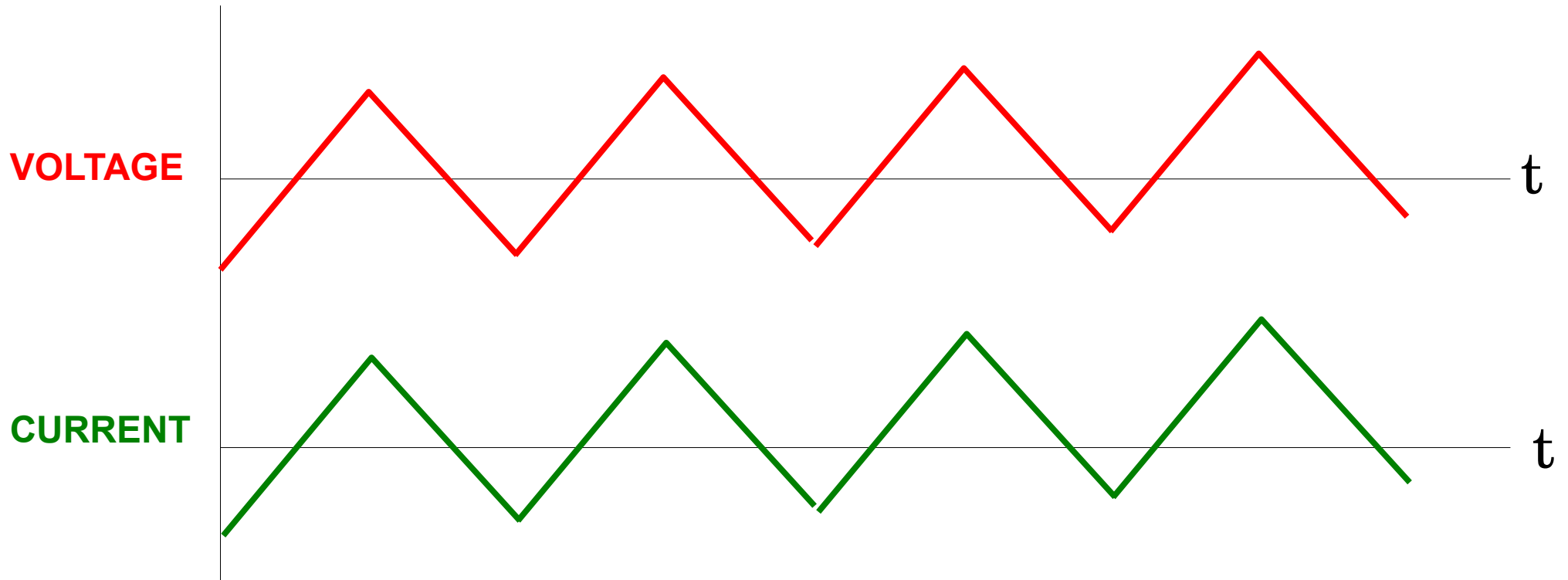

Sinusoidal wave source + dc offset

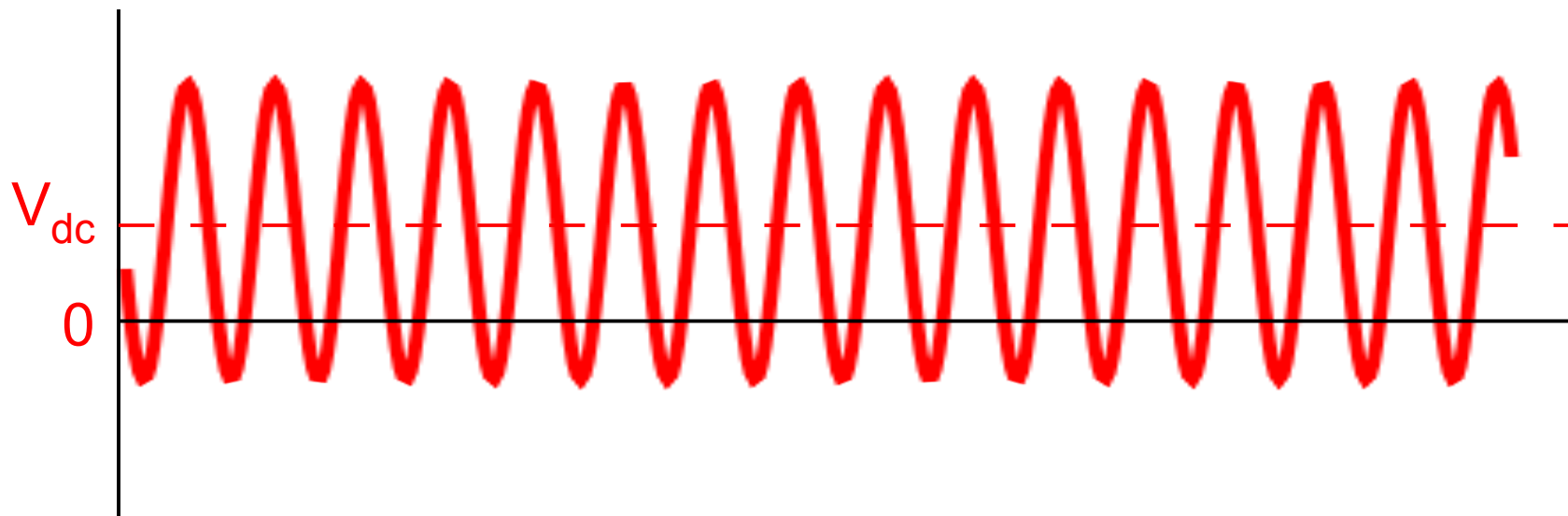


Characterizing an AC wave

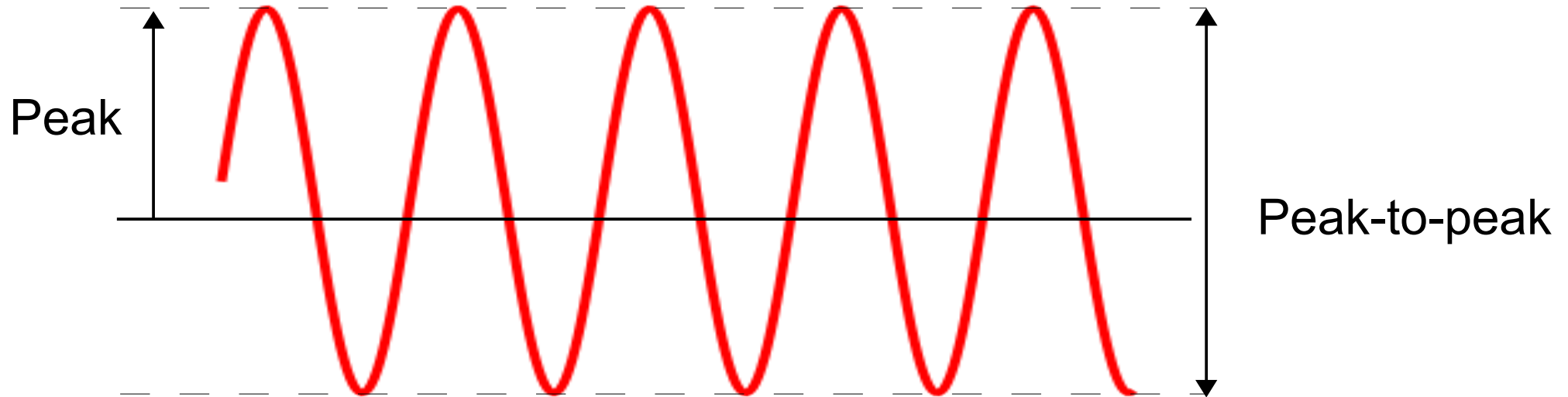


The average voltage of a pure sine wave is identically zero.


$$V(t) = V_p \sin(\omega t)$$

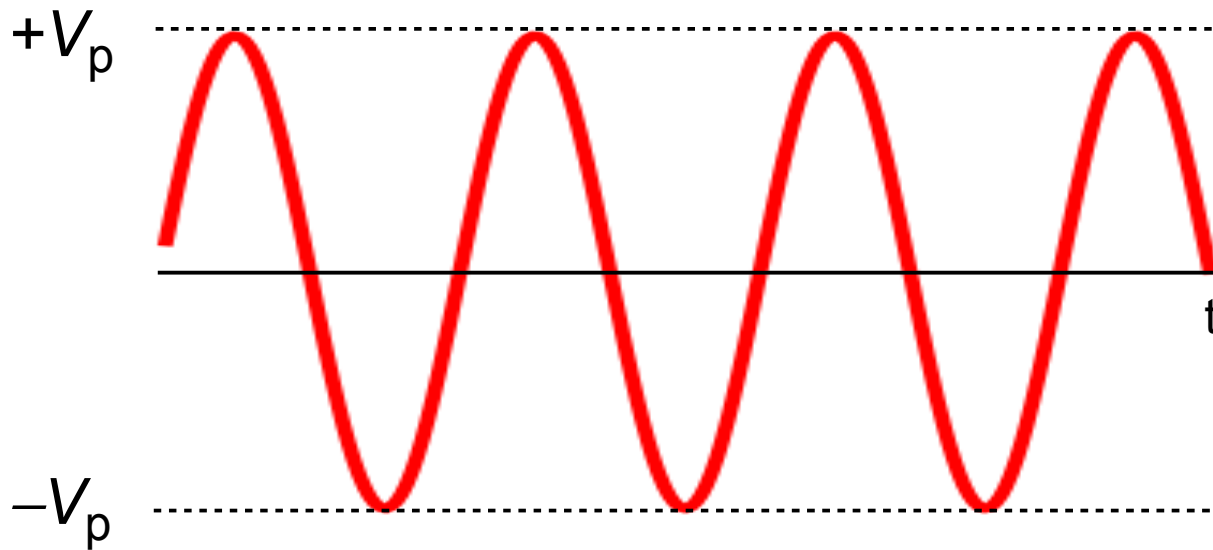

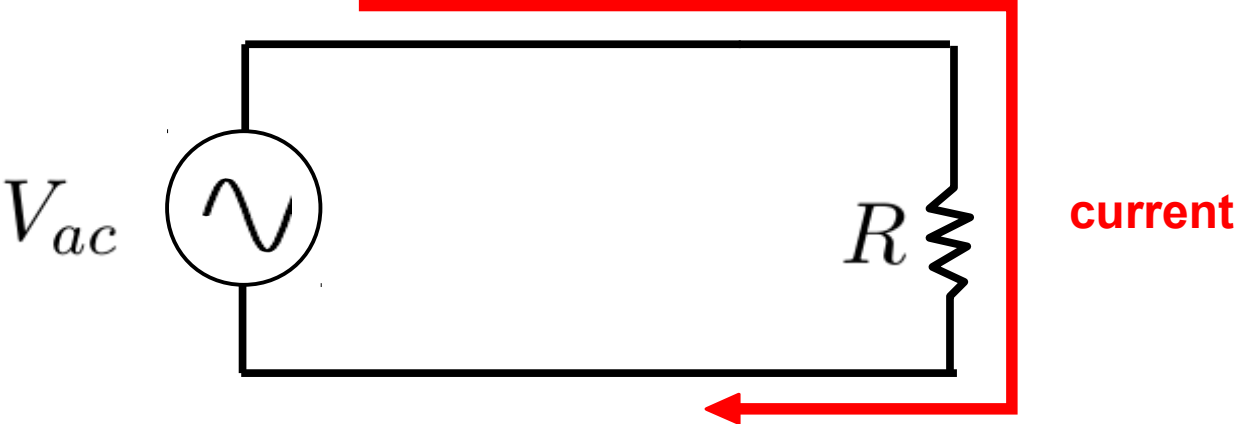
We know that an AC voltage can deliver plenty of power to a load



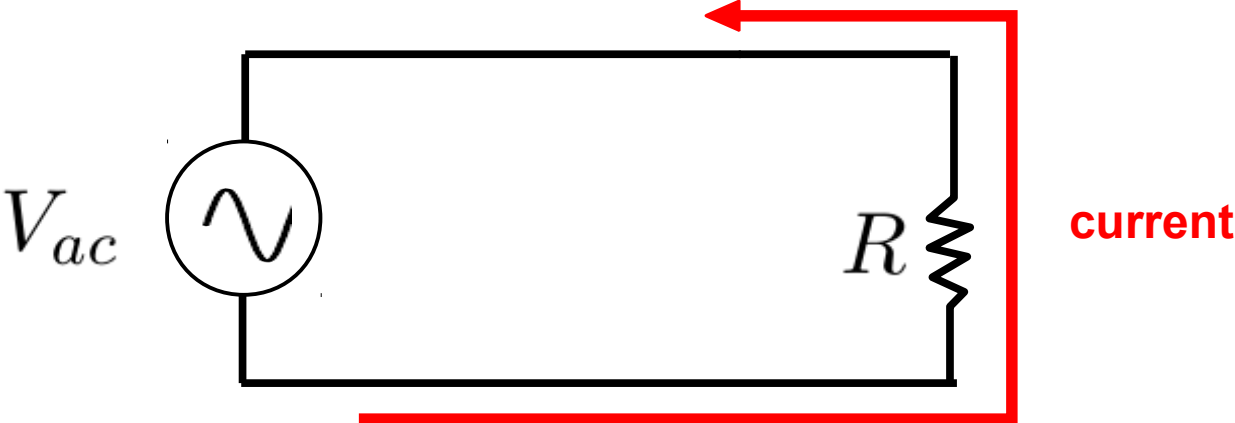We know that an AC voltage can deliver plenty of power to a load




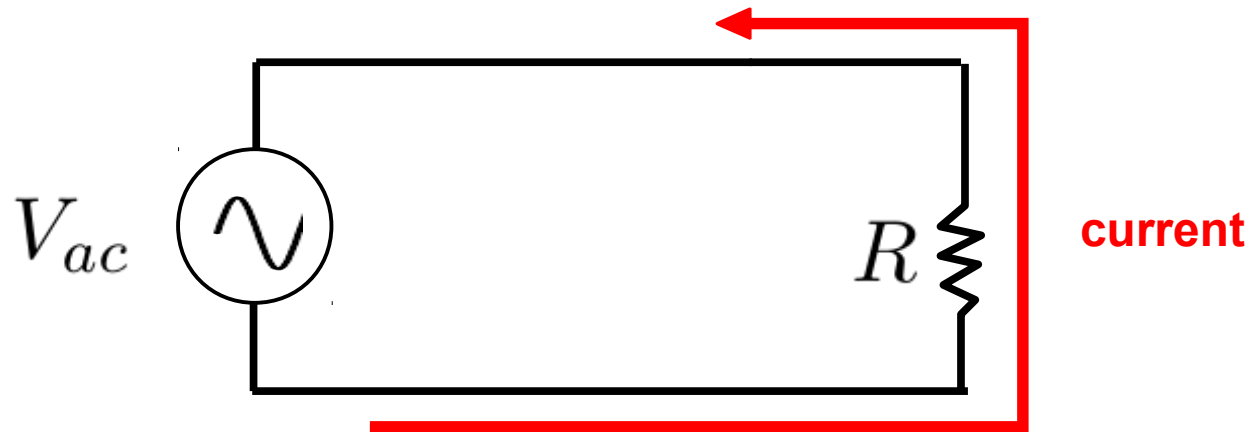We know that an AC voltage can deliver plenty of power to a load



How do we calculate this power if the average voltage and current is zero?

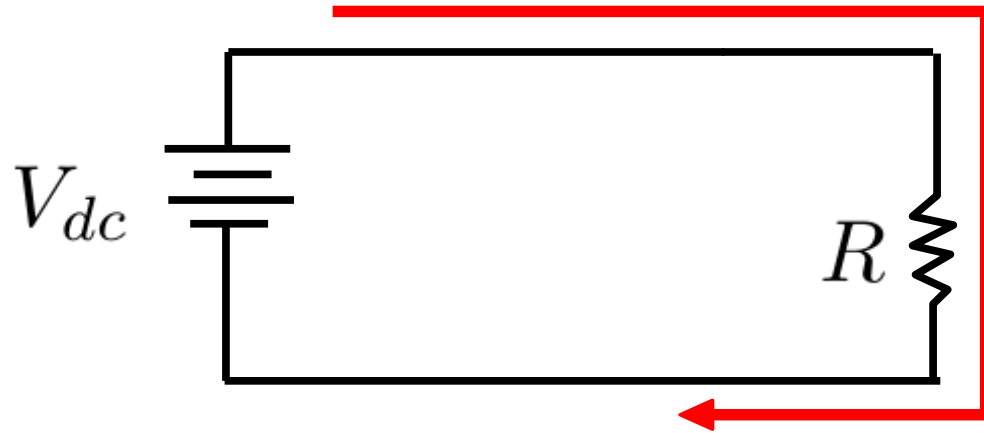
This is easy in a DC circuit: Use Ohm's Law



$$\text{POWER} = \frac{V_{dc}^2}{R}$$

Power dissipated in an AC circuit is time dependent:
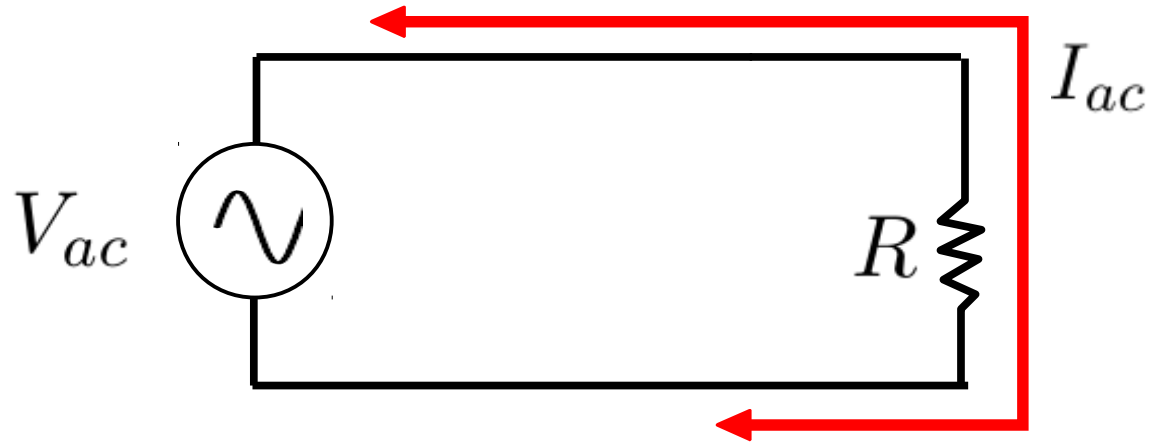
$$P(t) = V_{ac}I_{ac} = \frac{V_{ac}^2}{R}$$



What is the energy delivered in **one period**?
Temporally integrate the power over one period:

$$\frac{1}{T} \int_0^T P(t) dt = \frac{1}{TR} \int_0^T V_p^2 \sin(\omega t)^2 dt = \frac{V_p^2}{2R}$$

$$\text{AC power dissipation} = \frac{V_p^2}{2R}$$

$$\text{DC power dissipation} = \frac{V_{dc}^2}{R}$$


AC voltage producing
power dissipation equivalent $V_{RMS} = \frac{V_p}{\sqrt{2}}$

- An RMS measurement assumes a stable, periodic signal
- Characterized by a single value of voltage, current
- Measured with a multimeter or oscilloscope


The situation is often not that convenient!



OSCILLOSCOPE

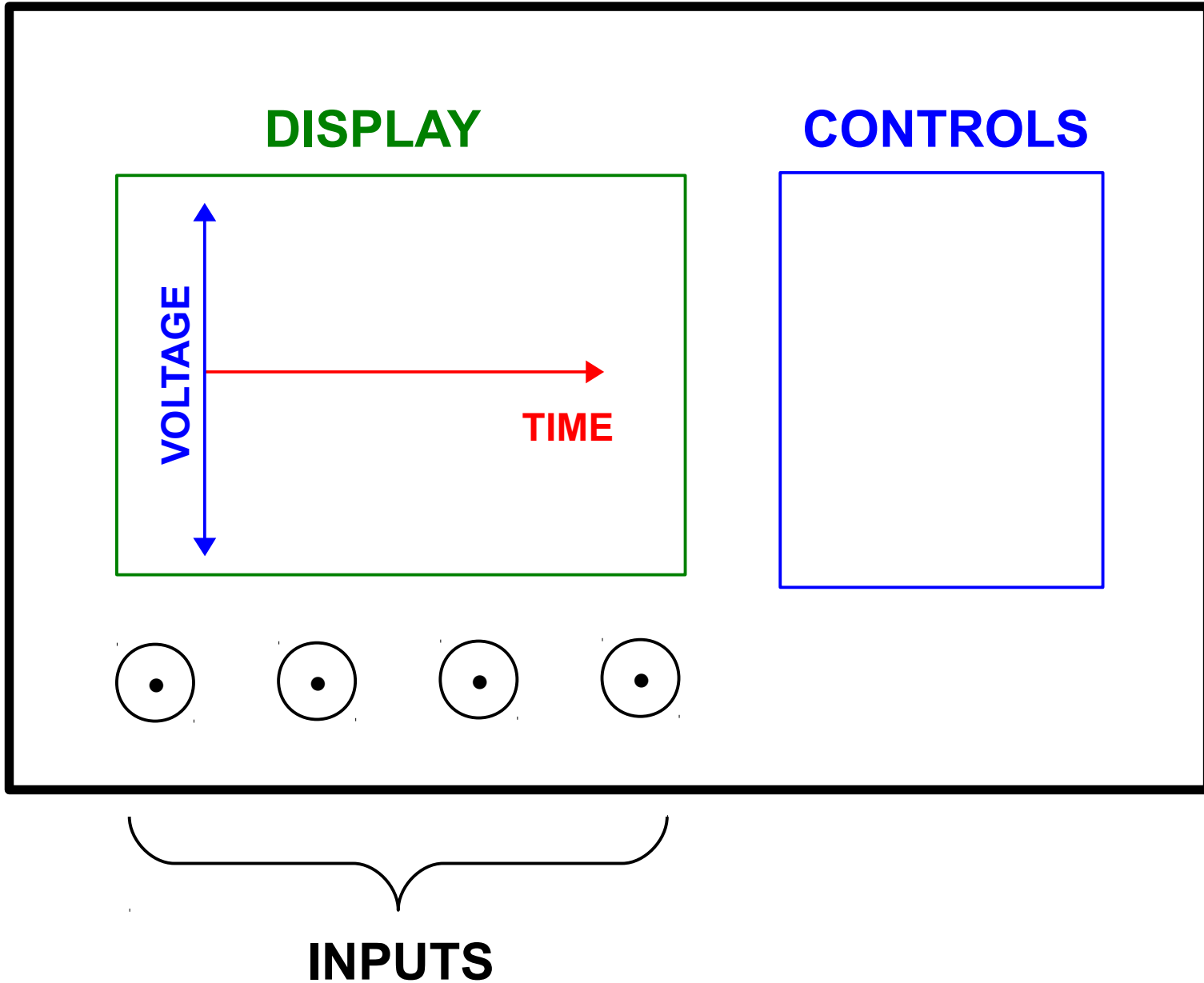


OSCILLOSCOPE

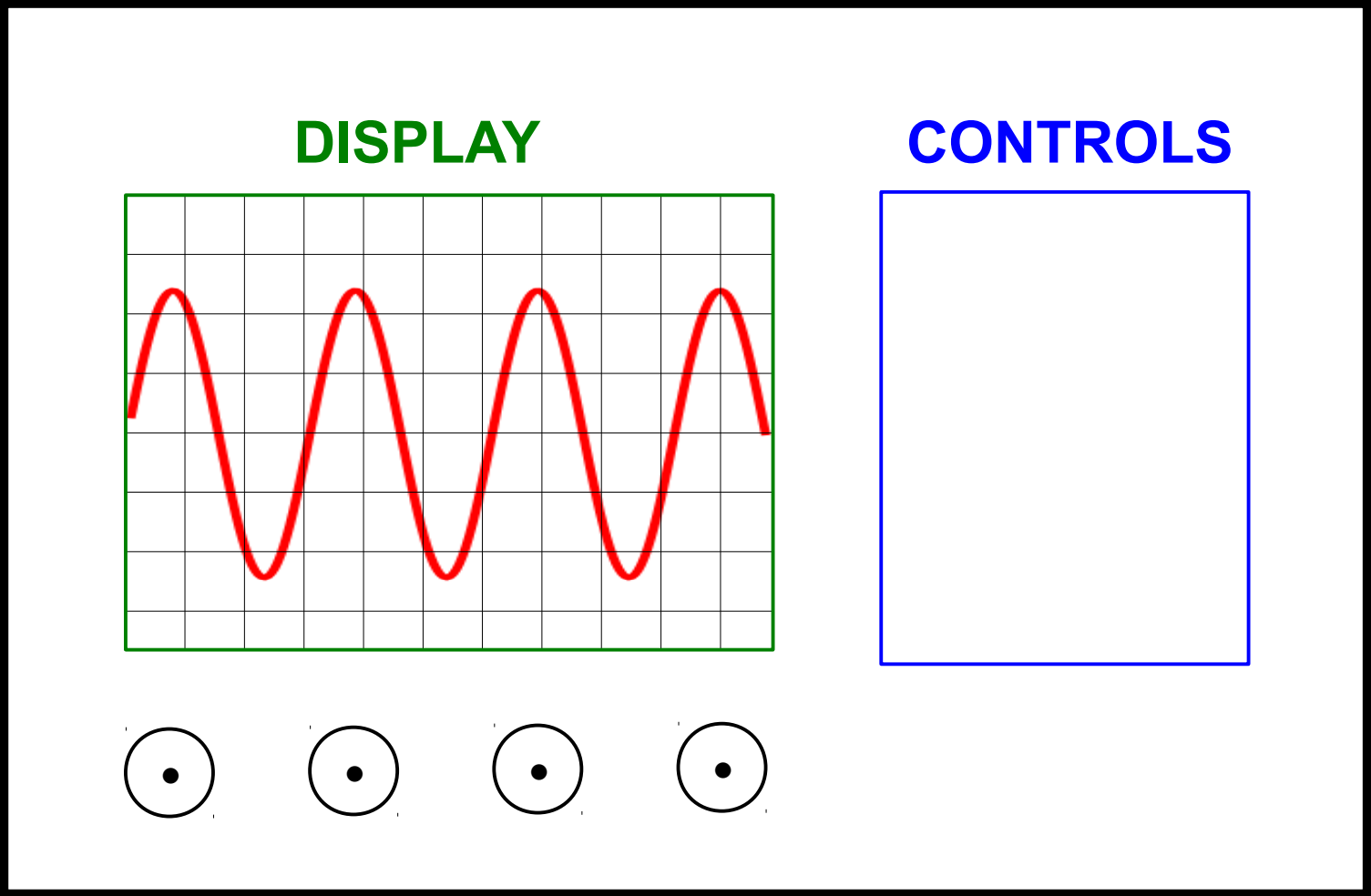

DISPLAY

CONTROLS

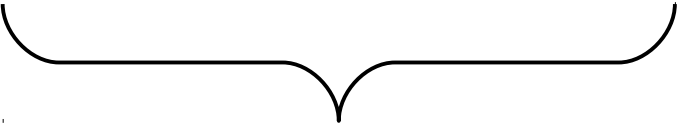


INPUTS

ANALOG: Cathode ray tube, swept electron beam


DIGITAL: A/D converter, LCD display

Although physical operation is completely different,
controls are nearly identical


DISPLAY ADJUSTMENT

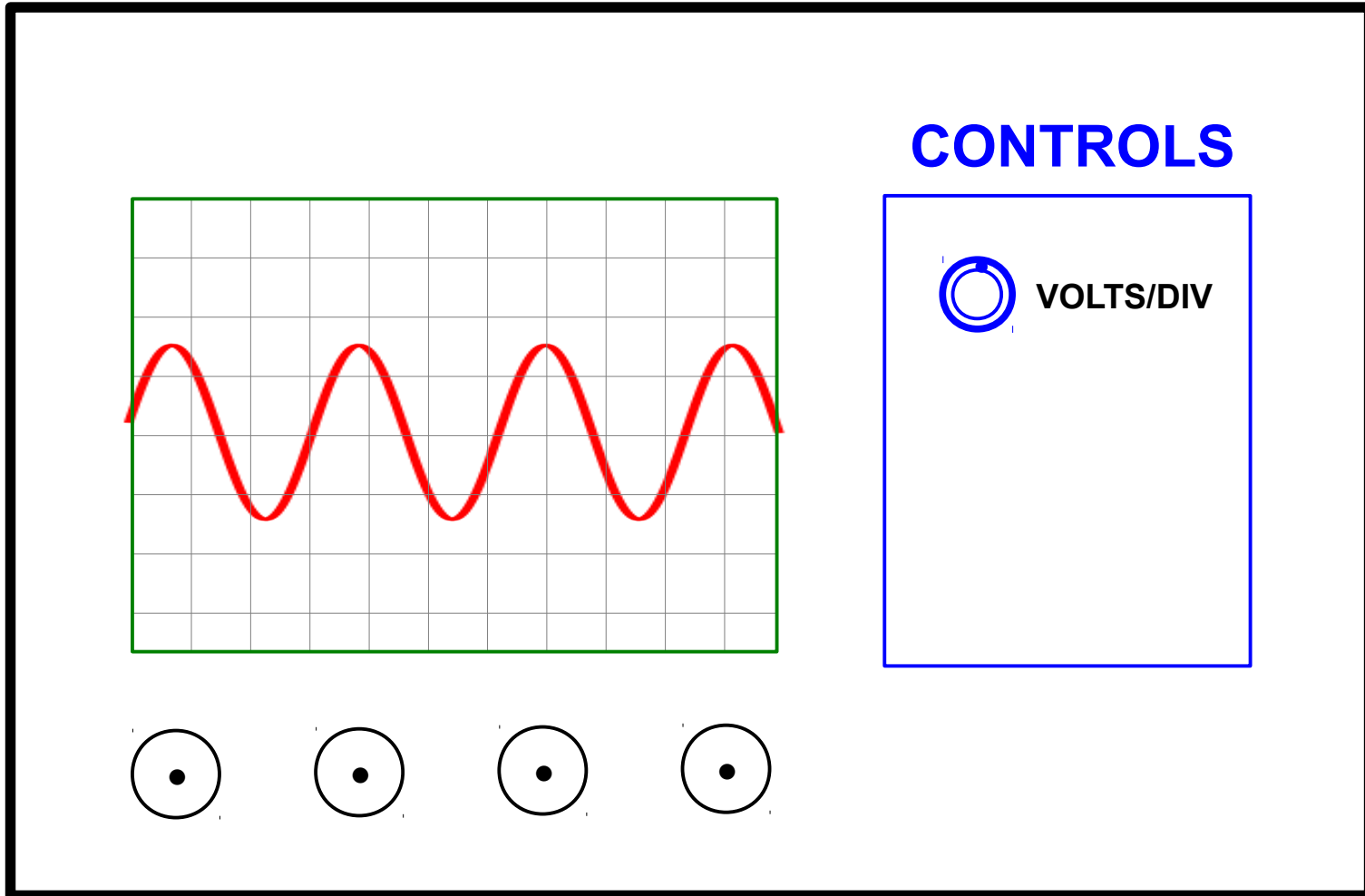


DISPLAY ADJUSTMENT

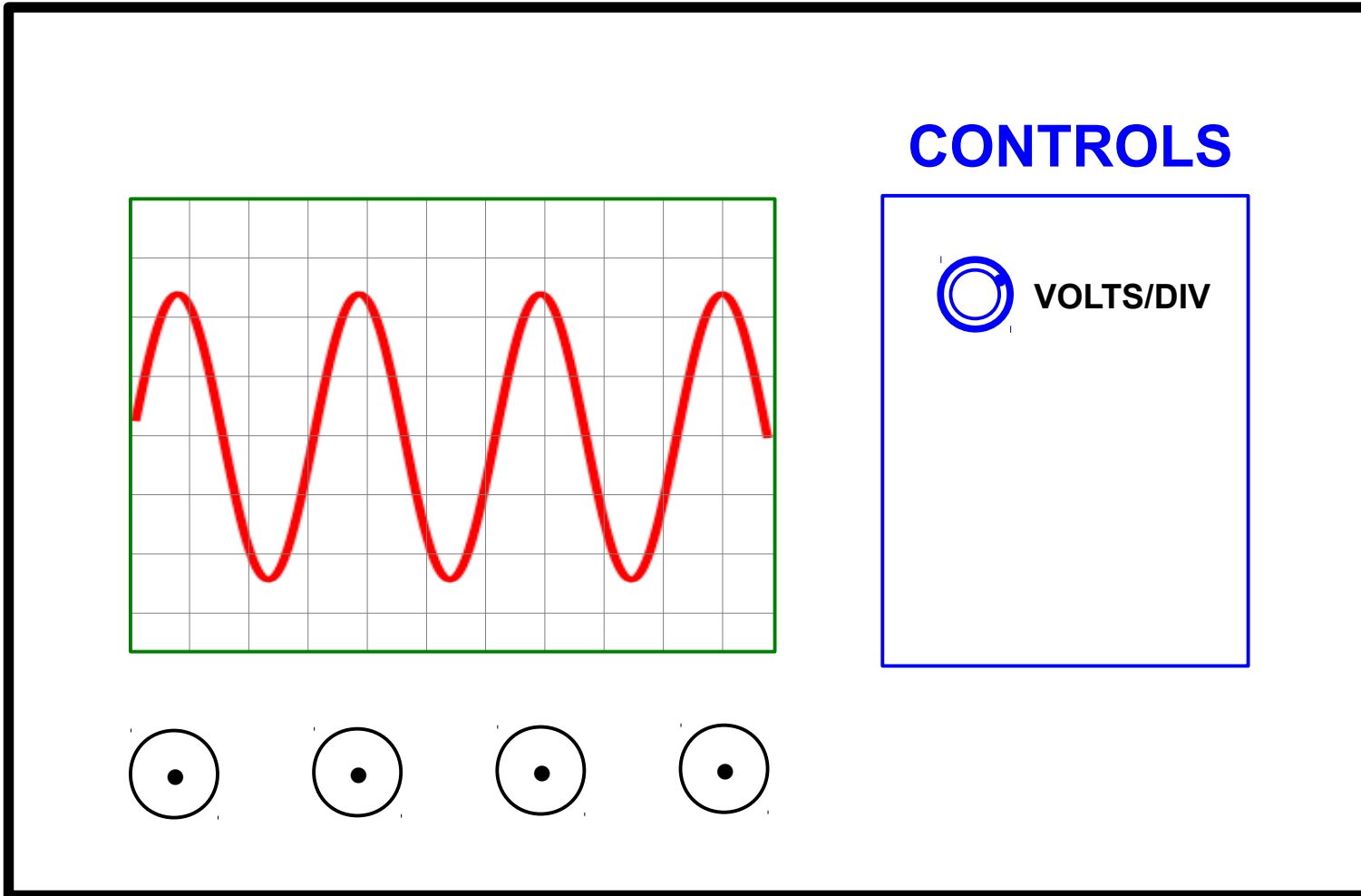


DISPLAY ADJUSTMENT

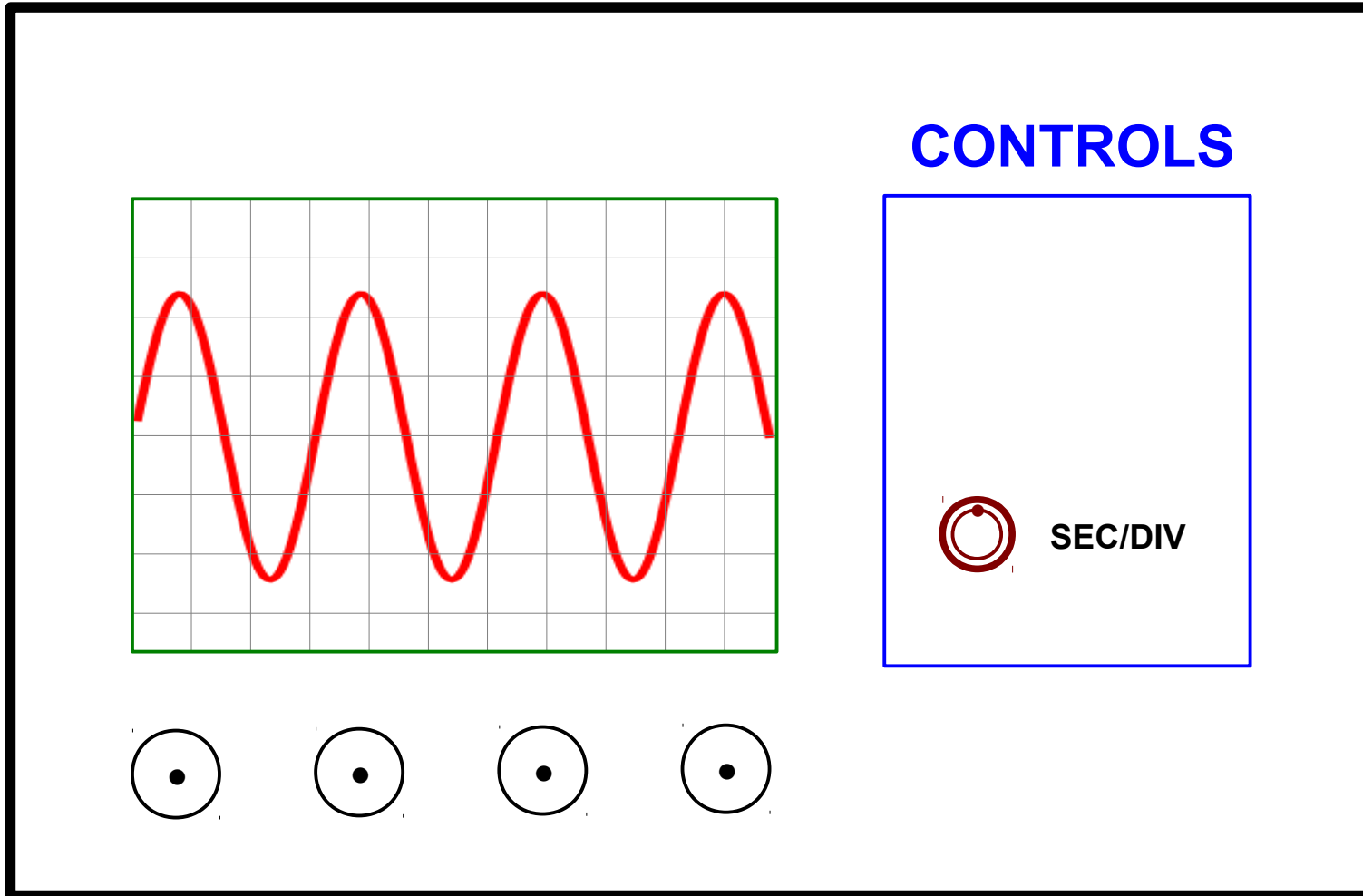


DISPLAY ADJUSTMENT

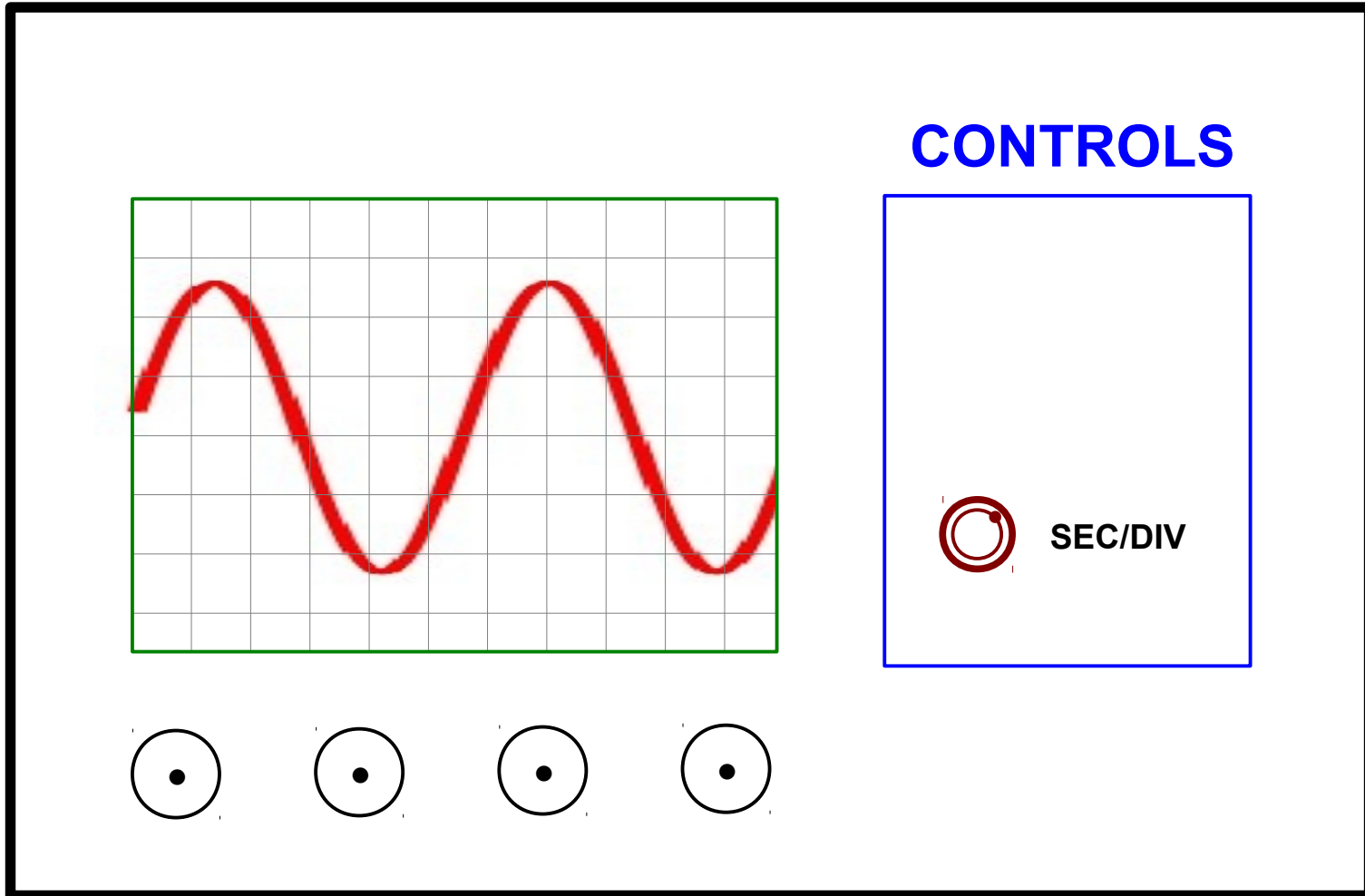


DC coupling, AC coupling, and Ground

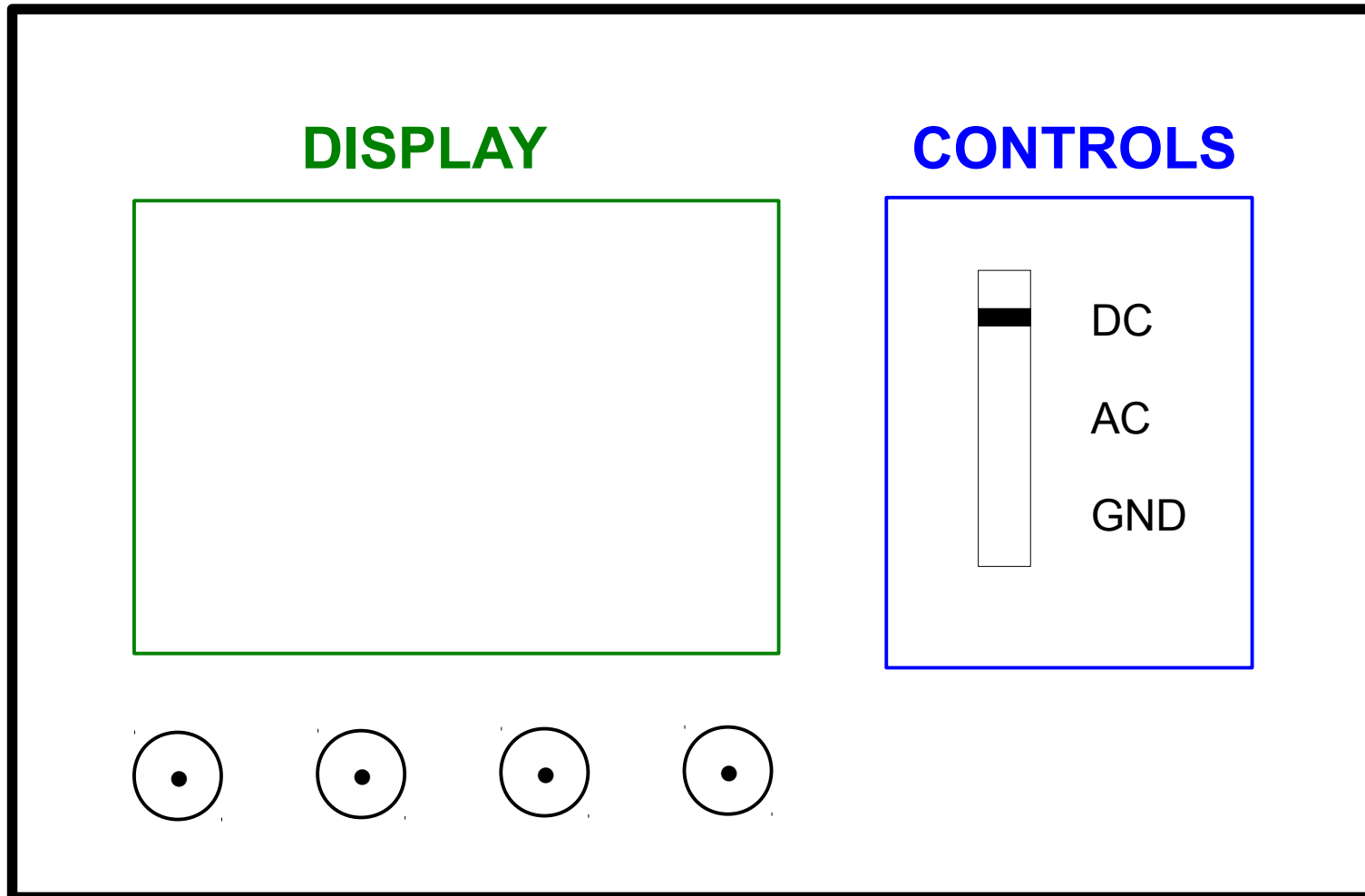

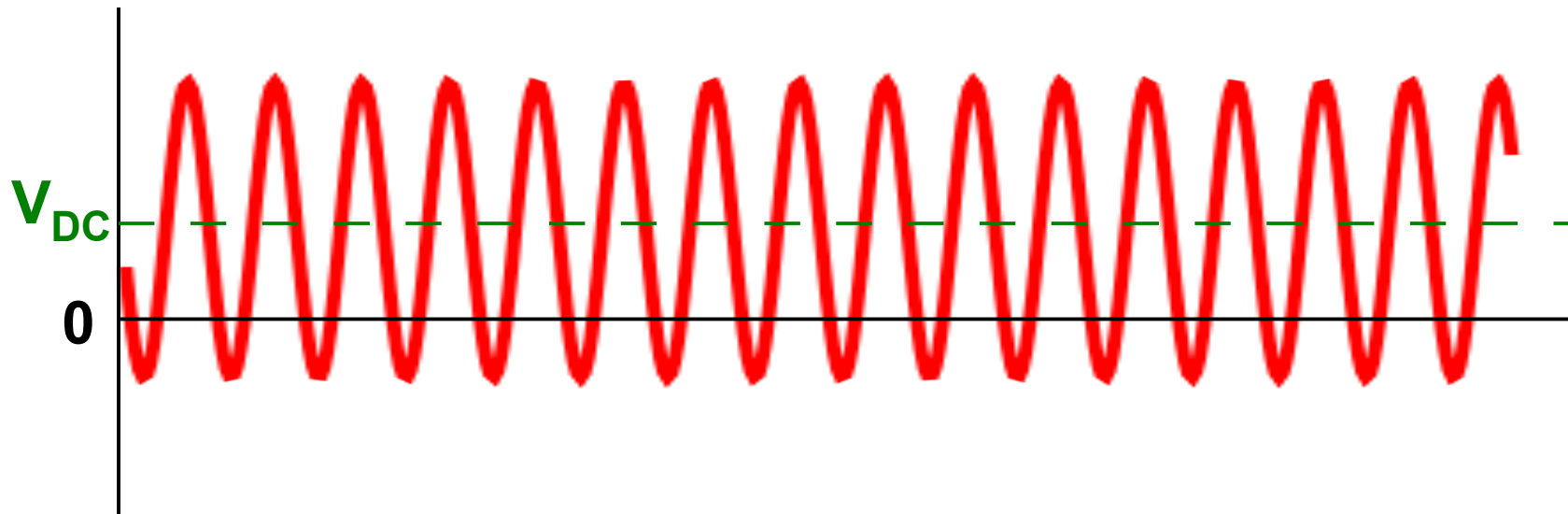
EXAMPLE: Sinusoidal wave source + DC offset




DC COUPLING

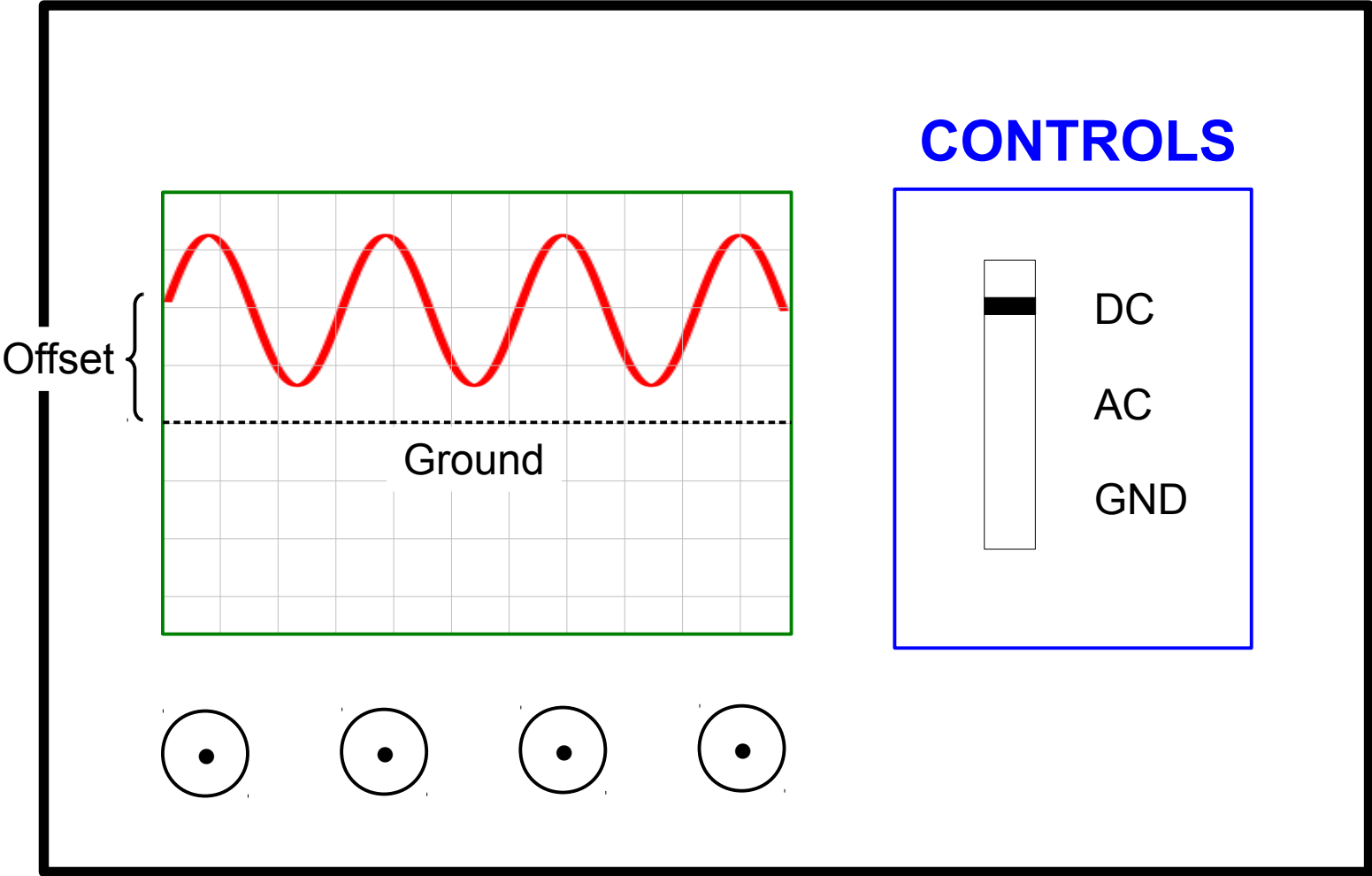


AC COUPLING

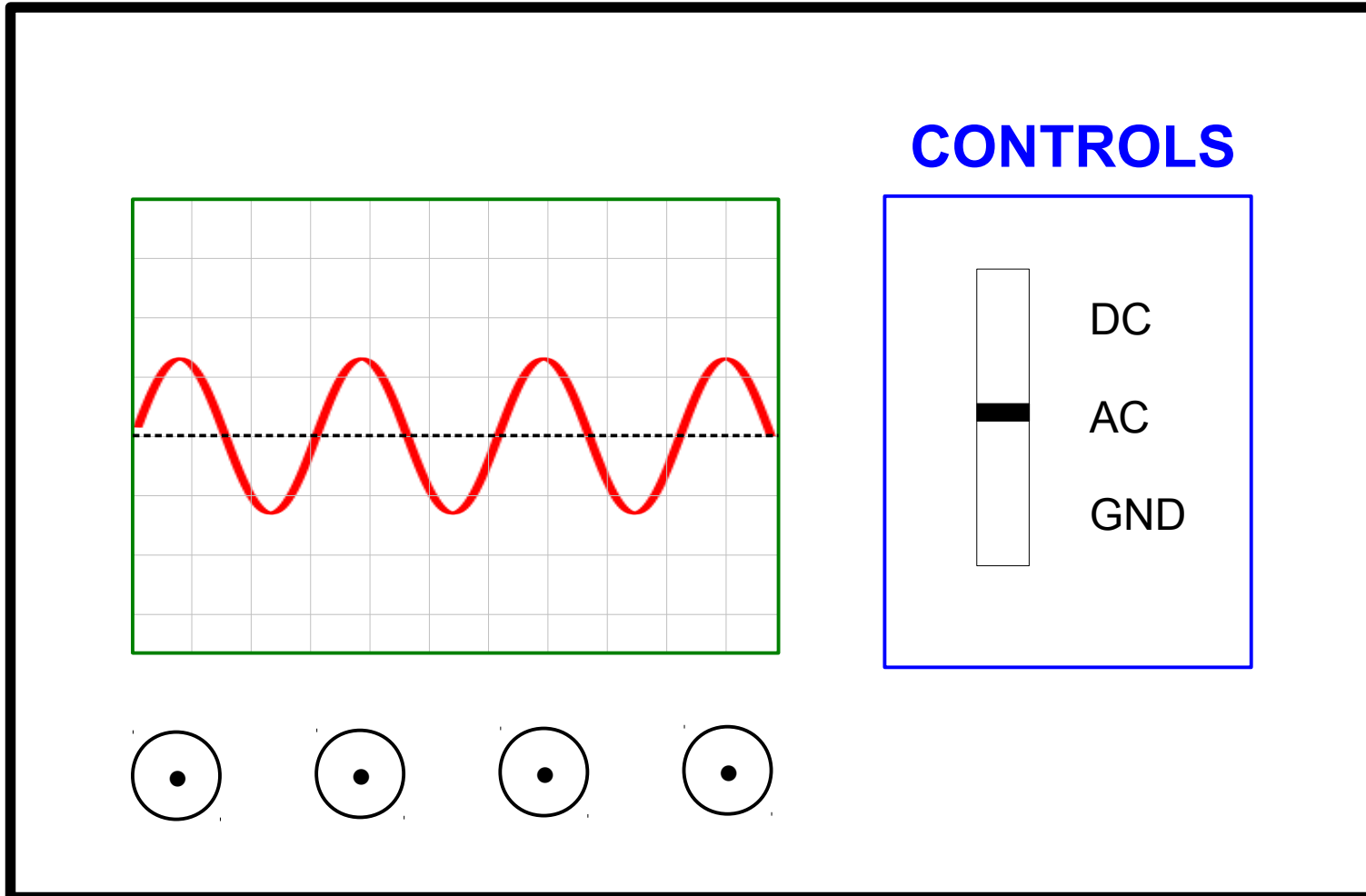


GROUND: Defines location of 0 Volts

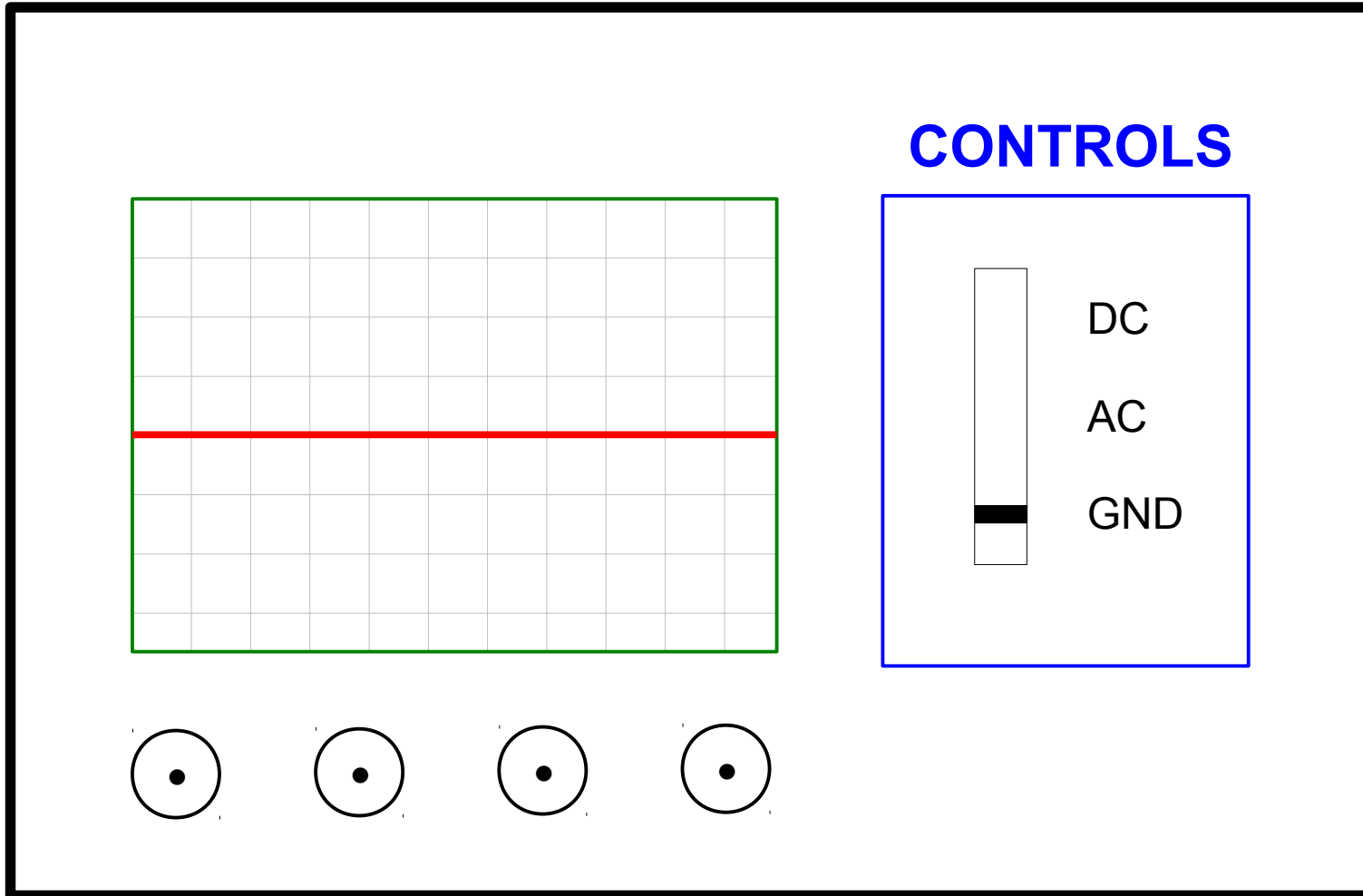

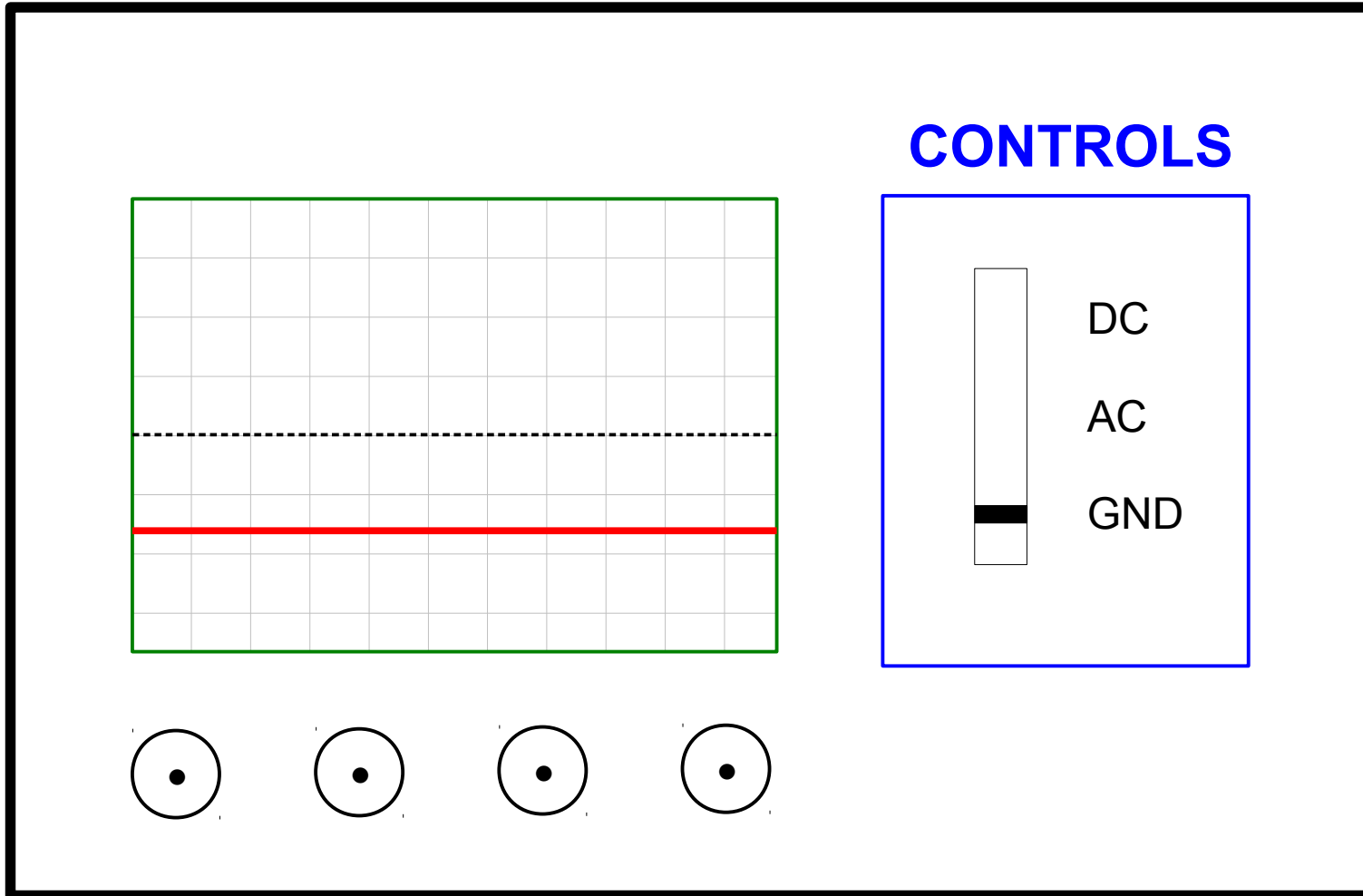
GROUND can be positioned at any convenient level



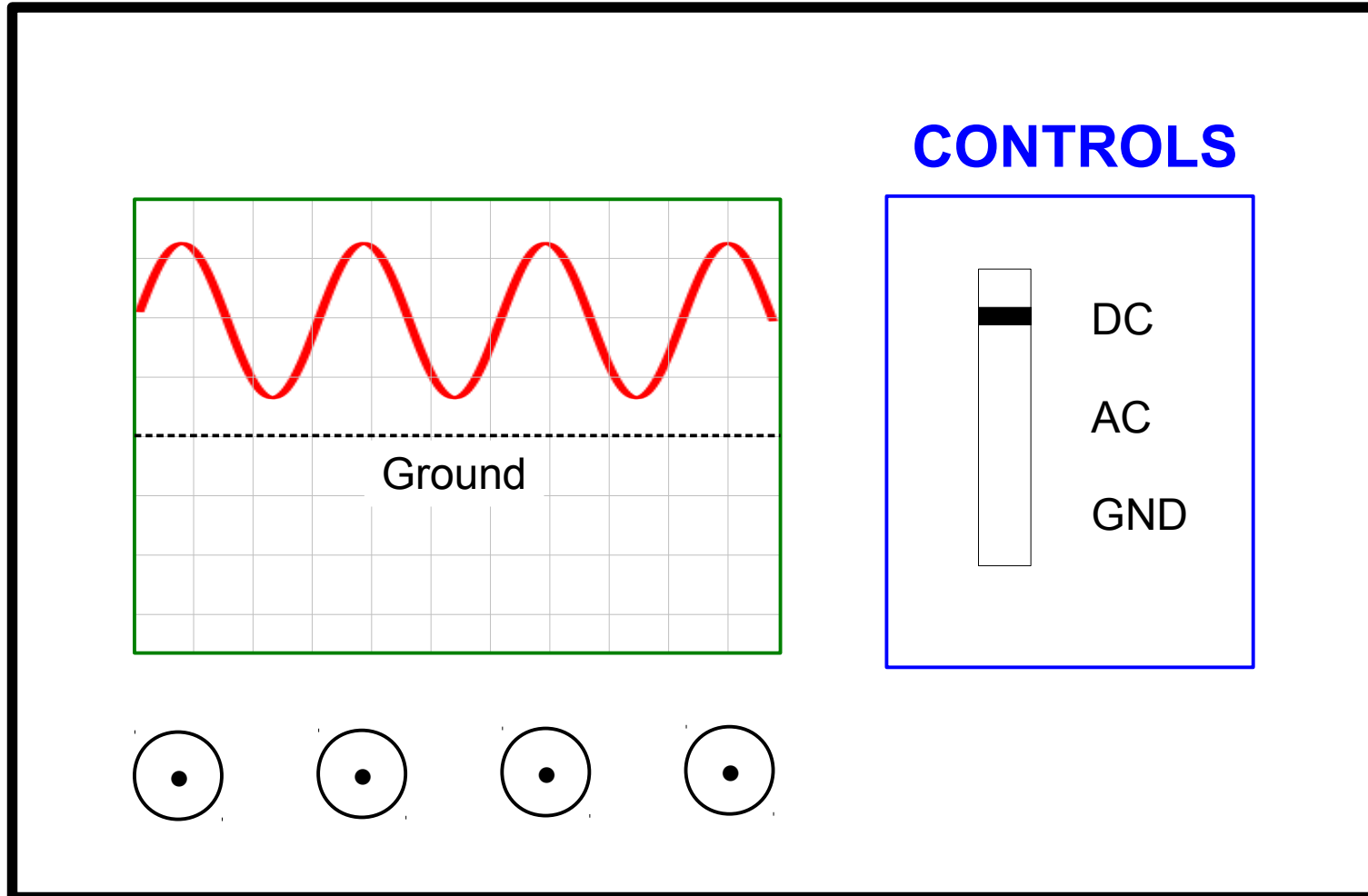
Why bother with AC coupling when DC coupling shows everything?



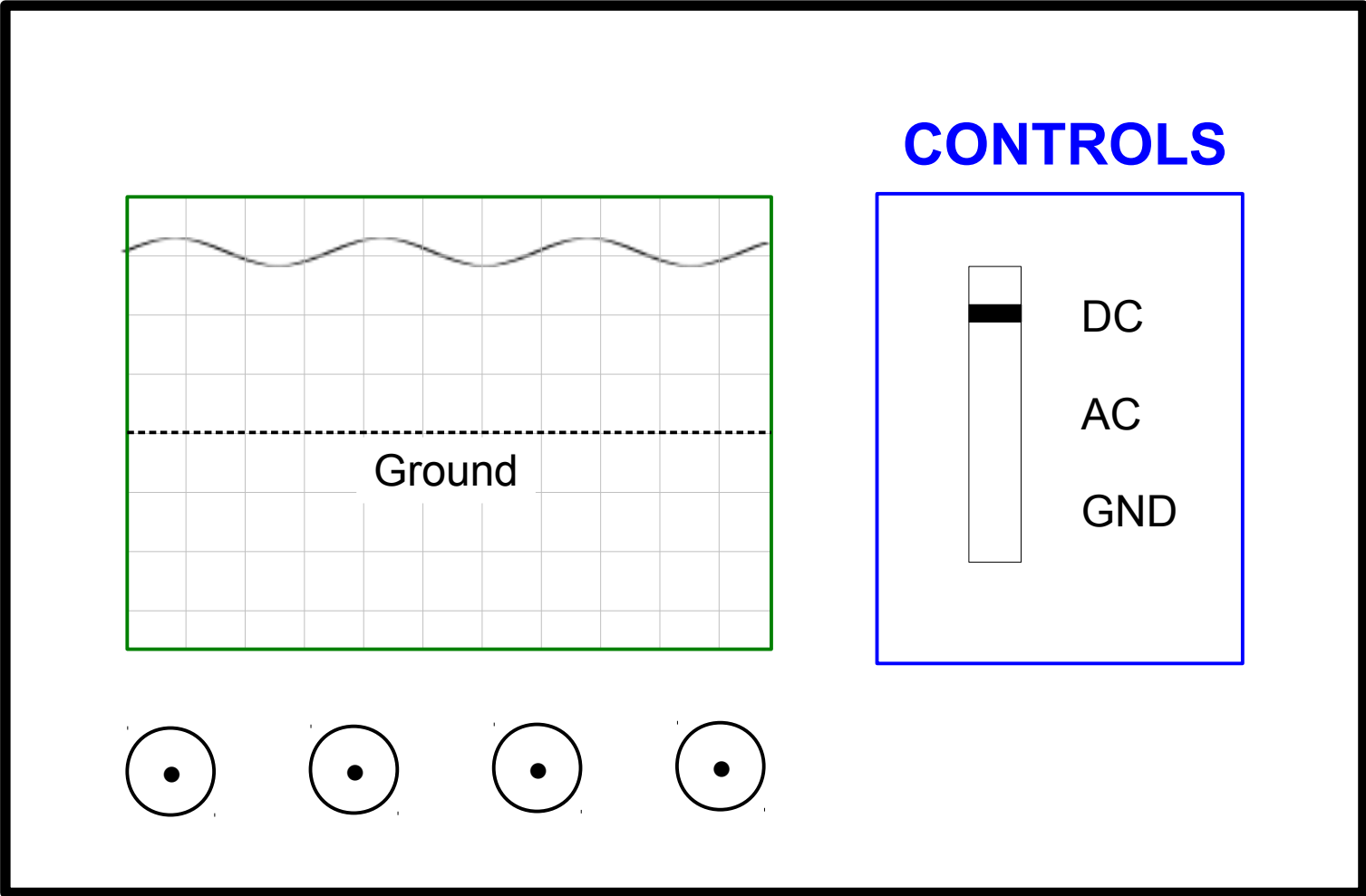Often we have very weak modulation of a DC signal



AC couple and change the vertical scale

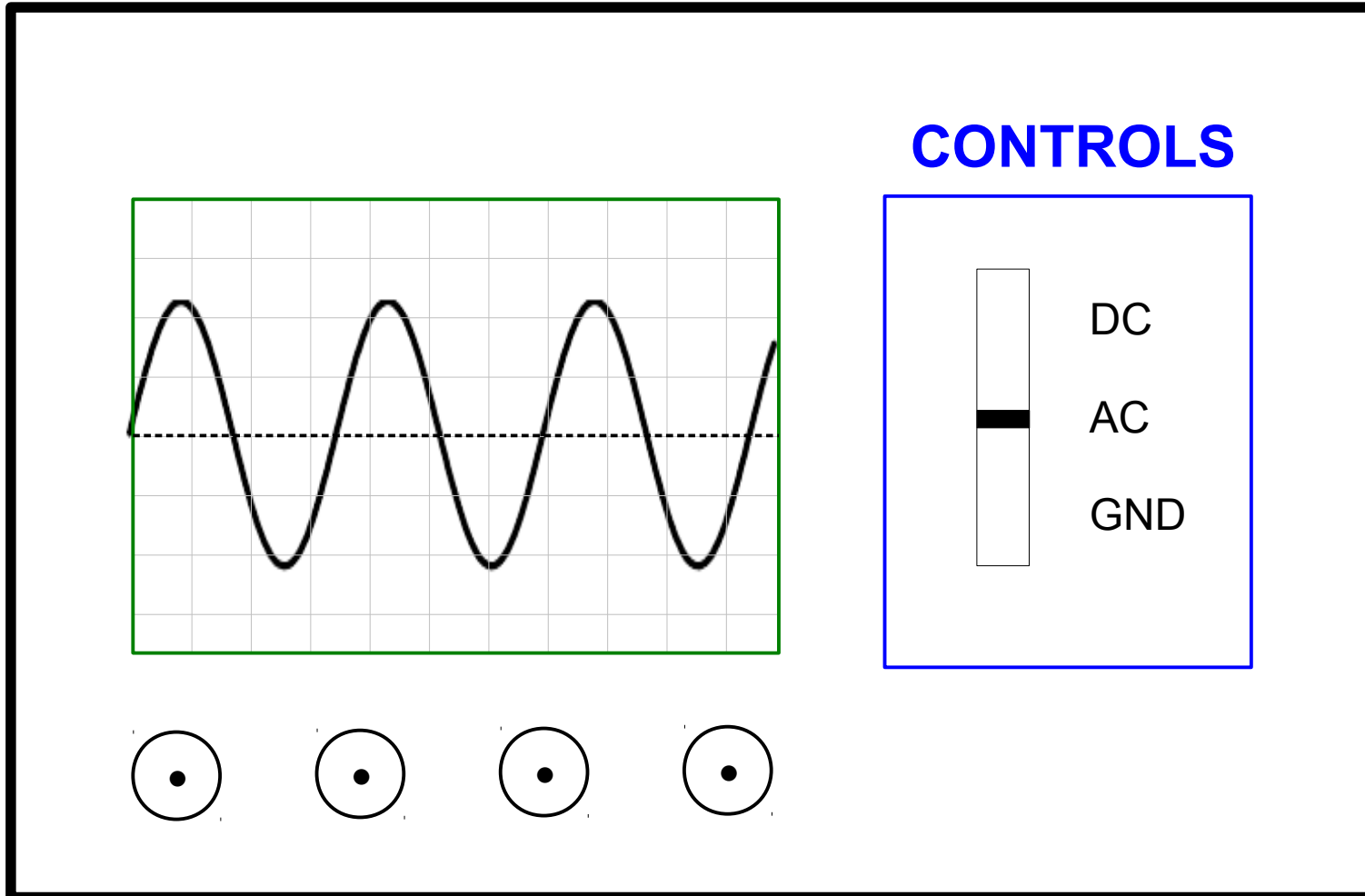

TRIGGERING

Auto: Scope gives continually updated display

Normal: User controls when the slope triggers; Level, Slope
Trigger source: Channel 1, Channel 2, etc


Line: Triggers on 60 Hz AC

Single event


External

Use **Auto-Set** only when all else fails!


TRIGGER LEVEL

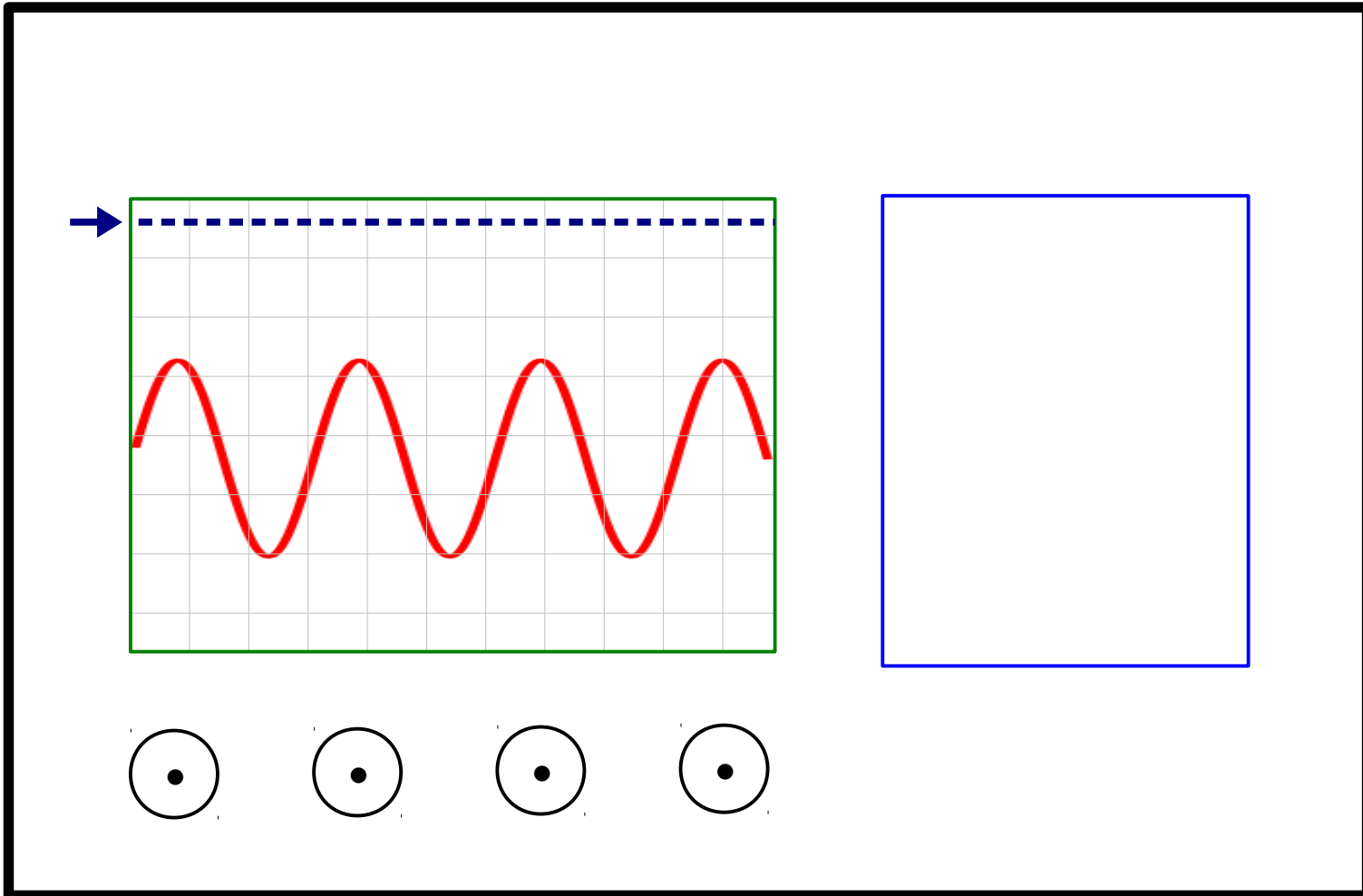

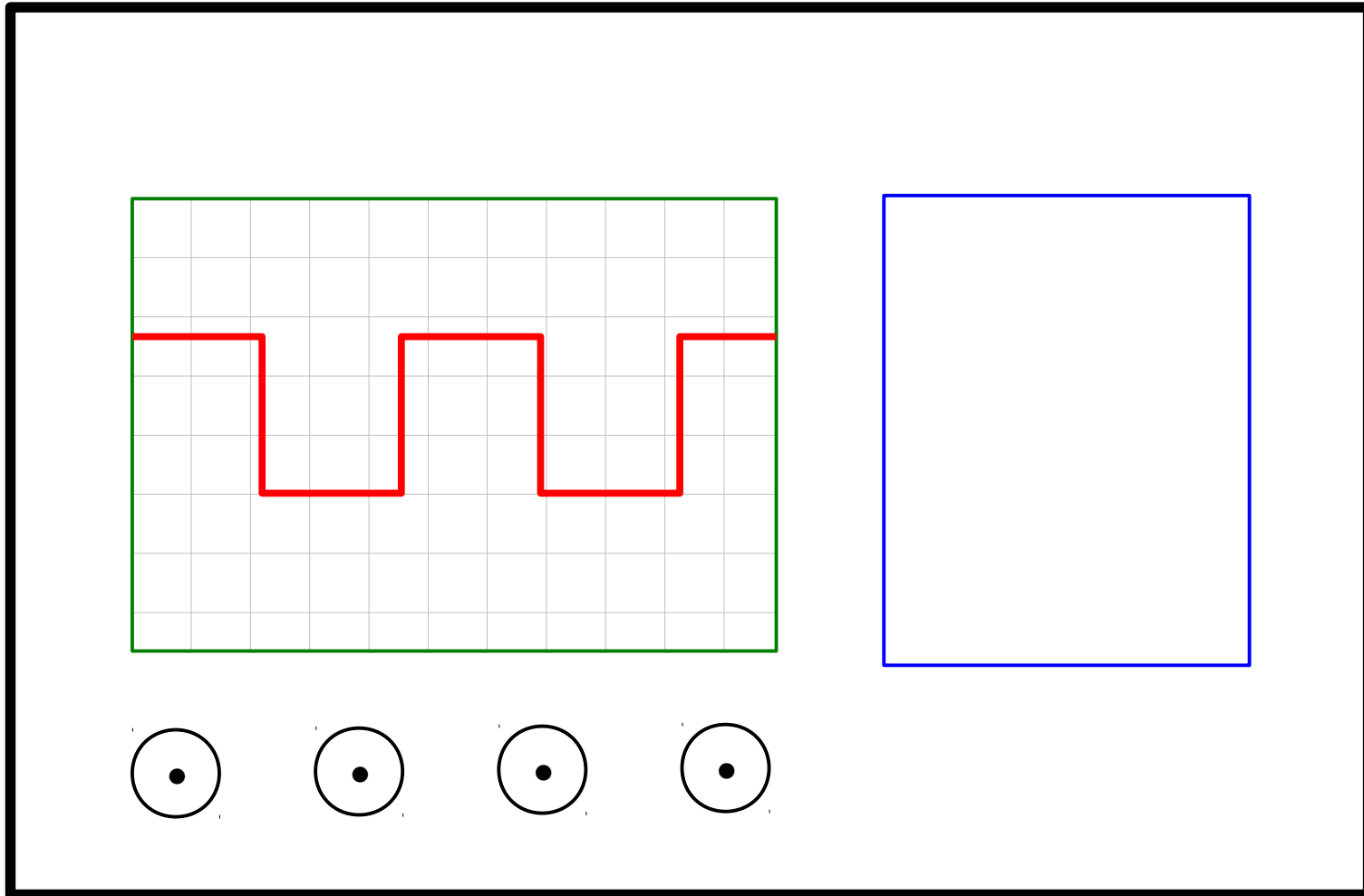
Example: Measure fall time of square wave




SOLUTION: Trigger on negative slope

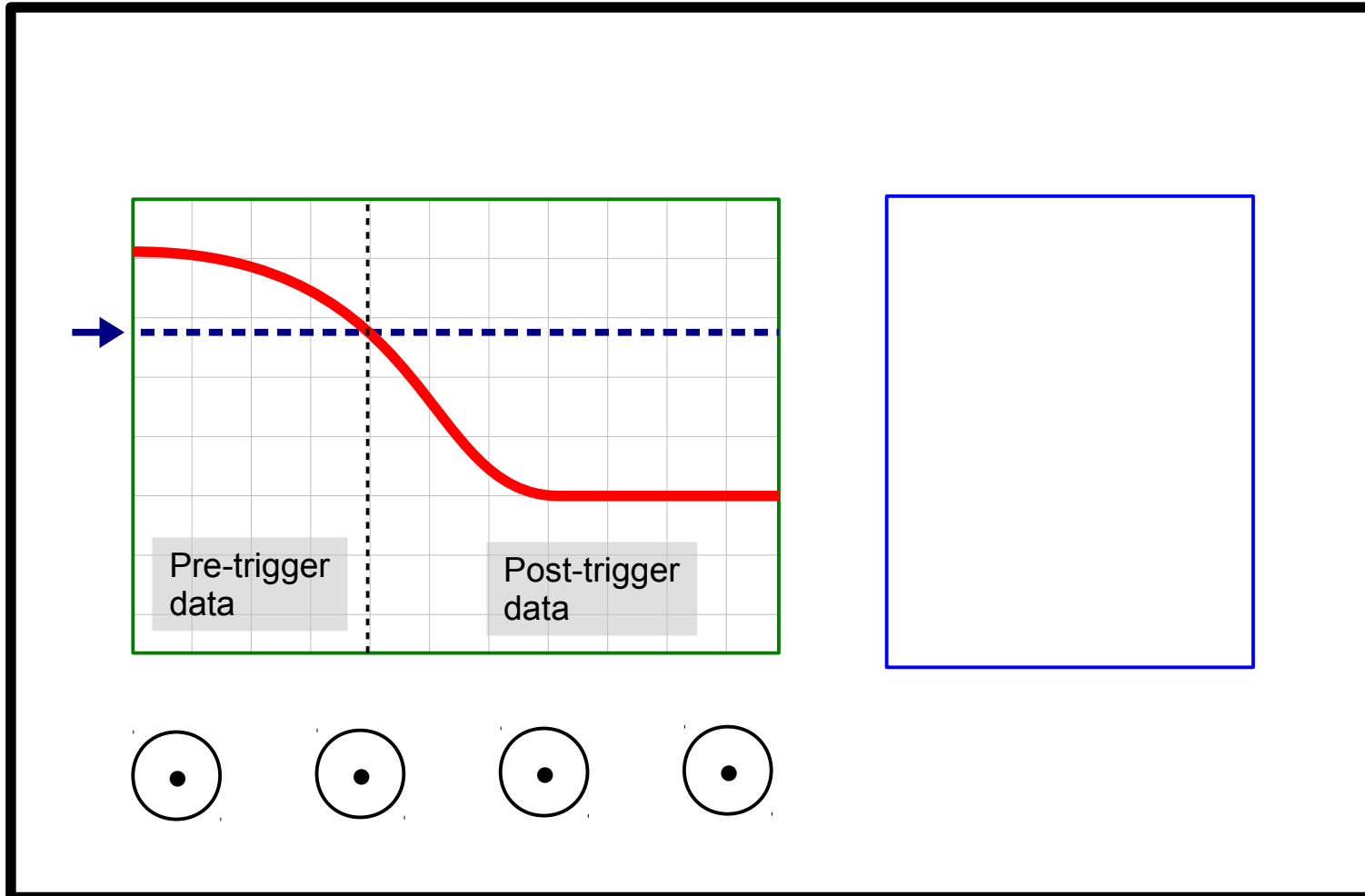

SAMPLING BANDWIDTH

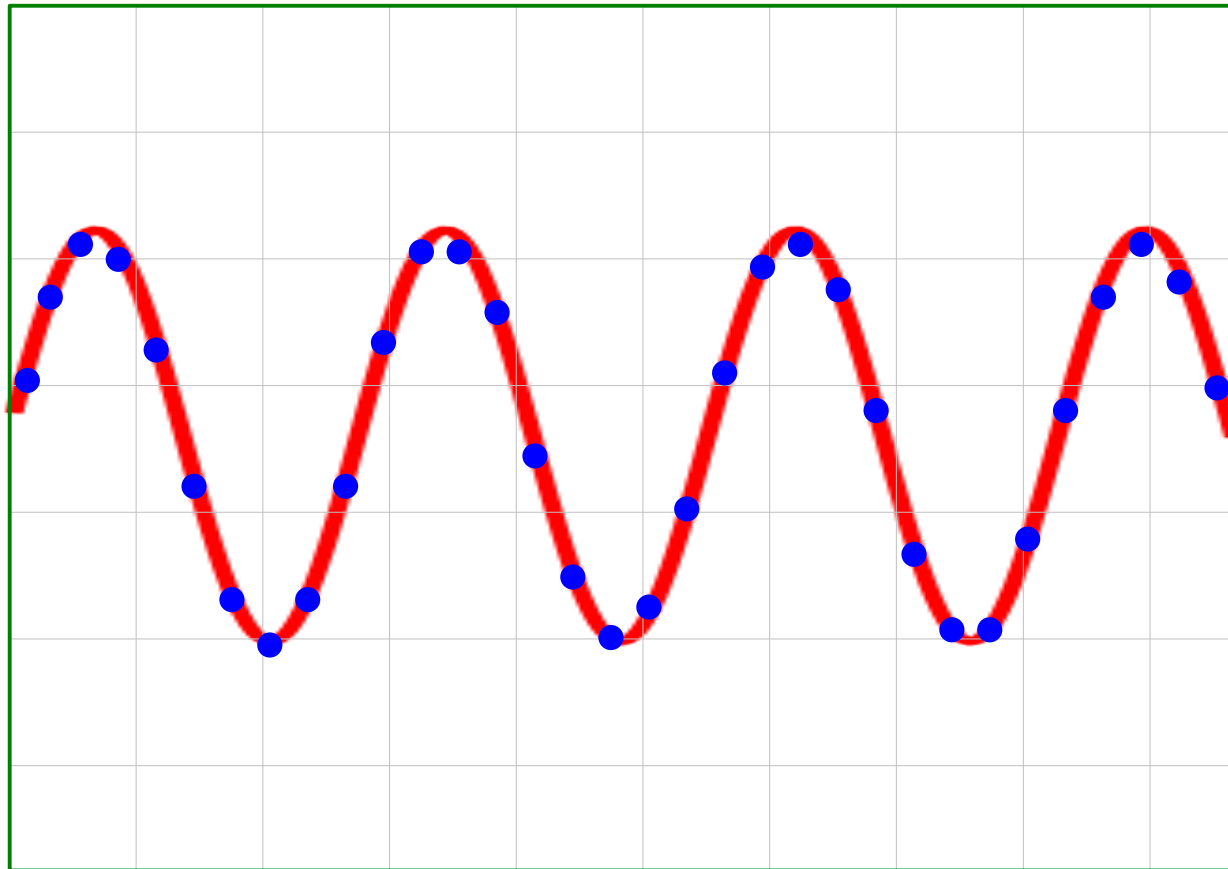


SAMPLING BANDWIDTH

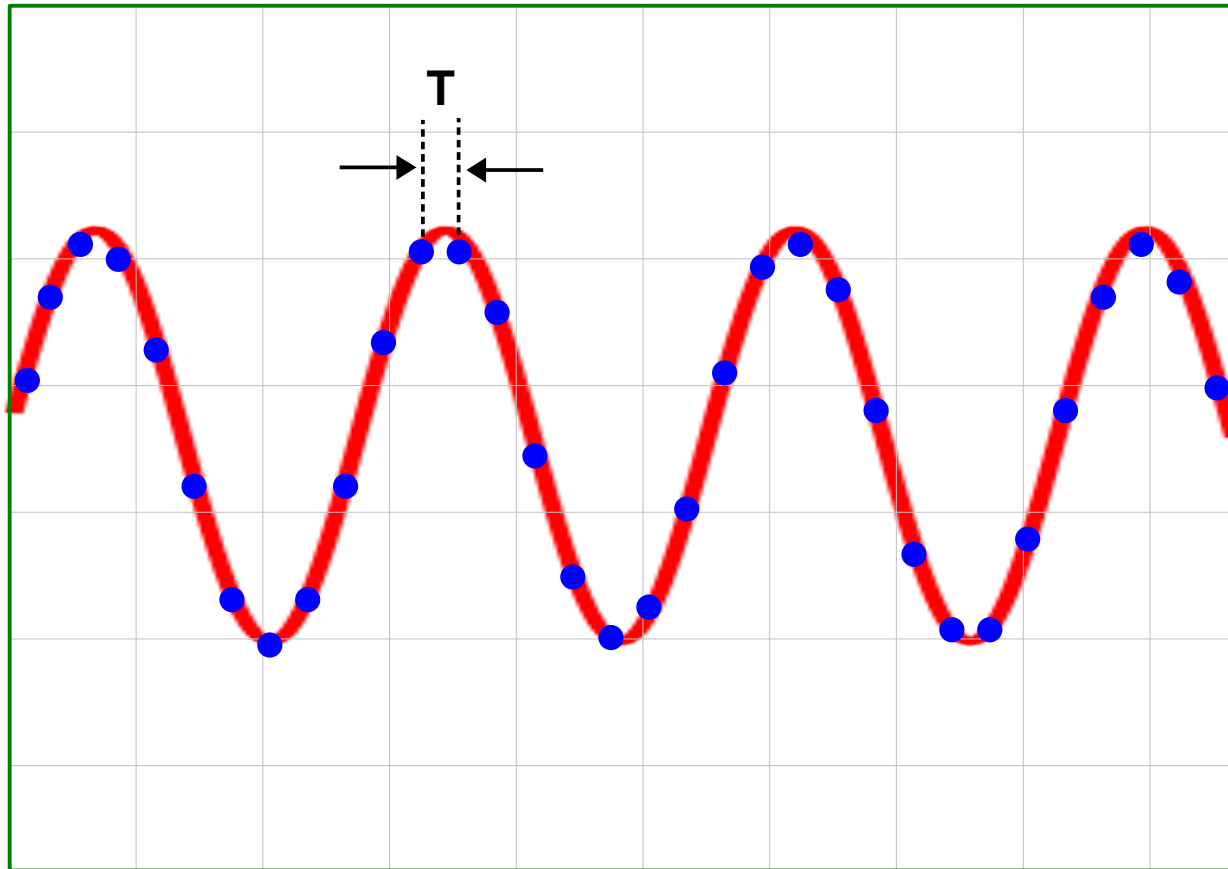

Sample spacing: T (sec)

Sampling bandwidth = $1 / T$ (samples/sec)


SAMPLING BANDWIDTH

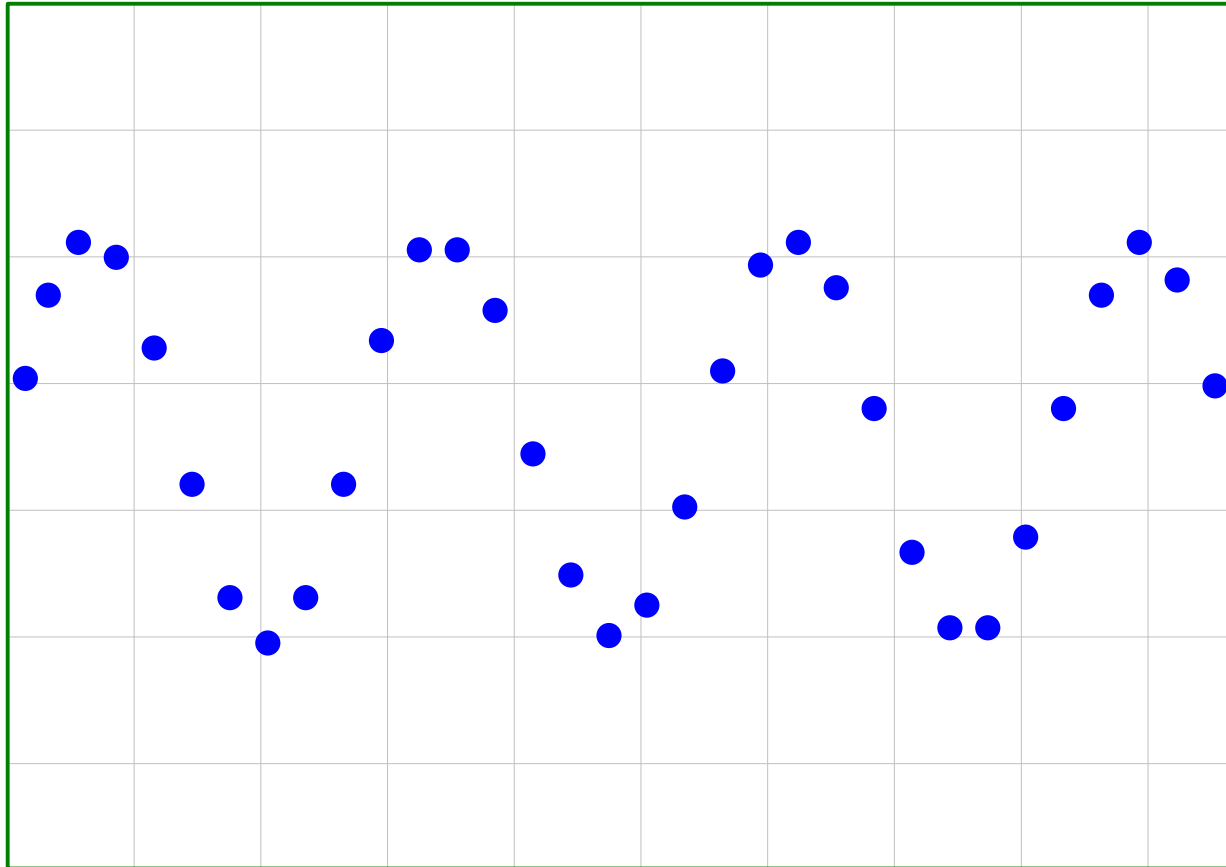

Sample spacing: T (sec)


Sampling bandwidth = $1 / T$ (samples/sec)

SAMPLING BANDWIDTH

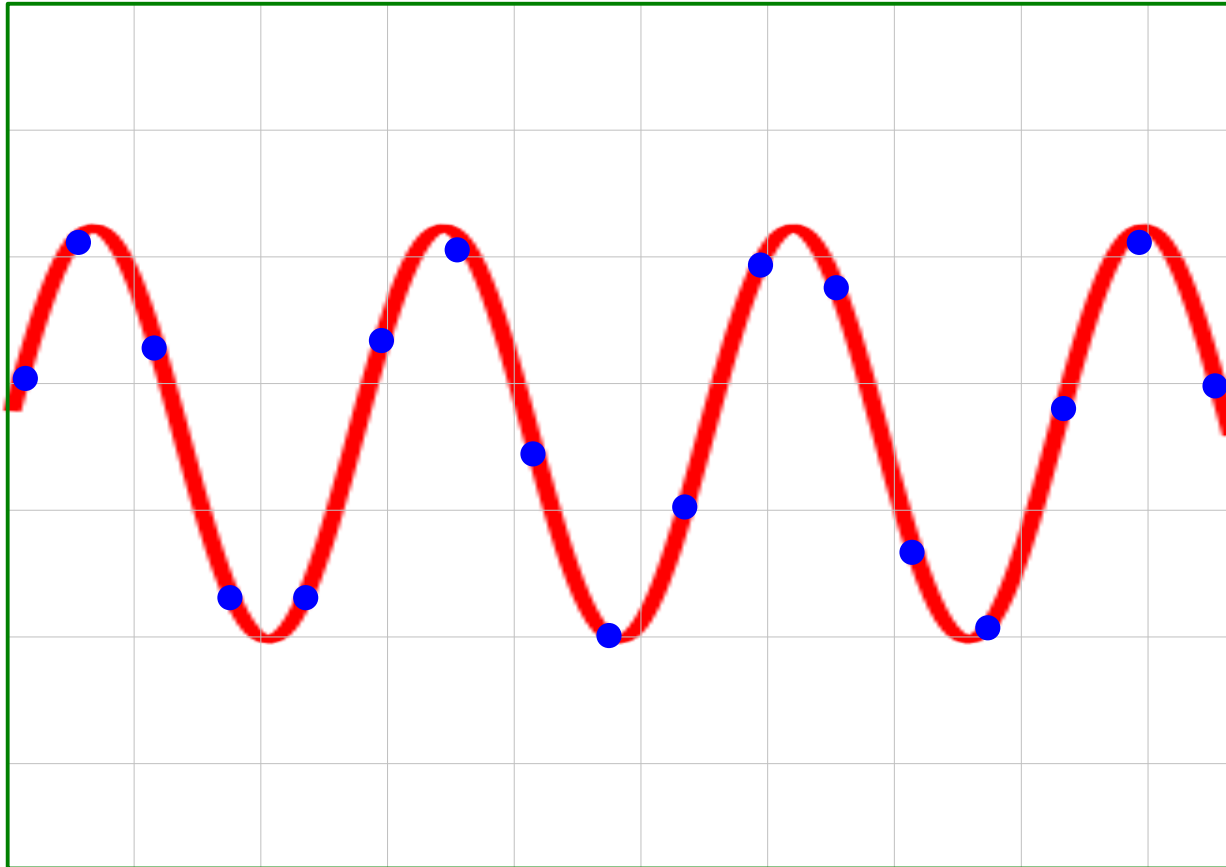

Reduce sample bandwidth $2x$ \Rightarrow Increase period $2x$

SAMPLING BANDWIDTH

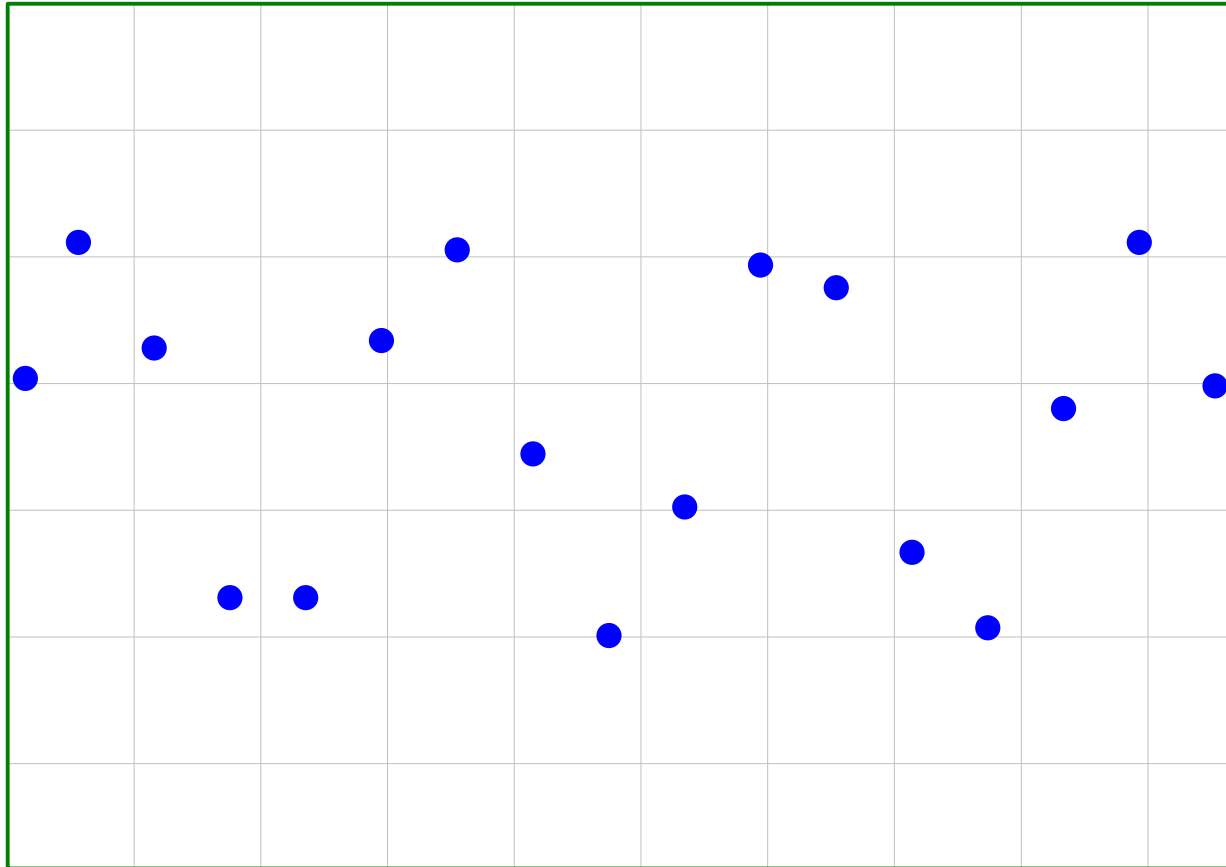

Reduce sample bandwidth 2x \Rightarrow Increase period 2x