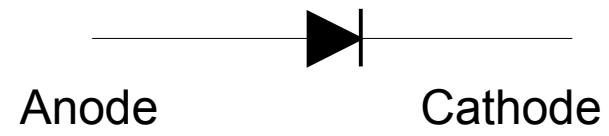



# Lab 6: Diodes

# Ideal Diode


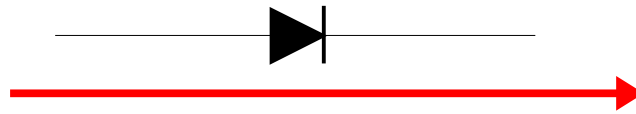
# Ideal Diode


$$V_{\text{Anode}} > V_{\text{Cathode}}$$



**Current flows without resistance**
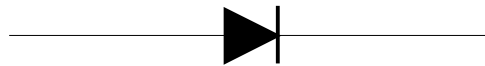
# Ideal Diode


$$V_{\text{anode}} < V_{\text{Cathode}}$$



**No current flow**

Current only flows in one direction

# Vacuum tube diode

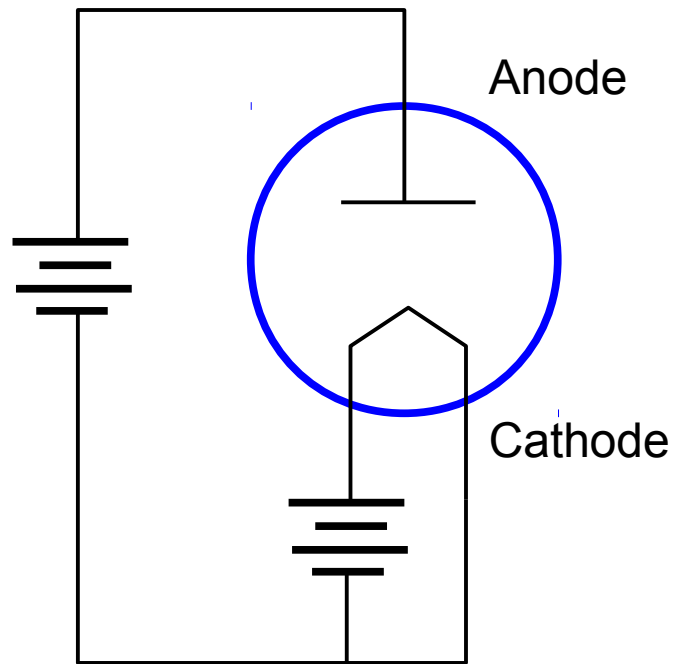


Fleming valve (1904)




J.A. Fleming


# Vacuum tube diode

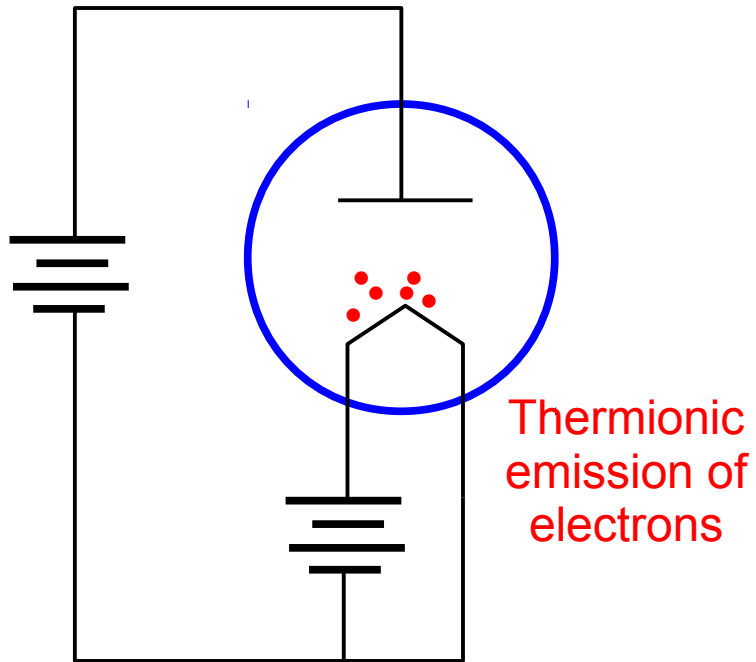

# Vacuum tube diode

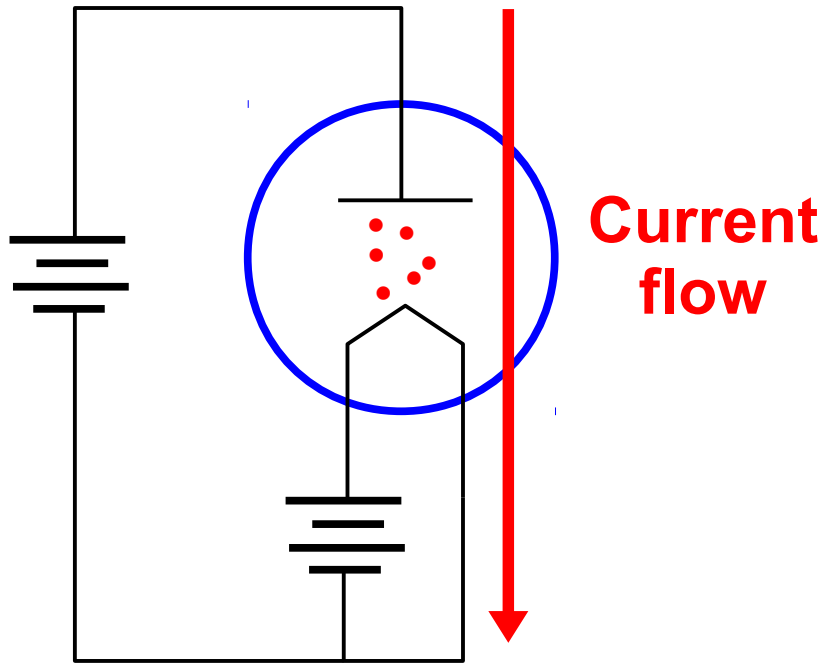


# Vacuum tube diode

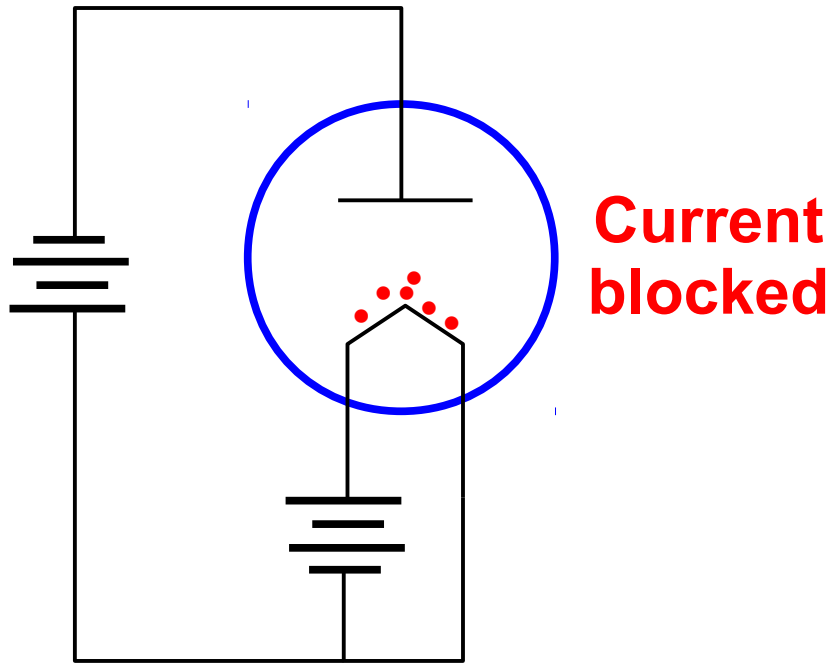




# Semiconductor p-n junction


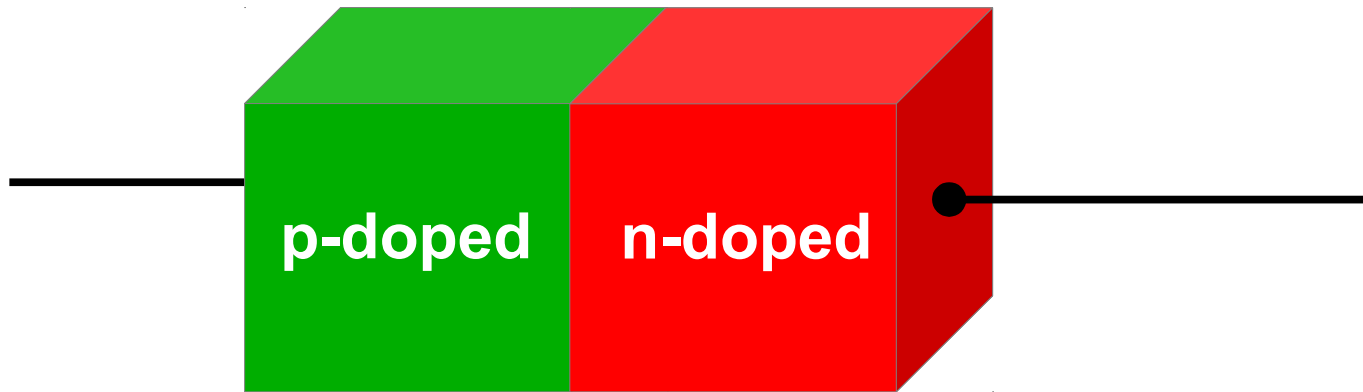


Russel Ohl (1939)

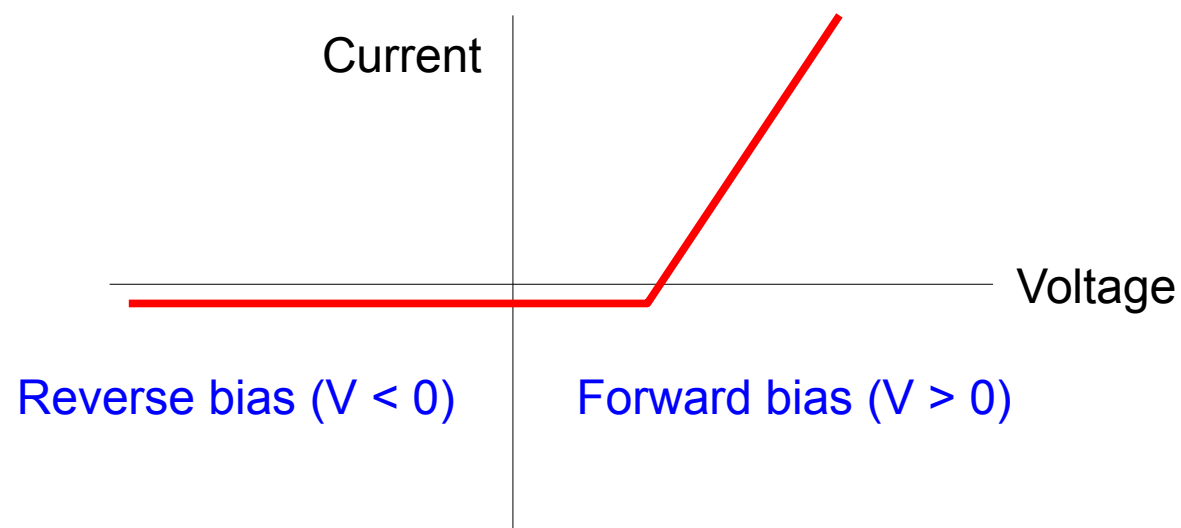
Voltage controlled alignment  
of quantum mechanical energy levels




# Semiconductor p-n junction

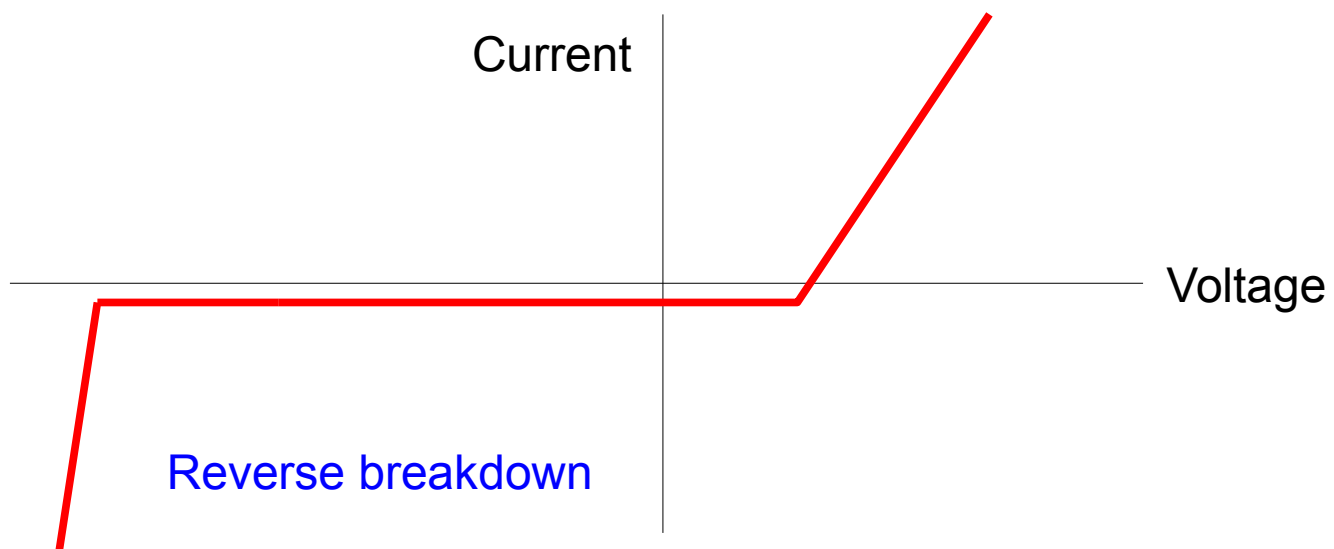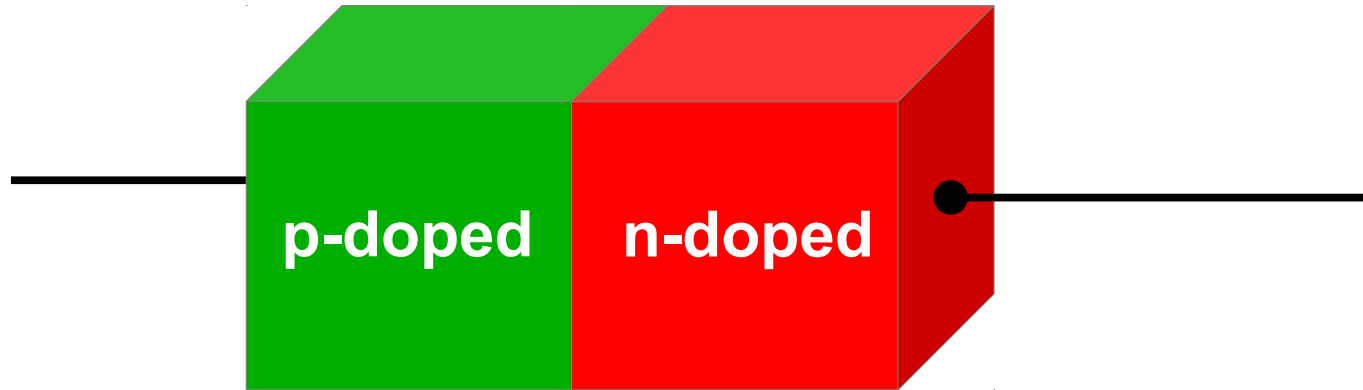


# RECTIFICATION: Half-wave rectifier

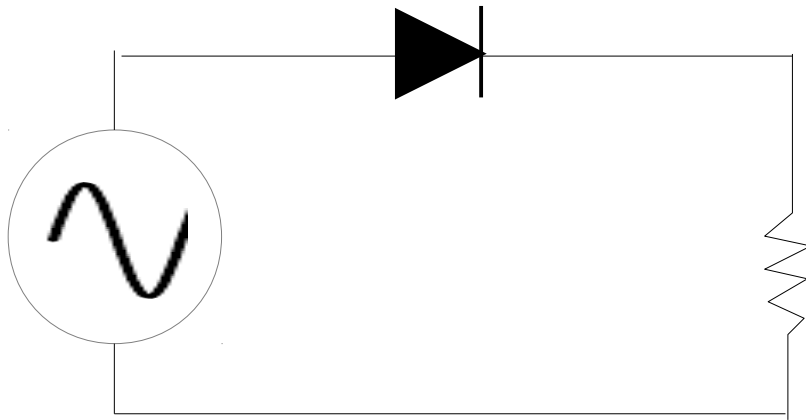


# RECTIFICATION: Half-wave rectifier

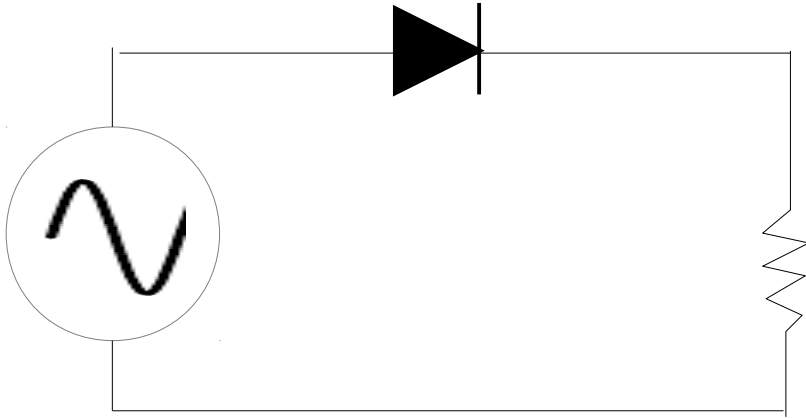


Input current

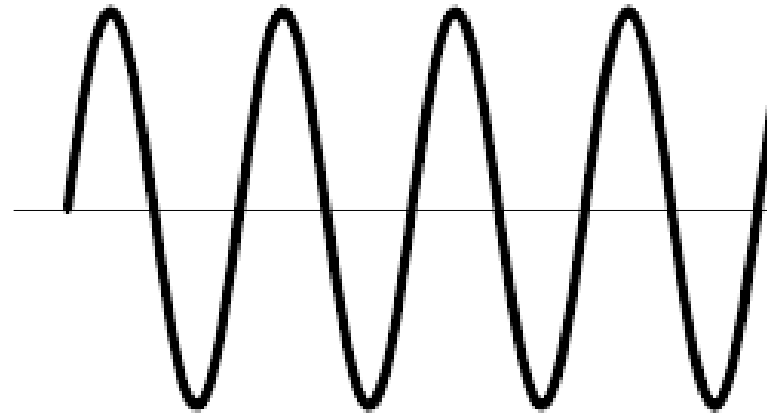


Resistor (output) current

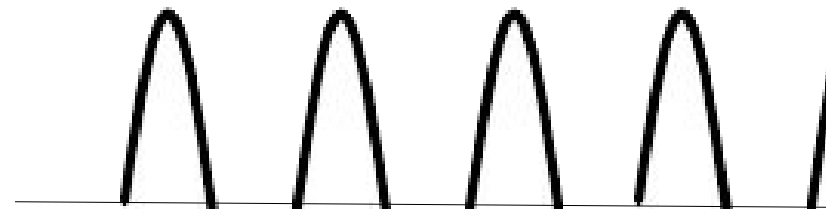


# RECTIFICATION: Bridge rectifier

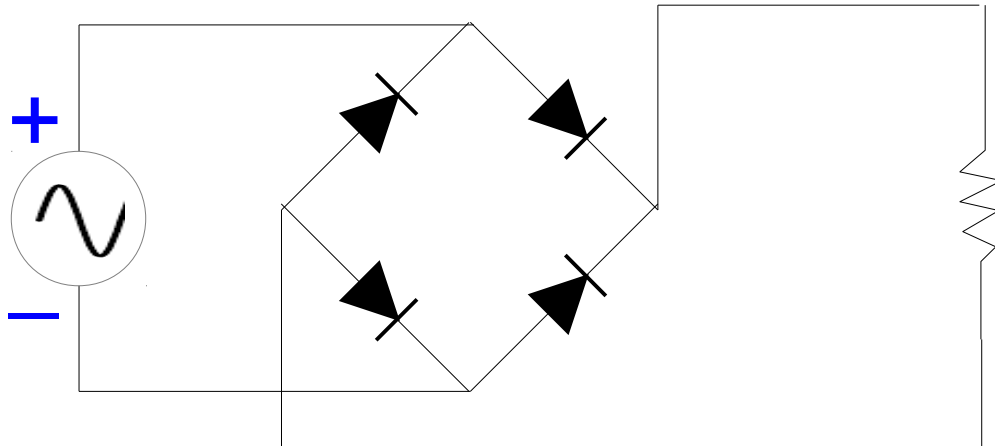


# RECTIFICATION: Bridge rectifier

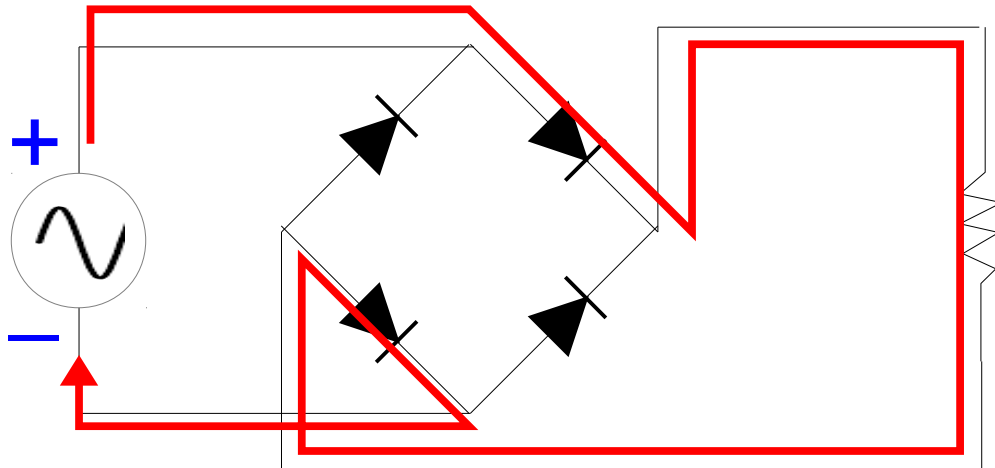

# RECTIFICATION: Bridge rectifier

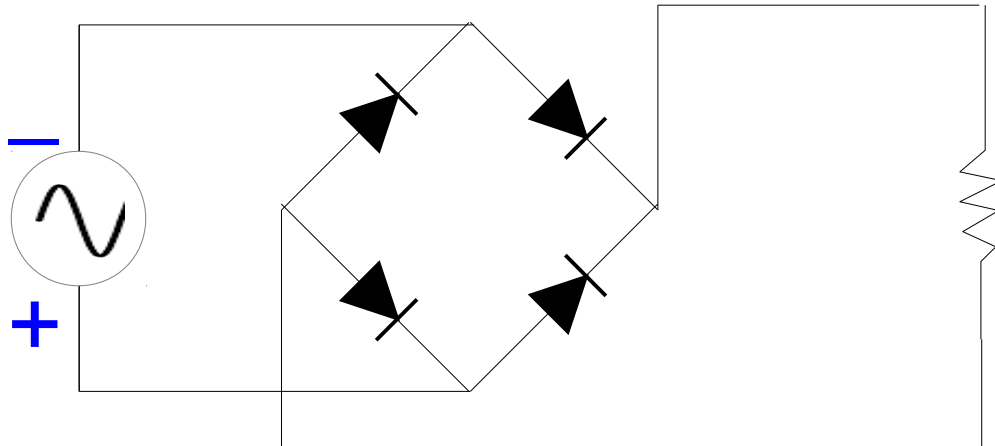


# RECTIFICATION: Bridge rectifier

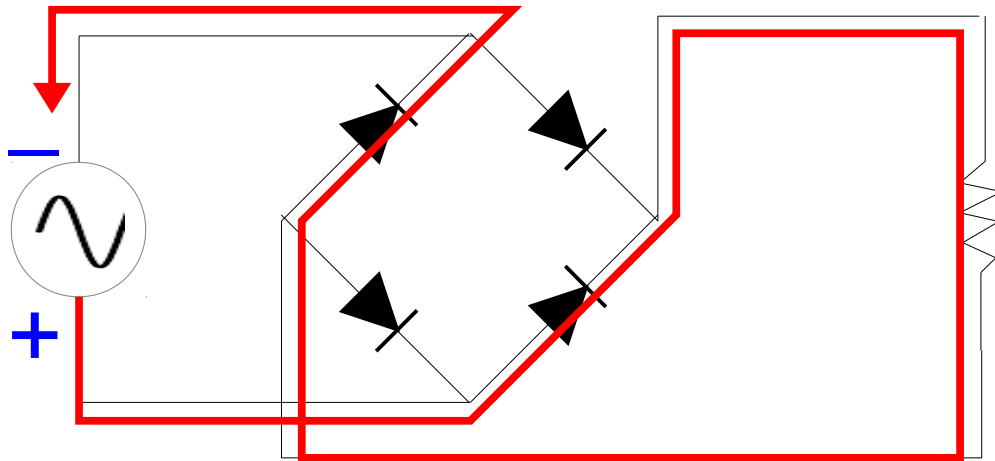





# RECTIFICATION: Bridge rectifier

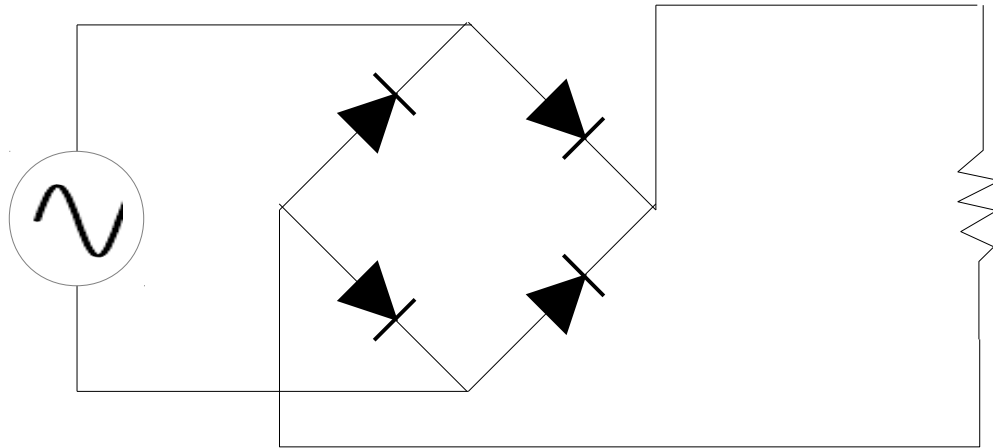


Input current

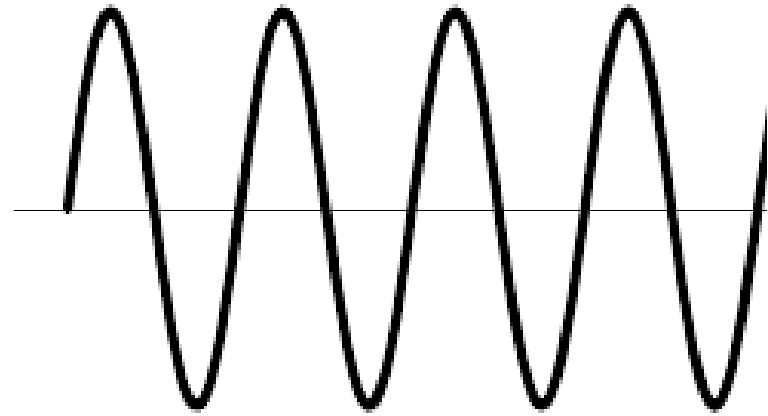


Resistor (output) current

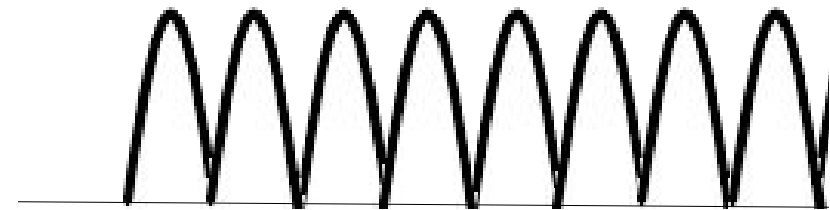

# FILTERED RECTIFICATION

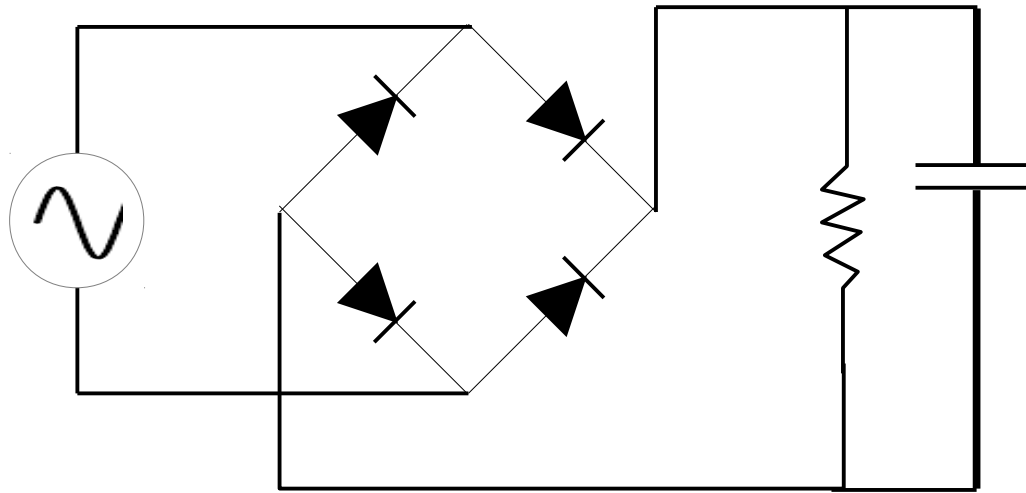

Input current

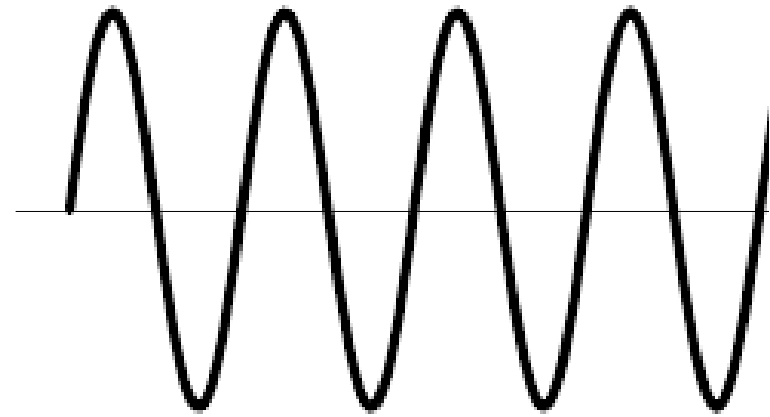

Resistor (output) current

VOLTAGE RIPPLE

