

# Lecture 7: Transistors

Largely replaced the vacuum tube

Heart of modern electronics

Three-terminal semiconductor device

Amplification and switching

Two basic forms (BJT and FET)

John Bardeen


William Shockley


Walter Brattain




**1956 Nobel Prize in Physics**

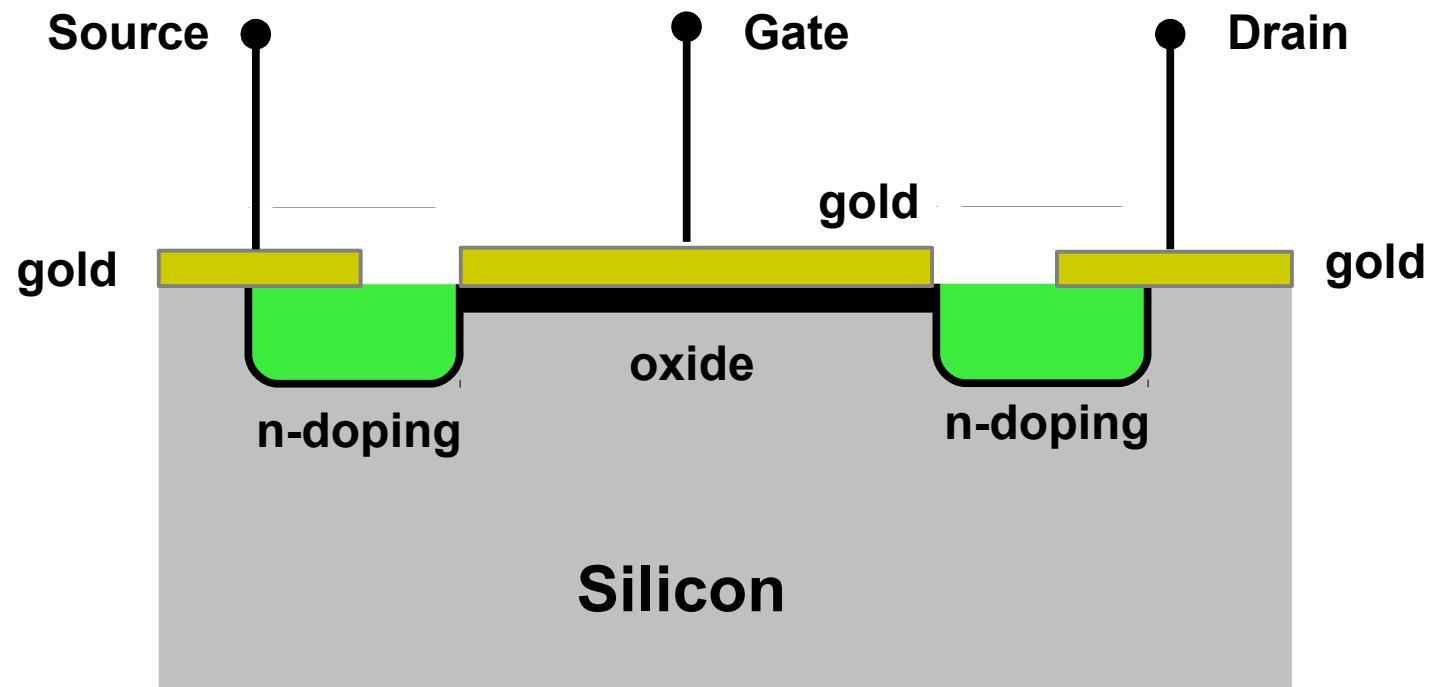
# MOSFET: Metal-Oxide-Semiconductor Field-Effect Transistor



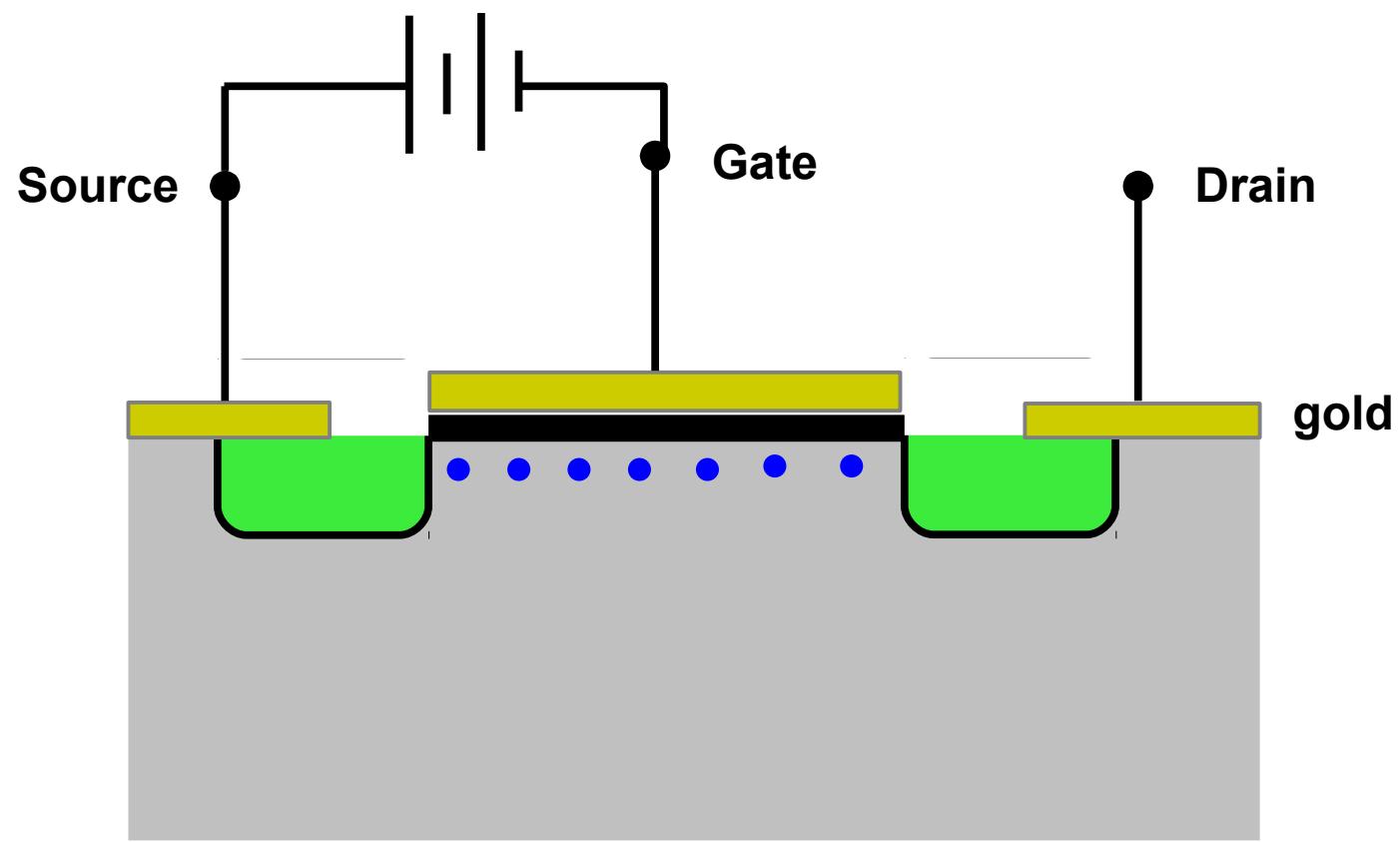


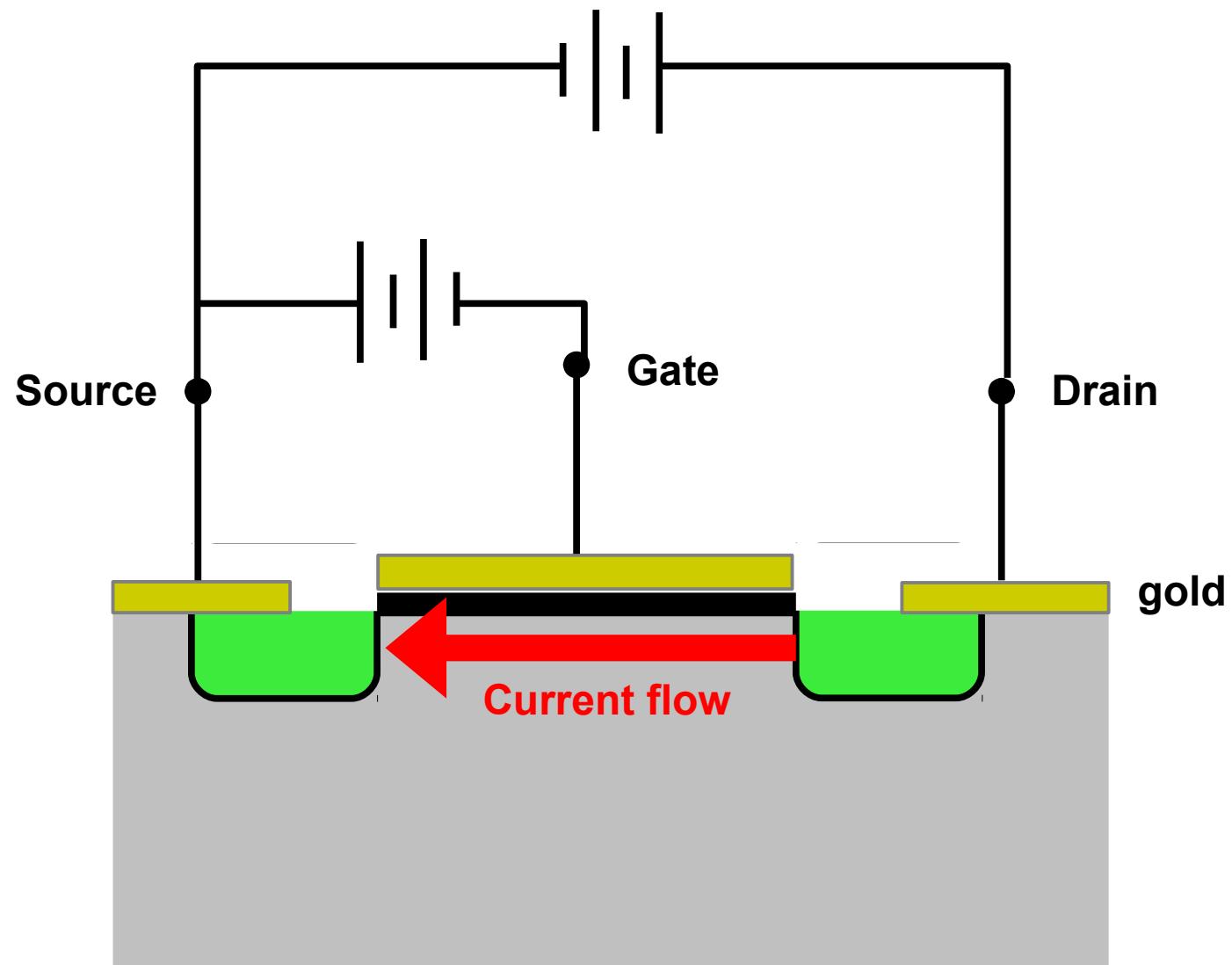


# BJT: Bipolar Junction Transistor

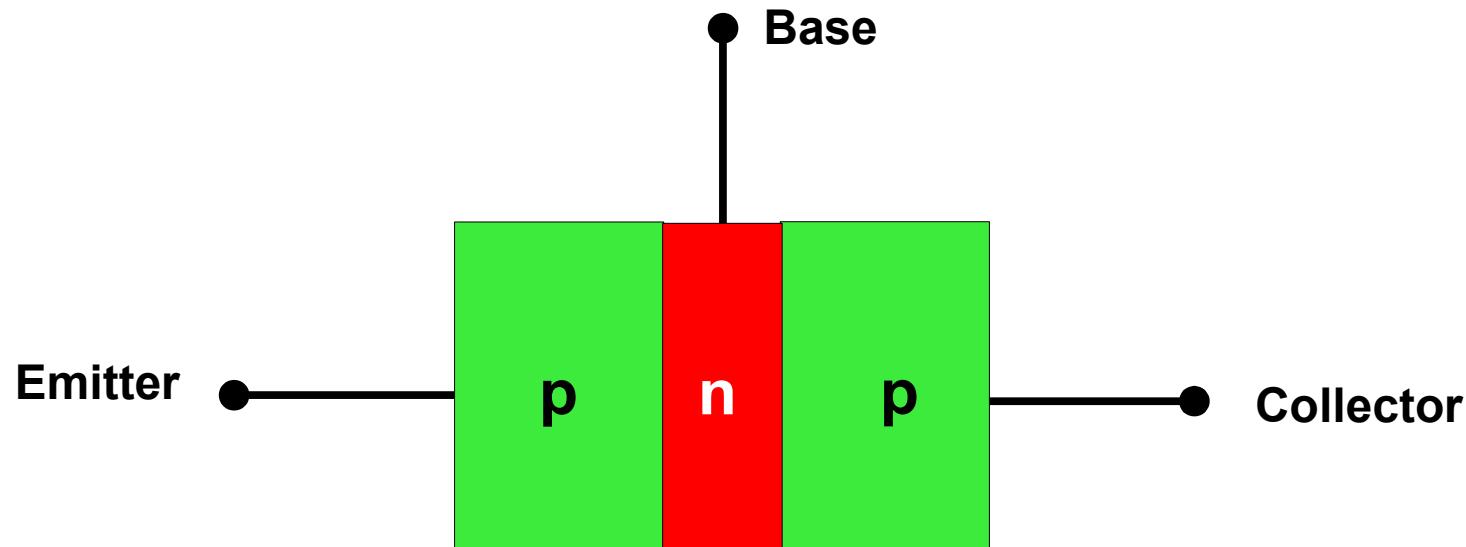





# BJT: Bipolar Junction Transistor

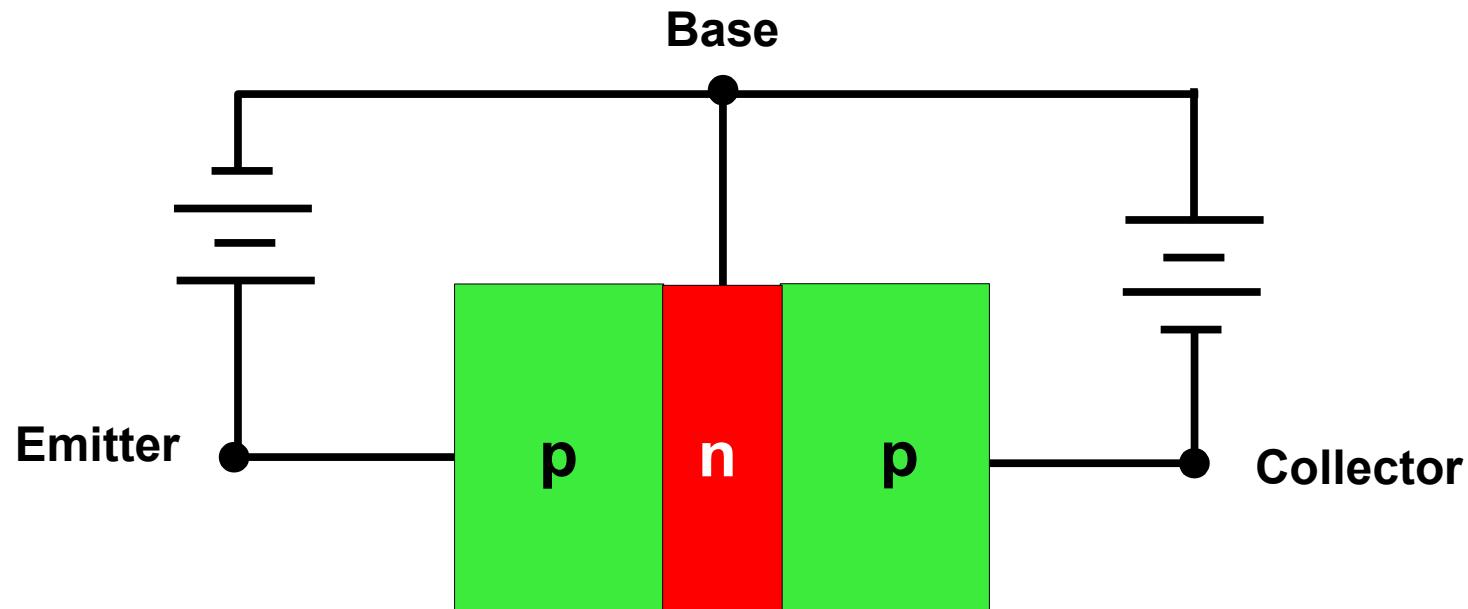

# BJT: Bipolar Junction Transistor


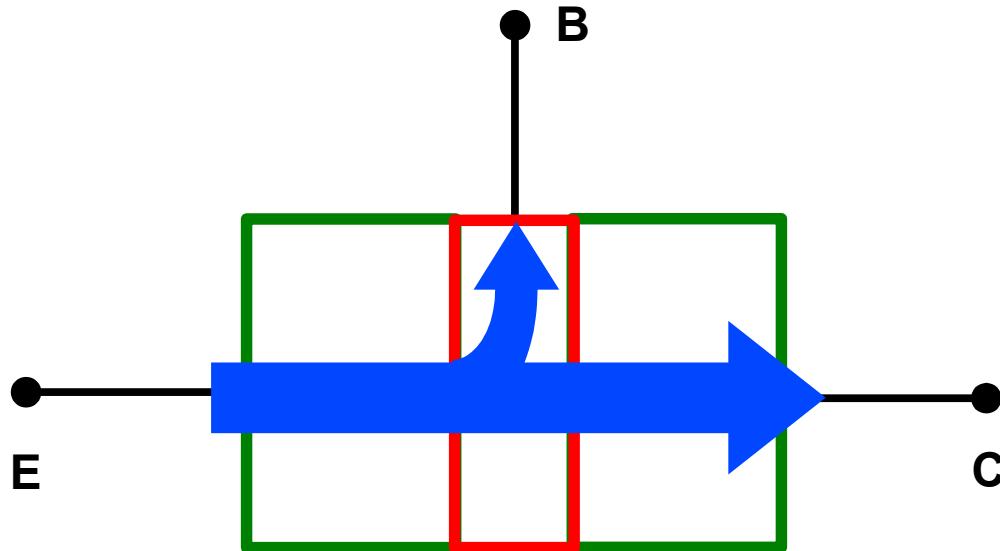


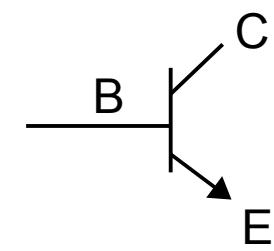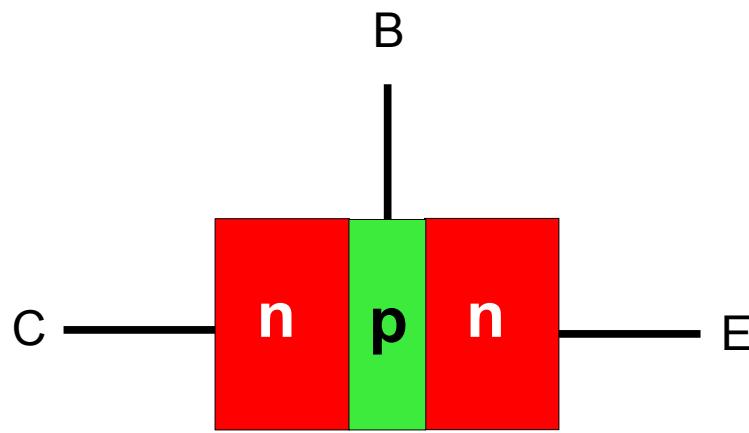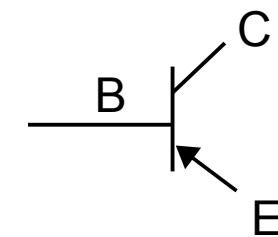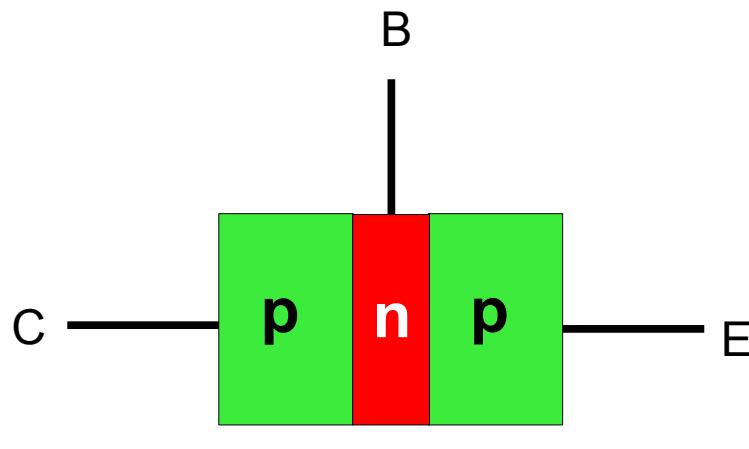**Small base current controls  
much larger collector current**





# Getting the dc voltages correct: **BIAS**

n-p-n transistor

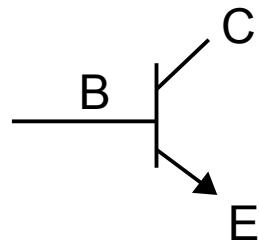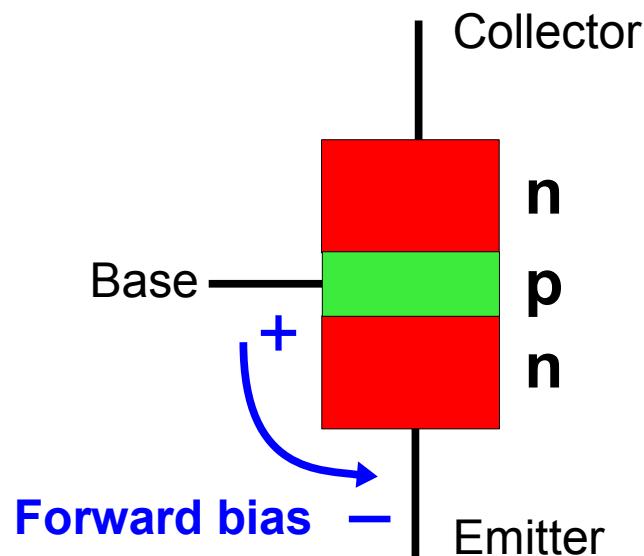




# Getting the dc voltages correct: **BIAS**

n-p-n transistor

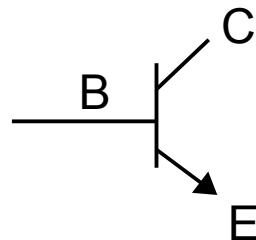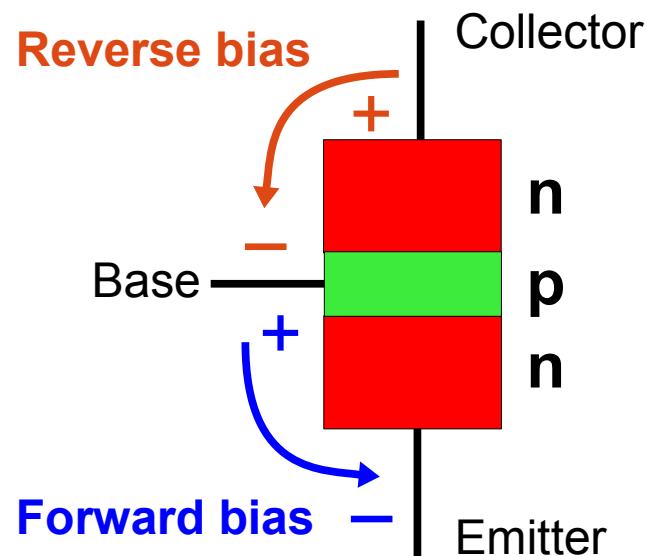


# Getting the dc voltages correct: BIAS


n-p-n transistor

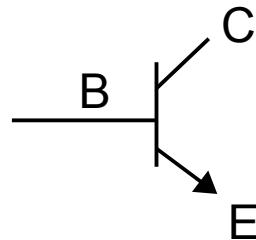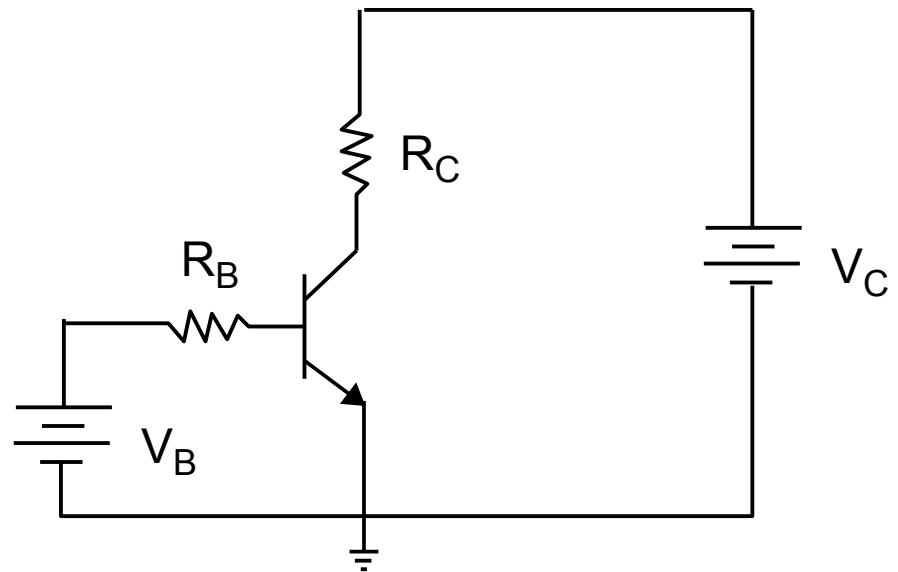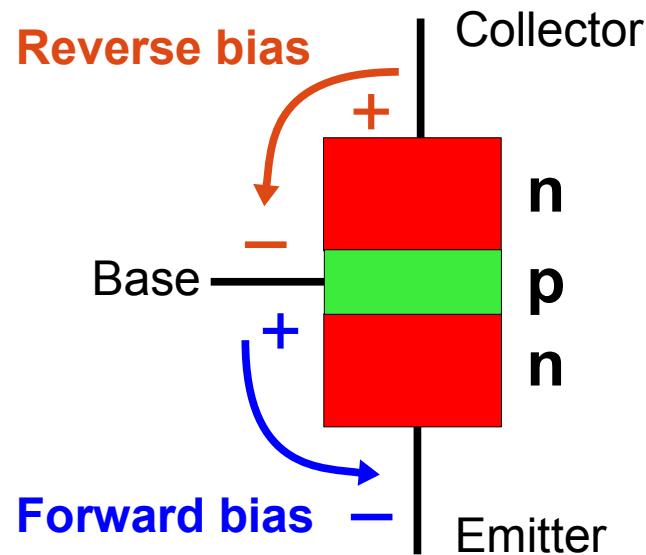

# The BJT Amplifier

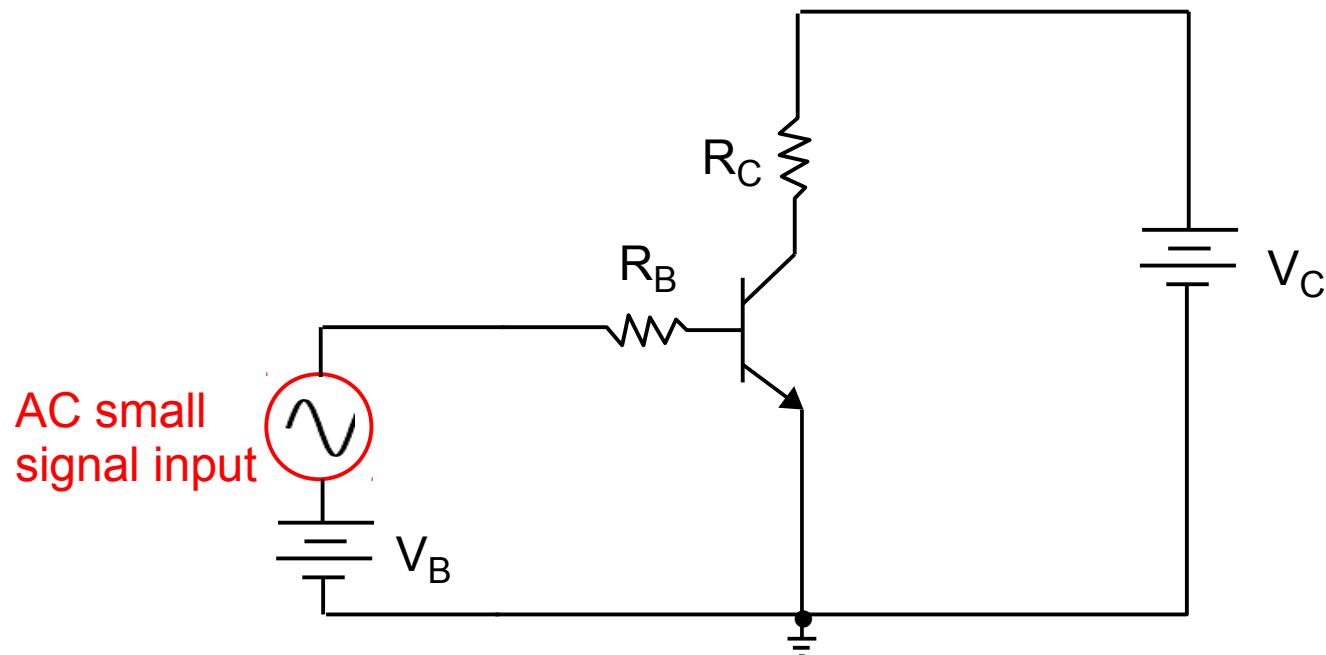


# The BJT Amplifier

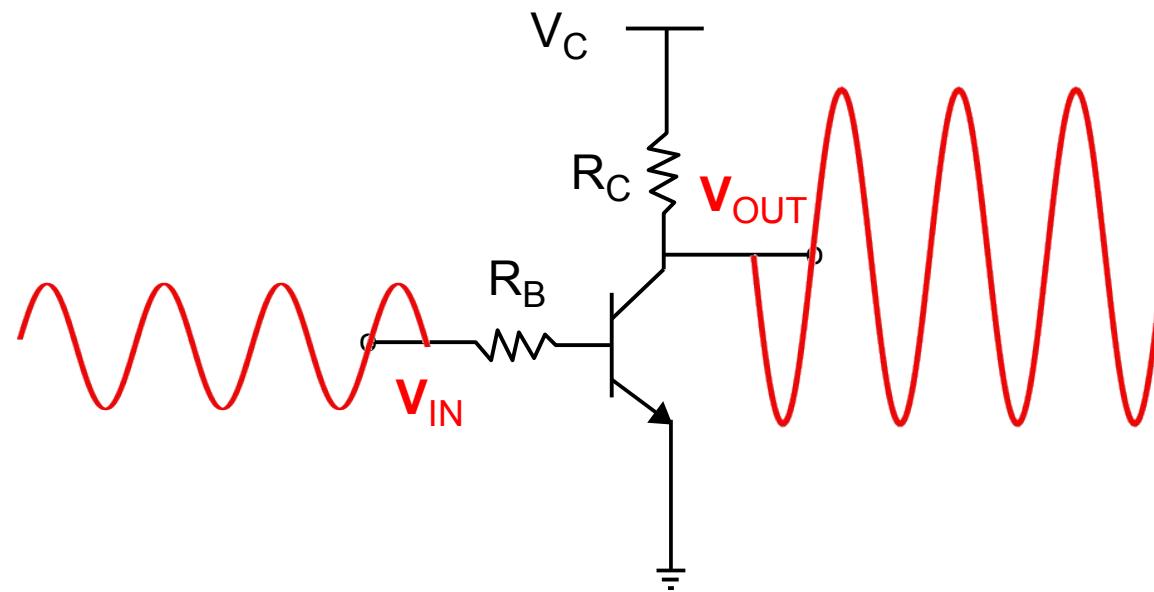


$$\frac{v_{OUT}}{v_{IN}} = \text{Gain}$$
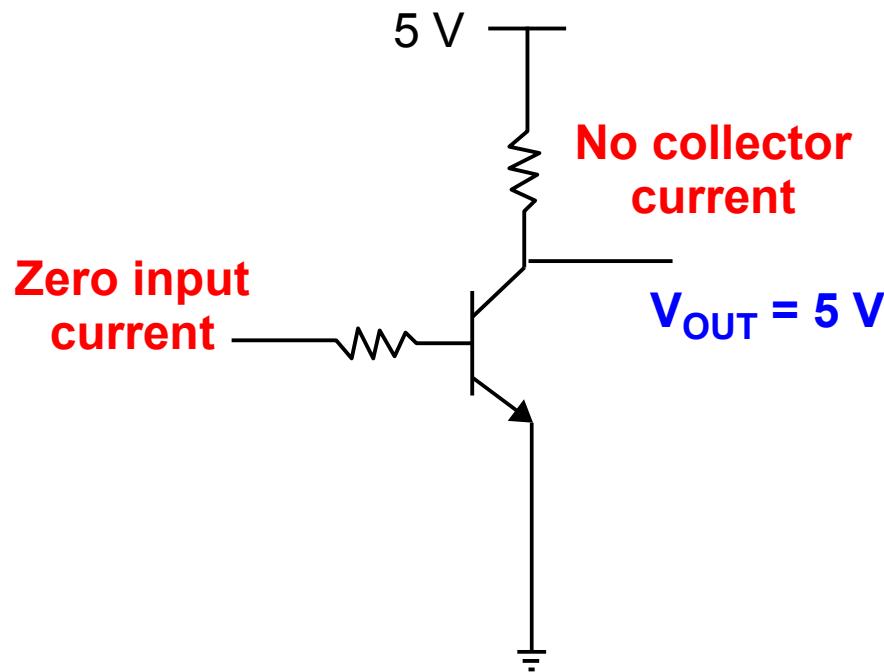
# The Transistor as a Switch

- No base bias voltage
- Input current turns transistor on and off




Transistor OFF

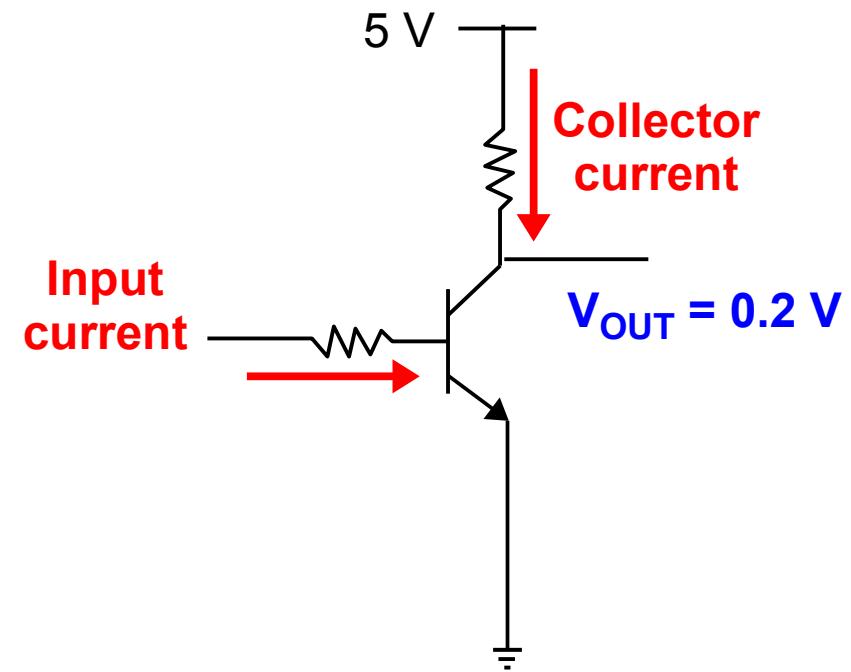

Transistor ON

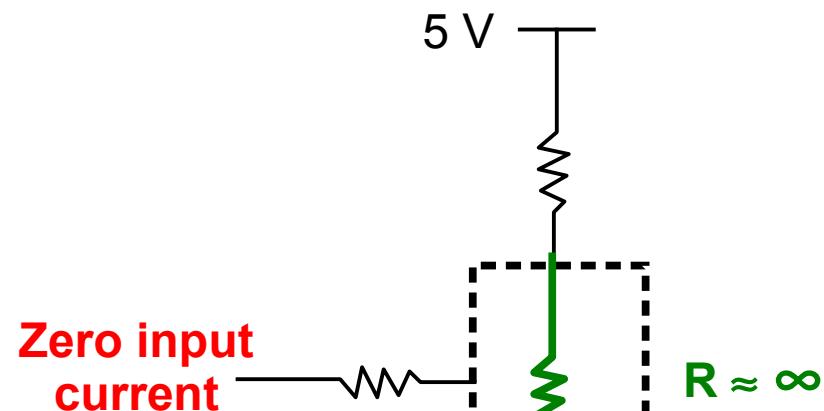
# Intuitive picture of the transistor switch: Current-controlled resistor



Zero input  
current

$R \approx \infty$

Transistor OFF

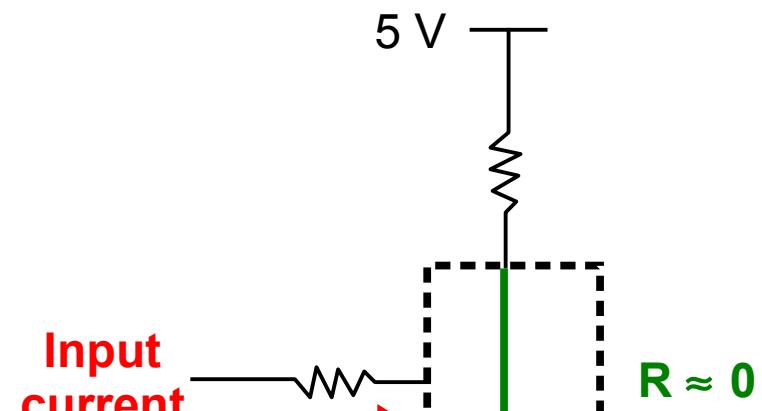


Input  
current

$R \approx 0$

Transistor ON


# The Transistor Switch: Boolean Logic Device

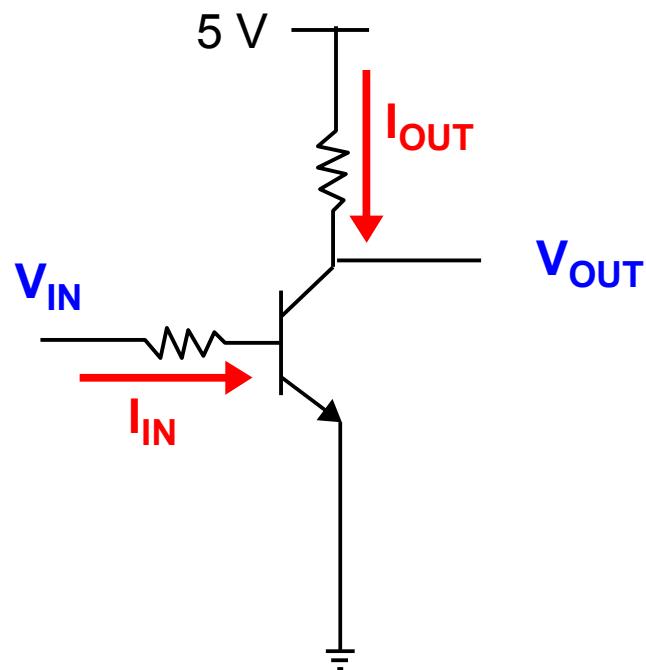

**LOGIC 0:** VOLTAGE  $< 0.4 \text{ V}$   
**LOGIC 1:** VOLTAGE  $> 3 \text{ V}$



$V_{IN}$	$I_{IN}$	$I_{OUT}$	$V_{OUT}$
Logic 0	0	0	Logic 1
Logic 1	$\mu\text{A}$	$\text{mA}$	Logic 0

**NOT Gate**

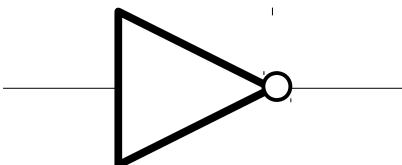



# The Transistor AND Gate

$V_1$	$V_2$	$V_{OUT}$
0	0	0
1	0	0
0	1	0
1	1	1

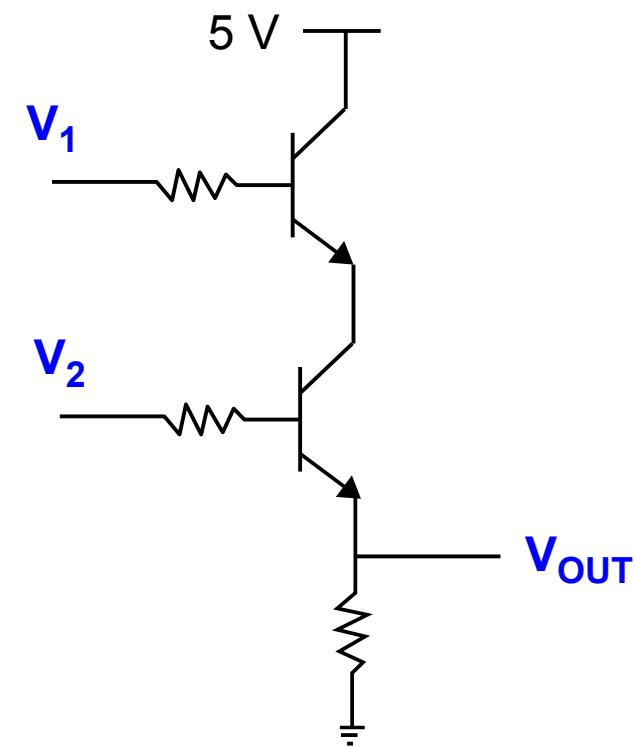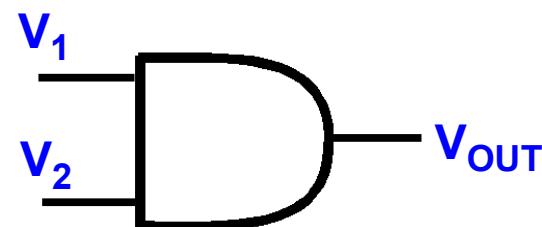


# The Transistor OR Gate

$V_1$	$V_2$	$V_{OUT}$
0	0	0
1	0	1
0	1	1
1	1	1

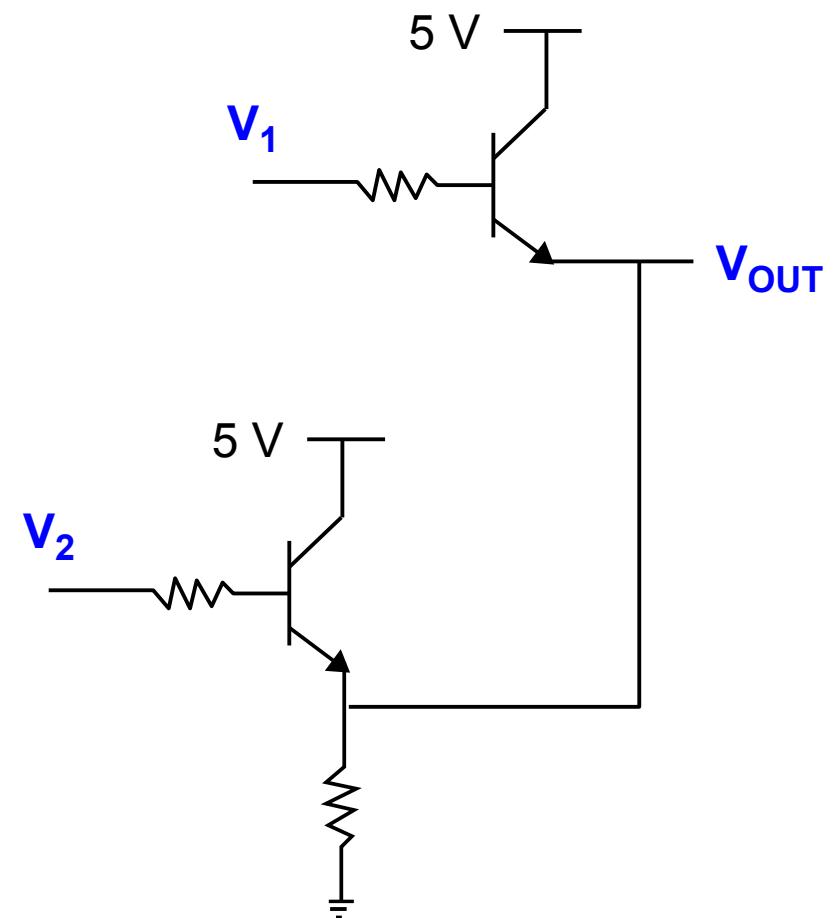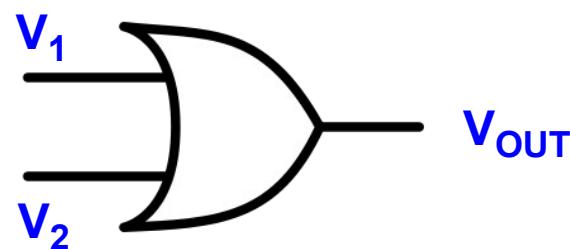


# The NOR Gate


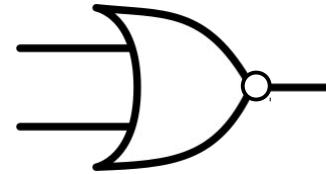


$V_1$	$V_2$	$V_{OUT}$
0	0	1
1	0	0
0	1	0
1	1	0


# The NOR Gate

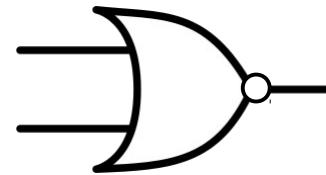


$V_1$	$V_2$	$V_{OUT}$
0	0	1
1	0	0
0	1	0
1	1	0

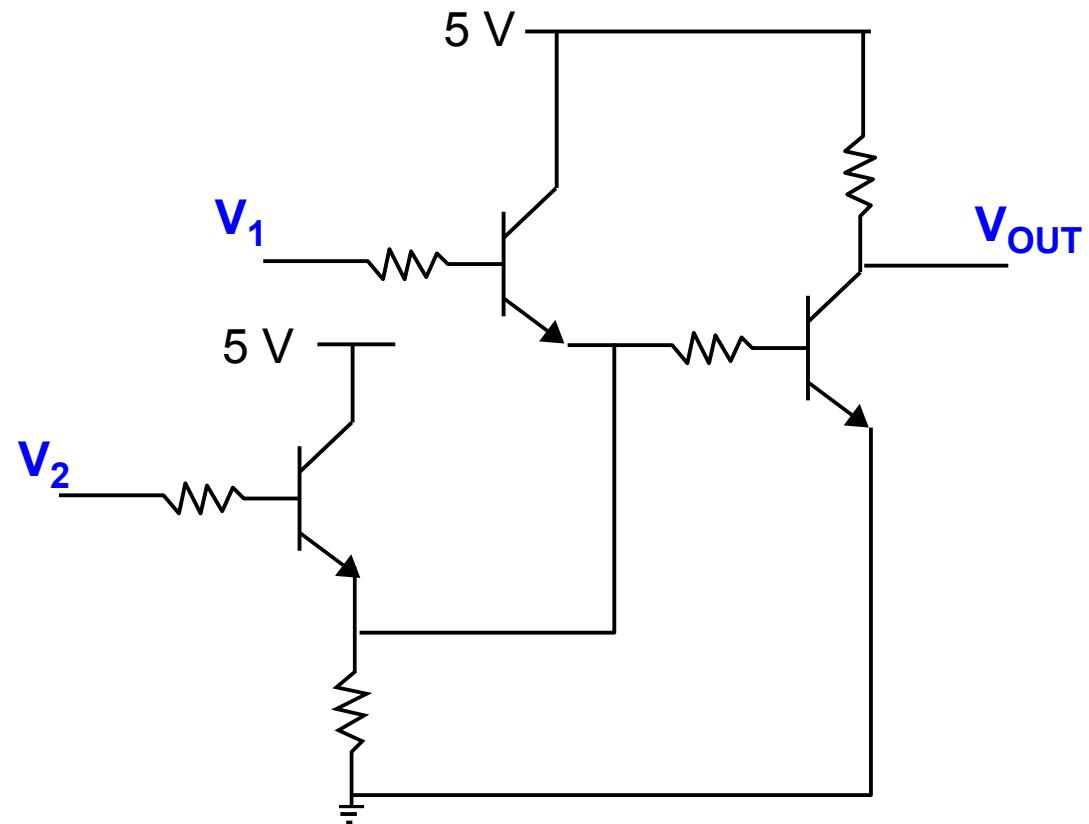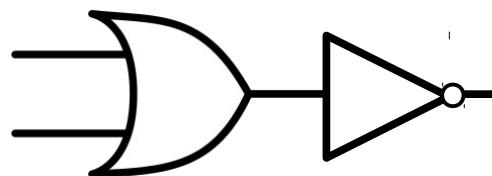


# The NOR Gate

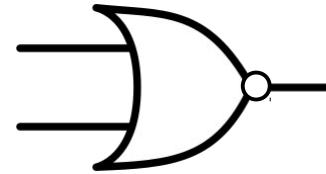

$V_1$	$V_2$	$V_{OUT}$
0	0	1
1	0	0
0	1	0
1	1	0

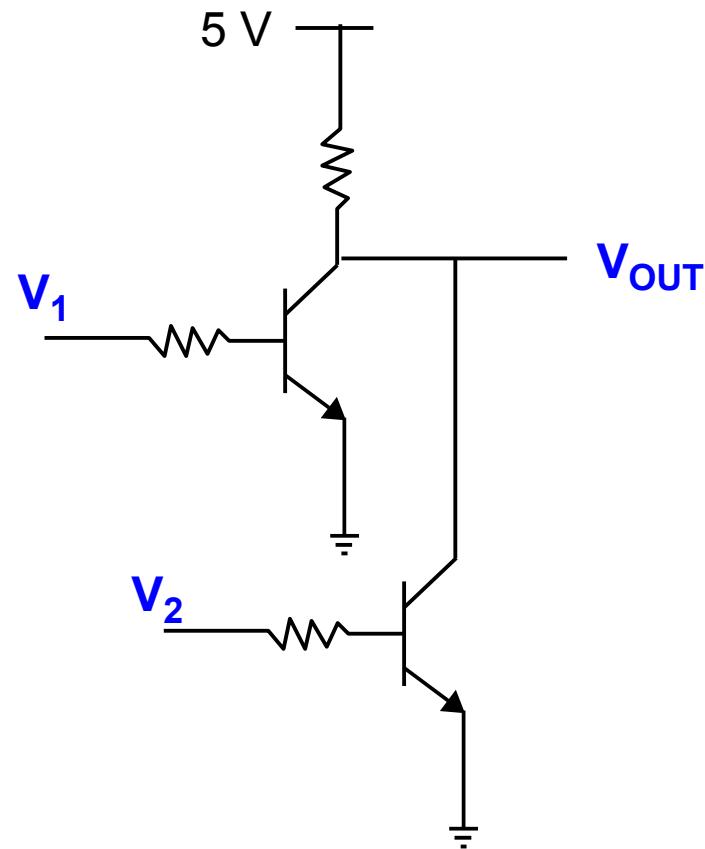

# The NOR Gate

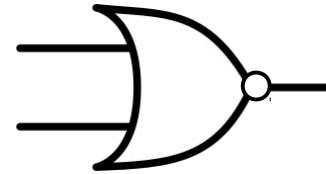

$V_1$	$V_2$	$V_{OUT}$
0	0	1
1	0	0
0	1	0
1	1	0

