


Lab 9: Active Filter Circuits

Active Filters

Frequency-dependent
transfer function $G(\omega) = V_{OUT}/V_{IN}$

Active: Supply current to
transistors, op-amps

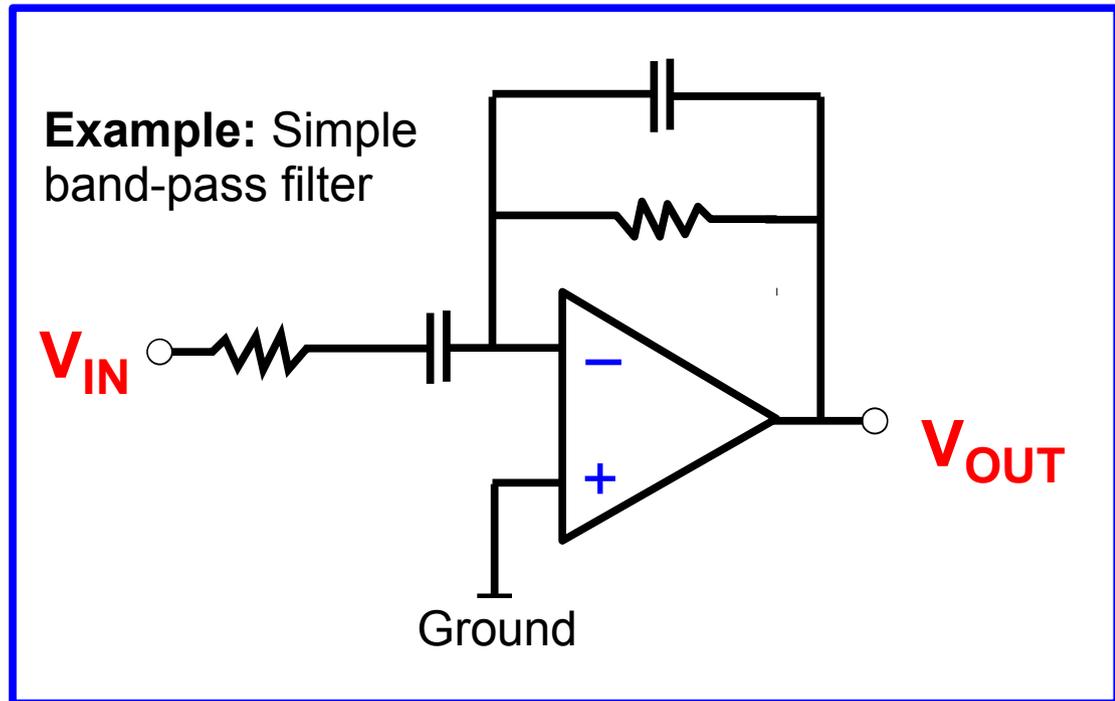Passive: Only resistors, capacitors,
inductors, diodes, etc (earlier labs)



Advantages of active filtering over passive filtering


- * Compensate for filter loss with amplification
- * Performance nearly immune from influence of input/output circuits
- * Don't need bulky, expensive inductors

Disadvantages

- * Consumes power
- * Can introduce electrical noise

Review of ideal Op-Amp

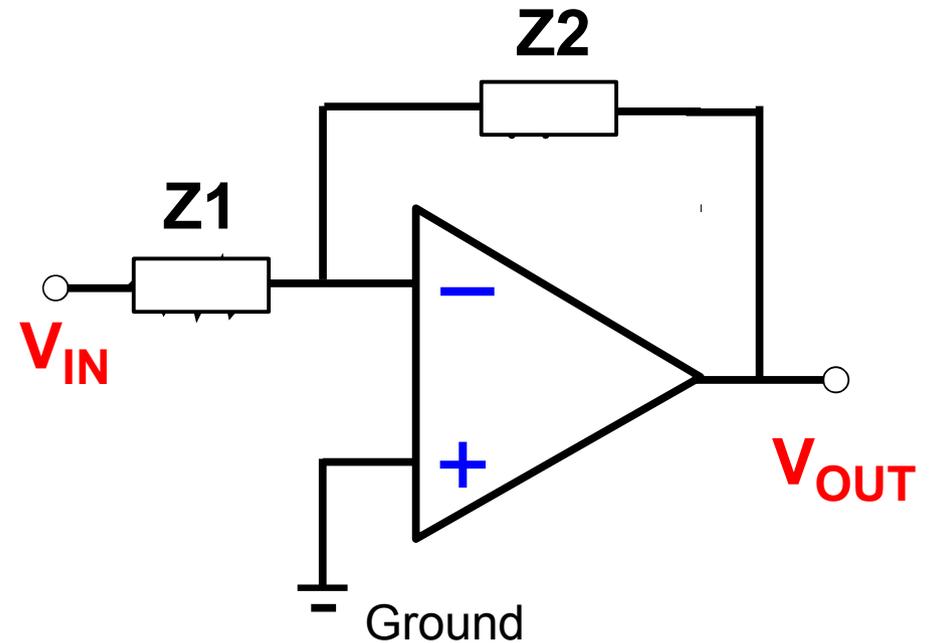
Very high input impedance
Negligible current flows into device
Inverting input (–)
Non-inverting input (+)
Extremely high amplification
Clever use of feedback



Inverting amplifier

$$\frac{V_{OUT}}{V_{IN}} = -\frac{Z2}{Z1}$$

Poles and Zeroes

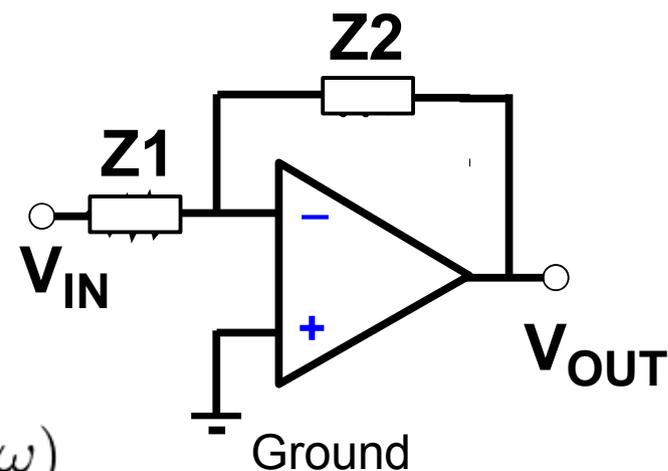

$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = -\frac{Z_2(\omega)}{Z_1(\omega)} = G(\omega) = \frac{N(\omega)}{D(\omega)}$$

Numerator: $N(\omega) = (\omega_{N1} + j\omega)(\omega_{N2} + j\omega) \times \dots (\omega_{Nm} + j\omega)$


Denominator: $D(\omega) = (\omega_{D1} + j\omega)(\omega_{D2} + j\omega) \times \dots (\omega_{Dm'} + j\omega)$

$$m \leq m'$$

Zeroes: Frequencies (ω_N) that make the numerator zero


Poles: Frequencies (ω_D) that make the denominator zero

Example: Low-pass filter

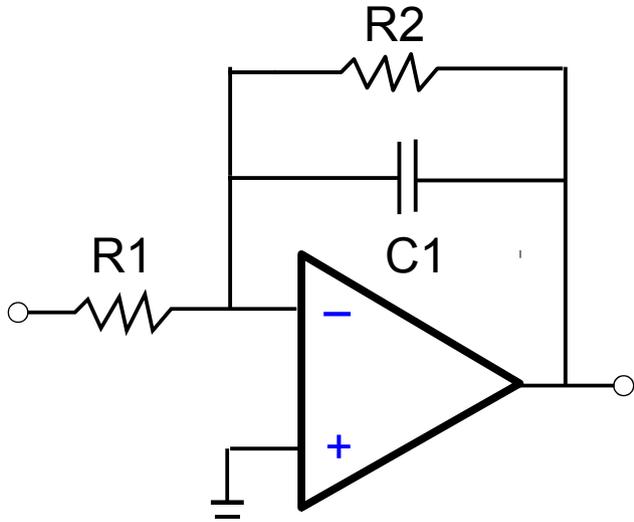


$$\frac{V_{OUT}}{V_{IN}} = -\frac{R2}{R1} \left(\frac{1}{1 + j\omega R2 C1} \right)$$


Pole in denominator

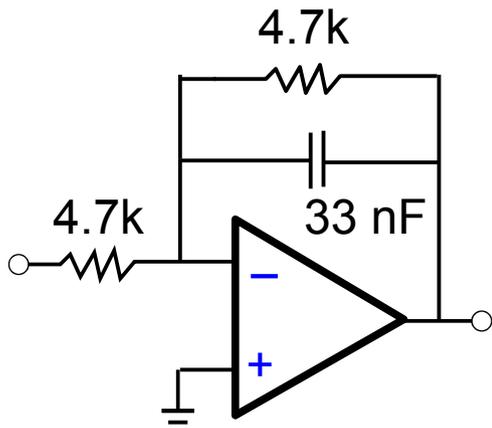

1-pole: 1 kHz


Pole at 1 kHz: -20 dB/decade

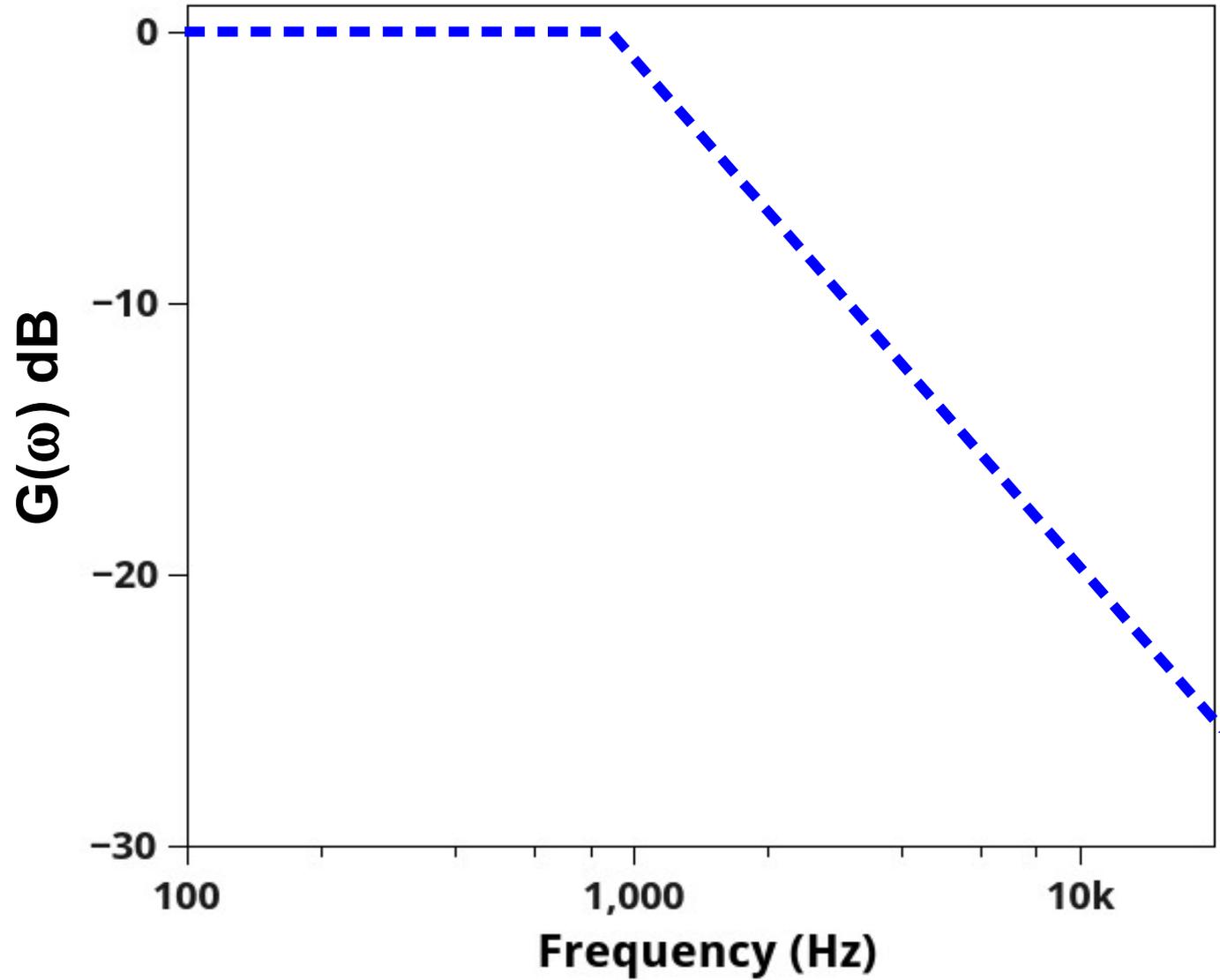

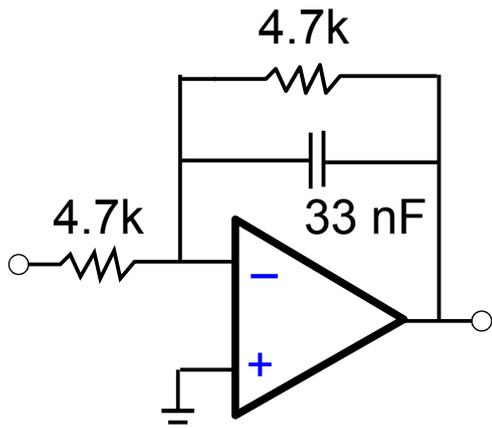


1-pole: 1 kHz


Red curve: Full-model calculation

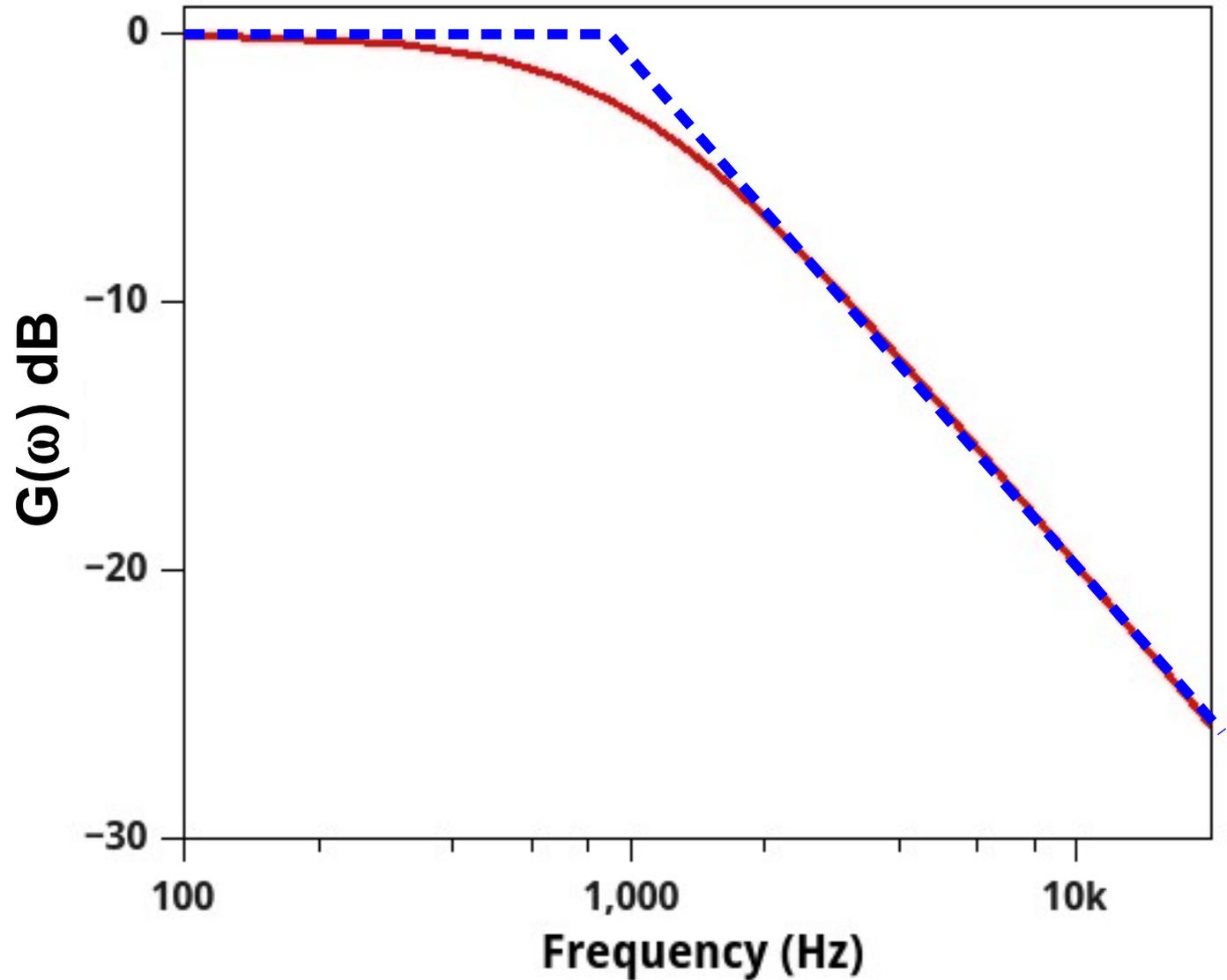


Example: Low-pass filter

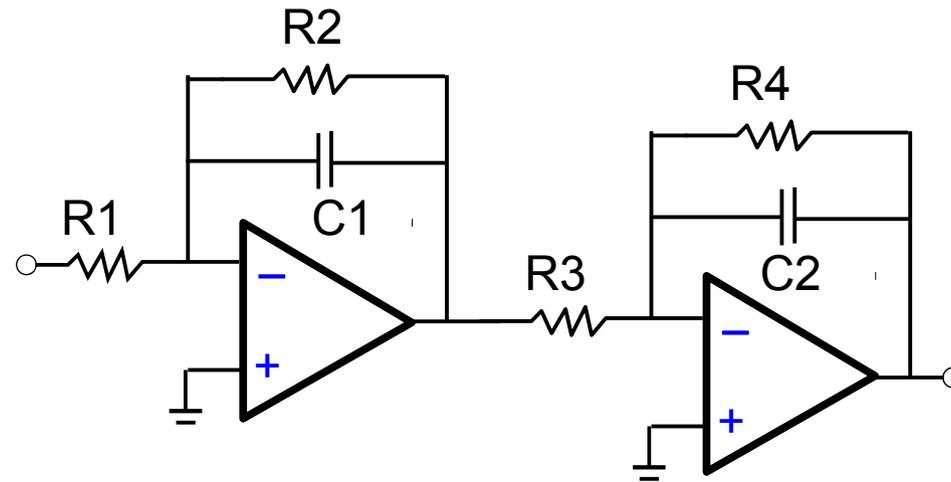
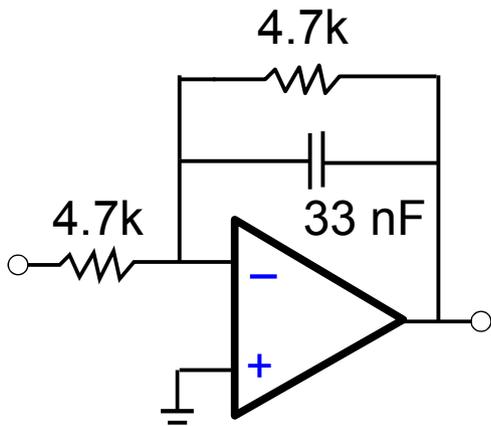
$$\frac{V_{OUT}}{V_{IN}} = \frac{R_2}{R_1} \underbrace{\left(\frac{1}{1 + j\omega R_2 C_1} \right)}_{\text{1st pole}} \frac{R_4}{R_3} \underbrace{\left(\frac{1}{1 + j\omega R_4 C_2} \right)}_{\text{2nd pole}}$$





1-pole: 1 kHz

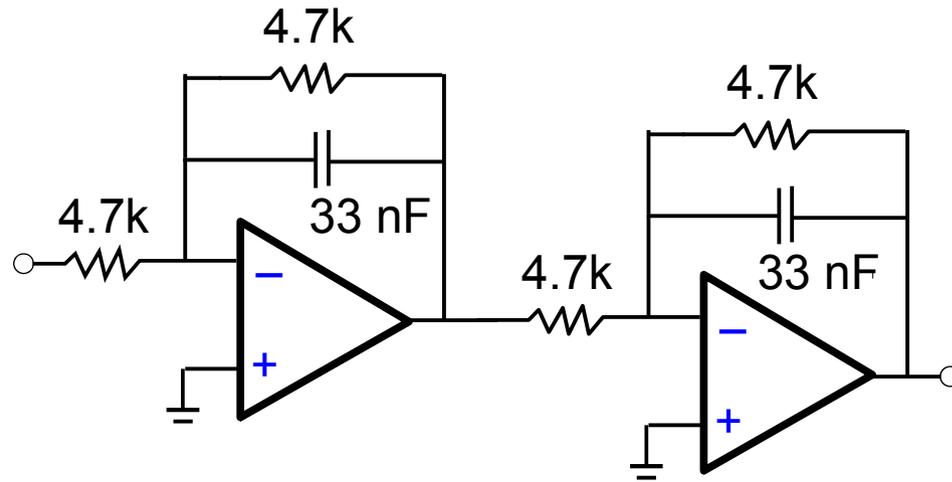


1st-pole: 1 kHz


2nd-pole: 1 kHz

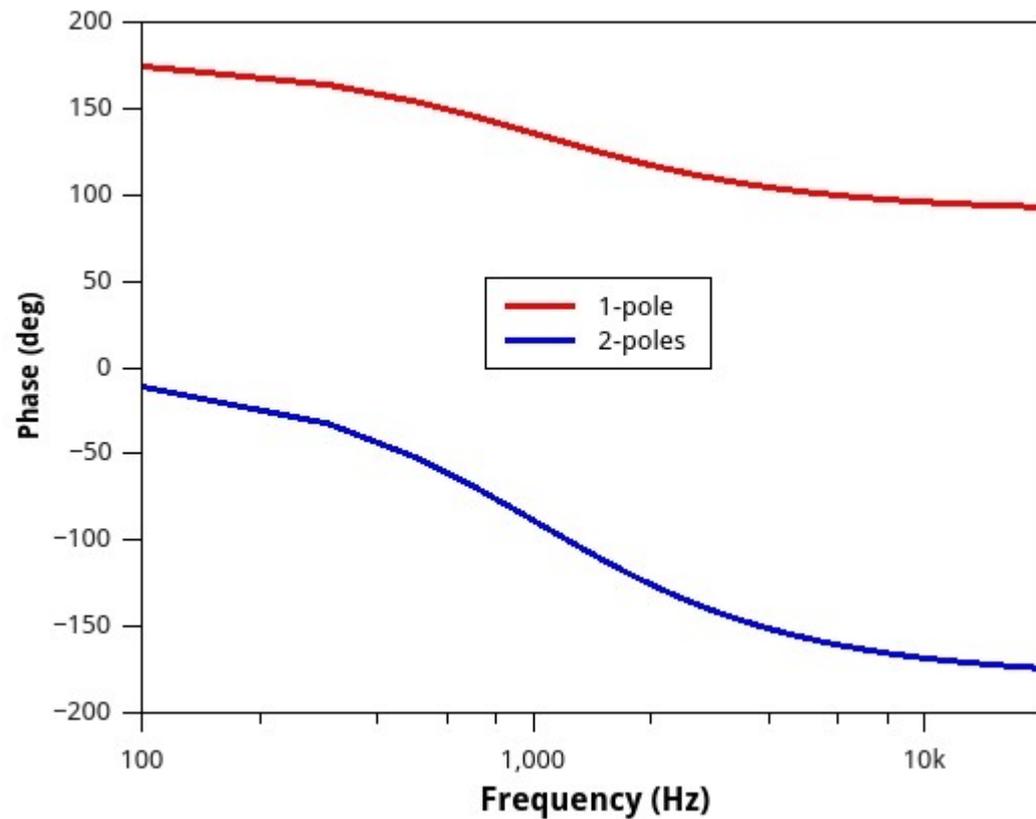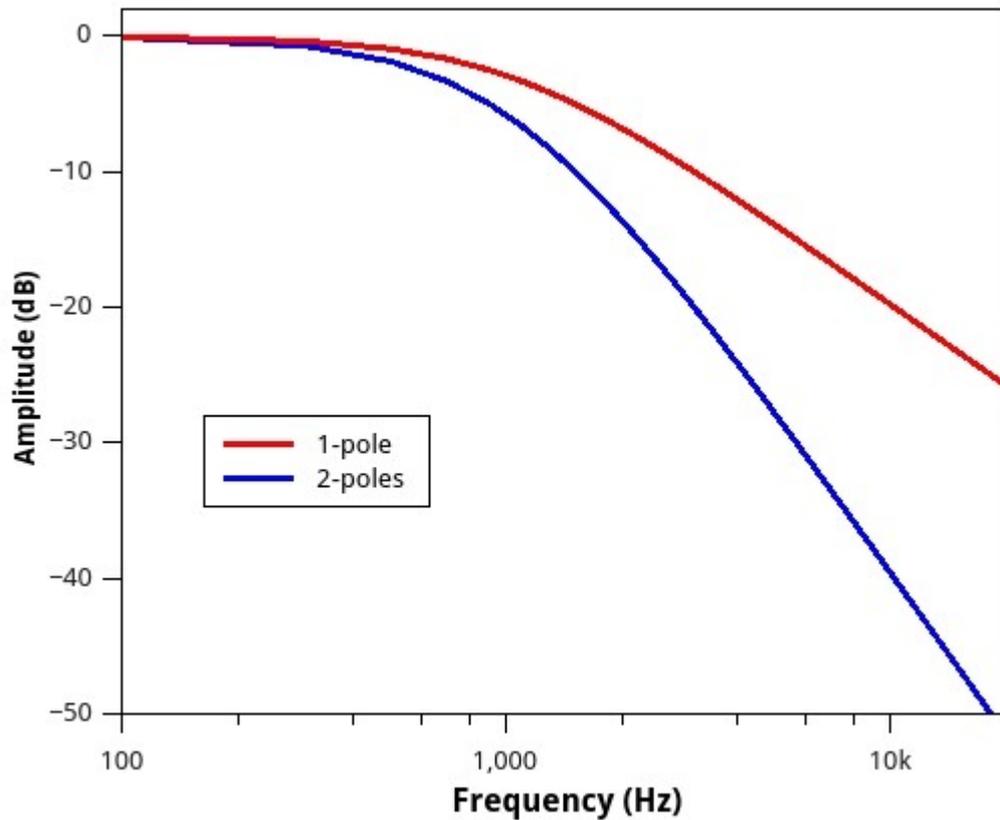



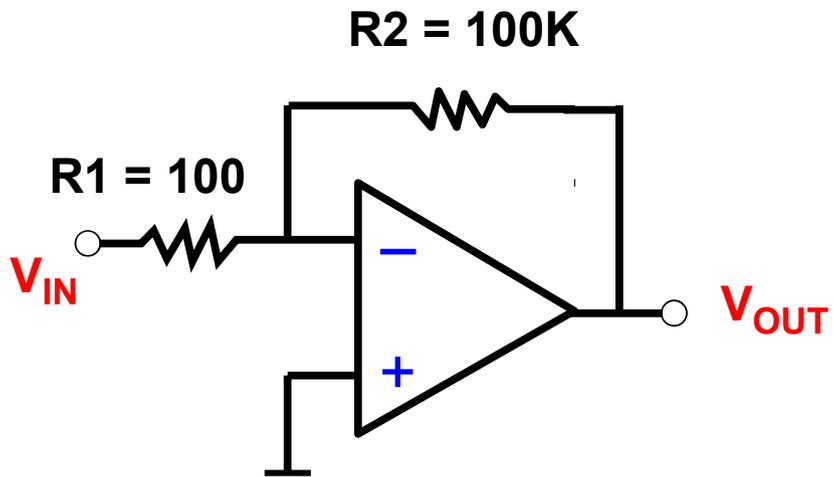
NON-IDEAL BEHAVIOR: GAIN-BANDWIDTH PRODUCT


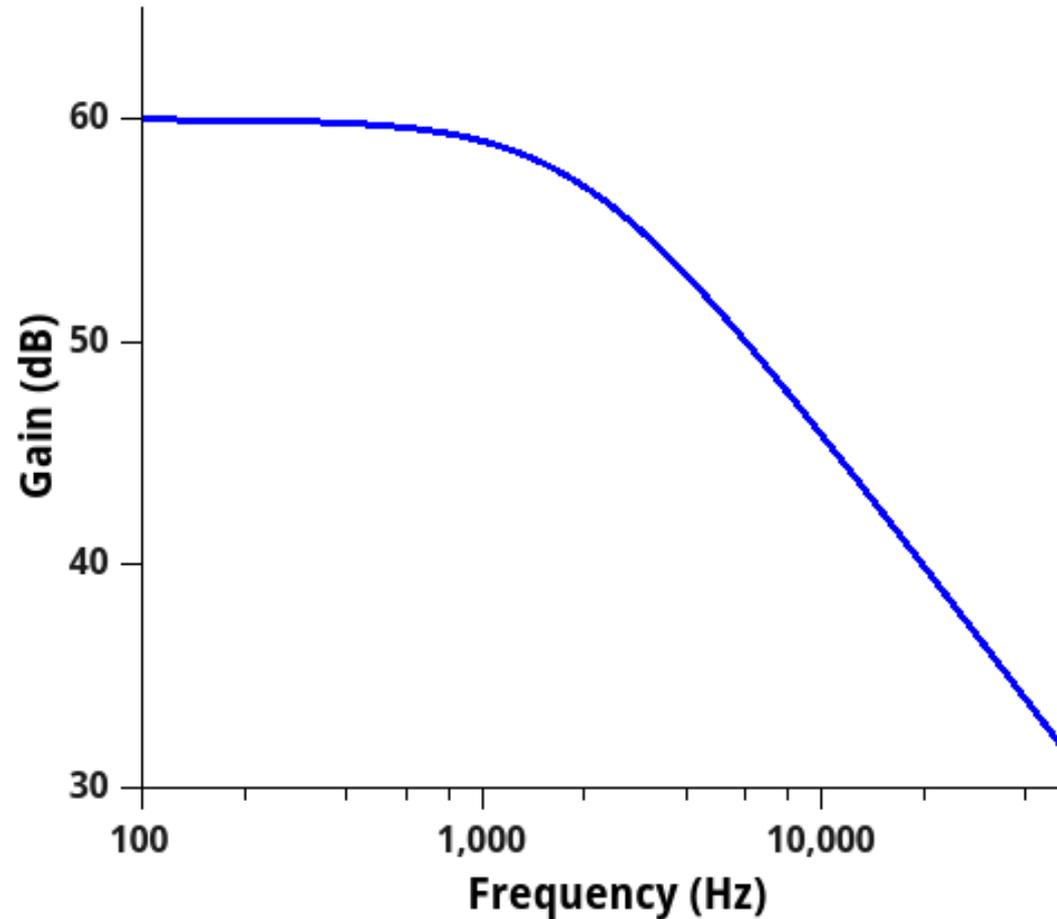
$$\text{GAIN} = -\frac{R2}{R1} = 60 \text{ dB}$$



NON-IDEAL BEHAVIOR: SLEWING

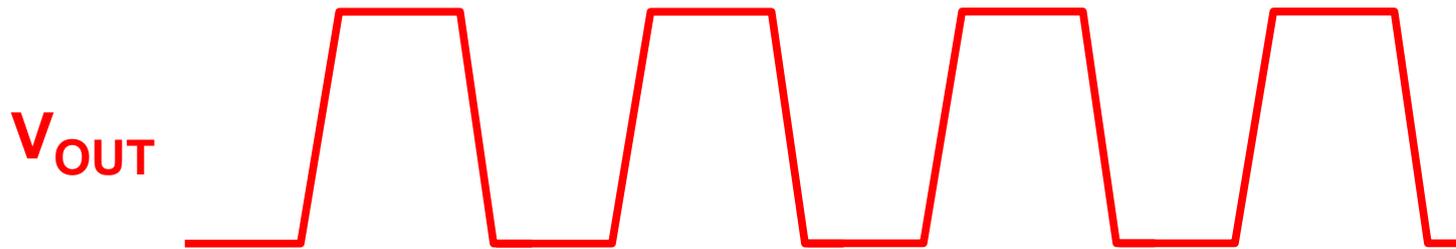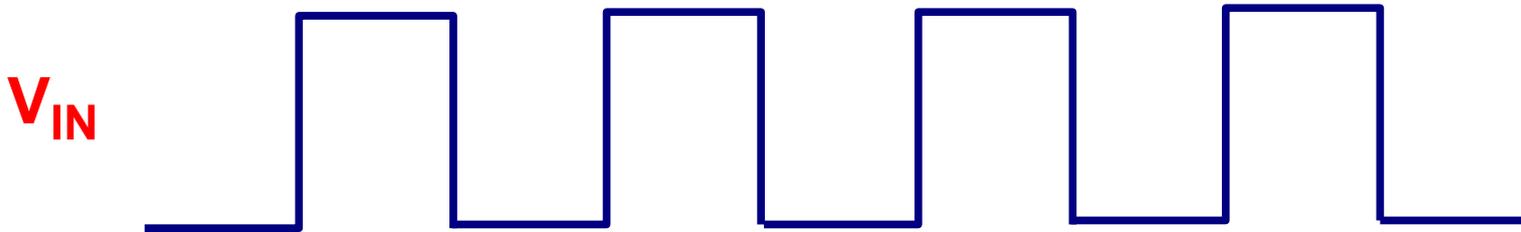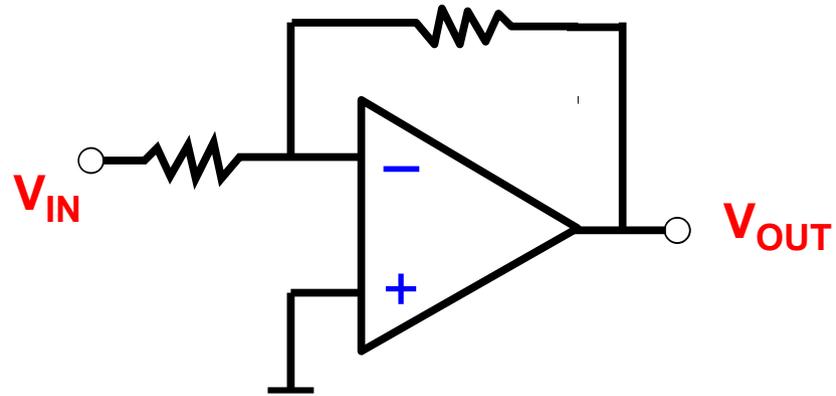

SLOPE:
 $V/\mu s$