

Lab 2 – Worksheet

1. Draw the truth table for the equation – $Y = A'B + BC + CD$.
2. Describe the circuit using VHDL and simulate it. (Hint: take the files and projects developed in the lab manual and modify it according to the new equation.
3. Simulate the new design and check it against the truth table from the first question.