## Lab 4 – Worksheet

Part I:

- 1. Design a 1 bit full adder with inputs: A, B, and  $C_{in}$ ; and outputs S and  $C_{out}$ .
- 2. Draw the truth table for your full adder.
- 3. Use a K-map, simplify and draw the resultant circuit.
- 4. Create a VHDL model of your testbench using simple gates (e.g., and, or, not, xor, etc.)
- 5. Create a VHDL testbench to verify your truth table.
- 6. Demonstrate the simulation of your testbench to the TA.

Part II:

- 1. Design a 4 bit twos-complement adder/subtracter using your full adder and simple gates.
- 2. The circuit should have two 4 bit inputs A(3 downto 0), B(3 downto 0) and a single bit to select addition or subtraction.
- 3. The circuit should also produce one output S(3 downto 0).
- 4. Draw a schematic and write VHDL.
- 5. Design a circuit to detect overflow and signal when overflow has occurred. (e.g., there should be a single bit output overflow that indicates overflow as occurred.) Write VHDL for the overflow as well.
- 6. Create a VHDL testbench to test at least 2 additions and one subtraction.
- 7. Demonstrate the simulation of your testbench to the TA.

Part III:

- 1. Next we will use our adder/subtracter in a simple ALU (Arithmetic Logic Unit).
- 2. Use your 4 to 1 mux select from the output of four different ALU operations:
  - (a) The adder/subtracter
  - (b) a AND b
  - (c) a OR b
  - (d) a and /not b

- 3. This simple ALU will have 5 inputs: Mux selects s0,s1; a(3..0) and b(3..0); and sub (setting add or subtract.)
- 4. The outputs will be 4 bits s(3..0) and overflow.
- 5. Draw the schematic and write VHDL.
- 6. Write a VHDL testbench testing all four separate operations.
- 7. Demonstrate the simulation of your testbench to the TA.
- 8. Take the DXCRP-lab4.zip design and open the lab4 ise project.
- 9. You will need to make sure you are targeting the correct device, an XPLA 3 CoolRunner XC3064, and will probably have to add all of the input files.
- 10. Insert your simple alu VHDL component into xrcpdemo.vhd and connect to the provided wires. There is a seven-segment display driver provided as well as all of the inputs are connected. You should only need to connect your ALU and overflow detection circuits to to the provided signals.
- 11. Download your design onto the board.
- 12. Demonstrate the proper execution of your design on the board to the TA.