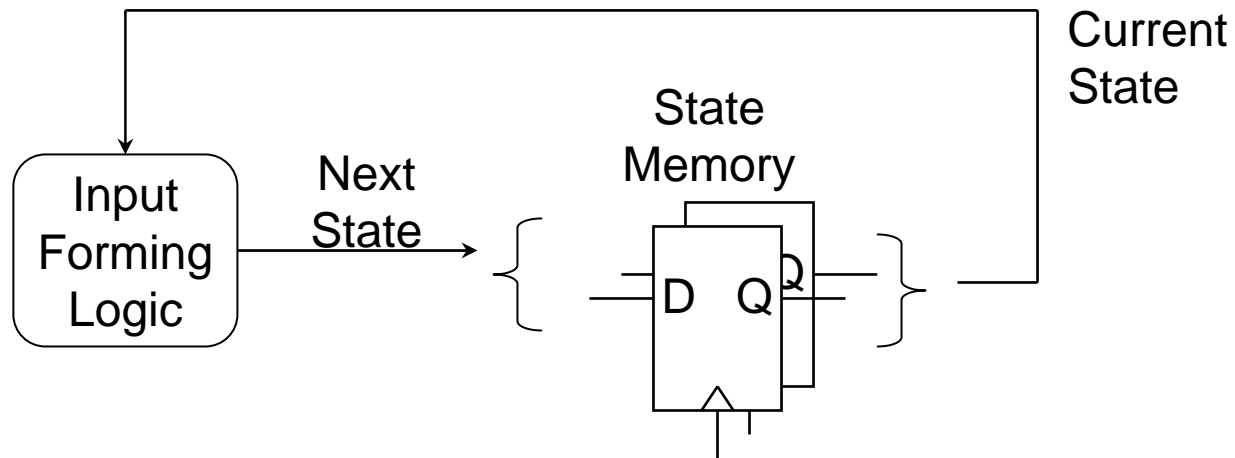



# Quick Overview of Counters

Counters  
Transition Tables  
Moore Outputs  
Stategraphs

# General Sequential Systems



# A Sequential Counter

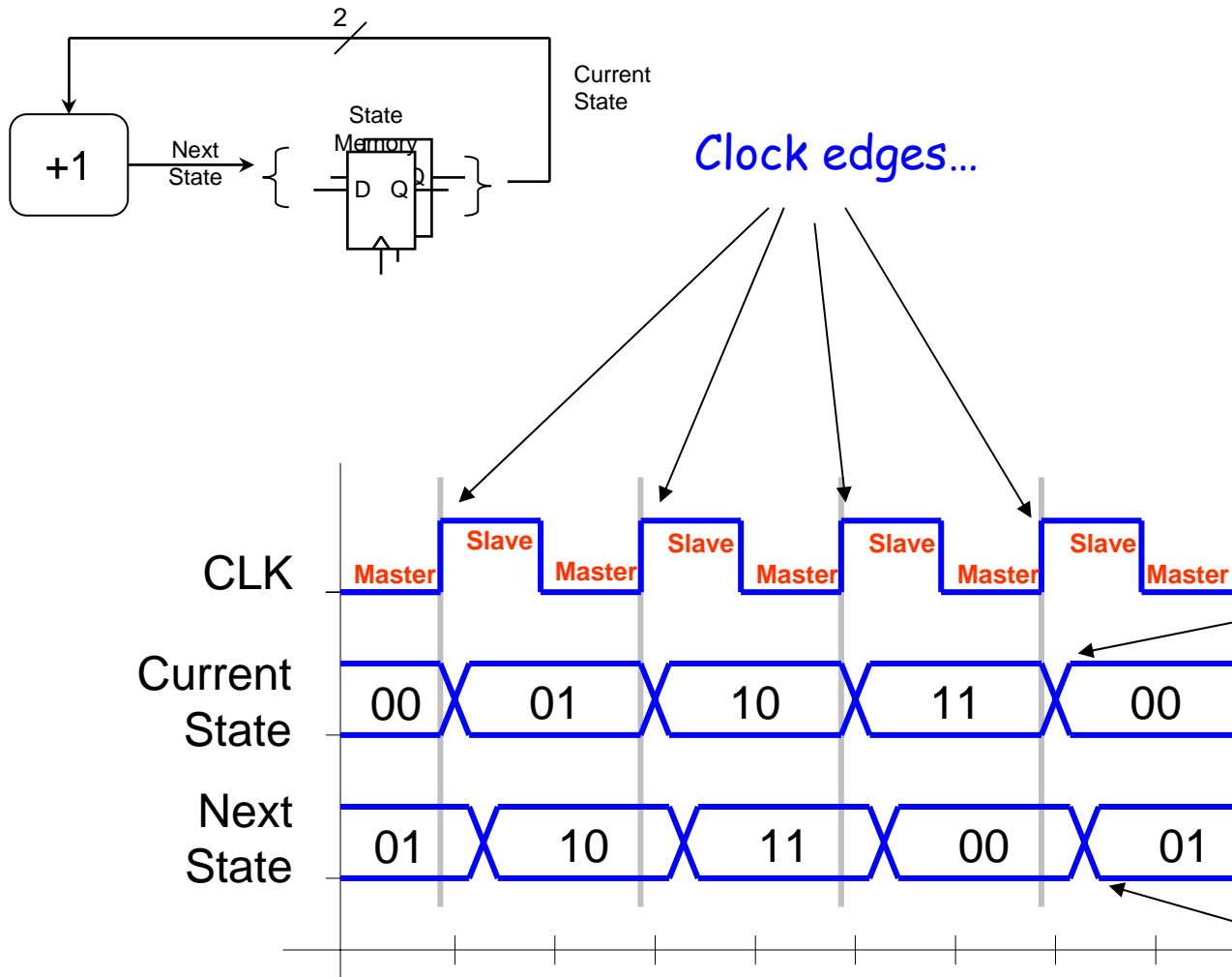

The current state loads the next state values in response to the clock edge.

IFL reacts after some gate delays to produce a new next state.

# Transition Table for 2-Bit Counter

Current State	Next State
00	01
01	10
10	11
11	00




Current State		Next State	
Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

It is the truth table for the input forming logic...

It describes what the *next state* values are as a function of the *current state* (clock is assumed)

# Implementation of 2-Bit Counter

Current State		Next State	
Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

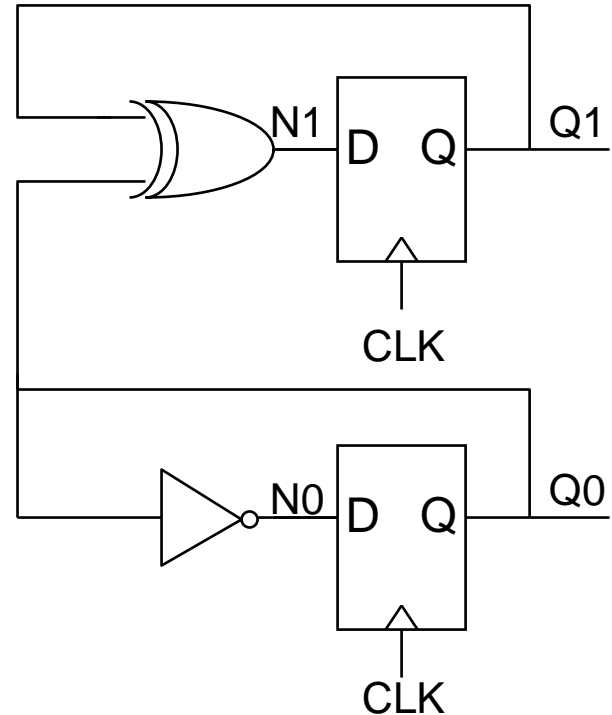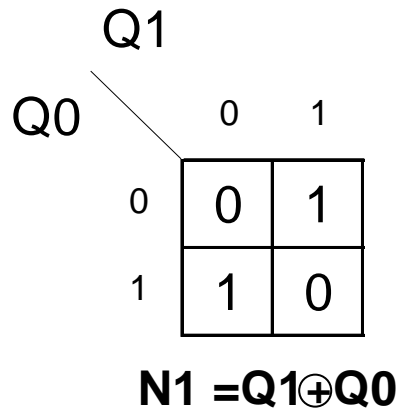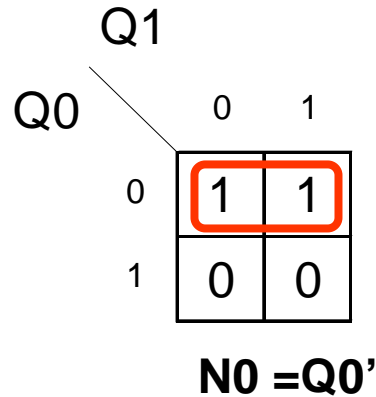

# Example 2 - A Gray Code Counter

Q1	Q0	N1	N0
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0

Ordering of TT rows  
chosen to make it easier  
to see the count pattern.


It doesn't change result.

		Q1	
		0	1
Q0	0	0	0
	1	1	1

$$N1 = Q0$$

		Q1	
		0	1
Q0	0	1	0
	1	1	0

$$N0 = Q1'$$

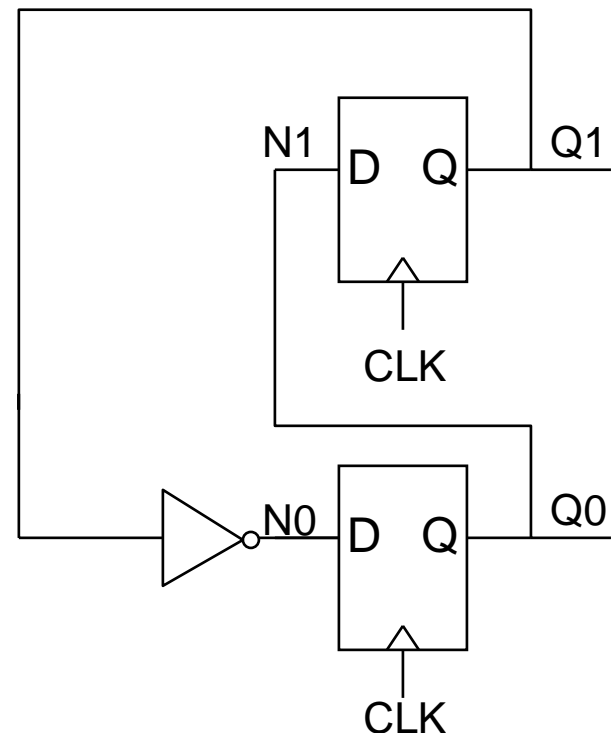

# Example 3 - Not All Count Values Used

Desired count sequence = 00 - 01 - 11 - 00 ...

Q1	Q0	N1	N0
0	0	0	1
0	1	1	1
1	1	0	0
1	0	?	?

What should next state for 10 be?

# Example 3 - Not All Count Values Used

Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	X	X
1	1	0	0

		Q1	
		0	1
Q0	0	0	X
	1	1	0

$$N1 = Q0 \oplus Q1$$

		Q1	
		0	1
Q0	0	1	X
	1	0	0

$$N0 = Q0'$$

Do the normal KMap w/don't cares minimization...



# Example 4 - A Ring Counter

Desired count sequence = 001 - 010 - 100 - 001 ...

Q2	Q1	Q0	N2	N1	N0
0	0	0	X	X	X
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	X	X	X
1	0	0	0	0	1
1	0	1	X	X	x
1	1	0	X	X	X
1	1	1	X	X	X

N2

		Q <sub>2</sub>	
		0	1
Q <sub>1</sub> Q <sub>0</sub>	00	X	
	01		X
	11	X	X
	10	1	X

N1

		Q <sub>2</sub>	
		0	1
Q <sub>1</sub> Q <sub>0</sub>	00	X	
	01	1	X
	11	X	X
	10		X

N0

		Q <sub>2</sub>	
		0	1
Q <sub>1</sub> Q <sub>0</sub>	00	X	1
	01		X
	11	X	X
	10		X

Doing KMaps leads to:


$$N2 = Q1$$

$$N1 = Q0$$

$$N0 = Q2$$

No big surprise here!!!!


## Example 4 - A Ring Counter

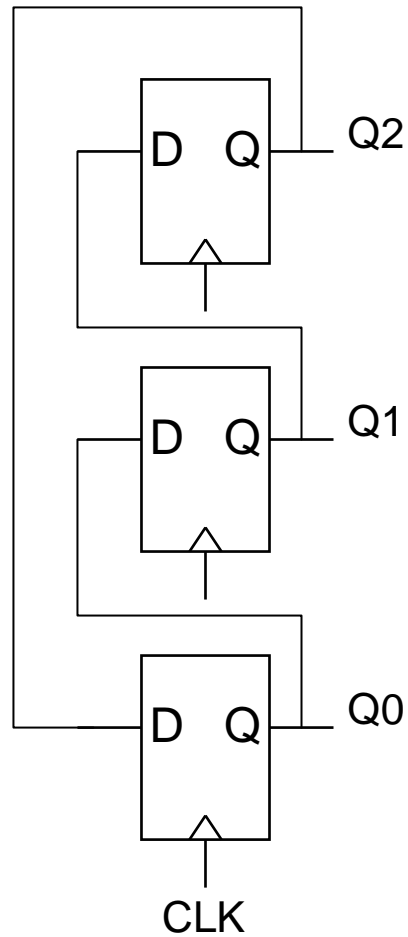

# General Counter Design Procedure

- Write transition table for counter
  - Use X's as appropriate
- Reduce each Nx variable to an equation
- Implement input forming logic (IFL) using gates
- Draw schematic using FF's + IFL

# Counters With Outputs

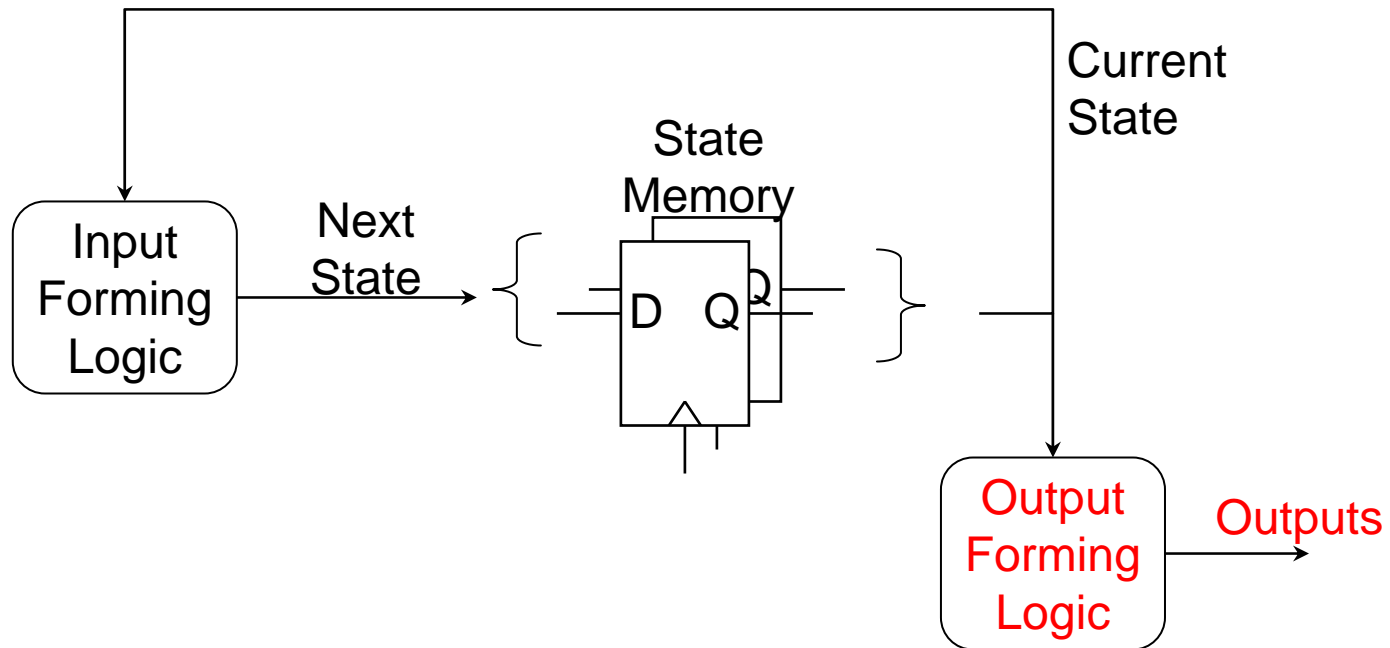

$$\text{Outputs} = f(\text{CurrentState})$$

# Counters With Outputs

**Z=1 when count={0,3,6}**

Q2	Q1	Q0	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

**Z is called a Moore or static output.  
It is a function only of the current state**


# Combined Transition Table

Q2	Q1	Q0	N2	N1	N0	Z
0	0	0	0	0	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	0
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	0	0
1	1	0	1	1	1	1
1	1	1	0	0	0	0

$$Z = Q2'Q1'Q0' + Q2'Q1Q0 + Q2Q1Q0'$$

(implement OFL with gates)

# Counter With A Moore Output

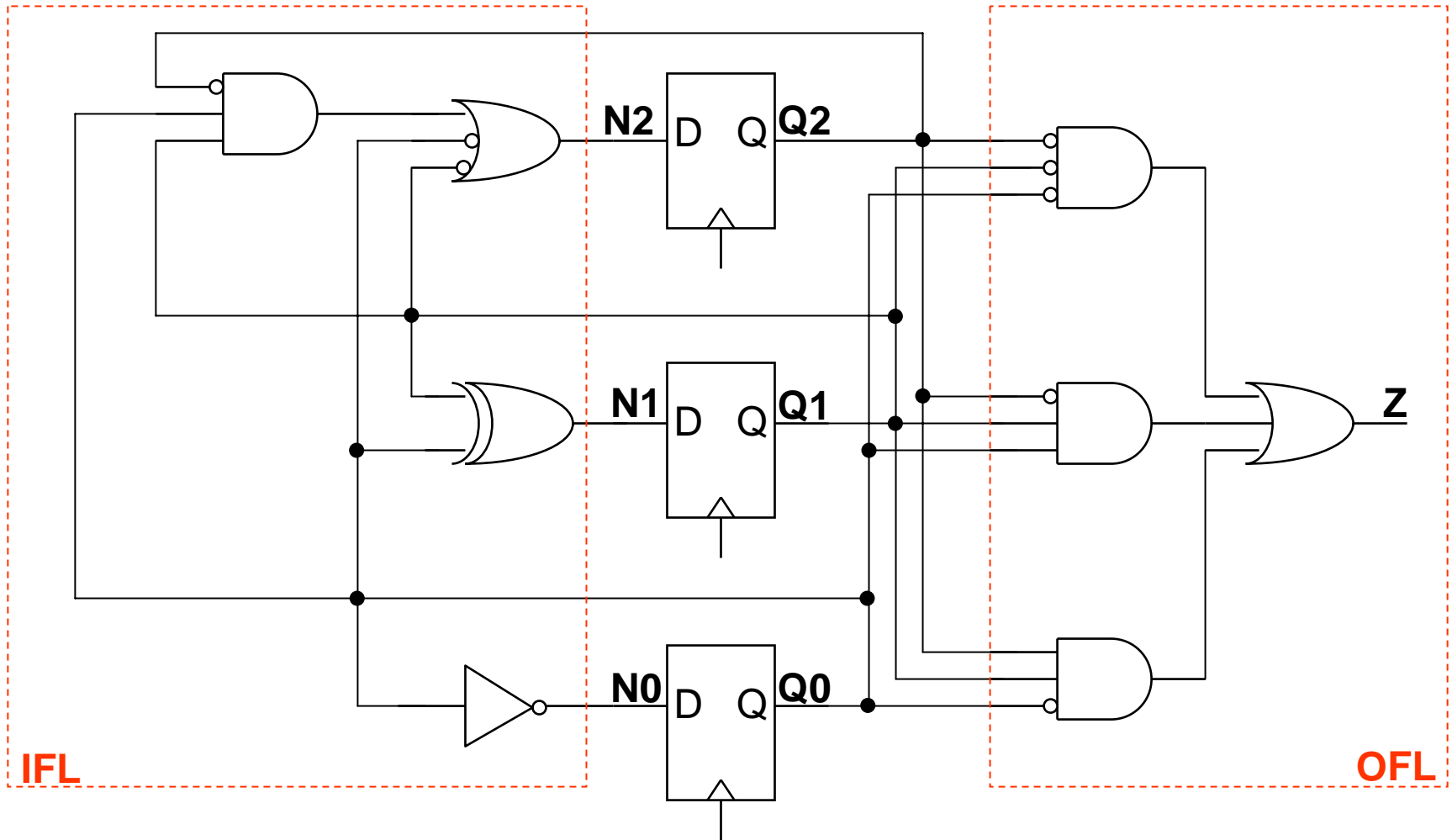


# State Graphs



# Binary Counter State Graph

Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

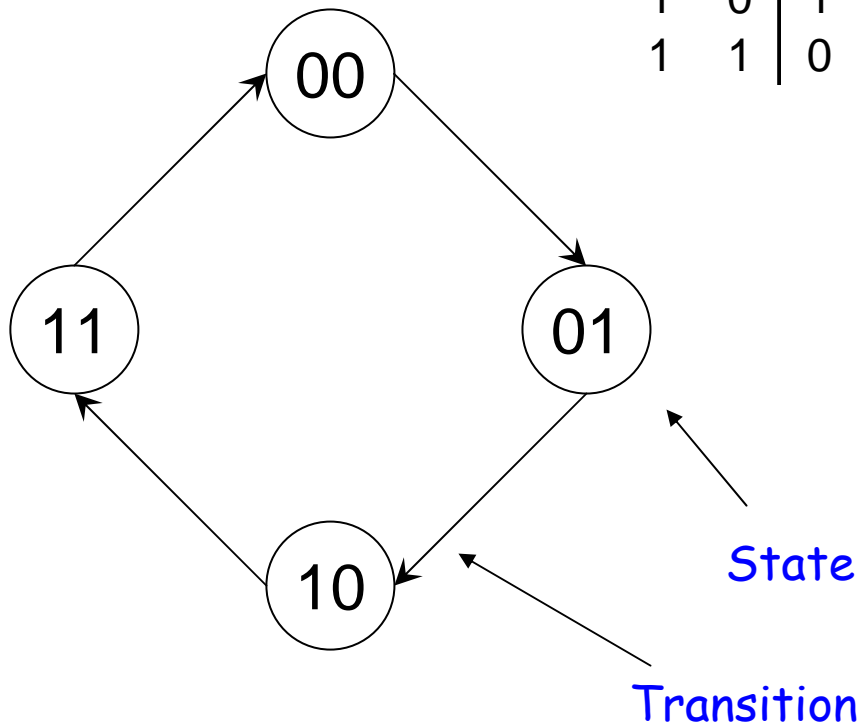


State graphs are graphical representations of TT's

They contain the same information: no more, no less


# Binary Counter State Graph

Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

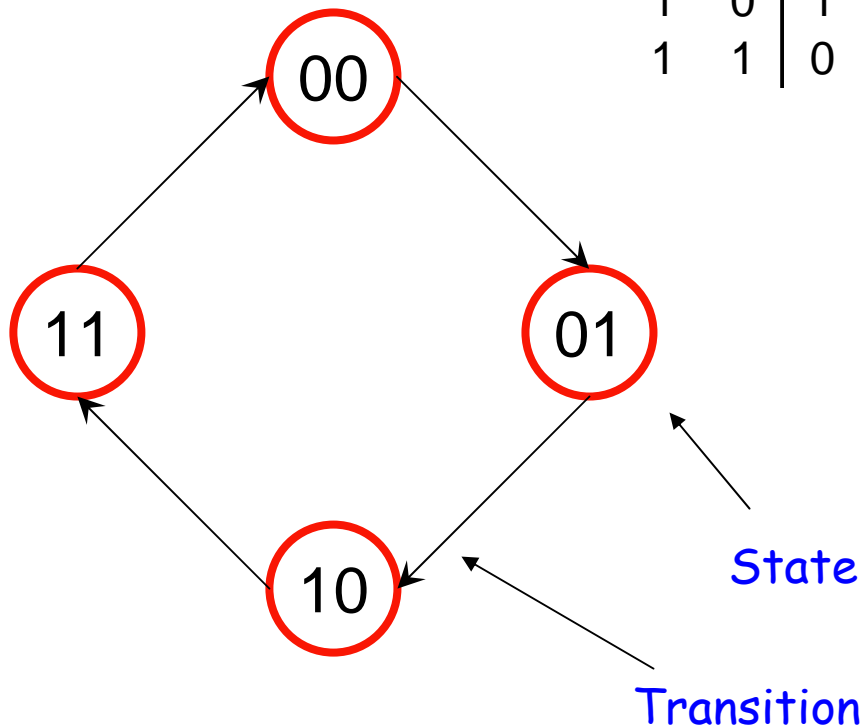

# Binary Counter State Graph

Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

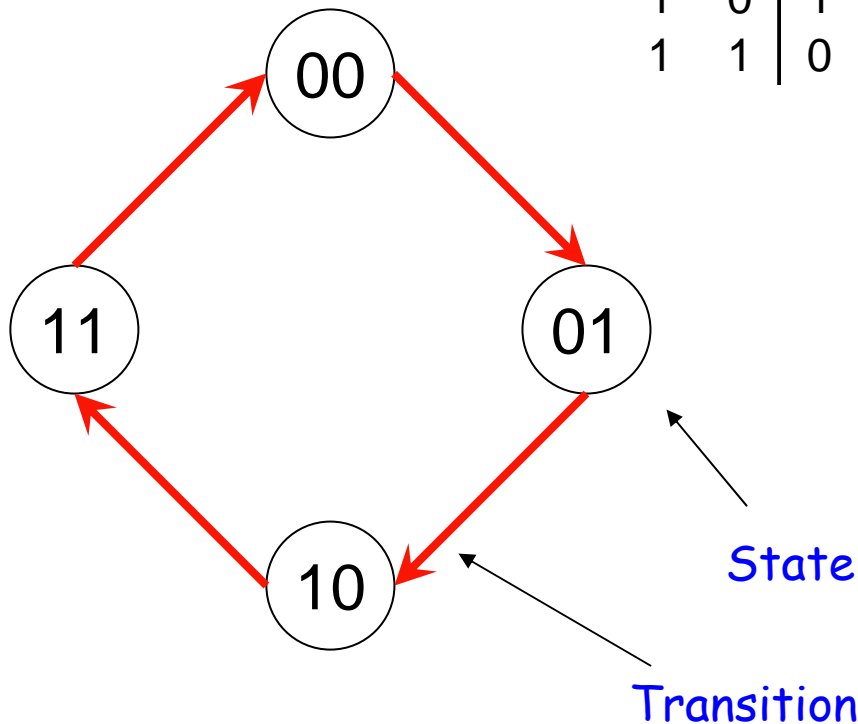


Each arc is a transition from one state to another


These arcs are unlabelled, meaning the transition is *always* taken on the clock edge

# Gray Code Counter State Graph

Q1	Q0	N1	N0
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0

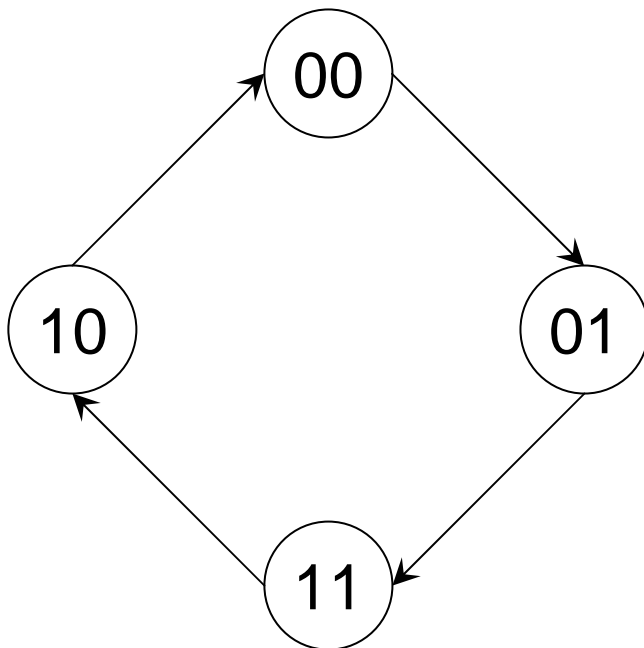

# State Graphs for Counters With Inputs

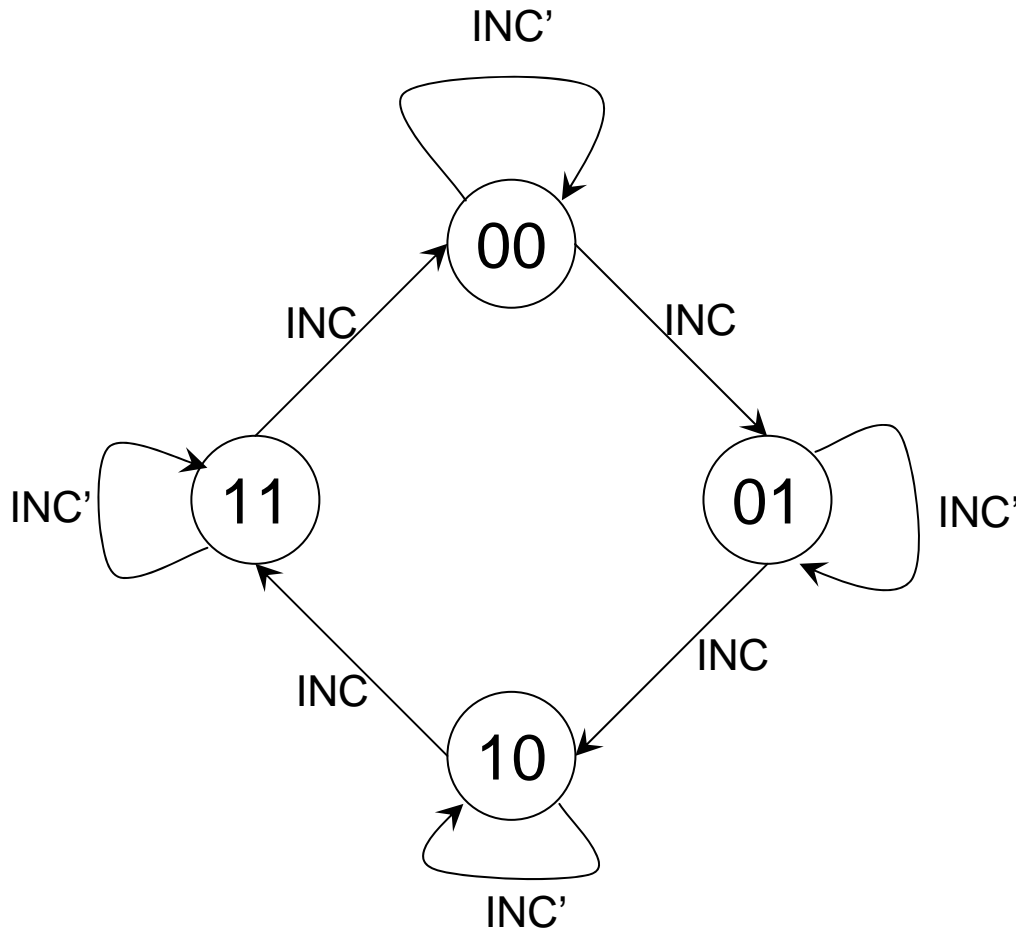


INC controls whether transition is taken or not...

INC	Q1	Q0	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

There is a one-to-one correspondence between the rows of the TT and the arcs in the SG


# State Graphs for Counters With Inputs

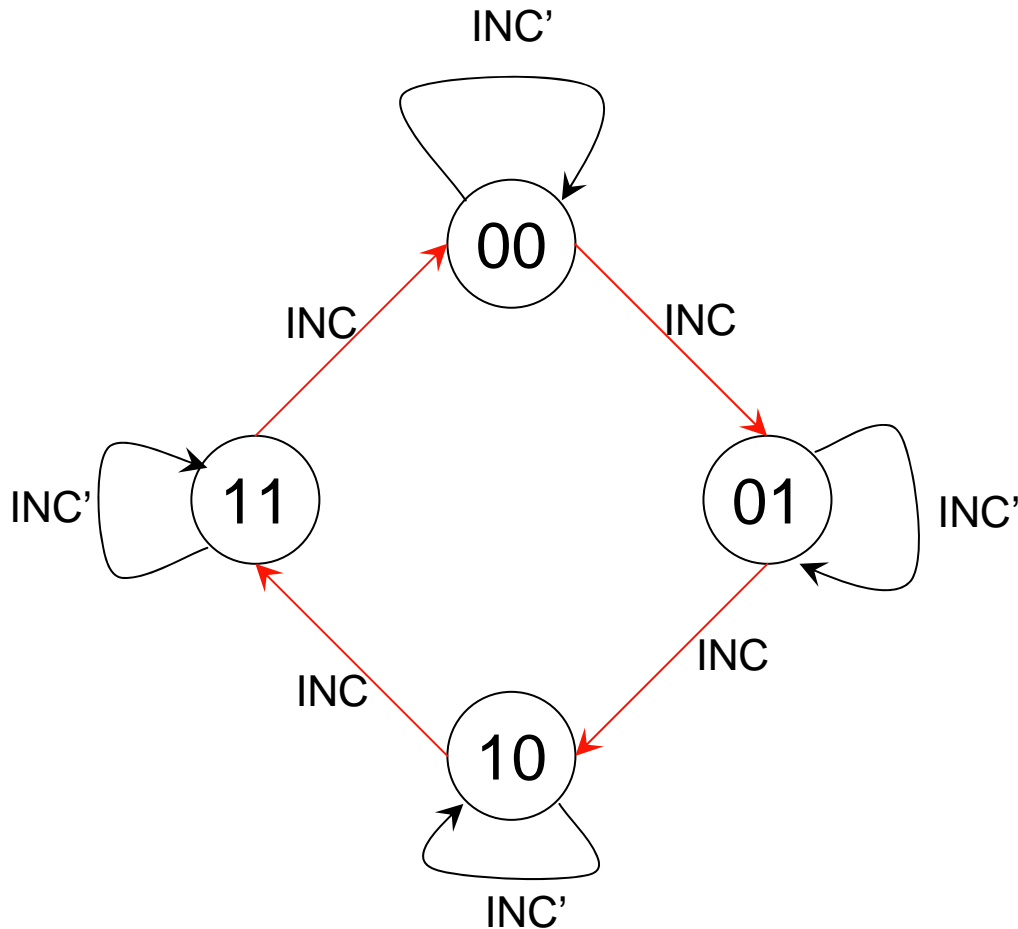

When INC=1, we change state...

INC	Q1	Q0	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0


# State Graphs for Counters With Inputs

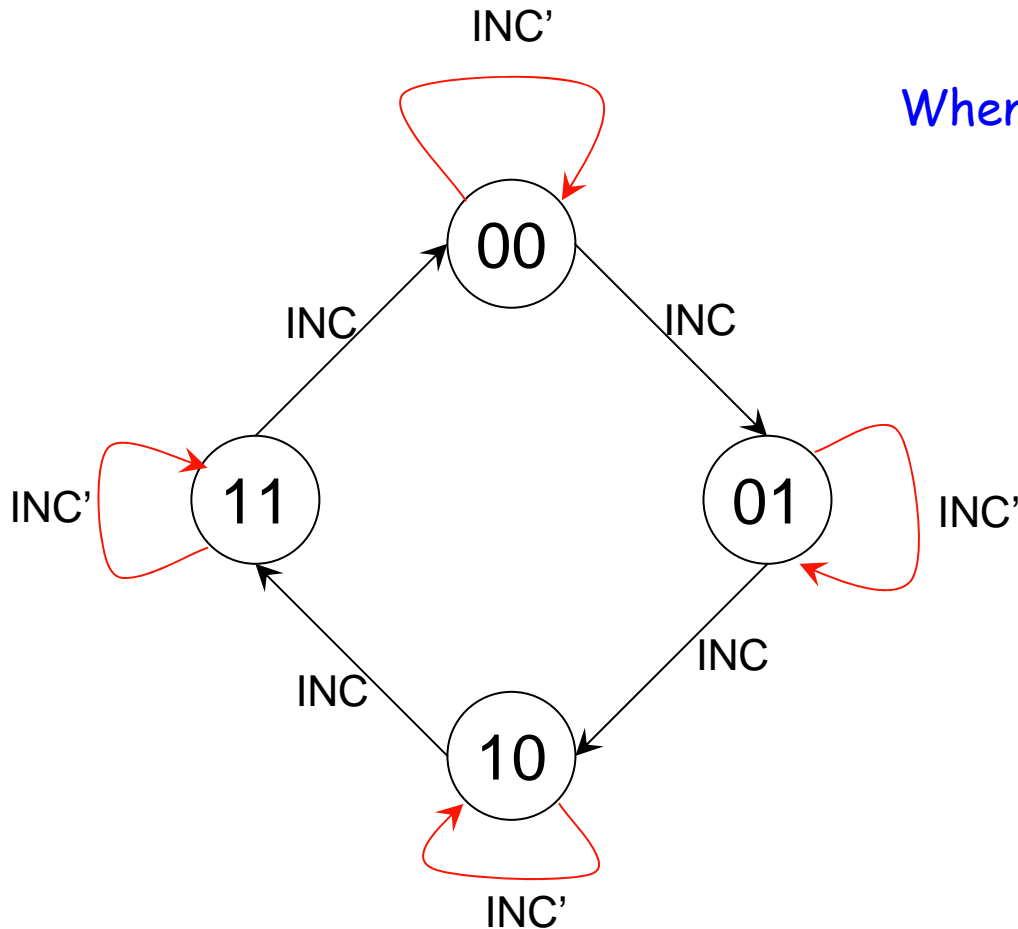

When INC=0, we stay in the same state...

INC	Q1	Q0	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

# SG for Counter With Multiple Inputs

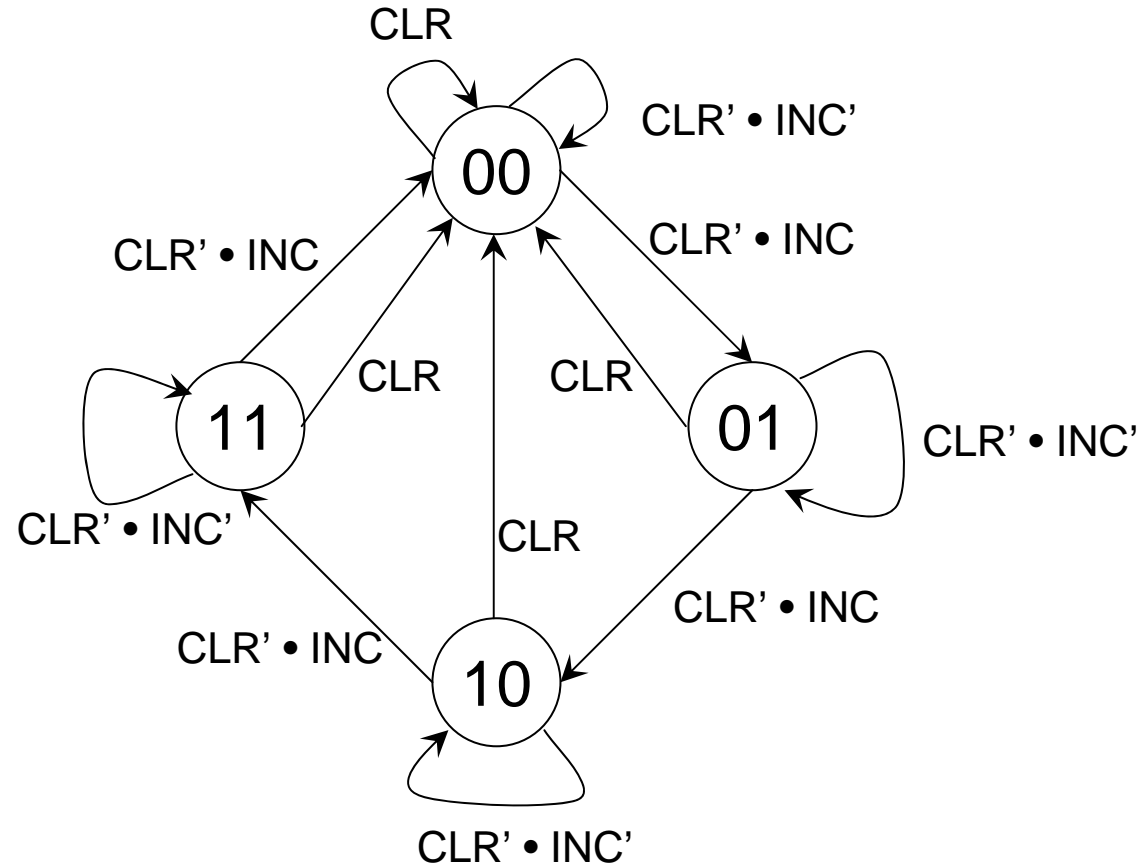


CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

NOT an exact correspondence between TT rows and SG arcs, why?



# SG for Counter With Multiple Inputs

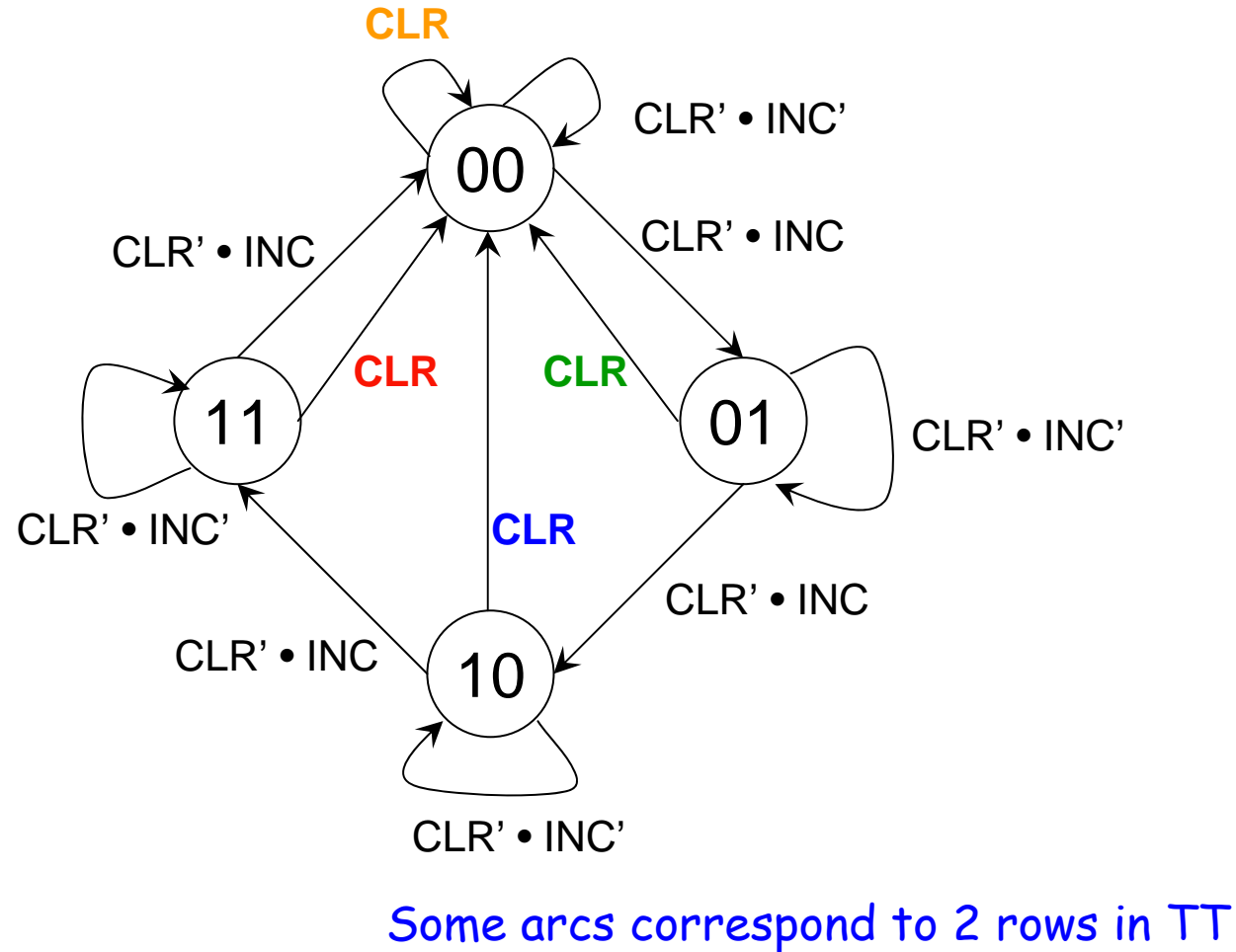

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

# Transition Table Simplification

CLR	INC	Q1	Q0	N1	N0		CLR	INC	Q1	Q0	N1	N0		CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0		0	0	0	0	0	0		0	0	0	0	0	0
0	0	0	1	0	1		0	0	0	1	0	1		0	0	0	1	0	1
0	0	1	0	1	0		0	0	1	0	1	0		0	0	1	0	1	0
0	0	1	1	1	1		0	0	1	1	1	1		0	0	1	1	1	1
0	1	0	0	0	1		0	1	0	0	0	1		0	1	0	0	0	1
0	1	0	1	1	0		0	1	0	1	1	0		0	1	0	1	1	0
0	1	1	0	1	1		0	1	1	0	1	1		0	1	1	0	1	1
0	1	1	1	0	0	→	0	1	1	1	0	0	→	0	1	1	1	0	0
1	0	0	0	0	0		1	-	0	0	0	0		1	-	-	-	0	0
1	0	0	1	0	0		1	-	0	1	0	0							
1	0	1	0	0	0		1	-	1	0	0	0							
1	0	1	1	0	0		1	-	1	1	0	0							
1	1	0	0	0	0														
1	1	0	1	0	0														
1	1	1	0	0	0														
1	1	1	1	0	0														


These are input don't cares.  
 They are a shorthand for the TT on the left  
 This TT exactly matches SG on previous page

# Simplified Transition Tables With Input Don't Cares

- Contain exactly same information as original
  - Shorthand way of writing
- Should be able to easily convert back/forth

# Simplified State Graph


CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	-	-	-	0	0

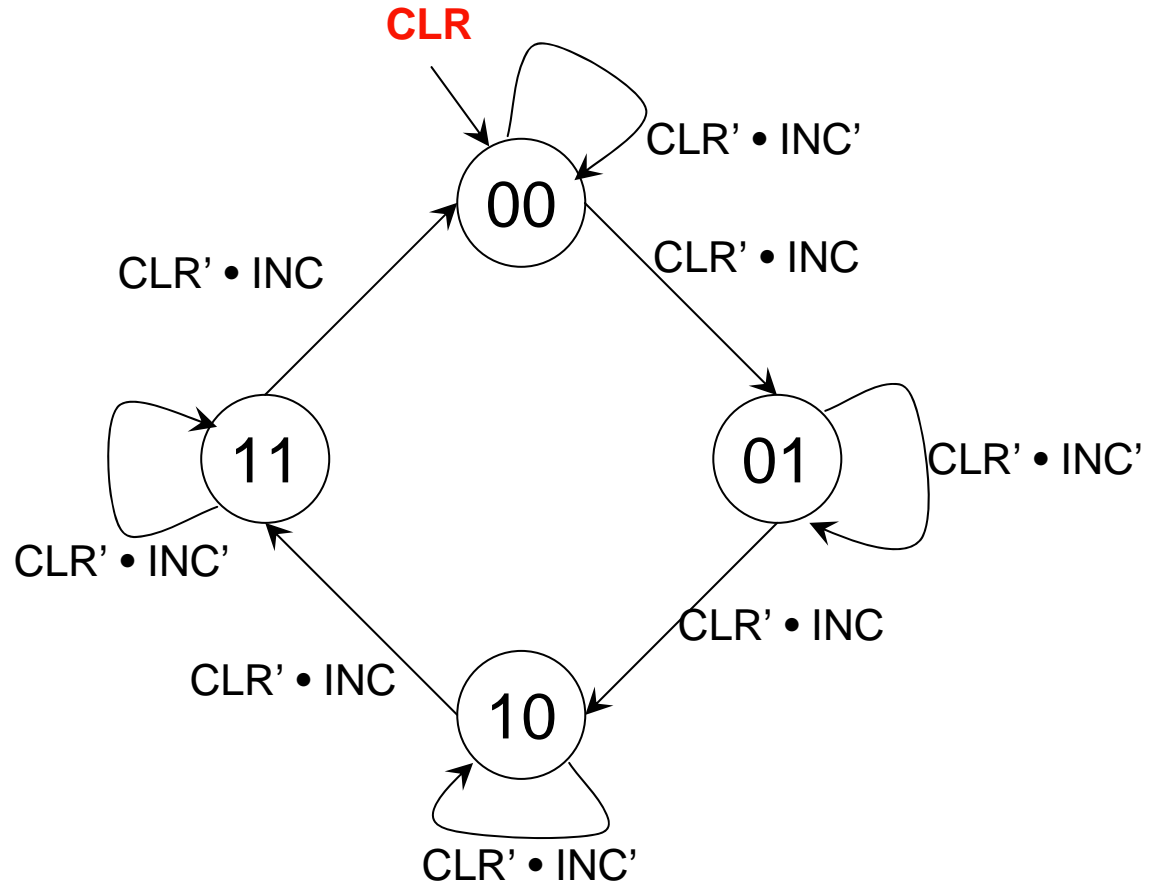

There is now a one-to-one correspondence between rows and arcs...
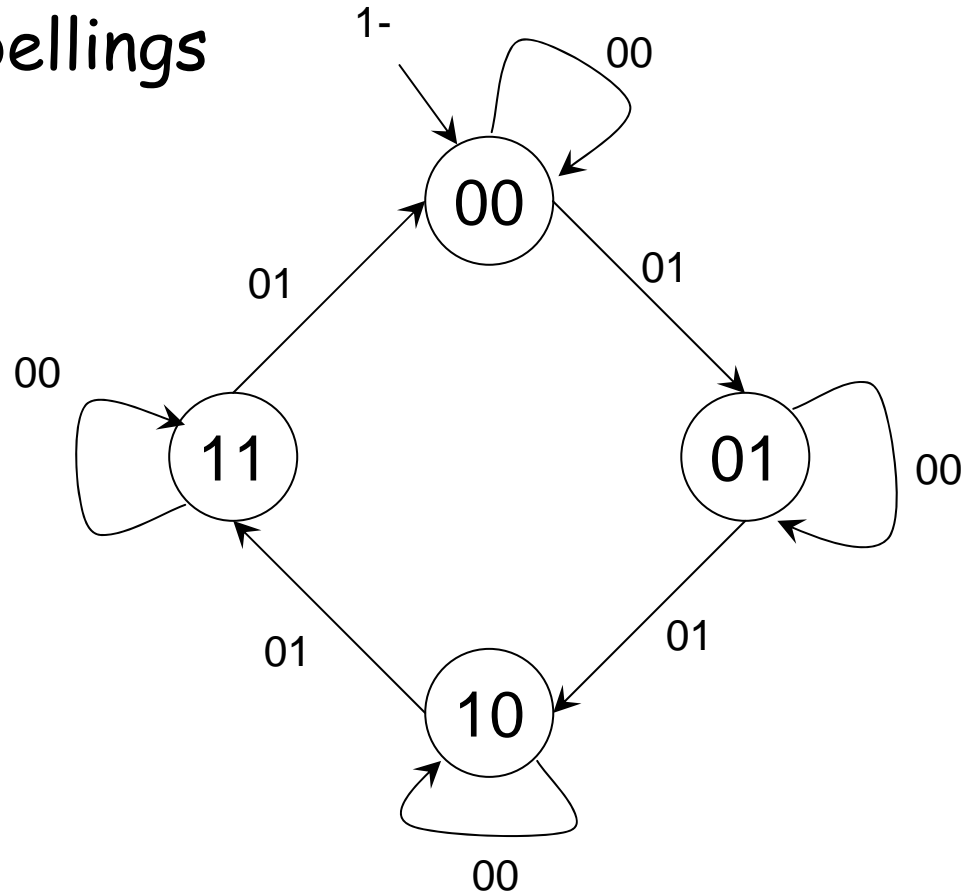
# More Simplified State Graphs

- If the order of inputs is known...
  - Use binary labellings



There is no **correct** way to draw a SG as long as you know precisely how it maps back to a transition table.

# Design Procedure Using State Graphs

1. Draw the state graph
2. Create an equivalent transition table
3. If transition table contains input don't cares,
  - *unfold* it to a full transition table
4. Complete the design using KMaps, gates, FF's

# Cover Examples in Book

- Page 260 - use white board
- Look @ process on 268
- Another Example on 276 - use whiteboard