 



COUNTERS

Counters
Transition Tables
Moore Outputs
Counter Timing

General Sequential Systems



A Sequential Counter

 

The current state loads the next state values in response to the clock edge.

IFL reacts after some gate delays to produce a new next state.

Transition Table for 2-Bit Counter

Current State	Next State
00	01
01	10
10	11
11	00




Current State		Next State	
Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

It is the truth table for the input forming logic...

It describes what the *next state* values are as a function of the *current state* (clock is assumed)

Implementation of 2-Bit Counter

Current State		Next State	
Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

 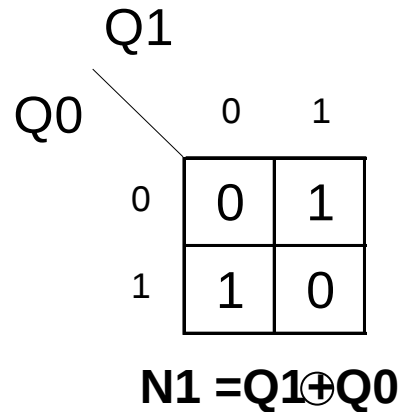 

Example 2 - A Gray Code Counter

Q1	Q0	N1	N0
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0

Ordering of TT rows
chosen to make it easier
to see the count pattern.


It doesn't change result.

		Q1	
		0	1
Q0	0	0	0
	1	1	1

$$N1 = Q0$$

		Q1	
		0	1
Q0	0	1	0
	1	1	0


$$N0 = Q1'$$

 

General Counter Design Procedure

- Write transition table for counter
 - Use X's as appropriate
- Reduce each Nx variable to an equation
- Implement input forming logic (IFL) using gates
- Draw schematic using FF's + IFL

Counters With Alternative FF's

 


Excitation Table for T Flip Flop

Transition Table

T	Q	Q+
0	0	0
0	1	1
1	0	1
1	1	0

Rearranging rows and/or columns...

 

Excitation Table

Q	Q+	T
0	0	0
0	1	1
1	0	1
1	1	0

Tells how inputs affect output

Tells what input to apply
to achieve desired
output transition

In the end, they are the same table, just rearranged...

TFF Counter Design Using Augmented Transition Table

Current State			Next State			TFF Inputs		
Q2	Q1	Q0	N2	N1	N0	T2	T1	T0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

T2

Q ₂ Q ₁ Q ₀	Q ₂	
	0	1
00		
01		
11	1	1
10		

$$T2 = Q1 \cdot Q0$$


$$T1 = Q0$$

$$T0 = '1'$$

Next state values

Inputs to apply to achieve desired next state

TFF Counter Design

 

Excitation Table for JK Flip Flop

J	K	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Tells how inputs affect output

Rearranging rows and/or columns...



Q	Q+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Tells what inputs to apply to achieve desired output transition

Do you see why the X's?

In the end, they are the same table, just rearranged...

JKFF Gray Code Counter Design

Q2	Q1	Q0	N2	N1	N0	J2	K2	J1	K1	J0	K0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0

$$J2 = Q1Q0'$$

$$K2 = Q1'Q0'$$

$$J1 = Q2'Q0$$

$$K1 = Q2Q0$$

$$J0 = Q2Q1 + Q2'Q1' = K0'$$

$$K0 = Q2'Q1 + Q2Q1' = Q2 \odot Q1$$


Next state values

Inputs to apply to achieve desired next state

General Counter Design Procedure

- Write transition table for counter
 - Use X's as appropriate
 - If not DFF's, augment table
- Reduce each FF input variable to equation
- Implement IFL with gates
- Draw schematic using FF's + gates

Counters With Outputs

 

$$\text{Outputs} = f(\text{CurrentState})$$

Counters With Outputs


Z=1 when count={0,3,6}

Q2	Q1	Q0	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

**Z is called a Moore or static output.
It is a function only of the current state**

Combined Transition Table


Q2	Q1	Q0	N2	N1	N0	Z
0	0	0	0	0	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	0
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	0	0
1	1	0	1	1	1	1
1	1	1	0	0	0	0

 
 Current state Next state Output



$$Z = Q2'Q1'Q0' + Q2'Q1Q0 + Q2Q1Q0'$$

(implement OFL with gates)

Counter With A Moore Output

 

Counter Delay Characteristics

  


$$T_{\text{ClockPeriod}} \geq t_{\text{CLK-Q}} + t_{\text{IFL}} + t_{\text{setup}}$$

Counter Delay Example

- $t_{\text{CLK} \rightarrow \text{Q}} = 1\text{ns}$
- $t_{\text{IFL}} = 7\text{ns}$
- $t_{\text{setup}} = 2\text{ns}$

- $T_{\text{ClockPeriod}} \geq 10\text{ns} \quad (10 \times 10^{-9} \text{ sec})$
- $\text{ClockRate} \leq 100\text{MHz} \quad (100 \times 10^6 \text{ Hz})$
 - $\text{Rate} = 1/\text{Period}$

Next State and Output Timings

 

More outputs appear $t_{\text{CLK} \rightarrow Q} + t_{\text{OFL}}$ after the clock edge.

Counters and Timing

- The count sequence affects the size of IFL
- The size of the IFL affects t_{IFL}
- t_{IFL} affects $T_{ClockPeriod}$
- Choosing binary counts is not always fastest or smallest

Example Problem

- Design a 3-bit binary counter
- The Z output is TRUE iff count value is even
- The Y output is TRUE iff count value is multiple of 3

COUNTERS WITH INPUTS

Inputs


Mealy Outputs

Mealy vs. Moore

Counters With Inputs

- What if you don't want counter to increment every single cycle?

An Incrementable Counter

 


Note that the next state is a function of the input 'INC' as well as the current state.


Incrementable Counter Derivation

Doing the KMaps for this results in:

INC	Q1	Q0	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

 

N1

 


N0

$$N1 = (INC \cdot Q1' \cdot Q0) + (INC' \cdot Q1) + (Q1 \cdot Q0')$$

$$N0 = (INC' \cdot Q0) + (INC \cdot Q0') = INC \oplus Q0$$

Incrementable Counter Behavior

 

The counter increments on the clock edge only when INC is asserted

Counters With More Inputs

	CLR	INC	Q1	Q0	N1	N0
'CLR' = 'INC' = 0 No state transition	0	0	0	0	0	0
	0	0	0	1	0	1
	0	0	1	0	1	0
	0	0	1	1	1	1
'CLR' = 0 'INC' = 1 Counter Increments	0	1	0	0	0	1
	0	1	0	1	1	0
	0	1	1	0	1	1
	0	1	1	1	0	0
'CLR' = 1 'INC' = 0 Counter resets to '00'	1	0	0	0	0	0
	1	0	0	1	0	0
	1	0	1	0	0	0
	1	0	1	1	0	0
'CLR' = 1 'INC' = 1 What should it do?	1	1	0	0	?	?
	1	1	0	1	?	?
	1	1	1	0	?	?
	1	1	1	1	?	?

Precedence of INC vs. CLR?

1. Could do nothing
 2. Could give INC precedence
 3. Could give CLR precedence
 4. Assume $\text{INC}=\text{CLR}=1$ will never occur
- You decide when you draw the transition table

Case 1 - Do Nothing

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	1	1

Q₁Q₀

Clr Inc	00	01	11	10
00				
01		1		
11	1		1	
10	1	1	1	

N1

$$\begin{aligned}
 N1 = & \text{CLR}' \cdot \text{INC} \cdot Q1' \cdot Q0 + \\
 & \text{CLR}' \cdot \text{INC}' \cdot Q1 + \\
 & \text{CLR} \cdot \text{INC} \cdot Q1 + \\
 & \text{INC} \cdot Q1 \cdot Q0'
 \end{aligned}$$

Q₁Q₀

Clr Inc	00	01	11	10
00		1		
01	1		1	
11	1		1	
10		1		

N0

$$\begin{aligned}
 N0 = & \text{CLR}' \cdot \text{INC}' \cdot Q0 + \\
 & \text{CLR} \cdot \text{INC} \cdot Q0 + \\
 & \text{CLR}' \cdot \text{INC} \cdot Q0'
 \end{aligned}$$

Case 2 - Give INC Precedence

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	0	0

Q₁Q₀

Clr Inc	00	01	11	10
00				
01		1	1	
11	1			
10	1	1	1	

N1

$$N1 = \text{INC} \cdot Q1' \cdot Q0 + \text{CLR}' \cdot \text{INC}' \cdot Q1 + \text{INC} \cdot Q1 \cdot Q0'$$

Q₁Q₀

Clr Inc	00	01	11	10
00		1	1	
01	1			
11	1			
10		1	1	

N0

$$N0 = \text{CLR}' \cdot \text{INC}' \cdot Q0 + \text{INC} \cdot Q0'$$

Case 3 - Give CLR Precedence

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

Q₁Q₀

Clr Inc	00	01	11	10
00				
01		1		
11	1			
10	1	1		

N1

$$N1 = CLR' \cdot INC \cdot Q1' \cdot Q0 + \\ CLR' \cdot INC' \cdot Q1 + \\ CLR' \cdot Q1 \cdot Q0'$$

Q₁Q₀

Clr Inc	00	01	11	10
00		1		
01	1			
11	1			
10		1		

N0

$$N0 = CLR' \cdot INC' \cdot Q0 + \\ CLR' \cdot INC \cdot Q0'$$

Case 4 - Assume INC=CLR=1 Will Never Occur

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

Q₁Q₀

Clr Inc	00	01	11	10
00			x	
01		1	x	
11	1		x	
10	1	1	x	

N1

$$N1 = CLR' \cdot INC' \cdot Q1 + INC \cdot Q1' \cdot Q0 + CLR' \cdot Q1 \cdot Q0'$$

$$N0 = CLR' \cdot INC' \cdot Q0 + INC \cdot Q0'$$

What happens in the real circuit
when INC=CLR=1?

It depends on the final equations...

Q₁Q₀

Clr Inc	00	01	11	10
00		1	x	
01	1		x	
11	1		x	
10		1	x	

N0

Case 4 - When INC=CLR=1

What Happens?

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	1
1	1	1	1	0	0

$$N1 = CLR' \cdot INC' \cdot Q1 + INC \cdot Q1' \cdot Q0 + CLR' \cdot Q1 \cdot Q0'$$

$$N0 = CLR' \cdot INC' \cdot Q0 + INC \cdot Q0'$$


In the end, X's in TT's result in *some* predictable behavior, you just don't care what that is...

Moore vs. Mealy

Sequential Machines


Moore Sequential Machine (static)

 - Outputs are a function of current state only



Mealy Sequential Machine (dynamic)

 - Outputs are a function of current state and inputs



Example: 2 Bit Counter


- Moore output (Z) on count=3
- Mealy output (Y) when count=3 and INC=1
 - Incrementing from 3 back to 0

INC	Q1	Q0	N1	N0	Z	Y
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	1	0	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	0
1	0	1	1	0	0	0
1	1	0	1	1	0	0
1	1	1	0	0	1	1

Moore outputs usually require multiple entries in TT.

Mealy outputs often require only one.

Mealy vs. Moore Timing

 

Z output is TRUE
whenever count=3
(it is static function
of current state)

Y output is TRUE
whenever count=3
AND INC=1
(it is dynamic function
of current state and
input)