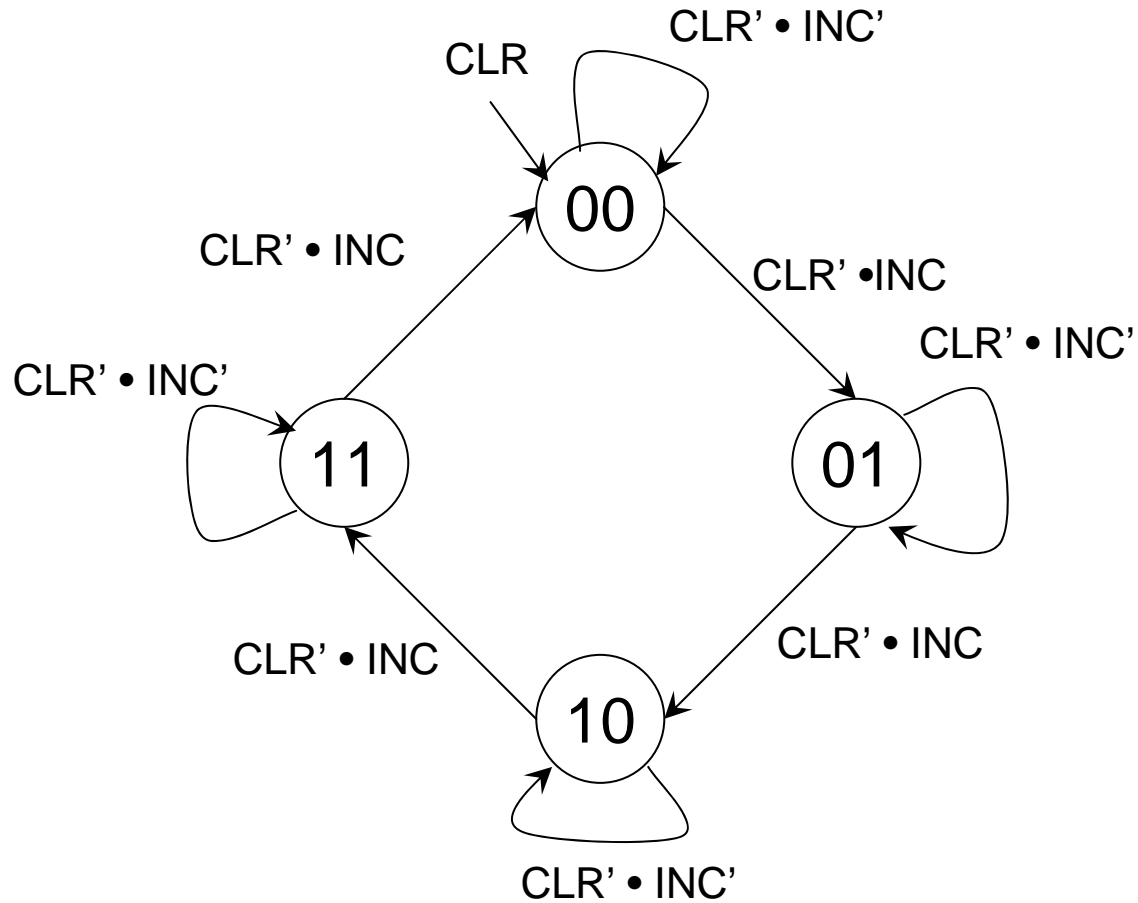


# Cascaded Counters


# A Mod4 Counter (A 2-bit counter)

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	-	-	-	0	0




# A Mod4 Counter With a Rollover Signal

CLR	INC	Q1	Q0	N1	N0	Rollover
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	0	0	1
1	-	-	-	0	0	0

 

Signal Rollover can be used to tell other circuitry that counter is rolling over to all 0's

# Cascading 2 Mod4 Counters

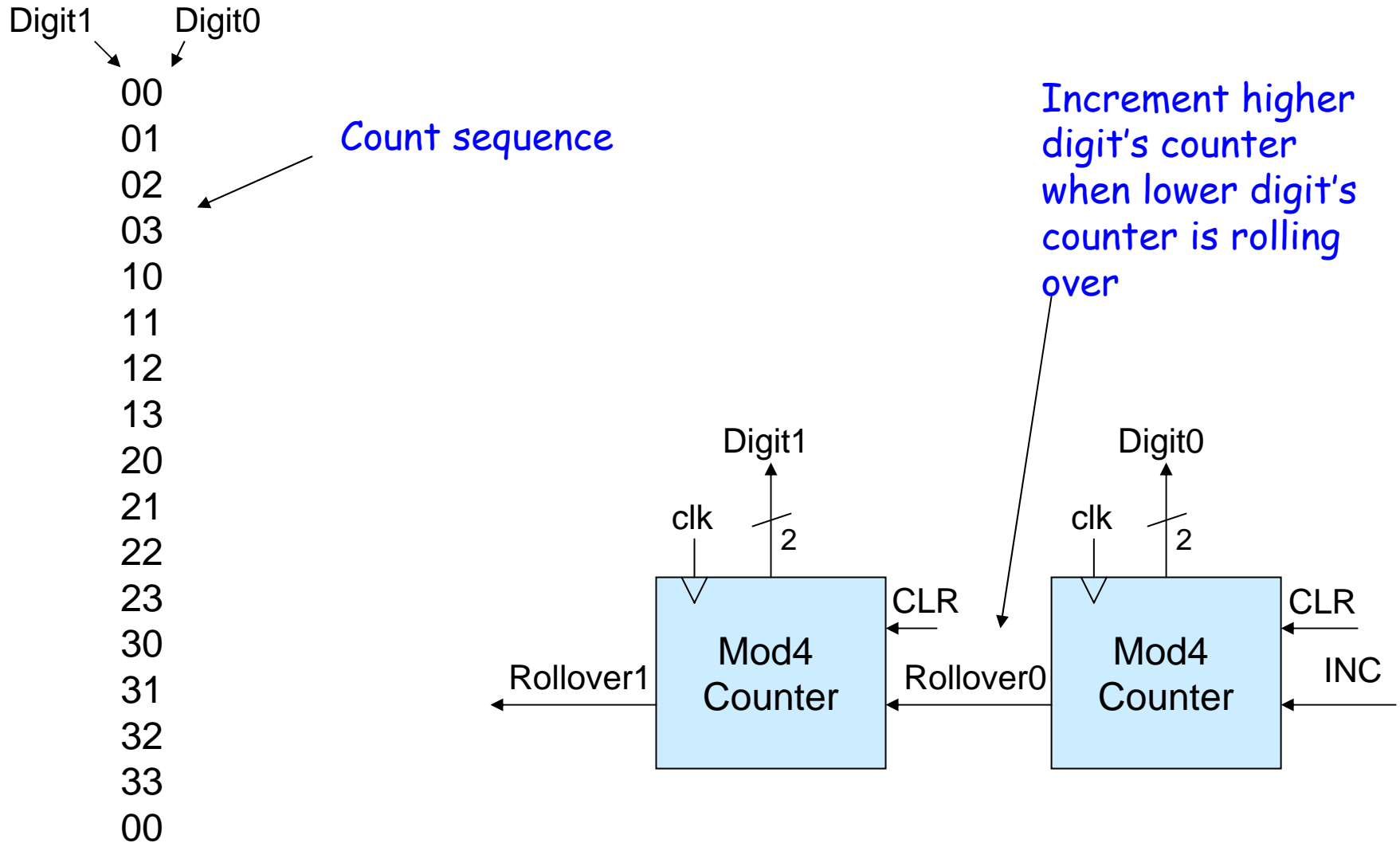


# 3 Digits' Worth

Could build a digital watch or clock circuit this way with Mod60 and Mod24 counters

Increment higher digit's counter when lower digit's counter is rolling over

 Can do this with any counter that has a Rollover output



# Cascading Counters

- A counter will increment only when
  - The counter below it is at its terminal count **and** it is being incremented
    - That is the definition of the Rollover signal
- Some people try to tie Rollover to the clk input of the next higher counter
  - Bad idea... Very bad idea...
  - Violates our Globally Synchronous policy
  - Doesn't work as intended

Sequence should be:

...-12-13-20-21-22-23-30-...

but we get:

...-12-23-20-21-22-33-30-...



?????

DO NOT TIE CLK

inputs on modules  
to anything but the  
clock !!!!!

Even if you *tinker* until  
you get the right count  
sequence, you must  
guarantee that signal  
Rollover0 has no hazards

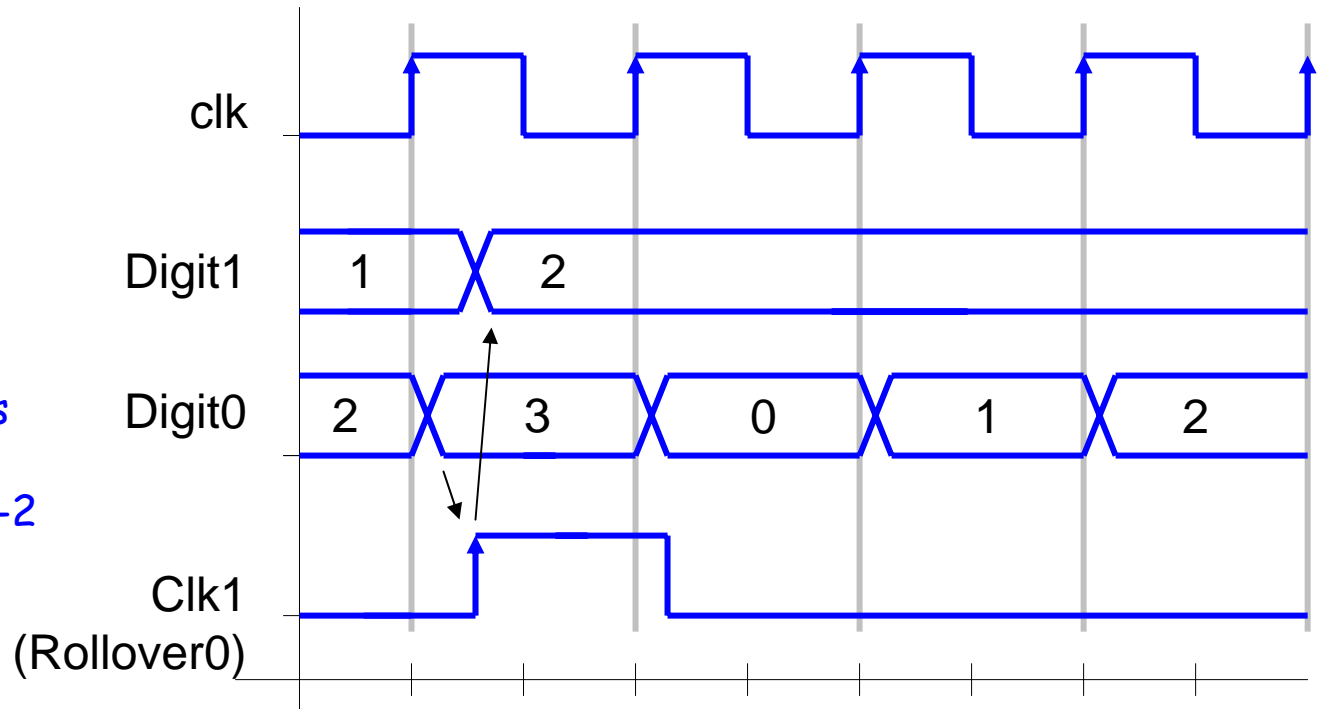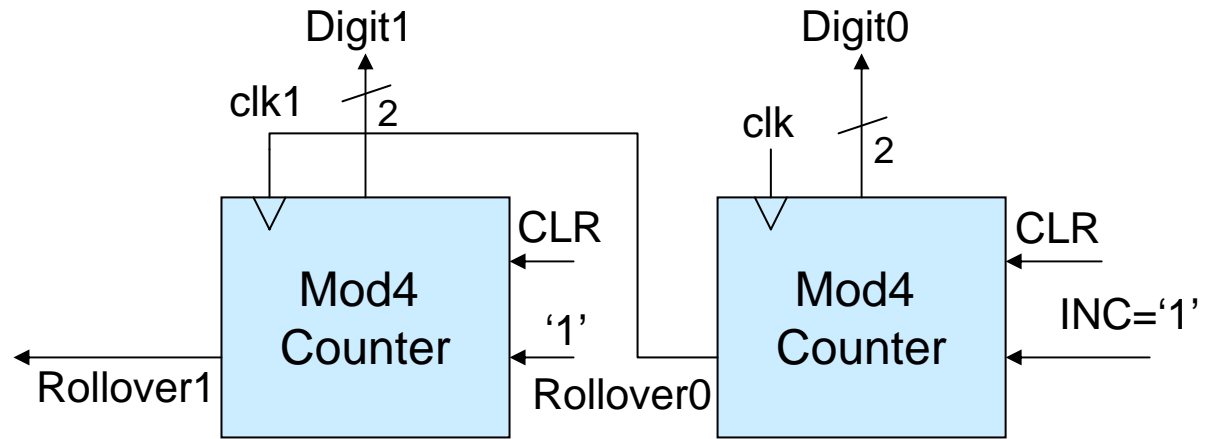Digit0 transition from 1-2  
makes this difficult if  
not impossible



Sequence should be:

...-12-13-20-21-22-23-30-...

but we get:

...-12-23-20-21-22-33-30-...



?????

DO NOT TIE CLK

inputs on modules  
to anything but the  
clock !!!!!

Even if you *tinker* until  
you get the right count  
sequence, you must  
guarantee that signal  
Rollover0 has no hazards

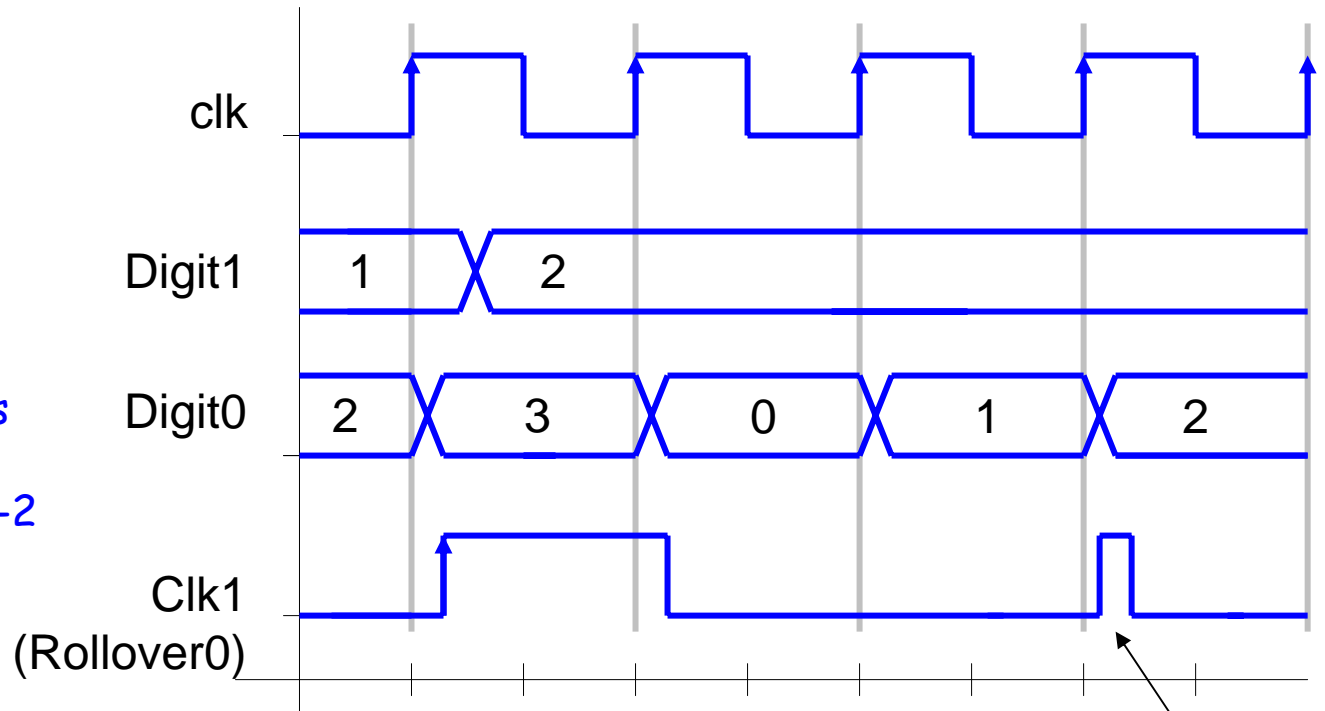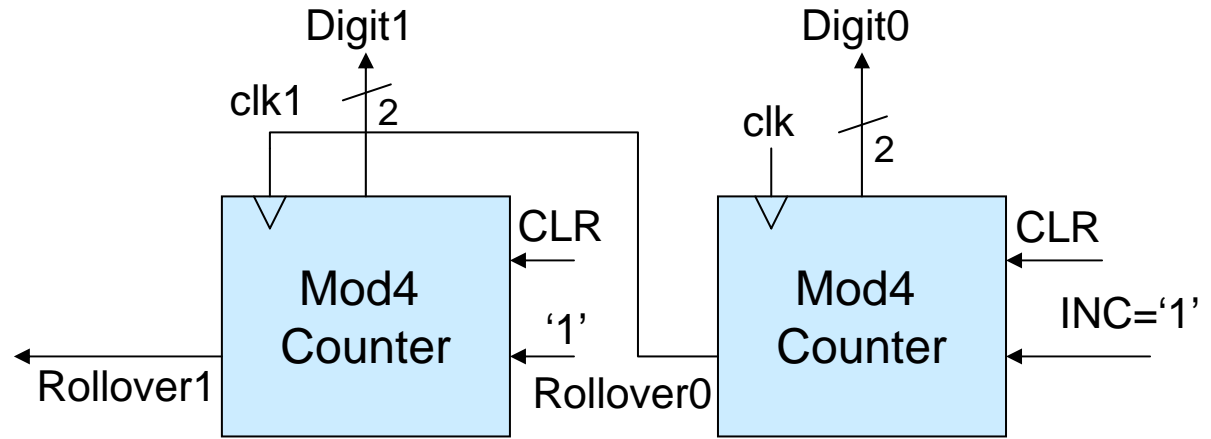Digit0 transition from 1-2  
makes this difficult if  
not impossible






# Ripple Counters

- When you tie a rollover-like signal to a clock on the next higher digit  $\Leftrightarrow$  ripple counter
- A ripple counter is an **ASYNCHRONOUS** counter
  - Transitions are not all synchronized to the clock
  - Different flip flops change at different times
  - Similar to gated clocks (seen earlier)
- Asynchronous circuits are an advanced topic
 
# Another Common Ripple Counter


Sequence is:

0000  
0001  
0010  
0011  
0100  
0101  
0110  
0111  
1000  
1001  
1010  
1011  
1100  
1101  
1110  
1111  
0000





So what is the problem?


# Timing Diagram

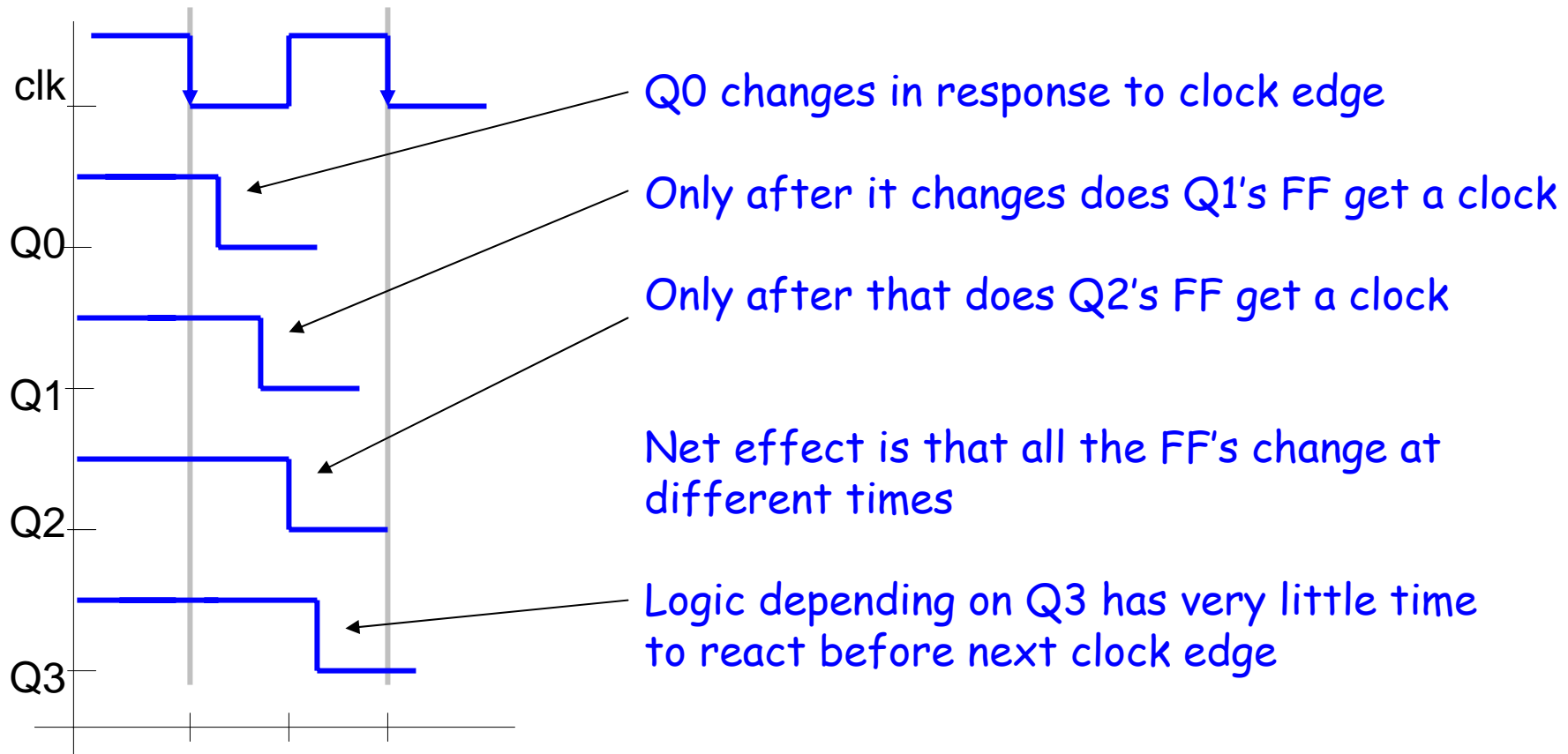

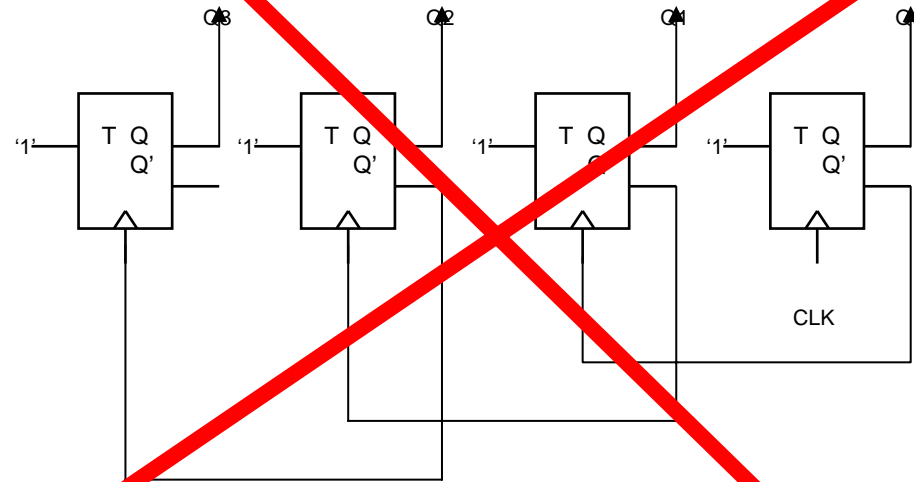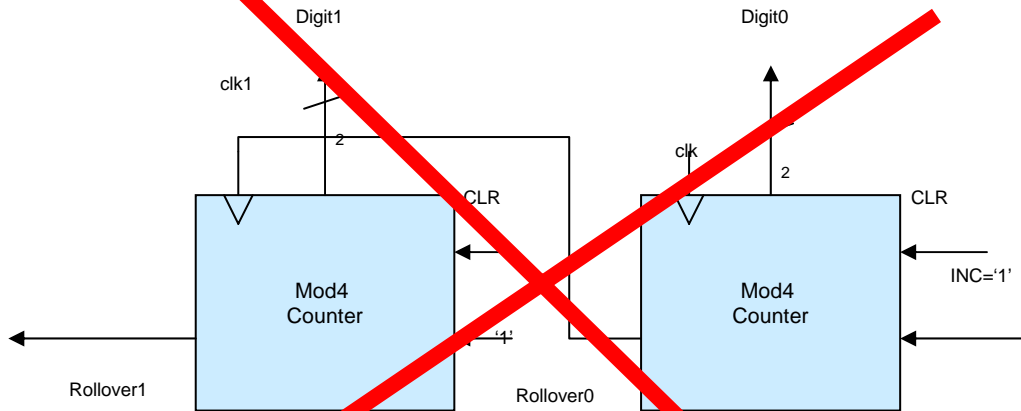
# Do Not Use Asynchronous or Ripple Counters




# Mod4 Counter

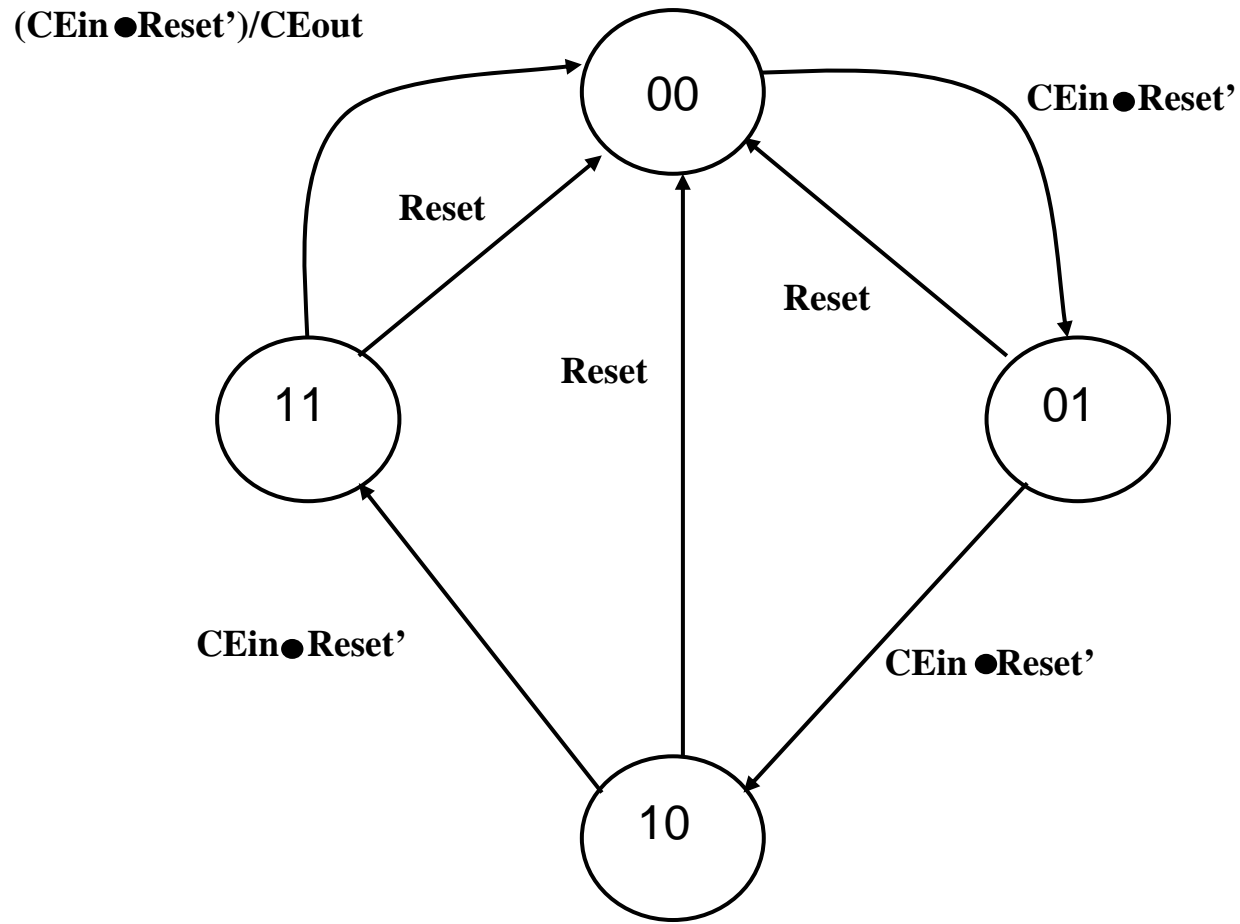

# The State Flip-Flop

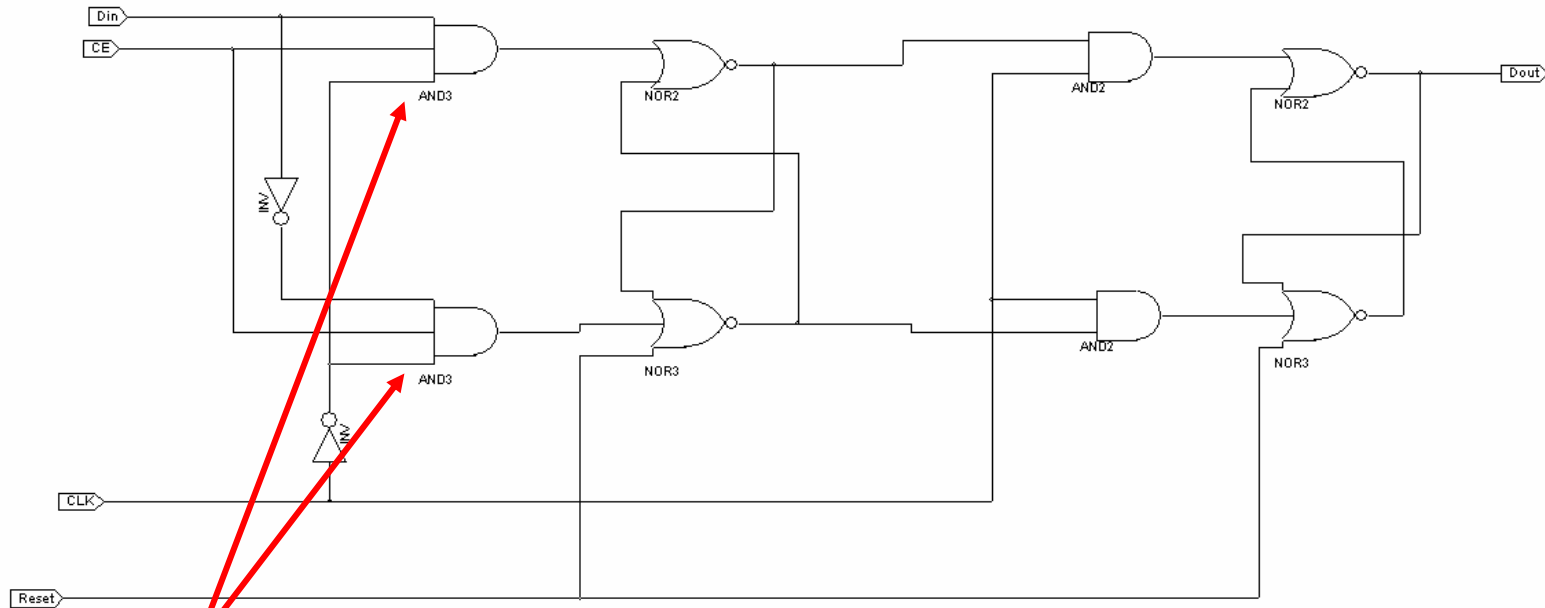

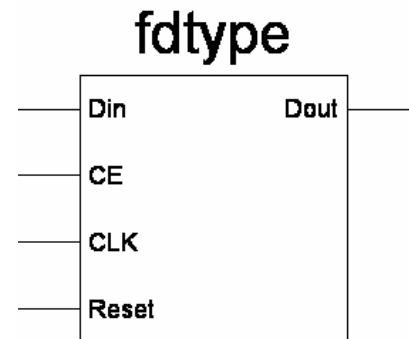**Note: Both CLK and CE are required to change the flip-flop**



# Mod4 Counter

CEin	Q1	Q0	N1	N0	CEout
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1

		Q1Q0		N1			
		00	01	11	10		
Ce							
0				1	1		
1		1			1		

$$N1 = Ce'Q_1 + Q_1Q_0' + CeQ_1'Q_0$$


		Q1Q0		N0			
		00	01	11	10		
Ce							
0			1	1			
1		1			1		

Note: No change when CEin=0

$$CEout = CeQ_1Q_0$$


$$N0 = Ce'Q_0 + CeQ_0'$$

# Mod4 Counter

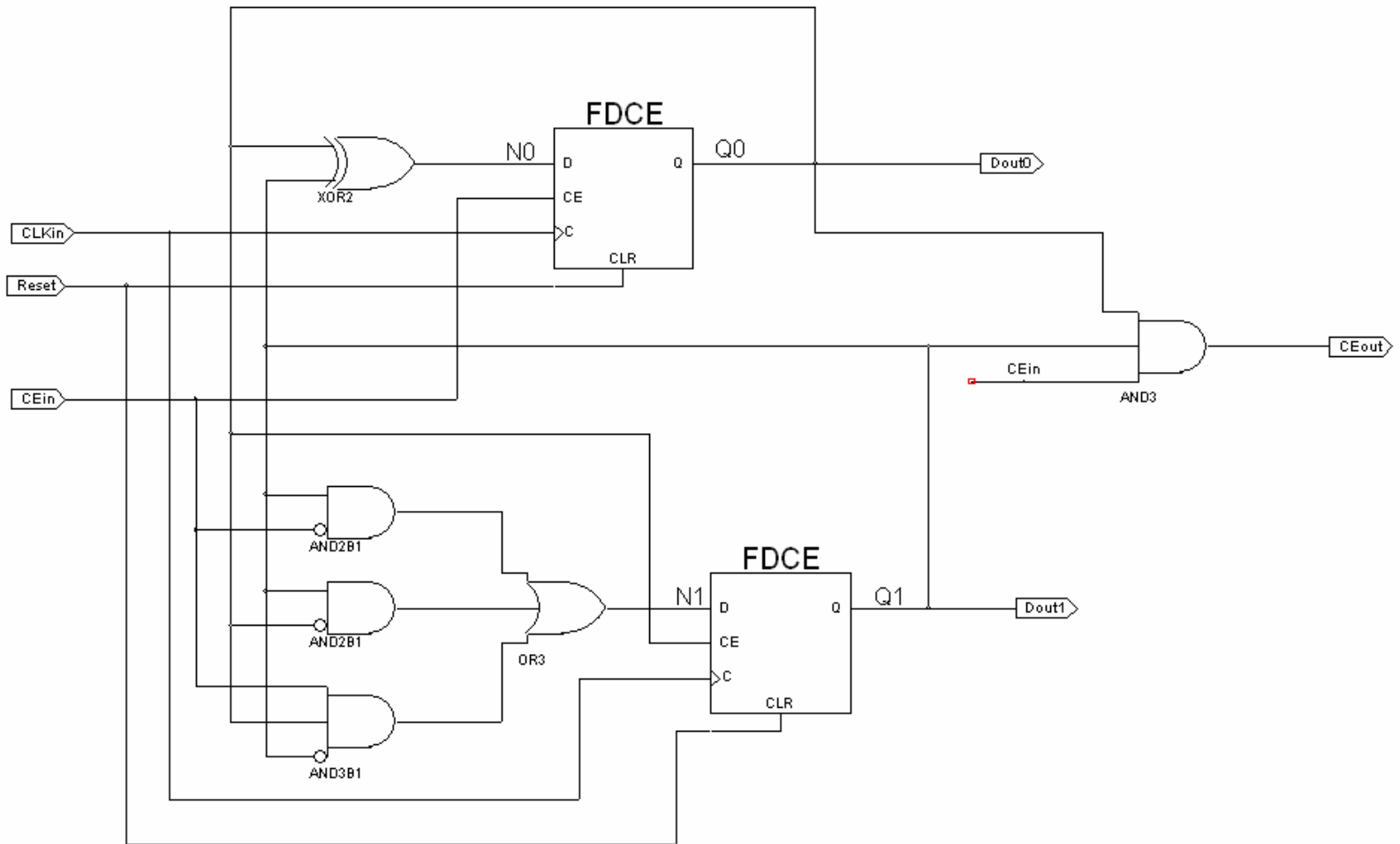




# Cascaded Ripple Counter

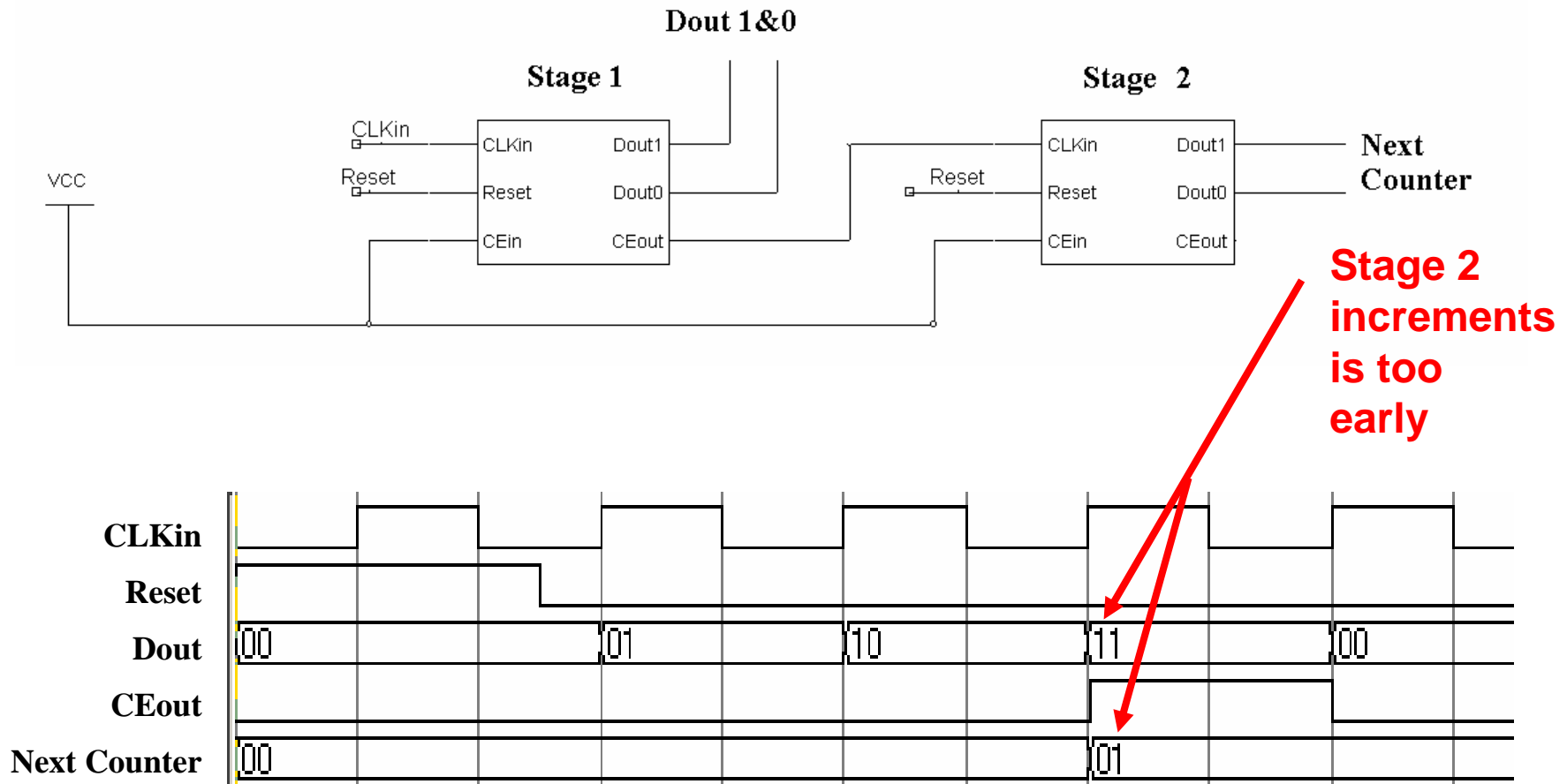

# Cascaded Ripple Counter

Why is Next Stage increment too early?

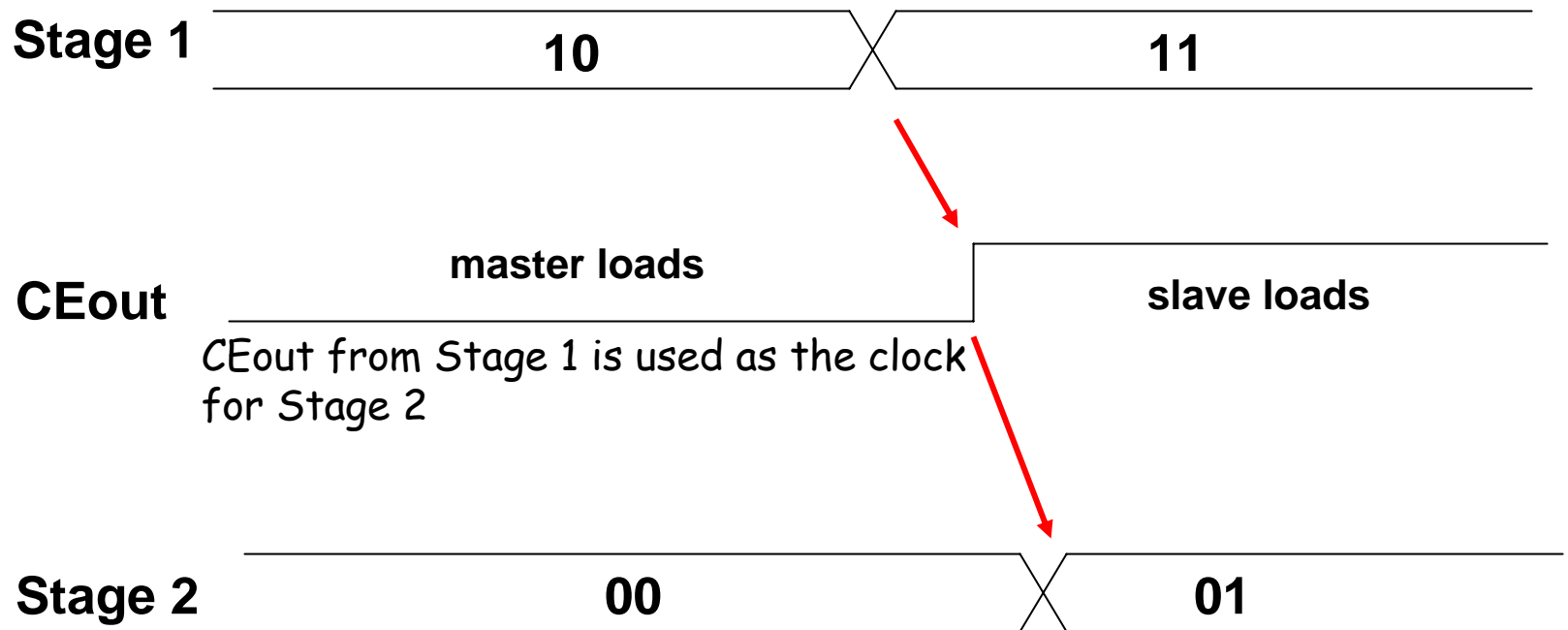


# Cascaded Ripple Counter


A Ripple Counter is an *ASYNCHRONOUS* counter since its transitions are **NOT** synchronized to the system clock.

In a *SYNCHRONOUS* counter, all stages transition with the system clock


# Cascaded Synchronous Counter

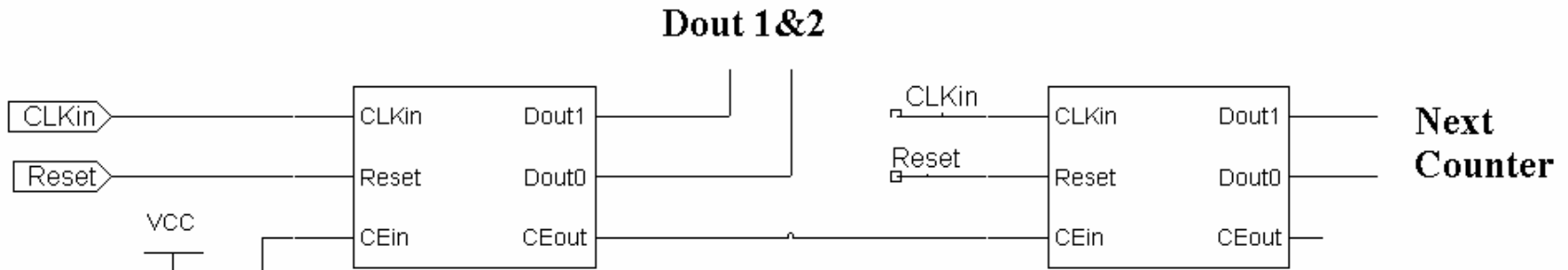

 Stage 2 is incremented at the correct time




# Cascaded Synchronous Counter

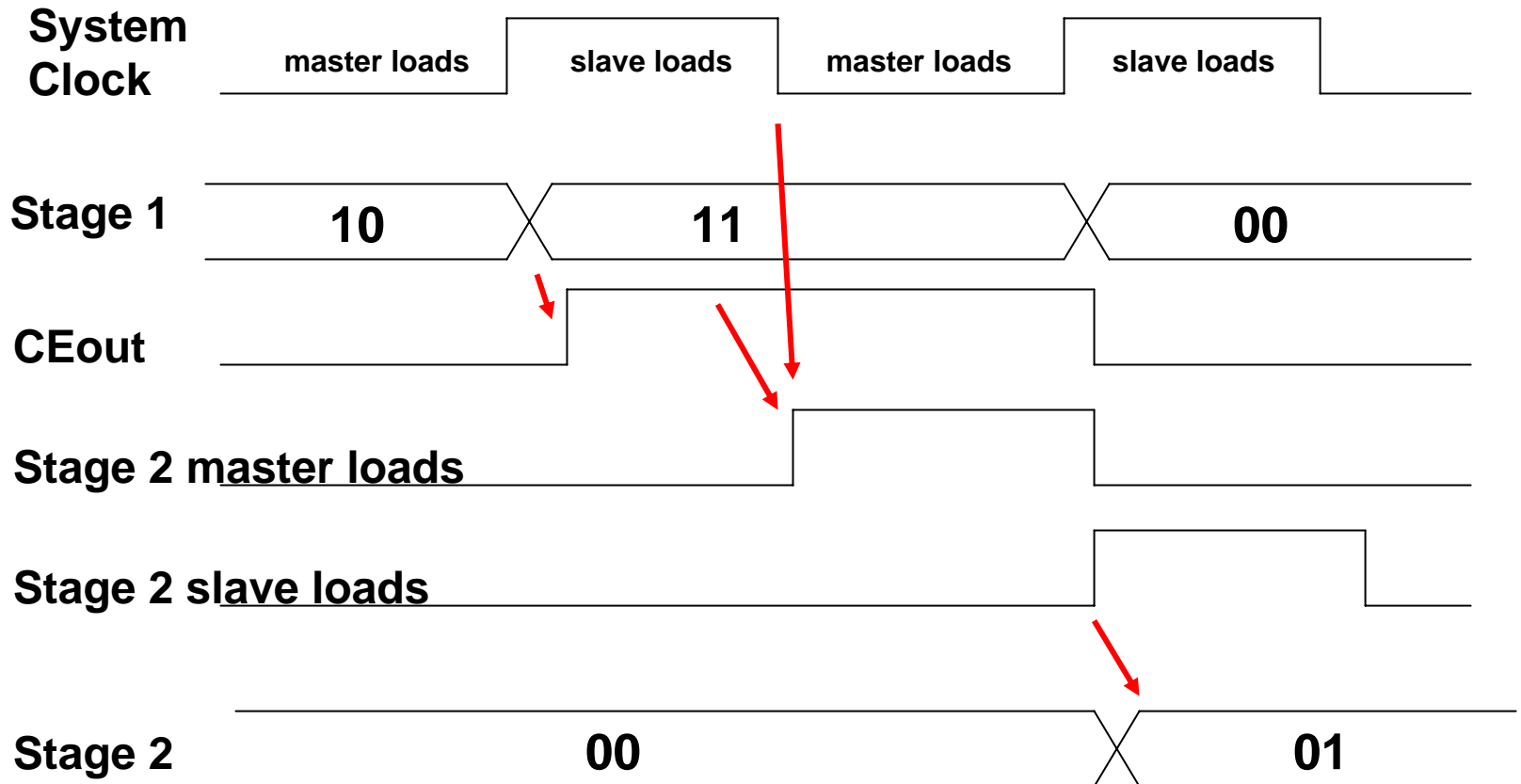

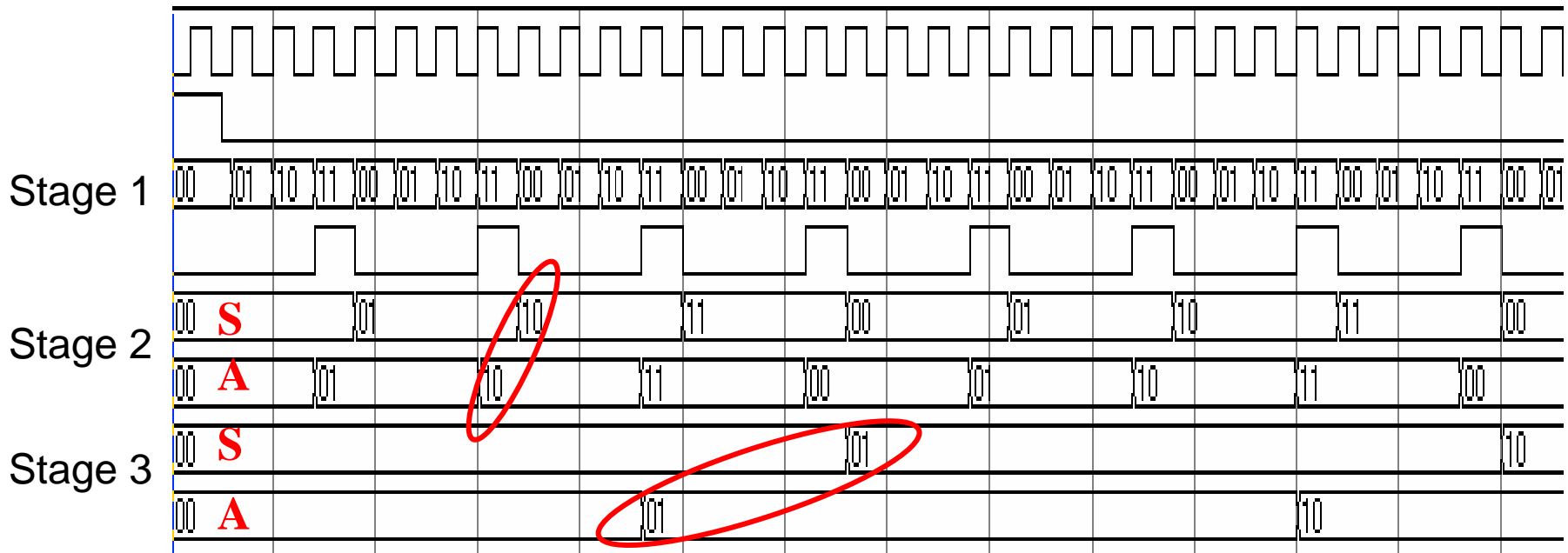
# Cascaded Counters

The more stages you add to the counter, the bigger the discrepancy between Synchronous and Asynchronous counters



# Cascaded Synchronous Counter


CEin controls when the S.M. can change

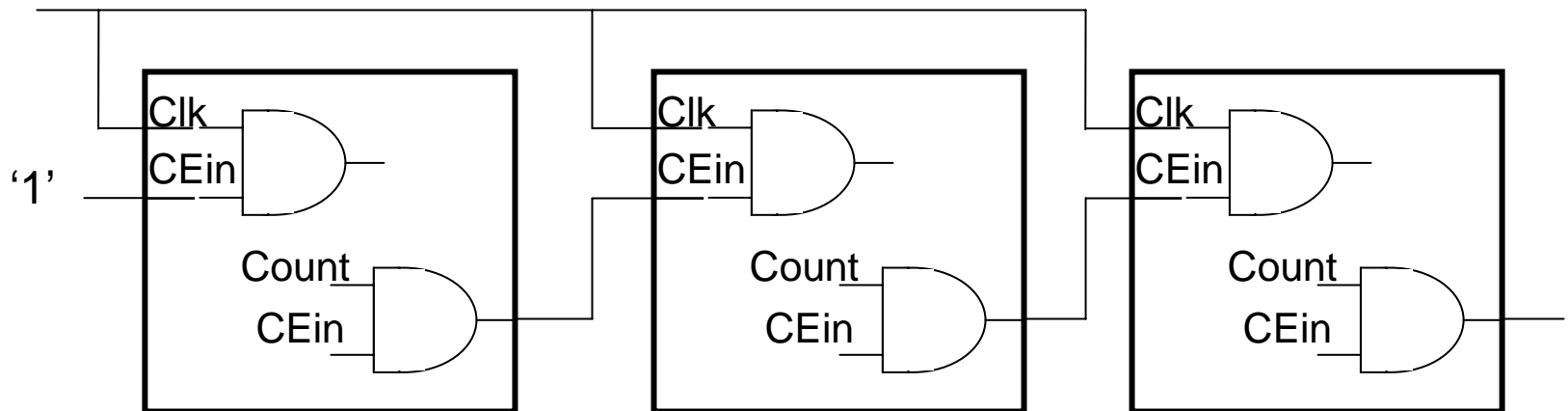

CEin also controls when the CEout will be generated
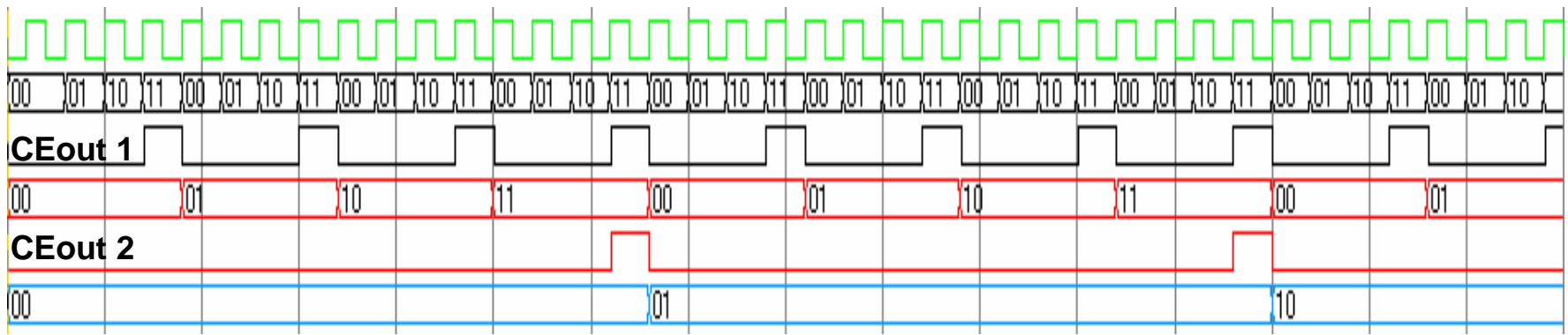
# Cascaded Synchronous Counter

Note that the  $CE_{out}$  from each stage is synchronized with the system clock *and* with each other. The stage transitions are all synchronized with the system clock



**Color Code:**

- Clock** (Green)
- Stage 1** (Black)
- Stage 2** (Red)
- Stage 3** (Blue)




# Cascaded Synchronous Counter

Lesson : Always use SYNCHRONOUS counters and timers.


# A Mod4 Counter

CLR	INC	Q1	Q0	N1	N0	RO
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	0	0	1
1	-	-	-	0	0	0

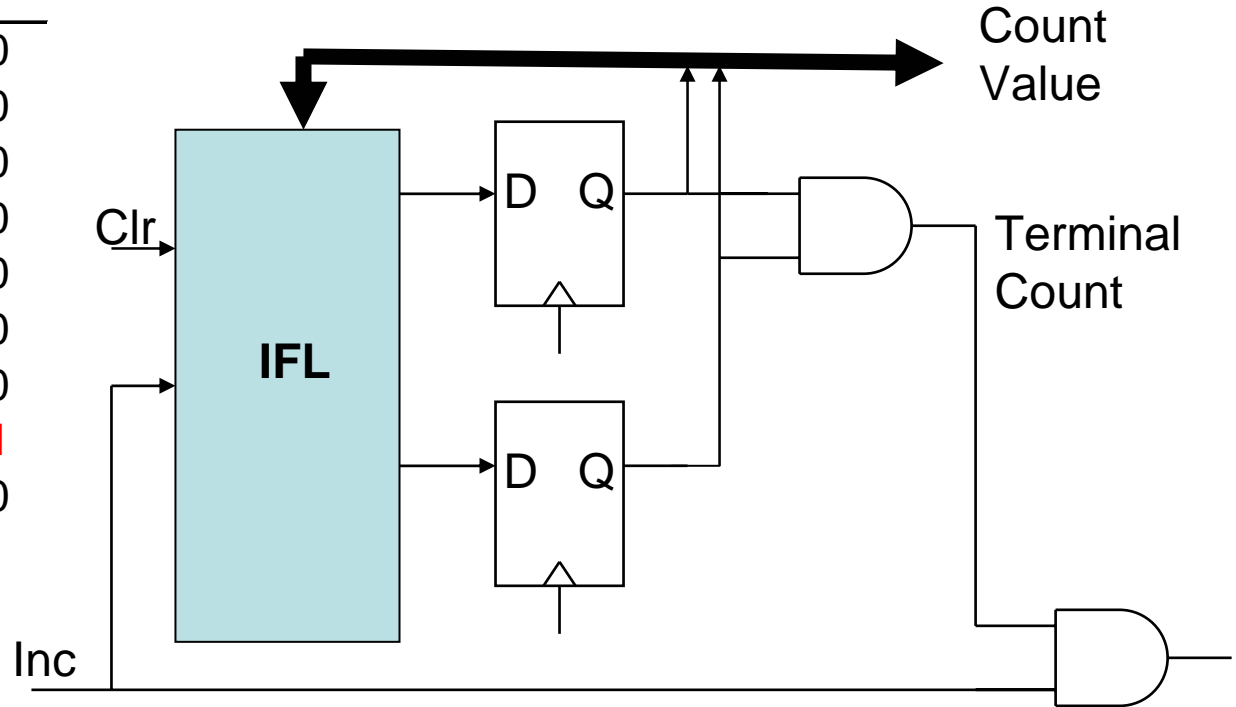


# A Mod4 Counter

CLR	INC	Q1	Q0	N1	N0	RO
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	0	0	1
1	-	-	-	0	0	0

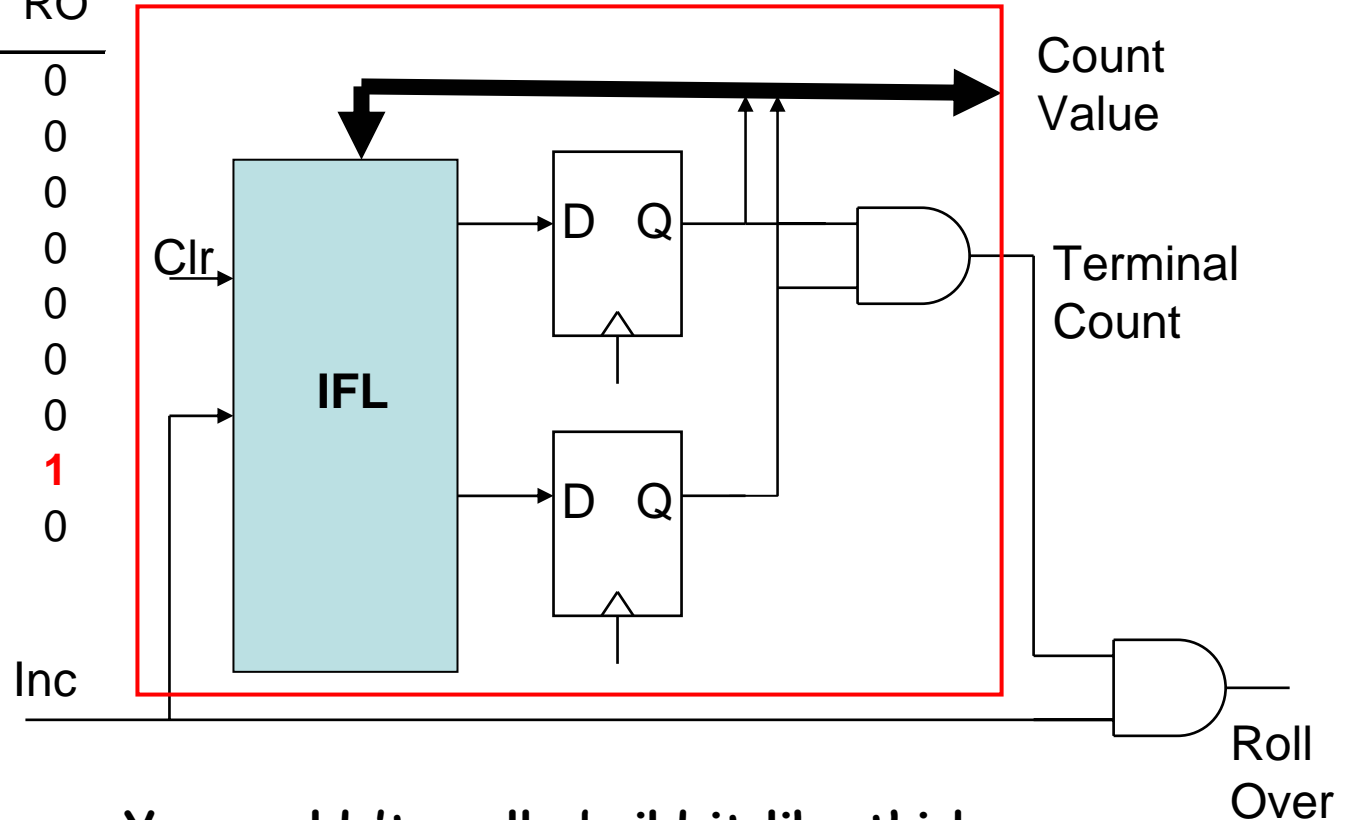


**You wouldn't really build it like this!**

# Cascaded Counters

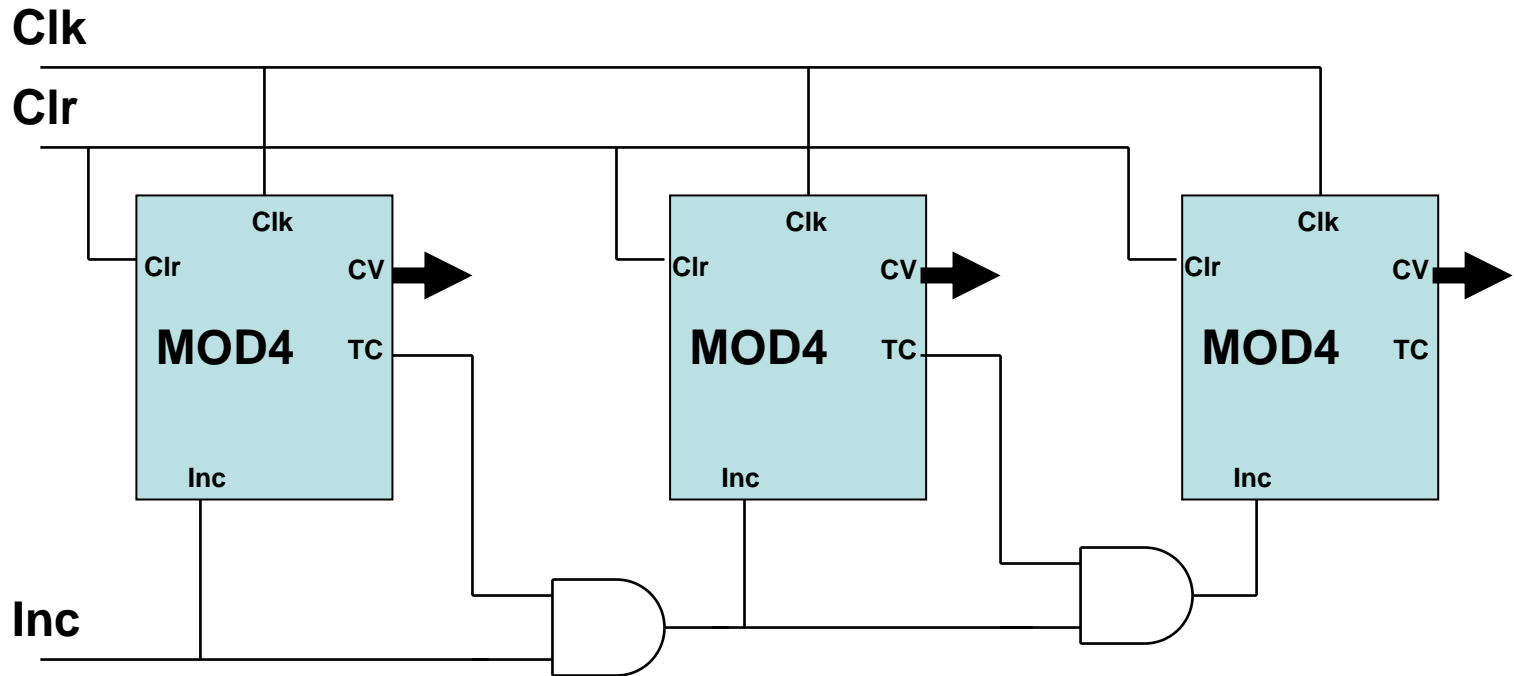


# Cascaded Counters

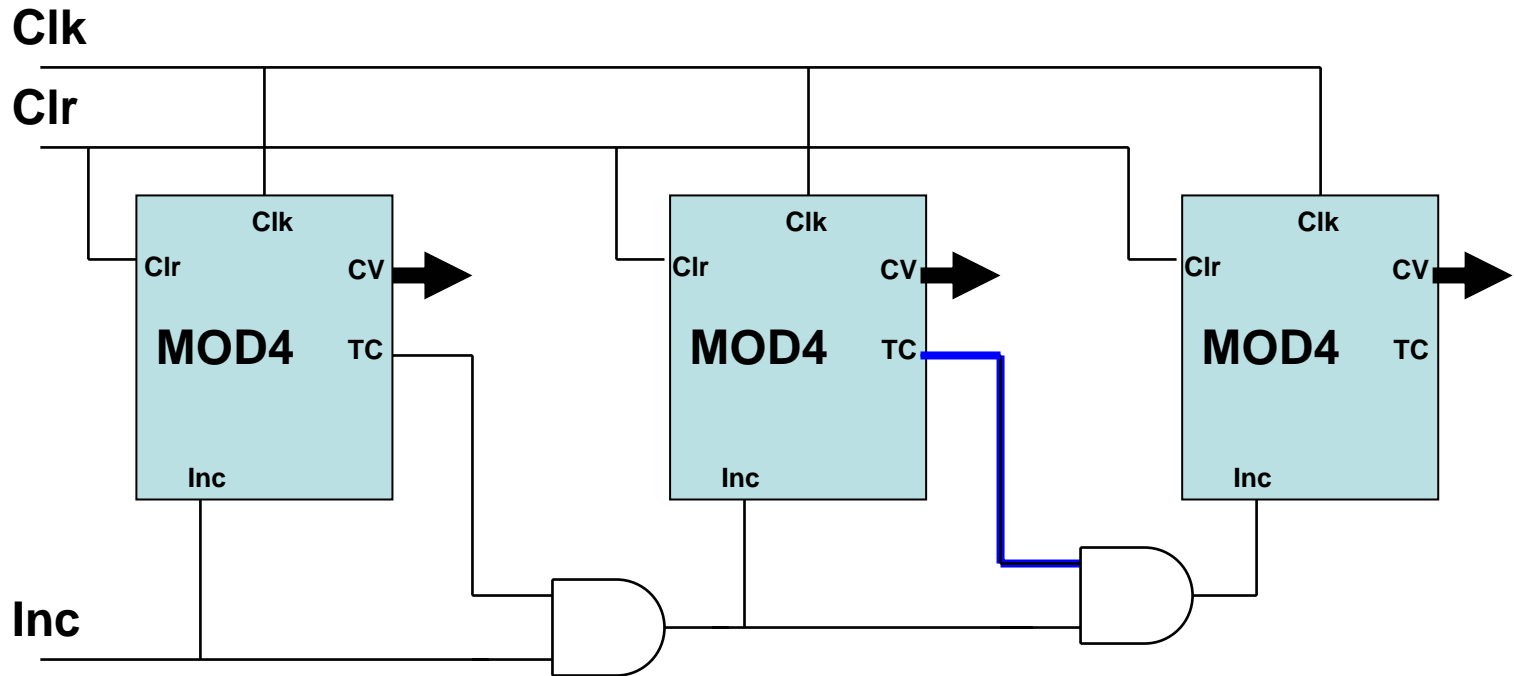


Assume that the second timer is already at the terminal count


# Cascaded Counters

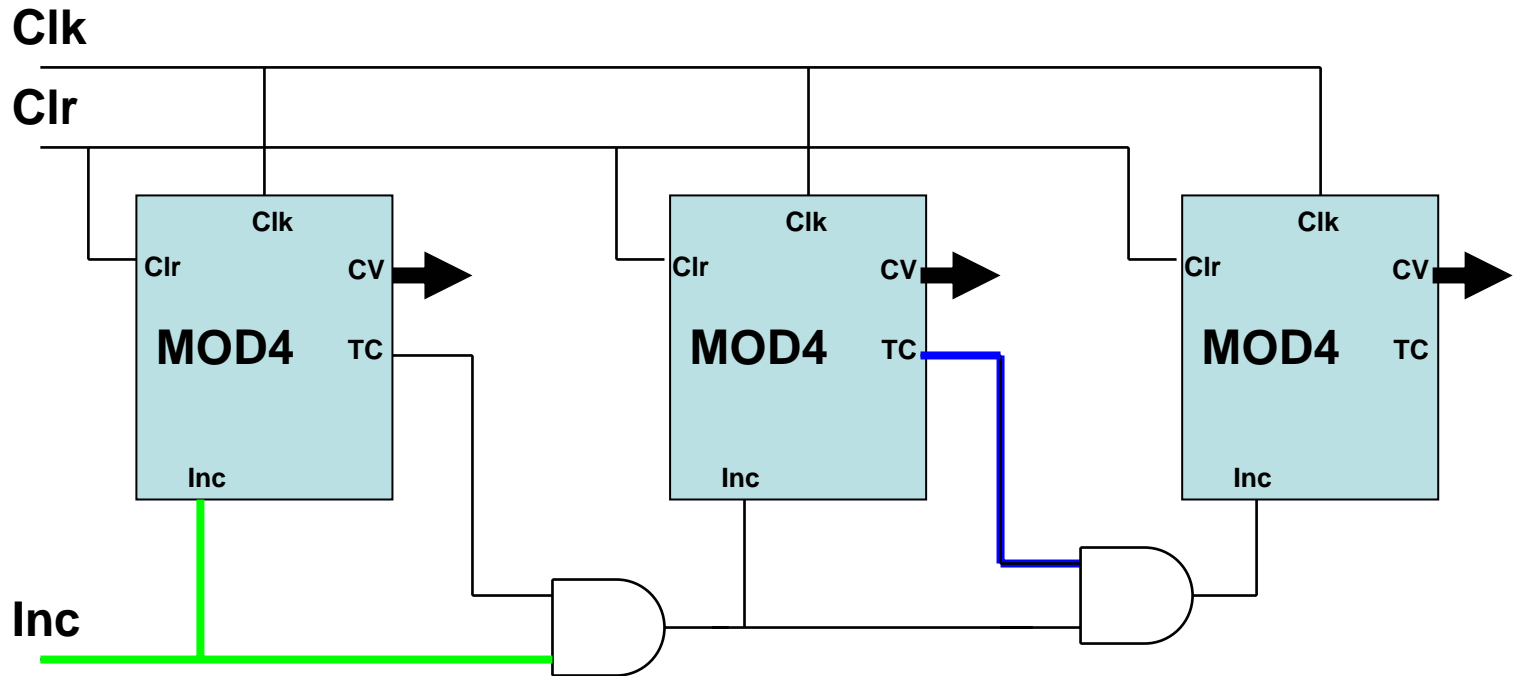

# Cascaded Counters

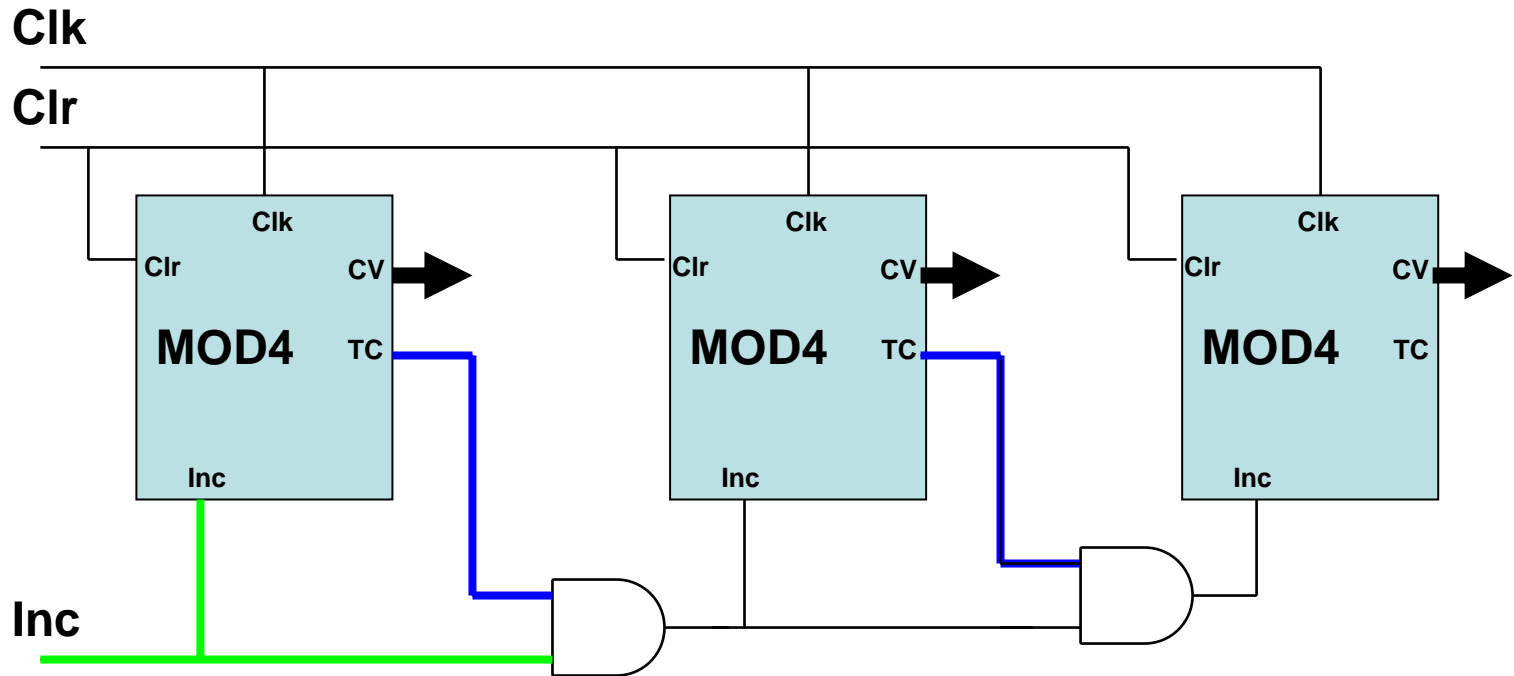


# Cascaded Counters

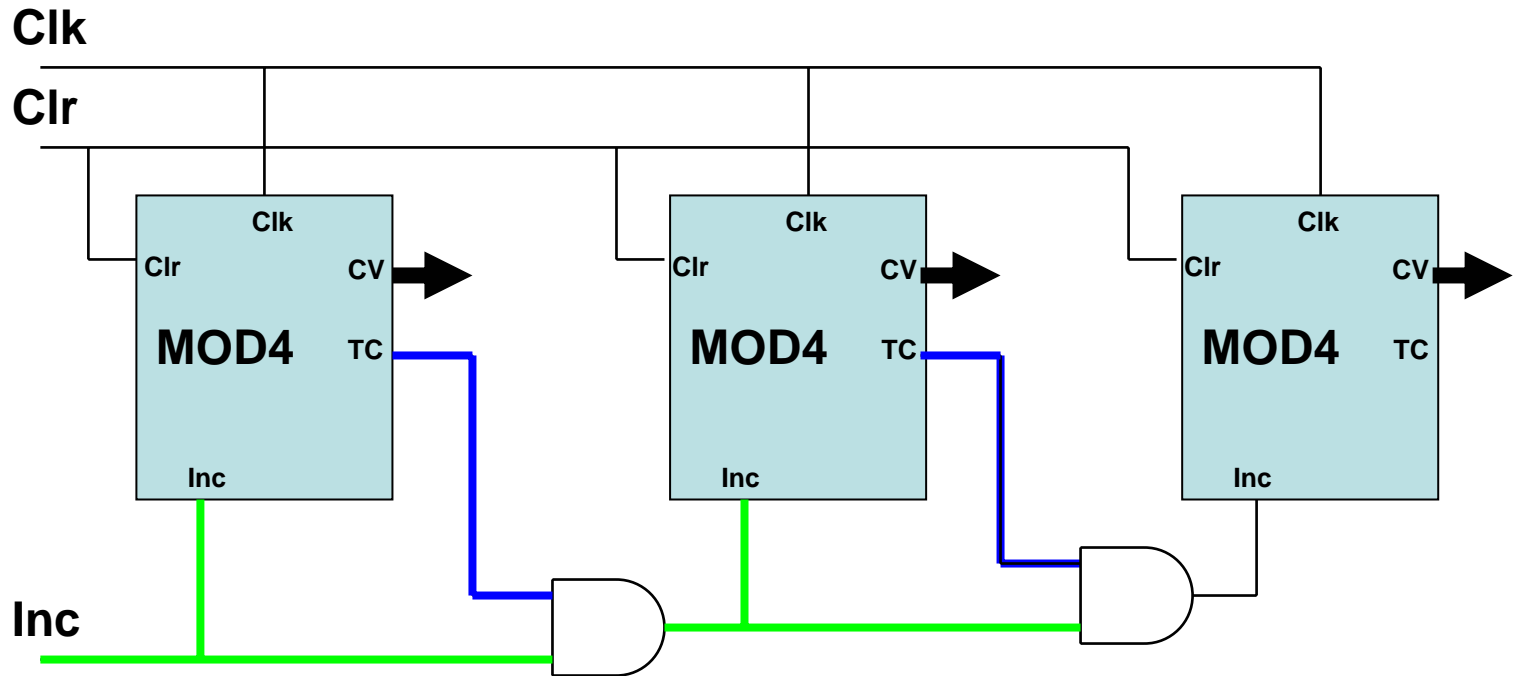






# Cascaded Counters

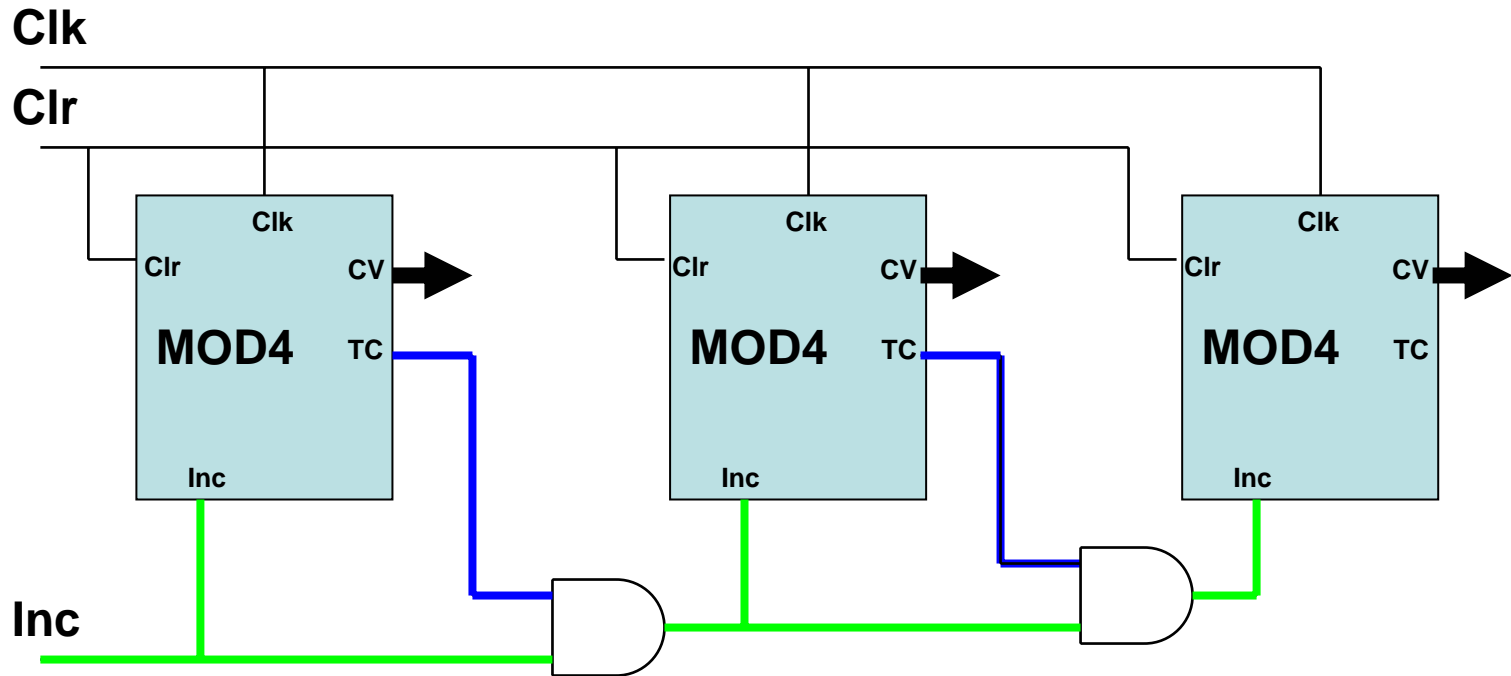

It looks like the Inc signal will ripple from counter to counter. Why is this any different from the toggle flip-flop example?

# A Mod4 Counter

The right way!

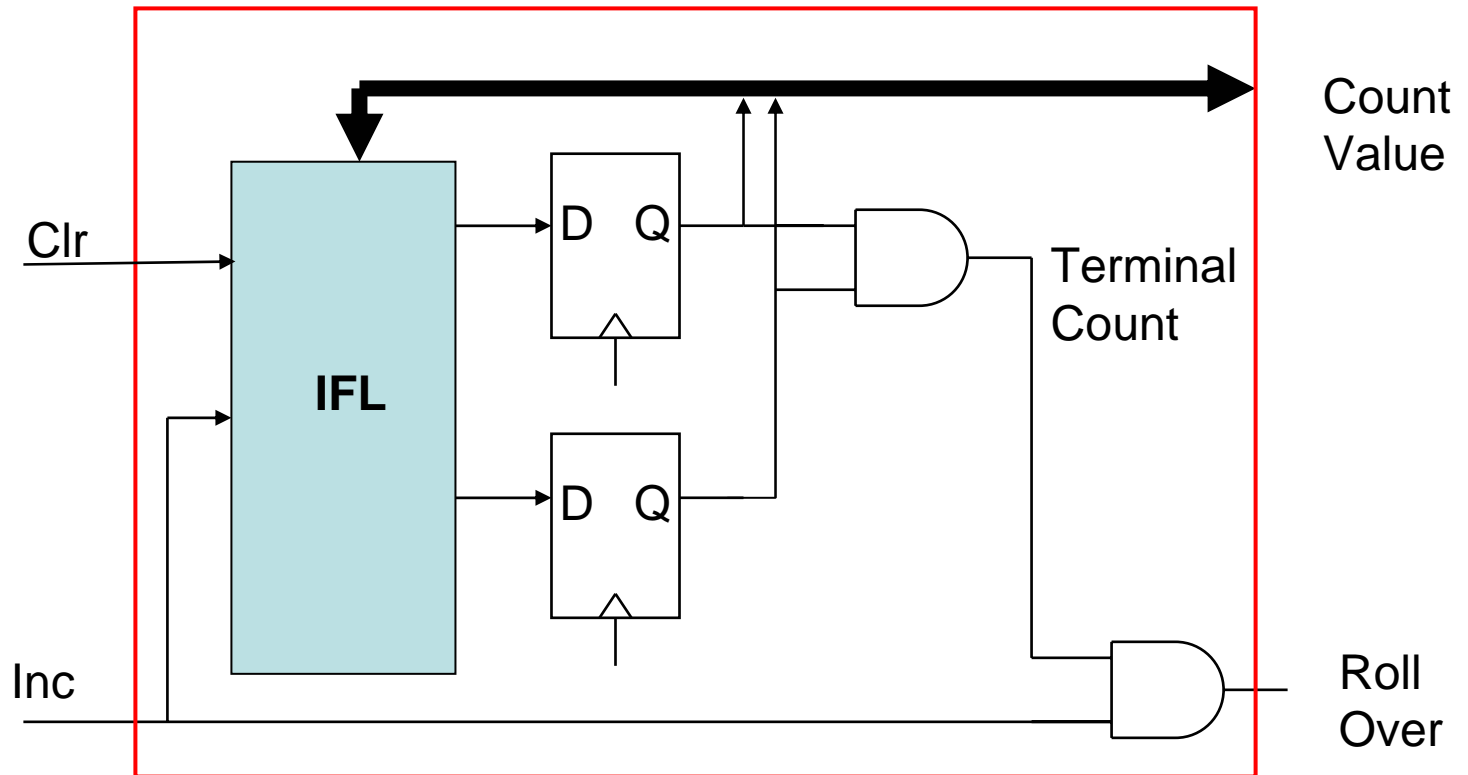

# A Mod4 Counter

