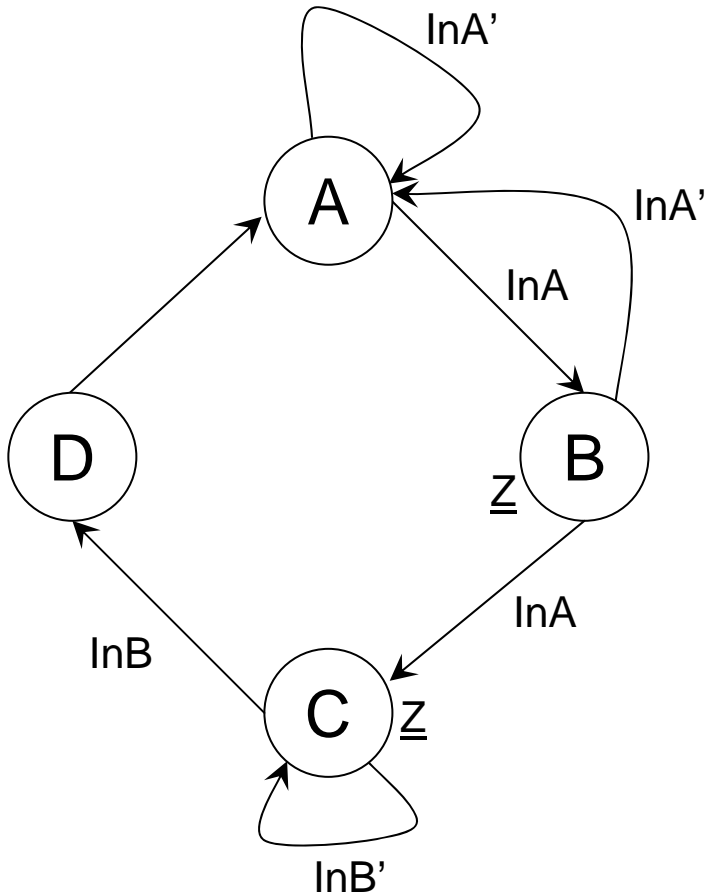


One-Hot Encoded Finite State Machines

Example State Machine




State A = 00
 State B = 01
 State C = 10
 State D = 11

InA	InB	CS	NS	Z
0	-	A	A	0
1	-	A	B	0
0	-	B	A	1
1	-	B	C	1
-	0	C	C	1
-	1	C	D	1
-	-	D	A	0



InA	InB	CS	NS	Z
0	-	00	00	0
1	-	00	01	0
0	-	01	00	1
1	-	01	10	1
-	0	10	10	1
-	1	10	11	1
-	-	11	00	0


Example Machine Implementation

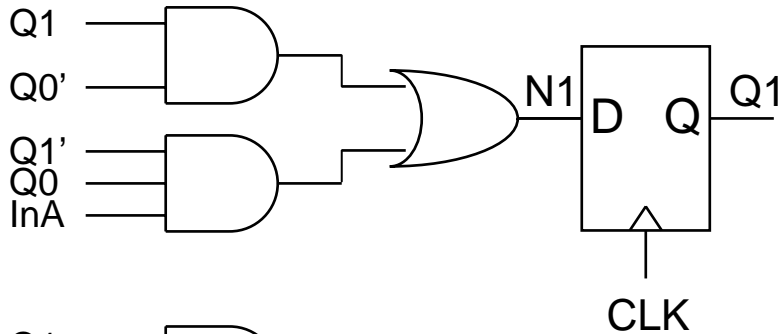


$$N1 = Q1 \cdot Q0' + Q1' \cdot Q0 \cdot \text{InA}$$

$$N0 = Q1 \cdot Q0' \cdot \text{InB} + Q1' \cdot Q0' \cdot \text{InA}$$

$$Z = Q1' \cdot Q0 + Q1 \cdot Q0'$$

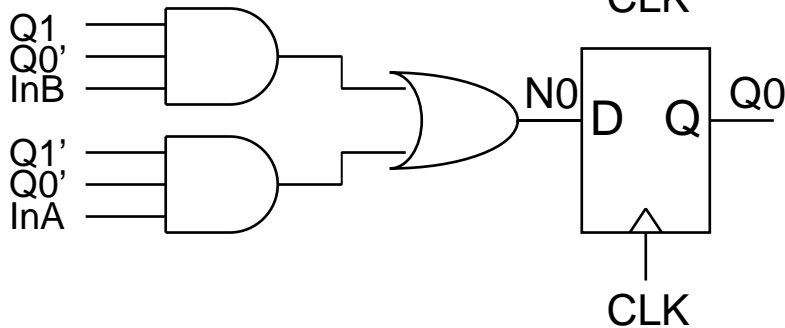

9 gates
21 gate inputs

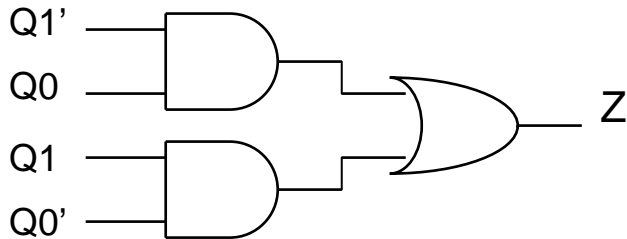

Choose a Different Encoding

- A=1000, B=0100, C=0010, D=0001

InA	InB	CS	NS	Z
0	-	1000	1000	0
1	-	1000	0100	0
0	-	0100	1000	1
1	-	0100	0010	1
-	0	0010	0010	1
-	1	0010	0001	1
-	-	0001	1000	0

This is called a *one-hot* encoding.

Only one state bit is on at a time

InA	InB	CS	NS	Z
0	-	1---	1000	0
1	-	1---	0100	0
0	-	-1--	1000	1
1	-	-1--	0010	1
-	0	--1-	0010	1
-	1	--1-	0001	1
-	-	---1	1000	0

Because of the state encodings, there are many illegal states.

This TT with all these input don't cares is the result

One-Hot Encoding Results

- Will require 4 flip flops
 - One per state
 - Call the current state bits A, B, C, and D
 - Call the next state bits NA, NB, NC, and ND

By inspection we see:


$$NA = A \cdot \text{InA}' + B \cdot \text{InA}' + D$$

$$NB = A \cdot \text{InA}$$






$$NC = B \cdot \text{InA} + C \cdot \text{InB}'$$

$$ND = C \cdot \text{InB}$$

$$Z = B + C$$

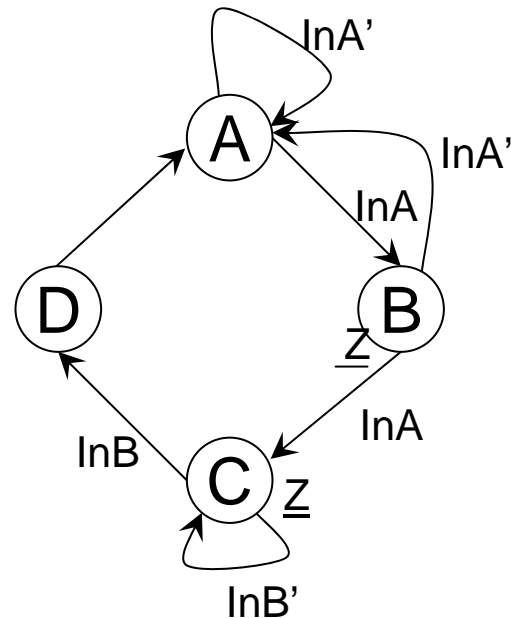

One-Hot Implementation

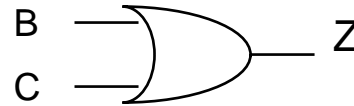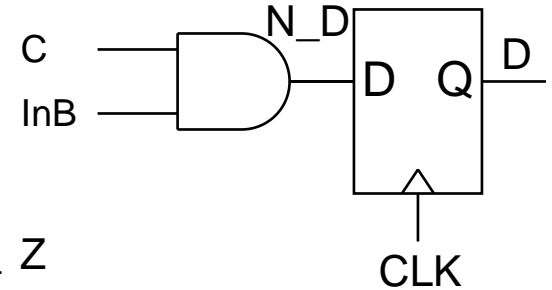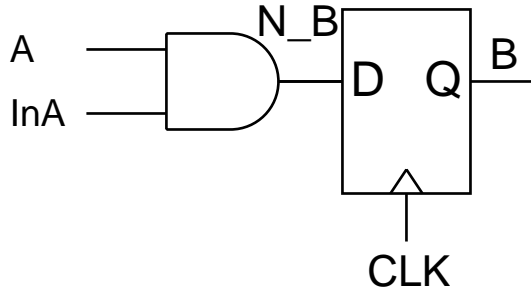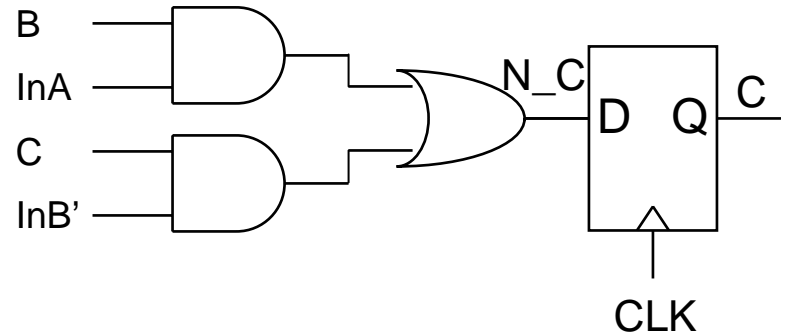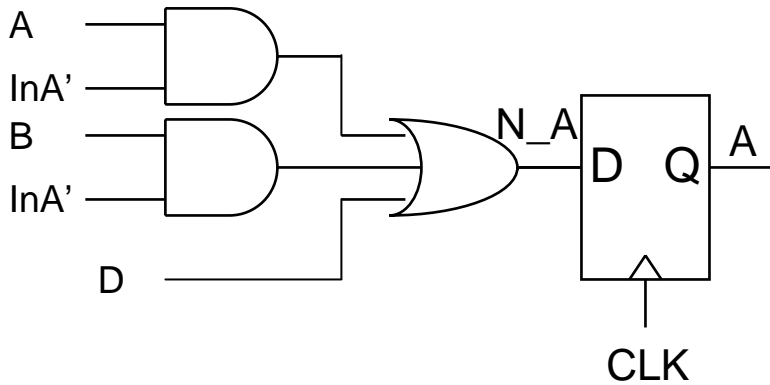


9 gates
19 gate inputs

One-Hot - Observations

- Choosing a one-hot encoding results in many, many don't cares in transition table
- Minimization results in simpler IFL and OFL
- Can do one-hot design by inspection
 - *without using transition tables...*


Another One-Hot Example

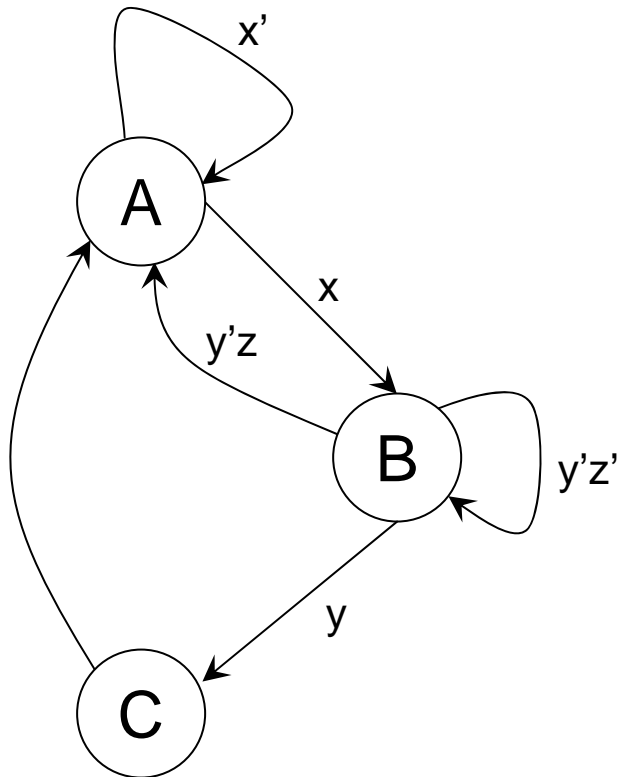

State	Encoding
A	100
B	010
C	001

State Encoding and Structure

State	Encoding
A	100
B	010
C	001

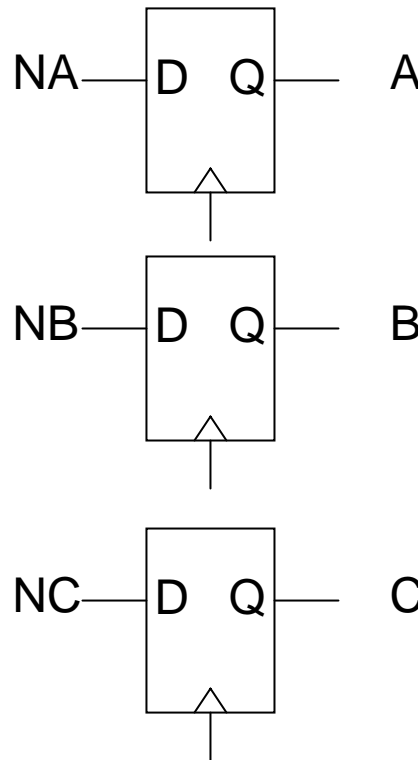


With one-hot encoding, each state has its own flip flop.

Note: 'A' is the name of a state. It is also the name of the wire coming out from the flip flop for state 'A'.

The same holds true for states 'B' and 'C'

One-Hot Encodings By Inspection

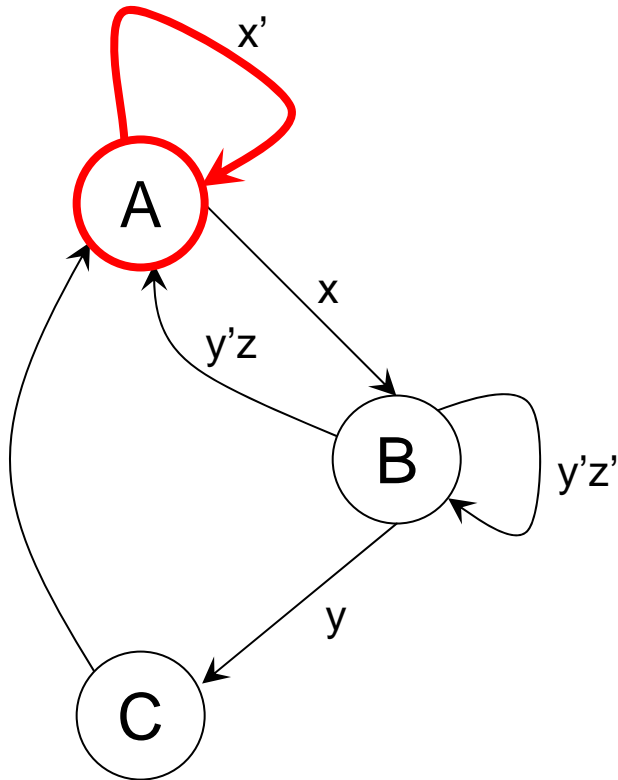


When is A the next state?

Look at the arcs entering state A

$$NA = A \cdot x' + B \cdot y'z + C$$

One-Hot Encodings By Inspection

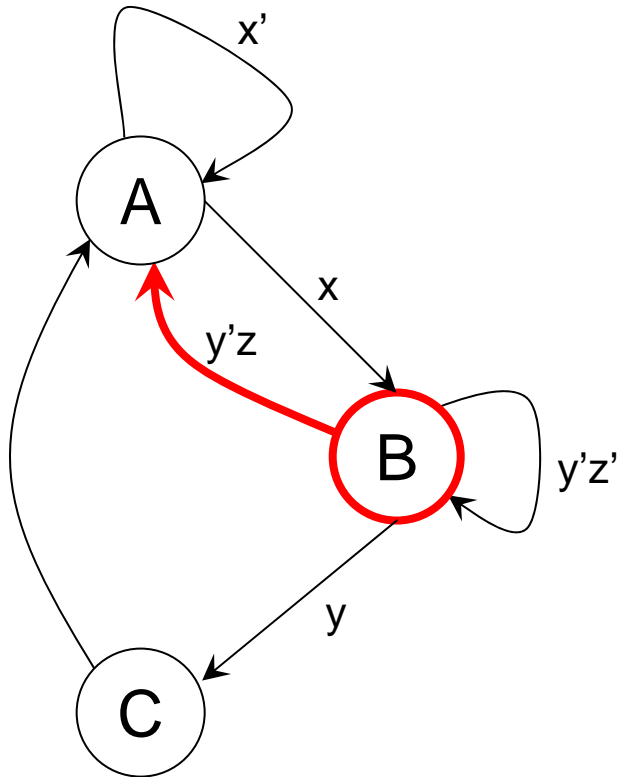


When is A the next state?

Look at the arcs entering state A

$$NA = A \cdot x' + B \cdot y'z + C$$

One-Hot Encodings By Inspection

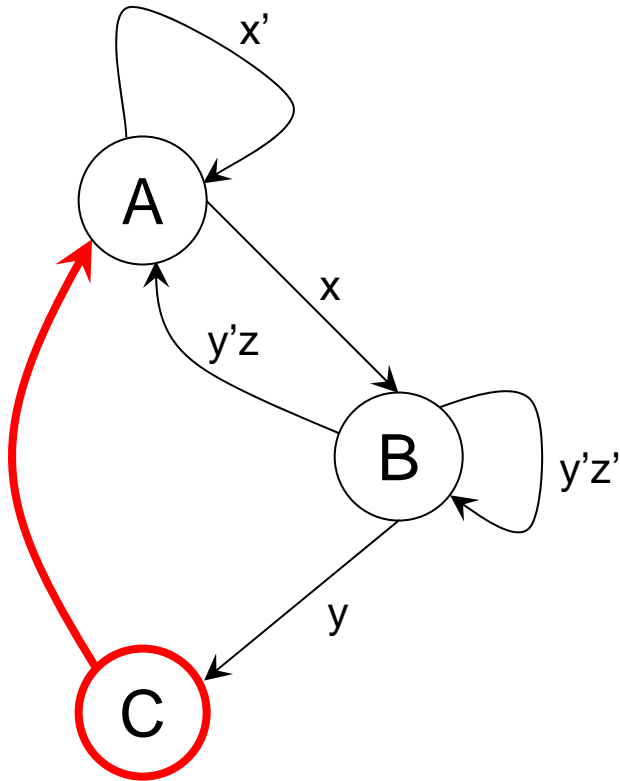


When is A the next state?

Look at the arcs entering state A

$$NA = A \cdot x' + B \cdot y'z + C$$

One-Hot Encodings By Inspection

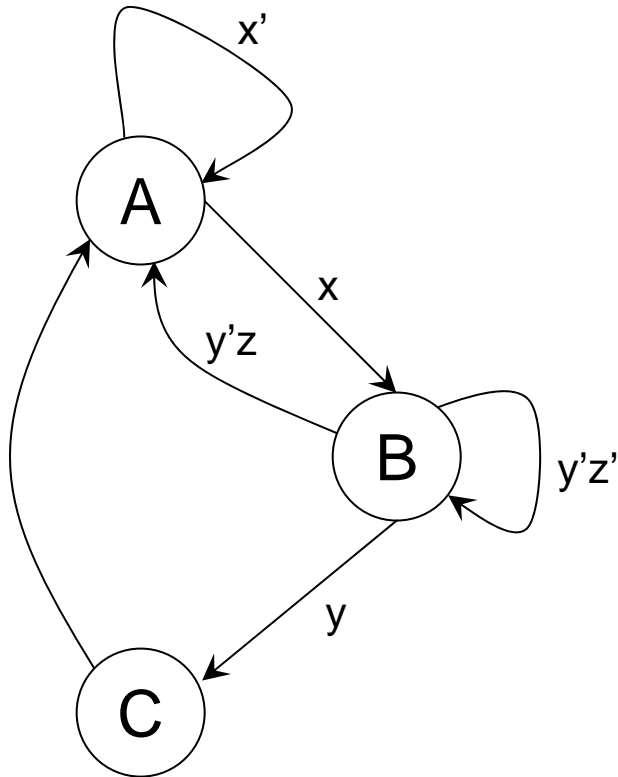

When is A the next state?

Look at the arcs entering state A


$$NA = A \cdot x' + B \cdot y'z + C$$

Similar reasoning leads to:

$$NB = A \cdot x + B \cdot y'z'$$

$$NC = B \cdot y$$


The Key Lock Problem - One-Hot Version

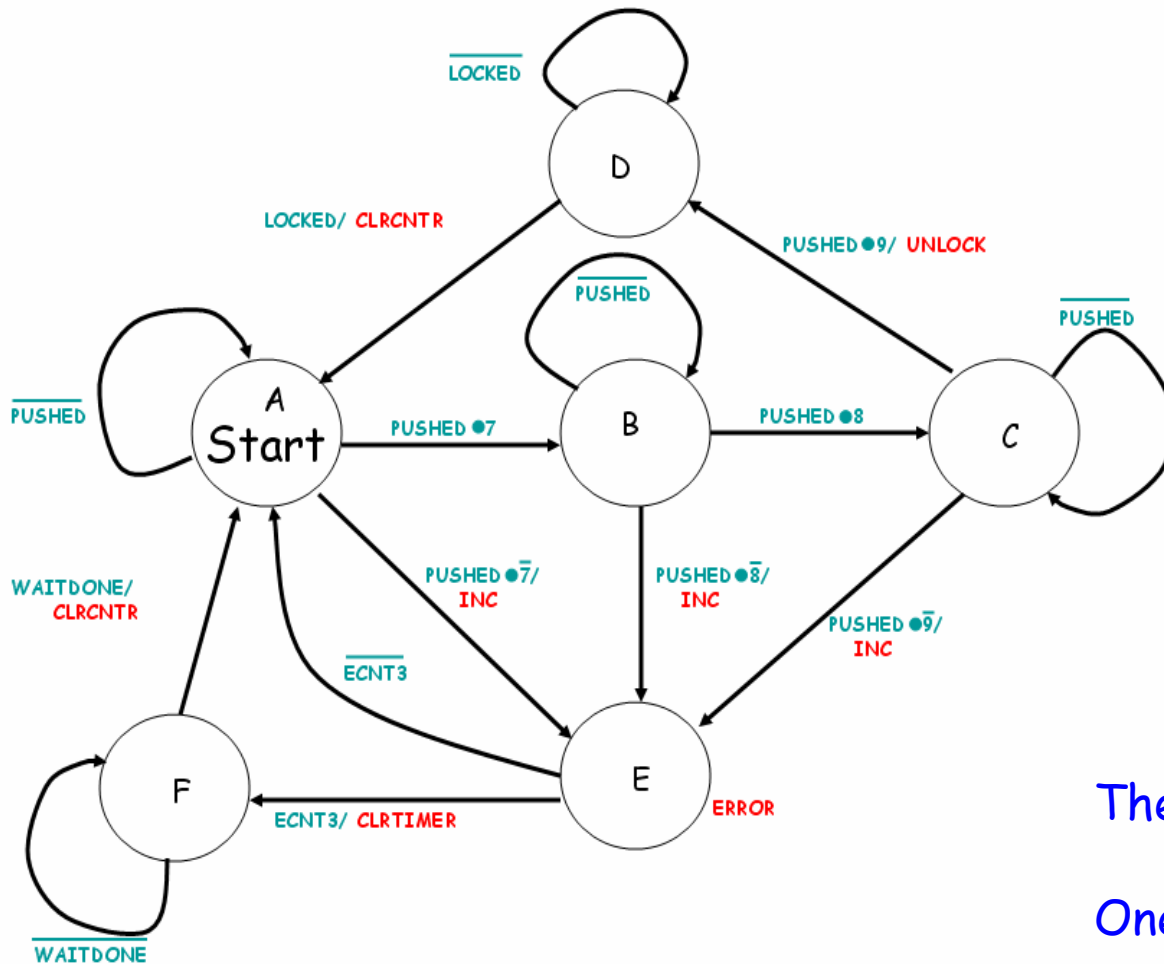


There will be 6 flip flops

One for each state

Key Lock Input Forming Logic

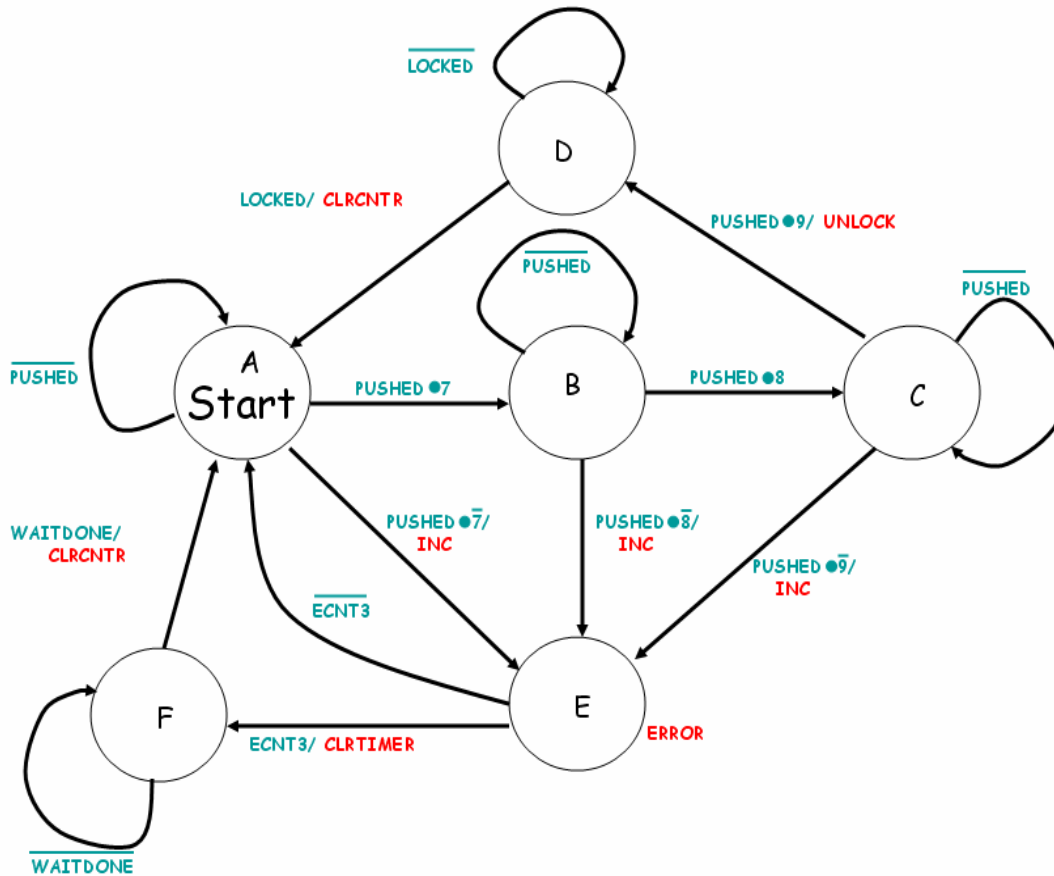


Key Lock Input Forming Logic

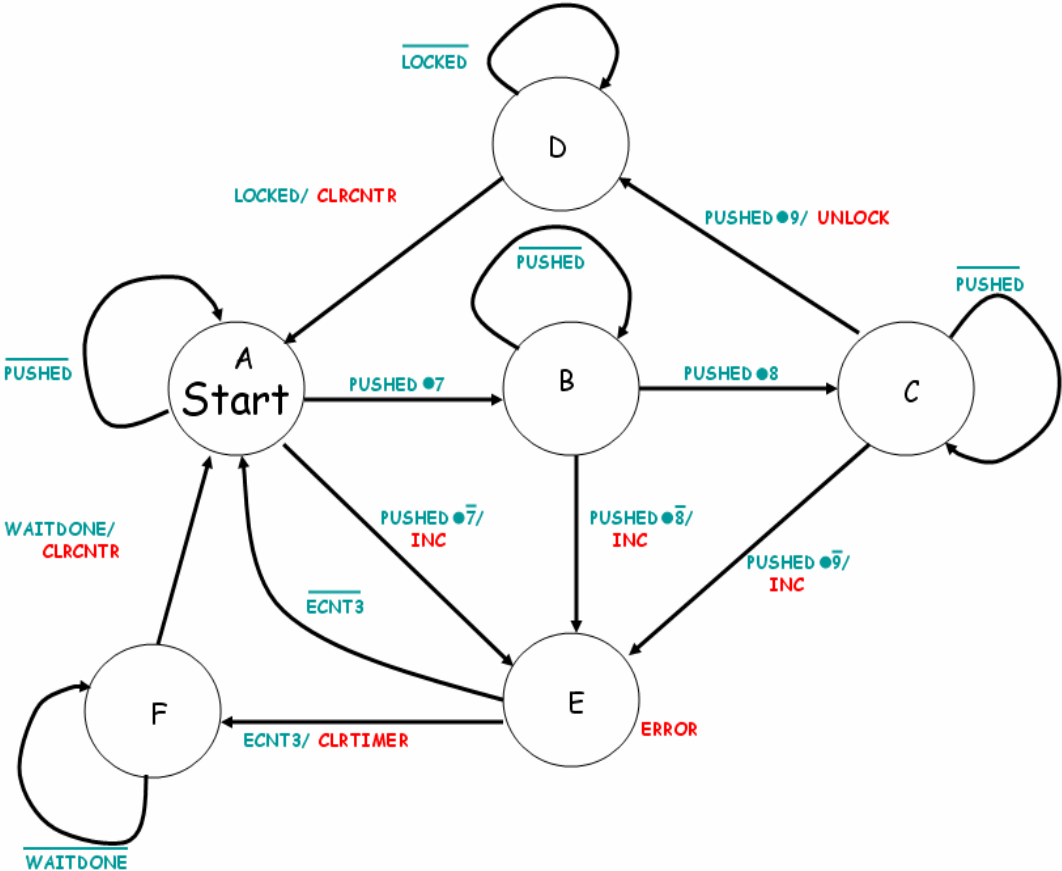

$$\begin{aligned}
 A+ = & (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) \\
 & + (\text{WAITDONE} \bullet F) \\
 & + (\text{LOCKED} \bullet D)
 \end{aligned}$$


Key Lock Input Forming Logic

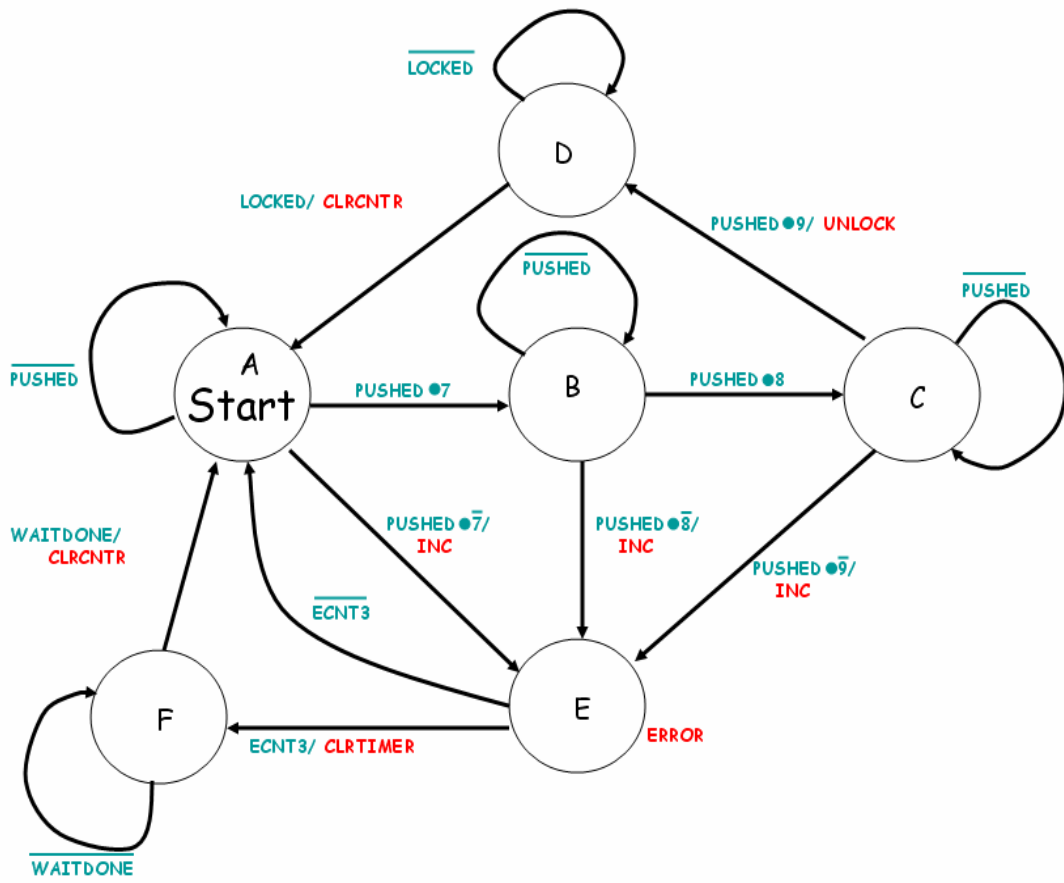

$$A+ = (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) + (\text{WAITDONE} \bullet F) + (\text{LOCKED} \bullet D)$$

$$B+ = (\text{PUSHED}' \bullet B) + (\text{PUSHED} \bullet 7 \bullet A)$$

Key Lock Input Forming Logic

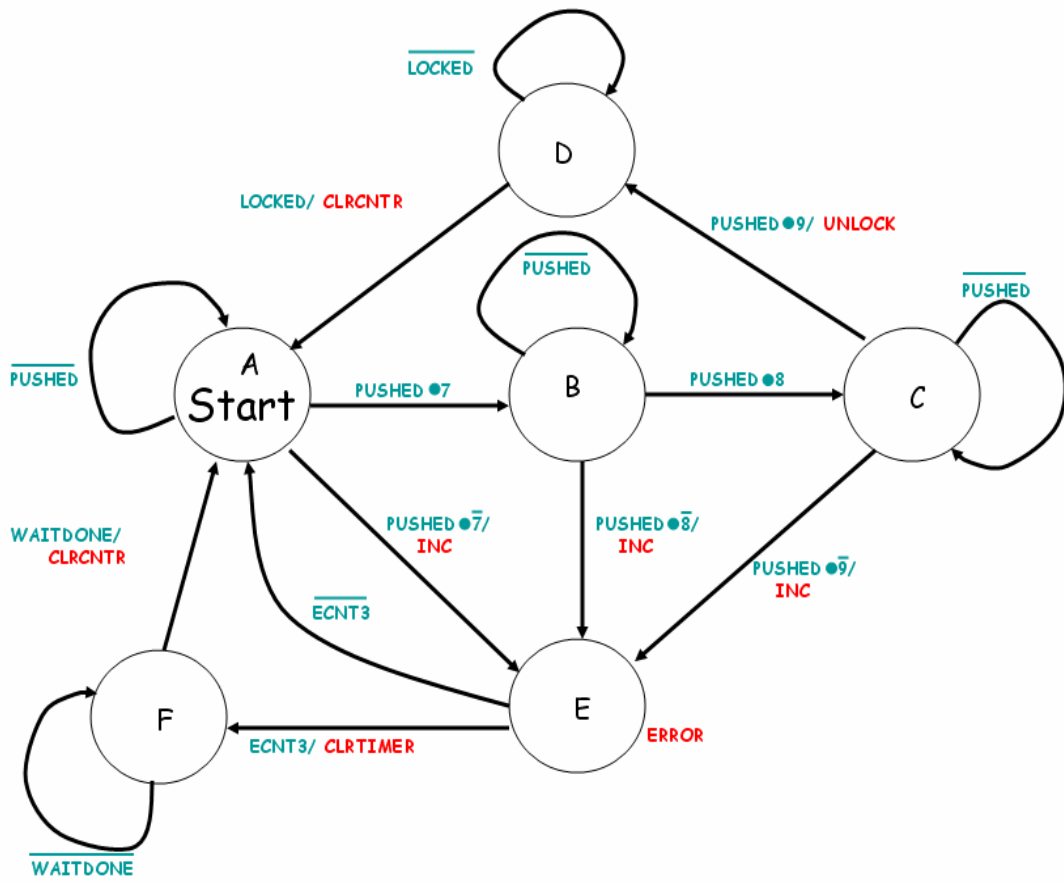


$$A+ = (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) + (\text{WAITDONE} \bullet F) + (\text{LOCKED} \bullet D)$$

$$B+ = (\text{PUSHED}' \bullet B) + (\text{PUSHED} \bullet 7 \bullet A)$$


$$C+ = (\text{PUSHED}' \bullet C) + (\text{PUSHED} \bullet 8 \bullet B)$$

Key Lock Input Forming Logic

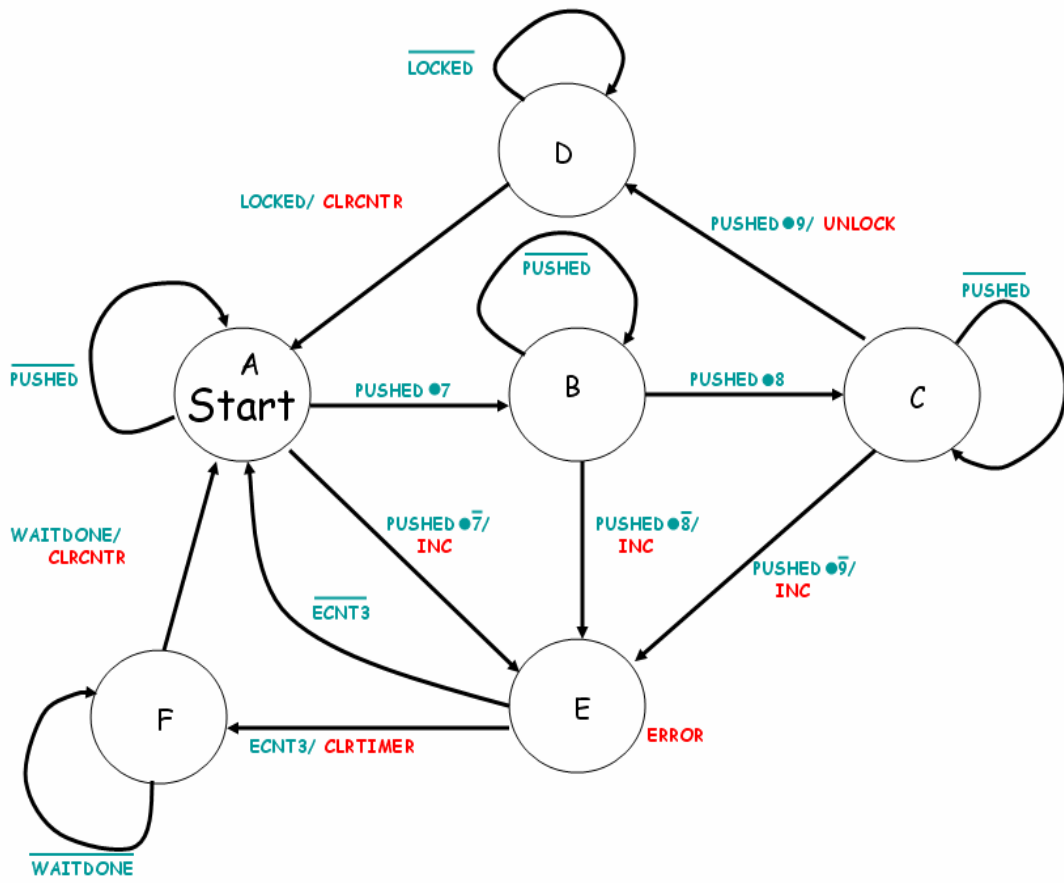


$$\begin{aligned}
 A+ &= (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) \\
 &\quad + (\text{WAITDONE} \bullet F) \\
 &\quad + (\text{LOCKED} \bullet D) \\
 B+ &= (\text{PUSHED}' \bullet B) + (\text{PUSHED} \bullet 7 \bullet A) \\
 C+ &= (\text{PUSHED}' \bullet C) + (\text{PUSHED} \bullet 8 \bullet B) \\
 D+ &= (\text{LOCKED}' \bullet D) + (\text{PUSHED} \bullet 9 \bullet C)
 \end{aligned}$$

Key Lock Input Forming Logic

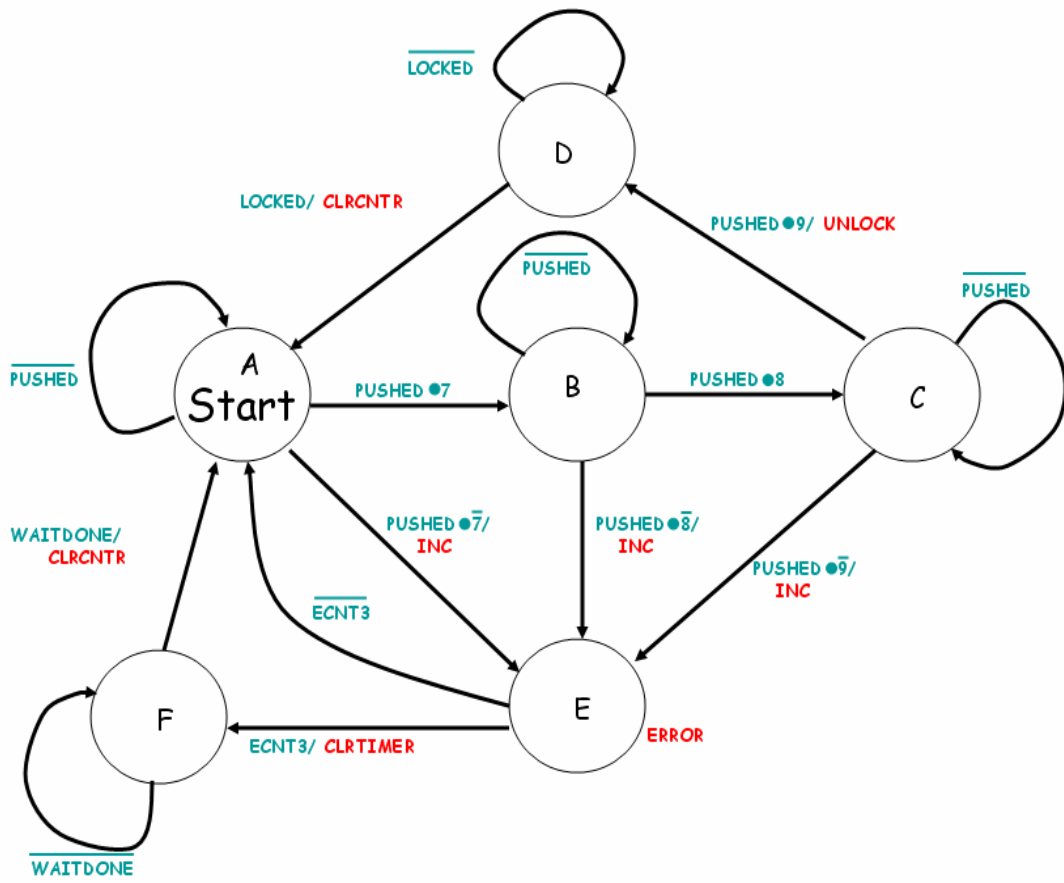


$$\begin{aligned}
 A+ &= (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) \\
 &\quad + (\text{WAITDONE} \bullet F) \\
 &\quad + (\text{LOCKED} \bullet D) \\
 B+ &= (\text{PUSHED}' \bullet B) + (\text{PUSHED} \bullet 7 \bullet A) \\
 C+ &= (\text{PUSHED}' \bullet C) + (\text{PUSHED} \bullet 8 \bullet B) \\
 D+ &= (\text{LOCKED}' \bullet D) + (\text{PUSHED} \bullet 9 \bullet C) \\
 E+ &= (\text{PUSHED} \bullet 7' \bullet A) \\
 &\quad + (\text{PUSHED} \bullet 8' \bullet B) \\
 &\quad + (\text{PUSHED} \bullet 9' \bullet C)
 \end{aligned}$$

Key Lock Input Forming Logic

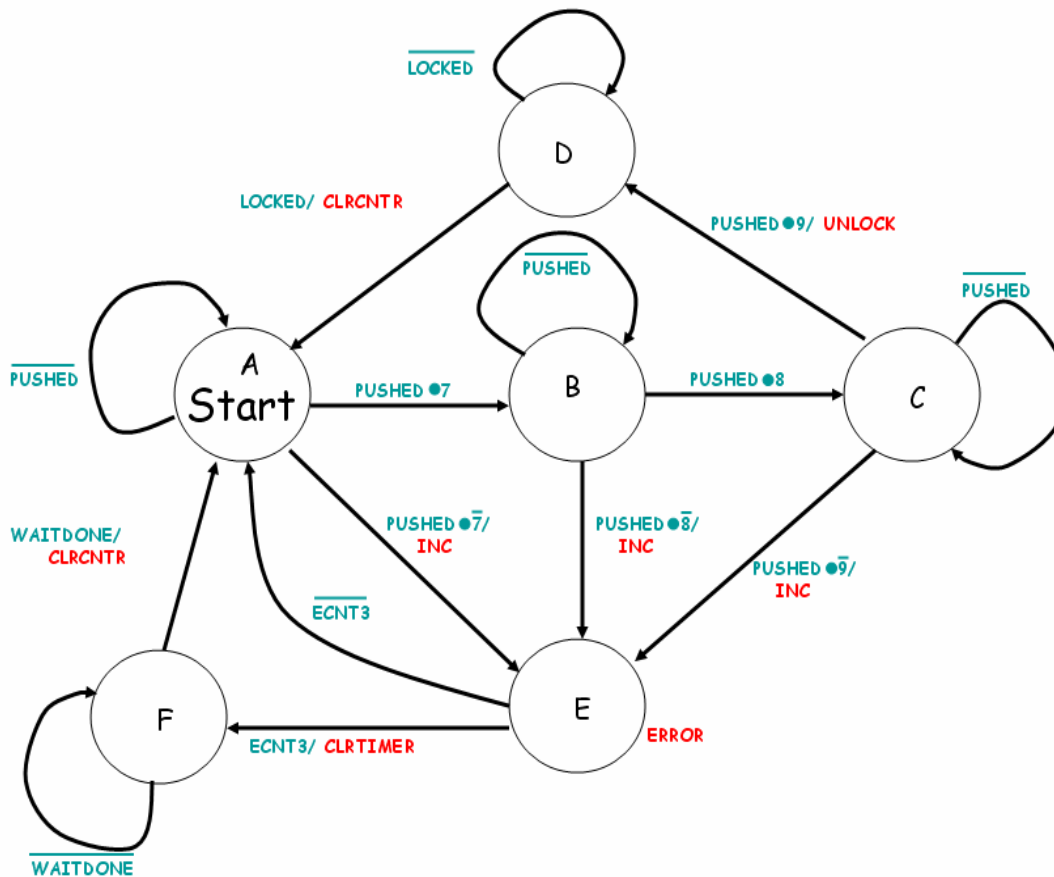


$$\begin{aligned}
 A+ &= (\text{PUSHED}' \bullet A) + (\text{ECNT3}' \bullet E) \\
 &\quad + (\text{WAITDONE} \bullet F) \\
 &\quad + (\text{LOCKED} \bullet D) \\
 B+ &= (\text{PUSHED}' \bullet B) + (\text{PUSHED} \bullet 7 \bullet A) \\
 C+ &= (\text{PUSHED}' \bullet C) + (\text{PUSHED} \bullet 8 \bullet B) \\
 D+ &= (\text{LOCKED}' \bullet D) + (\text{PUSHED} \bullet 9 \bullet C) \\
 E+ &= (\text{PUSHED} \bullet 7' \bullet A) \\
 &\quad + (\text{PUSHED} \bullet 8' \bullet B) \\
 &\quad + (\text{PUSHED} \bullet 9' \bullet C) \\
 F+ &= (\text{ECNT3} \bullet E) \\
 &\quad + (\text{WAITDONE}' \bullet F)
 \end{aligned}$$

Key Lock Output Forming Logic

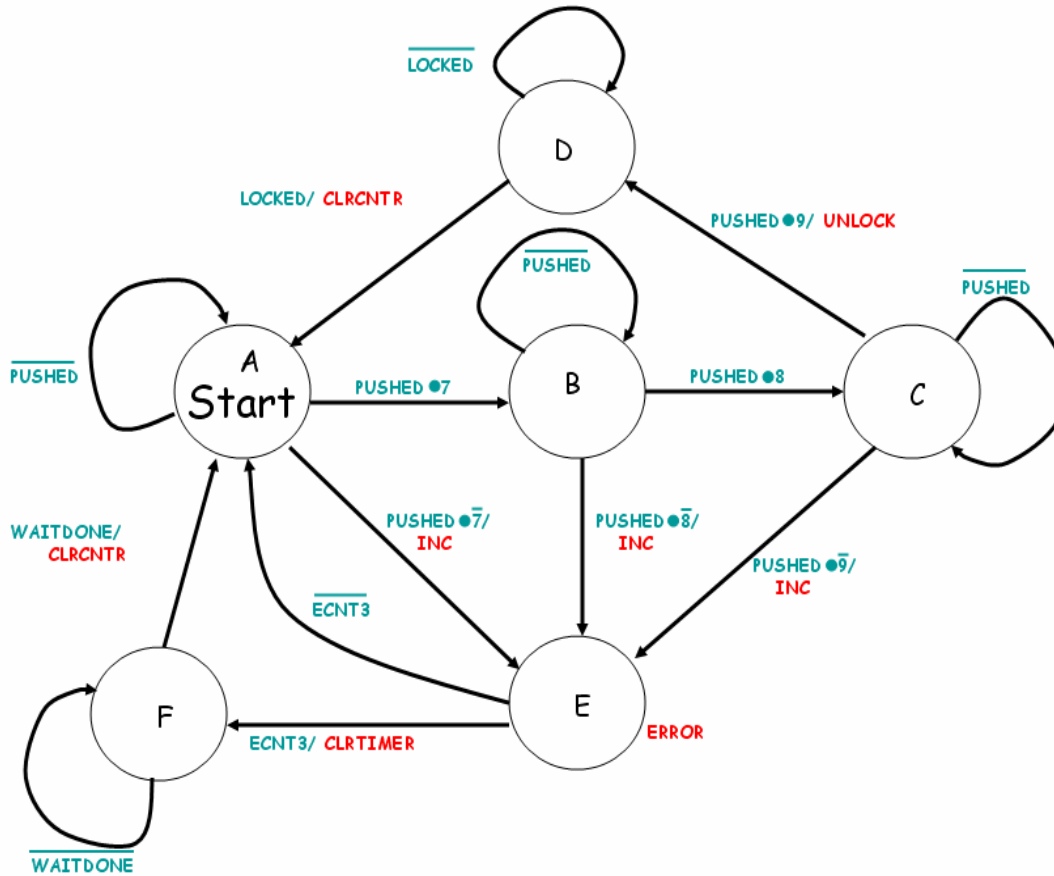


ERROR = E

Key Lock Output Forming Logic

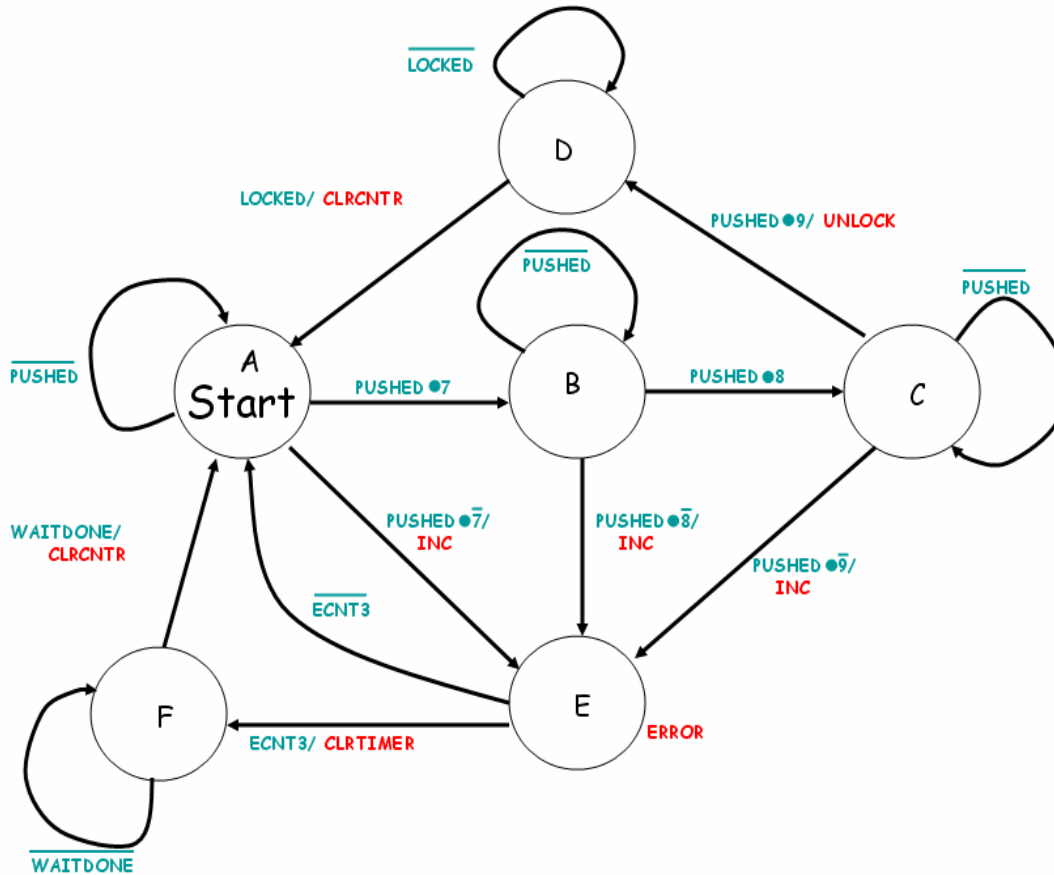


$$\begin{aligned}
 \text{ERROR} &= E \\
 \text{INC} &= (\text{PUSHED} \bullet 7' \bullet A) \\
 &+ (\text{PUSHED} \bullet 8' \bullet B) \\
 &+ (\text{PUSHED} \bullet 9' \bullet C)
 \end{aligned}$$

Key Lock Output Forming Logic

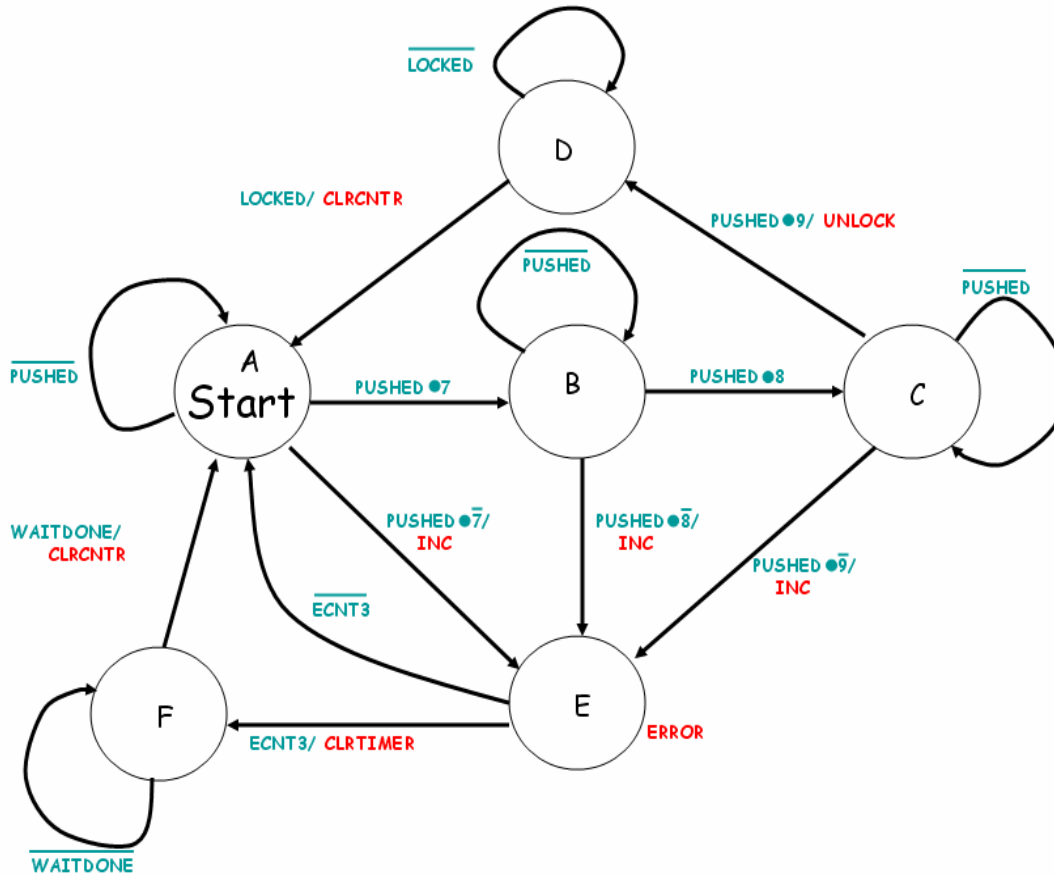


$$\begin{aligned} \text{ERROR} &= E \\ \text{INC} &= (\text{PUSHED} \bullet 7' \bullet A) \\ &\quad + (\text{PUSHED} \bullet 8' \bullet B) \\ &\quad + (\text{PUSHED} \bullet 9' \bullet C) \\ \text{CLRTIMER} &= \text{ECNT3} \bullet E \end{aligned}$$

Key Lock Output Forming Logic

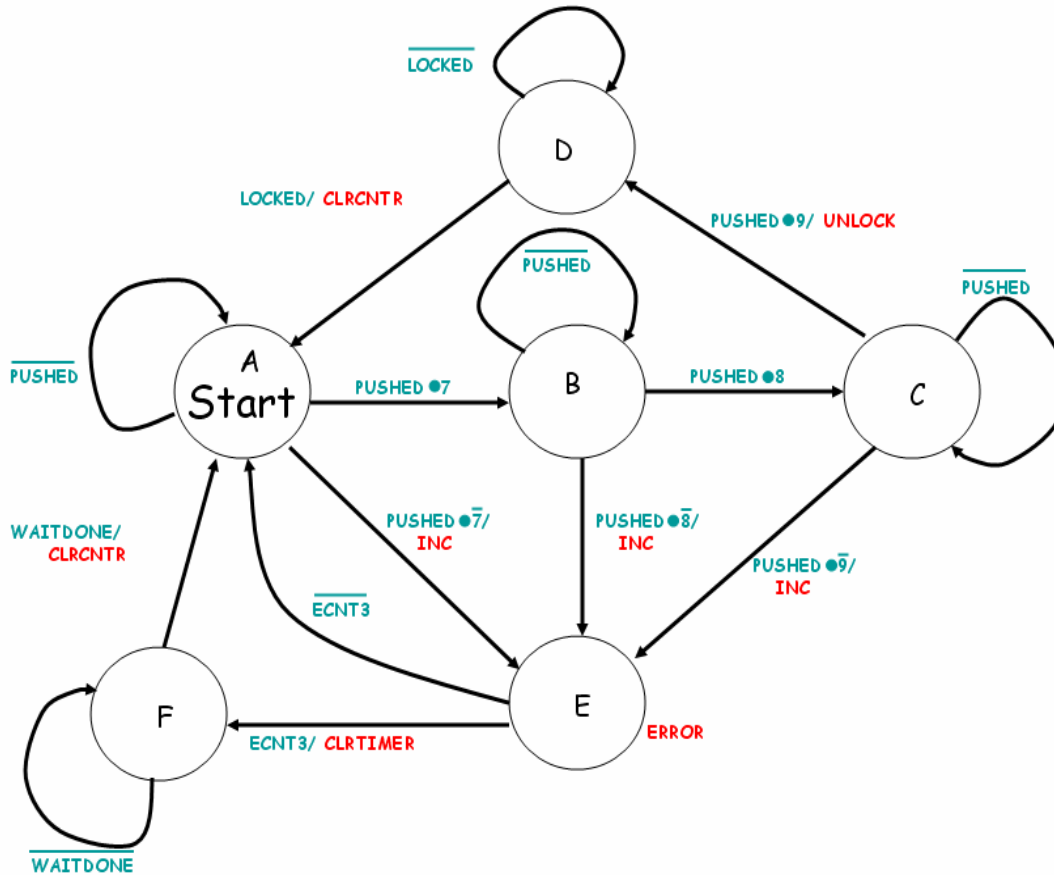

$$\begin{aligned} \text{ERROR} &= E \\ \text{INC} &= (\text{PUSHED} \bullet 7' \bullet A) \\ &\quad + (\text{PUSHED} \bullet 8' \bullet B) \\ &\quad + (\text{PUSHED} \bullet 9' \bullet C) \\ \text{CLR TIMER} &= \text{ECNT3} \bullet E \\ \text{CLR CNTR} &= (\text{WAITDONE} \bullet F) \\ &\quad + ((\text{LOCKED} \bullet D)) \end{aligned}$$

Key Lock Output Forming Logic

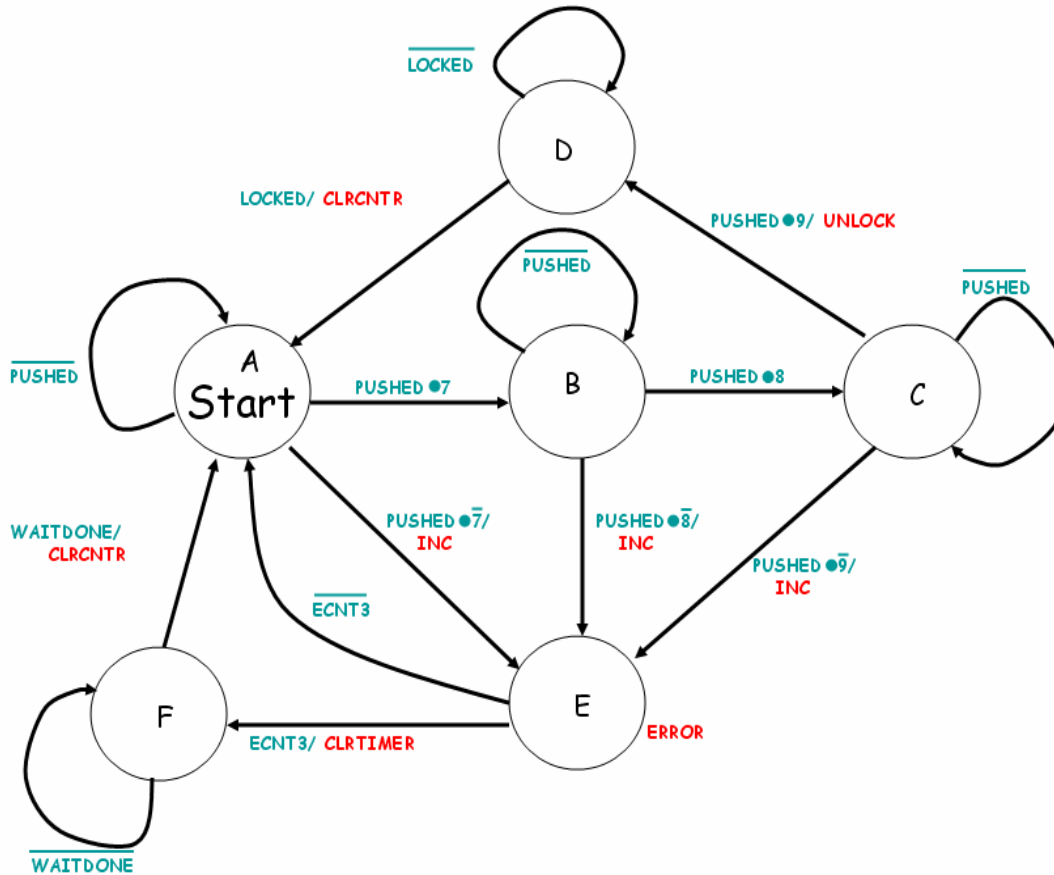

$$\begin{aligned}
 \text{ERROR} &= E \\
 \text{INC} &= (\text{PUSHED} \bullet 7' \bullet A) \\
 &\quad + (\text{PUSHED} \bullet 8' \bullet B) \\
 &\quad + (\text{PUSHED} \bullet 9' \bullet C) \\
 \text{CLRNTMR} &= \text{ECNT3} \bullet E \\
 \text{CLRNTMR} &= (\text{WAITDONE} \bullet F) \\
 &\quad + ((\text{LOCKED} \bullet D)) \\
 \text{UNLOCK} &= (\text{PUSHED} \bullet 9 \bullet C)
 \end{aligned}$$

Other State Encoding Techniques

- You have learned the 2 extremes
 - Fully encoded (8 states \Leftrightarrow 3 state bits)
 - One-hot encoded (8 states \Leftrightarrow 8 state bits)
- A range of options exist in between

- A good choice of encoding
 - Can minimize IFL and OFL complexity
 - Algorithms have been developed for this...
 - Beyond the scope of this class