


Debouncing a Switch

A Design Example


Background and Motivation

When you throw a switch (button or two-pole switch)...


- It often bounces...

 


Another switch...

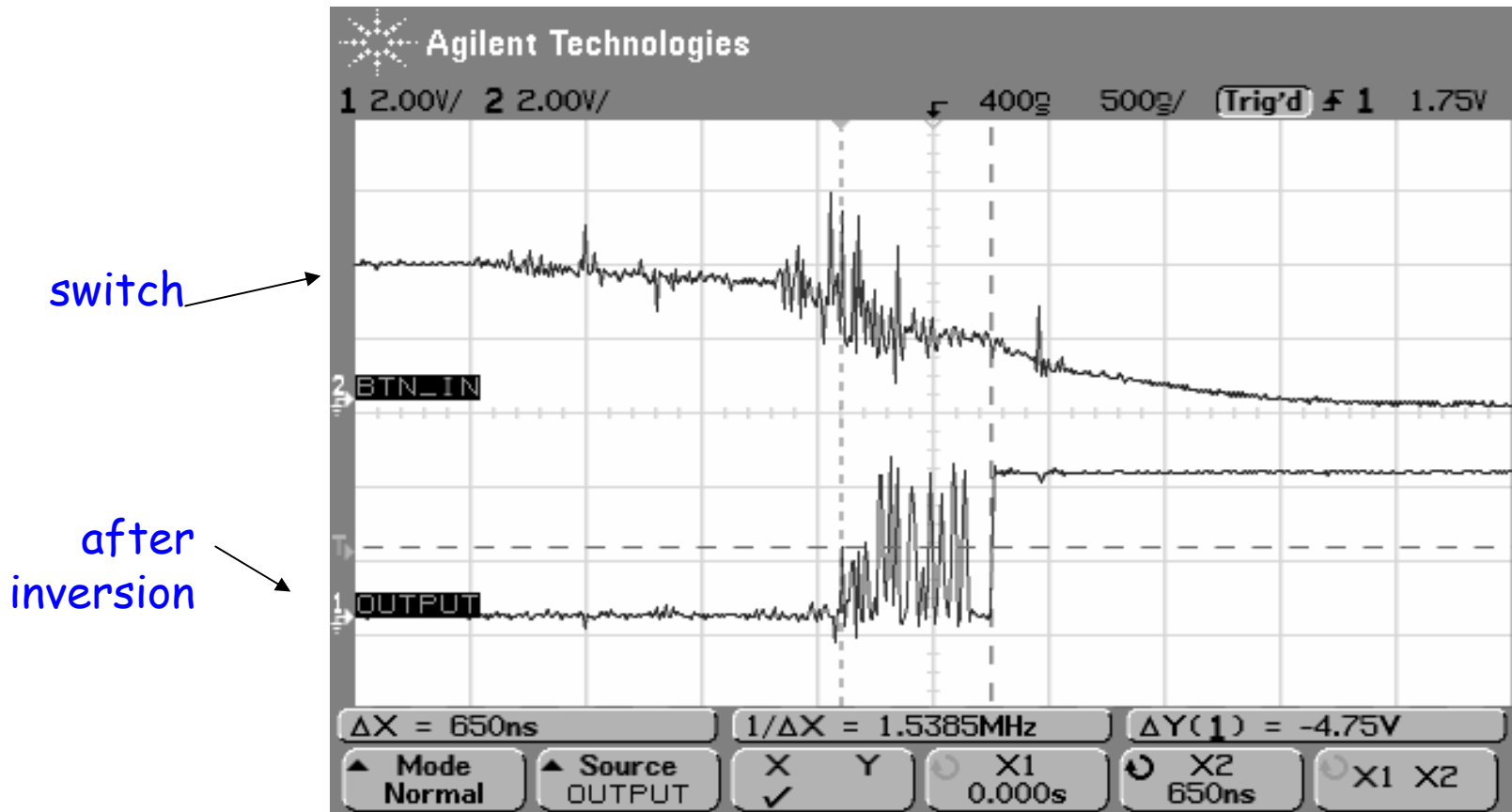

Yet Another...

 

Still Yet Another...

 


Causes

- Mechanical switch
 - Not an instant, once-only make-or-break
 - Spring loaded - contacts literally bounce

Source of Errors

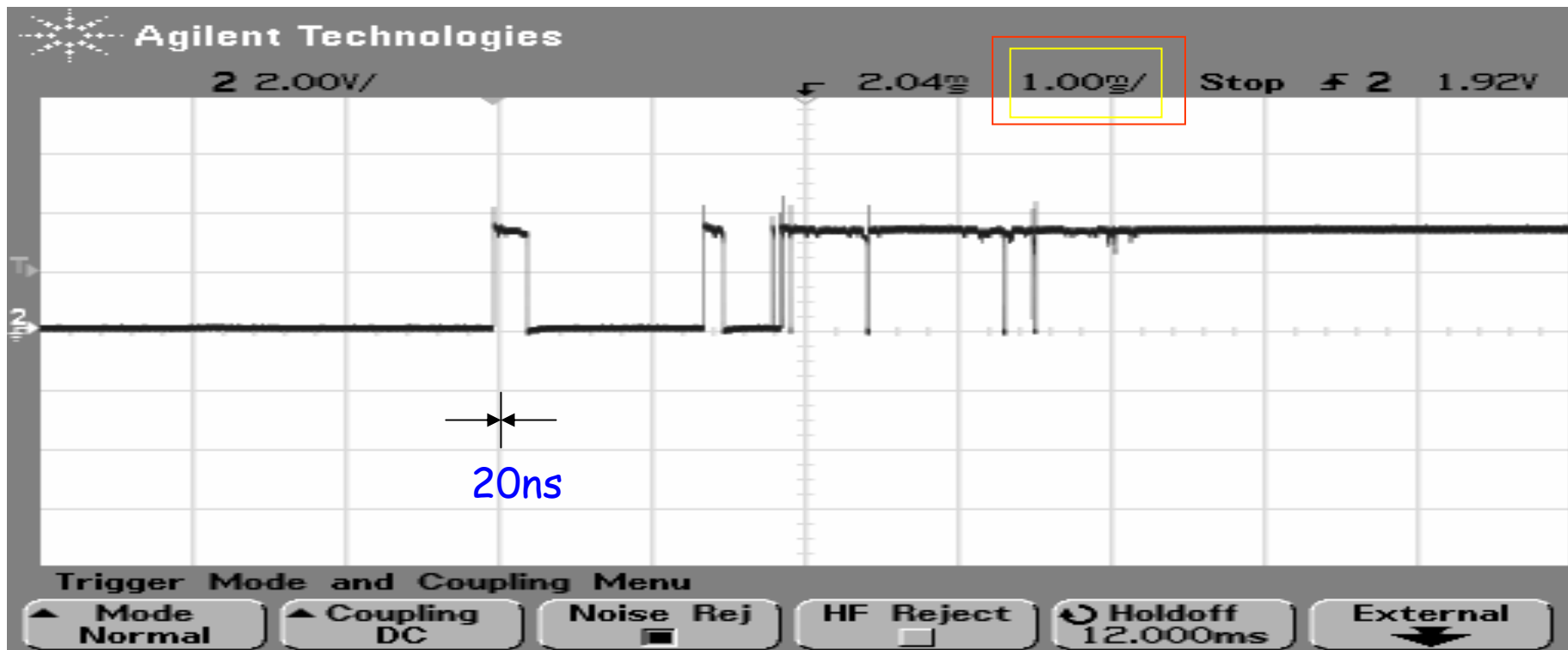- 20ns clock period is very short compared to bouncing...
- Downstream circuitry will see every bounce as an input change




FSM-Based Solution

Solutions

- Single-output switch
 - Since all you see is bouncing value
 - timing-based solution can be employed
- There are other solutions but they require a different kind of switch

Timing-Based Solution

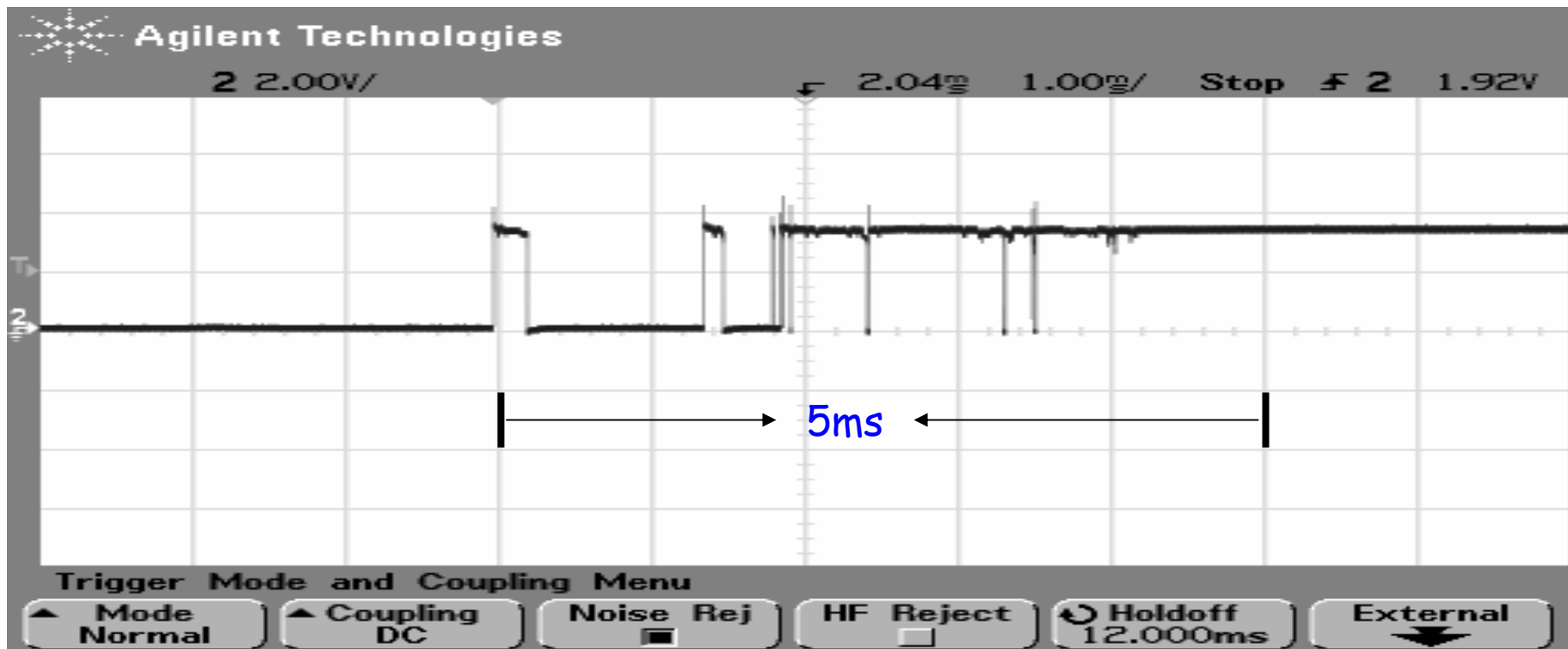
- Only declare an input change after signal has been stable for at least 5ms




FSM Solution

- Simple enough that an FSM might not be required
 - Easy to concoct a sequential circuit to do this with a counter and a single FF
- Let's do it with an FSM
 - If solution requires only a counter and a single FF, we will find that solution

Draw a Timing Diagram

 


Draw a System Block Diagram

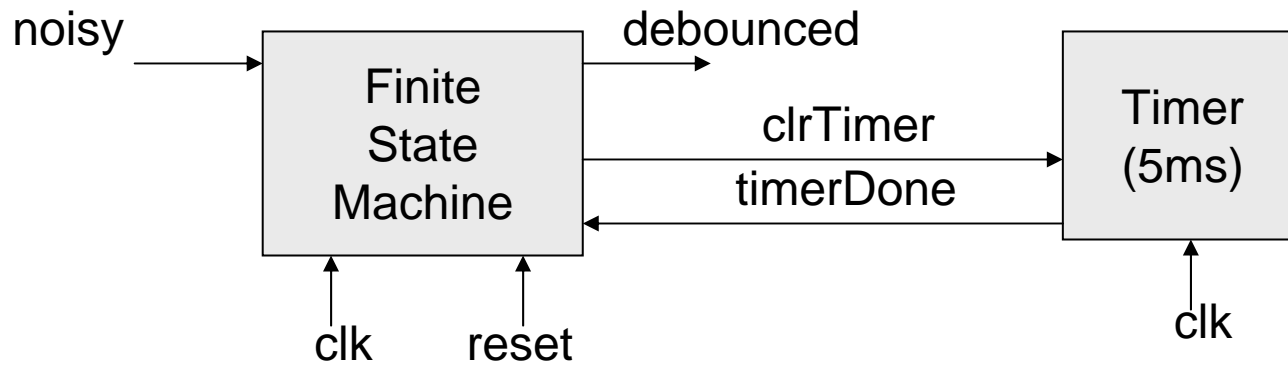


Very reminiscent of our car wash controller...

The Design of the FSM

Draw a State Graph

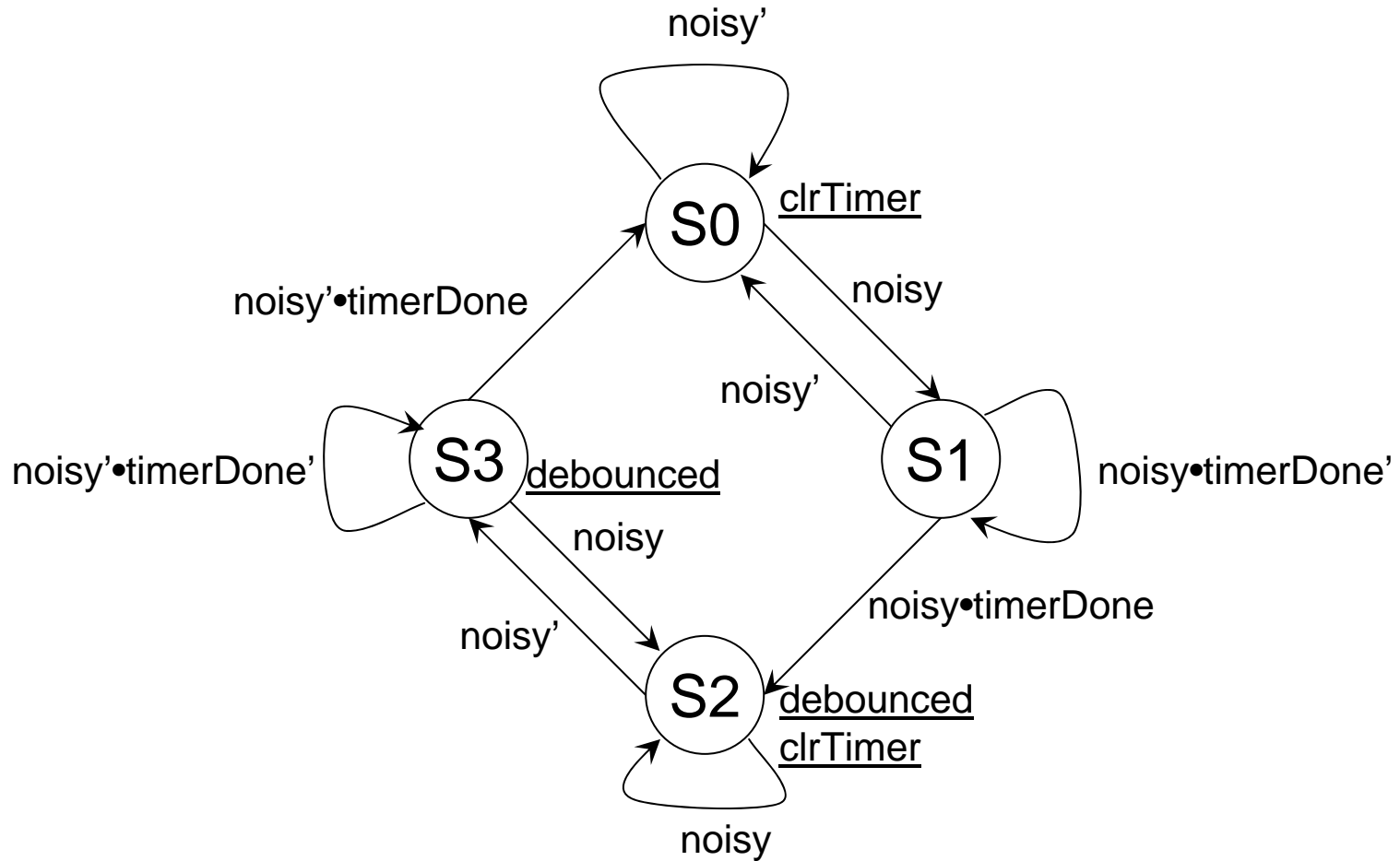


Draw a State Graph

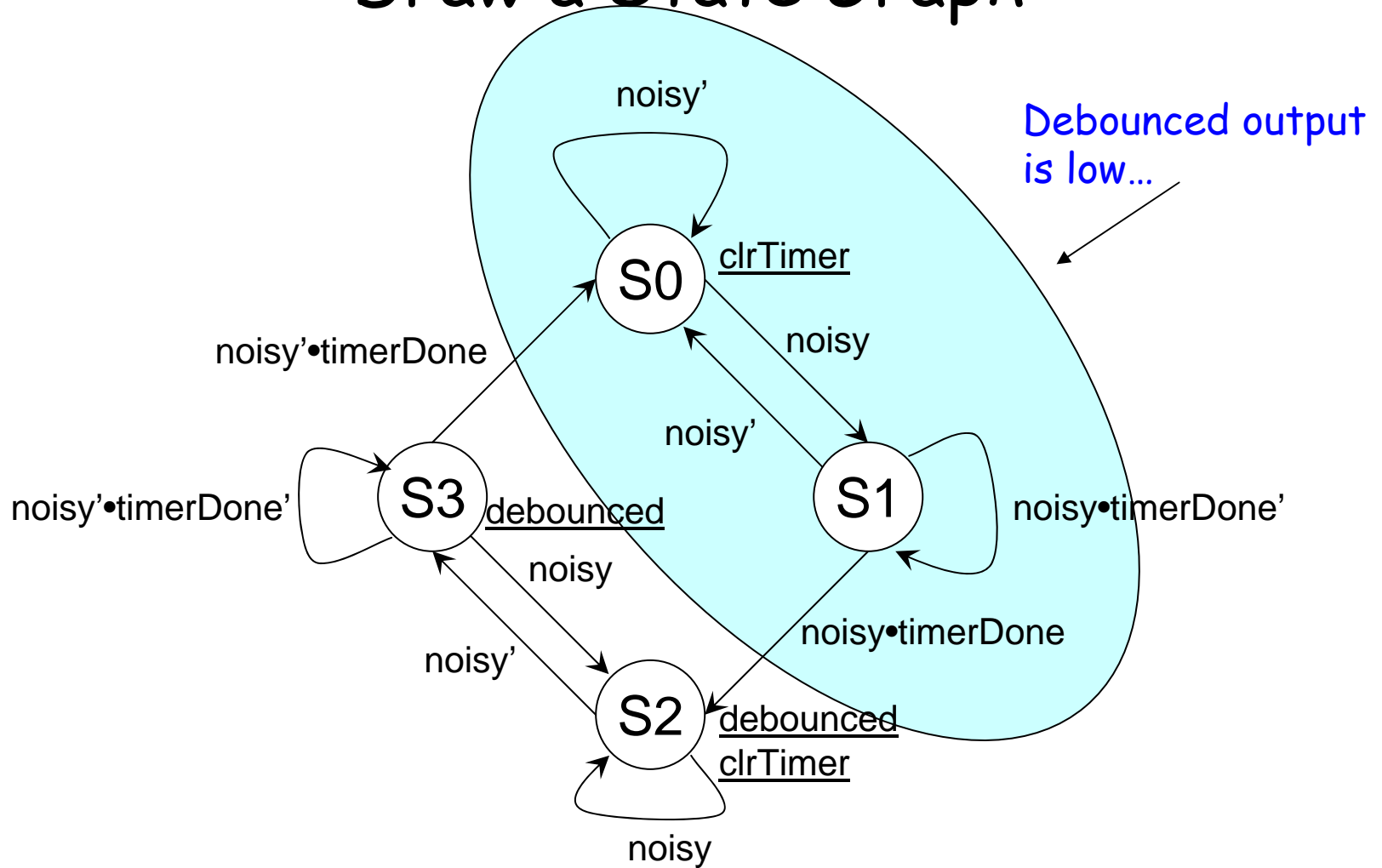


Draw a State Graph

Debounced output
is high...

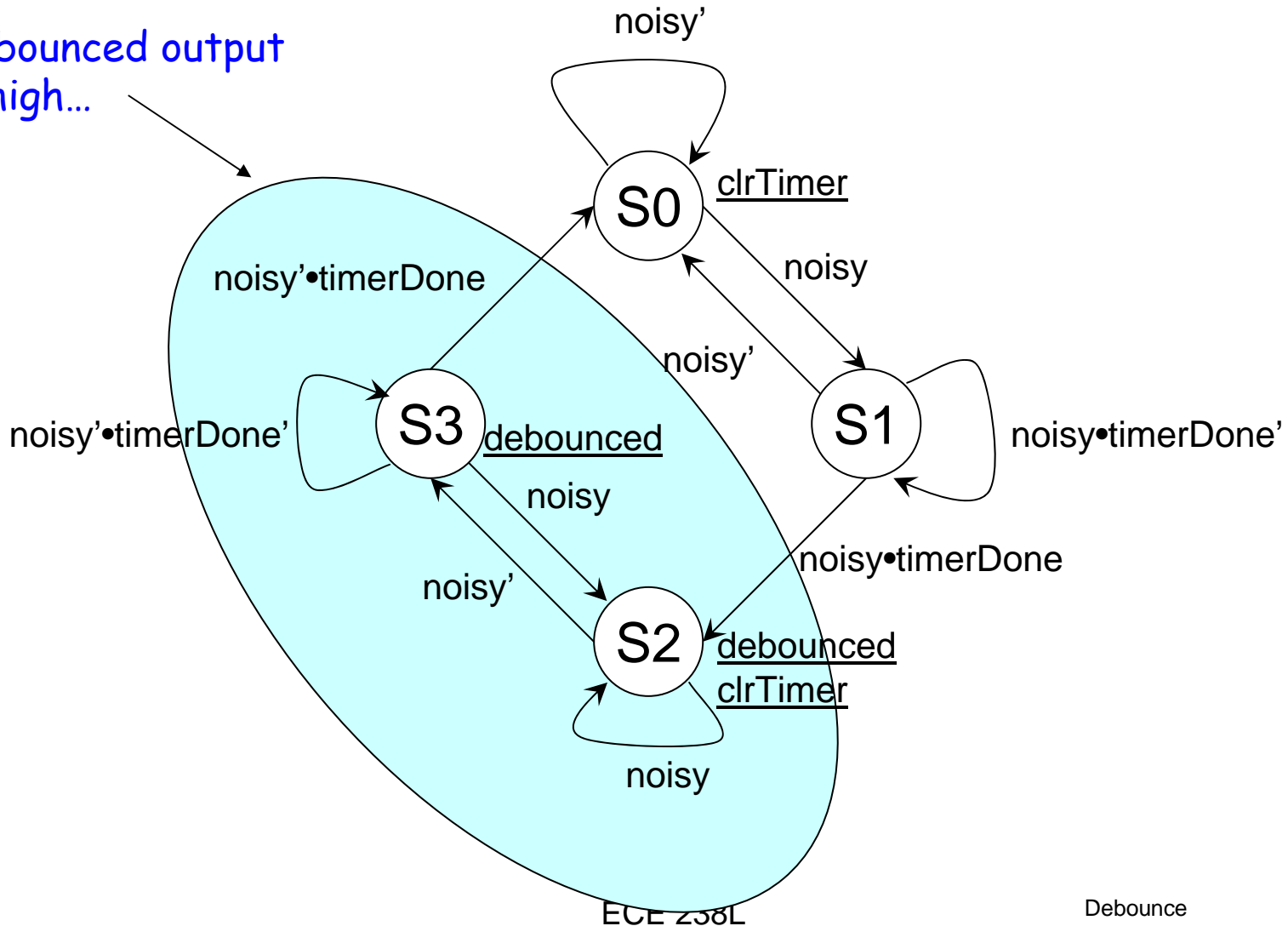

An Improved State Graph

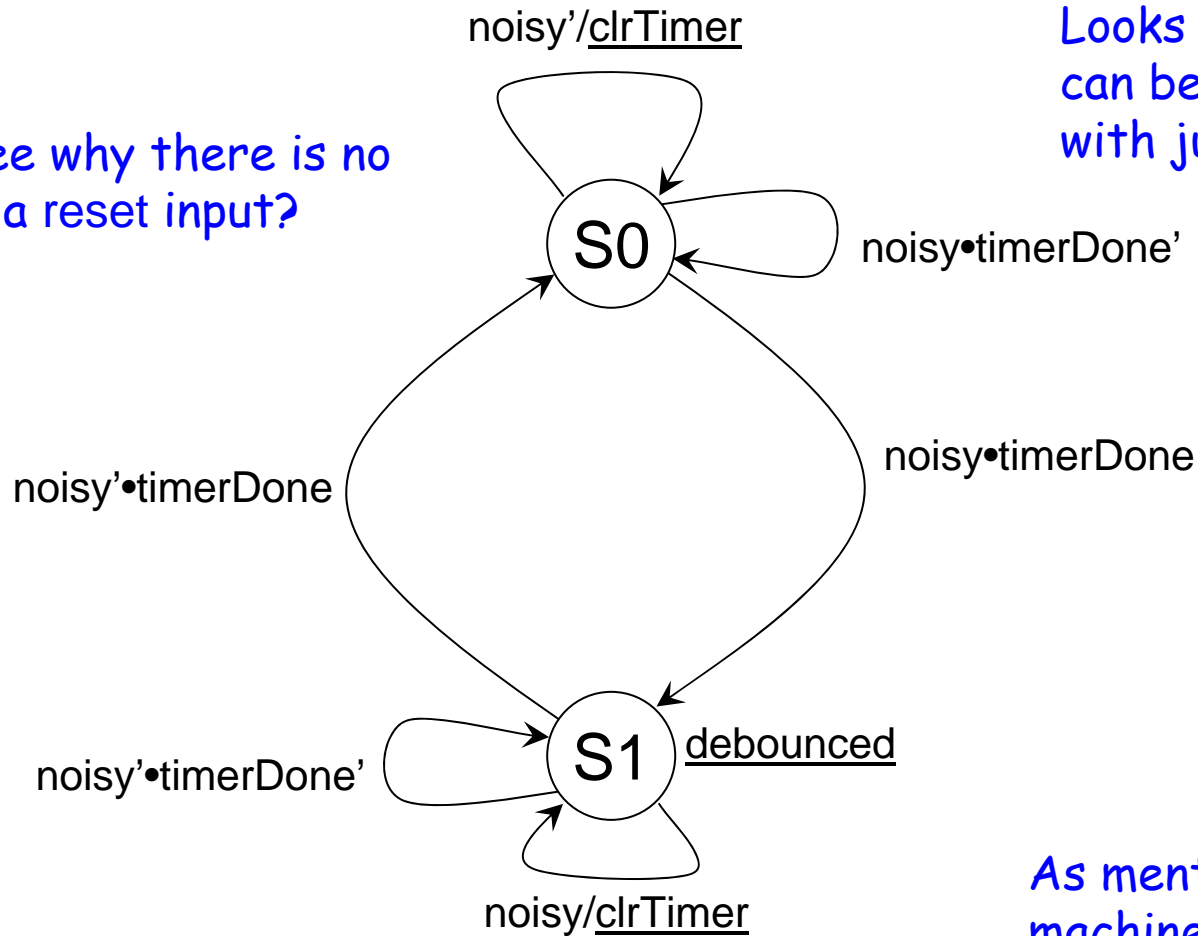Do you see why there is no need for a reset input?



Looks like the FSM can be implemented with just a single FF


As mentioned, Mealy machines often require fewer states...

Reduce FSM to Logic

$$NS = CS' \cdot \text{noisy} \cdot \text{timerDone} + CS \cdot \text{noisy} + CS \cdot \text{noisy}' \cdot \text{timerDone}'$$

$$S_0 = CS' \quad S_1 = CS \quad \text{noisy} = N \quad \text{timerDone} = T$$

	NT			
CS	00	01	11	10
0			1	
1	1		1	1

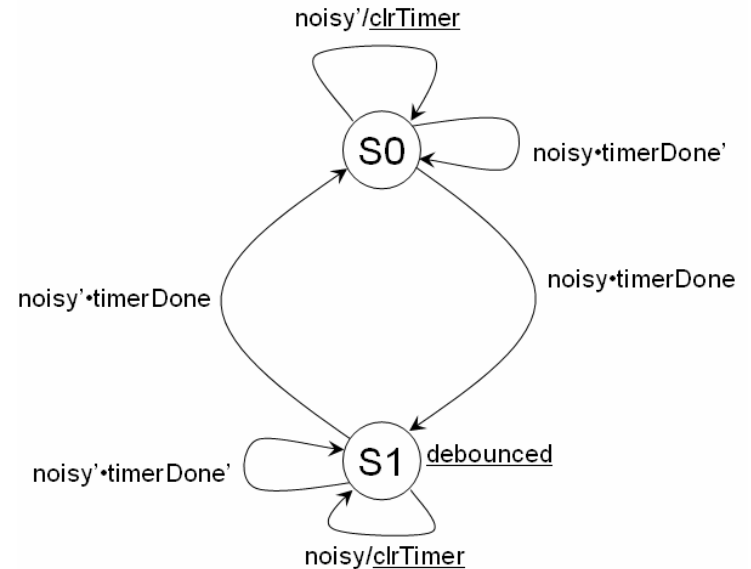

$$NS = \text{noisy} \cdot \text{timerDone} + CS \cdot \text{timerDone}'$$

$$\text{clrTimer} = \text{noisy}' \cdot CS' + \text{noisy} \cdot CS$$


$$\text{debounced} = CS$$

Reduce FSM to Logic

$$NS = \text{noisy} \cdot \text{timerDone} + \text{CS} \cdot \text{timerDone}'$$

$$\text{clrTimer} = \text{noisy}' \cdot \text{CS}' + \text{noisy} \cdot \text{CS}$$


$$\text{debounced} = \text{CS}$$

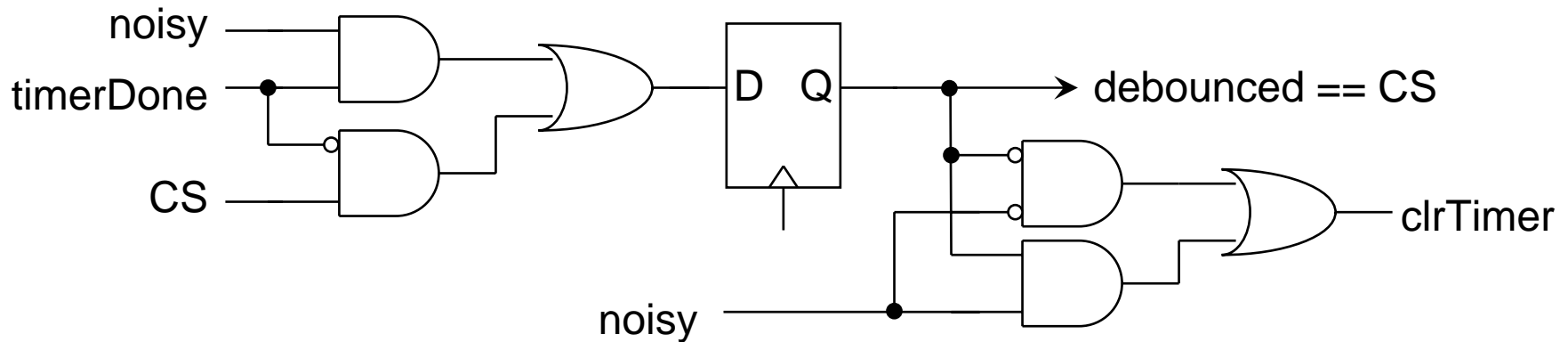

This is smaller than one-hot implementation


In addition, the one-hot would require a reset input to get it to state S0

noisy is an Asynchronous Input

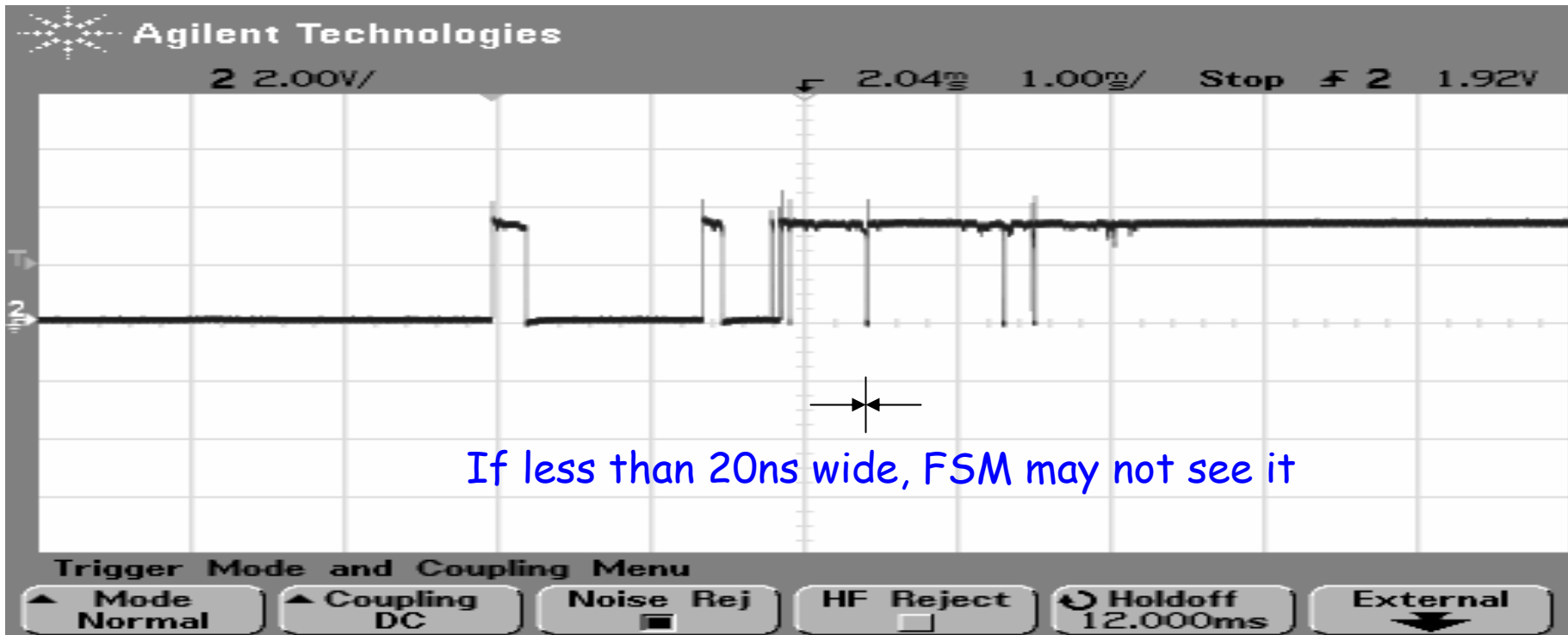

- Signal noisy is asynchronous
 - No restrictions on pulse widths
- We will live with this possibility...

More on Asynchronous Input

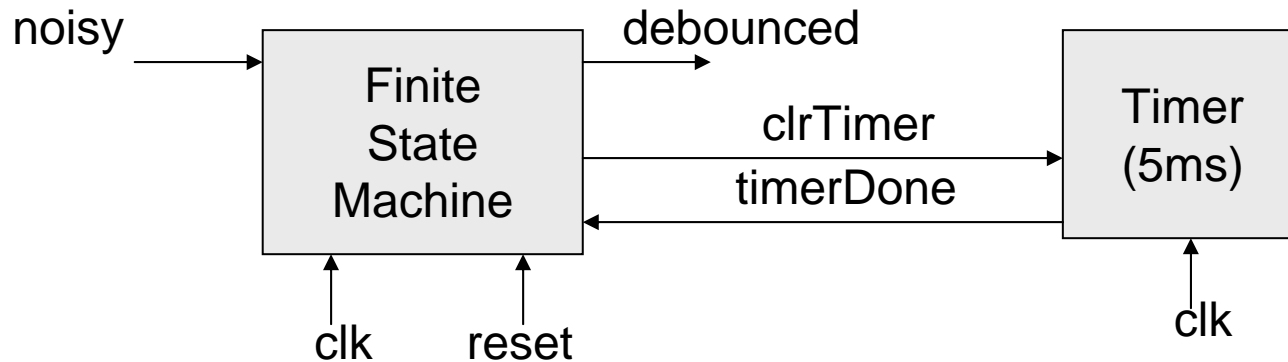


Classical asynch input handling problem:

1. FSM may see noisy change and change state
2. Timer may not see clrTimer that results

Or, the other way around may occur...

Will this cause incorrect operation?

Asynch Input Problem

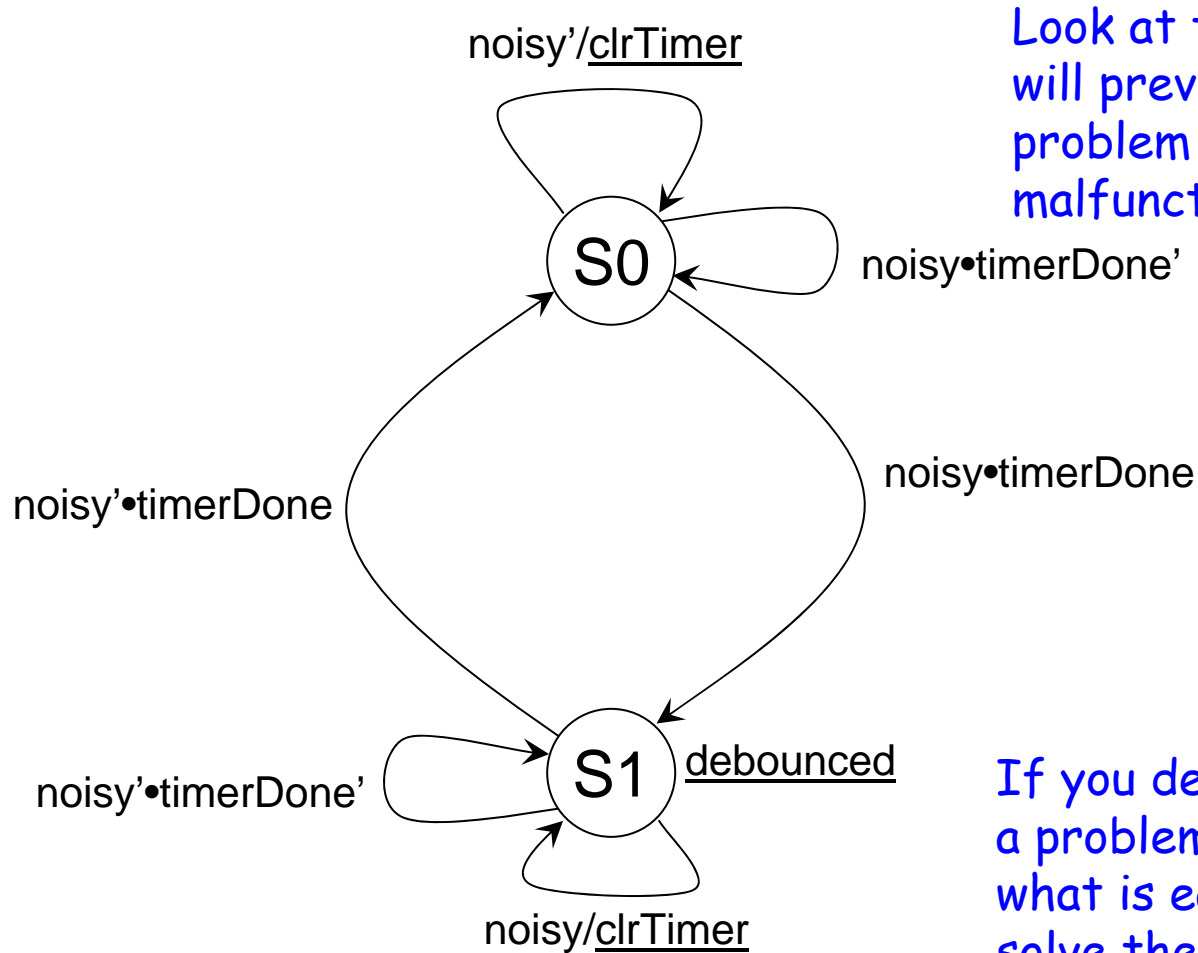

Look at the transitions - will previous slide's problem cause a malfunction??

If you determine that a problem may result, what is easiest way to solve the problem?

Design of the Timer


Timer Calculations

- Assume system runs at 50MHz (20ns period)
- $5\text{ms}/20\text{ns} = 250,000$
- An 18-bit counter will work...
- 2^{18} is a bit longer than 250,000 (262,144)
 - But is close enough to 5ms for our purposes


Timer Structure

- 19 inputs: 18 CS bits + 1 clrTimer bit
 - Very, very large truth table
- A better structure is:
 - Register that selects between CS+1 and 0
 - This is the technique of Chapter 12 (registers)

Timer Structure

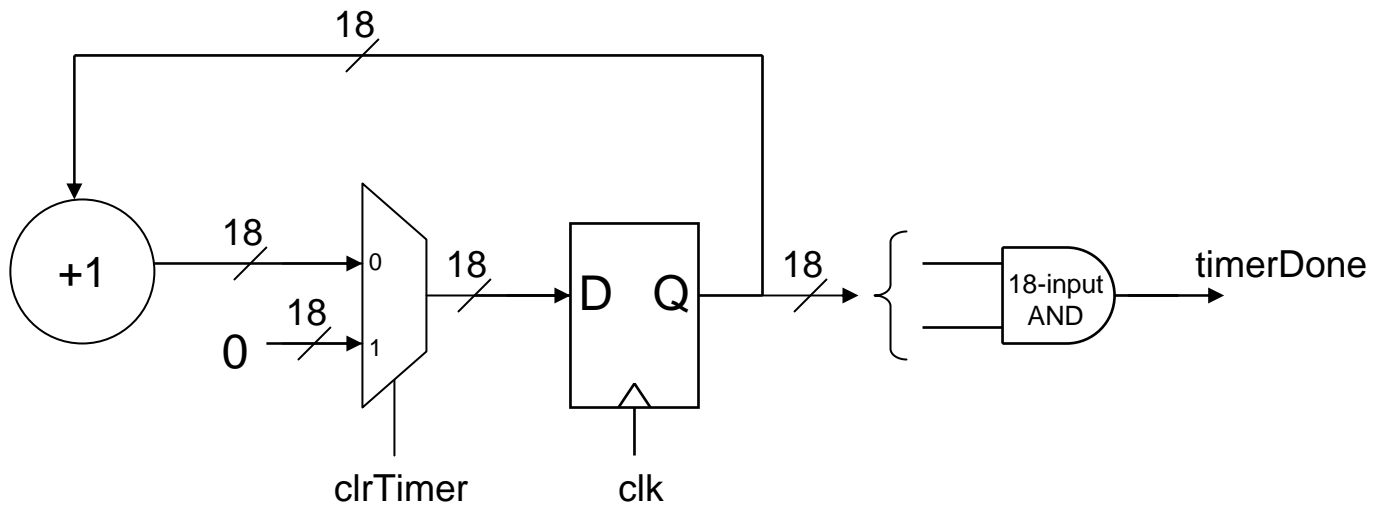


Improved Timer Structure

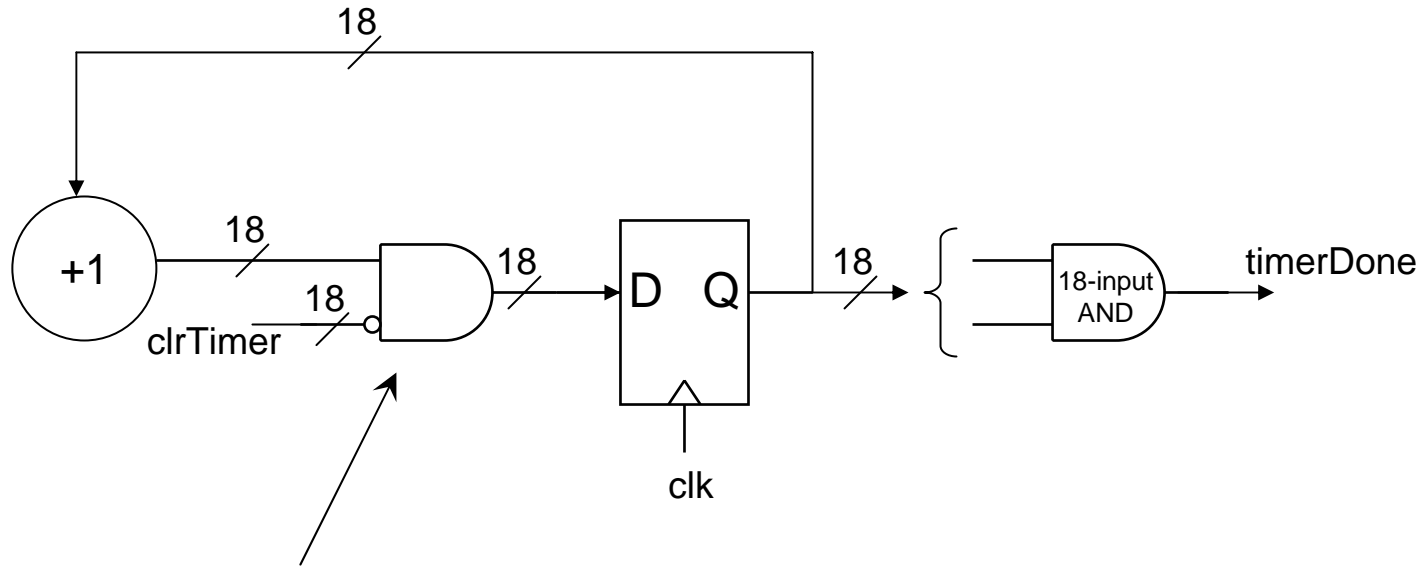

This is a simpler way to conditionally generate zeroes.

A synthesizer likely would have generated this from Verilog or VHDL code containing a MUX


Building the +1 Circuit - Version #1

 

The adder would be built as outlined back in Chapter 8 using full adder blocks.




However, half the full adder inputs will be '0' - there ought to be a better way...

A Full-Adder with '0' Inputs



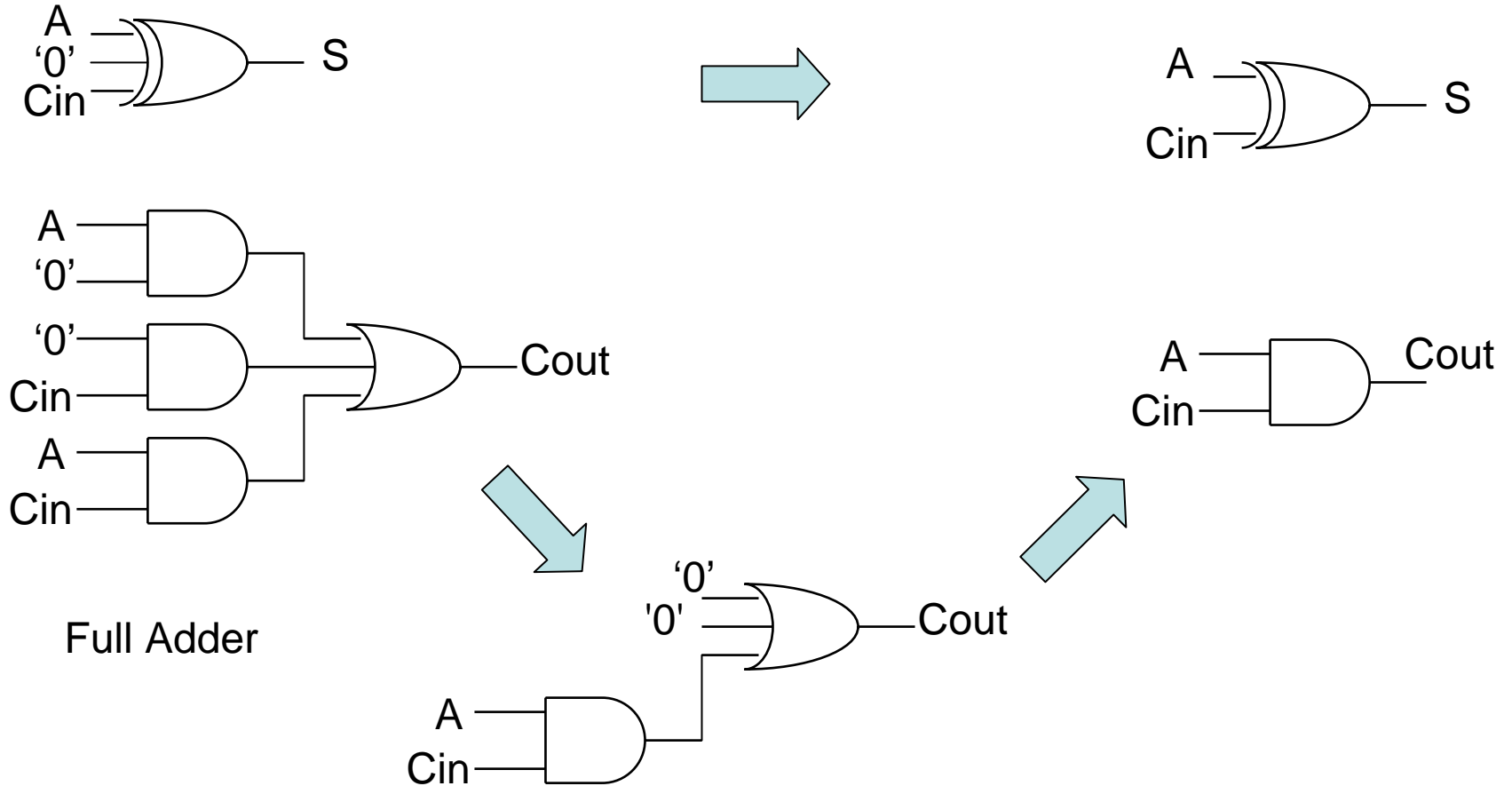


Full Adder

A Half-Adder

   


Full Adder

   

Called a half-adder


*Will add 2 bits together
and generate sum and carry.*

Building the +1 Circuit - Version #2

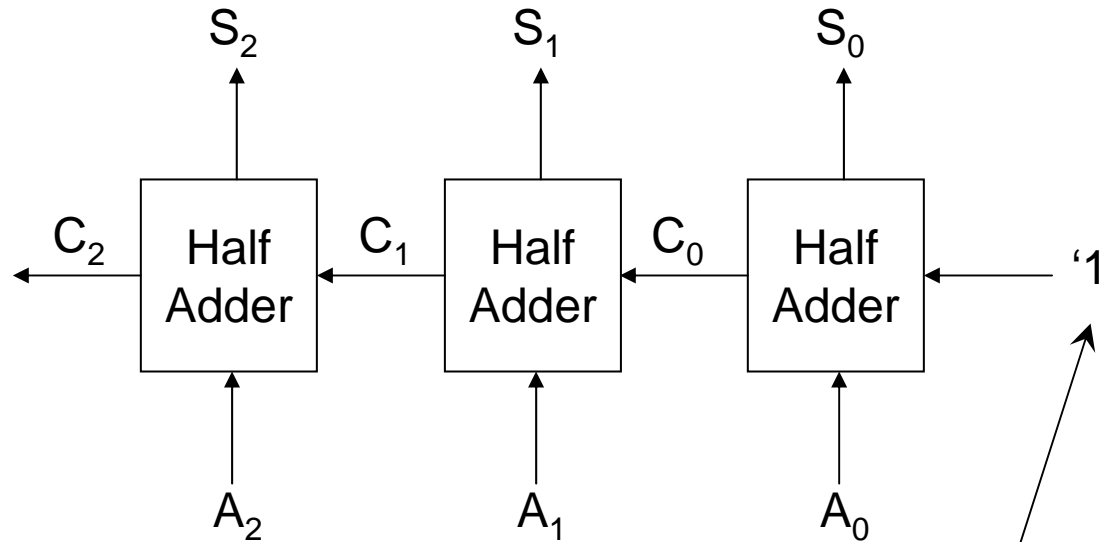

Half-adders add A 's and carries
'1' on right end is the +1

Building an 18-Bit AND

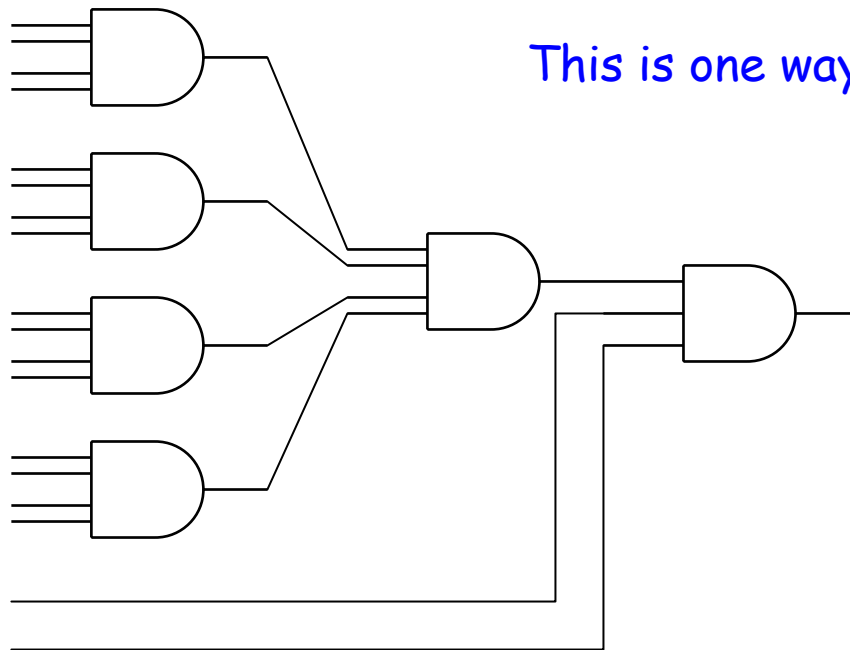

This is one way...

Synthesizers are good at building structures like this from lower-level building blocks. Just write an 18-bit AND in your Verilog or VHDL code...

If circuit has special structures for wide logic, synthesizer likely will use it (carry/cascade logic in an FPGA is an example)

Debouncer Summary

- Structure is timer + FSM
- 2-state FSM makes NS logic trivial
- Asynchronous input makes it possible (but unlikely) to miss a glitch on input noisy
 - If desired, synchronize noisy with a FF
- Counter too large for conventional techniques
 - Use MUX+register techniques of Chapter 12
- NOTE: FSM technique resulted in FF+counter mentioned previously...