

Midterm 2 - Review


LATCH

Storage
Bi-stability
Latches


Sequential Circuits

- The output of a Combinatorial Circuit depends only on the current inputs
- The output of a Sequential Circuit can remember something about the past

Bi-Stability = Key to Memory

 

 
This is a stable state -
it will sit like this forever




This is also a stable state -
it will sit like this forever

There are 2 stable states -
a **bi-stable** circuit...

SR Latch - A Bi-Stable Circuit

 


 This is a stable state -
it will sit like this forever




This is also a stable state -
it will sit like this forever

SR Latch Transition Table

 

S	R	Q	Q+	
0	0	0	0	No change
0	0	1	1	
0	1	0	0	Reset it
0	1	1	0	
1	0	0	1	Set it
1	0	1	1	
1	1	0	N/A	
1	1	1	N/A	


Symbology

 

GLATCH

Gated Latches

The Gated SR Latch

 

When $GATE = '0'$ \Leftrightarrow

$GR = GS = '0'$ \Leftrightarrow

latch cannot be modified

When $GATE = '1'$ \Leftrightarrow


$GR = R, GS = S$ \Leftrightarrow

works like an SR latch


The $GATE$ signal allows us to control
when
the latch will be loaded with a new value

Gated SR Latch

 - Sometimes known as a *loadable SR latch*
 - Can be loaded with new value



The Gated D Latch

 

GATE	D	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


$$Q+ = \text{GATE} \cdot D + \text{GATE}' \cdot Q$$

When $\text{GATE} = '1'$ \Leftrightarrow Q follows D (storage)
 When $\text{GATE} = '0'$ \Leftrightarrow Q retains old value (retention)

Gated D Latches

- Sometimes called a *transparent* latch
 - When $GATE = '1'$:
 - Q follows D
 - D is reflected on Q output
- Allows us to control *when* to store new data into latch
 - D = data to be stored
 - $GATE$ = control signal


Symbology

 

MSFF

Master/Slave Flip Flops

A Master/Slave Flip Flop (D Type)

 

Either:

The master is loading (the master is *on*)

or


The slave is loading (the slave is *on*)

But never both at the same time...

Alternative Flip Flops

T
JK

Toggle Flip Flop

 


T	Q	Q+	
0	0	0	No
0	1	1	Action
1	0	1	Toggle
1	1	0	

$$Q_+ = T' \cdot Q + T \cdot Q' = T \oplus Q$$

Clock edge is assumed
in this transition table...

JK Flip Flop

 

J	K	Q	Q+	
0	0	0	0	No Change
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

Kind of a cross between
a SR FF and a T FF


$$Q+ = K' \cdot Q + J \cdot Q'$$

Why Alternative FF's?

- With discrete parts (TTL family)
 - JK or T FF's could reduce gate count for the input forming logic
 - Extensively used
- With VLSI IC's and FPGA's
 - JK or T FF's must be built from DFF+gates
 - Larger, slower than a DFF
 - Not used

Flip Flops With Additional Control Inputs

What is this?

 


A falling edge triggered, D-type FF with enable

Master only loads when $CLK=Enable='1'$

The diagram shows a D flip-flop circuit. It has three inputs: D, Set, and CLK. The D input is connected to a network of logic gates. The Set input is connected to a red line that branches to the Set input of the flip-flop and the CLK input of the first two AND gates. The CLK input is connected to the CLK input of the last two AND gates. The output of the D flip-flop is Q, and the complement of Q is Q'.

If Set=1 then Q=>1, regardless of CLK or D

What is this?

 

A falling edge triggered, D-type FF with a synchronous set


If Set=1 then Q=>1 on the next falling edge of the clock, regardless of D

Flip Flops With Additional Control Inputs

- A variety of FF's have been made over the years
- They contain combinations of these inputs:
 - Enable
 - Set
 - Reset
- The Set and Reset can be either:
 - Asynchronous (independent of CLK)
 - Synchronous (work only on CLK edge)


Flip Flop Timing Characteristics

 Clock-to-Q Time ($t_{\text{CLK} \rightarrow Q}$)



The output does not change instantaneously...

Setup Time (t_{setup})

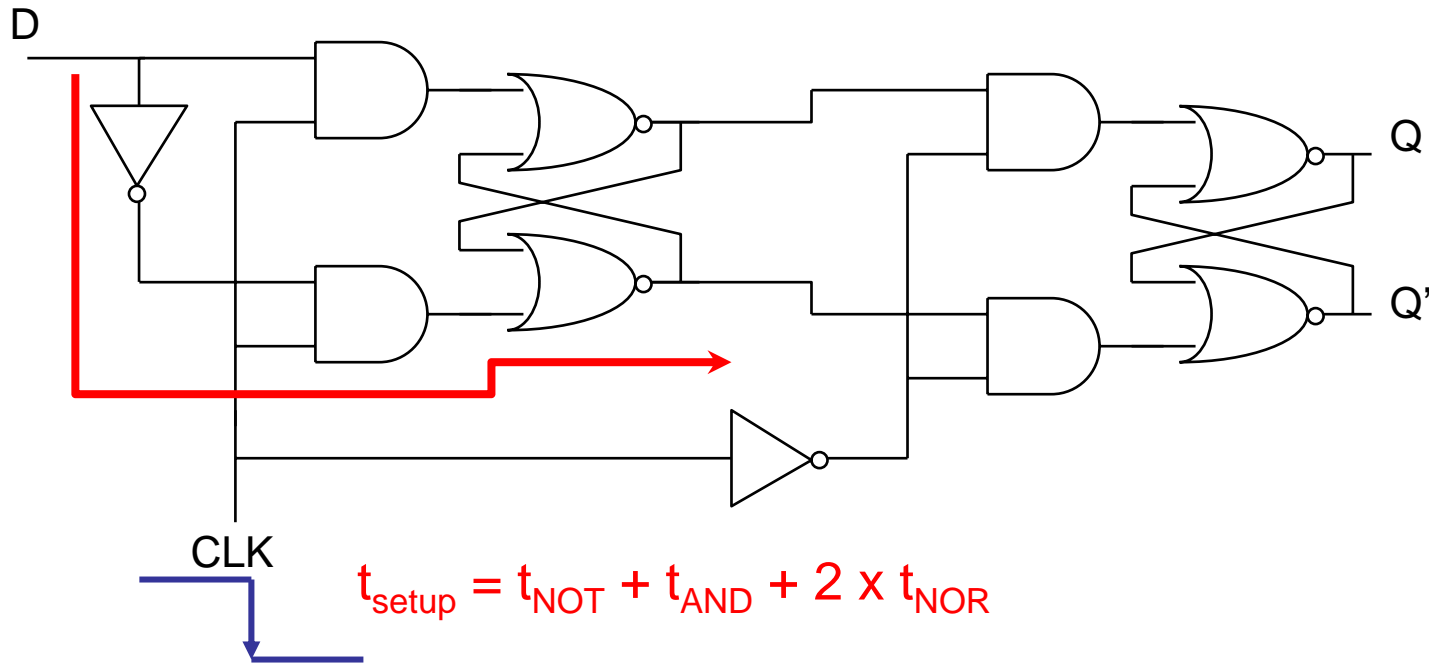

The input has to get there early enough
to set the master latch before
the clock turns off...


The diagram shows a D flip-flop circuit. The input **D** is connected to a NOT gate and two AND gates. The output of the NOT gate is connected to the other input of the two AND gates. The outputs of these two AND gates are connected to the inputs of a crossbar NAND gate. The output of the crossbar NAND gate is connected to the **Q** output and the input of another AND gate. The output of this second AND gate is connected to the input of a final crossbar NAND gate, which produces the **Q'** output. The clock input **CLK** is connected to a NOT gate, and its output is connected to the clock inputs of all four AND gates in the circuit. Red arrows indicate the signal path from **D** through the NOT gate and AND gates to the crossbar NAND gate. A blue arrow indicates the clock signal path from **CLK** through the NOT gate to the clock inputs of the AND gates. The text "Same setup time as before" and "Clock is delayed through the NOT gate" is present.

Same setup time as before

Clock is delayed through the NOT gate

Clock is delayed through the NOT gate


Falling Edge Hold Time (t_{hold})

 

$t_{\text{hold}} = 0\text{ns}$ (AND gates turn off immediately)


You have to keep the old D value there until the AND gates are shut off... (but no longer)

Rising Edge Hold Time (t_{hold})

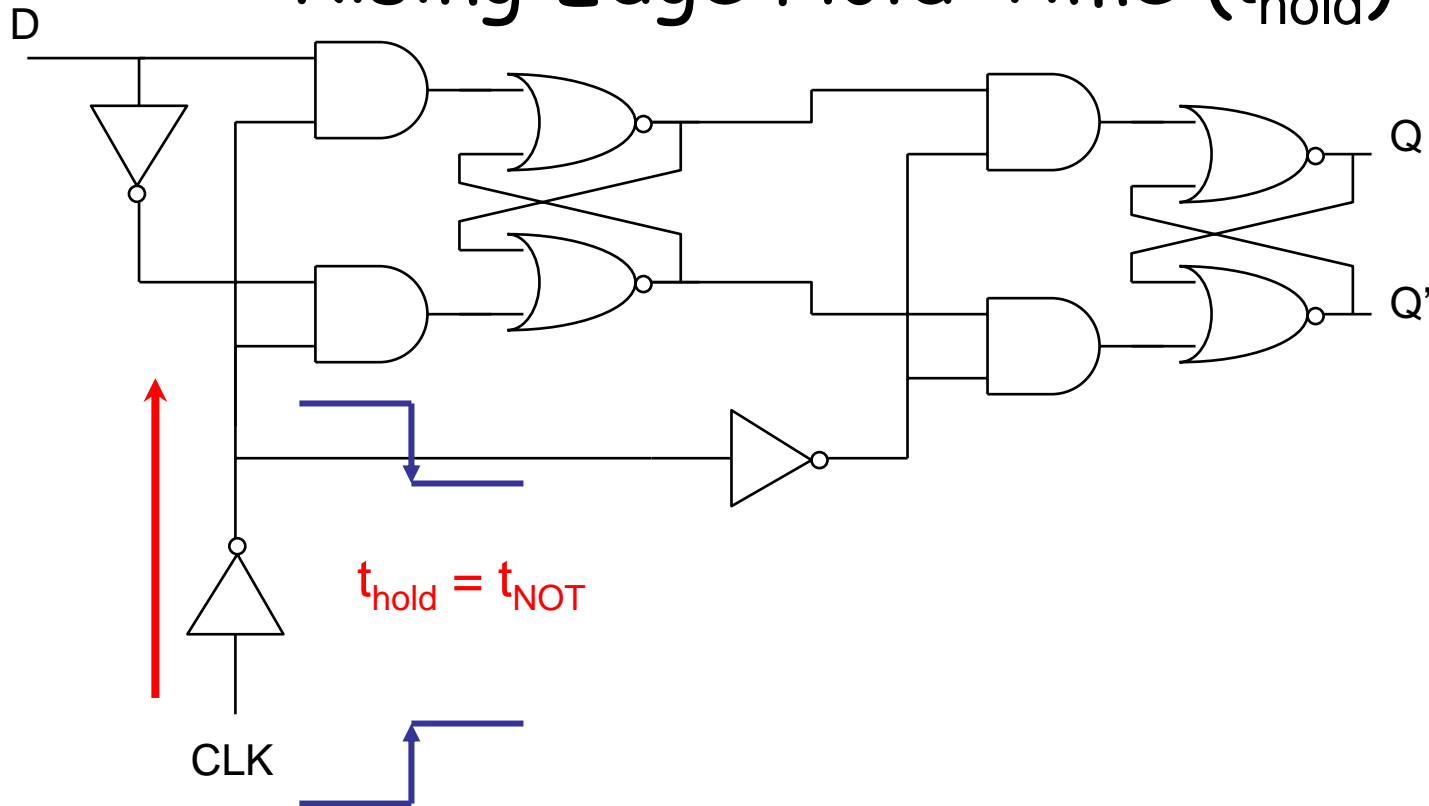


You have to keep the old D value there until the AND gates are shut off...


Timing of a Synchronous System

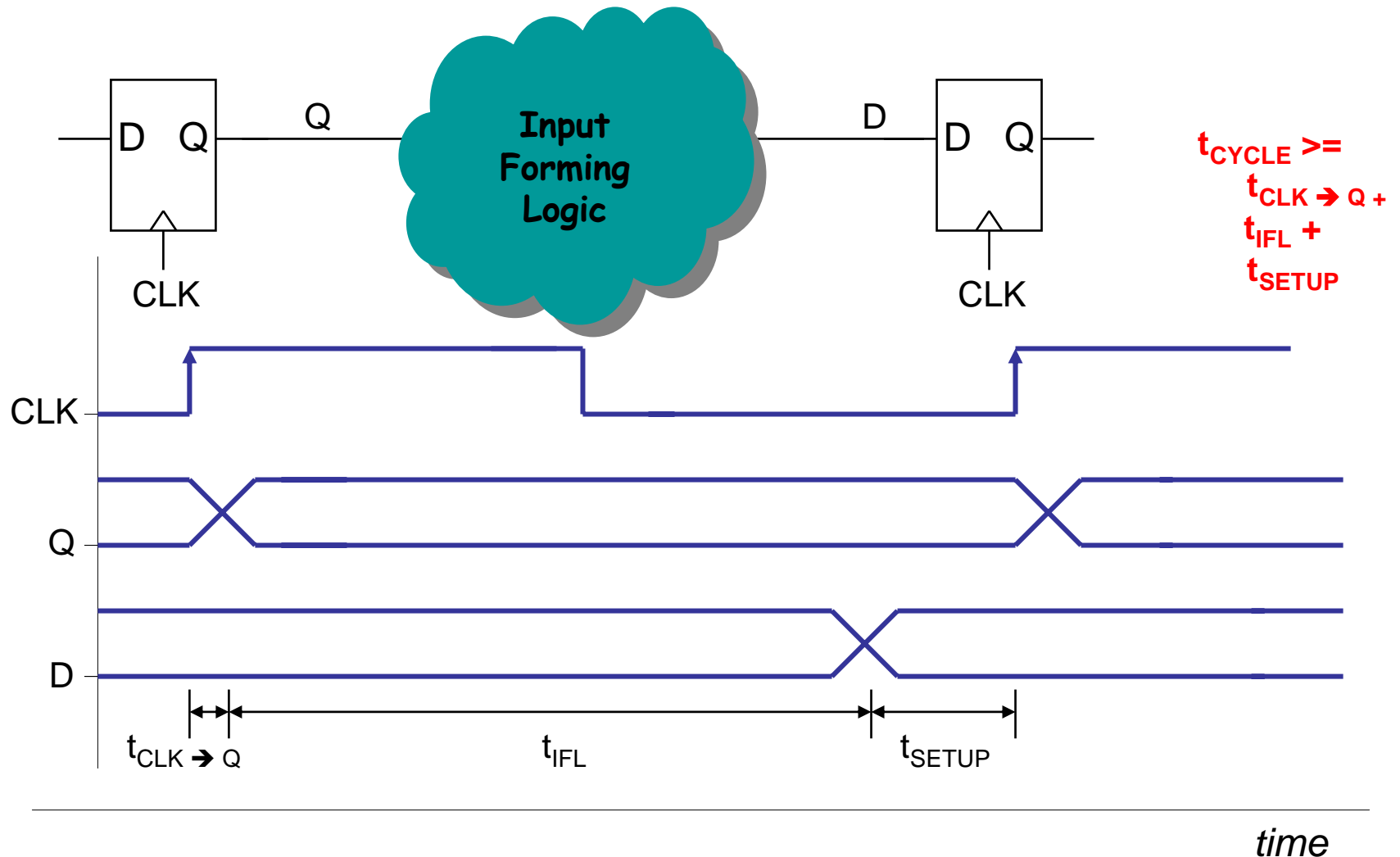


Example of a Synchronous System

 

General Sequential Systems

 

A Sequential Counter

 

Clock edges...

The current state loads the next state values in response to the clock edge.

IFL reacts after some gate delays to produce a new next state.

Transition Table for 2-Bit Counter

Current State	Next State
00	01
01	10
10	11
11	00

Current State		Next State	
Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0


It is the truth table for the input forming logic...

It describes what the *next state* values are as a function of the *current state* (clock is assumed)

General Counter Design Procedure

- Write transition table for counter
 - Use X's as appropriate
- Reduce each Nx variable to an equation
- Implement input forming logic (IFL) using gates
- Draw schematic using FF's + IFL

Counters With Outputs

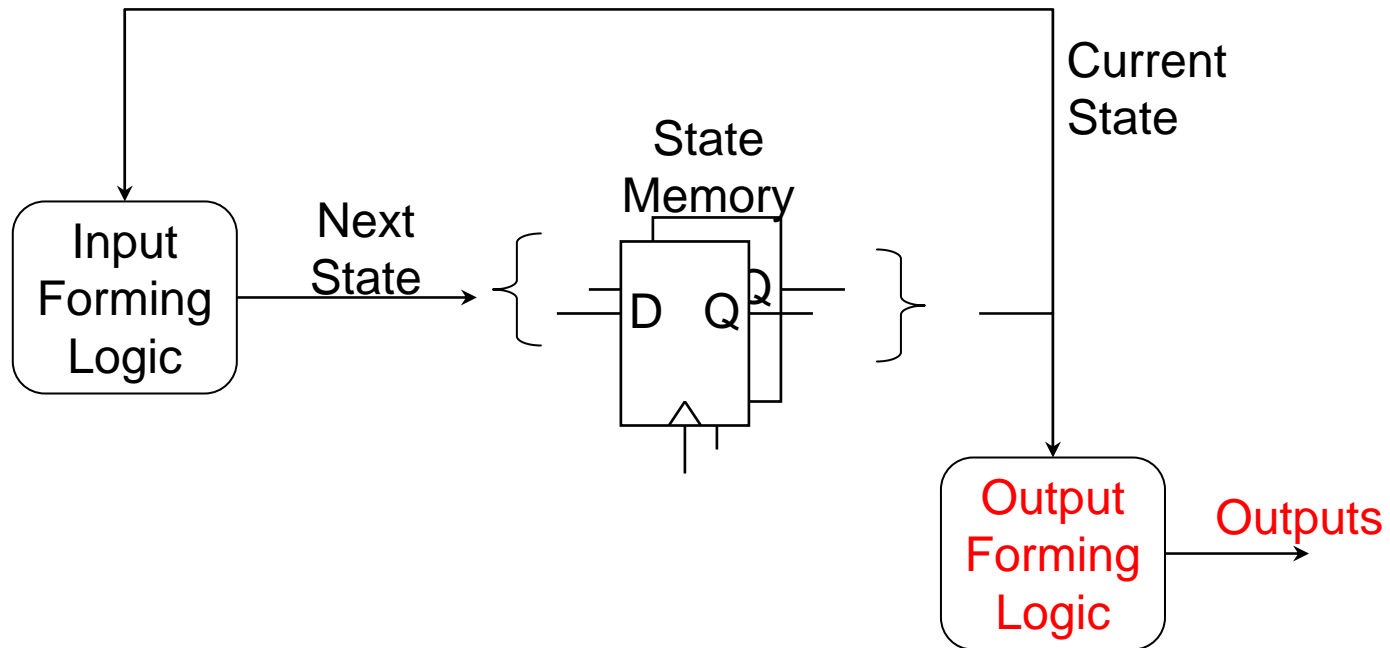

$$\text{Outputs} = f(\text{CurrentState})$$

Combined Transition Table

Q2	Q1	Q0	N2	N1	N0	Z
0	0	0	0	0	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	0
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	0	0
1	1	0	1	1	1	1
1	1	1	0	0	0	0


$$Z = Q2'Q1'Q0' + Q2'Q1Q0 + Q2Q1Q0'$$

(implement OFL with gates)

State Graphs

Binary Counter State Graph


Q1	Q0	N1	N0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

 

State graphs are graphical representations of TT's

They contain the same information: no more, no less

State Graphs for Counters With Inputs

 

INC controls whether transition is taken or not...

INC	Q1	Q0	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

There is a one-to-one correspondence between the rows of the TT and the arcs in the SG

Transition Table Simplification

CLR	INC	Q1	Q0	N1	N0		CLR	INC	Q1	Q0	N1	N0		CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0		0	0	0	0	0	0		0	0	0	0	0	0
0	0	0	1	0	1		0	0	0	1	0	1		0	0	0	1	0	1
0	0	1	0	1	0		0	0	1	0	1	0		0	0	1	0	1	0
0	0	1	1	1	1		0	0	1	1	1	1		0	0	1	1	1	1
0	1	0	0	0	1		0	1	0	0	0	1		0	1	0	0	0	1
0	1	0	1	1	0		0	1	0	1	1	0		0	1	0	1	1	0
0	1	1	0	1	1		0	1	1	0	1	1		0	1	1	0	1	1
0	1	1	1	0	0	→	0	1	1	1	0	0	→	0	1	1	1	0	0
1	0	0	0	0	0		1	-	0	0	0	0		1	-	-	-	0	0
1	0	0	1	0	0		1	-	0	1	0	0							
1	0	1	0	0	0		1	-	1	0	0	0							
1	0	1	1	0	0		1	-	1	1	0	0							
1	1	0	0	0	0														
1	1	0	1	0	0														
1	1	1	0	0	0														
1	1	1	1	0	0														

These are input don't cares.
 They are a shorthand for the TT on the left
 This TT exactly matches SG on previous page

Simplified Transition Tables With Input Don't Cares

- Contain exactly same information as original
 - Shorthand way of writing
- Should be able to easily convert back/forth

Design Procedure Using State Graphs


1. Draw the state graph
2. Create an equivalent transition table
3. If transition table contains input don't cares,
 - *unfold* it to a full transition table
4. Complete the design using KMaps, gates, FF's

Cascaded Counters


A Mod4 Counter With a Rollover Signal

CLR	INC	Q1	Q0	N1	N0	Rollover
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	0	0	1
1	-	-	-	0	0	0

 Signal Rollover can be used to tell other circuitry that counter is rolling over to all 0's



Cascading 2 Mod4 Counters

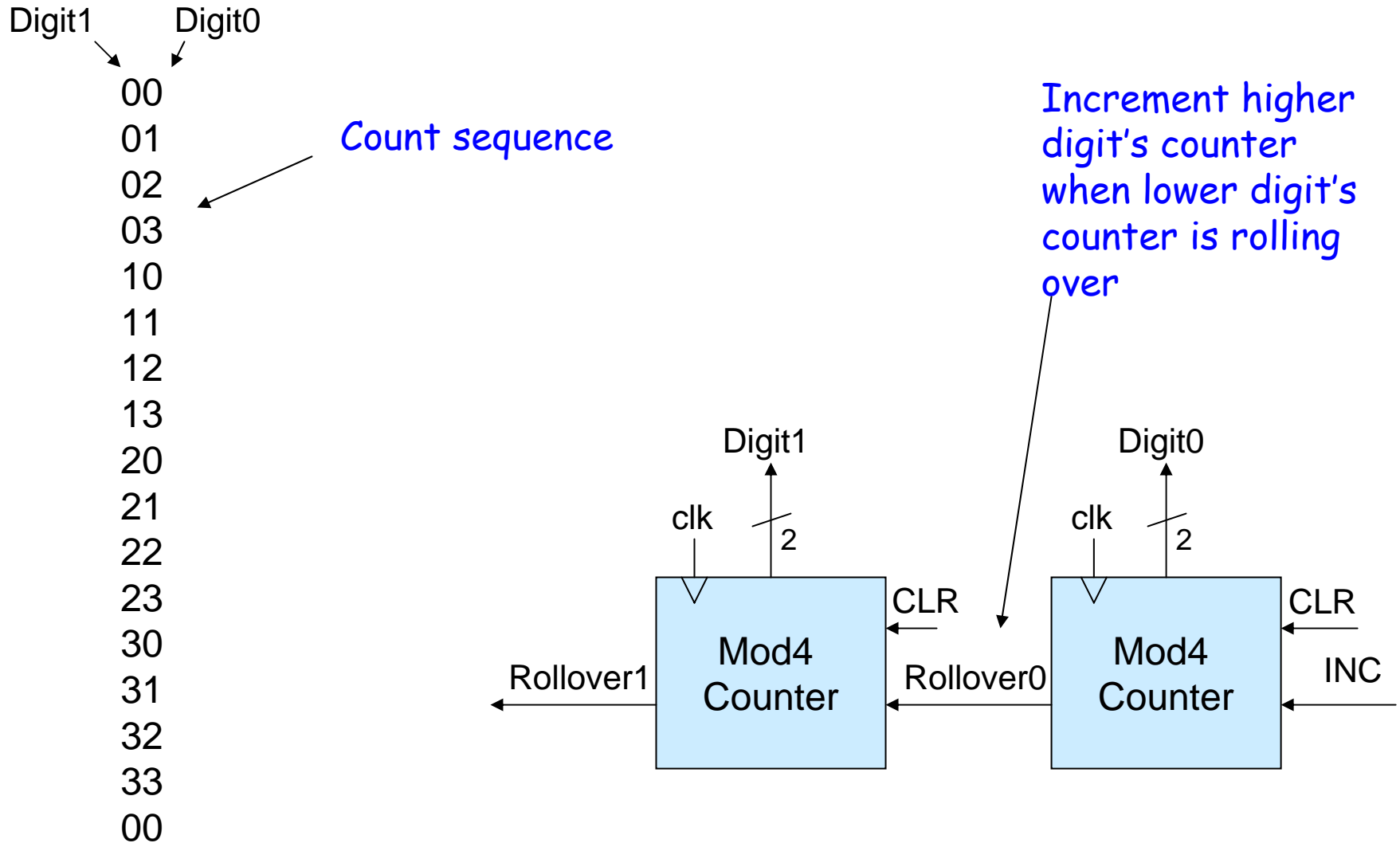


3 Digits' Worth

Increment higher
digit's counter
when lower digit's
counter is rolling
over

Can do this with any
counter that has
a Rollover output

 Could build a digital watch
or clock circuit this way with
Mod60 and Mod24 counters



Cascading Counters


- A counter will increment only when
 - The counter below it is at its terminal count **and** it is being incremented
 - That is the definition of the Rollover signal
- Some people try to tie Rollover to the clk input of the next higher counter
 - Bad idea... Very bad idea...
 - Violates our Globally Synchronous policy
 - Doesn't work as intended

Ripple Counters

- When you tie a rollover-like signal to a clock on the next higher digit \Leftrightarrow ripple counter
- A ripple counter is an **ASYNCHRONOUS** counter
 - Transitions are not all synchronized to the clock
 - Different flip flops change at different times
 - Similar to gated clocks (seen earlier)
- Asynchronous circuits are an advanced topic


Sequence is:

 0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111
0000




So what is the problem?

Mod4 Counter

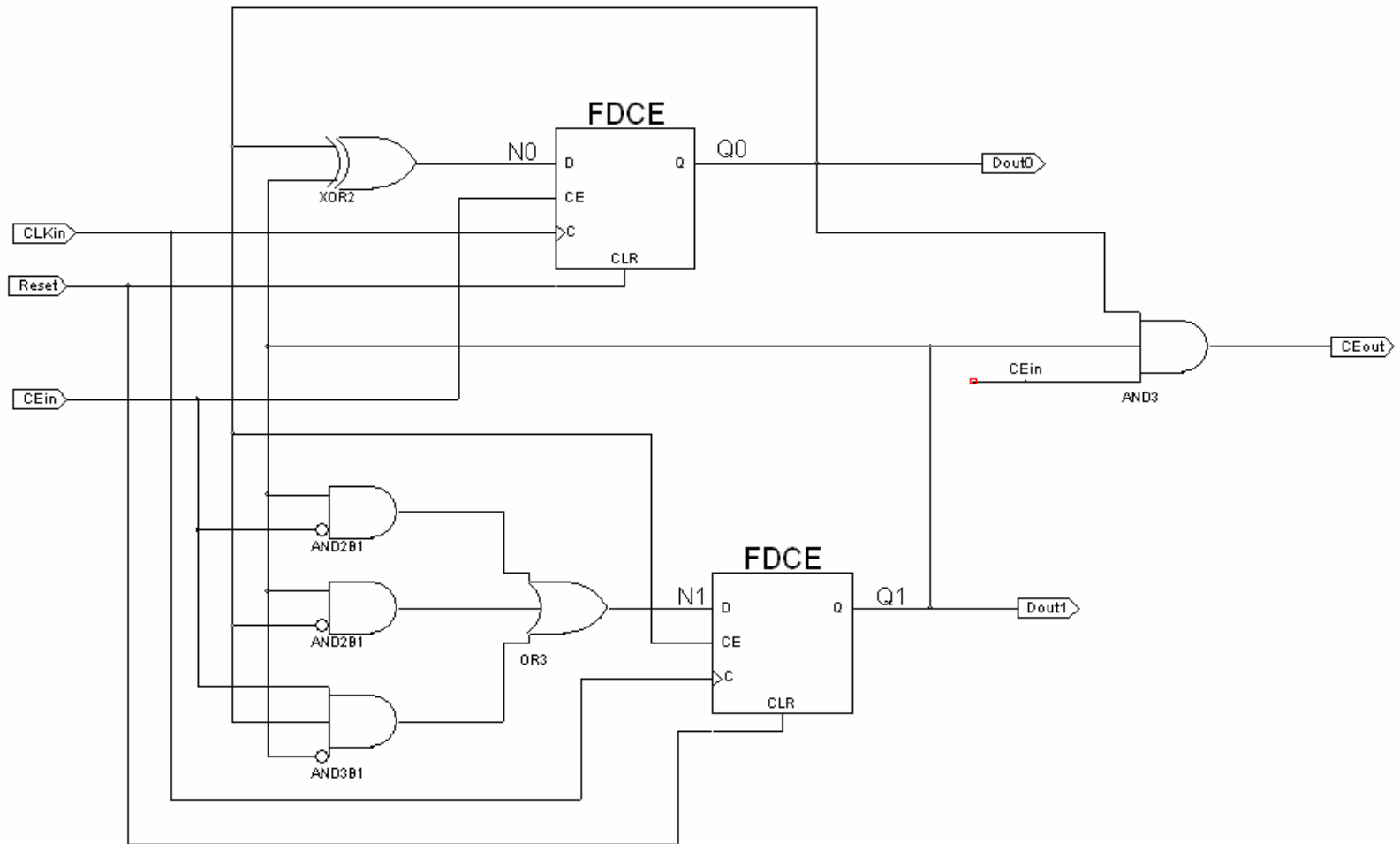


A Mod4 Counter

The right way!


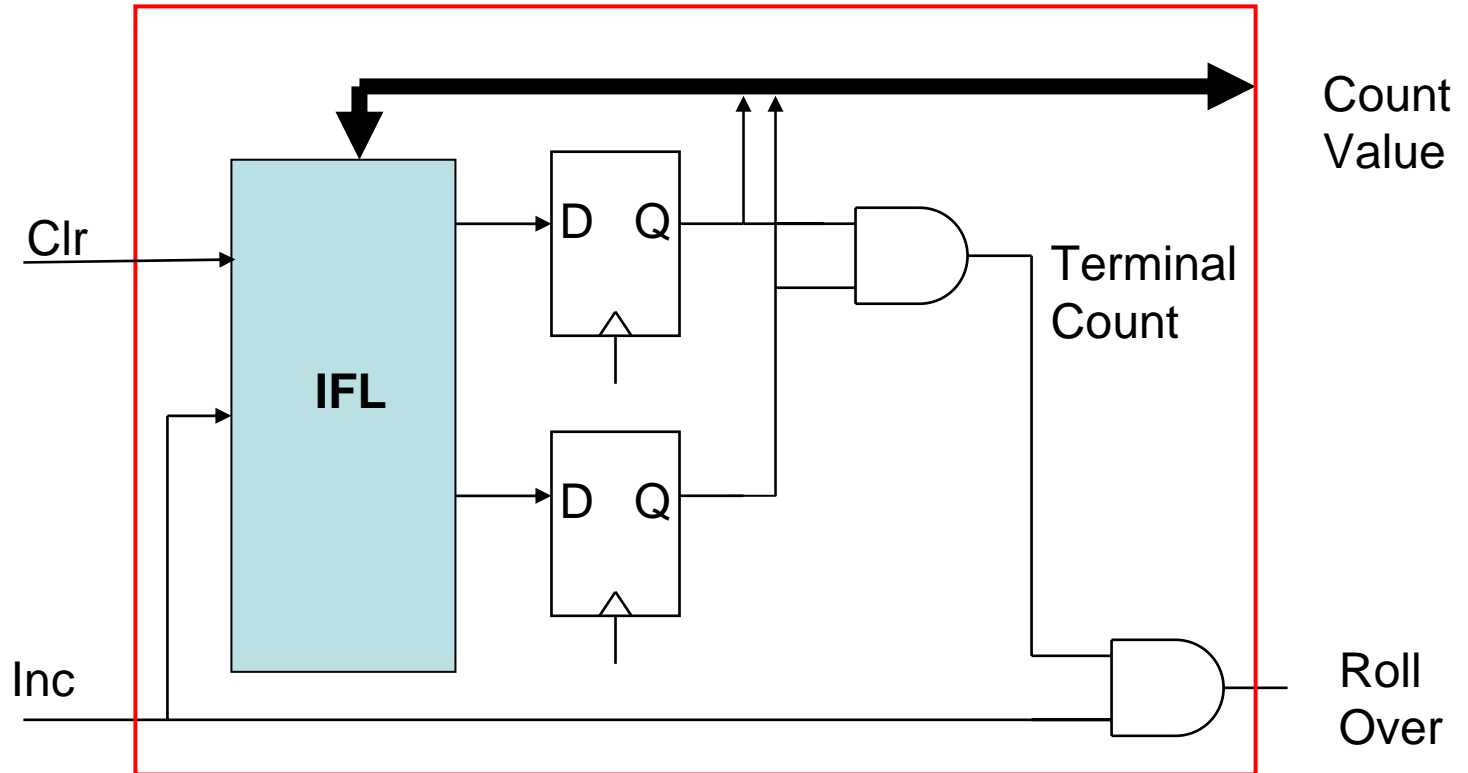


A Mod4 Counter

 

Registers


A 4-Bit Register

 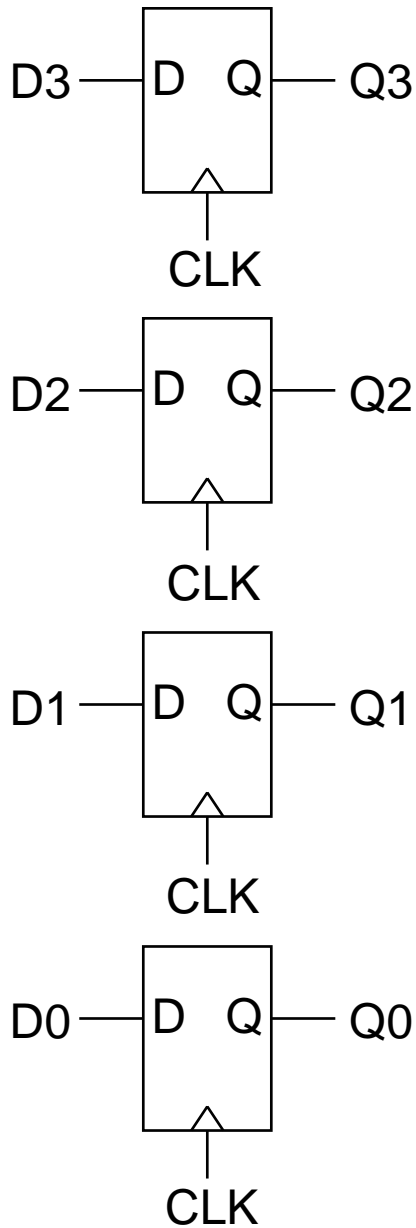

Could be called a parallel-in/parallel-out register.

Why?


A Shift Register

 


cycle 0	1	0	1	1
cycle 1	0	1	0	1
cycle 2	0	0	1	0
cycle 3	0	0	0	1
cycle 4	0	0	0	0

Called a serial-in, parallel-out shift register (SIPO)

SIPO Register (Serial-In/Parallel-Out)

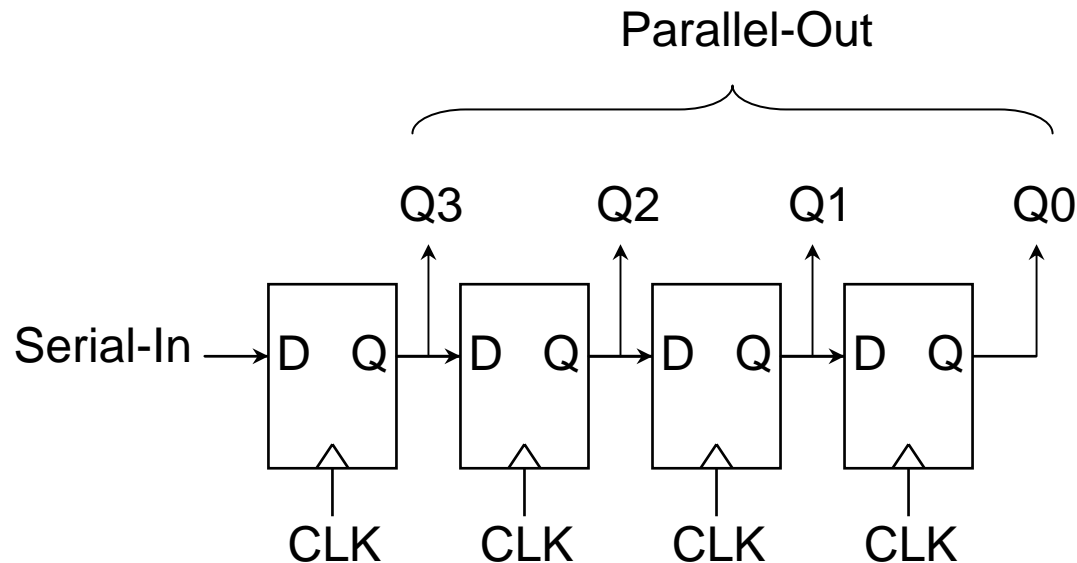

SISO Register (Serial-In/Serial-Out)

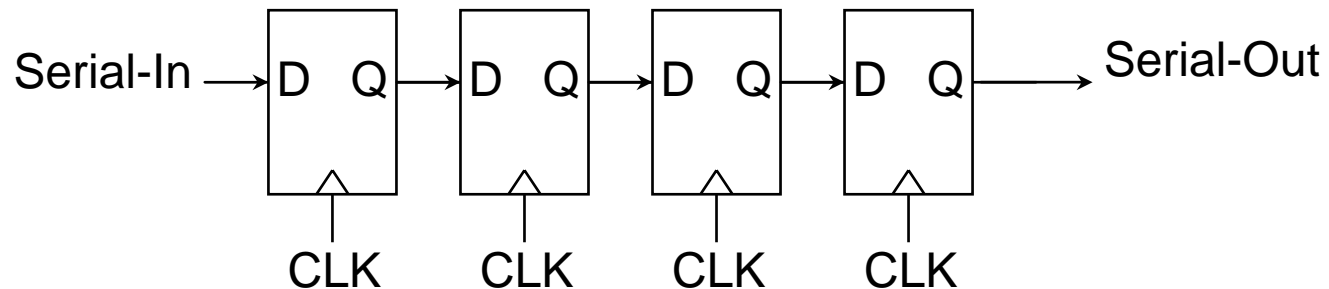

Useful for delaying a serial bit-stream some number of cycles...


Gated Clocking

- Different flip flops load at different times
 - A form of *clock skew*
 - Makes doing timing analysis more difficult
 - Can lead to circuits which run more slowly
 - Can lead to circuits which fail at any clock rate

Globally Synchronous Design

- One global clock
- All registers load on that clock's edge
- Control over loading done via input forming logic (IFL)
- Simplifies timing analysis and requirements
- Makes it possible for even novices to design large, functioning circuits
- Multi-clock circuits \Leftrightarrow next semester's topic

 
The Correct Way To Make A Loadable Register (1-Bit)



When $\text{LOAD} = '0'$, FF loads old value

When $\text{LOAD} = '1'$, FF loads DIN

 A Loadable Parallel-In, Parallel-Out Register



PIPO ?


MUX for Register Control

- Loadable register concept can be generalized
 - Provide any combination of inputs to register

Uses of Shift Registers

- Collecting serial input data into a parallel word
- Shifting out bits of a word
- Delaying a serial stream by some # of cycles

A Clearable Counter

 


CLR	INC	Q+
0	0	Q
0	1	Q+1
1	0	0
1	1	Q

From there to here, from here to there,
interesting circuits are everywhere...


(when you have a MUX and some flip flops)

An Up/Down Counter

 

How about an up/down counter + bi-directional shift register design?

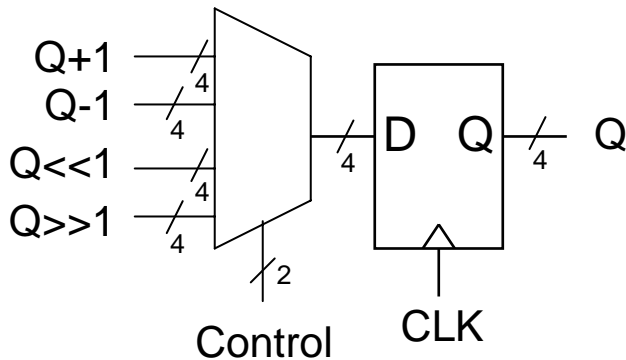Up/Down Counter + Bi-Directional Shift Register




Control	NextQ
00	$Q+1$
01	$Q-1$
10	Q shifted left
11	Q shifted right

An Accumulator


Values to be added are placed on A input, one per cycle. Register accumulates their sum.

Version A

 

This one loads 0 when CLR='1'

Version B

 


This one loads A when CLR='1'

Both work, they just have different timings...


Register Files

Small memories holding multiple words of data


Typical Register File

 

Building a Register File

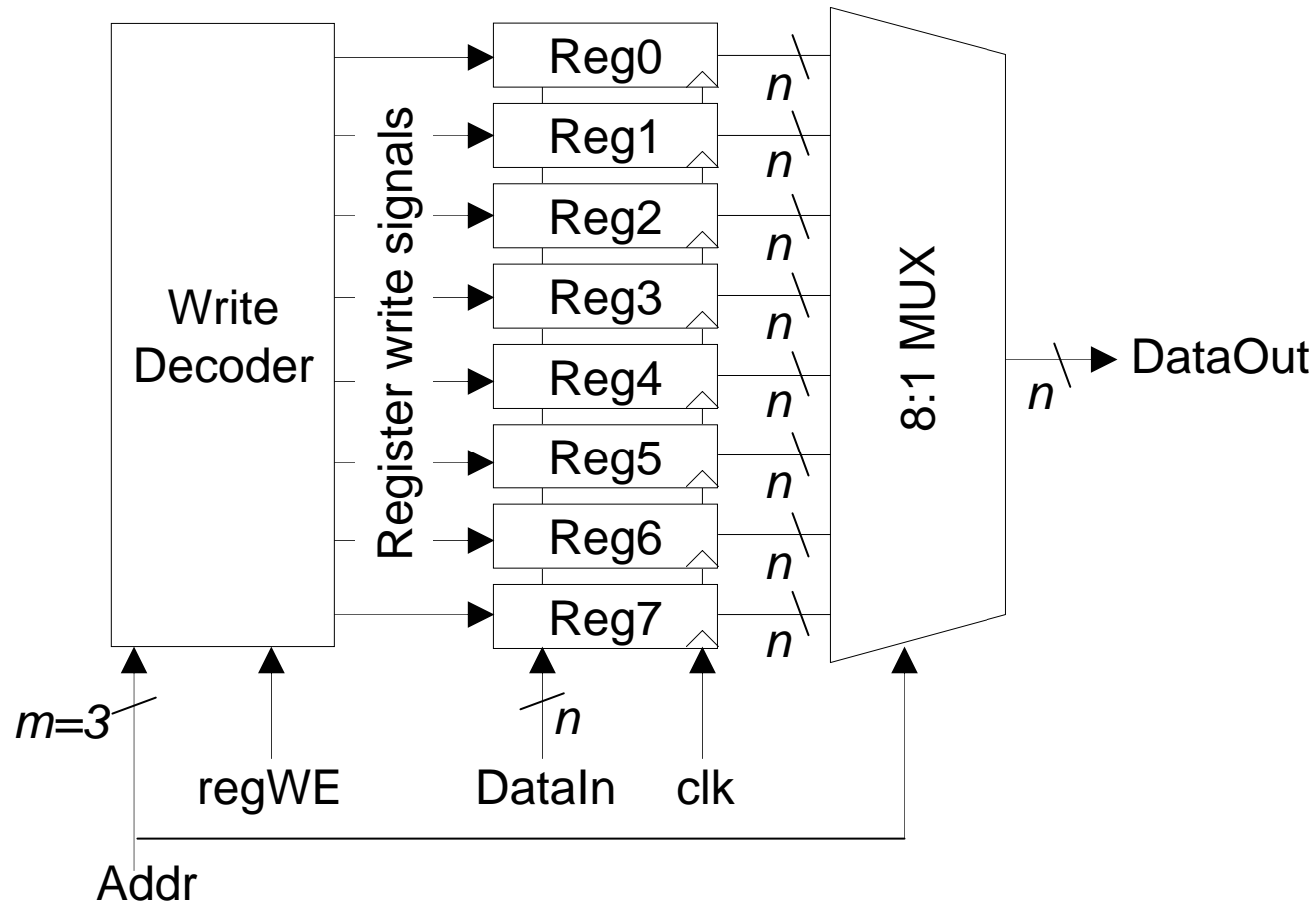

Multi-Ported Register File

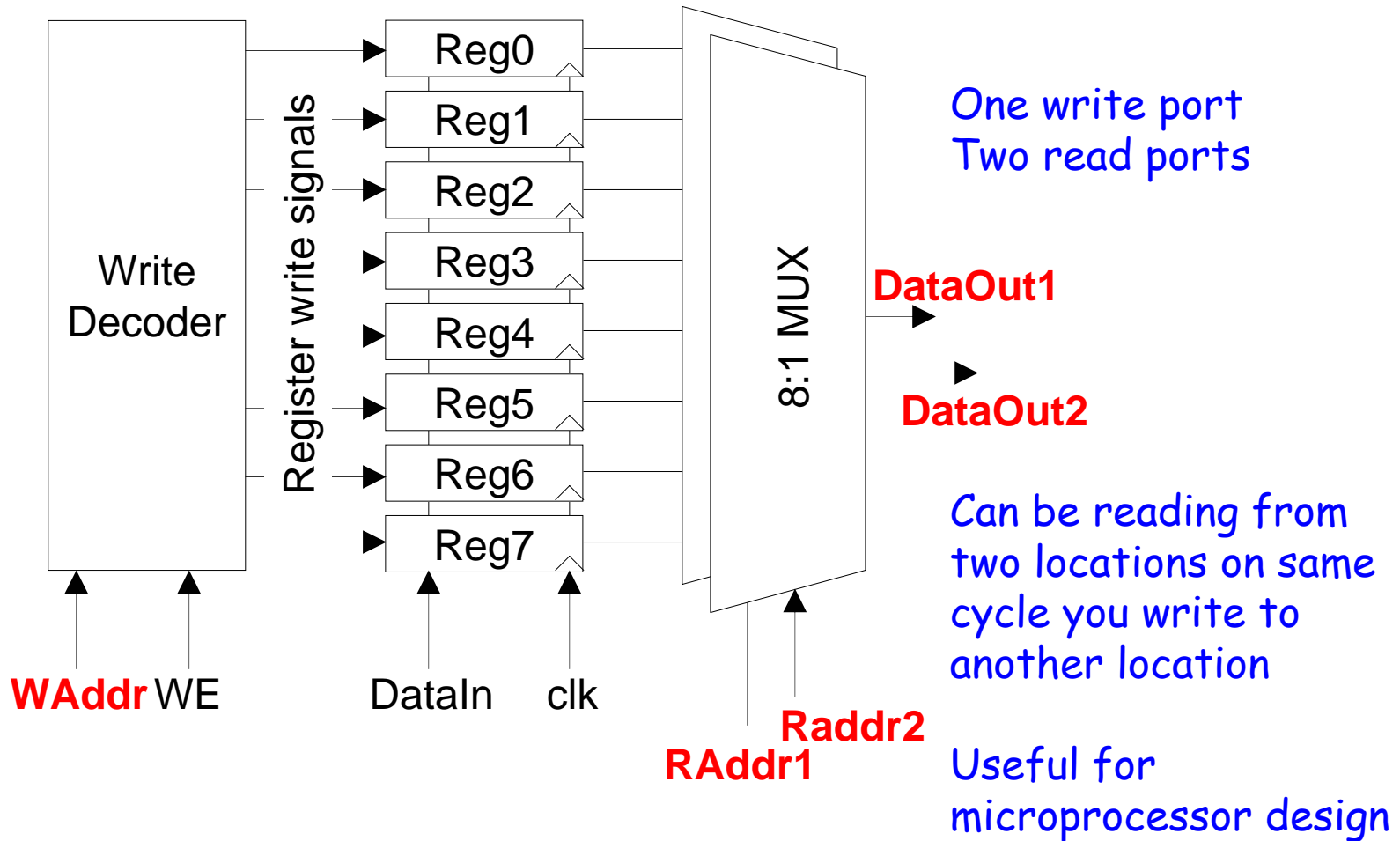

Memories vs. Register Files

- Random Access Memory (RAM) is similar to a register file
 - Stores many multi-bit words for reading/writing
- RAM usually only single-ported
- RAM usually much, much larger
 - Mbytes instead of bytes
- RAM implementation *conceptually* the same as register file
 - Transistor-level implementation different due to size/usage characteristics
- RAM design beyond the scope of this class

Finite State Machines

State Machine Concepts

- State, current state, next state, state registers
- IFL, OFL, Moore outputs, Mealy outputs
- Transition tables
 - With output don't cares (X's)
 - With input don't cares (-'s)
- State graphs
 - And their correspondence to TT's

State Machines

- A state machine is a *sequential circuit* which progresses through a series of states in response to inputs
 - The output values are usually significant
 - The state encodings are usually not significant
 - Unlike with counters

Implementing the Sequence Detector FSM

1. Create symbolic Transition Table
2. Assign state encoding
3. Create conventional Transition Table
4. Do standard implementation steps

Xin	CS	NS	Z
0	S0	S1	0
1	S0	S0	0
0	S1	S1	0
1	S1	S2	0
0	S2	S1	0
1	S2	S3	0
-	S3	S3	1

Symbolic TT

S0 = 00
 S1 = 01
 S2 = 10
 S3 = 11

State Assignment

Xin	Q1	Q0	N1	N0	Z
0	0	0	0	1	0
1	0	0	0	0	0
0	0	1	0	1	0
1	0	1	1	0	0
0	1	0	0	1	0
1	1	0	1	1	0
-	1	1	1	1	1


Conventional TT

Sequence Detector Implementation

$$N1 = Q1 \cdot Q0 + X_{in} \cdot Q1 + X_{in} \cdot Q0$$

$$N0 = X_{in}' + Q1$$

$$Z = Q1 \cdot Q0$$

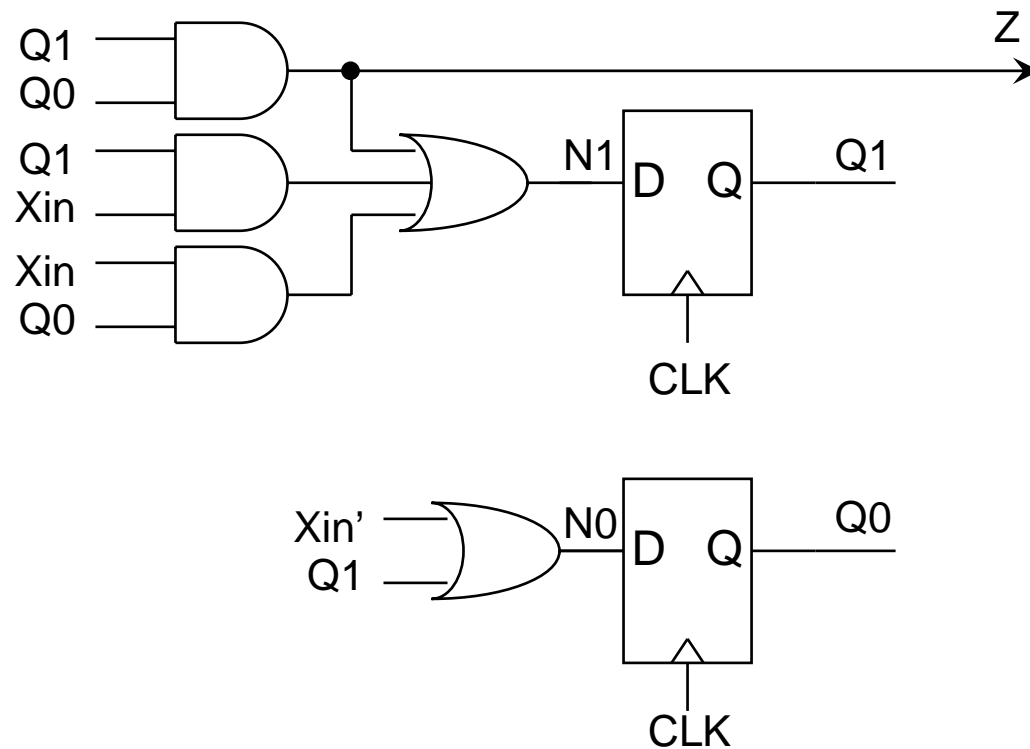

Resetting State Machines

- Ability to reset the FSM is essential for testing most systems
- Always include a reset capability
 - Add CLR signal to state graph
 - Use flip flops with clear inputs
 - Either method will work

One-Hot Encoded Finite State Machines

One-Hot - Observations

- Choosing a one-hot encoding results in many, many don't cares in transition table
- Minimization results in simpler IFL and OFL
- Can do one-hot design by inspection
 - *without using transition tables...*

Other State Encoding Techniques

- You have learned the 2 extremes
 - Fully encoded (8 states \Leftrightarrow 3 state bits)
 - One-hot encoded (8 states \Leftrightarrow 8 state bits)
- A range of options exist in between
- A good choice of encoding
 - Can minimize IFL and OFL complexity
 - Algorithms have been developed for this...
 - Beyond the scope of this class