
 


Microprogrammed Control


Sample Control Unit FSM

 

Sample Output Forming Logic



 One-hot encoding leads
to pretty simple OFL!




The Control Unit

- The LC-3 control lecture discussed a hard-wired approach to controller design
 - The functionality is fixed after the design
- **Microprogrammed controllers** allow functionality to be easily changed
 - Instructions can be added or changed with only minor changes to the *microcode*

Microprogrammed Control

An internal memory called the **control store** (or Microstore) contains the settings for all of the control signals for all.

 
Each memory location contains one complete set of control values.



Microprogrammed Control


An internal memory called the **control store** (or microstore) contains the settings for all of the control signals for all.

 Each memory location contains one complete set of control values.




Microprogrammed Control

 How do you determine which control string to use?




Microprogrammed Control

 
Use a register to select the address in memory which contains the appropriate control string.




Microprogrammed Control

 

Microprogrammed Control

 


Microprogrammed Control

 


Microprogrammed Control

 Use incrementer to get sequential control strings.



Decode

 


Use a lookup table to get to the appropriate control strings after an instruction has been loaded into the Instruction Register.

This occurs in the Decode stage of the instruction.


Decode

 Use a MUX to select between the sources for the μ Code Address.




Microprogrammed Control

Instruction Execution

 


Microprogrammed Control

How to return to the fetch cycle?

 


Microprogrammed Control

 Use a special field to designate the next address which should be executed!



Jump to a New μ Code Address

 Because of the Target Address field, the incrementer is no longer needed.




Selecting Operand and Destination Register Addresses

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCoffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCoffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	


LD	0010	DR	PCoffset9										
LDI	1010	DR	PCoffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCoffset9										
ST	0011	SR	PCoffset9										
STI	1011	SR	PCoffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												

Selecting Operand and Destination Register Addresses

 Two more control signals are required in the μ Store: SR1 and DR. These signals select the source for the register addresses.



 
Selecting Operand and Destination Register Addresses



Selecting Load Program Counter Sources


For a Branch instruction, loading of the PC depends upon the N, Z and P register flags and the n, z and p bits in the instruction.

 Another control signal is needed to select the source for the load PC control signal.



Selecting Load Program Counter Sources

 'Special Code' bit for branch instruction



Selecting Jump Subroutine MUX control sources

The two types of JSR instructions use different control signals but share the same opcode.

JSR	clock1	$R7 \leftarrow PC$	$enaPC \leftarrow 1$
			$DR \leftarrow 7$
			$regWE \leftarrow 1$
	clock2	$PC \leftarrow EAddr$	$selEAB1 \leftarrow 0$
			$selEAB2 \leftarrow 11$
			$selPC \leftarrow 01$
			$ldPC \leftarrow 1$
JSRR	clock1	$R7 \leftarrow PC$	$enaPC \leftarrow 1$
			$DR \leftarrow 7$
			$regWE \leftarrow 1$
	clock2	$PC \leftarrow EAddr$	$selEAB1 \leftarrow 1$
			$selEAB2 \leftarrow 00$
			$selPC \leftarrow 01$
			$ldPC \leftarrow 1$

Selecting Jump Subroutine MUX control sources


Use IR[11] to distinguish between the two forms of JSR.

JSR	0100	1
JSRR	0100	0

JSR	clock1	$R7 \leftarrow PC$	$enaPC \leftarrow 1$
			$DR \leftarrow 7$
			$regWE \leftarrow 1$
	clock2	$PC \leftarrow EAddr$	$selEAB1 \leftarrow 0$
			$selEAB2 \leftarrow 11$
			$selPC \leftarrow 01$
			$ldPC \leftarrow 1$
JSRR	clock1	$R7 \leftarrow PC$	$enaPC \leftarrow 1$
			$DR \leftarrow 7$
			$regWE \leftarrow 1$
	clock2	$PC \leftarrow EAddr$	$selEAB1 \leftarrow 1$
			$selEAB2 \leftarrow 00$
			$selPC \leftarrow 01$
			$ldPC \leftarrow 1$

Selecting Jump Subroutine MUX control sources

 Luckily, the control signals which differ are the complements of each other.



JSR **clock2** PC ← EAddr

selEAB1 ← 0

selEAB2 ← 11


JSRR **clock2** PC ← EAddr

selEAB1 ← 1

selEAB2 ← 00

 00: --
01: decode
10: branch
11: JSRcond


Again, we require 'Special Code' to specify when a JSR instruction is being executed.




Use XOR gates to perform the selective complement function.

Selecting Jump Subroutine

MUX control sources

 

00: --
01: decode
10: branch
11: JSRcond

 

MicroStore

		Special Codes		Target Address	Sr1	DR	ALU Ctrl	selPC	selEAB1	selEAB2	enaALU	regWE	enaMM	selMAR	enaPC	ldPC	ldIR	ldMAR	ldMDR	selMDR	memWE	enaMDR
0	Reset	0	0	00001	0	0	00	00	0	00	0	0	0	0	0	0	0	0	0	0	0	0
1	Fetch	0	0	00002	0	0	00	00	0	00	0	0	0	0	1	0	0	1	0	0	0	0
2		0	0	00003	0	0	00	00	0	00	0	0	0	0	0	0	0	0	1	1	0	0
3		0	0	00004	0	0	00	00	0	00	0	0	0	0	0	0	1	0	0	0	0	1
4	Decode	1	0	00000	0	0	00	00	0	00	0	0	0	0	0	0	0	0	0	0	0	0
5	ADD	0	0	00001	0	0	01	00	0	00	1	1	0	0	0	0	0	0	0	0	0	0
6	AND	0	0	00001	0	0	10	00	0	00	1	1	0	0	0	0	0	0	0	0	0	0
7	BR	0	1	00001	0	0	00	01	0	10	0	0	0	0	0	0	0	0	0	0	0	0
8	JMP	0	0	00001	0	0	00	01	1	00	0	0	0	0	0	1	0	0	0	0	0	0
9	JSR/R	0	0	01010	0	1	00	00	0	00	0	1	0	0	1	0	0	0	0	0	0	0
10		1	1	00001	0	0	00	01	1	00	0	0	0	0	0	1	0	0	0	0	0	0
11	LD	0	0	01100	0	0	00	00	0	10	0	0	1	0	0	0	0	1	0	0	0	0
12		0	0	01101	0	0	00	00	0	00	0	0	0	0	0	0	0	0	1	1	0	0
13		0	0	00001	0	0	00	00	0	00	0	1	0	0	0	0	0	0	0	0	0	1
14	LDI	0	0	01111	0	0	00	00	0	10	0	0	1	0	0	0	0	1	0	0	0	0
15		0	0	10000	0	0	00	00	0	00	0	0	0	0	0	0	0	0	1	1	0	0
16		0	0	01100	0	0	00	00	0	00	0	0	0	0	0	0	0	1	0	0	0	1
17	LDR	0	0	01100	0	0	00	00	1	01	0	0	1	0	0	0	0	1	0	0	0	0
18	LEA	0	0	00001	0	0	00	00	0	10	0	1	1	0	0	0	0	0	0	0	0	0
19	NOT	0	0	00001	0	0	11	00	0	00	1	1	0	0	0	0	0	0	0	0	0	0
20	ST	0	0	10101	0	0	00	00	0	10	0	0	1	0	0	0	0	1	0	0	0	0
21		0	0	10110	1	0	00	00	0	00	1	0	0	0	0	0	0	0	1	0	0	0
22		0	0	00001	0	0	00	00	0	00	0	0	0	0	0	0	0	0	0	0	1	0
23	STI	0	0	11000	0	0	00	00	0	10	0	0	1	0	0	0	0	1	0	0	0	0
24		0	0	11001	0	0	00	00	0	00	0	0	0	0	0	0	0	0	1	1	0	0
25		0	0	10101	0	0	00	00	0	00	0	0	0	0	0	0	0	1	0	0	0	1
26	STR	0	0	10101	0	0	00	00	1	01	0	0	1	0	0	0	0	1	0	0	0	0

Instruction Lookup Table

Op-code	Instruction	Next Address (decimal)	Next Address (binary)
0000	BR	7	00111
0001	ADD	5	00101
0010	LD	11	01011
0011	ST	20	10100
0100	JSR	9	01001
0101	AND	6	00110
0110	LDR	17	10001
0111	STR	26	11010
1000	RTI	----	---
1001	NOT	19	10011
1010	LDI	14	01110
1011	STI	23	10111
1100	JMP	8	01000
1101	----	----	----
1110	LEA	18	10010
1111	TRAP	----	----