


References

[1] F. A. Linholm IEEE J. Solid State Circuits, SC-10, 2, pp. 106–109, April 1975.

Exercises


Inverter Static Voltage Characteristics

 - 5-1.** A CMOS inverter has $V_{DD} = 1.2$ V. $V_{OH} = 1.15$ V, $V_{OL} = 0.15$ V, $V_{IH} = 1.05$ V, and $V_{IL} = 0.2$ V. Calculate NM_H , NM_L and draw the noise margin map with appropriate labels of numbers.




- 5-2.** A logic gate noise margin parameters are: $V_{IH} = 1.6$ V, $V_{IL} = 0.3$ V, $V_{OH} = 1.7$ V, and $V_{OL} = 0.2$ V.
- Calculate NM_H .
 - Calculate NM_L .
 - The input voltage is down to 1.7 V and a negative 50 mV noise spike appears. What happens to the circuit fidelity?
 - The input voltage is down to 1.7 V and a negative 150 mV noise spike appears. What happens to the circuit fidelity?

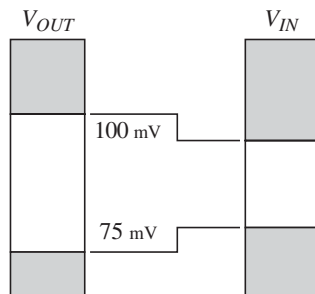
- 5-3.** Given the logic gate noise margins: $NM_H = 100$ mV, $NM_L = 75$ mV, and $V_{DD} = 2$ V.
- If $V_{IH} = 1.75$ V, what is V_{OH} ?
 - If $V_{IL} = 0.3$ V, what is V_{OL} ?



 - 5-4.** A CMOS inverter uses $V_{DD} = 0.9$ V. $V_{OH} = 0.8$ V, and $V_{OL} = 0.1$ V. If the noise margins must be 20% of V_{DD} , what are V_{IL} and V_{IH} ? Draw the noise margin map and label.




 - 5-5.** Graphically determine the change in logic threshold of the CMOS inverter transfer curve in the figure if the curve shifts 0.2 V to the right in the midregion.



- 5-6. (a)** Design the W_p/W_n ratios of a CMOS inverter for symmetrical static voltage transfer characteristic. $\mu_n = 1400$ $\text{cm}^2/\text{V} \cdot \text{s}$, $\mu_p = 500$ $\text{cm}^2/\text{V} \cdot \text{s}$, $V_m = 0.35$ V, $V_{tp} = -0.35$ V, and $V_{DD} = 1.3$ V.

(b) Redesign if $V_{tp} = -0.45$ V.

 

5-7. An inverter with a symmetrical voltage transfer curve has a restriction that $W_p/W_n = 4.6$. $V_{DD} = 1.2$ V, $\mu_n = 1530$ cm²/V · s, $\mu_p = 540$ cm²/V · s, and $V_{tp} = -0.4$. What must V_m be set to satisfy this condition?

5-8. A CMOS inverter has transistor parameters: $K_n(W/L)_n = 100$ $\mu\text{A/V}^2$, $K_p(W/L)_p = 300$ $\mu\text{A/V}^2$, $V_{tn} = 0.7$ V, $V_{tp} = -0.75$ V, and $V_{DD} = 2.5$ V. What fraction of the total output voltage swing will the nMOS transistor be in saturation?

5-9. A CMOS inverter has its nMOS transistor in nonsaturation and its pMOS transistor in saturation. Given $K_n = 50$ $\mu\text{A/V}^2$, $K_p = 25$ $\mu\text{A/V}^2$, $V_{tn} = 0.5$ V, $V_{tp} = -0.6$ V, $(W/L)_n = 2$, $(W/L)_p = 4$, $I_{DD} = 11$ μA , and $V_{DD} = 2$ V, calculate the inverter output voltage V_O .


Inverter Static Current Characteristics

5-10. Given an inverter with $V_{DD} = 1.5$ V, $V_m = 0.4$ V, and $V_{tp} = -0.4$ V, calculate the peak current during the transition if $(W/L)_n = 3$, $(W/L)_p = 7.5$, $K_p = 50$ $\mu\text{A/V}^2$, and $K_n = 125$ $\mu\text{A/V}^2$.


5-11. An inverter has $V_{DD} = 2$ V, $V_m = 0.5$ V, $V_{tp} = -0.5$ V, $K_n = 300$ $\mu\text{A/V}^2$, $K_p = 200$ $\mu\text{A/V}^2$, $(W/L)_n = 2$, and $(W/L)_p = 3$.

(a) If $V_{IN} = 0.8$ V, what is I_{DD} ?

 
(b) The I_{DD} solution in part (a) appears twice in the current transfer curve. Use the pMOS equations to calculate the other V_{IN} value to satisfy the current in part (a).



 
5-12. Given $V_{DD} = 1.5$ V, $K_p = 70$ μA , $K_n = 120$ μA , $(W/L)_p = 150$, and $(W/L)_n = 75$, use the ITC to calculate V_{tp} .



 5-13. Given that $V_{DD} = 1.8$ V, $V_m = 0.5$ V, and $K_n = 100$ $\mu\text{A/V}^2$, what is W/L of the nMOS transistor?



 
- 5-14.** $I_{DD} = 40 \mu\text{A}$, $(W/L)_n = 2$, $K_n = 100 \mu\text{A/V}^2$, $V_{in} = 0.5 \text{ V}$, $K_p = 50 \mu\text{A/V}^2$, $V_{tp} = -0.5 \text{ V}$, and $V_i < 1.5 \text{ V}$. What is V_i ?



- 5-15.** Given an inverter with $V_{in} = 0.4 \text{ V}$, $V_{tp} = -0.35 \text{ V}$, $K_n = 200 \mu\text{A/V}^2$, $K_p = 100 \mu\text{A/V}^2$, $(W/L)_n = 2$, and $(W/L)_p = 3$, calculate the peak drain current I_{peak} during an inverter transition for (a) $V_{DD} = 1.5 \text{ V}$ and (b) $V_{DD} = 1.0 \text{ V}$.

Inverter Speed Property

 - 5-16.** Use the transition time delay model where $C_L = 30 \text{ fF}$, $V_{DD} = 1.5 \text{ V}$, $(W/L)_n = 2$, $K'_n = 100 \mu\text{A/V}^2$, $(W/L)_p = 5$, $K'_p = 25 \mu\text{A/V}^2$, $V_{tp} = -0.35 \text{ V}$, and $V_{in} = 0.35 \text{ V}$. What is the difference between rise and fall time of the transition if defined between 0 V and 1.5 V?



- 5-17.** If a pMOS transistor in an inverter has $\mu\epsilon/2T_{ox} = 28 \mu\text{A/V}^2$, $V_{tp} = -0.6 \text{ V}$, and $W/L = 6$, what is the expected additional rise time delay if the gate power supply voltage is reduced from a normal $V_{DD} = 2.5 \text{ V}$ to $V_{DD} = 1.8 \text{ V}$ with $C_L = 25 \text{ fF}$.
- 5-18.** A CMOS inverter has $W/L = 6$ for both transistors, $V_{in} = 0.6 \text{ V}$, $V_{tp} = -0.6 \text{ V}$, and $V_{DD} = 2.3 \text{ V}$. If V_i is reduced to $|V_i| = 0.2 \text{ V}$ for

both transistors, what is the percent decrease in speed of transition?

Inverter Power

- 5-19.** Calculate the power dissipated by a cardiac pacemaker circuit if $f_{clk} = 32.6 \text{ kHz}$, $\alpha = 0.1$, $V_{DD} = 1.5 \text{ V}$, C_L (per gate) = 300 fF, and the number of logic gates = 10 k.
- 5-20.** A clock network has $C_L = 10 \text{ nF}$, $\alpha = 1$, and $V_{DD} = 1.2 \text{ V}$. The maximum power dissipation allowed is 5 W. What is the maximum clock frequency?
- 5-21.** Use Figure 5-12. $V_{DD} = 0.9 \text{ V}$, $V_{in} = 0.2 \text{ V}$, $V_{tp} = -0.2 \text{ V}$, $f_{clk} = 3 \text{ GHz}$, $W/L = 3$, $K_n = 250 \mu\text{A/V}^2$, and $t_r = t_f = 40 \text{ ps}$. Calculate the mean current during the logic transition and the average power dissipated in the chip.

Power Supply Scaling

- 5-22.** Given an inverter with: $V_{in} = 0.4 \text{ V}$, $V_{tp} = -0.4 \text{ V}$, $K_n = 200 \mu\text{A/V}^2$, $K_p = 100 \mu\text{A/V}^2$, $(W/L)_n = 2$, and $(W/L)_p = 3$. Calculate the peak drain current I_{peak} during an inverter transition for (a) $V_{DD} = 1.5 \text{ V}$ and (b) $V_{DD} = 1.0 \text{ V}$.
- 5-23.** P_{sc} must be kept under 1 W. The chip has $V_{DD} = 1.5 \text{ V}$, one million transistors, and $\alpha = 0.1$. Assume that 10^6 transistors represent an equivalent 500 k inverters for analysis. What is the mean drain current per inverter?

Sizing and Inverter Buffers

- 5-24.** An output buffer has an input capacitance of 95 fF and a load capacitance of 100 pF. How many inverters are required in a fixed tapered design to minimize the propagation delay?
- 5-25.** A fixed tapered buffer has an input capacitance of 1 pF. If the output stage must drive a load of 54 pF, how many stages are needed?
- 5-26.** The number of tapered buffers in a design must be kept at no more than five to accommodate chip area constraints.
- (a) If the input gate capacitance is 50 fF, what is the maximum load capacitance that can be driven?
- (b) What is the width ratio of the last inverter W_L to the first inverter in the chain W_{in} ?