

## HW # 2

1-21.


$$R_{eq} = 2k\Omega + \left[ (3k\Omega \parallel 4k\Omega) + 5k\Omega \right] \parallel 7k\Omega \parallel 6k\Omega$$

$$R_{eq} = 4.18k\Omega$$

$$V_{6k} = \frac{2k\Omega}{4.18k\Omega} \times 10V = 4.78V$$

1-22.

Step 1:

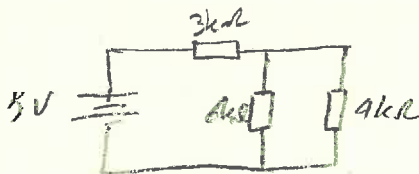


$$R_{eq} = 3k\Omega + (6k\Omega \parallel 4k\Omega) = 5.4k\Omega$$

$$I' = \frac{5}{5.4} = 0.925mA$$

$$I'_{6k} = \frac{4k\Omega}{6k\Omega + 4k\Omega} \times 0.925 = 0.37mA$$

Step 2:

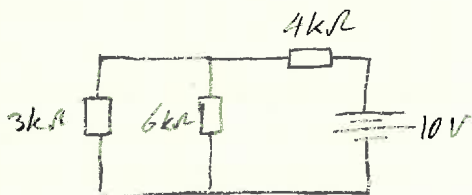





$$R_{eq} = 4k\Omega + (6k\Omega \parallel 3k\Omega) = 6k\Omega$$

$$I'' = \frac{10}{6} = 1.67mA$$

$$I''_{6k} = \frac{3k\Omega}{6k\Omega + 3k\Omega} \times 1.67 = 0.556mA$$

$$I_{6k} = I'_{6k} + I''_{6k} = 0.37 + 0.55 = 0.926mA$$



1-25.

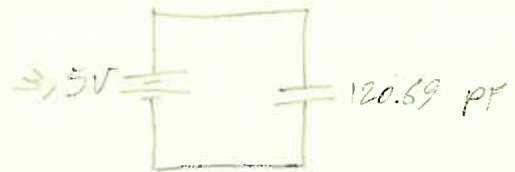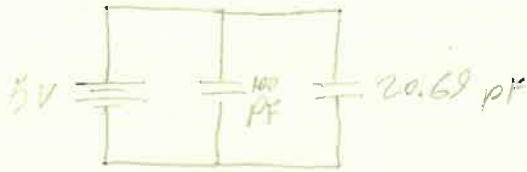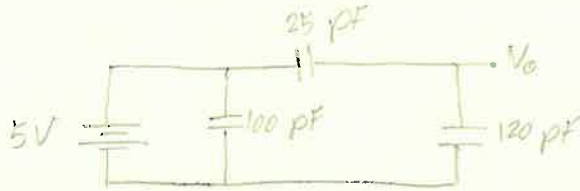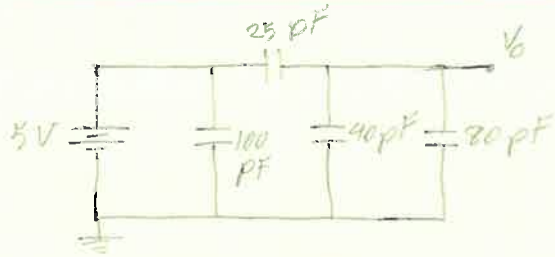

$$a) \quad W = \frac{1}{2} CV^2 = \frac{1}{2} \times 120.69 \times 10^{-12} \times 5^2 = 1.51 \text{ nJ}$$

$$b) \quad V_o = \frac{25 \text{ pF}}{(120 \text{ pF} + 25 \text{ pF})} \times 5 \text{ V} = 0.862 \text{ V}$$

1-26.

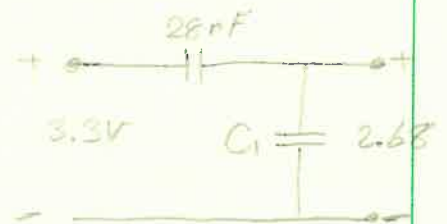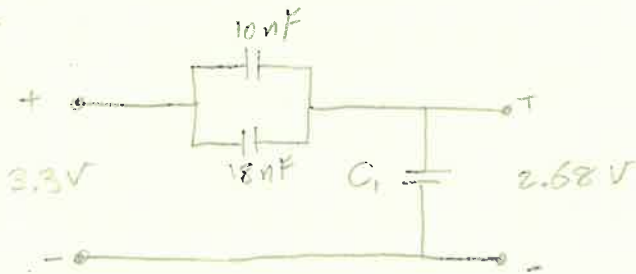

$$2.68 = \frac{28 \text{ nF}}{28 \text{ nF} + C_1} \times 3.3 \text{ V}$$

$$\frac{28 + C_1}{28} = \frac{3.3}{2.68} \Rightarrow 28 + C_1 = 28 \times 1.23$$

$$\Rightarrow C_1 = 6.48 \text{ nF}$$

$$W = \frac{1}{2} \times 6.48 \times 10^{-9} \times (2.68)^2 = 23.27 \text{ nJ}$$

1-27.

$$Q_T \text{ before switching} = Q_T \text{ after switching}$$

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V$$

$$(2+2) \times 10^{-9} \times 3 + 5 \times 10^{-9} \times 1.2 = (2+2+5) \times 10^{-9} \times V$$

$$12 + 6 = 9 \times V \quad \Rightarrow \quad V = \frac{18}{9} = 2V$$

1-28.

$$I_1 + I_3 = I_2$$

$$\frac{10 - V_0}{1 \text{ k}\Omega} + \frac{0 - (V_0 + 0.7)}{1.8 \text{ k}\Omega} = \frac{V_0 + 30}{1.5 \text{ k}\Omega}$$

$$\frac{10 - V_0}{1 \text{ k}\Omega} = \frac{V_0 + 30}{1.5 \text{ k}\Omega} + \frac{V_0 + 0.7}{1.8 \text{ k}\Omega}$$

$$10 - V_0 = \frac{1.8V_0 + 54 + 1.5V_0 + 1.05}{2.7}$$

$$27 - 2.7V_0 = 3.3V_0 + 55.05$$

$$-28.05 = 6V_0 \quad \Rightarrow \quad V_0 = -\frac{28.05}{6} = -4.675 \text{ V}$$

$$I_1 = \frac{10 + 4.675}{1 \text{ k}\Omega} = 14.675 \text{ mA}$$

$$I_2 = \frac{-4.675 + 30}{1.5 \text{ k}\Omega} = 16.88 \text{ mA}, \quad I_3 = \frac{4.675 - 0.7}{1.8 \text{ k}\Omega} = 2.21 \text{ mA}$$

$$1.29 \quad I_s = 10 \text{ nA}$$

$$a) \quad V_{EB} = 1 \text{ V}$$

KVL:

$$-1 + 50 \text{ k}\Omega \times I_D + V_D + 80 \text{ k}\Omega \times I_D = 0$$

$$V_D = 1 - 130 \times I_D$$

$$I_D = I_s \left( e^{\frac{V_D}{V_{th}}} - 1 \right)$$

$$= f(I_D)$$

$$I_D = 6.4 \text{ }\mu\text{A}$$

$$V_D = 1 - 130 \times 10^3 \times 6.4 \times 10^{-6} = 0.168 \text{ V}$$

$I_D$	$f(I_D)$
5 $\mu\text{A}$	7.01
6 $\mu\text{A}$	47.28
6.4 $\mu\text{A}$	6.4 $\mu\text{A}$

$$b) \quad V_{EB} = 10 \text{ V}$$

KVL:

$$V_D = 10 - 130 \times I_D$$

$$I_D = 10 \times 10^{-9} \times \left( e^{\frac{10 - 130 \text{ k}\Omega \times I_D}{0.026}} - 1 \right)$$

$$= f(I_D)$$

$$I_D = 75.138 \text{ }\mu\text{A}$$

$$V_D = 0.232 \text{ V}$$