

## HW#7

3.1 Circuit 1:

$$V_{GS} = \left[ \frac{2}{2+8} \right] \times 10 = 2 \text{ V}$$

$V_{DS} > V_{GS} - V_{th} \Rightarrow$  transistor in Saturation

$$I_D = k_n \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 = \frac{200}{2} \times 2 \times (2 - 0.4)^2 = 0.512 \text{ mA}$$

Circuit 2:

$$V_{GS} = \left[ \frac{2}{2+18} \right] \times 2 = 0.2 \text{ V}$$

$V_{GS} < V_{th} \Rightarrow$  transistor in cut off

$$I_D = 0$$

Circuit 3:

$$V_{GS} = \left[ \frac{8}{8+12} \right] \times 2 = 0.8 \text{ V}$$

$V_{DS} > V_{GS} - V_{th} \Rightarrow$  transistor in Saturation

$$I_D = k_n \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 = \frac{200}{2} \times 2 \times (0.8 - 0.4)^2 = 32 \text{ } \mu\text{A}$$

3.2

$$V_{DS} < V_{GS} - V_{th}$$

a)  $0.8 < 3 - 0.5 \Rightarrow$  Non-saturated (linear region)

$$I_D = k_n \left( \frac{W}{L} \right) \left[ 2(V_{GS} - V_{th})V_{DS} - V_{DS}^2 \right]$$

$$I_D = \frac{200}{2} \times 4 \left[ 2(3-0.5)10.8 - 0.8^2 \right] = 1.344 \text{ mA}$$

$$b) R_{d1} = \frac{1.5 - V_D}{I_D} = \frac{1.5 - 0.8}{1.344} = 520.83 \Omega$$

3.5.

$$I_D = \frac{V_0}{100k}$$

$$I_D = \frac{k_n'}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 = \frac{75}{2} \times 3 \times (1.5 - V_0 - 0.6)^2$$

$$\frac{V_0}{100k} = \frac{75}{2} \times 3 \times (1.5 - V_0 - 0.6)^2$$

$$V_0 = 0.658 \text{ V}$$

$$I_D = \frac{V_0}{100k} = \frac{0.658}{100k} = 6.58 \mu\text{A}$$

$$3.6. \quad V_{GS} = 6 - V_0, \quad V_{DS} = V_D - V_S = 5 - V_0$$

$$V_{GS} - V_{th} > V_{DS} \Rightarrow 6 - V_0 - 0.8 > 5 - V_0$$

5.2 > 5  
Non Saturated state

$$I_D = \frac{k_n'}{2} \left( \frac{W}{L} \right) \left[ 2(V_{GS} - V_{th})V_{DS} - V_{DS}^2 \right]$$

$$I_D = \frac{V_0}{5} = \frac{200}{2} \times 4 \times \left[ 2(6 - V_0 - 0.8)(5 - V_0) - (5 - V_0)^2 \right]$$

$$V_0 = 3.806 \text{ V}$$

3.10


Saturated State:  $I_D = \frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{tn})^2$

$$I_D = \frac{250 \times 10^{-6}}{2} \times 3 \times (2 - 0.5)^2 = 0.844 \text{ mA}$$

$$V_D = V_G - V_{tn} = 2 - 0.5 = 1.5 \text{ V}$$

$$R_L = \frac{5 - V_D}{I_D} = \frac{5 - 1.5}{0.844 \times 10^{-3}}$$

$$R_L = 4.147 \text{ k}\Omega$$

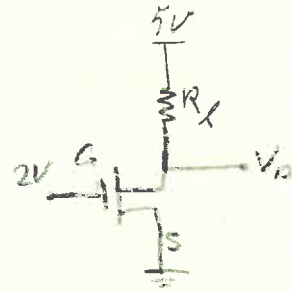

3.11

$$V_{DS} = V_G - V_{tn} = V_G - 0.5$$


$$I_D = \frac{5 - V_D}{4 \text{ k}} = \frac{5.5 - V_G}{4 \text{ k}}$$

$$\frac{5.5 - V_G}{4 \text{ k}} = \frac{250 \times 10^{-6}}{2} \times 3 \times (V_G - 0.5)^2$$


$$V_G = 2.023 \text{ V}$$

$$I_D = \frac{5.5 - 2.023}{4 \text{ k}} = 0.869 \text{ mA}$$
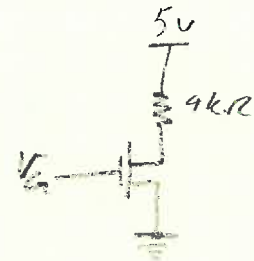
$$V_{DS} = V_{GS} - V_{tn} = 2.023 - 0.5 = 1.523 \text{ V}$$




3.15

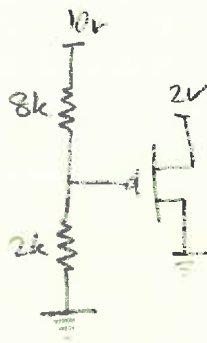

$$V_{GS} = 2 - 2 = 0 \text{ V}, \quad V_{DS} = 2 \text{ V}$$

$$V_{GS} > V_{tp} \rightarrow \text{transistor is off}$$

$$\boxed{I_D = 0}$$

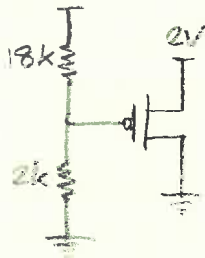

$$V_G = \left( \frac{2}{2+18} \right) \times 2 = 0.2 \text{ V}$$


$$V_{GS} = 0.2 - 2 = -1.8 \text{ V}, \quad V_{DS} = 0 - 2 = -2 \text{ V}$$

$$V_{GS} > V_{DS} + V_{tp}$$

$$-1.8 > -2 - 0.4$$

Saturation State
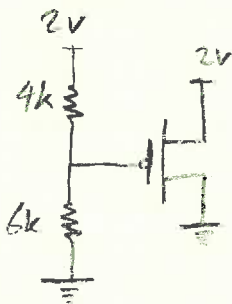
$$I_D = \frac{k_p'}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{tn})^2 = \frac{100}{2} \times 4 \times (-1.8 + 0.4)^2 = \boxed{392 \mu\text{A}}$$



$$V_G = 2 \times \left( \frac{6}{10} \right) = 1.2 \text{ V}$$

$$V_{DS} = 0 - 2 = -2 \text{ V}$$

$$V_{GS} > V_{DS} + V_{tp}$$


$$V_{GS} = 1.2 - 2 = -0.8 \text{ V}$$

$$-0.8 > -2 - 0.4$$

Saturation State

$$I_D = \frac{k_p'}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{tn})^2 = \frac{100}{2} \times 4 \times (-0.8 + 0.4)^2 = \boxed{32 \mu\text{A}}$$

3.21.

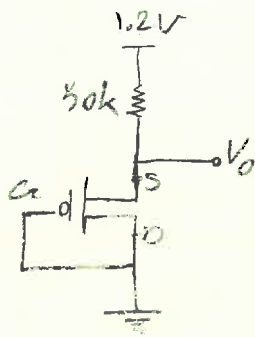

$$|V_{GS}| = V_O, \quad |V_{DS}| = V_O$$

$$|V_{DS}| > |V_{GS}| - |V_{tp}| \Rightarrow \text{Saturation}$$

$$I_D = \frac{k_p}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{tp})^2$$

$$I_D = \frac{40 \times 10^{-6}}{2} \times 6 \times (V_O - 0.3)^2 = \frac{1.2 - V_O}{50 \text{ k}\Omega}$$

$$V_O = 0.6128 \text{ V}$$

$$I_D = 11.756 \text{ }\mu\text{A}$$

3.24.

$$a) \quad V_{GS} = V_G - V_S = 0 - 1.8 \text{ V} = -1.8 \text{ V} \quad \text{at } t = 0^+$$

$$|I_D| = \frac{k_p}{2} \left(\frac{W}{L}\right) (|V_{GS}| - |V_{tp}|)^2 = \frac{40 \times 10^{-6}}{2} \times 5 \times (1.8 - 0.4)^2$$

$$I_D = 196 \text{ }\mu\text{A}$$

b) No current goes through the capacitor

Non Saturation

$$c) \quad W = \frac{1}{2} CV^2 = \frac{1}{2} (15 \times 10^{-9}) (1.8)^2 = 24.3 \text{ nJ}$$