

# HW #8

3.25


$$V_{tp} = -0.4$$

$$K_p = 50 \text{ } \mu\text{A/V}^2$$

$$\frac{W}{L} = 8$$

$$P_R = 10 \text{ } \mu\text{W}$$
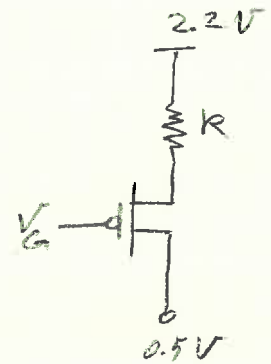
$$P_R = \frac{\Delta V^2}{R} = \frac{(2.2 - V_S)^2}{R} = 10 \text{ } \mu\text{W}$$



$$\Rightarrow R = \frac{(2.2 - V_S)^2}{10 \text{ } \mu\text{W}} \quad (1)$$

Transistor is biased at the boundary.

$$V_{DS} = V_{GS} - V_{tp} \Rightarrow V_D - V_S = V_G - V_S - V_{tp}$$

$$V_G = V_{tp} + V_D = 0.5 - 0.4 = 0.1$$

$$\begin{aligned} |I_D| &= \frac{K_p}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{tp})^2 = \frac{K_p}{2} \left(\frac{W}{L}\right) (V_G - V_S - V_{tp})^2 \\ &= \frac{50}{2} (8) (0.1 - V_S - (-0.4))^2 = \frac{50}{2} \times 8 \times (0.5 - V_S)^2 \quad (2) \end{aligned}$$

$$\text{Also } |I_D| = \frac{2.2 - V_S}{R} \quad \text{combine (1)} \Rightarrow \frac{2.2 - V_S}{\frac{(2.2 - V_S)^2}{10 \text{ } \mu\text{W}}} = \frac{10 \text{ } \mu\text{W}}{2.2 - V_S} \quad (3)$$

$$(2) = (3)$$

$$\frac{50}{2} \times 8 \times (0.5 - V_S)^2 = \frac{10 \text{ } \mu\text{W}}{2.2 - V_S}$$

$$V_S = 0.6815$$

$$V_S > V_D \therefore V_S \neq 0.336 \text{ V}$$

$$\text{from (1)} \Rightarrow R = \frac{(2.2 - 0.6815)^2}{10 \text{ } \mu\text{W}} = \underline{\underline{230.6 \text{ k}\Omega}}$$

3.26

$$(a) \quad V_{GS} = V_G - V_S = 0 - V_S$$

Assume Saturation

$$|I_{DS}| = \frac{75}{2} (5) (-V_S + 0.6)^2 = \frac{3 - V_S}{4 \text{ k}\Omega} = I_{DS}$$

$$\frac{3 - V_S}{4 \text{ k}\Omega} = \frac{75}{2} \times 5 \times (V_S^2 - 1.2V_S + 0.36)$$

$$\boxed{V_S = 1.842 \text{ V}} \quad \text{For PMOS } V_S > V_G$$

$$b) \quad I_{DS} = \frac{3 - V_S}{4 \text{ k}\Omega} = \frac{3 - 1.842}{4 \text{ k}\Omega} = 289.5 \times 10^{-4}$$

$$I_{DS} = \frac{V_D}{2 \text{ k}\Omega} \Rightarrow V_D = (2 \text{ k}\Omega) \times (289.5 \times 10^{-4}) = 0.579 \text{ V}$$

$$|V_{DS}| > |V_{GS}| - |V_{TP}|$$

$$1.263 > 1.242, \text{ so Saturation is true}$$

$$\text{Thus, } \boxed{V_D = 0.579 \text{ V}}$$

3.30)

$$V_{GS} = V_G - V_S = 0 - (-1) = 1 \text{ V}$$

$$\text{Since } V_{DS} > V_{GS} - V_{TN} \text{ i.e. } (2 > 1 - 0.6)$$

NMOS is in Saturation

$$I_{D_S} = \frac{k_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{Th})^2 = \frac{200 \mu A/V^2}{2} \times 3 \times (1 - 0.6)^2$$

$$I_{D_S} = 48 \mu A$$

$$R_1 = \frac{3 - V_D}{I_{D_S}} = \frac{3 - 1}{48 \mu A} = \underline{41.67 \text{ k}\Omega}$$

$$R_1 = R_2 = \underline{41.67 \text{ k}\Omega}$$

3.35.

$$V_G = V_D = V_0 \Rightarrow V_{D_S} = V_{G_S}$$

Transistor is saturated because drain and gate are connected

$$I_{D_S} = \frac{k_n}{2} \left(\frac{W}{L}\right) (V_{G_S} - V_{Th})^2 = \frac{90}{2} (10) (V_{D_S} - 0.5)^2$$

$$I_{D_S} = \frac{2.5 - V_D}{5 \text{ k}\Omega} = \frac{V_G}{2 \text{ k}\Omega} \Rightarrow V_D - V_G = V_{D_S} = 2.5 \text{ V} - (5 \text{ k}\Omega) I_{D_S} - (2 \text{ k}\Omega) I_{D_S}$$

$$I_{D_S} = \frac{90}{2} (10) (2.5 - 5 I_{D_S} - 2 I_{D_S} - 0.5)^2$$

$$I_D = 192.32 \mu A \quad \text{or} \quad I_D = 424.46 \mu A$$

$$\text{Saturation} \Rightarrow \underline{I_D = 192.32 \mu A}$$

For  $V_0$ ,  $I_D = \frac{2.5V - V_0}{5k\Omega} \Rightarrow V_0 = 2.5V - (5k\Omega) \times I_D$

$$V_0 = 2.5 - (5k\Omega)(192.32 \mu A) = \boxed{1.54V}$$

3.37.

$$V_T = V_{T0} + \gamma (\sqrt{|2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|})$$

$$\sqrt{|2\phi_F - V_{SB}|} = \sqrt{|2\phi_F|} + \frac{V_T - V_{T0}}{\gamma}$$

$$\Rightarrow V_{SB} = (\sqrt{|2\phi_F|} + \frac{V_T - V_{T0}}{\gamma})^2 - |2\phi_F| = 86.17 \text{ mV}$$

$$V_{BS} = -V_{SB} = -86.17 \text{ mV}$$

3.38.

$$V_T = V_{T0} + \gamma (\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$

$$V_T = 0.6V + 0.25 (\sqrt{0.7 + V_0} - \sqrt{0.7})$$

$$\text{maximum } V_0 = V_{dd} - V_T \rightarrow V_T = 2 - V_0$$

$$\Rightarrow \boxed{V_0 = 1.26V}$$

$$V_T = 0.74V$$