

Homework 9

5.2

a)  $NM_H = V_{OH} - V_{IH} = 1.7V - 1.6V = 0.1V$

b)  $NM_L = V_{IL} - V_{OL} = 0.3V - 0.2V = 0.1V$

c) Circuit fidelity is not compromised because  $1.7V - 0.05V > 1.6V$

d) Circuit fidelity is compromised because  $1.7V - 0.15V < 1.6V$

---

5.4

$NM_L = 0.9V \times 0.2 = 0.18V$

$NM_H = 0.18V$

$V_{IH} = V_{OH} - NM_H = 0.8 - 0.18 = 0.62V$

$V_{IH} = NM_L + V_{OL} = 0.18 + 0.1 = 0.28V$


---

5.5

$V_{M1} = 0.86V$

$V_{M2} = 1.02V$

$V_{M2} - V_{M1} = 1.02 - 0.86 = 0.16V$

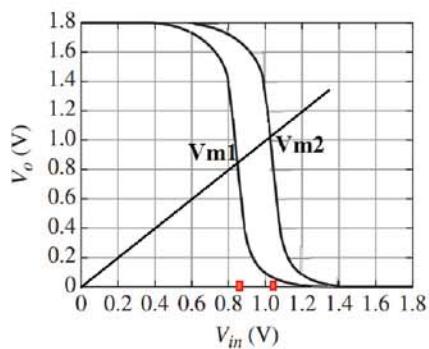


5.6

a)  $\frac{W_P}{W_n} = \frac{M_n}{M_P} \frac{\left(\frac{V_{DD}}{2} - V_{th,n}\right)^2}{\left(\frac{V_{DD}}{2} - |V_{th,p}|\right)^2} = \frac{\left(1400 \frac{cm^2}{V.s}\right) (0.65V - 0.35V)^2}{\left(500 \frac{cm^2}{V.s}\right) (0.65V - 1.0V)^2} = 2.8$

b)  $\frac{W_P}{W_n} = \frac{\left(1400 \frac{cm^2}{V.s}\right) (0.65V - 0.35V)^2}{\left(500 \frac{cm^2}{V.s}\right) (0.65V - 0.45V)^2} = 6.3$

5.8

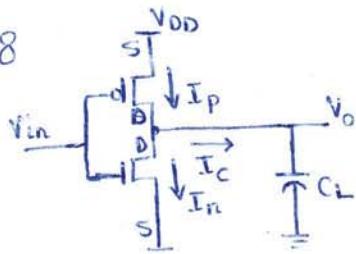

$$K_n * (V_{G_Sn} - V_{t_n})^2 = K_p * (V_{G_Sp} - V_{t_p})^2$$

$$K_p = 3 K_n$$

$$V_{G_Sn} = V_i$$

$$V_{G_Sp} = V_i - V_{DD}$$

$$V_i = V_o + V_{t_n}$$

$$\left. \begin{array}{l} (V_i - V_{t_n})^2 = 3(V_i - V_{DD} - V_{t_p})^2 \\ (V_o + V_{t_n} - V_{t_n})^2 = 3(V_o + V_{t_n} - V_{DD} - V_{t_p})^2 \end{array} \right\} ;$$

$$V_o = 0.665V$$

$$\frac{V_{DD} - V_o}{V_{DD}} = \frac{2.5V - 0.665V}{2.5V} = 0.734 = 73.4\%$$

5.9

$$I_{DD} = 5\mu A$$

$$\text{For PMOS: } 5\mu A = \frac{25\mu A V^2}{2} (4)(V_i - 21 - 1 - 0.61)^2 \Rightarrow V_i = 1.084V$$

$$\text{NMOS: } 5\mu A = 50\mu A V^2 (2) \left[ (1.084 - 0.5) V_{out} - \frac{V_{out}^2}{2} \right] \Rightarrow V_{out} = 0.4255$$