

HOMEWORK-9

52

$$a) NM_H = V_{OH} - V_{IH} = 1.7 - 1.6 = 0.1V$$

$$b) NM_L = V_{IL} - V_{OL} = 0.3 - 0.2 = 0.1V$$

c) circuit fidelity is not compromised because $1.7 - 0.05 > 1.6V$

d) circuit fidelity is compromised because $1.7 - 0.15V < 1.6V$

54)

$$NM_L = 0.9 \times 0.2 = 0.18V$$

$$NM_H = 0.18V$$

$$V_H = V_{OH} - NM_H = 0.8 - 0.18 = 0.62V$$

$$V_{DE} = NM_L + V_{OL} = 0.18 + 0.1 = 0.28V$$

55) From the graph we have

$$V_{M1} = 0.86V$$

$$V_{M2} = 1.02V$$

$$V_{M2} - V_{M1} = 1.02 - 0.86 = 0.16V$$

$$5.6) a) \frac{W_p}{W_n} = \frac{\mu_n \left(\frac{V_{DD}}{2} - V_{tn} \right)^2}{\mu_p \left(\frac{V_{DD}}{2} - V_{tp} \right)^2} = \frac{1400 (0.65 - 0.35)^2}{500 (0.65 - 0.35)^2} = 2.8$$

$$b) \frac{W_p}{W_n} = \frac{1400 (0.65 - 0.35)^2}{500 (0.65 - 0.45)^2} = 6.3$$

5.8) Given $K_n \left(\frac{W}{L}\right)_n = 100 \mu\text{A}/\text{V}^2$

Page-2

$K_p \left(\frac{W}{L}\right)_p = 300 \mu\text{A}/\text{V}^2 \Rightarrow K_p = 3K_n$

$V_{tn} = 0.7\text{V}, V_{tp} = -0.75, V_{DD} = 2.5\text{V}$

Equating the drain currents we have

$I_n = I_p$

$K_n \left(\frac{W}{L}\right)_n (V_{gsn} - V_{tn})^2 = K_p \left(\frac{W}{L}\right)_p (V_{gsp} - V_{tp})^2$


$K_n (V_{gsn} - V_{tn})^2 = 3K_n (V_{gsp} - V_{tp})^2 \quad \text{--- (1)}$

$V_{gsn} = V_i \quad V_{gsp} = V_i - V_{DD} \quad V_i = V_o + V_{tn}$

substituting the above values in (1)

we have $V_o = 0.665$

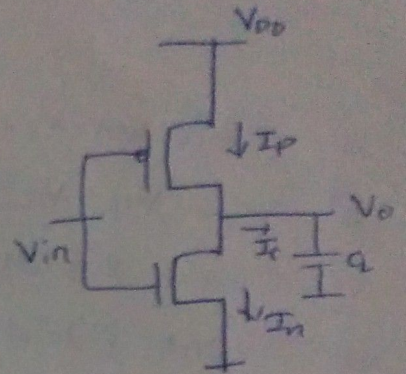$\frac{V_{DD} - V_o}{V_{DD}} = \frac{2.5 - 0.665}{2.5} = 73.4\%$



5.9) ~~Given~~ $K_n = 50 \quad K_p = 25 \quad V_{tn} = 0.5 \quad V_{tp} = -0.6$

$(W/L)_n = 2, (W/L)_p = 4. \quad I_{DD} = 11 \mu\text{A}, V_{DD} = 2\text{V}$

For PMOS

$11 \mu\text{A} = \frac{25 \mu\text{A}}{2} (4) (V_i - 2 + 0.6)^2$

Solving $V_i = 0.94$

For NMOS

$11 \mu\text{A} = \frac{50 \mu\text{A}}{2} (2) \left[(0.94 - 0.5) V_{out} - \frac{V_{out}^2}{2} \right]$

$-V_{out}^2 + 0.88 V_{out} - 0.44 = 0$

$V_{out} = -0.35 \text{ or } 1.235$