

# ECE321 – Electronics I

## Lecture 11: CMOS Inverter: VTC & ITC

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Tuesday 2:00-3:00PM or by appointment*

*E-mail: [pzarkesh.unm.edu](mailto:pzarkesh.unm.edu)*

# *Review of Last Lecture*

---

- ❑ **BASIC CMOS Inverter**
  - Resistive load inverter
- ❑ **Introduction to SPICE**

# *Today's Lecture*



---

---

- ❑ **CMOS Inverter**
- ❑ **Voltage Transfer Characteristics (VTC)**
  - **Switching threshold voltage**
  - **Output high voltage**
  - **Output low voltage**
  - **Input high voltage**
  - **Input low voltage**
- ❑ **Current Transfer Characteristics (ITC)**
  - **Peak current**

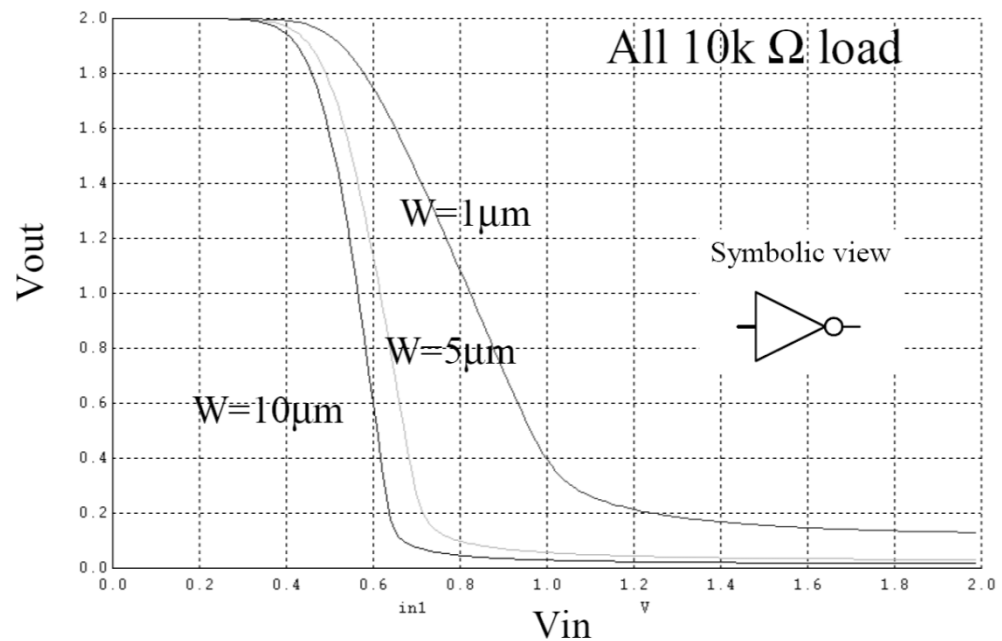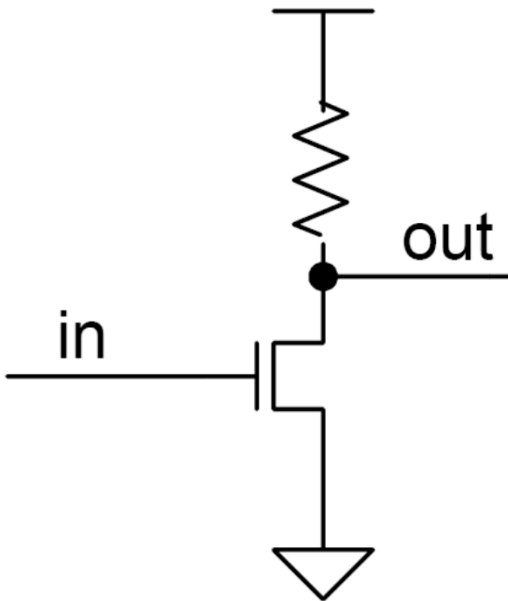
# Review: Resistive Load Inverter

- A resistive load inverter consists of a pull down NMOS and a pull up resistor
  - When the output is high, there is no current drawn from VDD
  - When the output is high, a DC current is drawn from VDD



 
# Pseudo NMOS Inverter

- ❑ Since a resistor is so big, it's better to use a single PMOS transistor that is always on:
  - PMOS pull up
  - NMOS pull down
- ❑ Why don't we use NMOS pull up?



 
# CMOS Inverter

- ❑ CMOS inverter is comprised of
  - PMOS pull up
  - NMOS pull down
- ❑ Advantages
  - No direct path from  $V_{DD}$  to GND (zero static power - except for leakage)
  - Better noise margin (Rail-to-rail output swing)
  - Ratio-less logic (output level not depend on gate size)
  - Always finite resistance to  $V_{DD}$  or GND
  - Very high input impedance



 
# Switching model of CMOS Inverter


- ❑ Treat each transistor as either on or off
- ❑ Each transistor has an on resistance
  - This isn't a bad model as long as the input transition is quite a bit faster than the output transition and it's very intuitive
- ❑ Delay of the gate depends of the effective transistor resistant and load capacitance


 
# Ideal Voltage Transfer Characteristic VTC




(a)

 


(b)




# CMOS Inverter VTC

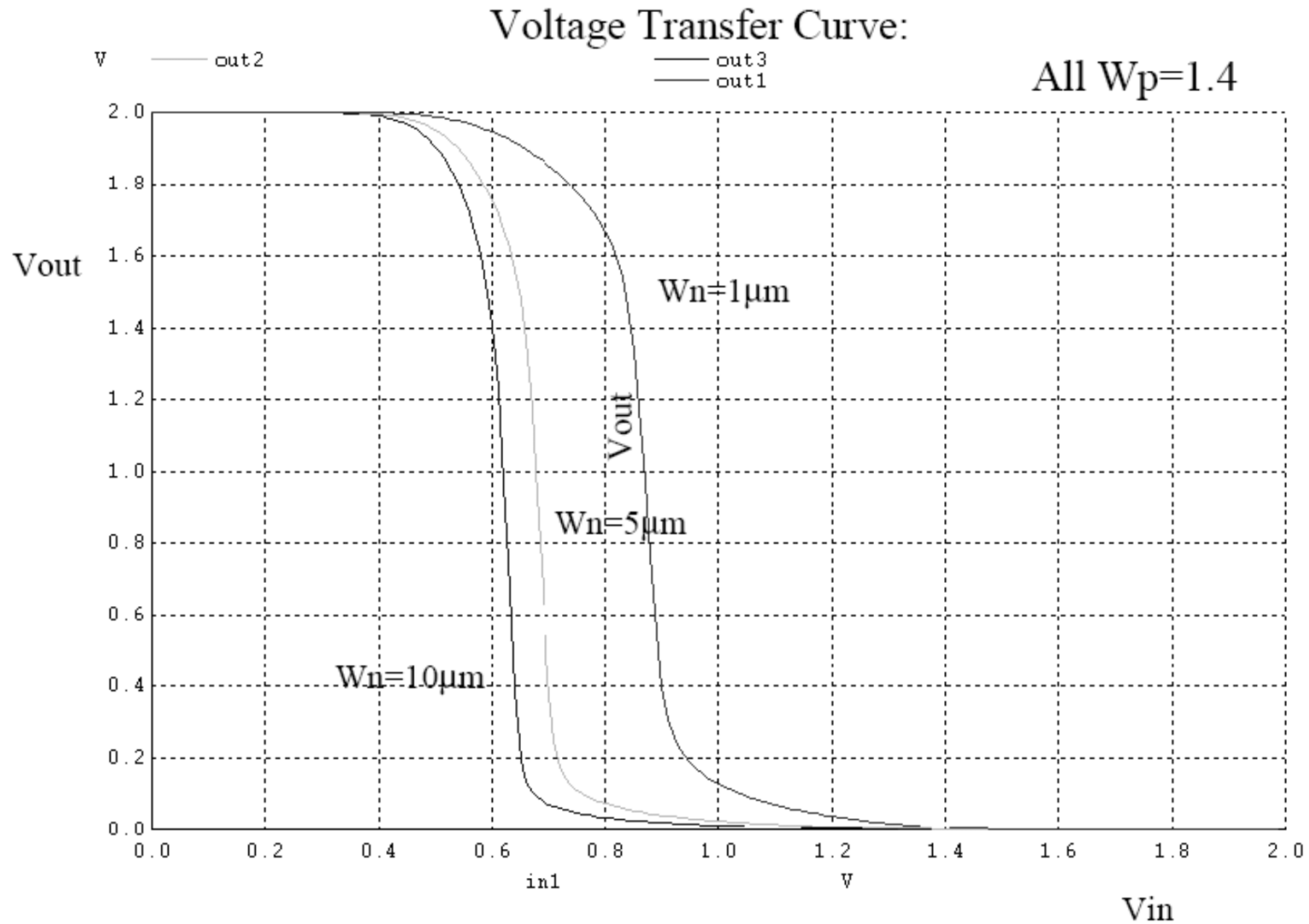


# Closer Look at CMOS Inverter VTC

 

 - Region I – NMOS off, PMOS ohmic
- Region II – NMOS saturated, PMOS ohmic
- Region III – NMOS saturated, PMOS saturated
- Region IV – NMOS ohmic, PMOS saturated
- Region V – NMOS ohmic, PMOS off




# VTC Characterization

 
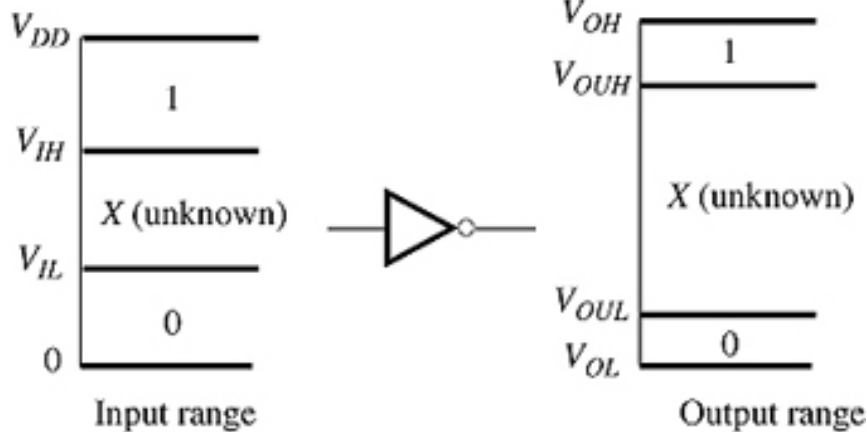
## Important Parameters on VTC:

- ❑ Switching Threshold Voltage  $V_S$  or  $V_M$
- ❑ Gain at  $V_S$  or  $V_M$
- ❑ Output High Voltage  $V_{OH}$
- ❑ Output Low Voltage  $V_{OL}$
- ❑ Input High Voltage  $V_{IH}$
- ❑ Input Low Voltage  $V_{IL}$



# CMOS Inverter Switching Threshold

- How to compute  $V_M$  in CMOS logic gate?
  - Use current equation in saturation to compute  $V_M$
  - Assume long channel model, we will get:

$$V_M = \frac{\sqrt{\frac{K'_p(W/L)_p}{K'_n(W/L)_n} (V_{DD} - |V_{Tp}|) + V_{Tn}}}{1 + \sqrt{\frac{K'_p(W/L)_p}{K'_n(W/L)_n}}}$$

- To set  $V_M = V_{DD}/2$  for a symmetric CMOS inverter, we need to have:

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} \left[ \frac{V_{DD} - 2V_{Tn}}{V_{DD} - 2|V_{Tp}|} \right]^2$$

# Example: Switching Threshold Voltage

---

---

Compute the ratio of  $n$ MOS and  $p$ MOS transistor width to obtain a symmetric inverter for a 0.18  $\mu\text{m}$  technology in which  $\mu_n = 360 \text{ cm}^2/\text{V}\cdot\text{s}$ ,  $\mu_p = 109 \text{ cm}^2/\text{V}\cdot\text{s}$ ,  $V_m = 0.35 \text{ V}$ ,  $V_{tp} = -0.4 \text{ V}$ , and  $V_{DD} = 1.8 \text{ V}$ .

*Solution:*

$$\frac{W_p}{W_n} = \frac{360 \text{ cm}^2/\text{V}}{109 \text{ cm}^2/\text{V}} \left[ \frac{1 - \frac{2(0.35)}{1.8}}{1 - \frac{2|-0.4|}{1.8}} \right]^2 = 4.0$$

# ***CMOS Inverter $V_{OH}$ and $V_{OL}$***

---

---


- **How to compute gain at  $V_{OH}$  and  $V_{OL}$  in CMOS logic gate?**
  - In an ideal CMOS inverter  $V_{OH}$  is  $V_{DD}$  and  $V_{OL}$  is zero.
  - In a resistive NMOS inverter or any non-CMOS inverter  $V_{OH}$  and  $V_{OL}$  needs to be computed.
  - $V_{OH}$  is the output of inverter when the input is zero.
  - $V_{OL}$  is the output of the inverter when the input is  $V_{DD}$ .

# ***CMOS Inverter $V_{IH}$ and $V_{IL}$***

---

- **How to compute gain at  $V_{IH}$  and  $V_{IL}$  in CMOS logic gate?**
  - $V_{IL}$  is the input voltage when the slope of VTC becomes -1 at the lower input voltage.
  - $V_{IH}$  is the input voltage when the slope of VTC becomes -1 at the higher input voltage.
  - Usually it is not easy to find  $V_{IH}$  is  $V_{IL}$  in CMOS inverter.
  - However, there is an approximation technique to find  $V_{IH}$  is  $V_{IL}$  that we will discuss in the next lecture.

# Current Transfer Characteristics

 



# CMOS Inverter Peak Current

---

---

- How to compute peak current in CMOS logic gate?
  - Use current equation in saturation and use  $V_M$
  - Assume long channel model, we will get:

$$I_{DD} = \frac{K'_n}{2} \left( \frac{W}{L} \right)_n (V_M - V_{Tn})^2 = \frac{K'_p}{2} \left( \frac{W}{L} \right)_p (V_{DD} - V_M - |V_{Tp}|)^2$$