

ECE321 – Electronics I

Lecture 12: CMOS Inverter: Noise Margin & Delay Model

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh.unm.edu


Review of Last Lecture

- ❑ **CMOS Inverter**
- ❑ **Voltage Transfer Characteristics (VTC)**
 - **Switching threshold voltage**
 - **Output high voltage**
 - **Output low voltage**
 - **Input high voltage**
 - **Input low voltage**
- ❑ **Current Transfer Characteristics (ITC)**
 - **Peak current**

Today's Lecture


- Noise Margin Definition**
- Approximation of Noise Margin for CMOS Inverter**
- Propagation Delay**
- Rise and Fall Times**
- Input and Self Loading (Load) Capacitances**
- Delay Approximation**

Review: Voltage Transfer Characteristics

 


Important Parameters on VTC:

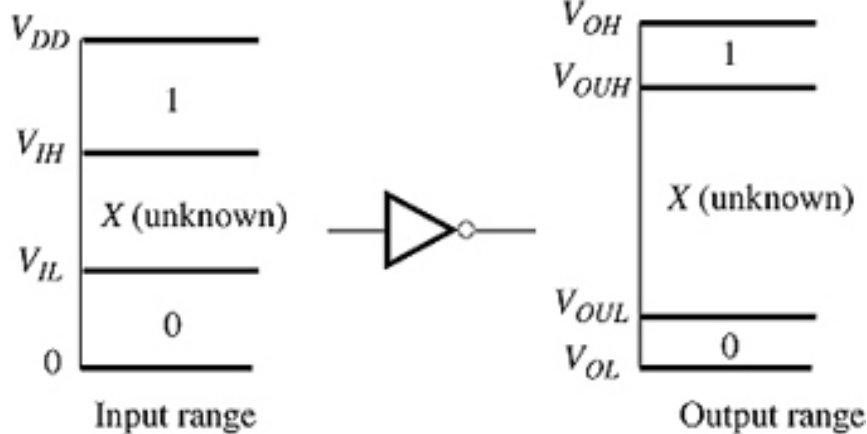
- ❑ Switching Threshold Voltage V_S or V_M
- ❑ Gain at V_S or V_M
- ❑ Output High Voltage V_{OH}
- ❑ Output Low Voltage V_{OL}
- ❑ Input High Voltage V_{IH}
- ❑ Input Low Voltage V_{IL}



Effect of Noise on a CMOS Inverter

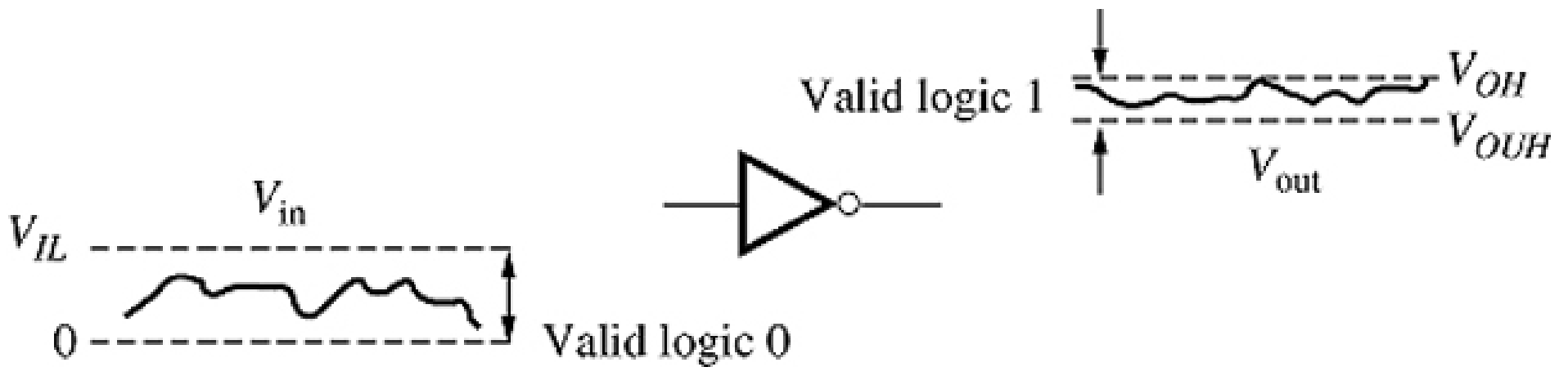


Noise Margin

 

□ Noise Margin

$$NM_H = V_{OH} - V_{IH}$$


$$NM_L = V_{IL} - V_{OL}$$

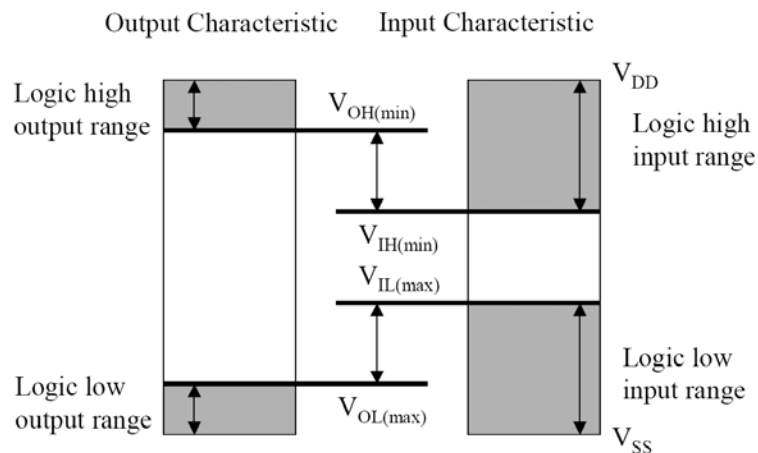


□ It is better to have:

- $V_{OH} = V_{DD}$
- $V_{OL} = V_{SS}$
- Large NM_H
- Large NM_L

Noise Margin in Inverter and Buffer

 

VTC of an inverter

 

VTC of a buffer

Example: Noise Margin Calculation

An IC with $V_{DD} = 1.5$ V shows $V_{OH} = 1.35$ V, $V_{OL} = 0.2$ V, $V_{IH} = 1.2$ V, and $V_{IL} = 0.3$ V. Calculate the NM_L and NM_H for this IC.

Sketch the NM rectangles

$$NM_H = 1.35 - 1.2 = 150 \text{ mV}$$

$$NM_L = 0.3 - 0.2 = 100 \text{ mV}$$



Noise Margin Approximation

□ How to compute Noise Margin

- Usually it is harder to compute the exact value of NM
- Use approximation (gain factor)
- Determine gain at V_M
- Extrapolate V_{IL} and V_{IH}
- V_{OL} and V_{OH} are easy to compute

□ Example:

- NM_L and NM_H in CMOS inverter


$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$

- where

$$g = \frac{-2}{\lambda_n + |\lambda_p|} \left(\frac{1}{V_M - V_{Tn}} + \frac{1}{V_{DD} - V_M - |V_{Tp}|} \right)$$

 

Example: Noise Margin Approximation

- A CMOS inverter has $V_{DD}=5V$ is designed to have $V_M=2.9V$. If $V_{Tn}=0.7$, $V_{Tp}=-0.5$, $\lambda_n=0.05 V^{-1}$ and $\lambda_p=-0.08 V^{-1}$. Find the noise margins NMH and NML.


$$g = \frac{-2}{0.05 + 0.08} \left(\frac{1}{2.9 - 0.7} + \frac{1}{5 - 2.9 - 0.5} \right) = -16.6$$

$$V_{IL} = 2.9 + \frac{5 - 2.9}{-16.6} = 2.77 V$$

$$V_{IH} = 2.9 - \frac{2.9}{-16.6} = 3.1 V$$



$$NMH = 5 - 3.1 = 1.9 V$$

$$NML = 2.77 - 0 = 2.77 V$$

 

Dynamic Behavior of CMOS Inverter

  - ❑ Changing of the input doesn't instantaneously change the output of an inverter
- ❑ This is mostly due to the time it takes to charge or discharge the output/load capacitor
- ❑ It is important to know how long it takes to get the signal out of the inverter or any CMOS logic gate




Definition: Propagation Delay

□ Definition of propagation delay


- is delay from where input crosses 50%Vdd to where output crosses 50%Vdd
- Remember: the value of 50%Vdd is from switching threshold voltage (V_M)
- t_{pHL} is propagation delay when output switches from “High to Low”
- t_{pLH} is propagation delay when output switches from “Low to High”

 □ To compute delay, the inverter must be simplified



Definition: 10%-90% Rise/Fall Times

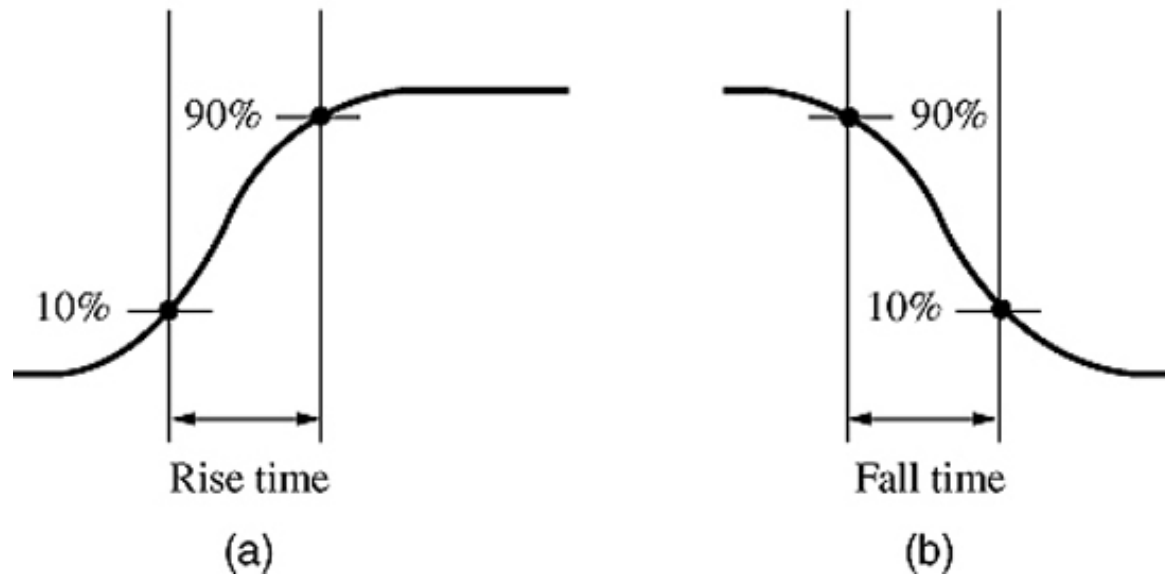- Definition of 10%-90% rise time
 - is delay from 10%Vdd to 90%Vdd in the output
 - t_r is the rise time when output switches from “Low to High”
- Definition of 90%-10% fall time
 - is delay from 90%Vdd to 10%Vdd in the output
 - t_f is the fall time when output switches from “High to Low”






Definition: Linear Rise/Fall Times

□ Definition of rise time (Hawkin's book)

- is delay from 0 to V_{DD} in the output assuming a constant current source model
- t_r is the rise time when output switches from “Low to High”

□ Definition of fall time (Hawkin's book)

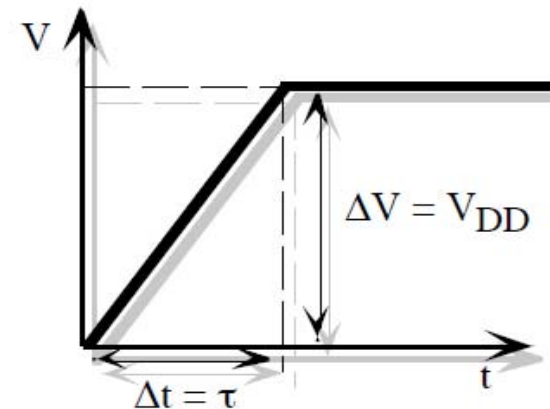  
- is delay from V_{DD} to 0 in the output assuming a constant current source model
- t_f is the fall time when output switches from “High to Low”



Delay Calculation in CMOS Inveretr

- ❑ **It is not easy to accurately calculate delay in CMOS inverter, because**
 - **CMOS inverter is a non-linear circuit, therefore exact delay calculation requires solving a non-linear differential equation**
 - **Most of the elements in the circuit is voltage dependent (transistor drive current, parasitic capacitances, channel length modulation, etc.)**
- ❑ **A simplified model is required for basic calculations and design process**
- ❑ **Note that SPICE actually does solve the non-linear circuit accurately, but is only good for final verification, not the design**


Gate Input/Output Capacitance Components

 

$$C_{in} = (C_{GDp} + C_{GSp} + C_{GBp}) + (C_{GDn} + C_{GSp} + C_{GBn})$$

$$C_{out} = (2C_{GDp} + C_{DBp}) + (2C_{GDn} + C_{DBn})$$


Propagation Delay Model

 

$$Q = I \cdot \Delta t = C \cdot \Delta V$$

$$\Delta t = \frac{C \cdot \Delta V}{I}$$

 - ❑ Propagation delay is defined as the time between the input reaching $V_{DD}/2$ and the output reaching $V_{DD}/2$
- ❑ To simplify the model, let's assume I is a constant I_{av}




$$t_{pLH} = t_2 - t_1 = \frac{C_L \cdot (V_{DD}/2)}{I_{av}}$$

Propagation Delay Model

□ How to compute I_{av} ?

- Assume step input
- NMOS goes into cutoff and stays there
- PMOS goes into saturation at first because $|V_{DS}| > |V_{GS}| - |V_T|$
- PMOS will transition to linear, however, before V_{out} reaches $V_{DD}/2$

 

$$I_{av} = \frac{I_{DS}(V_{out} = 0) + I_{DS}(V_{out} = V_{DD}/2)}{2}$$

$$I_{av} = \left(\frac{K'_p}{2} \right) \left(\frac{W_p}{L_p} \right) \left(\frac{(V_{DD} - |V_{tp}|)^2}{2} + \frac{V_{DD}(V_{DD} - |V_{tp}|)}{2} - \frac{V_{DD}^2}{8} \right)$$

Propagation Delay Model

- A simpler model for I_{av} can be obtained by assuming that the PMOS stays in saturation the whole time, therefore acts as an ideal current source

$$I_{av} = \left(\frac{K'_p}{2} \right) \left(\frac{W_p}{L_p} \right) (V_{DD} - |V_{tp}|)^2$$

$$t_{pLH} = t_2 - t_1 = \frac{C_L \cdot (V_{DD}/2)}{I_{av}} \Rightarrow t_{pLH} = \frac{C_L \cdot V_{DD}}{K'_p \left(\frac{W_p}{L_p} \right) (V_{DD} - |V_{Tp}|)^2}$$

- Assuming $V_{DD} \gg V_{Tp}$

$$t_{pLH} = \frac{C_L}{K'_p \left(\frac{W_p}{L_p} \right) V_{DD}}$$

- Same arguments hold for t_{pHL}

Minimum Delay Design Techniques

- ❑ Reduce C_{in} and C_{out} – Careful layout, keep drain diffusion area as small as possible
- ❑ Reduce wiring capacitance – Careful layout, keep devices as close as possible
- ❑ Increase (W/L) of devices – Need to be careful not to get into self-loading effect
- ❑ Increase V_{DD} – Need to be careful not to get into V_{DSAT} or velocity saturation

Example: CMOS Inverter Delay

- A CMOS inverter has $V_{DD}=5V$ is designed such that $(W/L)_n=10$ and $(W/L)_p=20$. Assume that $V_{Tn}=0.7$, $V_{Tp}=-0.6$, $K'_n=100 \mu A/V^2$, $K'_p=-60 \mu A/V^2$, and the load capacitance is 100fF.

1) Use I_{av} model to find t_{pHL} , t_{pLH} , $t_{r(10\%-90\%)}$, and $t_{f(90\%-10\%)}$.

2) Use constant current source model to find t_{pHL} , t_{pLH} , $t_{r(10\%-90\%)}$, $t_{f(90\%-10\%)}$, t_r , and t_f .

- *Answers:*

1) $t_{pHL}=29.64 \text{ ps}$, $t_{pLH}=23.73 \text{ ps}$, $t_{r(10\%-90\%)=56.71 \text{ ps}$, and $t_{f(90\%-10\%)=70.98 \text{ ps}$

2) $t_{pHL}=27.04 \text{ ps}$, $t_{pLH}=21.52 \text{ ps}$, $t_{r(10\%-90\%)=34.43 \text{ ps}$, and $t_{f(90\%-10\%)=43.27 \text{ ps}$, $t_r=43.04 \text{ ps}$ and $t_f=54.98 \text{ ps}$.