

ECE321 – Electronics I

Lecture 13: CMOS Inverter: Dynamic Power

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh.unm.edu


Review of Last Lecture

- Propagation Delay
- Rise and Fall Times
- Input and Self Loading (Load) Capacitances
- Delay Approximation

Today's Lecture

- ❑ **Mostly Review of Lecture 2 for Dynamic Power Calculation**

CMOS Dynamic Power Consumption

 

Energy / transition = $C_L \cdot V_{DD}^2$
 Power = Energy / transition * $f = C_L \cdot V_{DD}^2 \cdot f$

$$P_d = \frac{1}{T} \int_0^T i_{VDD}(t) \cdot V_{DD} dt = \frac{V_{DD}}{T} \int_0^T C_L \frac{dV_{out}}{dt} dt = \frac{C_L V_{DD}}{T} \int_0^{V_{DD}} dV_{out} = \frac{C_L V_{DD}^2}{T} = C_L V_{DD}^2 f$$

□ Need to reduce C_L , V_{DD} , or f to reduce power

Computing Active Power


- For clock circuit that toggles twice in each period (low-to-high and high-to-low), the active power consumption is computed as:

$$P_{active} = C_L V_{DD}^2 f$$

- For non-clock circuits that toggles occasionally (with probability of α) once in each period, the active power consumption is computed as:

$$P_{active} = \frac{1}{2} \alpha C_L V_{DD}^2 f = \frac{1}{2} (\alpha_{0 \rightarrow 1} + \alpha_{1 \rightarrow 0}) C_L V_{DD}^2 f$$

Example: Active Power in a Clock Driver

 

In this circuit, compute the power consumption in the inverter.

Answer: 2.17 W

Minimum Power Design Techniques

- Prime choice: Reduce voltage!**
 - Recent years have seen an acceleration in supply voltage reduction
 - Design at very low voltages still open question (0.6 ... 0.9 V by 2015!)
- Reduce switching activity**
- Reduce physical capacitance**
- Reduce clock frequency, but use multi-core architecture to enhance performance**