

ECE321 – Electronics I

Lecture 14: CMOS Inverter: Short Circuit Power

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh.unm.edu


Review of Last Lecture

- ❑ **Mostly Review of Lecture 2 for Dynamic Power Calculation**

Today's Lecture


- ❑ **Short Circuit Power Analysis**
- ❑ **Short Circuit Power Reduction Techniques**

CMOS Short Circuit Power Consumption

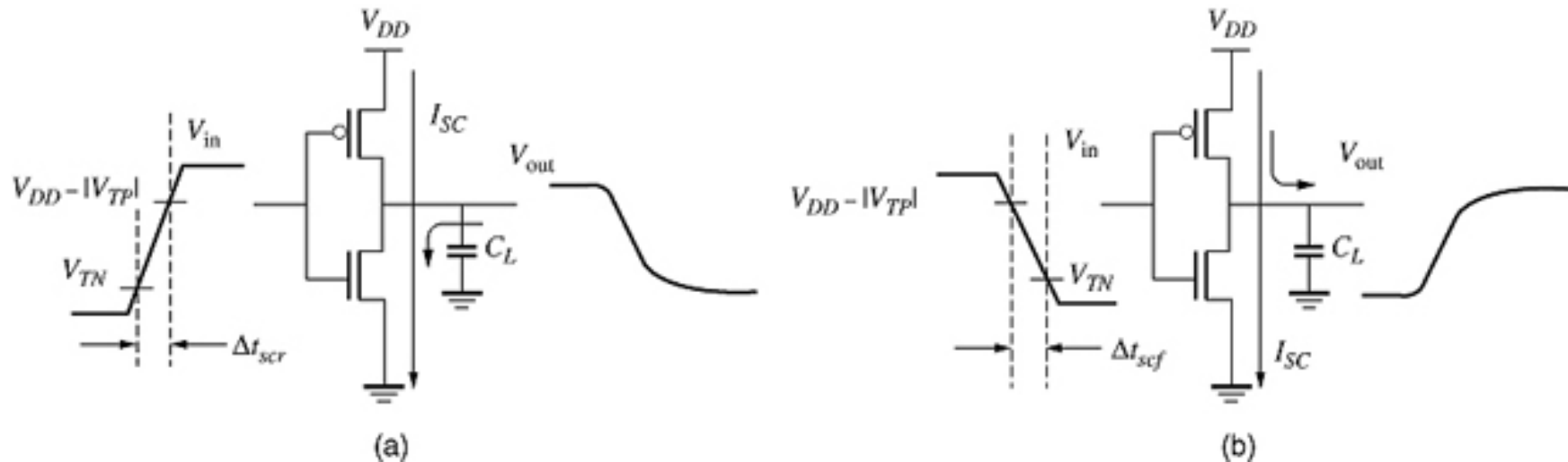

- ❑ Short circuit or crowbar current is the current that flows directly from VDD to GND during switching transition, when both transistors are ON, i.e. $V_{tn} < V_{in} < V_{DD} - V_{tp}$
- ❑ Short circuit current can be significantly large when NMOS and PMOS are large. (Why?)

Computing Short-Circuit Power

 

- For clock circuit that toggles twice in each period (low-to-high and high-to-low), the active power consumption is computed as:

Computing Short-Circuit Power

- Assuming a symmetric inverter, where $V_{tn} = |V_{tp}|$ and $K'_n(W/L)_n = K'_p(W/L)_p$, then the short circuit currents for rise and fall will be symmetric, and therefore

$$I_{mean} = \frac{1}{T} \int_0^T I(t) dt = \frac{4}{T} \int_{t_1}^{t_2} \frac{K'_n W}{2L} (V_{in}(t) - V_t)^2 dt$$

$$V_{in} = \frac{V_{DD}}{\tau} t \quad t_1 = \frac{V_t}{V_{DD}} \tau \quad \text{and} \quad t_2 = \frac{\tau}{2}$$

$$I_{mean} = \frac{K'_n}{12} \left(\frac{W}{L}\right) \frac{1}{V_{DD}} (V_{DD} - 2V_t)^3 \frac{\tau}{T} \quad \Rightarrow \quad P_{sc} = V_{DD} I_{mean}$$

Example: Short Circuit Power in an Inverter

What is the short circuit power in an inverter if: $V_{DD} = 2 \text{ V}$, $V_{tn} = -V_{tp} = 0.5 \text{ V}$, $T = 500 \text{ ps}$, $f = 2 \text{ GHz}$, $K_n = 200 \mu\text{A}/\text{V}^2$, $W/L = 2$, and the pulse rise and fall times are 100 ps .

$$I_{mean} = \left(\frac{1}{12}\right) \left(\frac{200 \mu\text{A}}{2 \text{ V}}\right) \left(\frac{2}{1}\right) (2 - 1)^3 \left(\frac{100 \text{ ps}}{500 \text{ ps}}\right) = 3.33 \mu\text{A}$$

so

$$P_{sc} = 2 \text{ V} \times 3.33 \mu\text{A} = 6.7 \mu\text{W}$$

Minimum SC Power Design Techniques

- ❑ Prime choice: Reduce voltage!
 - Recent years have seen an acceleration in supply voltage reduction
 - Design at very low voltages still open question (0.6 ... 0.9 V by 2015!)
- ❑ Faster rise and fall times
- ❑ Smaller transistors (will increase delay)
- ❑ Higher V_t (will increase delay)
- ❑ Lower frequency (will decrease performance)

$$I_{mean} = \frac{K'_n}{12} \left(\frac{W}{L}\right) \frac{1}{V_{DD}} (V_{DD} - 2V_t)^3 \frac{\tau}{T}$$