

ECE321 – Electronics I

Lecture 22: Combinational Logic: Transmission Gates

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh.unm.edu

Review of Last Lecture

NAND Gate

- **Basic circuit for CMOS NAND Gate**
- **Circuit analysis techniques**
- **Proper transistor sizing**

NOR Gate


- **Basic circuit for CMOS NOR Gate**
- **Circuit analysis techniques**
- **Proper transistor sizing**

Today's Lecture

□ **Transmission Gates**

- **Basic circuit for Transmission Gate**
- **Circuit analysis Techniques**
- **Complex Logic Gates using Pass Transistors**


NMOS and PMOS as Switching Elements

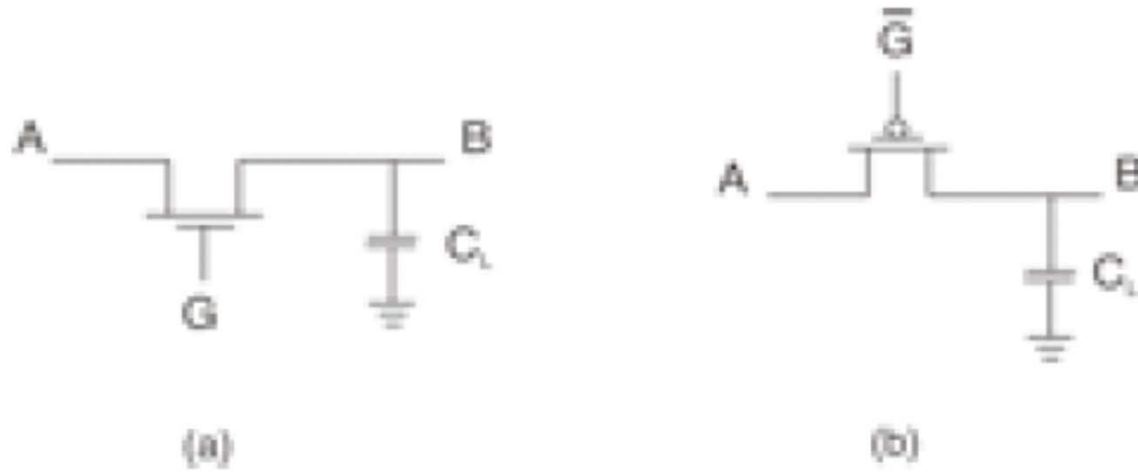

- ❑ In circuit (a), if A has a full swing, what is the range of output voltages?
- ❑ In circuit (b), if A has a full swing, what is the range of output voltages?



Example 1: Transmission Buffer

- Assuming $|V_{tp}| = V_{tn} = 0.5V$, what is V_{out} ?

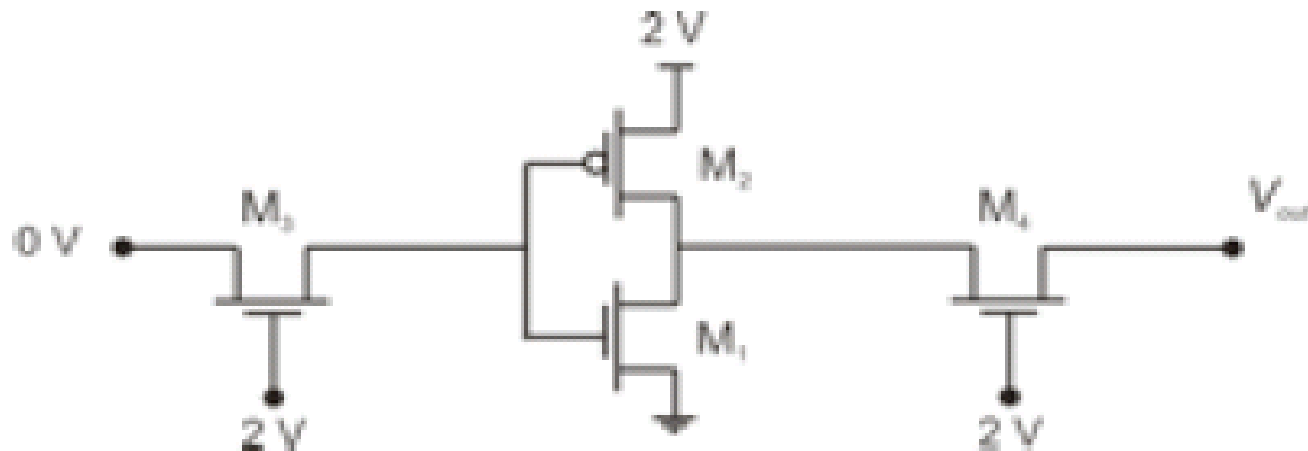


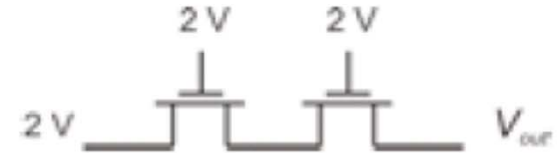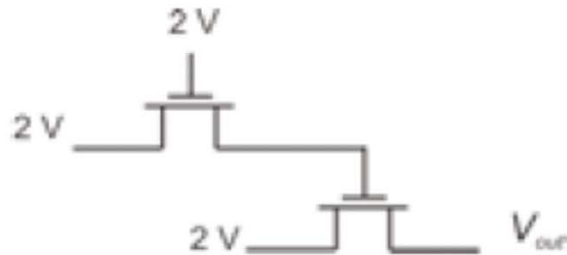Example 2: Some Other Examples

Given the pass transistor circuit with $V_{in} = 0.5$ V. Ignore the body effect. What is the output voltage?




CMOS Transmission Gate

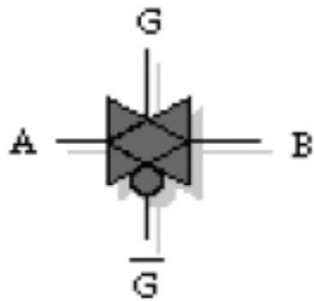

(a)



A	G	C
0	1	0
1	1	1
0	0	Z
1	0	Z

(b)

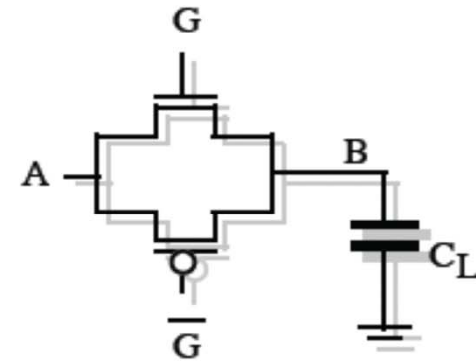

(c)


Tri-state CMOS Inverter

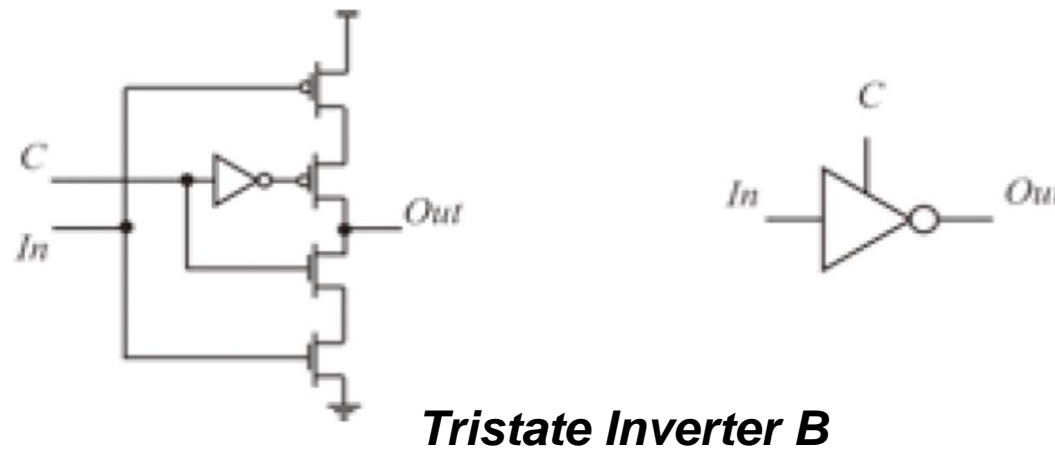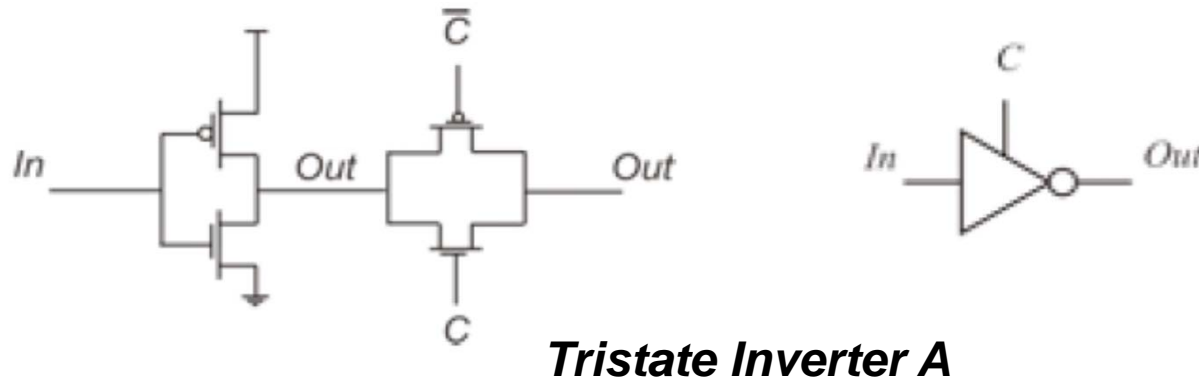

□ Which circuit, A, or B, is better to use?

Complex Logic with Transmission Gates

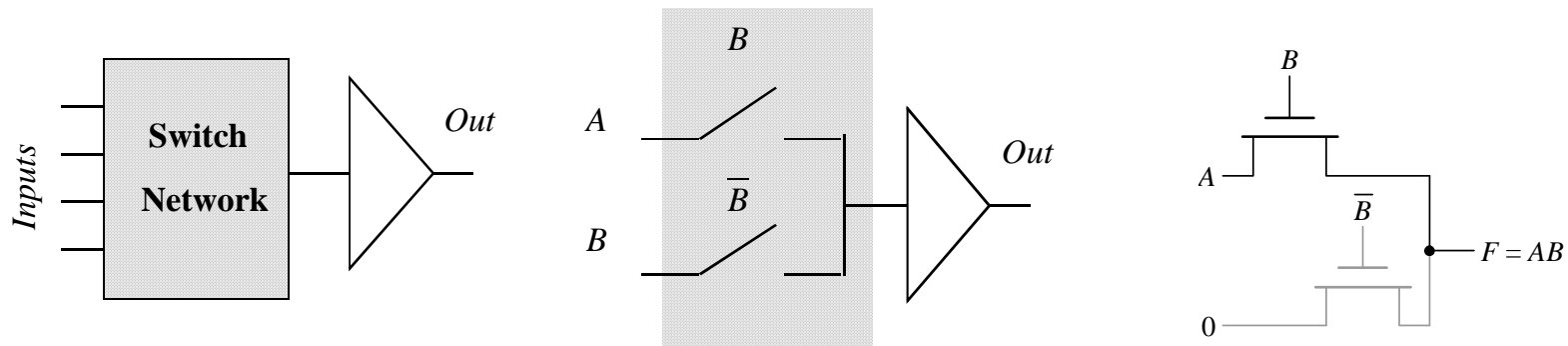- ❑ Another way of reducing the number of transistors in complex logic gate is to use switch network.
- ❑ For instance AND gate can be implemented by only 4 transistors (instead of 6 transistor in CMOS implementation)



- N transistors
- No static consumption

Examples: Pass Transistor Networks

- Differential logics can be implemented using pass-transistor logic.
- These examples show that a complicated logic gate can be implemented with only few transistors

