

# ECE321 – Electronics I

## Lecture 23: Logic Design Style: Static

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Tuesday 2:00-3:00PM or by appointment*

*E-mail: [pzarkesh.unm.edu](mailto:pzarkesh.unm.edu)*

# *Review of Last Lecture*

---

## □ **Transmission Gates**

- **Basic circuit for Transmission Gate**
- **Circuit analysis Techniques**
- **Complex Logic Gates using Pass Transistors**

# *Today's Lecture*


---

---

## □ CMOS Static Gates

- Implementation of a Complex Logic
- Circuit Analysis for CMOS Static Gates
- Transistor Sizing


# Static CMOS Logic Gate

 

PUN and PDN are **dual** logic networks

- ❑ Static Logic is a gate where the output is maintained at 0 or 1 as long as power is applied
- ❑ PUN and PDN are dual (Complimentary) to drive the output from 0 to 1 and 1 to 0 full rail ( $V_{SS}$  to  $V_{DD}$ )

# PUN and PDN Networks

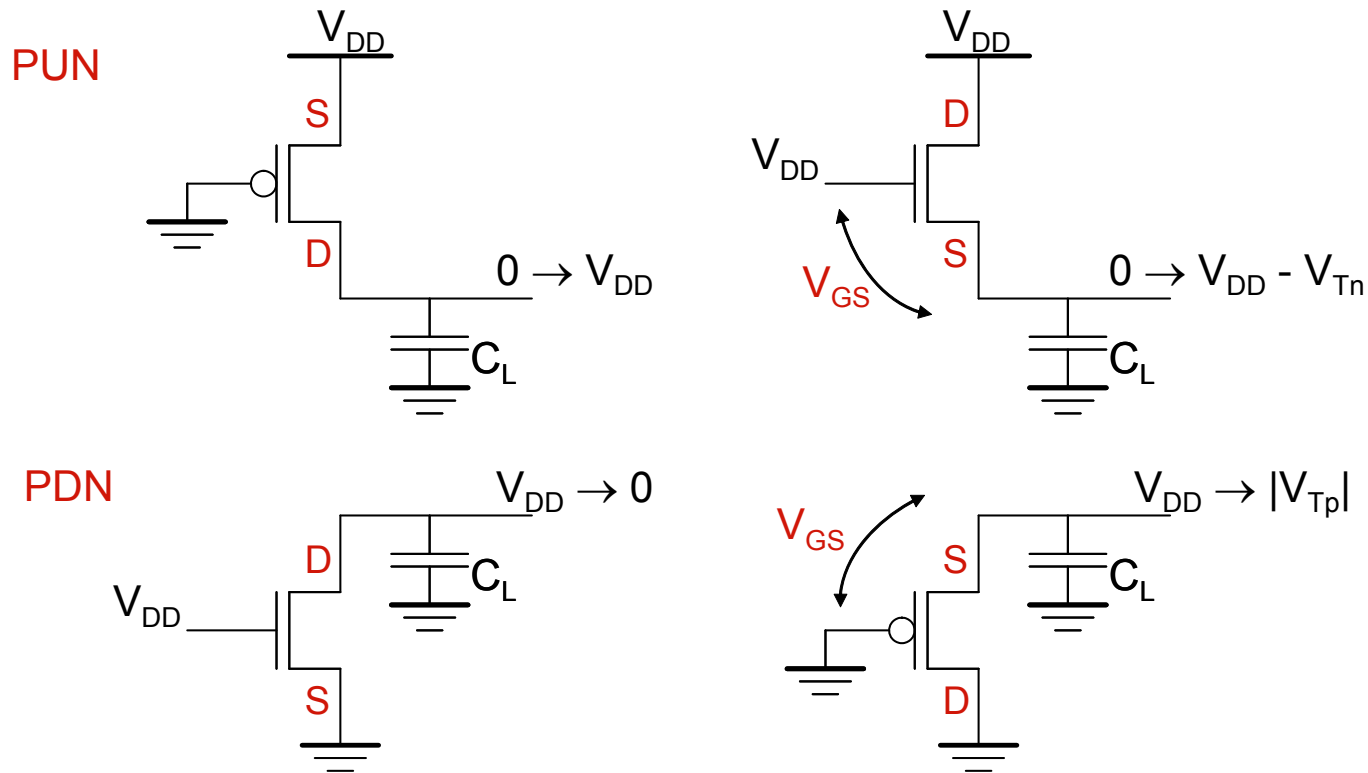


- ❑ NMOS is a good pull down device (PDN)
- ❑ PMOS is a good pull up device (PUN)

# Example: NAND Gate

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


PUN:  $\overline{A+B}=\overline{AB}$  (Conduction to VDD)

PDN:  $AB$  (Conduction to GND)


- How do you size transistors to have approximately the same delay as an inverter?
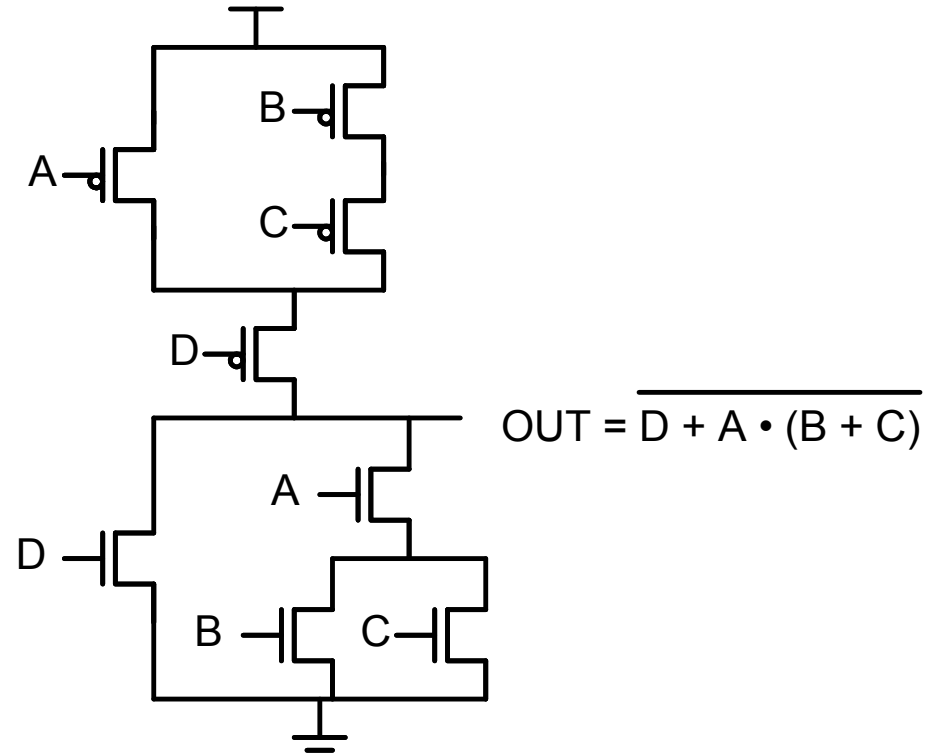
# Example: More Complicated Gate

- Consider  $F = D + A(B + C)$ 
  - Stacks give the AND function
  - Parallel gates give the OR function
- Derive the PDN in hierarchical fashion
- Build the complement for the PUN
  - Convert stacks to parallel
  - Convert parallel to stacks


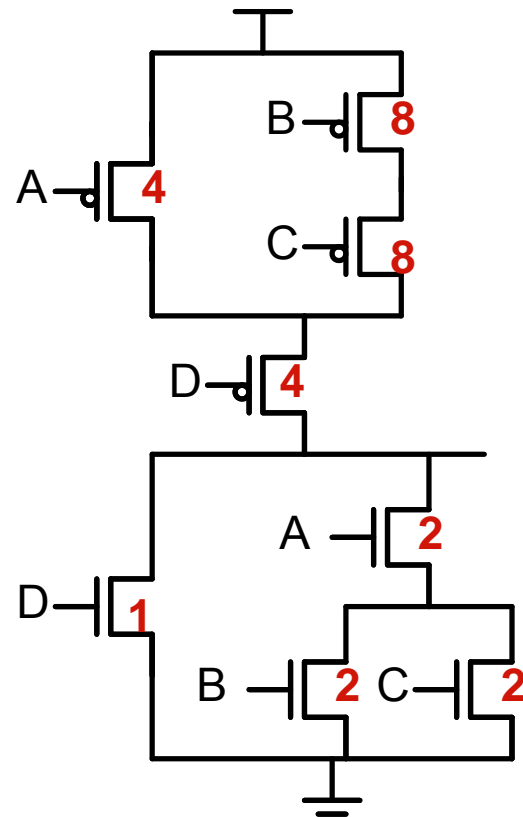
# Transistor Sizing of a Complex CMOS Gate




$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

- Size of transistors to have the same delay of an inverter when  $(W/L)_P=2$  and  $(W/L)_N=1$


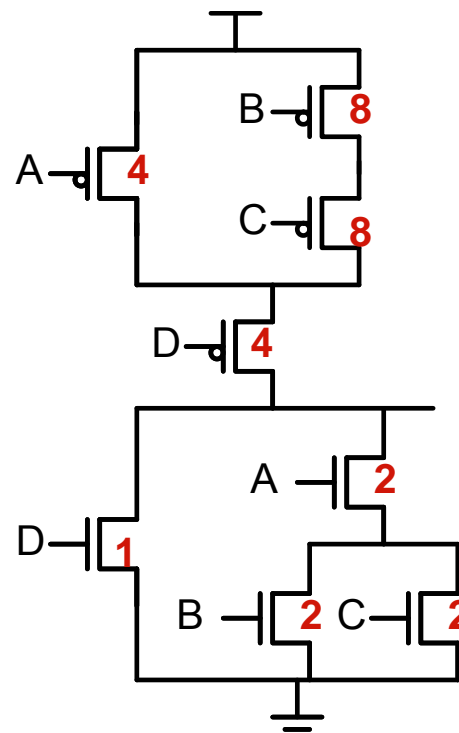
# Circuit Analysis for Complex Gates

- ❑ To analyze complex gates for delay, power, and VTC, use the same concepts you have learned for inverter.
- ❑ Example: A CMOS gate with  $V_{DD}=5V$  is designed such that the base  $(W/L)=10$ . Assume that  $V_{Tn}=0.7$ ,  $V_{Tp}=-0.6$ ,  $K'_n=100 \mu A/V^2$ ,  $K'_p=-60 \mu A/V^2$ , and the load capacitance is  $100fF$ . Use the constant current source model to find the best case and the worst case  $t_{pHL}$  and  $t_{pLH}$



$$OUT = D + A \cdot (B + C)$$