

ECE321 – Electronics I

Lecture 27: SRAM Memories

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh.unm.edu

Review of Last Lecture


- **Timing Issues**
 - **Critical Path**
 - **Timing Constraints**

Today's Lecture

- ❑ **Static Random-Access Memory (SRAM)**
 - SRAM cell
 - SRAM architecture
 - Sense amplifier


SRAM Cell

 - ❑ SRAM cell is quite similar to flip-flop without any protective circuitry
- ❑ Therefore, reliable operation imposes transistor sizing constraints.
- ❑ Cell is selected by word line (WL=1) and read and write are often differential




Memory Read and Write Timing

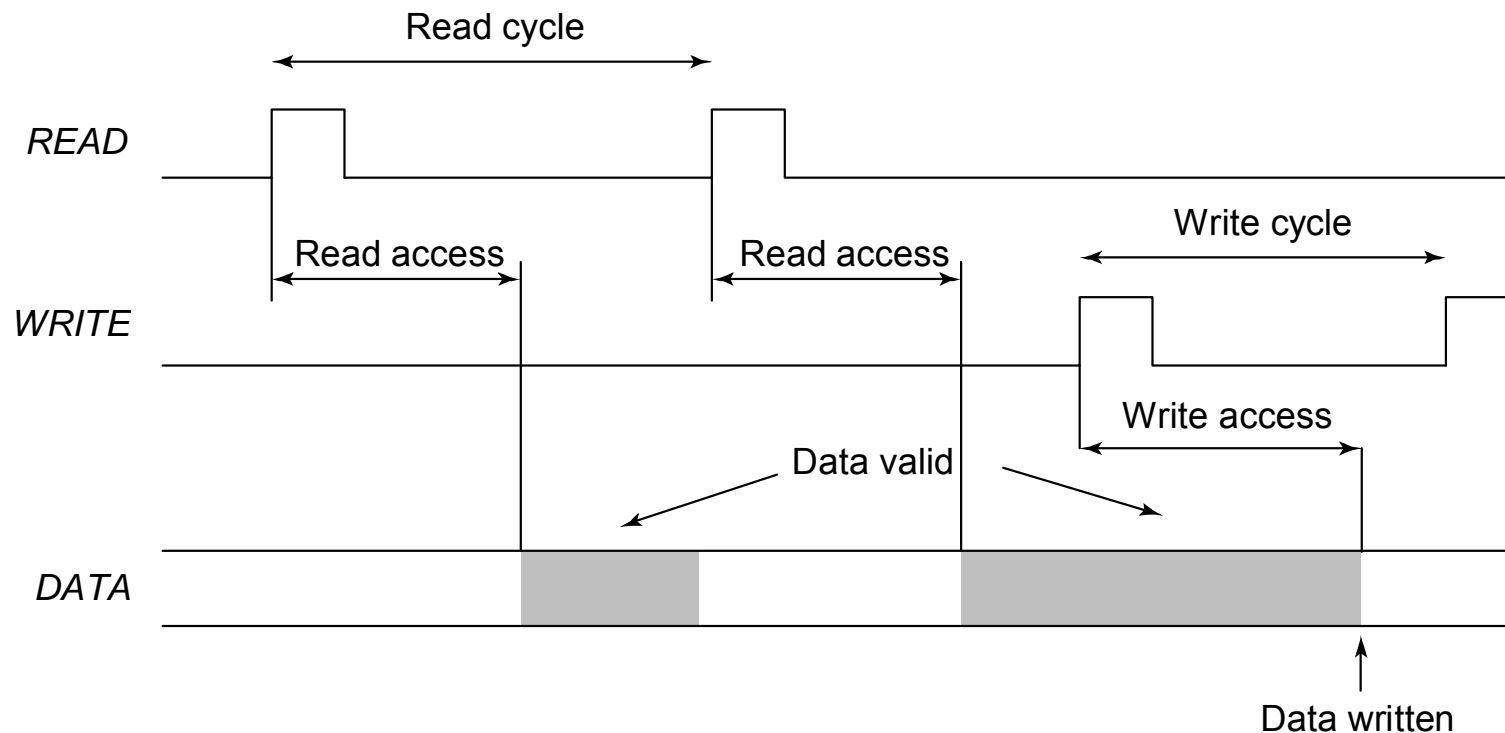- Memory timing parameters includes: *read-access time*, *write-access time*, *read-cycle time*, and *write-cycle time*





6-T SRAM Cell

 - ❑ SRAM cell consists of 6 transistors (6T cell) with differential BL
- ❑ When reading, BLs are at VDD and have high capacitance
 - This is essentially a short to VDD for both side of the cell
 - The side at logic one is unaffected. e.g. Q at VDD and BL at VDD
 - Node \bar{Q} is pulled up by the voltage divider of two NMOS transistors




SRAM Layout

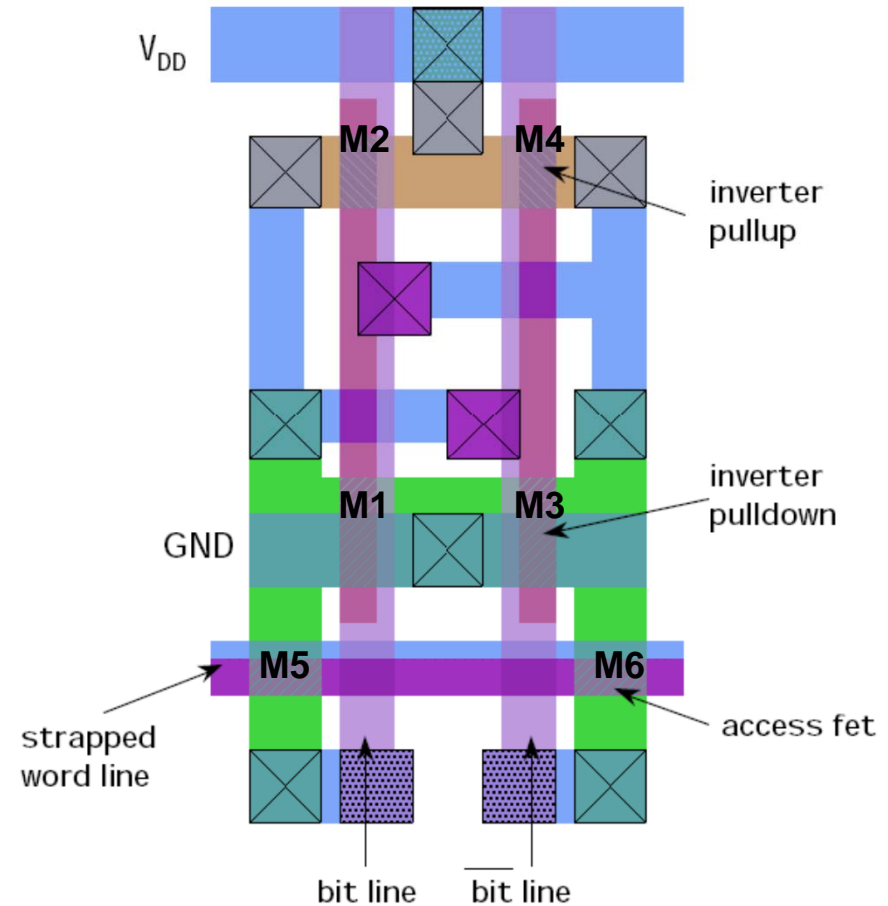 - Layout must be symmetric to reduce process variation



Real SRAM Cell

- ❑ Real cells will have extensive corner rounding and layer misalignment
 - Hence the cell will not be symmetric in reality
 - Note rounding and misalignment!
- ❑ Since there are a lot of statistics in a large SRAM, e.g., 1MB L2 has nearly 10M cells (including ECC) so random variation will work against full yield
 - This can be partly made up by redundancy
 - But solid cell design is essential
 - Worst case process corners must be used

 

SRAM Read - Sensing

- ❑ **The simplest reading is an inverter sense**
 - This is slow unless the BL is very short
- ❑ **Generally, we want to use a sense amplifier**
 - Smaller swing on BLs (only about 50mv is necessary)
 - The SRAM cell transistors are small and weak and BL has high capacitance. Therefore, BL swing is very slow. Faster operation requires smaller swing.
 - Smaller swing saves power (as long as we don't drive the BLs with the sense amplifier) by limiting swing on the BLs

Sense Amplifier : Static

- ❑ A simple OPAMP can be used as sense amplifier
 - Unfortunately in practice, it is very slow to respond
 - This is static, since the output is only as a function of input
- ❑ This circuit has serious CMRR problems, particularly when both inputs are near the VDD rail

