

# ECE321 – Electronics I

## Lecture 7: Basic Circuits with MOSFETs

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Tuesday 2:00-3:00PM or by appointment*

*E-mail: [pzarkesh.unm.edu](mailto:pzarkesh.unm.edu)*

# *Review of Last Lecture*

---

- ❑ **Threshold Voltage Equation**

# *Today's Lecture*

---

---


- ❑ **Some Example of MOS Circuits**

# Example 1: Region of Operation

In the circuit configurations below:

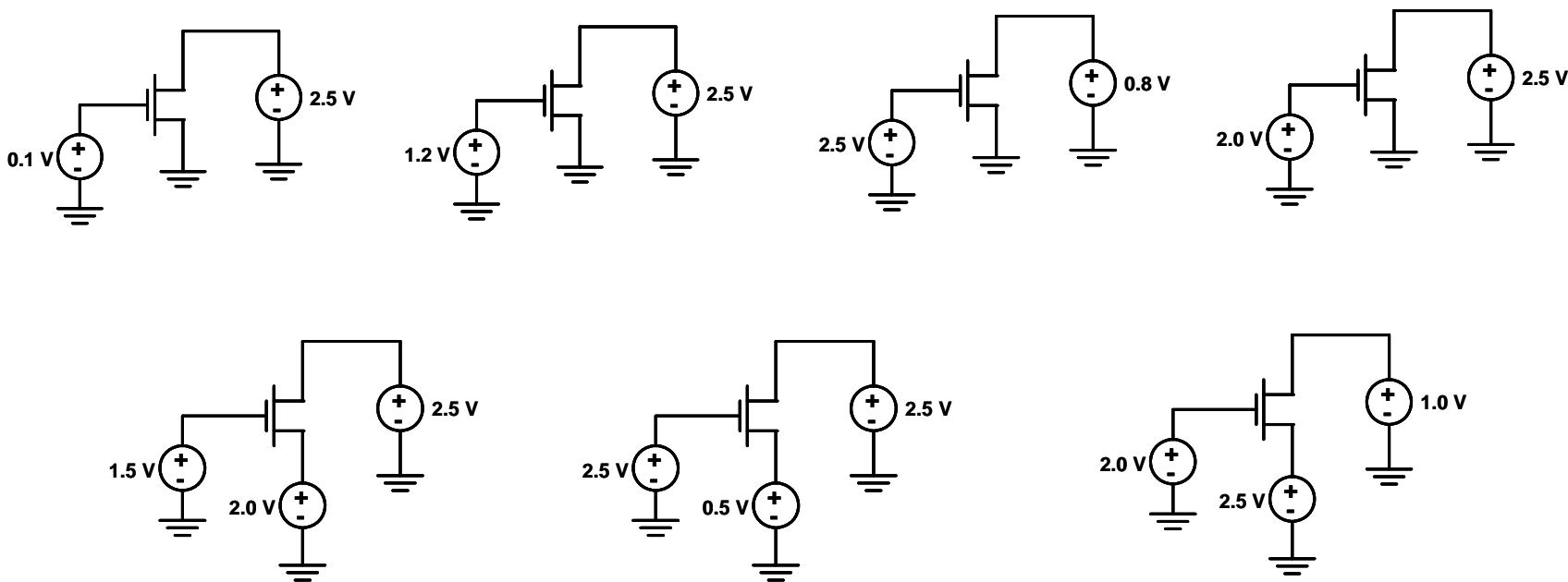- 1) Identify Drain and Source terminals assuming the device is an NMOS
- 2) Identify operating region of each transistor (cutoff, linear, saturation)
- 3) Write the drain current equation


Assume  $V_T = 0.5 \text{ V}$ ,  $K'_n \left(\frac{W}{L}\right) = 1 \frac{\text{mA}}{\text{V}^2}$ . Ignore the body effect.



## Example 2: Gate Bias Problem


---

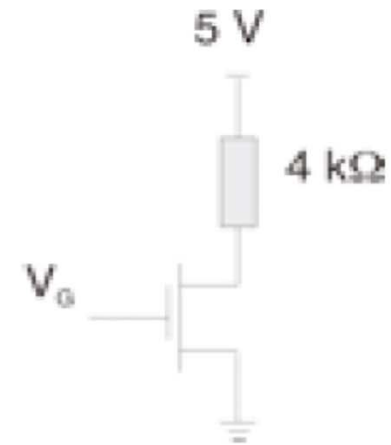- 3.7. Given that  $K_n = 250 \mu\text{A}$ ,  $V_{tn} = 0.5 \text{ V}$ , and  $W/L = 3$ . What  $V_G$  makes transistor biased at the saturated/non-saturated boundary.



# Example 3: PMOS Circuit

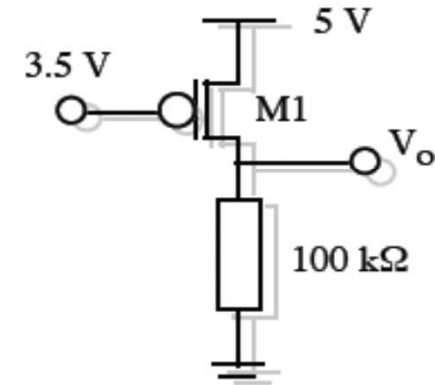- 3.12. Calculate  $I_D$  and  $V_O$  for circuit where  $V_{tp} = -0.8$  V,  $K_p = 30$   $\mu\text{A}/\text{V}^2$ , and  $W/L = 2$ .



## Example 4: Current Equation

- Find  $I_{in}$  as a function of  $V_{in}$  assuming  $V_T < V_{in} < V_{DD} - V_T$  (assume long channel device and ignore channel length modulation)

