

University of New Mexico
Department of Electrical and Computer Engineering

ECE 520 - VLSI Design (spring 2026)

Homework #5

Due in class: Thursday March 5, 2026

1. Design a CMOS inverter using 0.25um CMOS devices, such that $V_M = V_{DD}/2$. Assume that the NMOS and PMOS device parameters are given below and $V_{DD} = 2.5V$ and $(W/L)_n = 1.5$.

- In our generic 0.25 micron CMOS process, using the process parameters from table a $V_{DD} = 2.5V$, and a minimum size NMOS device ($(W/L)_n$ of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-0.8	-30×10^{-6}	-0.1

2. Estimate all static parameters of the inverter in problem 1, including V_{OL} , V_{OH} , V_M , V_{IL} , V_{IH} , NML , and NMH .