

Homework 6 Solutions

Problem 1

a) V_{OL} is limited by the PMOS. The source of the PMOS is on the output node.

$V_{SG} > V_T$ to be on


The PMOS is on when $V_G = 0V$

The output capacitor is then connected to ground and continues to discharge until $V_{SG} = V_T$ and the connection to ground is broken.

$$V_{out,min} = V_{Tp}$$

$$\text{Similarly, } V_{OH} = V_{DD} - V_{tn}$$
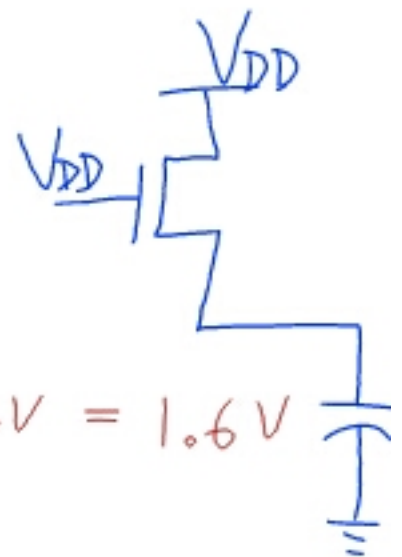
$$V_{swing} = V_{OH} - V_{OL} = 2.1 - 0.5V = 1.6V$$



b)

For input $0 \rightarrow 2.5$

Energy supplied:

$$E = \int P dt = \int i(t) V_{DD} dt$$

$$\begin{aligned}
&= \int C \frac{dV_c}{dt} V_{DD} dt = C V_{DD} \int dV_c \\
&= C V_{DD} V_c = C V_{DD} [V_{DD} - V_{tn} - V_{tp}] \\
&= 0.6 \text{ pJ}
\end{aligned}$$

Energy dissipated:

energy in capacitor

$$\begin{aligned}
E &= \int P dt = \int i(t) V_c dt \\
&= \int C \frac{dV_c}{dt} V_c dt = \int C V_c dV_c \\
&= \frac{1}{2} C V_c^2 \Big|_{V_{tp}}^{V_{DD} - V_{tn}} \\
&= \frac{1}{2} C [(V_{DD} - V_{tn})^2 - V_{tp}^2] \\
&= 3.12 \times 10^{-13} \text{ J}
\end{aligned}$$

$$E_{diss} = E_{supp} - E_{cap}$$

$$E_{diss} = 0.288 \text{ pJ}$$

for input $2.5 \rightarrow 0$

$$E_{supp} = 0 \text{ J} \quad \text{Capacitor is discharging}$$

$$E_{diss} = E_{cap} = 0.312 \text{ J}$$

$$\text{c) } t_{PLH} = C \Delta V / I_{av}$$

$$\Delta V = (V_{OH} + V_{OL}) / 2 - V_{OL} = 0.8 \text{ V}$$

$$I_{av} = (I_1 + I_2) / 2$$

$$I_1: V_{out} = V_{OL} = 0.5V$$

$$V_{DS} = 2V$$

$$V_G = V_{DD}$$

$$V_{GS} = V_{DD} - V_{out} = 2V$$

$$V_{DS} > V_{GS} - V_{tn}$$

Sat!

$$I_1 = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_{tn})^2 = 768 \mu A$$

$$I_2: V_{out} = (V_{OH} + V_{OL}) / 2 = 1.3V$$

$$V_{DS} = 1.2V$$

$$V_{GS} = 1.2V$$

Sat

$$I_2 = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_{tn})^2 = 192 \mu A$$

Because $V_G = V_D$ for all values of V_{out} , the device stays in saturation.

$$\text{So then } I_{av} = (I_1 + I_2) / 2 = 480 \mu A$$

$$\Delta t = C \Delta V / I_{av} = (150 \text{ fF}) (0.8V) / 480 \mu A$$

$$\Delta t = 2.5 \times 10^{-10} = 0.25 \text{ ns}$$

$$d) V_{OH} = V_{DD} - V_{tn}$$

$$V_{tn} = V_{t0} + \gamma [\sqrt{|2\phi_F| + |V_{SB}|} - \sqrt{|2\phi_F|}]$$

$$V_{OH} = V_{DD} - (V_{t0} + \gamma [\sqrt{|2\phi_F| + |V_{SB}|} - \sqrt{|2\phi_F|}])$$

$$V_{OH} = V_{DD} - (V_{t0} + \gamma [\sqrt{|2\phi_F| + V_{OH}} - \sqrt{|2\phi_F|}])$$

$$V_{OH} = 1.791V$$

Problem 2

$$a) I_D = I_0 \exp(V_{GS}/(n kT/q)) (1 - \exp[-V_{DS}/(kT/q)])$$

$$I_{Dp} = I_{Dn}$$

$$|V_{GSp}| = 0.4 - V_m$$

$$V_{GSn} = V_m$$

$$|V_{DSp}| = 0.4 - V_m$$

$$V_{DSn} = V_m$$

Focus on $(1 - \exp[-V_{DS}/(kT/q)])$ for a moment

assuming $V_m = \frac{1}{2} V_{DD} = 0.2V$ since V_m is usually near the center of the voltage rails

$$V_{DSn} = |V_{DSp}| = 0.2$$

$$1 \gg \exp[-V_{DS}/V_t]$$

$$\text{so } (1 - \exp[-V_{DS}/(kT/q)]) \approx 1$$

now back to $I_{Dn} = I_{Dp}$

$$\exp(V_{GSn}/nV_t) = \exp(|V_{GSp}|/nV_t)$$

$$V_{GSn} = |V_{GSp}|$$

$$V_m = 0.4 - V_m$$

$$V_m = 0.2 \text{ V}$$

$$b) g = -\frac{1}{n} (\exp[V_{DD}/2V_t] - 1)$$

$$n = 1.5$$

$$g = -1504$$

$$V_{IL} = V_m + (V_{DD} - V_m)/g = 0.1999 \text{ V}$$

$$V_{IH} = V_m - \frac{V_m}{g} = 0.2001 \text{ V}$$

$$c) V_{OL} = 0 \text{ V}, V_{OH} = V_{DD}$$

$$NM_H = V_{OH} - V_{IH} = 0.1999 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.1999 \text{ V}$$