

ECE520 – VLSI Design

Lecture 12: Gate Sizing (Inverter Chain)

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Wednesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Review of Last Lecture

Combinational Logic


- **Logic Design**
- **Transistor Sizing**
- **Delay Analysis**

Today's Lecture

- Quiz #2
- Gate Sizing (Inverter Chain)

Sizing Logic Path for Speed

 
- ❑ Frequently, input capacitance of a logic path is constrained
- ❑ Logic also has to drive some capacitance
 - Example: ALU load in an Intel's microprocessor is 0.5pF
- ❑ How do we size the ALU data path to achieve maximum speed?



- ❑ Wide gate to drive a large load must be driven in turn
 - Large block inputs “push their load into the chip”


Definition: Fan-out

 - ❑ Fan-out is the ratio between gate external load capacitance to its input capacitance, i.e. $f = C_{out} / C_{in}$.
- ❑ Another way: Fan-out is the “effective” number of gates that are connected to the output of the gate.
- ❑ Examples:




Inverter Chain Driving a Load Capacitance

- ❑ Assume inverter chain with fan-out factor of $f = C_{out} / C_{in}$
- ❑ Delay of i^{th} stage is $t_{p,i} \approx f_i \cdot t_{p0}$, where t_{p0} is intrinsic delay of an inverter
- ❑ Intuitively, for N stages the delay through each stage should be equal (this is true for most optimization problems)
- ❑ Therefore, delay and fan-out of every stage must be identical and equal to $t_p = f \cdot t_{p0}$

 


Example 1: Buffer Design

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

Example 2: Buffer Design

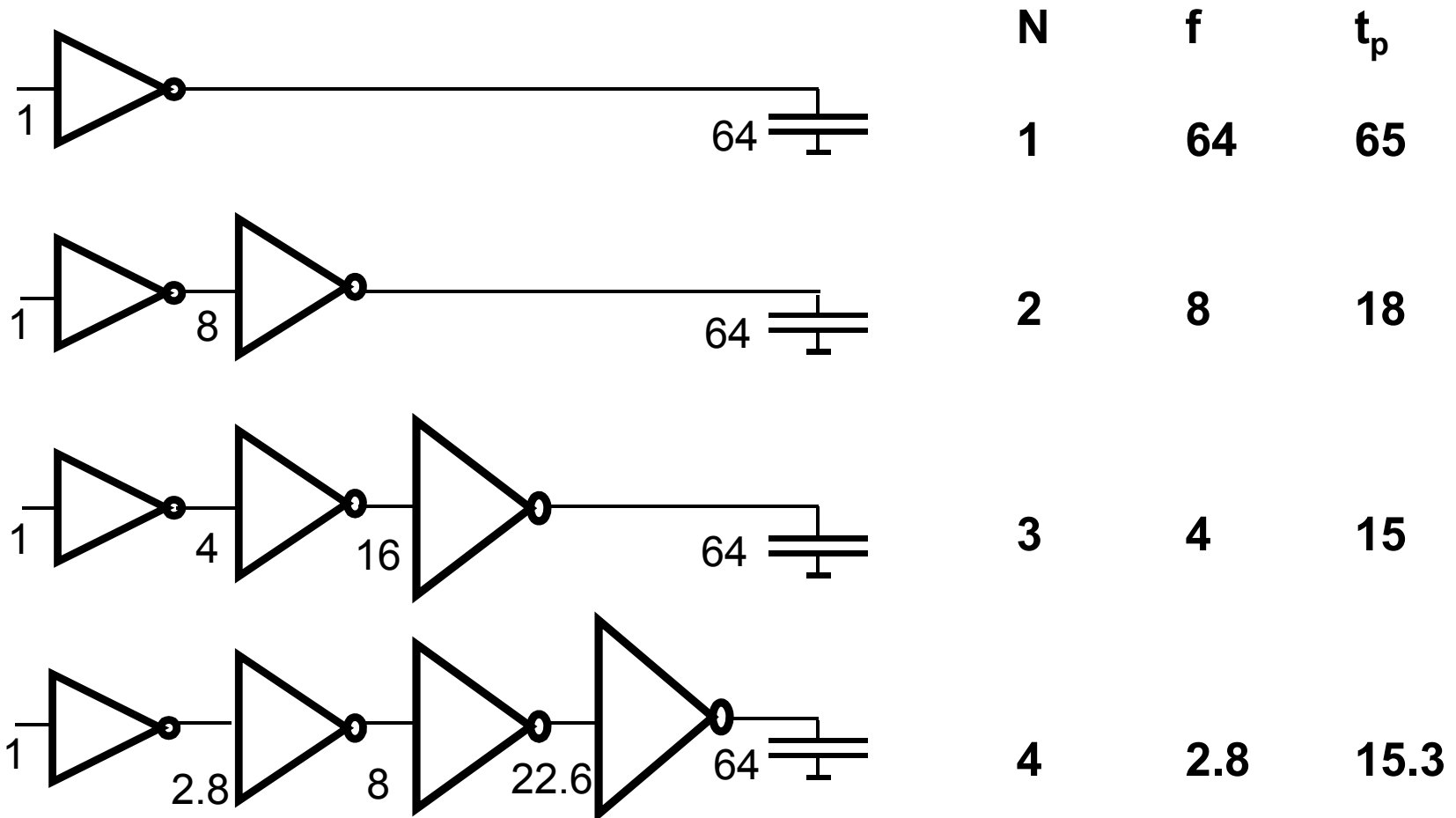

How to Compute Optimum N?


- ❑ Delay of a chain of N inverters is $t_p(\text{chain}) = N \cdot f \cdot t_{p0}$
- ❑ Define the ratio of load capacitance to input capacitance as $F = C_L / C_G$ (total for path, as opposed to f for each stage)
- ❑ C_L is the load driven, C_G is the load presented by the driving inverter
- ❑ Therefore, $F = f^N$
- ❑ Solving for $t_p(\text{chain})$ gives:

$$t_p(\text{chain}) = \text{Ln}(F) \left(\frac{f}{\text{Ln}(f)} \right) t_{p0}$$

- ❑ When $f = e = 2.72$, minimum delay is:

$$t_p(\text{chain}) = e \text{Ln}(F) t_{p0}$$

Normalized Delay versus f

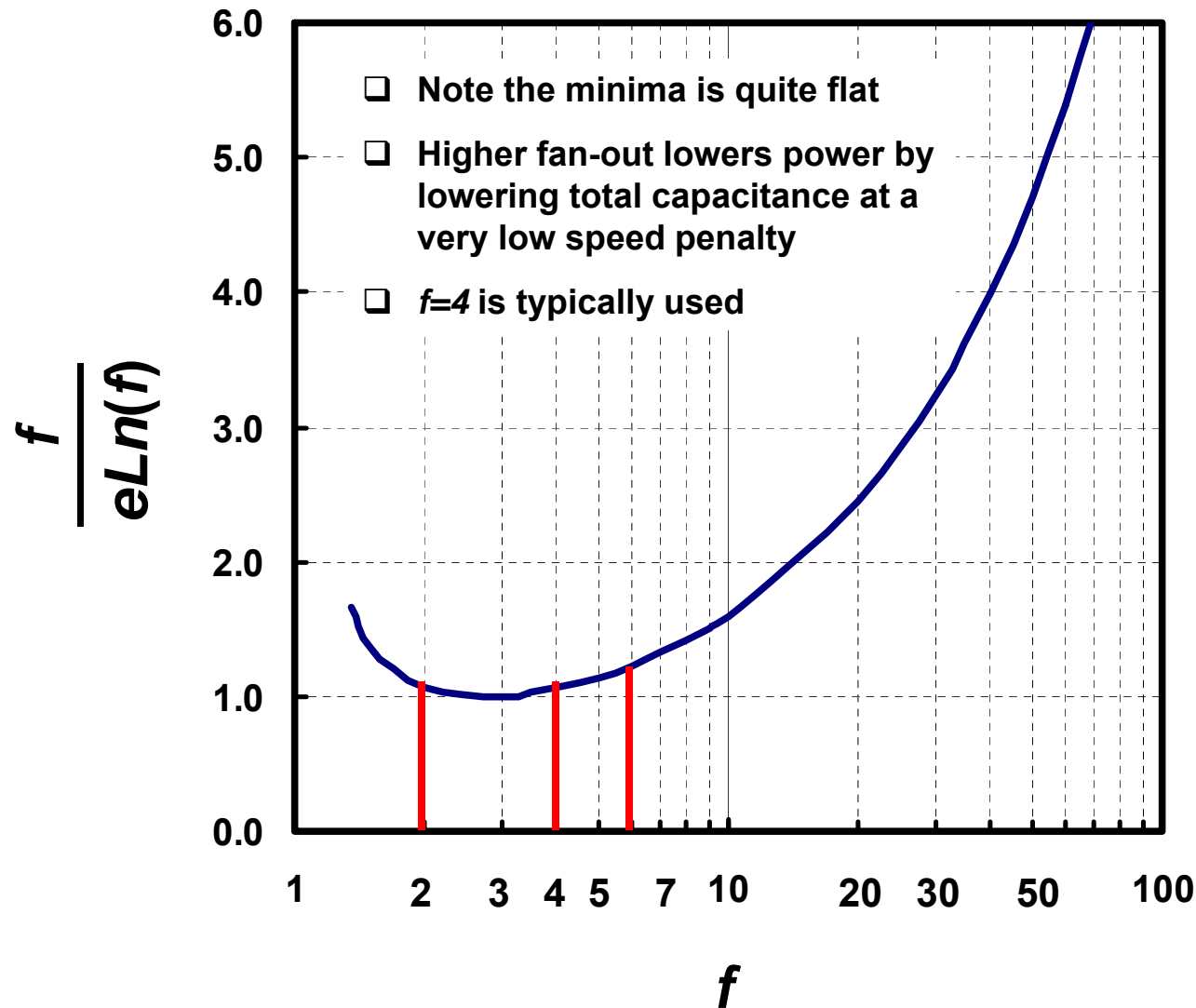

Design Guideline

- ❑ Fan out should be approximately 4 unless path is very critical, i.e., limiting the entire chip speed
- ❑ This is so fundamental that speed is frequently discussed as the “fan out of 4 delay” as a figure of merit
- ❑ Start from the driven load and work backwards
- ❑ Driven load may be: Global or local routing load, clock distribution, and high fan-out net
- ❑ Take the time to size well, power and performance are the value added in custom design