

ECE520 – VLSI Design

Lecture 18: Timing Issues

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Wednesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Review of Last Lecture

- **Sequential Logic**
 - Latches and Flip-Flops
 - Timing Characteristics
 - Design of Latches and Flip-Flops
 - Setup and Hold Time Issues


Today's Lecture

Timing Issues

- **Critical Path**
- **False Path**
- **Clock Skew**
- **Clock Jitter**


Pipelined Data path Circuit

 - ❑ Flip flops synchronize data at each pipe stage start and finish
- ❑ Logic between them is combinational
- ❑ Since each stage begins and ends on a clock edge we can divide and conquer to determine the system timing
- ❑ This is called “timing analysis”




Timing Analysis

 - ❑ Measure each path through the logic between FF's
- ❑ We really only care about the longest path, called maximum delay for setup
- ❑ Similarly, we only care about the shortest path, called minimum delay (or contamination delay) for hold
- ❑ The path that gives the maximum delay on the whole chip is called "critical path"



False Path

 
- ❑ Be careful! If a critical path cannot be exercisable, it is a “false path”.
- ❑ In this case, you have to continue your search for maximum delay path that is exercisable.
- ❑ In general, finding “false path” is not easy and requires function evaluation
- ❑ Example: What is the minimum and maximum delays in this circuit?



gate	delay
NOT	2
AND	4
OR	4


Minimum Clock Period

 - ❑ Don't forget to consider delay of flip flops (setup, C2Q, and hold time) in maximum delay computation
- ❑ Example: Assuming that the setup time is 1ns, hold time is 1ns, and C2Q delay is 2ns, what is the minimum clock period? Why?



Generating Clocks

- ❑ Clocks are usually generated at a single origin
- ❑ A phase locked loop (PLL) is generally used to generate a high quality clock for the chip
 - Phase locked with the outside reference clock
 - PLL's can multiply the reference clock speed
 - E.g., $T_{REF} = 10\text{ns}$ (100MHz), $T_{CLK} = 1\text{ns}$ (1GHz)
- ❑ The clock must then be driven through many stages to generate enough drive strength to drive all the flip flops and latches on the chip
 - These can number in the 100's of thousands
 - Large equivalent load - add the gate widths of transistors in "clk" path
 - Usually the widest transistors are clock drivers

 


Clock Uncertainty

❑ Clock skew

- Spatial variation in temporally equivalent clock edges; includes: deterministic + random


❑ Clock jitter

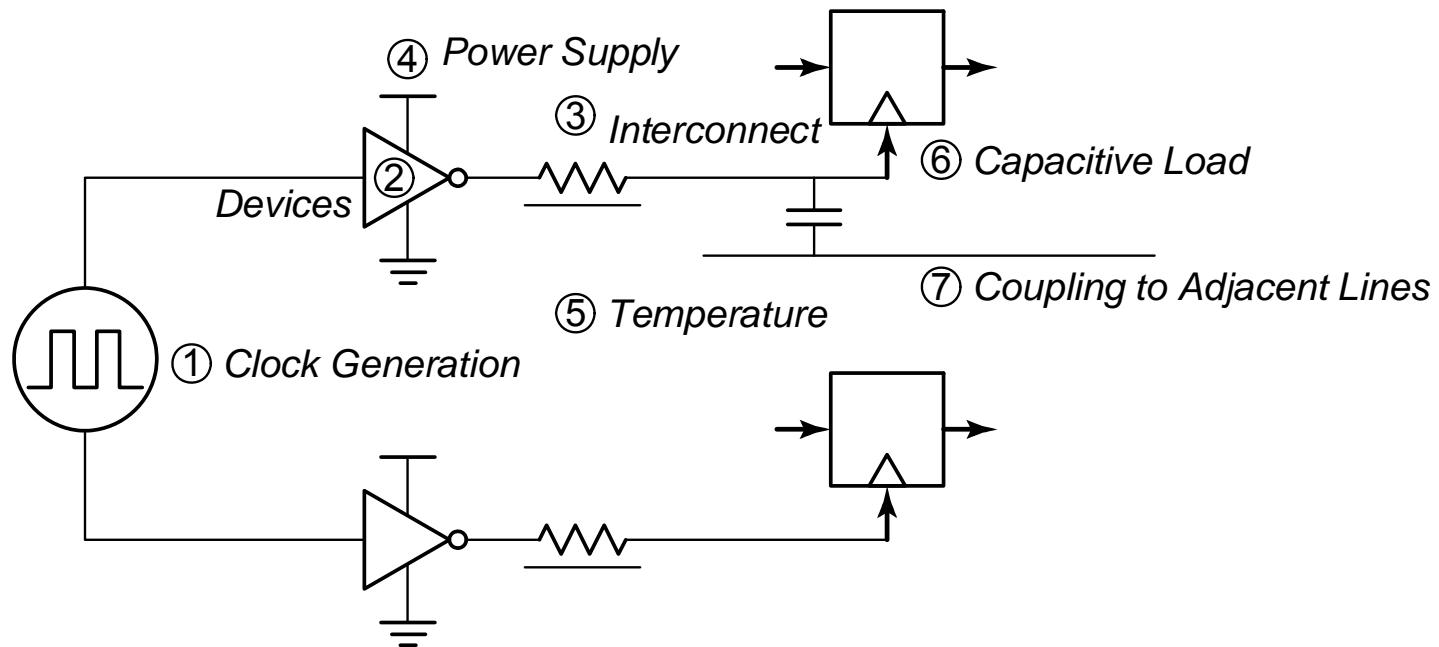- Temporal variations in consecutive edges of the clock signal; includes: modulation + random noise



Clock Skew and Setup Time Constraint

 - ❑ Worst case is when receiving edge arrives early (positive δ)
- ❑ Maximum delay is impacted since a clock cycle can be shorter than ideal
 - Simply subtract the expected clock skew and jitter from the cycle time when designing
 - A failure here is not too bad: It means that you missed a setup time
 - The part is then “slow”—It will still work at a reduced clock rate




Minimum cycle time:

$$T - \delta = t_{c-q} + t_{su} + t_{logic}$$

Clock Skew and Hold Time Constraint

- ❑ Worst case is when receiving edge arrives late, (positive δ)
- ❑ Minimum delay is impacted since a receiving clock edge can be later than ideal
 - Means that the hold time at the receiving latch is more easily violated
 - A failure here is pretty much catastrophic
 - Since skew is built-in, there is nothing you can do post-silicon to fix it!
 - It is generally worth-while to add more design guard-band (margin) to your min-delay timing!

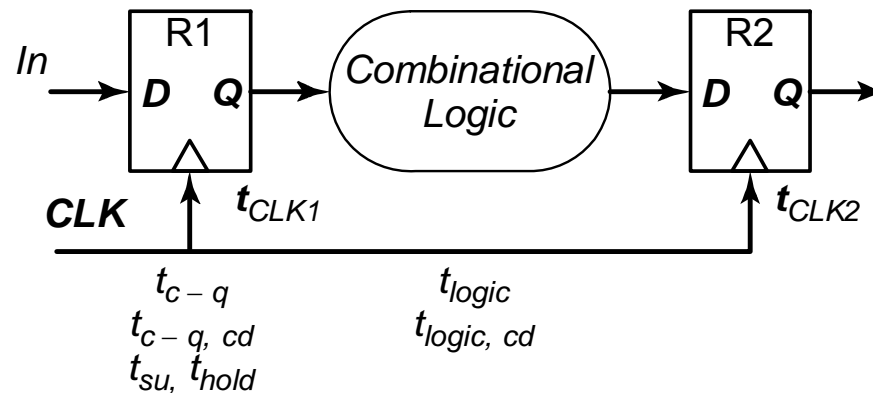


Hold time constraint:

$$t_{(c-q, cd)} + t_{(logic, cd)} > t_{hold} + \delta$$

 
Example: Effect of Clock Skew

- ❑ Assume $t_{c2Q} = 350\text{ps}$ and $T_{\text{hold}} = 100\text{ps}$. What happens?
- ❑ Assume $t_{c2Q} = 150\text{ps}$ and $T_{\text{hold}} = 100\text{ps}$. What happens?




Clock Distribution Design: Balanced-Tree

 - ❑ True H-tree clock routing is often not possible.
- ❑ In this case, the clock distribution designer balances the length of each clock branch to reduce skew as much as possible.




Clock Distribution Design: Mesh Clock

 - ❑ Mesh clock distribution is used in some high end processor
- ❑ They often provide less clock skew
- ❑ They often consume some wiring resources
- ❑ They use a lot of power to drive all that metal load capacitance




Clock Distribution Design: Hybrid Clock

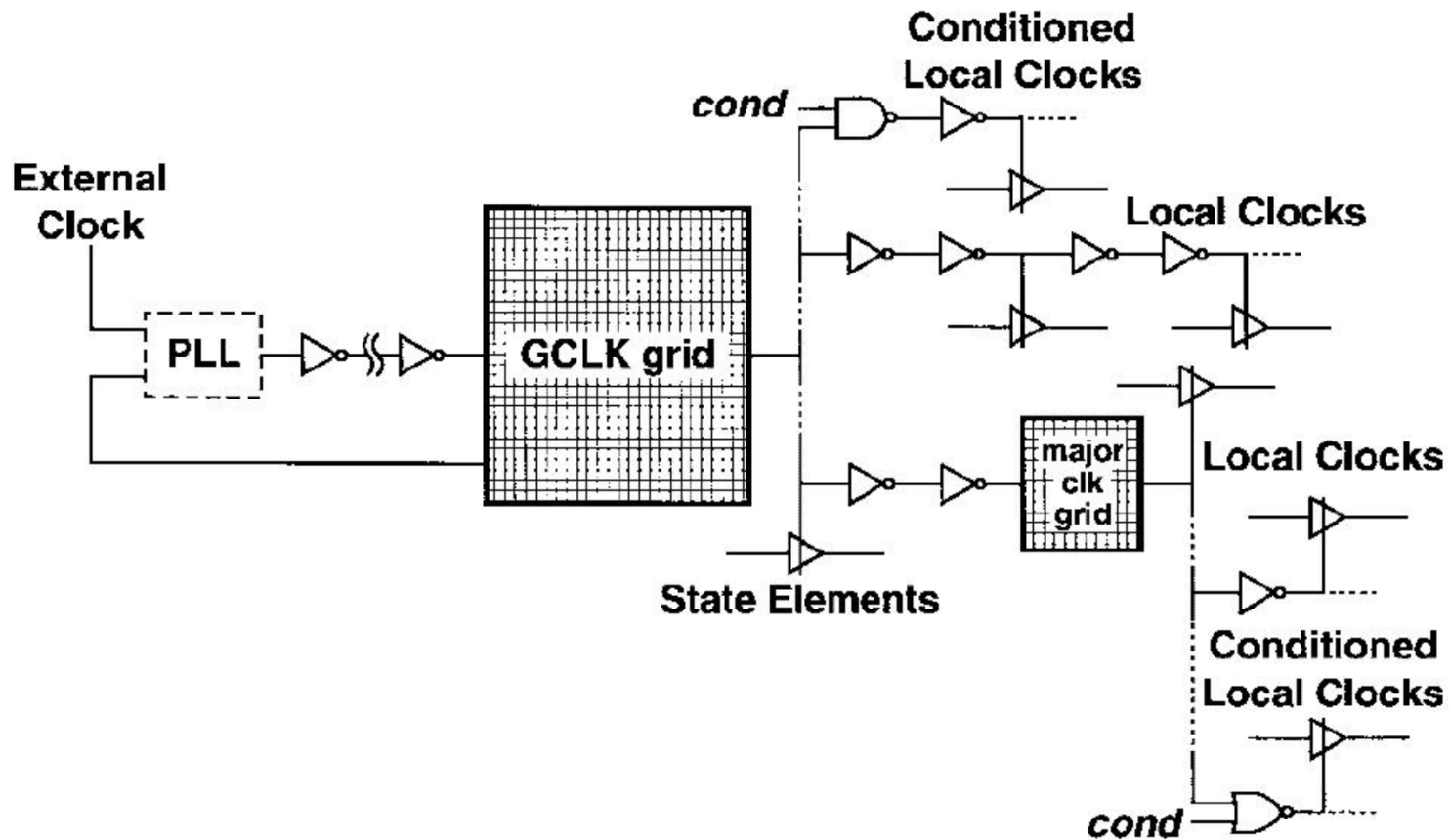


Clock Hierarchy for the Alpha 21264 Processor

Flip-Flop versus Latch-Based Clocking

Flip flop Clocking

 


Latch-Based Clocking (Time Borrowing)

 

 Example: Time (Slack) Borrowing

- Assume $t_{c2Q} = T_{su} = 0$. How fast is this path?



- Assume $t_{c2Q} = T_{su} = 0$. How fast is this path?

