

ECE520 – VLSI Design

Lecture 19: Clock Distributions - PLL

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Wednesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Review of Last Lecture

Timing Issues

- **Critical Path**
- **False Path**
- **Clock Skew**
- **Clock Jitter**

Today's Lecture

□ **Clock Distribution Network**


- **Clock generation (PLLs)**
- **Clock distribution**
- **Clock gaters**

Physical Clock

- ❑ **Distributing a single clock across a chip is challenging**
- ❑ **Distributing more than one clock signal is almost impossible**
- ❑ **Most systems distribute a single GLOBAL CLOCK even if the system needs multiple logical clocks**
- ❑ **Local clock gates located close to the clocked elements produce the actual physical clocks and drive the clock to the elements along short wires**
- ❑ **Clock gates are:**
 - **Buffers**
 - **AND gates for clock gating**
 - **Inverters to produce complementary clocks**
 - **Pulse generators for pulsed latches**

Clock System Architecture

- ❑ IC receives an external clock signal through the I/O pads
- ❑ The clock generation unit adjusts the phase and/or frequency of the global clock by either
 - Phase-locked loop (PLL)
 - or Delay-locked loop (DLL)
- ❑ The generated global clock is then distributed to points near all of the clocked elements via a clock distribution network
- ❑ Local gates receive this global clock and drive the physical clock signals along short wires to small groups of clocked elements

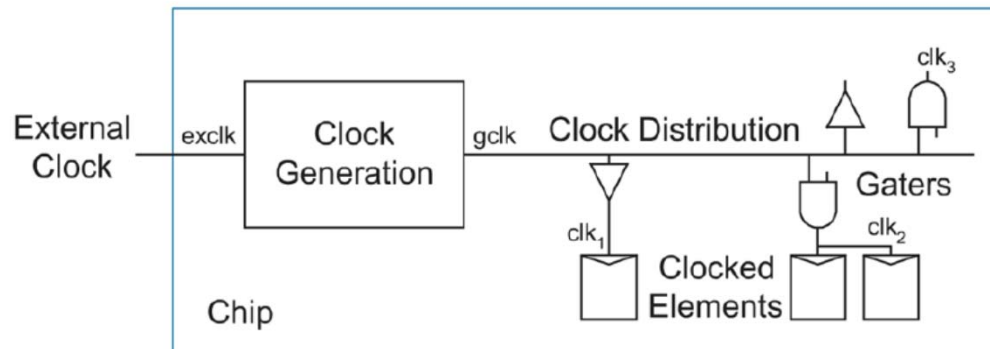


Global Clock Generation

- ❑ **Global clock generator receives an external clock signal and produces the global clock that is distributed across the die**
- ❑ **Simplest clock generator: a buffer to drive the large capacitance of the clock distribution network**
 - **Delay of input pads, buffers, distribution network, and gates cause a large skew between the external clock and the physical clocks received at the clocked elements**
 - **Clock skew varies with process and environment variations**
- ❑ **Because of clock skew, clocked elements on the chip are not synchronized with the external I/O signals**
 - **Guaranteeing signal arrival times (setup and hold time requirements) becomes difficult**


Global Clock Generation

 - ❑ PLLs are used to compensate for this delay from the input pads of the IC to the individual clocked elements for achieving synchronization with the outside world
- ❑ PLLs are also used for frequency multiplication to provide an on-chip clock at a higher frequency than the external clock
 - Ex: Pentium 4 uses a 100MHz external system clock that is multiplied to obtain a 3GHz core clock




Global Clock Generation

 - ❑ Chip1 sends a clock and data to chip2
- ❑ Chip2 sends data to chip1
- ❑ The data must be synchronized to the clock so that each chip can sample the data on the positive clock edge
- ❑ However, the internal clock in chip2 is delayed through the clock distribution network
- ❑ PLL adjusts the internal clock in chip2 to correct for this delay and keep the clock synchronized with the incoming data




Phase Locked Loop (PLL)

- ❑ PLL receives a reference clock and a feedback clock and produces an output clock
- ❑ The phase and frequency of the output clock is adjusted until the feedback clock is exactly aligned with the external reference clock
 - Eliminates the systematic clock skew caused by the clock distribution delay
- ❑ The feedback clock is tapped off one of the physical clock wires that also drives the registers
- ❑ The output clock is the signal sent to the clock distribution network

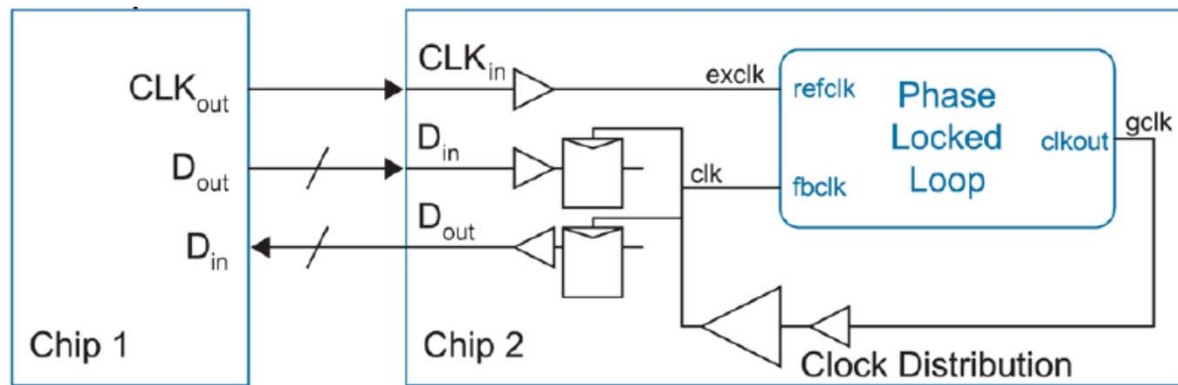

PLL Block Diagram

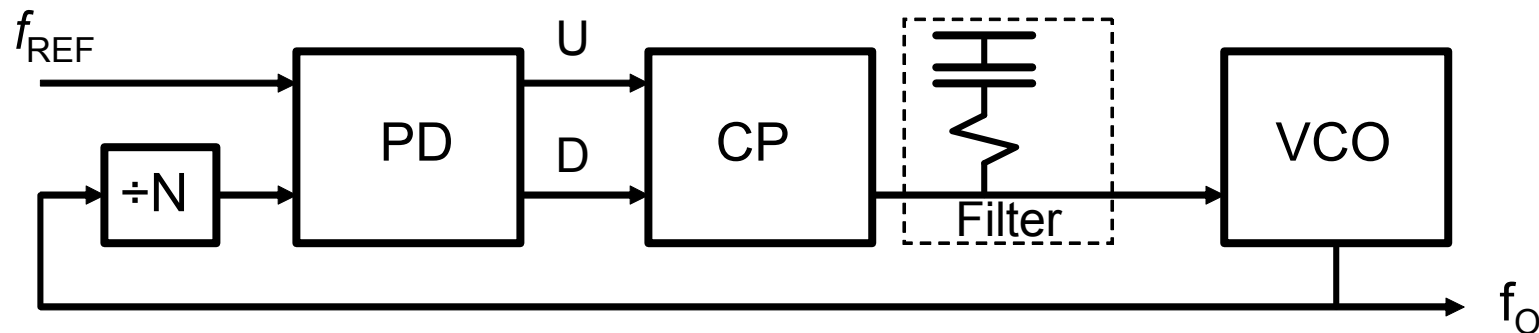- ❑ PLL is an analog circuit with the following functional composition
- ❑ Phase detector (PD) determines whether the feedback clock leads or lags the reference clock
- ❑ Charge pump (CD) is an analog circuit that converts Up (U) and Down (D) pulses into an analog voltage
- ❑ VCO generates a periodic signal with a frequency that is a liner function of the input control voltage




PLL Properties

□ Lock Range

- The range of input frequencies over which the loop can maintain functionality


□ Lock Time

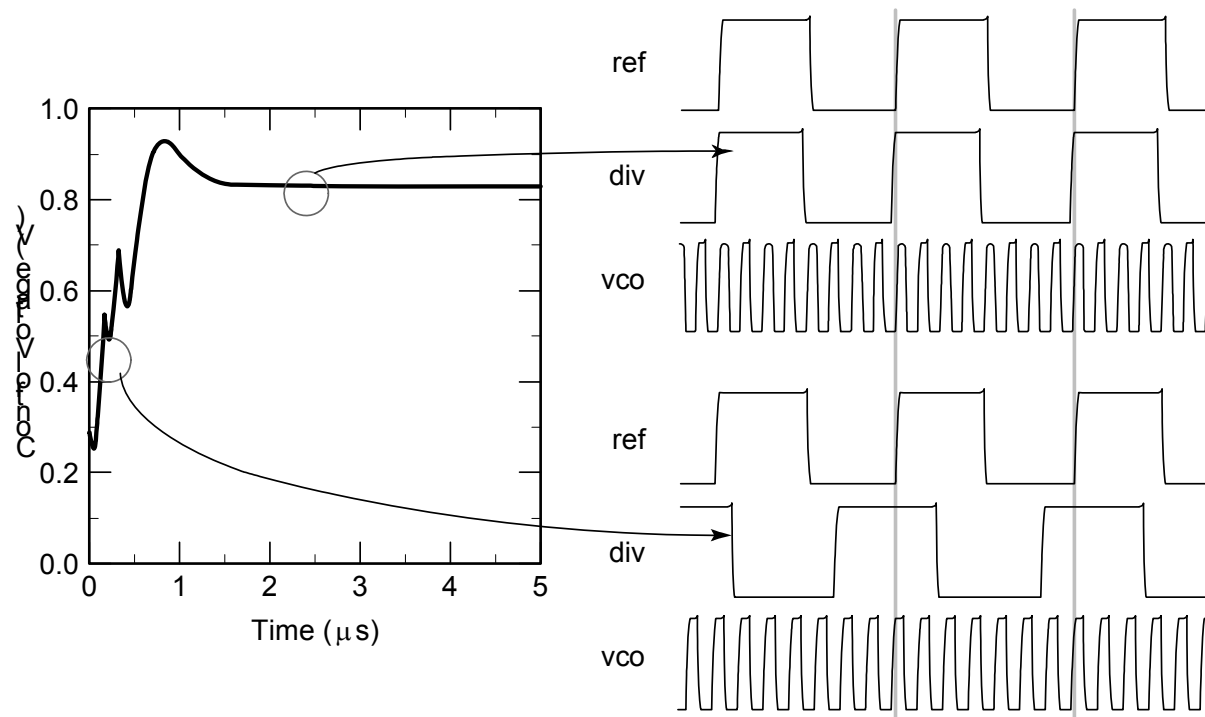- The time it takes for the PLL to lock onto a given input signal




Detailed PLL Structure

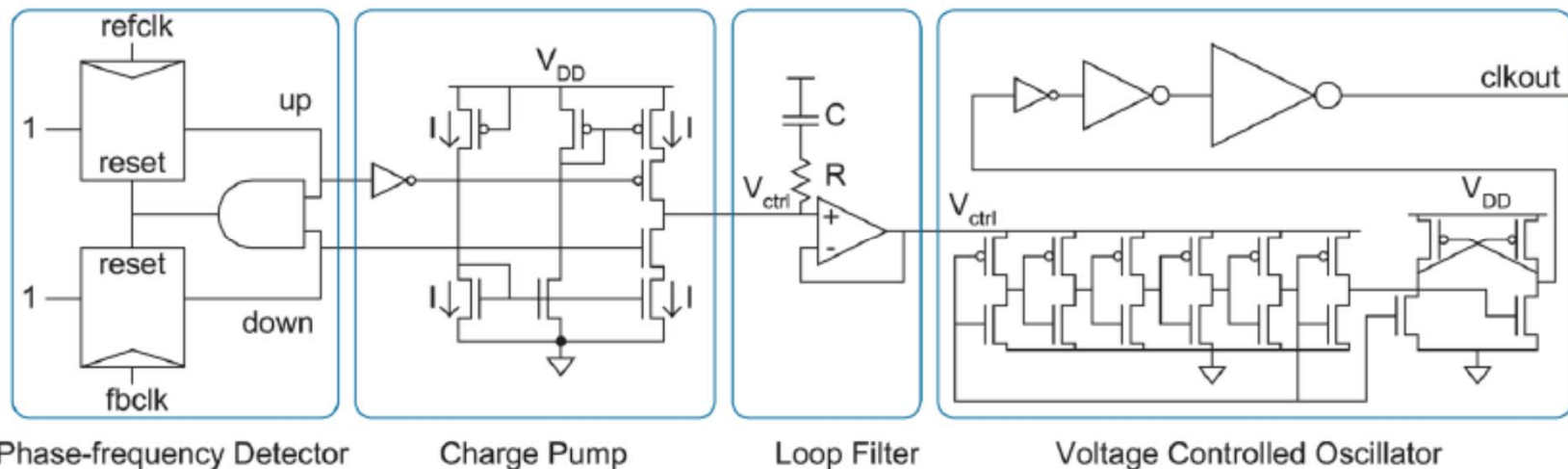- ❑ The phase detector consists of a pair of FFs with asynchronous reset that produces pulses to drive the frequency up or down depending upon which clock arrives first
- ❑ The charge pump is composed of a pair of current sources enabled by the up and down signals to adjust the voltage on V_{ctrl} until the feedback clock is aligned with the reference clock




Detailed PLL Structure

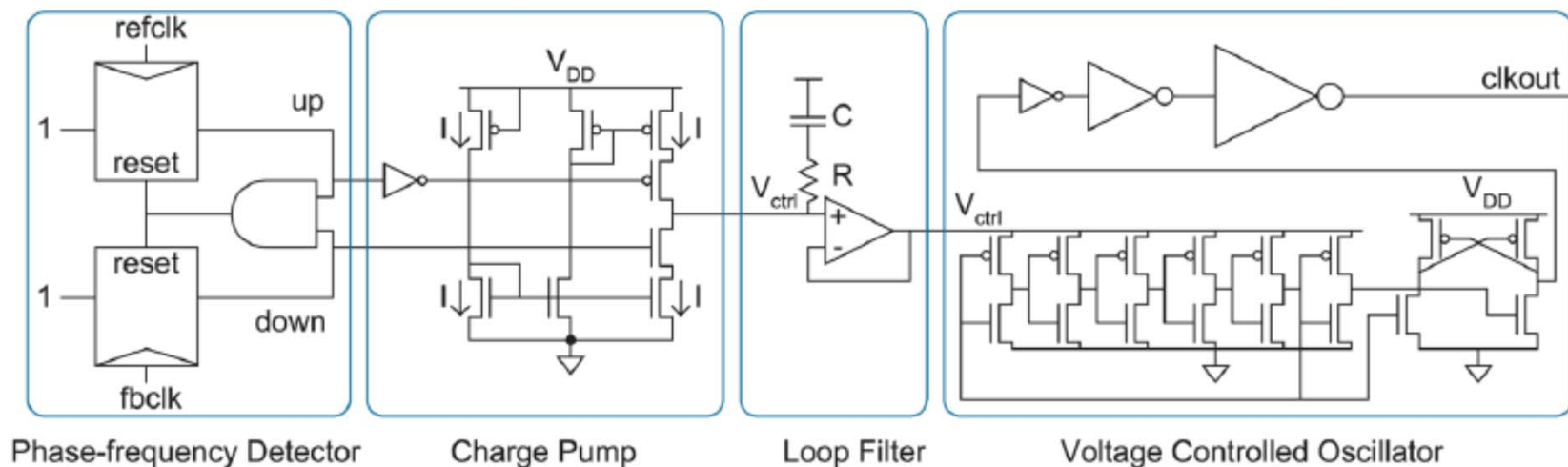- ❑ Voltage-controlled oscillator (VCO)
 - A ring oscillator
- ❑ The control voltage is adjusted until the oscillator produces an output clock of proper phase and desired frequency
- ❑ The control voltage is generated by a charge pump and RC filter



Detailed PLL Structure

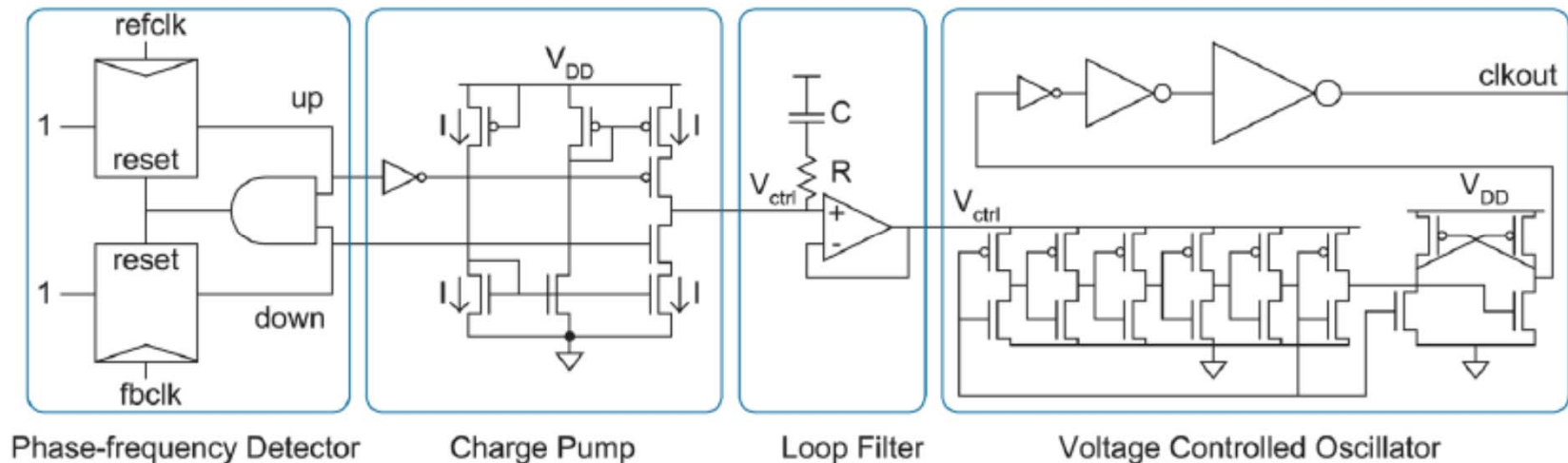- ❑ VCO is very sensitive to noise on V_{ctrl}
- ❑ Primary sources of jitter in PLLs
 - Power supply noise
 - Substrate coupling noise
- ❑ Guard rings should surround all the devices for reducing jitter



Cycle Time and Skew Trend




- ❑ **Much of CPU performance comes from higher clock frequency**
 - Clock frequency is enhanced faster than that can be attributed to technology scaling only
 - Skew budget shrinks together with the clock period
- ❑ **Wires are longer and thinner**
 - Higher resistance and capacitance
 - Longer RC delay
- ❑ **Clock loads are increasing**
 - More devices
 - More wire capacitance
- ❑ **Clock distribution delay and skew tend to **GO UP****
- ❑ **Systematic skew can be controlled by a good distribution network design**
- ❑ **Alternatively, random and drift skew and jitter budgets are becoming an increasing portion of the total cycle time**

Challenges

- ❑ **Reduce clock skew**
 - Careful clock distribution network design
 - Plenty of metal wiring resources
- ❑ **Characterize clock skew**
 - Only budget actual, not worst case skews
 - Difficult to guess
 - Local vs. global skew budgets
- ❑ **Tolerate clock skew**
 - Choose circuit structures less sensitive to skew

Global Clock Distribution Techniques

   - ❑ H-Tree (most used technique, less power consumption)
- ❑ Balanced tree (easier to implement)
- ❑ Mesh distribution (less skew, high power consumption)
- ❑ Hybrid (combined tree and mesh)




Local Clock Gaters

- ❑ Generate the local physical clock from the global clock signal**
- ❑ Outputs of clock gaters run short distances**
- ❑ Can be used to**
 - Adjust clock delay (skew management)**
 - Gate the clock**
 - Generate pulses**
 - Stretch the clock**
 - Generate non-overlapping clocks**
 - Double the clock frequency**
- ❑ Gaters can be an important source of clock skew due to random and drift parameter variations**

Local Clock Gaters Examples


Clock Buffer

 



Enabled, Qualified, or Gated Clock



Stretched Clocks

 


Nonoverlapping Clocks

  


Complementary Clock



Delayed Clocks

 

Pulsed Clocks

 

Clock Doubler

