

# ECE520 – VLSI Design

## Lecture 21: Memories

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Wednesday 2:00-3:00PM or by appointment*

*E-mail: [pzarkesh@unm.edu](mailto:pzarkesh@unm.edu)*

# *Review of Last Lecture*

---

## **Power Distribution Network**

- IR drop
- Switching noise
- Decoupling capacitor
- Electromigration

## **I/O Circuits**

- Output buffer
- Level shifters
- Schmitt trigger
- Tri-state outputs
- ESD protection

# *Today's Lecture*

---

Memory architectures

ROM

- NOR ROMs
- NAND ROMs

# *Types of VLSI Memories*

---

## Register files

- Fastest and largest--sub 200ps access times possible
- Readily implemented with multiple ports

## SRAM

- Next fastest--sub 1ns access times possible
- This includes cache memory--they are all SRAM based
- Volatile, but retains state as long as power is applied

## DRAM

- Quite slow > 50ns access times
- Volatile--state retained for ms and must be refreshed often

## ROM


- Mask programmable Read Only Memory

## Non-volatile memories

- Slow--50ns access times
- EPROM, EEPROM, Flash
- Emerging technologies: Ferroelectric, ferromagnetic...

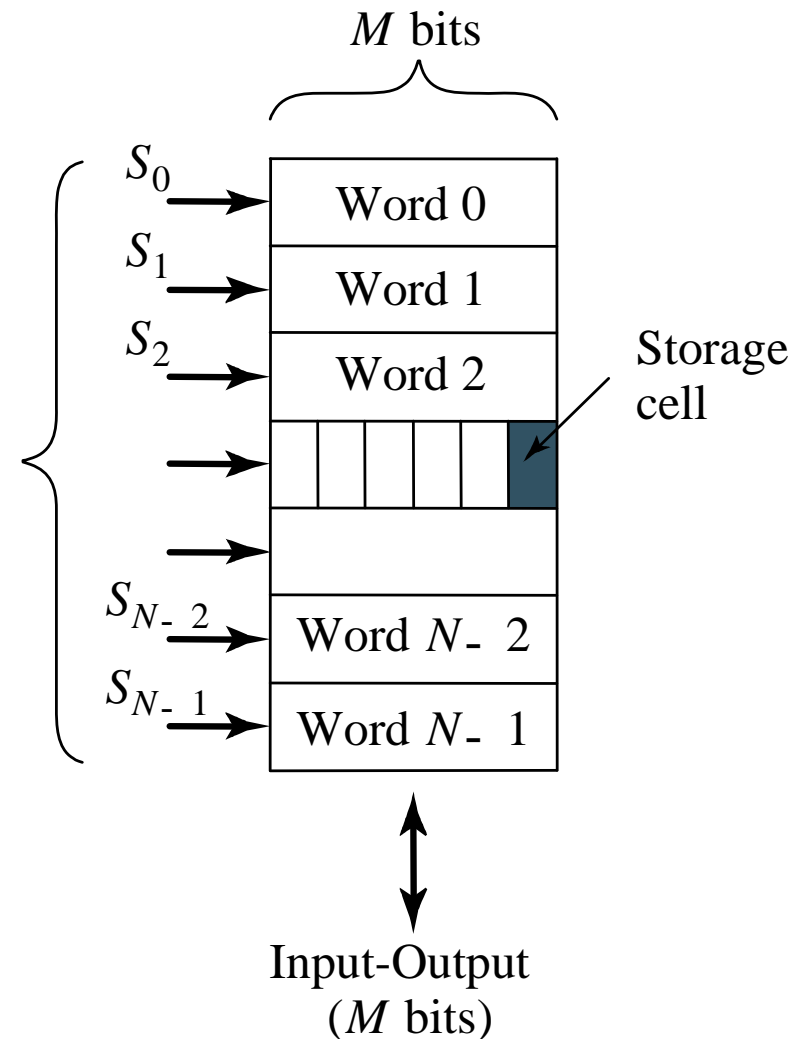
# A Generic Memory Architecture

- ❑ Words are horizontal and accessed by applying the appropriate word line
- ❑ Each cell in a row is a bit in the corresponding word
- ❑ This is not practical. Why?



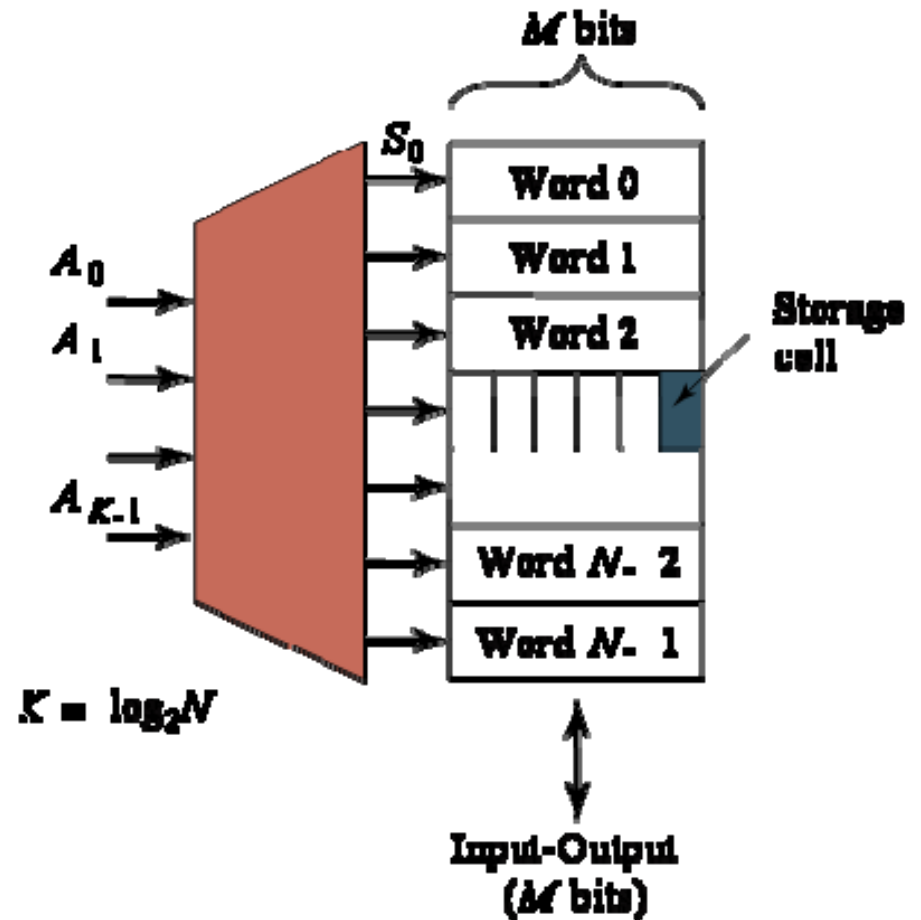
# Memory with Decoder

- ❑ Decoder reduces the number of select signal significantly
- ❑ In this case  $k = \log_2 N$
- ❑ Is this a reasonable architecture for 256 8-bit words?



 
# Real Memory Block Organization

- ❑ To improve Aspect Ratio, memory arrays are organized so that vertical and horizontal dimensions are the same order
- ❑ The row address enables one row of the memory for R/W, while the column address picks one particular word from the address



 
# Memory Banking (Hierarchical Architecture)

- ❑ The length of the local word and bit lines is kept within bounds, resulting faster access time
- ❑ Only the addressed block is activated resulting in a substantial power saving. Power dissipation is a major concern in very large memories.




# Example: Physical Memory Organization

 


- ❑ It is fastest to drive a wire from the center
- ❑ It is generally best to place the sense amplifiers and decoders at the center point of the word lines and bit lines
 
# Memory Read and Write Timing

- Memory timing parameters includes: *read-access time*, *write-access time*, *read-cycle time*, and *write-cycle time*



# Read Only Memory (ROM)

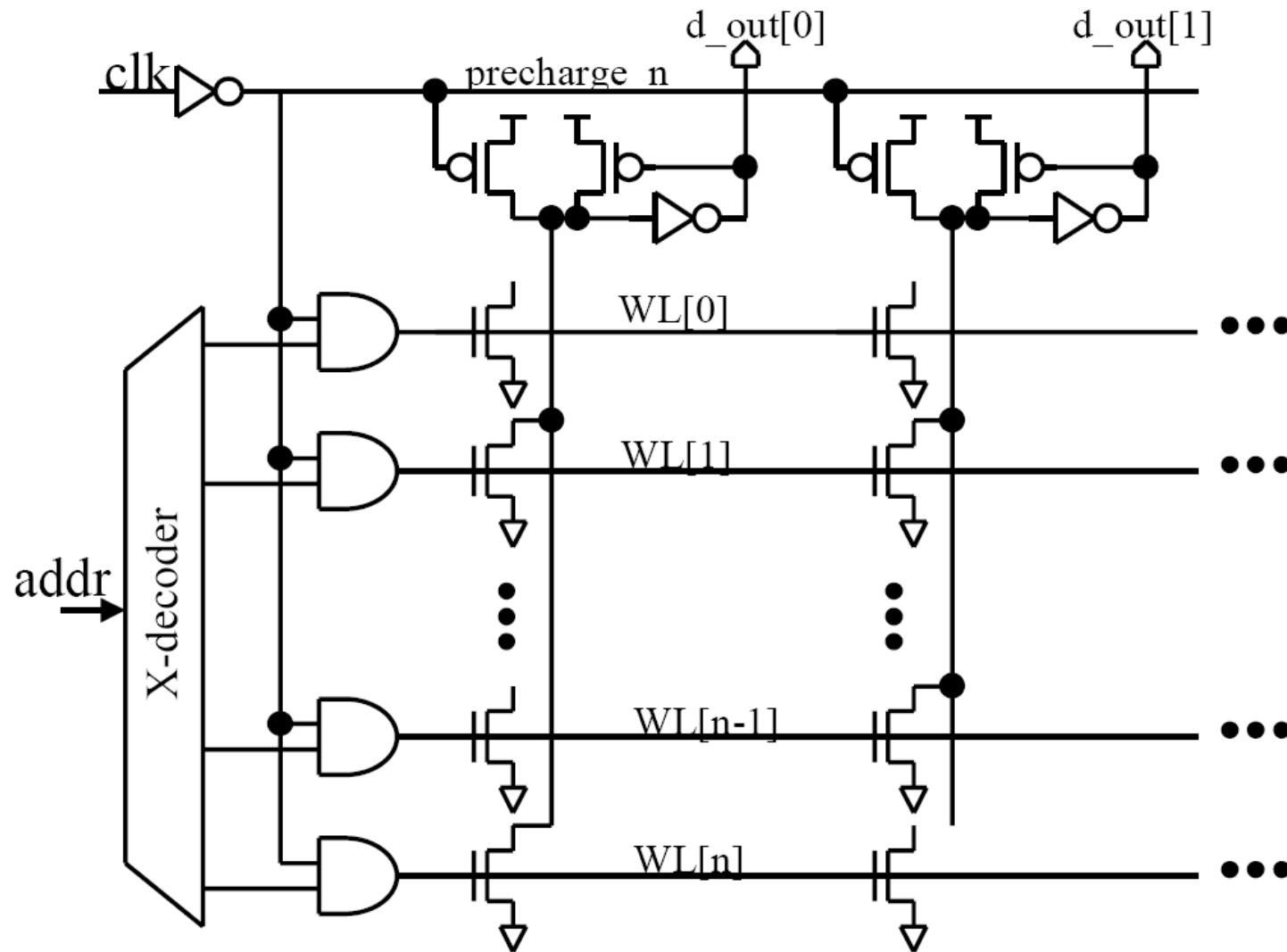

# ***Read Only Memory (ROM)***

---

---

## **□ ROM operation**


- Bit lines are pre-charged during clock high in this example
- Word lines are enabled during the low phase of the clock
- Note that the cells are simple domino circuits - just a simple pull-down
- PMOS keepers keep the bit lines from discharging due to leakage if the bit read is a logic one, i.e., the no pull down case

## **□ ROM programming**

- Logic 0 or 1 in a cell is programmed during manufacture by including a drain connection or not
- No drain connection, the cell cannot pull low
- Drain connection exists, when selected the cell will pull low
- Programming Schemes: 1) Diffusion programming (allows contact sharing), 2) Contact/via programming--generally not as small and 3) Vt implant programming

 
# ROM Programming Using Active Layer

- ❑ M1 is used for the bit lines
- ❑ Poly is used for the word lines
- ❑ Diffusion is either absent or present to form for pull-down or not
- ❑ Contacts shared between adjacent cells




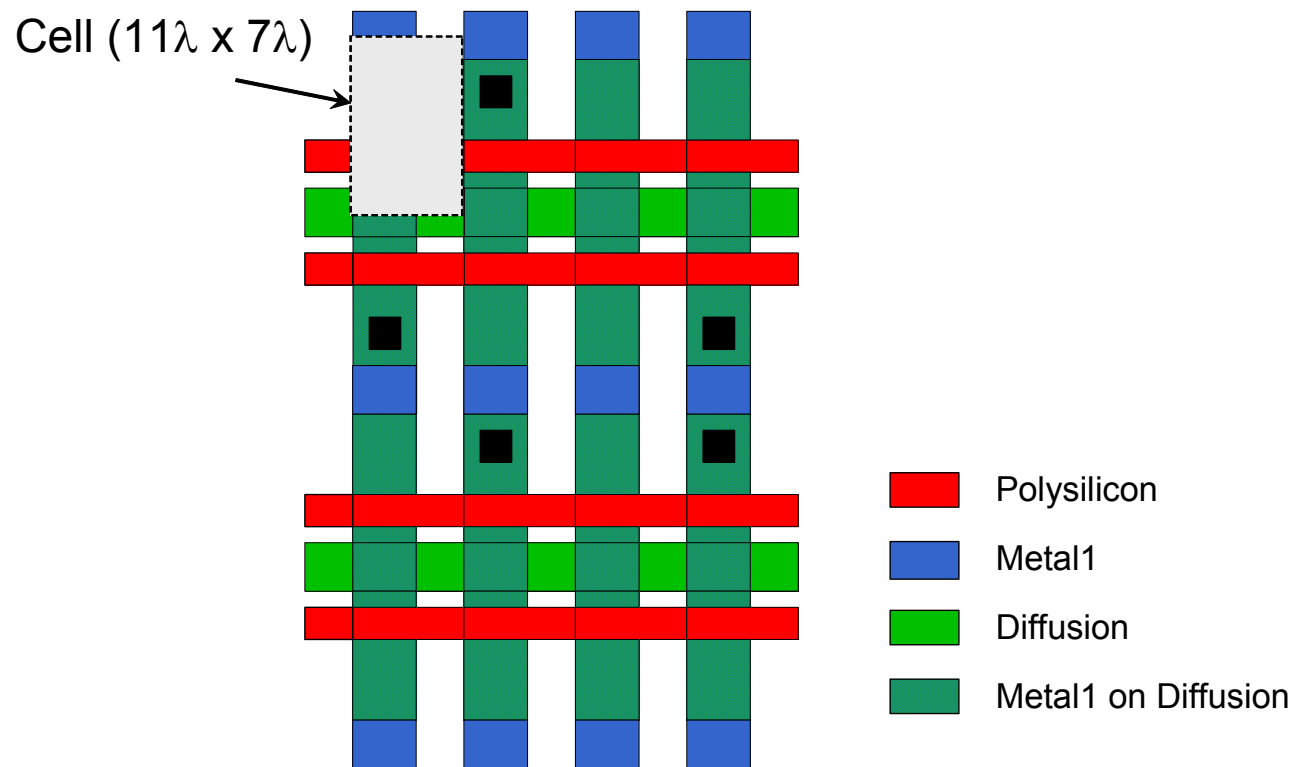
# ROM Programming Using Contacts

- ❑ M1 is used for the bit lines
- ❑ Poly is used for the word lines
- ❑ Contact is either absent or present to form for pull-down or not
- ❑ Contacts cannot be shared – results in larger layout area



  
# NOR versus NAND ROM

- ❑ NAND ROM doesn't need any connection to supply voltage, which results in smaller area
- ❑ NAND ROM operates in reverse-logic mode, i.e. all word lines are high by default except the selected row which is 0
- ❑ All transistors in the pull down chain must be on to produce 0
- ❑ If a transistor exists on the selected row it creates 1 (pull down will be off), otherwise it creates 0 (pull down is on)



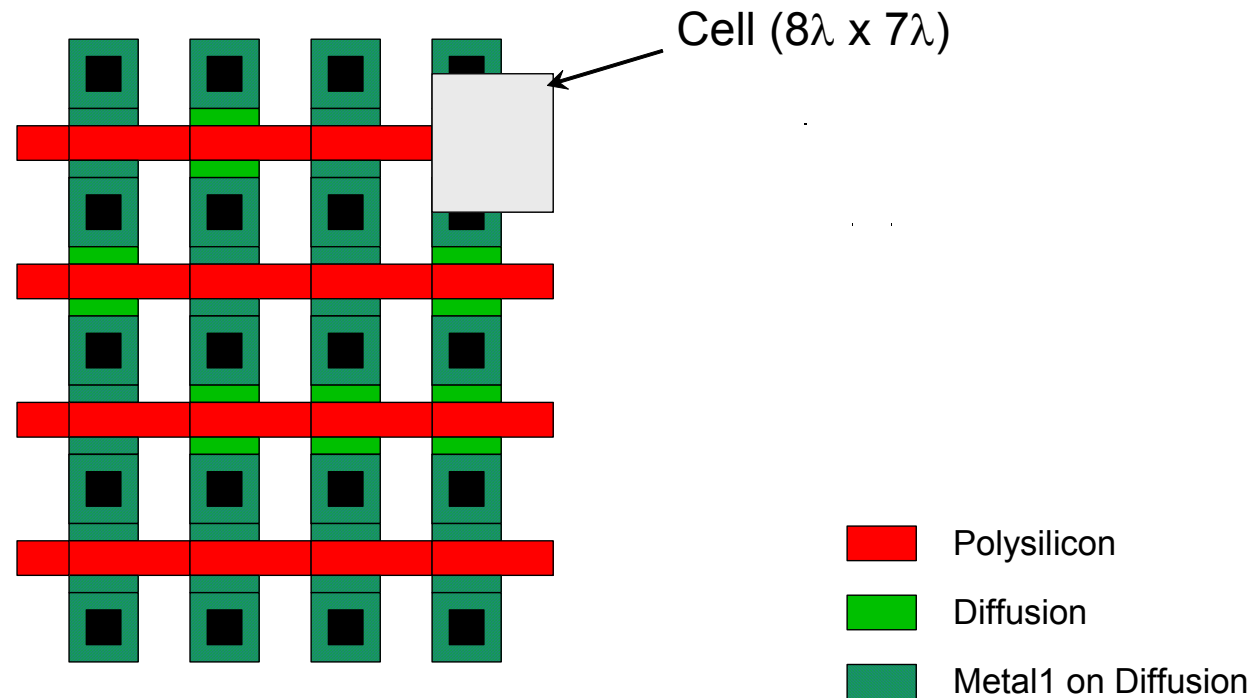
# NAND ROM Programming Using Metal 1

- ❑ M1 is used for the bit lines and to selectively short circuit the transistors
- ❑ Poly is used for the word lines


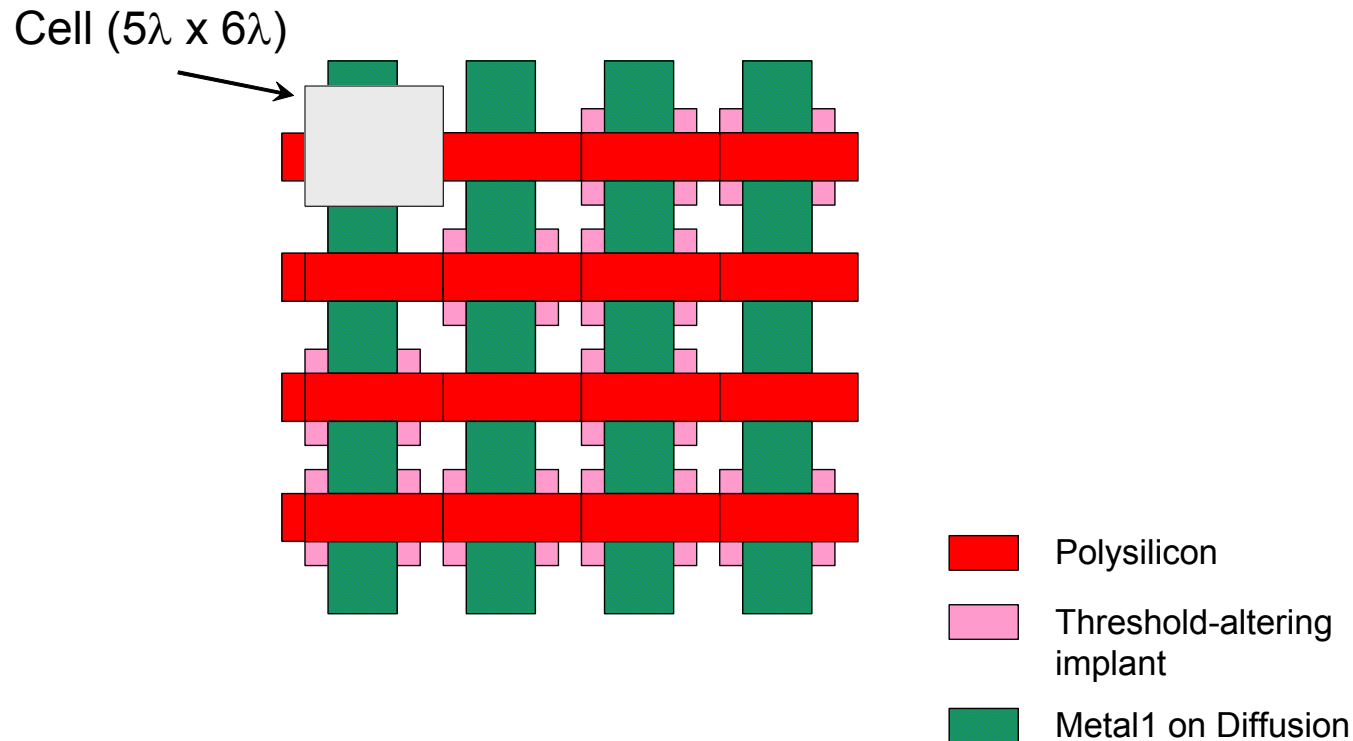
# NAND ROM Programming Using Implant

- ❑ Implant (n-type) can be used to selectively turns the devices into depletion mode transistor, which is always on, regardless of applied word line voltage
- ❑ This has even less layout area



# *Problems with NAND ROMs*

---

---

- ❑ **The improved density of NAND ROMs comes at a price:**
  - It is only useful for small memory arrays. why?
  - It results in a considerable performance loss. Why?