

ECE520 – VLSI Design

Lecture 5: Basic CMOS Inverter

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Wednesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Review of Last Lecture

- ❑ **Short Channel Effects**
 - Source-Drain resistance
 - Subthreshold conduction
 - Velocity saturation
 - Mobility degradation
 - Threshold voltage rolloff
 - DIBL effect
 - Punch through
 - Hot electron
 - Narrow channel effect

- ❑ **Device Scaling Issues**

Today's Lecture

- ❑ Overview of T-SPICE
- ❑ BASIC CMOS Inverter
 - Resistive load inverter
 - VTC curves
 - Power dissipation estimation
- ❑ Static Behavior of CMOS Inverter
 - Switching threshold
 - Noise margin
 - CMOS Voltage-Transfer Characteristic (VTC)
- ❑ CMOS Inverter Robustness
 - Device variations
 - V_{dd} scaling (minimum supply voltage)

Overview of TSPICE (input file)

* Test Circuit for VLSI Class

```
Vdd Vp gnd DC 5V
```

```
RL Vp Vout 10K
```

```
M1 Vout Vin gnd gnd CMOSN W=8um L=1.6um
```

```
Vin Vin gnd DC 5V
```


```
.DC Vin 0 5 0.05
```

```
.plot Vout
```

```
.include 'device_model.modlib'
```



```
.end
```

Overview of TSPICE (output waveform)

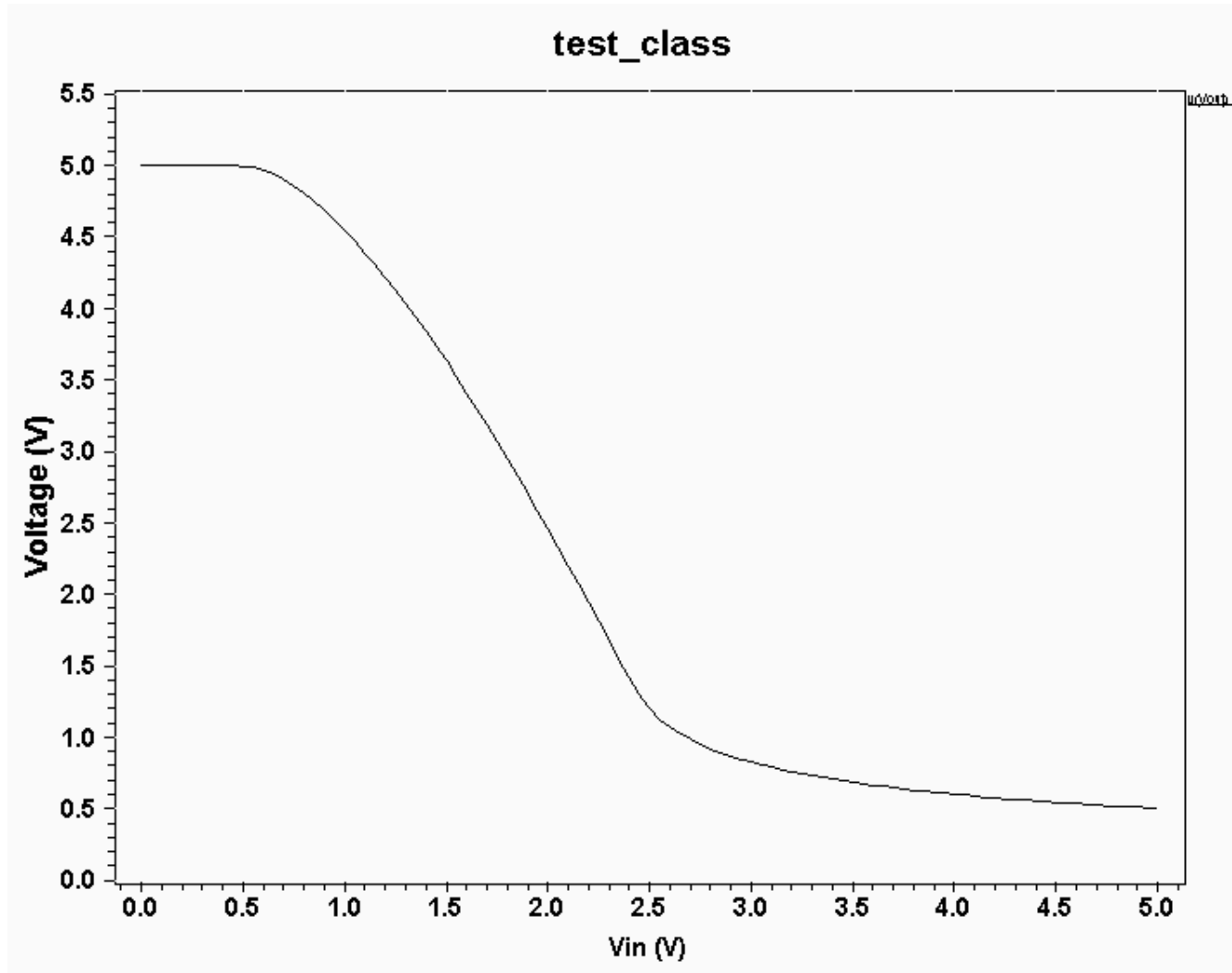


Resistive Load Inverter

  - A resistive load inverter consists of a pull down NMOS and a pull up resistor
 - Voltage Transfer Characteristic (VTC) is a function of transistor size and resistor value
 - A good inverter provide a fast transition in VTC curve




Resistive Load Inverter Design

 - ❑ The pull up resistor must be calculated to maintain a specific low level voltage (V_{OL}) at the output
- ❑ Example:
 - $K'_n = 100 \mu\text{A}/\text{V}^2$
 - $V_{T0} = 0.7 \text{ V}$
 - $V_{OL} = 0.25 \text{ V}$
- ❑ How to compute R_L as a function of (W/L) ?
- ❑ How much is R_L for $(W/L)=5$?




Power in Resistive Load Inverter

 - ❑ When the output is high, there is no current drawn from V_{DD}
- ❑ When the output is low, a DC current is drawn from V_{DD}
- ❑ Assuming probability is 50% for logic high and logic low
- ❑ How to compute Power in the previous example?




- ❑ How much is the power for a design with 100K similar resistive load logic gate?

Review of Resistive Load Inverter

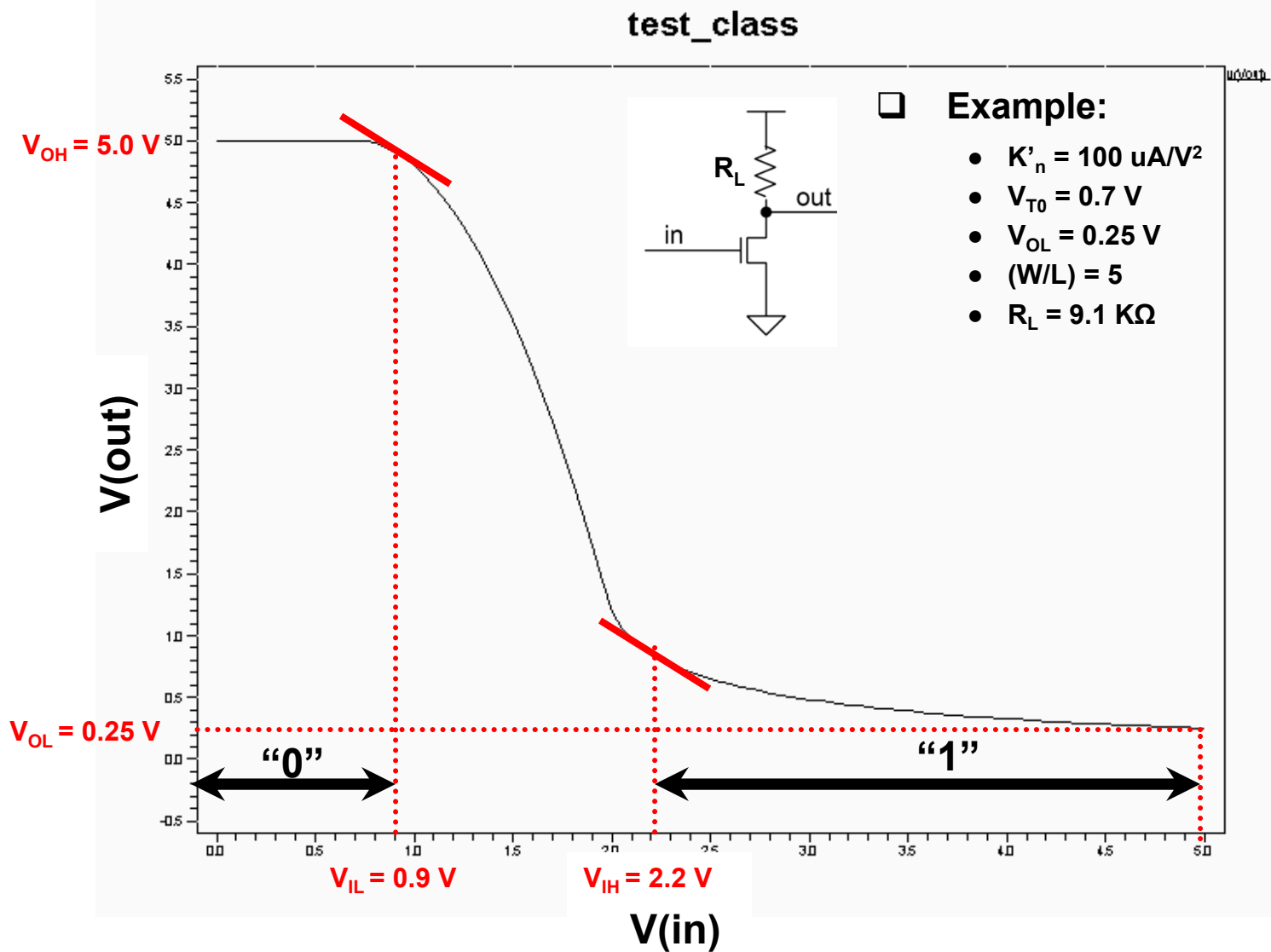


Noise Margin

 

□ Noise Margin

$$NM_H = V_{OH} - V_{IH}$$


$$NM_L = V_{IL} - V_{OL}$$

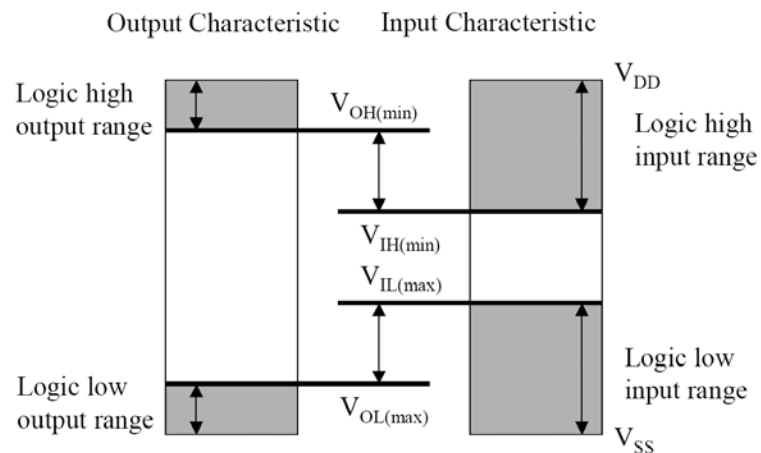

□ It is better to have:

- $V_{OH} = V_{DD}$
- $V_{OL} = V_{SS}$
- Large NM_H
- Large NM_L

Switching Threshold Voltage

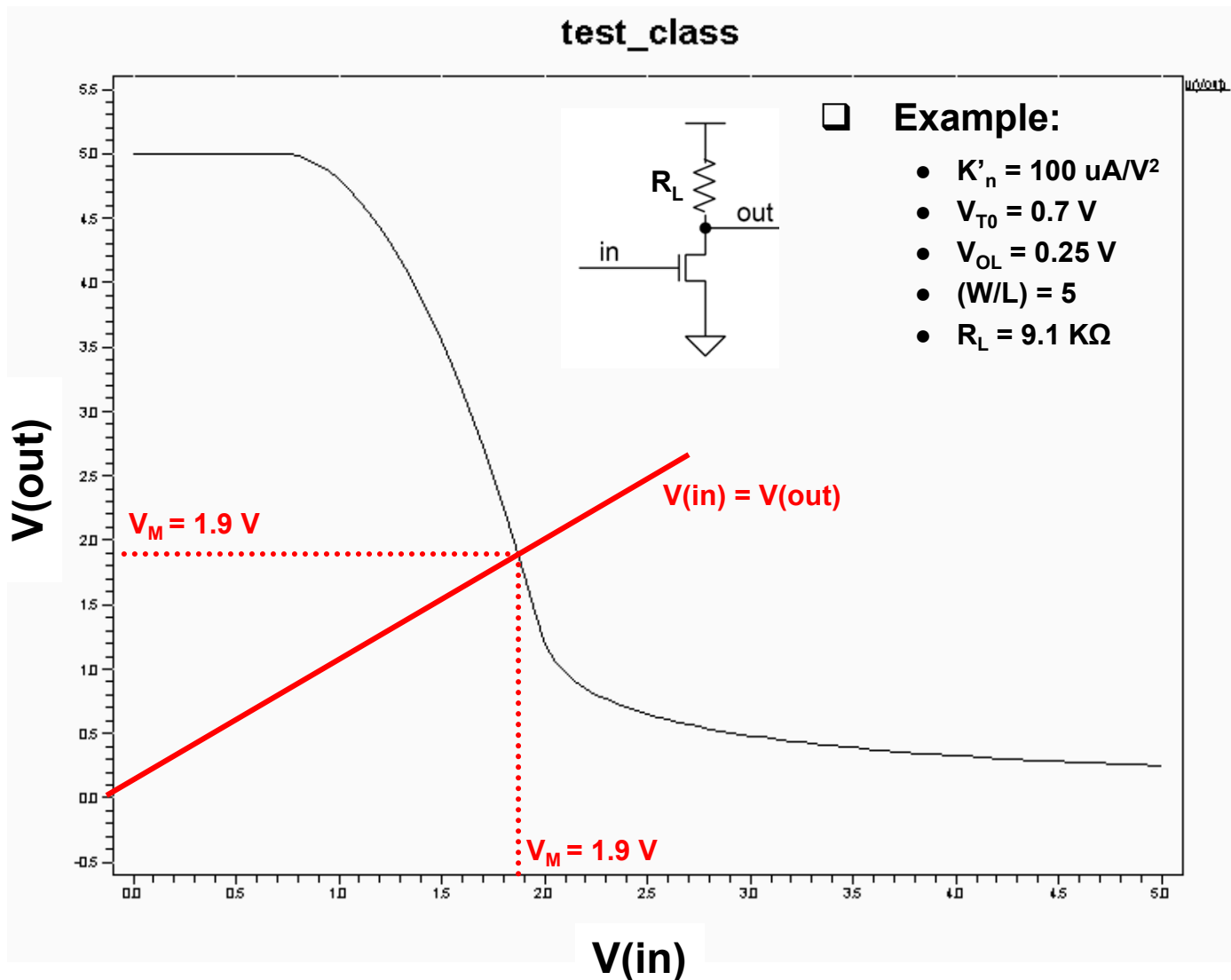

Switching Threshold Voltage Calculation

- How to compute V_M
 - Connect output to the input pin
 - Find out MOS operating region
 - Write the equations for current
 - Calculate V_M

- Example:
 - V_M in resistive load inverter


Noise Margin Estimation

□ How to compute Noise Margin

- Usually it is harder to compute the exact value of NM
- Use approximation (gain factor)
- Determine gain at V_M
- Extrapolate V_{IL} and V_{IH}
- V_{OL} and V_{OH} are easy to compute


□ Example:

 - NM_L and NM_H in resistive load inverter




NMOS Inverter

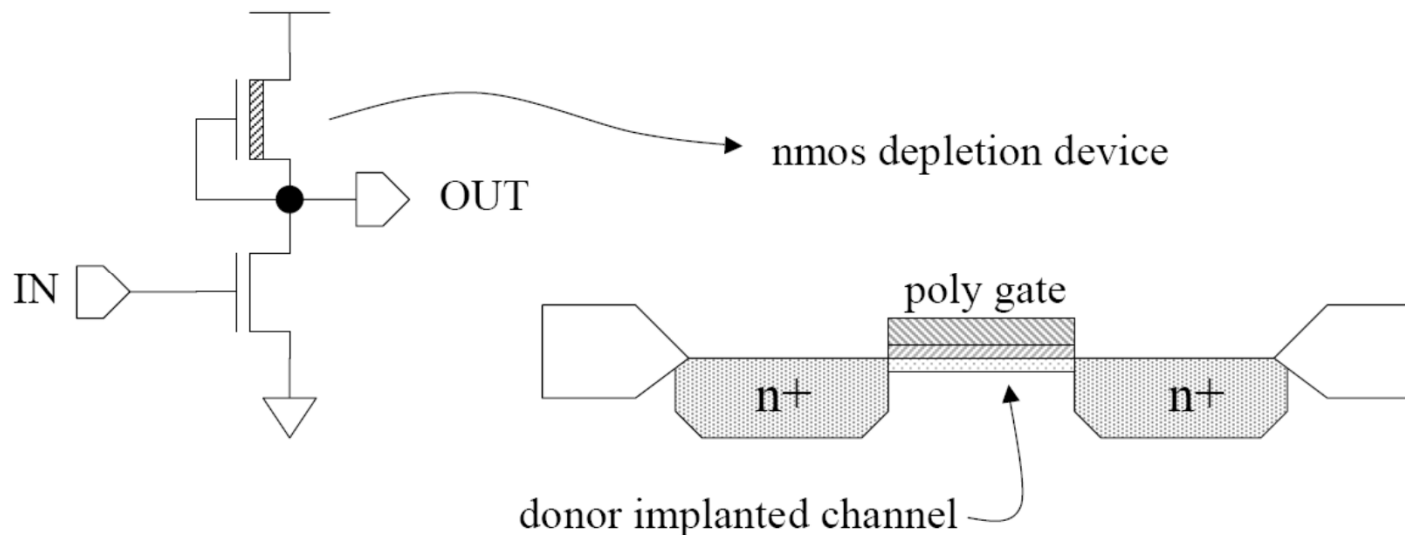- ❑ Large pull up resistor was a problem for resistive load inverter
- ❑ Depletion mode NMOS was an efficient way to implement a resistive pull up
 - Depletion device has an implant in the channel to give it a negative V_T and so it is always on — it was a very effective non-linear load device
 - This solved the area, but not the noise margin or power problems




Pseudo NMOS Inverter

 - ❑ Since a resistor is so big, it's better to use a single PMOS transistor that is always on:
 - PMOS pull up
 - NMOS pull down
- ❑ Why don't we use NMOS pull up?




CMOS Inverter

 - ❑ CMOS inverter is comprised of
 - PMOS pull up
 - NMOS pull down
- ❑ Advantages
 - No direct path from V_{DD} to GND (zero static power - except for leakage)
 - Better noise margin (Rail-to-rail output swing)
 - Ratio-less logic (output level not depend on gate size)
 - Always finite resistance to V_{DD} or GND
 - Very high input impedance




Switching model of CMOS Inverter

 - ❑ Treat each transistor as either on or off
- ❑ Each transistor has an on resistance
 - This isn't a bad model as long as the input transition is quite a bit faster than the output transition and it's very intuitive
- ❑ Delay of the gate depends of the effective transistor resistant and load capacitance



CMOS Inverter VTC

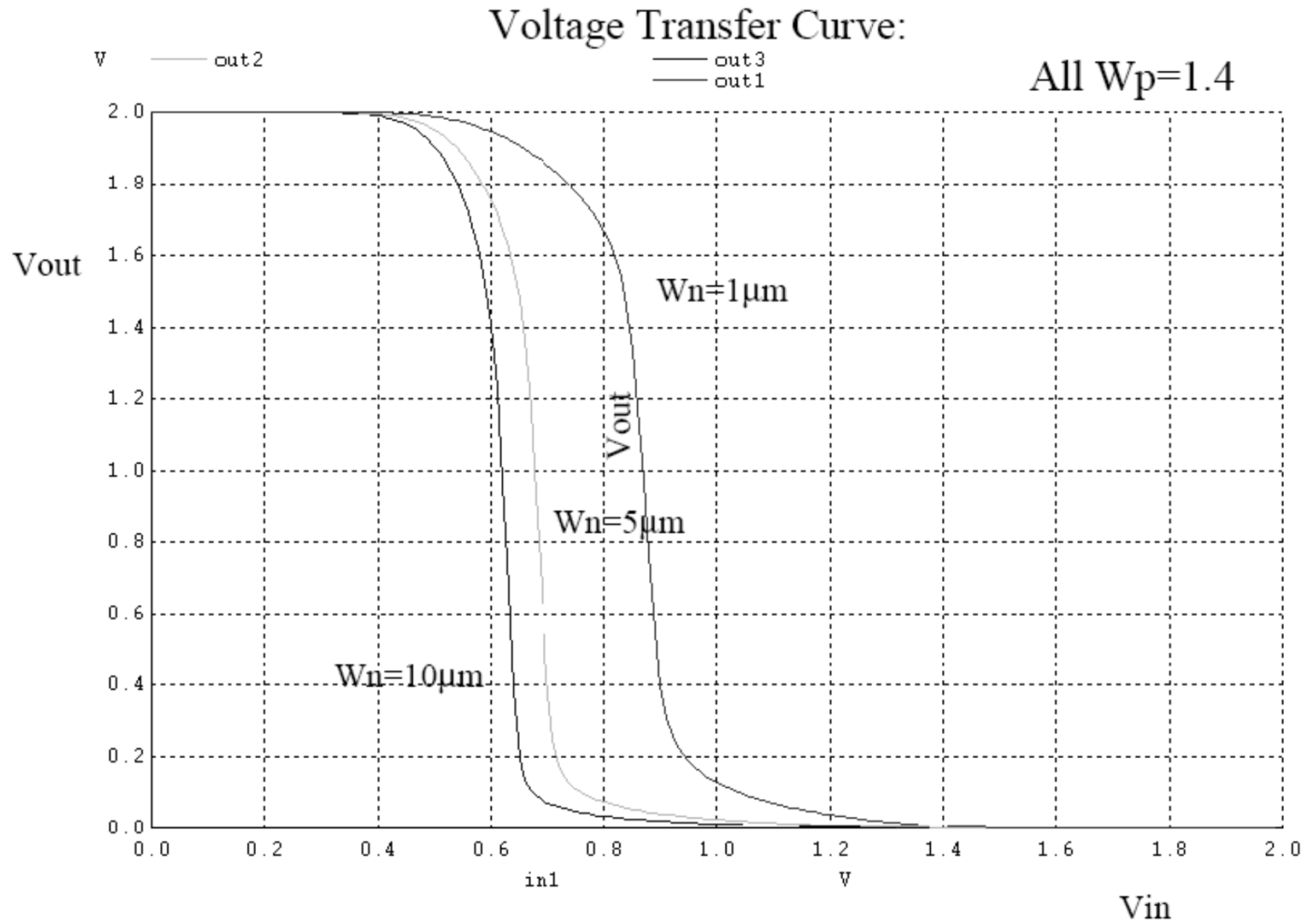

CMOS Inverter Switching Threshold

□ How to compute V_M in CMOS logic gate?

- Use the previous method to compute V_M
- Assume velocity saturation model


$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2}\right) + r\left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2}\right)}{1 + r} \quad \text{with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$

- Assume long channel model

$$V_M = \frac{\sqrt{\frac{k_p}{k_n}} V_{DD} + V_t \left(1 - \sqrt{\frac{k_p}{k_n}}\right)}{\left(1 + \sqrt{\frac{k_p}{k_n}}\right)}$$

CMOS Inverter Noise Margin

 - How to compute noise margin in CMOS logic gate?
 - Use the previous method to approximate Noise Margin



$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$


where

$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$

$$\approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

Design of CMOS Inverter

 
- ❑ For typical CMOS processes, $\mu_n = 2$ to 3 times μ_p
 - To get maximum noise margin we can make $W_p = 2.5W_n$
 - We don't actually implement this ideal case...
- ❑ Switching threshold voltage is not sensitive to (W_p/W_n) ratio
 - This means NM's are not seriously compromised by (w_p/w_n) ratios not equal to 1





What (W_p/W_n) Ratio to Use?

- ❑ We really want the best speed/power ratio
- ❑ At $W_p = 2.5 W_n$ the rise and fall times for the gate (assuming that they are equal at the input) will be equal
- ❑ Each gate is a load for a preceding gate
- ❑ As we widen the PMOS we slow down the previous gate
 - Every increment of width adds C
 - C is important term in power (the one we can control!)
- ❑ It turns out that it's best to use a ratio of about 1.5 rather than 2.5-3 that would give us equal rise and fall times
- ❑ In this case, NMOS are faster and PMOS slower, but the faster falling input helps make up for the slower rising output and the overall C

Robustness of CMOS Inverter

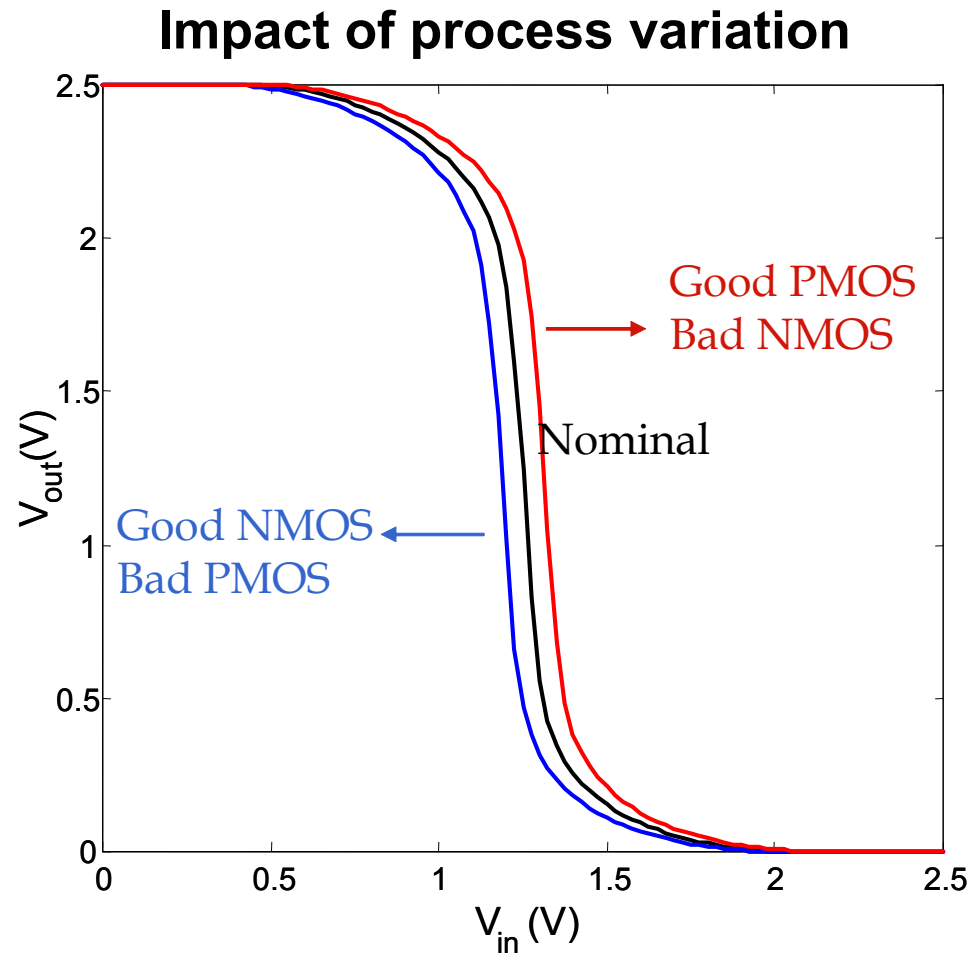

Minimum Supply Voltage

  

Minimum Supply Voltage

- ❑ Once V_{DD} drops below threshold voltage, the transistors operate in the subthreshold region.
- ❑ Using equation for subthreshold region we can prove:

$$g = -\left(\frac{1}{n}\right)\left(e^{V_{DD}/2\phi_T} - 1\right)$$