

ECE 523/421 - Analog Electronics
University of New Mexico
Solutions Homework 4

Problem 6.11

Show that for a transistor with α close to unity, if α changes by a small per-unit amount ($\Delta\alpha/\alpha$), the corresponding per-unit change in β is given approximately by

$$\frac{\Delta\beta}{\beta} \cong \beta \left(\frac{\Delta\alpha}{\alpha} \right)$$

Now, for a transistor whose nominal β is 100, find the percentage change in its α value corresponding to a drop in its β of 10%.

The relationship between α and β is

$$\begin{aligned}\beta &= \frac{\alpha}{1 - \alpha} \\ \alpha &\rightarrow \alpha + \Delta\alpha \\ \beta &\rightarrow \beta + \Delta\beta \\ \beta + \Delta\beta &= \frac{\alpha + \Delta\alpha}{1 - \alpha - \Delta\alpha}\end{aligned}$$

Subtracting $\beta + \Delta\beta$, β we obtain $\Delta\beta$

$$\begin{aligned}\Delta\beta &= \frac{\alpha + \Delta\alpha}{1 - \alpha - \Delta\alpha} - \frac{\alpha}{1 - \alpha} \\ \Delta\beta &= \frac{\Delta\alpha}{(1 - \alpha - \Delta\alpha)(1 - \alpha)}\end{aligned}$$

Dividing this by β

$$\frac{\Delta\beta}{\beta} = \left(\frac{1}{1 - \alpha - \Delta\alpha} \right) \left(\frac{\Delta\alpha}{\alpha} \right)$$

For $\Delta\alpha \ll 1$ The first part is approximately β


$$\frac{\Delta\beta}{\beta} \cong \beta \left(\frac{\Delta\alpha}{\alpha} \right)$$

To a drop in its β of 10% and β is 100 using the equation,

$$\left(\frac{\Delta\alpha}{\alpha} \right) \cong \frac{-10\%}{100} = -0.1$$

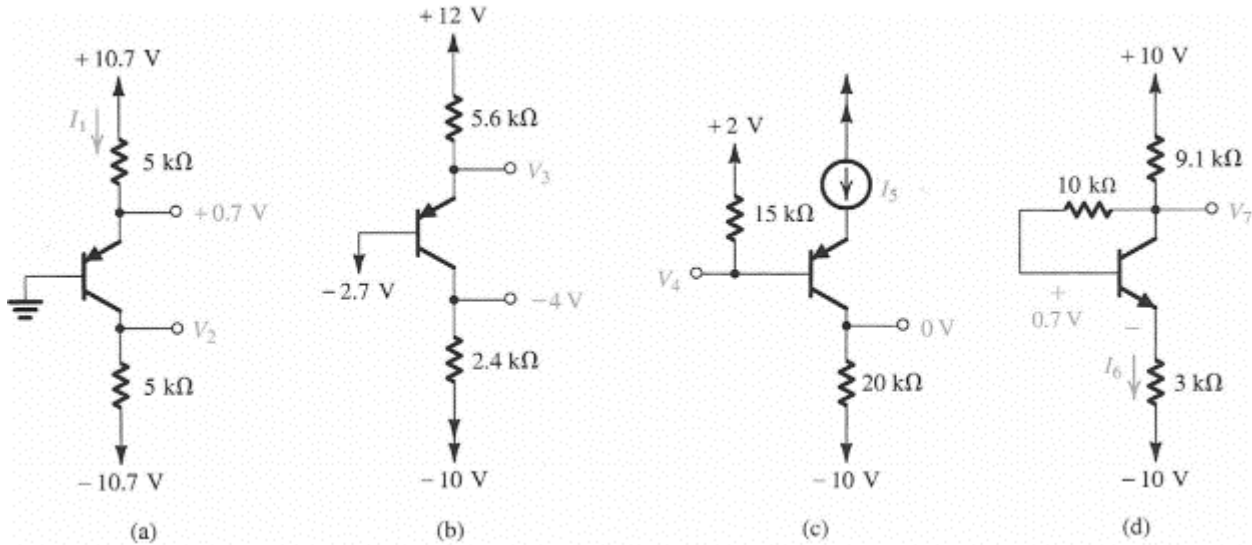Problem 6.28

For the circuits in Fig. P6.28, assume that the transistors have very large β . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.



- For circuit a

$$I_1 = \frac{10.7 - 0.7}{5\text{ k}\Omega} = 2\text{ mA}$$

$$I_1 = 2\text{ mA}$$

$$I_1 = I_C$$

$$V_2 - (-10.7) = 2\text{ mA} \times 5\text{ k}\Omega$$

$$V_2 = -0.7\text{ V}$$

- For circuit b

$$I_C = \frac{-4 - (-10)}{2.4\text{ k}\Omega} = 2.5\text{ mA}$$

$$I_E = \frac{I_C}{\alpha} \cong 2.5\text{ mA}$$

$$\frac{12 - V_3}{5.6\text{ k}\Omega} = 2.5\text{ mA}$$

$$V_3 = -2\text{ V}$$

- For circuit c

Due to I_B is approximately equal to 0

$$V_4 \cong 2V$$

$$I_C = \frac{0 - (-10)}{20 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$I_5 = I_E = \frac{I_C}{\alpha} \cong 0.5 \text{ mA}$$

- For circuit d

Due to I_B is approximately equal to 0

$$V_7 = V_B$$

$$V_E = V_B - 0.7$$

$$I_6 = \frac{V_E - (-10)}{3 \text{ k}\Omega} = \frac{V_7 - 0.7 - (-10)}{3 \text{ k}\Omega}$$

$$I_6 = \frac{V_7 + 9.3}{3 \text{ k}\Omega}$$

Also due to I_B is approximately equal to 0

$$I_C = \frac{10 - V_7}{9.1 \text{ k}\Omega}$$

Since $\alpha \cong 1$

$$I_6 = I_E \cong \frac{I_C}{\alpha}$$


$$\frac{V_7 + 9.3}{3 \text{ k}\Omega} = \frac{10 - V_7}{9.1 \text{ k}\Omega}$$

$$V_7 = -4.5V$$

$$I_6 = 1.6 \text{ mA}$$

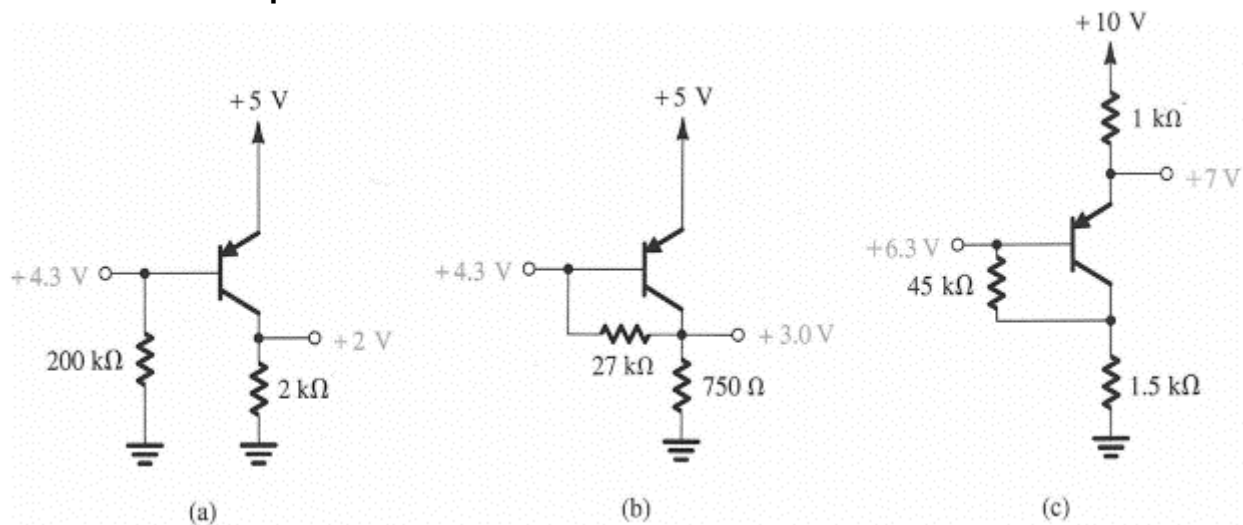Problem 6.29

Measurements on the circuits of Fig. P6.29 produce labeled voltages as indicated. Find the value of β for each transistor.



- For circuit a

Calculating base and collector currents

$$I_B = \frac{4.3}{200k\Omega} = 0.0215 \text{ mA}$$

$$I_C = \frac{2}{2k\Omega} = 1 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 46.5$$

- For circuit b

Calculating base and collector currents

$$I_B = \frac{4.3 - 3}{27k\Omega} = 0.048 \text{ mA}$$

$$I_x = \frac{3}{0.75k\Omega} = 4 \text{ mA}$$

$$I_C = 4 - 0.048 = 3.952 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 82.3$$

- For circuit c

Calculating base and emitter currents

$$I_E = \frac{10 - 7}{1k\Omega} = 3 \text{ mA}$$

$$V_C = 3 \text{ mA} \times 1.5k\Omega$$

$$V_C = 4.5V$$


$$I_B = \frac{6.3 - 4.5}{45k\Omega} = 0.04 \text{ mA}$$

$$I_C = I_E - I_B = 3 - 0.04 = 2.96 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 74$$

Problem 6.35

For each of the circuits shown in Fig. P6.35, find the emitter, base, and collector voltages and currents. Use $\beta=50$, but assume $|V_{BE}| = 0.8 \text{ V}$ independent of current level.

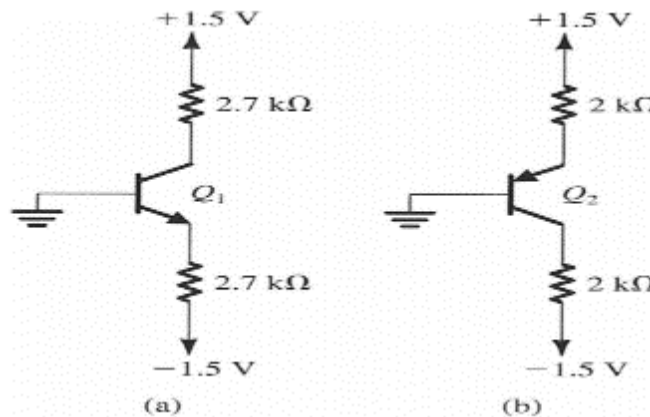

For circuit a


$$\begin{aligned}
 V_{BE} &= 0.8 \text{ V} \\
 V_E &= -0.8 \text{ V} \\
 I_E &= \frac{-0.8 - (-1.5)}{2.7 \text{ k}\Omega} = 0.26 \text{ mA} \\
 \alpha &= \frac{\beta}{\beta + 1} \\
 I_C &= \alpha I_E = 0.255 \text{ mA} \\
 V_C &= 1.5 - I_C \times 2.7 \\
 V_C &= 0.81 \text{ V} \\
 I_B &= I_E - I_C = 5 \mu\text{A}
 \end{aligned}$$

For circuit b

$$\begin{aligned}
 V_{BE} &= 0.8 \text{ V} \\
 V_E &= 0.8 \text{ V} \\
 I_E &= \frac{1.5 - 0.8}{2 \text{ k}\Omega} = 0.35 \text{ mA} \\
 \alpha &= \frac{\beta}{\beta + 1} \\
 I_C &= \alpha I_E = 0.343 \text{ mA} \\
 V_C &= -1.5 + I_C \times 2 \\
 V_C &= -0.81 \text{ V} \\
 I_B &= I_E - I_C = 7 \mu\text{A}
 \end{aligned}$$

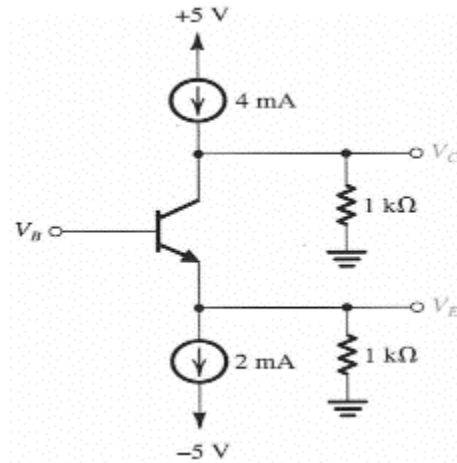Problem 6.54

For the transistor shown in Fig. P6.54, assume $\alpha \cong 1$ and $V_{BE} = 0.5 \text{ V}$ at the edge of conduction. What are the values of V_E and V_C for $V_B = 0 \text{ V}$? For what value of V_B does the transistor cut off? Saturate? In each case, what values of V_E and V_C result?



For $V_B = 0 \text{ V}$


$$\begin{aligned}
 V_E &= -0.7 \text{ V} \\
 I_X &= \frac{-0.7}{1 \text{ k}\Omega} = -0.7 \text{ mA} \\
 I &= 2 - 0.7 = 1.3 \text{ mA} \\
 I_{CC} &= 1.3 \text{ mA} \\
 I_C &= 4 - 1.3 = 2.7 \text{ mA} \\
 V_C &= 2.7 \text{ mA} \times 1 \text{ k}\Omega \\
 V_C &= 2.7 \text{ V}
 \end{aligned}$$

For cut off the two currents in the collector and emitter are zero

$$\begin{aligned}
 I_E &= I_C = 0 \\
 V_E &= 2 \text{ mA} \times 1 \text{ k}\Omega \\
 V_E &= -2 \text{ V} \\
 V_B &= V_E + 0.5 \\
 V_B &= -1.5 \text{ V} \\
 V_C &= 4 \text{ mA} \times 1 \text{ k}\Omega \\
 V_C &= 4 \text{ V}
 \end{aligned}$$

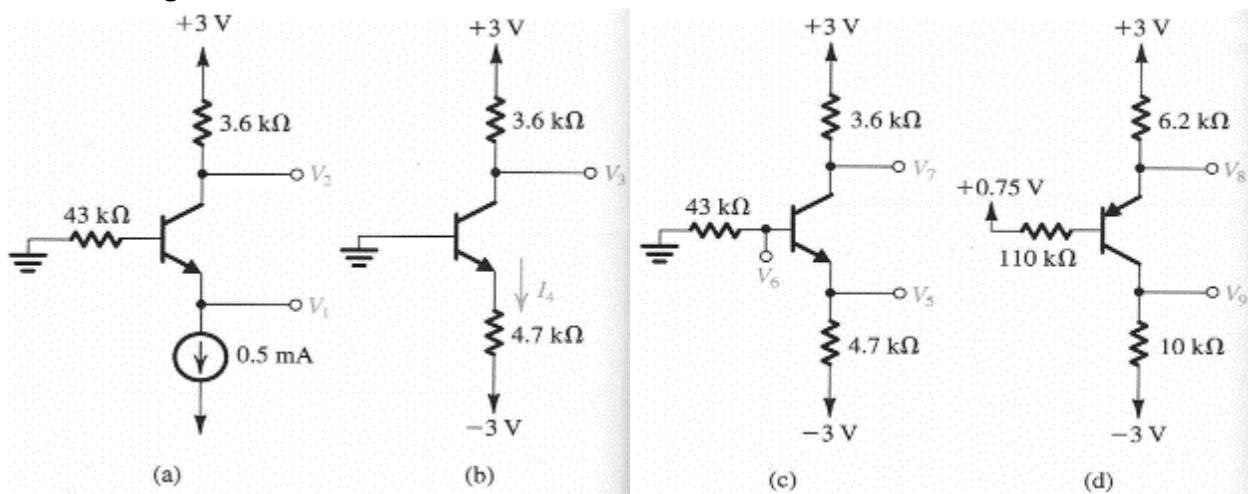Problem 6.62

Repeat the analysis of the circuits in Problem 6.61 using $\beta=100$. Find all the labeled node voltages and branch currents.



- For circuit a

$$\begin{aligned}
 I_E &= 0.5 \text{ mA} \\
 I_C &= \alpha I_E = 0.99 \times 0.5 \\
 I_C &= 495 \text{ } \mu\text{A} \\
 I_B &= \frac{I_E}{\beta + 1} = \frac{0.5}{101} \\
 I_B &= -0.005 \text{ mA} \\
 V_B &= I_B \times R_B = -0.005 \times 43 \\
 V_B &= -0.215 \text{ V} \\
 V_1 &= -0.215 - 0.7 \\
 V_1 &= -0.915 \text{ V} \\
 V_2 &= 3 - 0.495 \times 3.6 \\
 V_2 &= 1.218 \text{ V}
 \end{aligned}$$

- For circuit b

$$\begin{aligned}
 V_E &= -0.7 \text{ V} \\
 I_4 &= \frac{-0.7 - (-3)}{4.7 \text{ k}\Omega} \\
 I_E &= I_4 = 0.5 \text{ mA} \\
 I_B &= \frac{I_E}{\beta + 1} = \frac{0.5}{101} \\
 I_B &= 0.005 \text{ mA}
 \end{aligned}$$

$$I_C = \alpha I_E = 0.99 \times 0.5$$

$$I_C = 495 \text{ mA}$$

$$V_3 = 3 - 0.495 \times 3.6$$

$$V_3 = 1.218 \text{ V}$$

- For circuit c

Applying KVL

$$43I_B + 0.7 + 4.7I_E = 3$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E = 0.449 \text{ mA}$$

$$V_5 = -3 + 0.449 \times 4.7$$

$$V_5 = -0.9 \text{ V}$$

$$V_6 = -0.9 + 0.7$$

$$V_6 = -0.2 \text{ V}$$

$$I_C = \alpha I_E = 0.99 \times 0.449$$

$$I_C = 0.444 \text{ mA}$$

$$V_7 = 3 - 0.444 \times 3.6$$

$$V_7 = 1.4 \text{ V}$$

- For circuit d

Applying KVL

$$0.75 + 110I_B + 0.7 + 6.2I_E = 3$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E = 0.213 \text{ mA}$$

$$V_8 = 3 - 0.213 \times 6.2$$

$$V_8 = 1.7 \text{ V}$$

$$I_C = \alpha I_E = 0.99 \times 0.213$$

$$I_C = 0.21 \text{ mA}$$

$$V_7 = -3 + 0.21 \times 10$$

$$V_7 = -0.9 \text{ V}$$

Problem 6.65

Consider the circuit shown in Fig. P6.65. It resembles that in Fig. 6.30 but includes other features. First, note diodes D_1 and D_2 are included to make design (and analysis) easier and to provide temperature compensation for the emitter-base voltages of Q_1 and Q_2 . Second, note resistor R , whose purpose is to provide negative feedback (more on this later in the book!). Using $|V_{BE}|$ and $V_D = 0.7\text{ V}$ independent of current, and $\beta = \infty$, find the voltages V_{B1} , V_{E1} , V_{C1} , V_{B2} , V_{E2} , and V_{C2} , initially with R open-circuited and then with R connected. Repeat for $\beta = 100$, with R open-circuited initially, then connected.

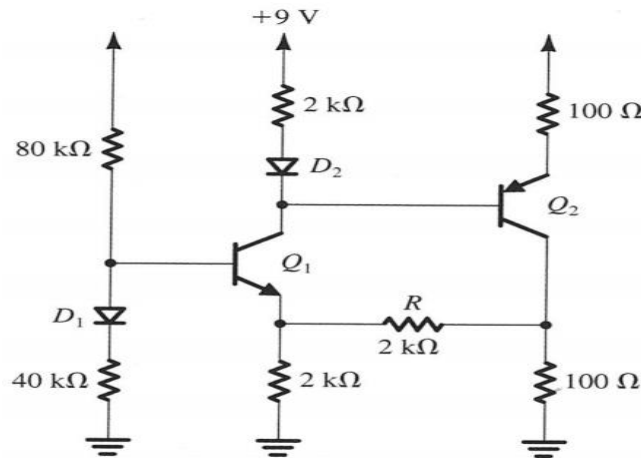


Figure P6.65

For $\beta = \infty$ and R open-circuited

$$\begin{aligned}
 V_{D1} &= V_{BE1} \\
 V_1 &= V_{E1} \\
 40I_{D1} &= 2I_{E1} \\
 I_{D1} &= \frac{9 - 0.7}{80 + 40} = 0.07\text{ mA} \\
 I_{E1} &= 1.4\text{ mA} \\
 V_{E1} &= 2I_{E1} = 2.8\text{ V} \\
 V_{B1} &= V_{E1} + 0.7 = 3.5\text{ V} \\
 I_{C1} &= I_{E1} = 1.4\text{ mA} \\
 V_2 &= 9 - 2I_{C1} = 6.2\text{ V} \\
 V_{C1} &= V_2 - V_{D2} = 5.5\text{ V} \\
 V_{E2} &= V_2 = 6.2\text{ V} \\
 I_{E2} &= \frac{9 - 6.2}{100} = 28\text{ mA} \\
 I_{C2} &= I_E = 28\text{ mA} \\
 V_{C2} &= 28 \times 0.1 = 2.8\text{ V}
 \end{aligned}$$

For $\beta=\infty$ and $R = 2k\Omega$

There will be no current through R, so all the voltages and currents are the same

For $\beta=100$ and R open-circuited

$$\begin{aligned}V_1 &= V_{E1} \\40I_{D1} &= 2I_{E1} \\I_{D1} &= 0.05I_{E1} \\I_{B1} &= \frac{I_{E1}}{101} = 0.01I_{E1}\end{aligned}$$

The current through the 80k Ω resistor is


$$\begin{aligned}I_{D1} + I_{B1} &= 0.06I_{E1} \\V_{B1} &= V_{E1} + 0.7 = 2I_{E1} + 0.7 \\0.06I_{E1} &= \frac{9 - V_{B1}}{80} \\I_{E1} &= 1.22 \text{ mA} \\V_{E1} &= 2I_{E1} = 2.44V \\V_{B1} &= V_{E1} + 0.7 = 3.14V \\I_{C1} &= \alpha I_{E1} = 1.21 \text{ mA}\end{aligned}$$

Voltage across the 2k Ω resistor is equal to voltage in 100 Ω resistor

$$\begin{aligned}2I_{D2} &= 0.1I_{E2} \\I_{D2} &= 0.05I_{E2} \\I_{D2} &= I_{C1} - 0.01I_{E2} \\I_{E2} &= \frac{I_{C1}}{0.06} = 20.13 \text{ mA} \\I_{D2} &= 1 \text{ mA} \\V_{C1} &= 9 - 2I_{D2} = 6.3V \\V_{E2} &= V_{C1} + 0.7 = 7V \\I_{C2} &= \alpha I_{E2} = 20 \text{ mA} \\V_{C2} &= 20 \times 0.1 = 2V\end{aligned}$$

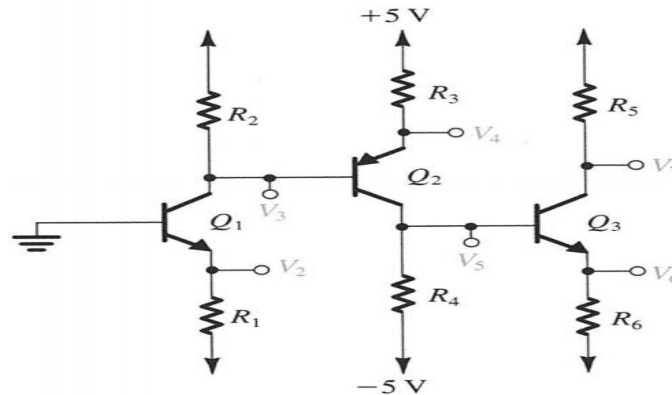Problem 6.67

Using $\beta = \infty$, design the circuit shown in Fig. P6.67 so that the emitter currents of Q_1 , Q_2 , and Q_3 are 0.5 mA, 0.5 mA, and 1 mA, respectively, and $V_3 = 0$, $V_5 = -2$ V, and $V_7 = 1$ V. For each resistor, select the nearest standard value utilizing the table of standard values for 5% resistors in Appendix J. Now, for $\beta = 100$, find the values of V_3 , V_4 , V_5 , V_6 , and V_7 .



For $\beta = \infty$, and calculating the values of the resistors

$$V_2 = -0.7V$$

$$R_1 = \frac{V_2 - (-5)}{0.5 \text{ mA}}$$

$$R_1 = 8.6 \text{ k}\Omega$$

$$R_2 = \frac{(5) - V_3}{0.5 \text{ mA}}$$

$$R_2 = 10 \text{ k}\Omega$$

$$V_4 = 0 + 0.7 = 0.7V$$

$$R_3 = \frac{(5) - V_4}{0.5 \text{ mA}}$$

$$R_3 = 8.6 \text{ k}\Omega$$

$$R_4 = \frac{V_5 - (-5)}{0.5 \text{ mA}}$$

$$R_4 = 6 \text{ k}\Omega$$

$$V_6 = V_5 - 0.7 = -2.7V$$

$$R_6 = \frac{V_6 - (-5)}{1 \text{ mA}}$$

$$R_6 = 2.3 \text{ k}\Omega$$

$$R_5 = \frac{(5) - V_7}{1 \text{ mA}}$$

$$R_5 = 4 \text{ k}\Omega$$

Using the table for 5% resistors

$$R_1 = 8.2 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$R_4 = 6.2 \text{ k}\Omega$$

$$R_5 = 3.9 \text{ k}\Omega$$

$$R_6 = 2.4 \text{ k}\Omega$$

Then for $\beta=100$

$$V_2 = -0.7V$$

$$I_{E1} = \frac{V_2 - (-5)}{8.2 \text{ k}\Omega}$$

$$I_{E1} = 0.524 \text{ mA}$$

$$I_{C1} = \alpha I_{E1} = 0.99 \times 0.524$$

$$I_{C1} = 0.52 \text{ mA}$$

The current I_1 through $10 \text{ k}\Omega$

$$I_1 = I_{C1} - I_{B1} = I_{C1} - \frac{I_{E2}}{101}$$

Also the voltage through $10 \text{ k}\Omega$

$$I_{E2} \times 8.2 \text{ k} + 0.7$$

Using the voltages

$$10I_1 = 8.2 I_{E2} + 0.7$$

$$10 \left(I_{C1} - \frac{I_{E2}}{101} \right) = 8.2 I_{E2} + 0.7$$

$$I_{E2} = 0.542 \text{ mA}$$

$$V_4 = 5 - 0.542 \times 8.2 = 0.56V$$

$$V_3 = 0.56 - 0.7 = -0.14V$$

$$I_{C2} = \alpha I_{E2} = 0.99 \times 0.542$$

$$I_{C2} = 0.537 \text{ mA}$$

The current I_2 through $6.2\text{ k}\Omega$

$$I_2 = I_{C2} - I_{B3} = 0.537 - \frac{I_{E3}}{101}$$

Also the voltage through $6.2\text{ k}\Omega$

$$I_{E2} \times 2.4\text{ k} + 0.7$$

Using the voltages

$$6.2I_2 = 2.4I_{E3} + 0.7$$

$$6.2 \left(0.537 - \frac{I_{E3}}{101} \right) = 2.4I_{E3} + 0.7$$

$$I_{E3} = 1.07\text{ mA}$$

$$V_6 = -5 + 1.07 \times 2.4 = -2.43\text{ V}$$

$$V_5 = V_6 + 0.7 = -1.73\text{ V}$$


$$I_{C3} = \alpha I_{E3} = 0.99 \times 1.07$$

$$I_{C3} = 1.06\text{ mA}$$

$$V_7 = -3.9 \times 1.06 = 0.87\text{ V}$$

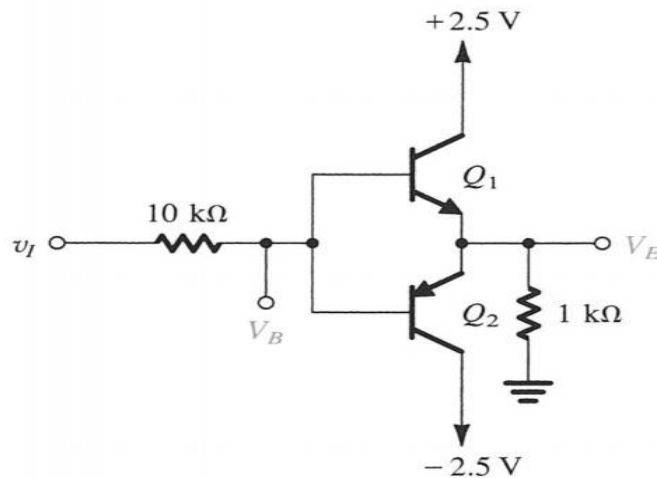Problem 6.68

For the circuit in Fig. P6.68, find V_B and V_E for $v_I = 0\text{ V}$, $+2\text{ V}$, -2.5 V , and -5 V . The BJTs have $\beta=50$.



For $V_I = 0\text{ V}$ both transistors are cut off and all the currents are zero

$$V_B = V_E = 0$$

For $V_I = 2\text{ V}$ Q_1 will be conducting and Q_2 will be cut off.

$$I_E = \frac{2 - 0.7}{1 + \frac{10}{51}}$$

$$I_E = 1.1\text{ mA}$$

$$V_E = 1.1\text{ V}$$

$$V_B = 1.8\text{ V}$$

For $V_I = -2.5\text{ V}$ Q_1 will be cut off and Q_2 will be conducting.

$$I_E = \frac{2.5 - 0.7}{1 + \frac{10}{51}}$$

$$I_E = 1.5\text{ mA}$$

$$V_E = -I_E \times 1 = -1.5\text{ V}$$

$$V_B = -2.2\text{ V}$$