

ECE 523/421 - Analog Electronics
University of New Mexico
Solutions Homework 5

Problem 7.128

The CE amplifier circuit of Fig. P7.128 is biased with a constant-current source I . It is required to design the circuit (i.e., find values for I , R_B , and R_C) to meet the following specifications:

- (a) $R_{in} \cong 10 \text{ k}\Omega$.
- (b) The dc voltage drop across R_B is approximately 0.2 V.
- (c) The open-circuit voltage gain from base to collector is the maximum possible, consistent with the requirement that the collector voltage never fall by more than approximately 0.4 V below the base voltage with the signal between base and emitter being as high as 5 mV.

Assume that v_{sig} is a sinusoidal source, the available supply $V_{CC}=5 \text{ V}$, and the transistor has $\beta=100$. Use standard 5% resistance values, and specify the value of I to one significant digit. What base-to-collector open-circuit voltage gain does your design provides? If $R_{sig} = R_L = 20 \text{ k}\Omega$, what is the overall voltage gain?

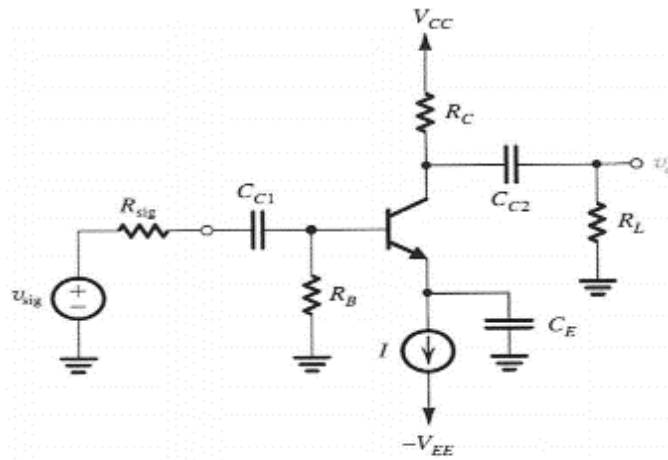


Figure P7.128

For $R_B = 0.2 \text{ V}$

$$\begin{aligned}
 I_B R_B &= 0.2 \text{ V} \\
 \frac{I}{\beta + 1} R_B &= 0.2 \text{ V} \\
 I R_B &= 0.2 \times 101 \\
 R_{in} = R_B \parallel r_{\pi} &= 10 \text{ k}\Omega \\
 R_B \parallel \frac{V_T}{I_B} &= 10
 \end{aligned}$$

$$R_B \parallel \frac{0.025}{\frac{I}{\beta + 1}} = 10$$

Solving the parallel

$$\frac{0.025 \times 101 R_B}{I R_B + 0.025 \times 101} = 10$$

$$R_B = 90 k\Omega$$

$$I = \frac{0.2 \times 101}{90 k\Omega} = 0.22 \text{ mA}$$

For meeting the third specification

$$V_C - |A_{vo}| \times 0.005 = V_B + 0.005 - 0.4$$

Where

$$V_C = V_{CC} - I_C R_C$$

$$V_C = 5 - 0.22 R_C$$

$$|A_{vo}| = g_m R_C$$

$$|A_{vo}| = 8.7 R_C$$

$$V_B = -\frac{0.22}{101} \times 90 = -0.2 \text{ V}$$

Values into the equation

$$5 - 0.22 R_C - 8.7 R_C \times 0.005 = -0.2 + 0.005 - 0.4$$

$$R_C = 21.2 k\Omega$$

Selecting the 5% resistors and I to one significant digit

$$R_B = 91 k\Omega$$

$$R_C = 22 k\Omega$$

$$I = 0.2 \text{ mA}$$

Calculating the gain

$$g_m = \frac{\alpha I_C}{V_T} \cong \frac{0.2}{0.025} = 8 \text{ mA/V}$$

$$A_{vo} = -g_m R_C = -176$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{8} = 12.5 \text{ k}\Omega$$

$$R_{in} = R_B \parallel r_\pi = 11 k\Omega$$

$$G_v = -\frac{11}{20 + 11} \times 8(22 \parallel 20) = -29.7$$

Problem 7.129

In the circuit of Fig. P7.129, v_{sig} is a small sine-wave signal with zero average. The transistor β is 100.

- Find the value of R_E to establish a dc emitter current of about 0.5 mA.
- Find R_C to establish a dc collector voltage of about +0.5 V.
- For $R_L = 10\text{ k}\Omega$, draw the small-signal equivalent circuit of the amplifier and determine its overall voltage gain.

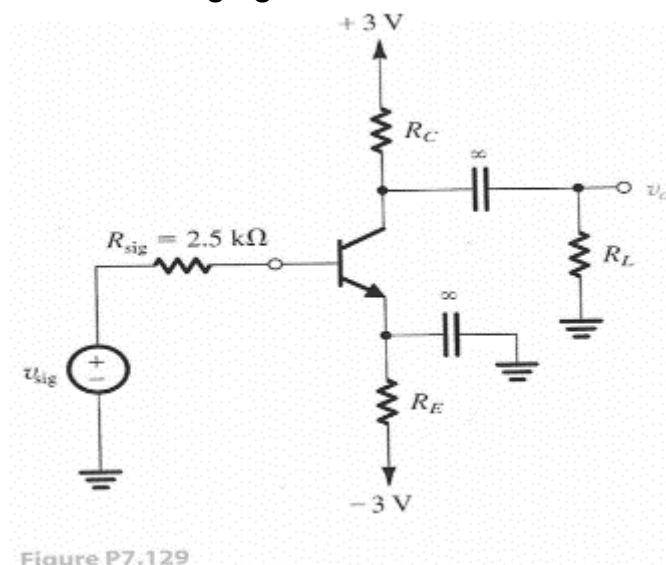


Figure P7.129

For $I_E = 0.5\text{ mA}$, and applying KVL

$$I_B R_{sig} + V_{BE} + I_E R_E = 3$$

$$\frac{0.5}{101} \times 25 + 0.7 + 0.5 R_E = 3$$

$$R_E = 46\text{ k}\Omega$$

$$I_C = \alpha I_E \cong 0.5\text{ mA}$$

$$V_C = 0.5 = 3 - 0.5 R_C$$

$$R_C = 5\text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5}{0.025} = 20\text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{20} = 5\text{ k}\Omega$$


$$G_v = \frac{v_o}{v_{sig}} = -\frac{5}{5 + 2.5} \times 20(5 || 10)$$

$$G_v = -44.4$$

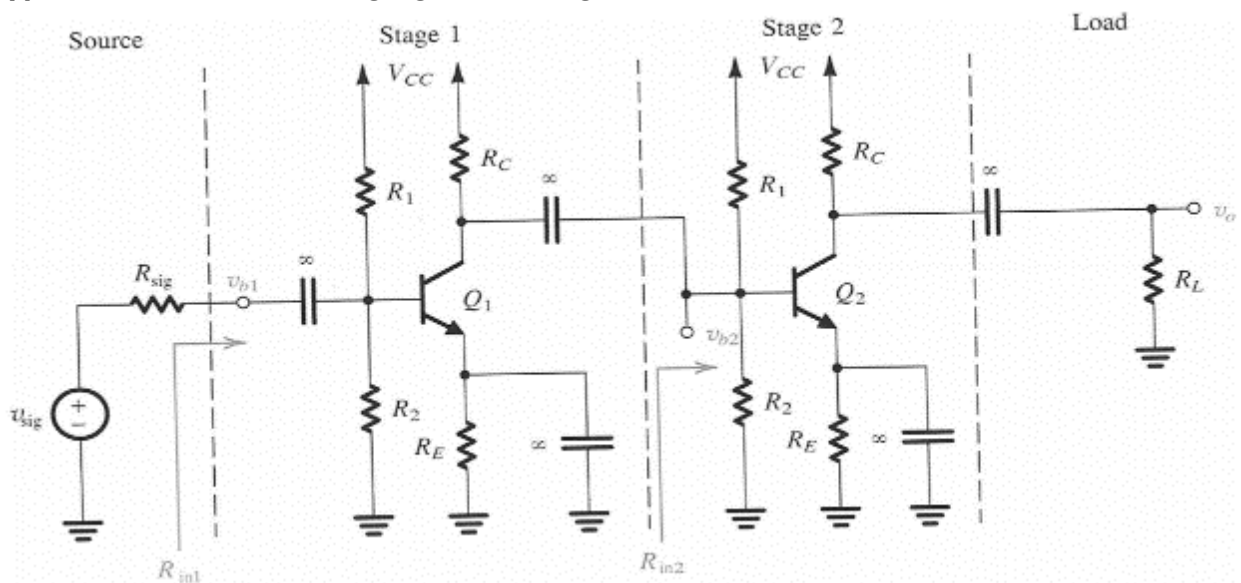Problem 7.130

The amplifier of Fig. P7.130 consists of two identical common-emitter amplifiers connected in cascade. Observe that the input resistance of the second stage, R_{in2} , constitutes the load resistance of the first stage.

- For $V_{CC} = 15\text{ V}$, $R_1 = 100\text{ k}\Omega$, $R_2 = 47\text{ k}\Omega$, $R_E = 3.9\text{ k}\Omega$, $R_C = 6.8\text{ k}\Omega$, and $\beta = 100$, determine the dc collector current and dc collector voltage of each transistor.
- Draw the small-signal equivalent circuit of the entire amplifier and give the values of all its components.
- Find R_{in1} and v_{b1}/v_{sig} for $R_{sig} = 5\text{ k}\Omega$.
- Find R_{in2} and v_{b2}/v_{b1} .
- For $R_L = 2\text{ k}\Omega$, find v_o/v_{b2} .
- Find the overall voltage gain v_o/v_{sig} .



$$V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 15 \frac{47}{100 + 47} = 4.8\text{V}$$

$$R_B = R_1 || R_2 = 100 || 47 = 32\text{k}\Omega$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_B + \frac{R_E}{\beta + 1}} = 0.97\text{ mA}$$

$$I_C = \alpha I_E \cong 1\text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 15 - 1 \times 6.8 = 8.2\text{V}$$

b)

$$g_m = \frac{I_C}{V_T} = \frac{1}{0.025} = 40\text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5\text{ k}\Omega$$

c)

$$R_{in1} = R_1 || R_2 || r_\pi = 2.32k\Omega$$
$$\frac{v_{b1}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{2.32}{2.32 + 5} = 0.32$$

d)

$$R_{in2} = R_1 || R_2 || r_\pi = 2.32k\Omega$$
$$\frac{v_{b2}}{v_1} = \frac{v_{b2}}{v_{\pi1}} = -g_m(R_C || R_2)$$
$$\frac{v_{b2}}{v_1} = -40(6.8 || 2.32) = -69.2$$

e)


$$\frac{v_o}{v_{b2}} = \frac{v_o}{v_{\pi2}} = -g_m(R_C || R_L)$$
$$\frac{v_o}{v_{b2}} = -40(6.8 || 2) = -61.8$$

f)

$$\frac{v_o}{v_{sig}} = \frac{v_o}{v_{b2}} \times \frac{v_{b2}}{v_{b1}} \times \frac{v_{b1}}{v_{sig}} = 1368.5$$

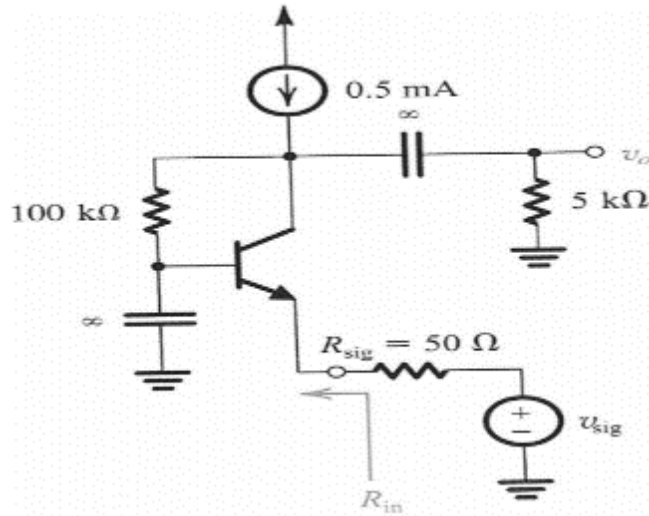Problem 7.133

For the circuit in Fig. P7.133, find the input resistance R_{in} and the voltage gain v_o/v_{sig} . Assume that the source provides a small signal v_{sig} and that $\beta=100$.



$$I_C = \alpha I_E \cong 0.5 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$R_{in} = r_e = 50 \Omega$$

$$i_e = \frac{-v_{sig}}{r_e + R_{sig}} = \frac{-v_{sig}}{50 + 50} = \frac{-v_{sig}}{0.1 \text{ k}\Omega}$$

$$v_o = -\alpha i_E (5 || 100)$$

$$v_o = -\alpha \frac{-v_{sig}}{0.1 \text{ k}\Omega} (5 || 100)$$

$$\frac{v_o}{v_{sig}} = \alpha \frac{(5 || 100)}{0.1 \text{ k}\Omega} = 47.6$$

Problem 7.135

For the emitter follower in Fig. P7.135, the signal source is directly coupled to the transistor base. If the dc component of v_{sig} is zero, find the dc emitter current. Assume $\beta=100$. Neglecting r_o , find R_{in} , the voltage gain v_o/v_{sig} , the current gain i_o/i_i , and the output resistance R_{out} .

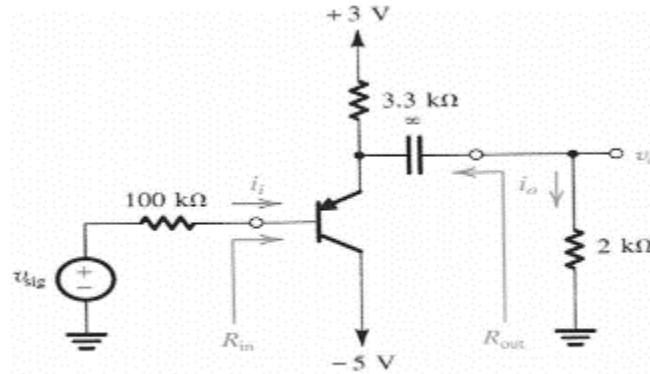


Figure P7.135

$$I_E = \frac{V_{CC} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} = \frac{3 - 0.7}{3.3 + \frac{100}{100 + 1}}$$

$$I_E = 0.54 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.54 \text{ mA}} = 46.3 \Omega$$

$$R_{in} = (\beta + 1)[r_e + (3.3 || 2)] = 130.4 \text{ k}\Omega$$

$$\frac{v_b}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{130.4}{130.4 + 100} = 0.566$$

$$\frac{v_o}{v_b} = \frac{(3.3 || 2)}{(3.3 || 2) + r_e} = \frac{1.245}{1.245 + 0.0463} = 0.964$$

$$\frac{v_o}{v_{sig}} = \frac{v_o}{v_b} \times \frac{v_b}{v_{sig}} = 0.55$$

$$i_o = \frac{v_o}{2 \text{ k}\Omega}$$

$$i_i = \frac{v_b}{130.4 \text{ k}\Omega}$$

$$\frac{i_o}{i_i} = \frac{v_o}{v_b} \times \frac{130.4}{2} = 62.9$$

$$R_{out} = 3.3 || (r_E + \frac{R_B}{\beta + 1})$$

$$R_{out} = 789 \Omega$$