

ECE 523/421 - Analog Electronics: University of New Mexico

Problem 8.42

Figure P8.42 shows an IC MOS amplifier formed by cascading two common-source stages. Assuming that $V_{an} = |V_{Ap}|$ and that the biasing current sources have output resistances equal to those of Q_1 and Q_2 , find an expression for the overall voltage gain in terms of g_m and r_o of Q_1 and Q_2 . If Q_1 and Q_2 are to be operated at equal overdrive voltages, $|V_{OV}|$, find the required value of $|V_{OV}|$ if $|V_A| = 5$ V and the gain required is 400 V/V.

 


Figure P8.42

Using the π model of the two transistors.

$$v_{gs2} = -g_{m1}v_i(r_{o1} || r_{o1})$$

$$v_{gs2} = -g_{m1}v_i\left(\frac{r_{o1}}{2}\right)$$

We do the same for the second transistor

$$v_o = -g_{m2}v_{gs2}(r_{o2} || r_{o2})$$

$$v_o = -g_{m2}v_{gs2}\left(\frac{r_{o2}}{2}\right)$$

Since the r_o and g_m is equal for both transistors, and solving

$$v_o = -g_{m2}\left(-g_{m1}v_i\left(\frac{r_{o1}}{2}\right)\right)\left(\frac{r_{o2}}{2}\right)$$

$$G_v = \frac{v_o}{v_i} = g_m^2\left(\frac{r_o^2}{4}\right)$$

For calculating V_{ov}

$$g_m = \frac{2I_D}{V_{OV}}$$

$$r_o = \frac{V_A}{I_D}$$

$$G_v = \frac{1}{4} \left(\frac{2I_D}{V_{OV}} \right)^2 \left(\frac{V_A}{I_D} \right)^2$$

$$G_v = \left(\frac{V_A}{V_{OV}} \right)^2$$


Using $|V_A| = 5 \text{ V}$ and gain = 400 V/V.

$$V_{OV} = 0.25$$

Problem 8.47

Consider the circuit shown in Fig. 8.16(a), using a 3.3-V supply and transistors for which $|V_t| = 0.8$ V and $L = 1$ μm . For Q_1 , $k_n = 100$ $\mu\text{A/V}^2$, $V_A = 100$ V, and $W = 20$ μm . For Q_2 and Q_3 , $k_p = 50$ $\mu\text{A/V}^2$ and $|V_A| = 50$ V. For Q_2 , $W = 40$ μm . For Q_3 , $W = 10$ μm .

- If Q_1 is to be biased at 100 μA , find I_{REF} . For simplicity, ignore the effect of V_A .
- What are the extreme values of v_o for which Q_1 and Q_2 just remain in saturation?
- What is the large-signal voltage gain?
- Find the slope of the transfer characteristic at $v_o = V_{\text{DD}}/2$.
- For operation as a small-signal amplifier around a bias point at $v_o = V_{\text{DD}}/2$, find the small-signal voltage gain and output resistance.

 

Calculating the reference current

$$\begin{aligned}
 I_{D2} &= I_{D1} = 100 \mu\text{A} \\
 \frac{I_{D3}}{I_{D2}} &= \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_2} = \frac{W_3}{W_2} = \frac{10}{40} \\
 I_{D3} &= \frac{1}{4} I_{D2} \\
 I_{\text{REF}} &= I_{D3} = 25 \mu\text{A}
 \end{aligned}$$

Calculating the output resistance

$$\begin{aligned}
 R_{\text{out}} &= r_{o1} || r_{o2} \\
 r_{o1} &= \frac{V_{A1}}{I_D} = \frac{100}{0.1\text{m}} = 1\text{M}\Omega \\
 r_{o2} &= \frac{V_{A2}}{I_D} = \frac{50}{0.1\text{m}} = 500\text{k}\Omega \\
 R_{\text{out}} &= 333.3 \text{ k}\Omega
 \end{aligned}$$

Calculating the small signal voltage gain


$$g_m = \sqrt{2k_n I_{D1}}$$
$$g_m = \sqrt{2(100\mu)(20/1)(100\mu)}$$
$$g_m = 0.632 \text{ mA/V}$$

$$A_v = -g_{m1}(r_{o1} || r_{o2})$$
$$A_v = -210.6$$

Problem 8.55

In the common-gate amplifier circuit of Fig. P8.55, Q_2 and Q_3 are matched. $k_n(W/L)_n = k_p(W/L)_p = 4 \text{ mA/V}^2$, and all transistors have $|V_t| = 0.8 \text{ V}$ and $|V_A| = 20 \text{ V}$. The signal v_{sig} is a small sinusoidal signal with no dc component.

 - Neglecting the effect of V_A , find the dc drain current of Q_1 and the required value of V_{BIAS} .
- Find the values of g_{m1} and r_o for all transistors.
- Find the value of R_{in} .
- Find the value of R_{out} .
- Calculate the voltage gains v_o/v_i and v_o/v_{sig} .
- How large can v_{sig} be (peak-to-peak) while maintaining saturation-mode operation for Q_1 and Q_2 ?



a) The drain currents of Q_2 is equal to Q_3 , so the drain current of Q_1 is equal to drain current of transistor 3.

$$I_{D1} = 100 \mu A$$

Using the expression of I_{D1} and substituting the values we can obtain v_{GS1}

$$I_{D1} = \frac{1}{2} k_n (v_{GS1} - V_t)^2$$

$$100 \mu = \frac{1}{2} 4m (v_{GS1} - 0.8)^2$$

$$v_{GS1} = 1.024 \text{ V}$$

For calculating V_{BIAS}

$$V_{BIAS} = I_{D1} R + v_{GS1}$$

$$V_{BIAS} = 100 \mu A 50 \Omega + 1.024 \text{ V}$$

$$V_{BIAS} = 1.029 \text{ V}$$

b) For calculating g_m

$$g_m = \sqrt{2k_n I_{D1}}$$
$$g_m = \sqrt{2(4m)(100\mu)}$$
$$g_m = 0.89 \text{ mA/V}$$

For calculating r_o

$$r_o = \frac{V_A}{I_D}$$
$$r_o = \frac{20}{100 \mu A}$$
$$r_o = 200 \text{ K}\Omega$$

c) For calculating R_{in}

$$R_{in} = \frac{r_{o1} + r_{o2}}{1 + r_{o1}g_{m1}}$$
$$R_{in} = \frac{200k + 200k}{1 + 200k(0.89m)}$$
$$R_{in} = 2.247 \text{ k}\Omega$$

d) For calculating R_{out}

$$R_{out} = r_{o1} + 50(1 + r_{o1}g_{m1})$$
$$R_{out} = 200k + 50(1 + 200k(0.89m))$$
$$R_{out} = 209 \text{ k}\Omega$$

e) For calculating the gains

$$v_o = v_i \left(\frac{(1 + r_{o1}g_{m1})r_{o2}}{r_{o1} + r_{o2}} \right)$$
$$\frac{v_o}{v_i} = \left(\frac{(1 + 200k(0.89m))200k}{200k + 200k} \right)$$
$$\frac{v_o}{v_i} = 89.5$$
$$v_i = v_{sig} \left(\frac{R_{in}}{R_{in} + 50} \right)$$
$$v_o = v_{sig} \left(\frac{R_{in}}{R_{in} + 50} \right) \left(\frac{(1 + r_{o1}g_{m1})r_{o2}}{r_{o1} + r_{o2}} \right)$$
$$\frac{v_o}{v_{sig}} = \left(\frac{2.247 \text{ k}}{2.247 \text{ k} + 50} \right) \left(\frac{(1 + 200k(0.89m))200k}{200k + 200k} \right)$$
$$G_V = 87.5$$

Problem 8.62

In a MOS cascode amplifier, the cascode transistor is required to raise the output resistance by a factor of 50. If the transistor is operated at $V_{OV} = 0.2$ V, what must its V_A be? If the process technology specifies V_A as 5 V/ μm , what channel length must the transistor have?

As we saw in class, the factor that the problem state is

$$K = g_{m2} r_{o2}$$

$$g_m = \frac{2I_D}{V_{OV}}$$

$$r_o = \frac{V_A}{I_D}$$

$$K = \frac{2I_D}{V_{OV}} \frac{V_A}{I_D}$$

$$K = \frac{2V_A}{V_{OV}}$$

From here

$$V_A = 5V$$

For calculating the channel length

$$V_A = V_A' L$$

$$L = \frac{5V}{5 \text{ V}/\mu\text{m}}$$

$$L = 1\mu\text{m}$$

Problem 8.65

Design the cascode amplifier of Fig. 8.30(a) to obtain $g_{m1} = 2 \text{ mA/V}$ and $R_o = 200 \text{ k}\Omega$. Use a $0.18\text{-}\mu\text{m}$ technology for which $V_{tn} = 0.5 \text{ V}$, $V_A = 5 \text{ V}/\mu\text{m}$, and $k_n = 400 \mu\text{A/V}^2$. Determine L , W/L , V_{G2} , and I . Use identical transistors operated at $V_{OV} = 0.25 \text{ V}$, and design for the maximum possible negative signal swing at the output. What is the value of the minimum permitted output voltage?

For calculating the current

$$g_m = \frac{2I_D}{V_{OV}}$$

$$I_D = \frac{g_m V_{OV}}{2}$$

$$I_D = \frac{2 \text{ mA} \cdot 0.25}{2}$$

$$I_D = 0.25 \text{ mA}$$

For calculating the length

$$R_o = g_{m1} r_{o1} r_{o2}$$

$$r_o = \frac{V_A' L}{I_D}$$

$$R_o = g_{m1} \frac{V_A' L}{I_D} \frac{V_A' L}{I_D}$$

$$200 \text{ k}\Omega = 2 \text{ mA} \frac{(5 \text{ V}/\mu\text{m})^2 L^2}{0.25 \text{ mA}^2}$$

$$L = 0.5 \mu\text{m}$$

For calculating W/L

$$I_{D1} = \frac{1}{2} k_n' \frac{W}{L} (v_{GS1} - V_t)^2$$

$$0.25 \text{ mA} = \frac{1}{2} 400 \mu \frac{W}{L} (0.25)^2$$

$$\frac{W}{L} = 20$$

For maximum negative signal swing

$$V_{DS} = V_{OV} = 0.25 \text{ V}$$

$$V_{G2} = V_{DS} + V_{GS}$$

$$V_{G2} = V_{DS} + V_{OV} + V_{tn}$$

$$V_{G2} = 0.25 + 0.25 + 0.5$$

$$V_{G2} = 1 \text{ V}$$

For minimum output voltage

$$\begin{aligned}V_{out} &= V_{DS} + V_{DS} \\V_{out} &= 0.25 + 0.25 \\V_{out} &= 0.5V\end{aligned}$$

Problem 8.69

The cascode transistor can be thought of as providing a “shield” for the input transistor from the voltage variations at the output. To quantify this “shielding” property of the cascode, consider the situation in Fig. P8.69. Here we have grounded the input terminal (i.e., reduced v_i to zero), applied a small change v_x to the output node, and denoted the voltage change that results at the drain of Q_1 by v_y . By what factor is v_y smaller than v_x ?

 


Figure P8.69

From the circuit we can see $v_{gs1} = 0$

$$v_i = v_{gs1} = 0$$

$$v_y = -v_{gs2}$$

Using the small signal model with the dependent source of Q_1 in open circuit and using KCL in the V_y node

$$\frac{v_y}{r_{o1}} - g_{m2}v_{gs2} + \frac{v_y - v_x}{r_{o2}} = 0$$

$$\frac{v_y}{r_{o1}} - g_{m2}v_y + \frac{v_y}{r_{o2}} = \frac{v_x}{r_{o2}}$$

Calculating $\frac{v_y}{v_x}$ from the formula

$$\frac{v_y}{v_x} = \frac{1}{g_{m2}r_{o2}}$$