 


ECE 523/421 - Analog Electronics: University of New Mexico

Problem 9.24

A design error has resulted in a gross mismatch in the circuit of Fig. P9.24. Specifically, Q2 has twice the W/L ratio of Q1. If v_{id} is a small sine-wave signal, find:

- I_{D1} and I_{D2} .
- VOV for each of Q1 and Q2.
- The differential gain A_d in terms of R_D , I , and VOV.



a) For I_D

$$I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$I_{D2} = \frac{1}{2} k_n' \left(2 \frac{W}{L} \right) (V_{GS2} - V_t)^2$$

From the circuit

$$\begin{aligned} V_{GS1} - V_t &= V_{GS2} - V_t \\ I_{D2} &= \frac{1}{2} k_n' \left(2 \frac{W}{L} \right) (V_{GS2} - V_t)^2 \\ (V_{GS2} - V_t)^2 &= \frac{I_{D2}}{\frac{1}{2} k_n' \left(2 \frac{W}{L} \right)} \end{aligned}$$

Substituting that on equation for Id1

$$I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) \frac{I_{D2}}{\frac{1}{2} k_n' \left(2 \frac{W}{L} \right)}$$
$$I_{D1} = \frac{I_{D2}}{2}$$

Also

$$I = I_{D1} + I_{D2}$$

Solving for this equations

$$I_{D1} = \frac{I}{3}$$
$$I_{D2} = \frac{2I}{3}$$

b) Substituting values


$$I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{OV1})^2$$
$$\frac{I}{3} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{OV1})^2$$
$$V_{OV1} = \sqrt{\frac{2}{3} \frac{I}{k_n' \left(\frac{W}{L} \right)}}$$

$$I_{D2} = \frac{1}{2} k_n' \left(2 \frac{W}{L} \right) (V_{OV2})^2$$
$$\frac{2I}{3} = \frac{1}{2} k_n' \left(2 \frac{W}{L} \right) (V_{OV2})^2$$
$$V_{OV2} = \sqrt{\frac{2}{3} \frac{I}{k_n' \left(\frac{W}{L} \right)}}$$

Problem 9.61

The differential amplifier circuit of Fig. P9.61 utilizes a resistor connected to the negative power supply to establish the bias current I .

- For $v_{B1} = vid/2$ and $v_{B2} = -vid/2$, where vid is a small signal with zero average, find the magnitude of the differential gain, $|v_o/vid|$.
- For $v_{B1} = v_{B2} = vicm$, where $vicm$ has a zero average, find the magnitude of the common-mode gain, $|v_o/vicm|$.
- Calculate the CMRR.
- If $v_{B1} = 0.1 \sin 2\pi \times 60t + 0.005 \sin 2\pi \times 1000t$, volts, and $v_{B2} = 0.1 \sin 2\pi \times 60t - 0.005 \sin 2\pi \times 1000t$, volts, find v_o .

 

a) For calculating the current of the resistor

$$I = \frac{5 - 0.7}{4.3 \text{ k}\Omega}$$

$$I = 1 \text{ mA}$$

$$I_E = \frac{I}{2}$$

$$I_E = 0.5 \text{ mA}$$

$$r_e = \frac{V_T}{I_E}$$

$$r_e = 50 \Omega$$

$$A_d = \frac{\alpha}{2r_e} (R_C)$$

$$A_d = \frac{\alpha}{2r_e} (R_C)$$

$$A_d = 20 \text{ V/V}$$

b) For the gain in common mode

$$A_{cm} = \frac{\alpha}{2R_e + r_e} (R_C)$$
$$A_{cm} = \frac{1}{2(4.3k) + 50} (2k)$$
$$A_{cm} = 0.23 \text{ V/V}$$

c) For the common-mode reject ratio


$$CMRR = 20 \log \left(\frac{A_d}{A_{cm}} \right)$$
$$CMRR = 20 \log \left(\frac{29}{0.23} \right)$$
$$CMRR = 38.8 \text{ dB}$$

Problem 9.98

Figure P9.98 shows a differential cascode amplifier with an active load formed by a Wilson current mirror. Utilizing the expressions derived in Chapter 8 for the output resistance of a bipolar cascode and the output resistance of the Wilson mirror, and assuming all transistors to be identical, show that the differential voltage gain A_d is given approximately by

$$A_d = \frac{1}{3}(\beta g_m r_o)$$

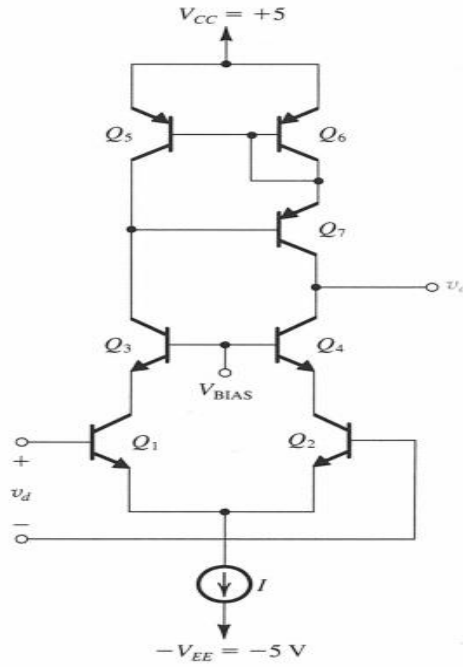Evaluate A_d for the case of $\beta = 100$ and $V_A = 20$ V.



$$A_{vo} = G_m(R_o)$$

$$G_m = g_m$$

$$R_o = R_{oc} || R_{ow}$$

$$R_{oc} = \text{Output resistance of cascode stage} = \beta r_o$$

$$R_{ow} = \text{Output resistance of wilson stage} = \frac{\beta r_o}{2}$$

$$R_o = \beta r_o || \frac{\beta r_o}{2}$$

$$R_o = \frac{\beta r_o}{3}$$

$$A_{vo} = g_m \left(\frac{\beta r_o}{3} \right)$$

$$A_{vo} = \frac{1}{3}(\beta g_m r_o)$$

Evaluating

$$g_m = \frac{I/2}{V_t}$$

$$r_o = \frac{V_A}{I/2}$$

$$A_{vo} = \frac{\beta}{3} \frac{I/2}{V_t} \frac{V_A}{I/2}$$

$$A_{vo} = \frac{\beta}{3} \frac{V_A}{V_t}$$


$$A_{vo} = 26666.7$$

$$A_{vo} = 88.5 \text{ dB}$$

 Problem 9.114

The two-stage CMOS op amp in Fig. P9.114 is fabricated in a 0.18- μm technology having $k'_n = 4k'_p = 400 \mu\text{A/V}^2$, $V_{tn} = -V_{tp} = 0.4 \text{ V}$.

- With A and B grounded, perform a dc design that will result in each of Q_1 , Q_2 , Q_3 , and Q_4 conducting a drain current of $100 \mu\text{A}$ and each of Q_6 and Q_7 a current of $200 \mu\text{A}$. Design so that all transistors operate at 0.2-V overdrive voltages. Specify the W/L ratio required for each MOSFET. Present your results in tabular form. What is the dc voltage at the output (ideally)?
- Find the input common-mode range.
- Find the allowable range of the output voltage.



- For obtaining the W/L ratios we will use the current equation

$$I_{D1,2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_{1,2} (V_{OV})^2$$

$$100 \mu = \frac{1}{2} 400 \mu \left(\frac{W}{L} \right)_{1,2} (0.2)^2$$

$$\left(\frac{W}{L} \right)_{1,2} = 12.5$$

$$I_{D3,4} = \frac{1}{2} k'_p \left(\frac{W}{L} \right)_{3,4} (V_{OV})^2$$

$$100 \mu = \frac{1}{2} 100 \mu \left(\frac{W}{L} \right)_{3,4} (0.2)^2$$

$$\left(\frac{W}{L} \right)_{3,4} = 50$$

$$I_{D6} = \frac{1}{2} k_p' \left(\frac{W}{L} \right)_6 (V_{OV})^2$$

$$200 \mu = \frac{1}{2} 100 \mu \left(\frac{W}{L} \right)_6 (0.2)^2$$

$$\left(\frac{W}{L} \right)_6 = 100$$

$$I_{D5,7,8} = \frac{1}{2} k_n' \left(\frac{W}{L} \right)_{5,7,8} (V_{OV})^2$$

$$200 \mu = \frac{1}{2} 400 \mu \left(\frac{W}{L} \right)_{5,7,8} (0.2)^2$$

$$\left(\frac{W}{L} \right)_{5,7,8} = 25$$

IF A and B are connected to ground, the output voltage should be 0V

b) For the input common-mode range

Lower limit

$$V_{LOW} = -0.9 + 0.4 + 0.4$$

$$V_{LOW} = -0.1V$$

Upper limit

$$V_{HIGH} = 0.9 - 0.2$$

$$V_{HIGH} = 0.7V$$

C) For the allowable range of the output voltage

Lower limit

$$V_{LOW} = -V_{SS} + V_{OV}$$

$$V_{LOW} = -0.7V$$

Upper limit

$$V_{HIGH} = V_{DD} - V_{OV}$$


$$V_{HIGH} = 0.7V$$

Problem 119

Figure P9.119 shows a bipolar op-amp circuit that resembles the CMOS op amp of Fig. 9.40. Here, the input differential pair Q_1 – Q_2 is loaded in a current mirror formed by Q_3 and Q_4 . The second stage is formed by the current-source-loaded common-emitter transistor Q_5 . Unlike the CMOS circuit, here there is an output stage formed by the emitter follower Q_6 . The function of capacitor C_C will be explained later, in Chapter 11. All transistors have $\beta = 100$, $|V_{BE}| = 0.7$ V, and $r_o = \infty$.

(a) For inputs grounded and output held at 0 V (by negative feedback, not shown) find the emitter currents of all transistors.

 (b) Calculate the gain of the amplifier with $R_L = 1$ k Ω .



a) Finding the emitter currents

$$I_{E1} = I_{E2} = 0.2 \text{ mA}$$

$$I_{E3} = I_{E4} \approx 0.2 \text{ mA}$$

$$I_{E5} \approx 0.5 \text{ mA}$$

Since the output is held at 0V

$$I_{E6} = 1 \text{ mA}$$

b) Calculating the gain

$$r_e = \frac{V_T}{I_E}$$

$$r_{e1} = r_{e2} = \frac{25 \text{ mV}}{0.2 \text{ mA}} = 125 \Omega$$

$$r_{e5} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$r_{e6} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

The gain for the first stage

$$G_{m1} = g_{m1} = \frac{1}{r_{e1}} = 8 \text{ mA/V}$$

$$A_{1st} = G_{m1}(\beta + 1)r_{e5}$$

$$A_{1st} = 40.4 \text{ V/V}$$

For the second stage

The common-emitter

$$A_5 = g_{m5}R_{e5} \cong \frac{-\beta R_L}{r_{e5}}$$

$$A_5 = \frac{-100 \times 1k}{50}$$

$$A_5 = -2000 \text{ V/V}$$

For the emitter follower

$$A_6 \approx 1$$

$$A_{2nd} = A_5 \times A_6$$

$$A_{2nd} = -2000 \text{ V/V}$$

$$A_{total} = A_{1st} \times A_{2nd}$$

$$A_{total} = -80800$$


Problem 9.124

Figure P9.124 shows a three-stage amplifier in which the stages are directly coupled. The amplifier, however, utilizes bypass capacitors, and, as such, its frequency response falls off at low frequencies. For our purposes here, we shall assume that the capacitors are large enough to act as perfect short circuits at all signal frequencies of interest.

(a) Find the dc bias current in each of the three transistors. Also find the dc voltage at the output. Assume $|V_{BE}| = 0.7V$, $\beta = 100$, and neglect the Early effect.

(b) Find the input resistance and the output resistance.

 (c) Use the current-gain method to evaluate the voltage gain v_o/v_i .



a) Calculating the voltage of the node and Applying KVL

$$V_x = \frac{10V \times 33k}{33k + 68k} = 3.3V$$

$$33k || 68k = 22.2k$$

$$I_{E1} = \frac{3.3 - 0.7}{4.7k + \frac{22.2k}{101}}$$

$$I_{E1} = 0.53 \text{ mA}$$

$$I_{C1} = 0.52 \text{ mA}$$

$$V_{C1} = 5 - 0.52 \text{ mA} \times 8.2k = 0.74V$$

$$I_{E2} = \frac{5 - 0.7 - 0.74}{3.3k}$$

$$I_{E2} = 1.07 \text{ mA}$$

$$I_{C2} = 1.06 \text{ mA}$$

$$V_{C2} = 1.06 \text{ mA} \times 5.6k - 5 = 0.94V$$

$$v_o = 0.94 - 0.7 = 0.24$$

$$I_{E3} = \frac{0.24 - (-5)}{2.4k}$$

$$I_{E3} = 2.2mA$$

$$I_{C3} = 2.1mA$$

b) The input and output resistance

$$R_{in} = 68k || 33k || r_{\pi 1}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{20.8 m} = 4.8 k\Omega$$

$$R_{in} = 3.95 k\Omega$$

$$R_{out} = 2.4k || \left(r_{e3} + \frac{5.6k}{\beta + 1} \right)$$

$$R_{out} = 2.4k || \left(11.4 + \frac{5.6k}{101} \right)$$

$$R_{out} = 65.3 \Omega$$

c) The voltage gain

$$\frac{I_{C1}}{v_i} = g_{m1} = 20.8 mA/V$$

$$\frac{I_{b2}}{I_{C1}} = \frac{8.2k}{8.2k + r_{\pi 2}} = \frac{8.2k}{8.2k + 2.4k} = 0.77$$

$$\frac{I_{C2}}{I_{b2}} = \beta = 100$$

$$\frac{I_{b3}}{I_{C2}} = \frac{5.6k}{5.6k + (\beta + 1)(r_{e3} + 2.4k)} = 0.02248$$

$$\frac{I_{e3}}{I_{b3}} = \beta + 1 = 101$$

$$v_o = I_{e3} \times 2.4k$$

$$\frac{v_o}{v_i} = 2.4k \times 101 \times 0.02248 \times 100 \times 0.77 \times 20.8$$

$$\frac{v_o}{v_i} = 8730 V/V$$