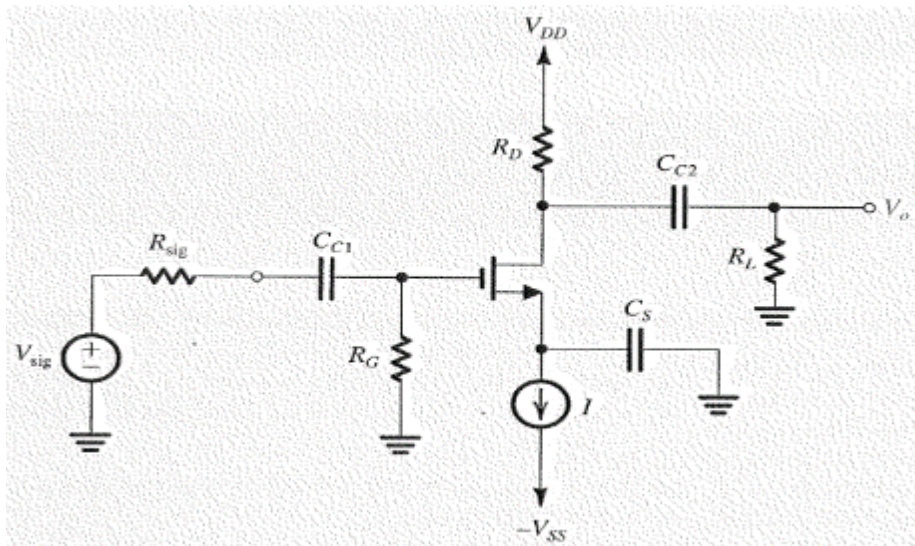


ECE 523/421 - Analog Electronics: University of New Mexico

Problem 10.6

Figure P10.6 shows a CS amplifier biased by a constant-current source I . Let $R_{sig} = 0.5\text{ M}\Omega$, $R_G = 2\text{ M}\Omega$, $g_m = 3\text{ mA/V}$, $R_D = 20\text{ k}\Omega$, and $R_L = 10\text{ k}\Omega$. Find A_m . Also, design the coupling and bypass capacitors to locate the three low-frequency poles at 100 Hz, 10 Hz, and 1 Hz. Use a minimum total capacitance, with the capacitors specified only to a single significant digit. What value of f_L results?



Finding A_m

$$A_m = -\left(\frac{R_g}{R_{sig} + R_g}\right) g_m (R_D || R_L)$$

$$A_m = -\left(\frac{2M}{0.5M + 2M}\right) 3\text{ mA/V} (20k || 10k)$$

$$A_m = -16$$

Finding the capacitances

$$f_{lp1} = \frac{1}{2\pi(R_{sig} + R_g)C_{C1}} = \frac{1}{2\pi(2.5M)C_{C1}}$$

$$C_{C1} = \frac{1}{2\pi(2.5M)1} = 63.7\text{ nF}$$

$$f_{lp2} = \frac{1}{2\pi(R_D + R_L)C_{C2}} = \frac{1}{2\pi(30k)C_{C2}}$$

$$C_{C2} = \frac{1}{2\pi(30k)10} = 531 \text{ nF}$$

$$f_{lp3} = \frac{1}{2\pi(1/g_m)C_s}$$

$$C_s = \frac{1}{2\pi\left(1/3 \text{ mA/V}\right)100} = 4.77 \text{ }\mu\text{F}$$

$$f_L = 100 + 10 + 1 = 111 \text{ Hz}$$

Problem 10.52

An amplifier with a dc gain of 60 dB has a single-pole, high-frequency response with a 3-dB frequency of 100 kHz.

- Give an expression for the gain function $A(s)$.
- Sketch Bode diagrams for the gain magnitude and phase.
- What is the gain–bandwidth product?
- What is the unity-gain frequency?
- If a change in the amplifier circuit causes its transfer function to acquire another pole at 1 MHz, sketch the resulting gain magnitude and specify the unity-gain frequency. Note that this is an example of an amplifier with a unity-gain bandwidth that is different from its gain–bandwidth product.

a) For the gain function

$$A(s) = \frac{A_m}{1 + \frac{s}{w_H}}$$

$$60 \text{ dB} = 20 \log A_m$$

$$A_m = 1000$$

$$f_H = \frac{1}{2\pi CR}$$

$$w_H = \frac{1}{CR} = 2 \times 10^5 \pi$$

$$A(s) = \frac{1000}{1 + \frac{s}{2\pi \times 100 \text{ kHz}}}$$

c) Gain-Bandwidth

$$GBW = f_T = 1000 \times 100 \text{ kHz}$$

$$GBW = 100 \text{ MHz}$$


d) Unity-gain frequency

$$f_T = 1000 \times 100 \text{ kHz}$$

$$\text{Unity gain frequency } f_T = 100 \text{ MHz}$$

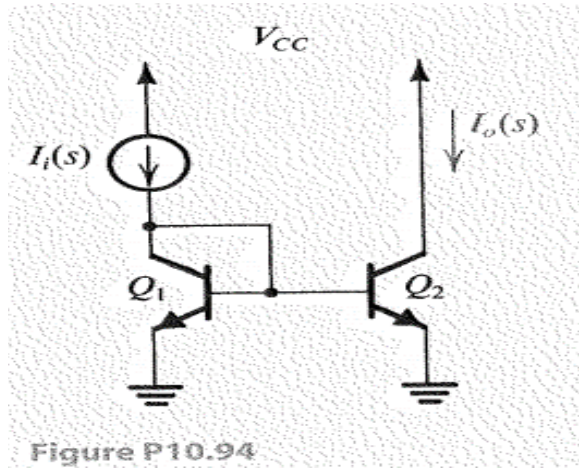Problem 10.94

For the current mirror in Fig. P10.94, derive an expression for the current transfer function $I_o(s)/I_i(s)$ taking into account the BJT internal capacitances and neglecting r_x and r_o . Assume the BJTs to be identical. Observe that a signal ground appears at the collector of Q_2 . If the mirror is biased at 1 mA and the BJTs at this operating point are characterized by $f_T = 500$ MHz, $C_{\mu} = 2$ pF, and $\beta_0 = 100$, find the frequencies of the pole and zero of the transfer function.



From the small signal model

$$V_{\pi} = \frac{I_i(s)}{\left(\frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{\pi 2}}\right) + s(C_{\pi 1} + C_{\pi 2} + C_{\mu 2})}$$

$$I_o(s) = g_{m2}V_{\pi} - sC_{\mu 2}V_{\pi}$$

$$\frac{I_o(s)}{I_i(s)} = \frac{g_{m2} - sC_{\mu 2}}{\left(\frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{\pi 2}}\right) + s(C_{\pi 1} + C_{\pi 2} + C_{\mu 2})}$$

Frequency of the zero

$$g_{m2} - sC_{\mu 2} = 0$$

$$f_{pz} = \frac{g_{m2}}{2\pi C_{\mu 2}}$$

$$g_{m2} = \frac{I_c}{V_t} = 40 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_{m2}} = 2.5 \text{ k}\Omega$$

$$f_{pz} = \frac{40 \text{ mA/V}}{2\pi(2 \times 10^{-12})} = 3.18 \text{ GHz}$$

$$f_T = \frac{g_m}{2\pi(C_{\Pi} + C_{\mu})}$$

$$C_{\Pi} = 10.7 \text{ pF}$$

Pole

$$\left(\frac{1}{r_{\Pi 1}} + \frac{1}{r_{\Pi 2}}\right) + s(C_{\Pi 1} + C_{\Pi 2} + C_{\mu 2}) = 0$$

$$f_p = \frac{\frac{2}{r_{\pi}} + g_m}{2\pi(C_{\Pi 1} + C_{\Pi 2} + C_{\mu 2})}$$


$$f_p = \frac{\frac{2}{2500} + 40 \text{ mA/V}}{2\pi(10.7 + 10.7 + 2) \times 10^{-12}}$$

$$f_p = 277.5 \text{ MHz}$$

Problem 10.106

Figure P10.106 shows an amplifier formed by cascading two CS stages. Note that the input bias voltage is not shown. Each of Q_1 and Q_2 is operated at an overdrive voltage of 0.2 V, and $|V_A| = 10$ V. The transistor capacitances are as follows: $C_{gs} = 20$ fF, $C_{gd} = 5$ fF, and $C_{db} = 5$ fF. The signal-source resistance $R_{sig} = 10$ k Ω .

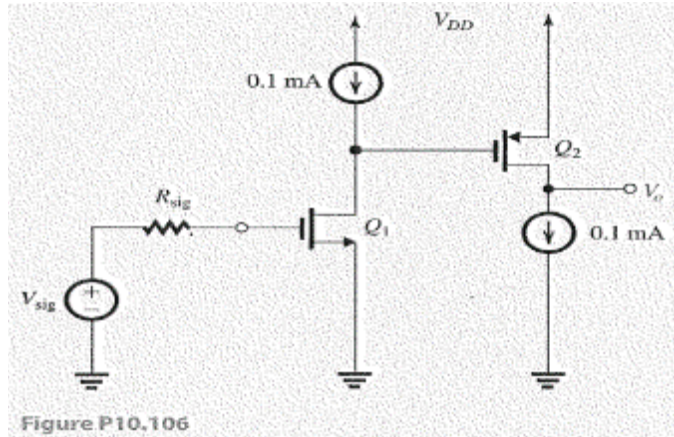- Find the dc voltage gain.
- Use the method of open-circuit time constants to determine an estimate for the 3-dB frequency f_H .



a) DC voltage gain

$$g_{m1} = g_{m2} = \frac{2 I_D}{V_{OV}} = 1 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{V_A}{I_D} = 100 \text{ k}\Omega$$

$$\frac{v_o}{v_{sig}} = g_{m1} r_{o1} \times g_{m2} r_{o2}$$

$$\frac{v_o}{v_{sig}} = 10000$$

b) Finding the high frequency

$$f_{p1} = \frac{1}{2\pi[C_{gs1} + C_{gd1}(1 + g_{m1}r_{o1})]R_{sig}}$$

$$f_{p1} = 30.32 \text{ MHz}$$

$$f_{p2} = \frac{1}{2\pi[C_{gd1} + C_{db1} + C_{gd2}(1 + g_{m2}r_{o2}) + C_{gs2}]r_{o1}}$$

$$f_{p2} = 2.97 \text{ MHz}$$

$$f_{p3} = \frac{1}{2\pi[C_{gd2} + C_{db2}]r_{o2}}$$

$$f_{p3} = 159 \text{ MHz}$$

$$\frac{1}{f_H} = \frac{1}{f_{p1}} + \frac{1}{f_{p2}} + \frac{1}{f_{p3}}$$

$$f_H = 2.66 \text{ MHz}$$