

ECE 523/421 – Analog Electronics

Lecture 1: Introduction to Analog Electronics

Payman Zarkesh-Ha

Office: ECE Bldg. 230B


Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Textbook and Background

- ❑ **Main reference material is your notes in the class and the handouts**
- ❑ **The main textbook is:**
 - A. Sedra and K. Smith, "Microelectronic Circuits", 7th edition, Oxford University Press, 2014, ISBN-978-0199339136
- ❑ **Lecture Notes: combination of slides, homework and announcements**
 - Slides will be posted on the class webpage
 - Class webpage: www.unm.edu/~pzarkesh/ECE523

Textbooks and Outline

 

- Basic CMOS Amplifiers
- Basic BJT Amplifiers
- Cascode Amplifiers
- Current Mirrors
- Differential Amplifiers
- Frequency Response
- Feedback Analysis
- Stability Analysis with Feedback
- Frequency Compensation
- Power Amplifiers

Grading Policy

- ❑ Your grade in the course will be comprised of:

ECE523 and ECE421 Students

- Homework (20%)
 - Design Project (20%)
 - Tests (30%)
 - Final Exam (30%)
- ❑ There will be 2 midterm tests, but only 1 will be considered and the worst test will be ignored. Therefore, there is no makeup tests or exams.
 - ❑ Final letter grade will be based on curve and class performance
 - ❑ Your participation in class is very important
 - ❑ Suggestions for success:
 - Participate in the class and ask questions
 - Read the textbook
 - Work on problems

Homework Policy

- ☐ Homework will be assigned for each week. Please refer to the class website for the homework assignments.
- ☐ Homework due at the beginning of the lecture. No exception!
- ☐ Solutions will be posted on the class website as soon as it is available.
- ☐ Late homework and projects will not be accepted

Course Project

- ☐ **There will be design project assigned including:**
 - **Circuit Design at the transistor level**
 - **SPICE simulation to confirm functionality and measure specs**
 - **No layout is needed for this project**
- ☐ **The design problem will be an individual project.**
- ☐ **Project grade will be based on:**
 - **Quality of report**
 - **Meeting all the required specifications**
 - **Simplicity, yet reliability**
- ☐ **There will be a 10% extra credit for any design that is selected as the best project based on the opinion of an external reviewer.**

Course Objectives



- ☐ Design of advanced analog electronic circuits.
- ☐ BJT and MOSFET operational amplifiers.
- ☐ BJT and MOSFET current mirrors and output stages.
- ☐ Frequency response and compensation.
- ☐ Feedback and stability.

Class Schedule


Warning: Lecture schedule subject to change!!

Date	Day	Topic	Reading/Coverage
August 18	Mon	Introduction to Analog Electronics	Handout
August 20	Wed	Review of Basic MOSFET Amplifiers I	5.2 - 5.4
August 25	Mon	Review of Basic MOSFET Amplifiers II	7.1 - 7.5 (CMOS)
August 27	Wed	Review of Basic BJT Amplifiers I	6.2 - 6.4
September 1	Mon	Labor Day	-
September 3	Wed	Review of Basic BJT Amplifiers II	7.1 - 7.5 (BJT)
September 8	Mon	Analog IC Building Blocks: Basic Gain Cells	8.1 - 8.2
September 10	Wed	Analog IC Building Blocks: Cascode Amplifier	8.3
September 15	Mon	Analog IC Building Blocks: Current Sources	8.4
September 17	Wed	Analog IC Building Blocks: Improved Current Mirrors	8.5
September 22	Mon	Analog IC Building Blocks: Transistor Pairings	8.6
September 24	Wed	Differential Amplifiers: MOS Differential Pair	9.1
October 29	Mon	Differential Amplifiers: Small Signal Operation	9.2
October 1	Wed	Midterm Exam #1	-
October 6	Mon	Differential Amplifiers: BJT Differential Pair	9.3
October 8	Wed	Differential Amplifiers: Nonideal Characteristics	9.4
October 13	Mon	Differential Amplifiers: with Active Loads	9.5 - 9.6
October 15	Wed	Frequency Response: Low-frequency Response	10.1
October 20	Mon	Frequency Response: High-frequency Device Models	10.2
October 22	Wed	Frequency Response: High-frequency Response	10.3
October 27	Mon	Frequency Response: Useful Tools for HF Analysis	10.4.3 & 10.5
October 29	Wed	Frequency Response: Examples (CG & Cascode)	10.6
November 3	Mon	Frequency Response: More Examples	10.9 & 10.10
November 5	Wed	Midterm Exam #2	-
November 10	Mon	Feedback: Introduction	11.1
November 12	Wed	Feedback: Negative Feedback Properties	11.2
November 17	Mon	Feedback: Stability Analysis using Bode Plots	11.12
November 19	Wed	Feedback: Frequency Compensation	11.13
November 24	Mon	Output Stages: Power Amplifiers	12.1 - 12.6
November 26	Wed	Basic Analog Systems: ADC and DAC Circuits	Handout
December 1	Mon	Op-Amp Design Concepts	13.1 - 13.3
December 3	Wed	Class Final Review	-
December 10	Wed	Final Exam (3:00-5:00PM)	-

 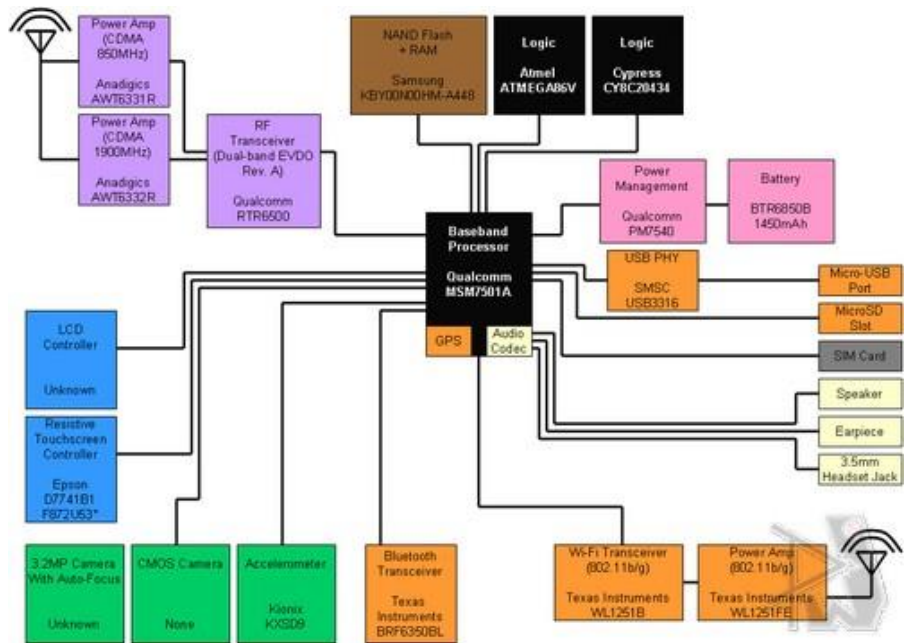
Example of an Analog ICs in HTC Touch Pro



 
Example of an Analog ICs in Motorola Droid



Example of an Analog ICs in a DVD Drive

 


Intel's Microprocessor Evolution

 

Intel386™

 
Transistor Count: 280 thousand
Frequency: 16 MHz
Cores: 1
Cache Size: None
I/O Peak Bandwidth: 64 MB/sec
Adaptive Circuits: None



Nehalem

731 million
>3.6 GHz
4
8 MB
50 GB/sec
Sleep Mode
Turbo Mode
Power Gating
Adaptive Frequency Clocking

Analog Subcircuits in 45nm Nehalem CPU


 


- 23 master DLL circuits
- 11 PLL circuits
- 5 digital thermal sensors
- 4 arrays of sense amplifiers for cache

Review of MOSFET Amplifiers


- ☐ **Concepts of:**
 - **Load Line**
 - **Static Resistance**
 - **Dynamic Resistance**
- ☐ **MOSFET I-V Characteristics**
- ☐ **MOSFET Circuits at DC**

Concept of Load Line, Dynamic and Static R

  

NMOS I-V Characteristics

Table 5.1 Regions of Operation of the Enhancement NMOS Transistor

 

- $v_{GS} < V_{in}$: no channel; transistor in cut-off; $i_D = 0$
- $v_{GS} = V_{in} + v_{OV}$: a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched-off at the drain end;

Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{in}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left(\frac{W}{L}\right) \left[(v_{GS} - V_{in}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left(\frac{W}{L}\right) \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{in}$$

or equivalently:

$$v_{DS} \geq v_{OV}$$


Then

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (v_{GS} - V_{in})^2$$

or equivalently,


$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) v_{OV}^2$$

Concept of V_{OV} and V_{DS-MIN} in NMOS

 

How about PMOS?


Dynamic D/S Resistance in Triode Region

 

D/S Resistance in Triode Region:

$$r_{DS} = \frac{1}{K'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)}$$


Channel Length Modulation Effect

 

$$1) \quad r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

$$2) \quad V_A \propto L \Rightarrow r_o \propto L$$

Large Signal MOSFET Model in Saturation

 

Output Resistance in Saturation:


$$r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

Notes:

 - 1) For DC analysis, we normally assume $\lambda \approx 0$.
- 2) It is easier to think of overdrive voltages for DC analysis.

MOSFET Circuits at DC: Example 1

Design the following circuit, so that the transistor operates at $I_D = 0.4$ mA and $V_D = +0.5$ V. The NMOS transistor has $V_t = 0.7$ V, $K'_n = 100$ $\mu\text{A}/\text{V}^2$, $L = 1$ μm , and $W = 32$ μm . Neglect the channel-length modulation effect.



MOSFET Circuits at DC: Example 2

D5.9 For the circuit in Fig. E5.9, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_{tn} = 0.5$ V, $\mu_n C_{ox} = 0.4$ mA/V², $W/L = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}$, and $\lambda = 0$.

Ans. 13.9 k Ω

 


Figure E5.9

D5.10 Figure E5.10, shows a circuit obtained by augmenting the circuit of Fig. E5.9 considered in Exercise 5.9 with a transistor Q_2 identical to Q_1 and a resistance R_2 . Find the value of R_2 that results in Q_2 operating at the edge of the saturation region. Use your solution to Exercise 5.9.

Ans. 20.8 k Ω


 


Figure E5.10


MOSFET Circuits at DC: Example 3

 Analyze the circuit shown below to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1\text{ V}$ and $K'_n(W/L) = 1\text{ mA/V}^2$. What is the largest value that R_D can have while the transistor remains in the saturation mode.



MOSFET Circuits at DC: Example 4

 Design the circuit shown below so that the transistor operates in saturation with $I_D = 0.5 \text{ mA}$ and $V_D = +3 \text{ V}$. Let $V_{tp} = -1 \text{ V}$ and $K'_p(W/L) = 1 \text{ mA/V}^2$. What is the largest value that R_D can have while the transistor remains in the saturation mode?



MOSFET Circuits at DC: Example 5

For the circuit below, find the value of R that results in the PMOS transistor operating with an overdrive voltage $|V_{OV}| = 0.6$ V. The threshold voltage is $V_{tp} = -0.4$ V, the process transconductance parameter $K'_p = 0.1$ mA/V² and $W/L = 10\mu\text{m}/0.18\mu\text{m}$.

