

ECE 523/421 – Analog Electronics

Lecture 12: Differential Amplifiers: Small Signal Operation

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu



Review of Last Lecture

- ☐ **MOS Differential Amplifier**
- ☐ **Common Mode Input**
- ☐ **Differential Model Input**
- ☐ **Large Signal Operation**

Today's Lecture

- ☐ MOS Small Signal Differential Amplifier
- ☐ Half-Circuit Differential Mode
- ☐ Half-Circuit Common Mode
- ☐ Active Load Differential Amplifier
- ☐ CMRR


MOS Differential Gain

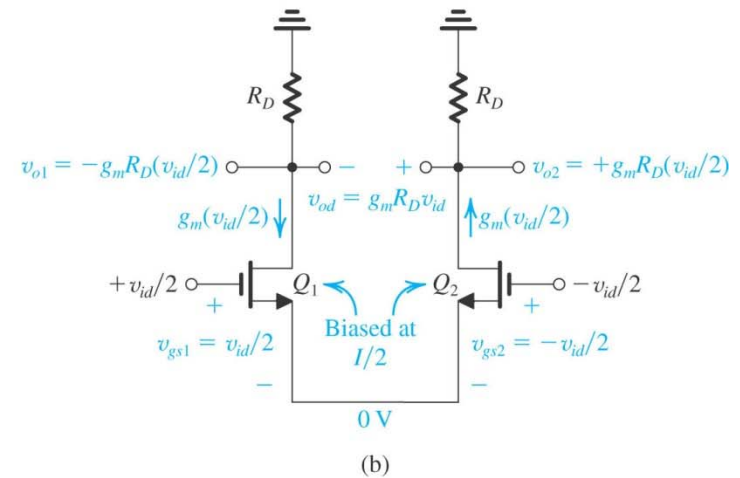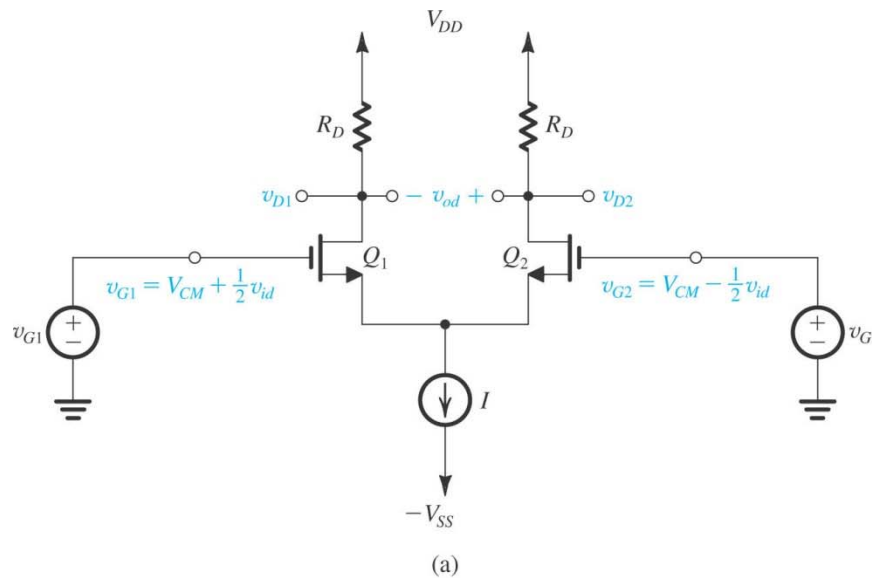

$$g_m = \frac{2I_D}{V_{OV}} = \frac{I}{V_{OV}}$$



$$A_d = \frac{v_{od}}{v_{id}} = g_m R_D$$

Differential Half-Circuit

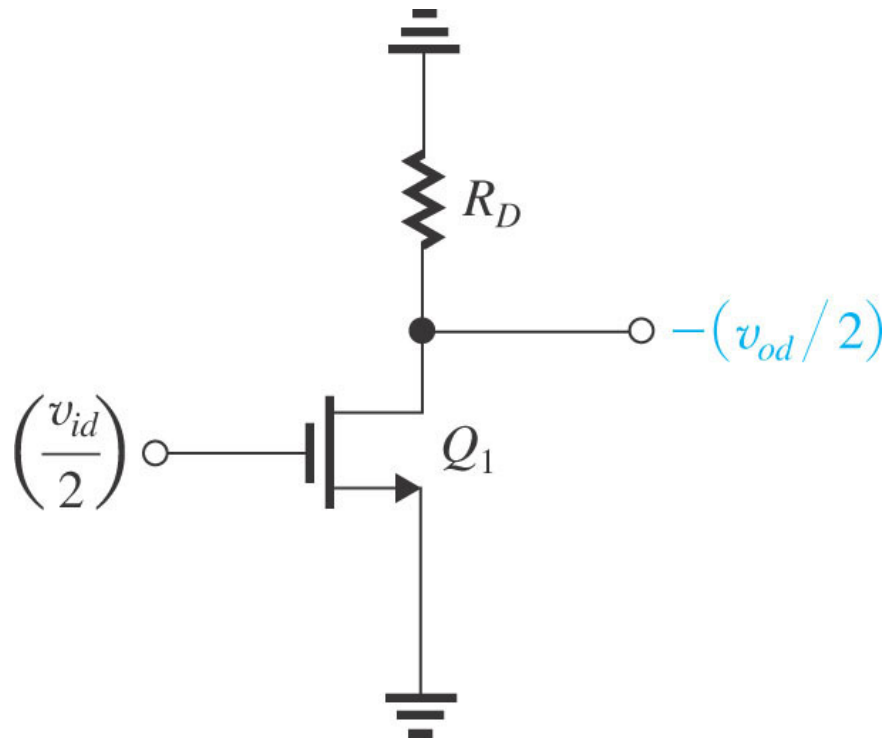

$$A_d = \frac{v_{od}}{v_{id}} = g_m (R_D \parallel r_o)$$


Example: Differential Half-Circuit

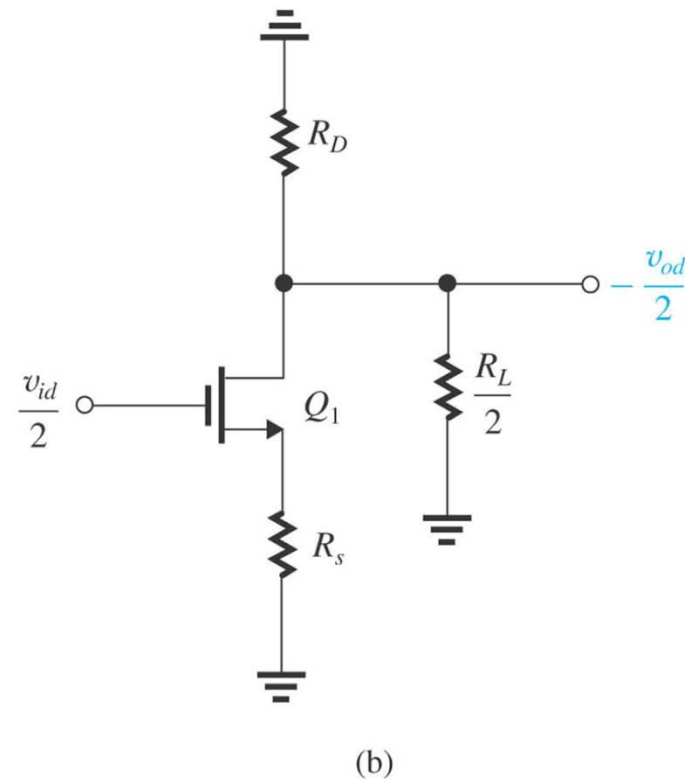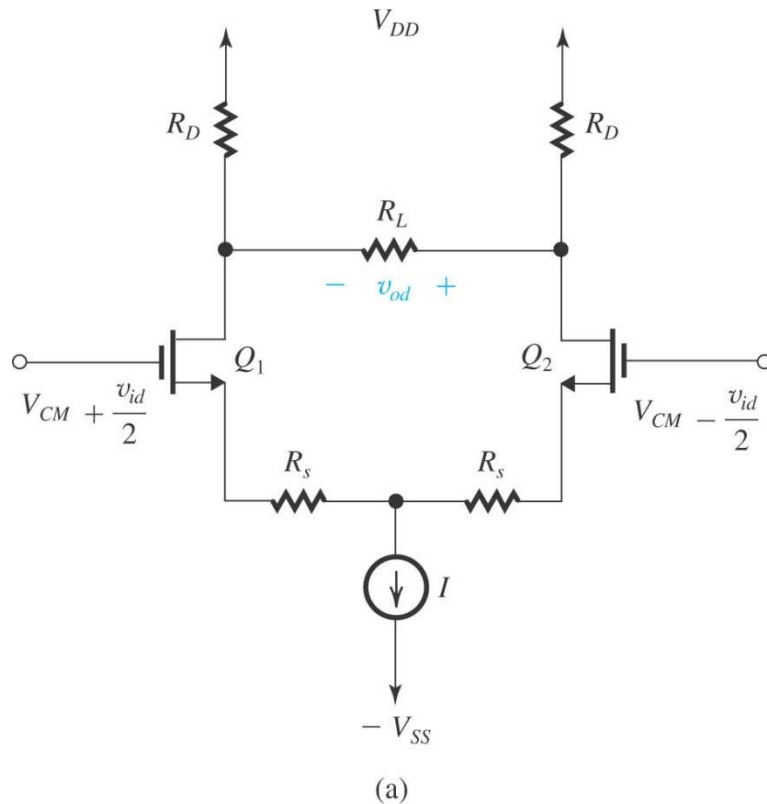


$$A_d = \frac{v_{od}}{v_{id}} = \frac{R_D \parallel (R_L/2)}{1/g_m + R_S}$$

Example: MOS Differential Amplifier

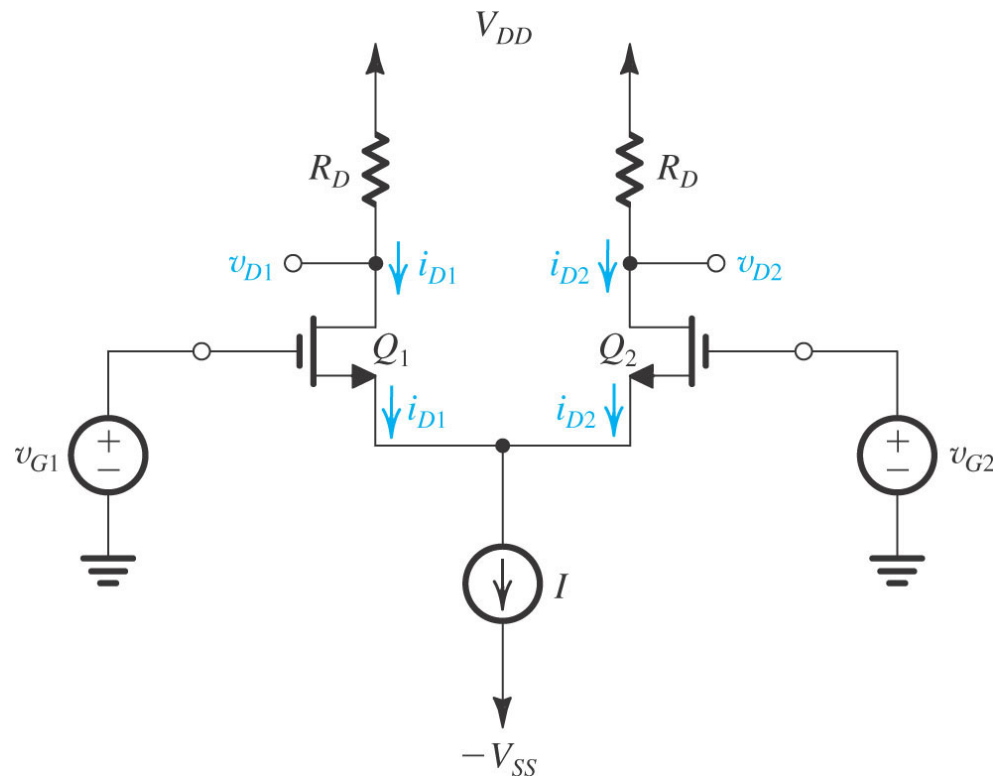- 1) Let $I=0.8\text{mA}$, $(W/L)=100$, $K'_n=0.2\text{mA/V}^2$, $V_A=20\text{V}$, $R_D=5\text{K}\Omega$. Find V_{OV} , g_m , r_o , and A_d .




Differential Amplifier with Active Load

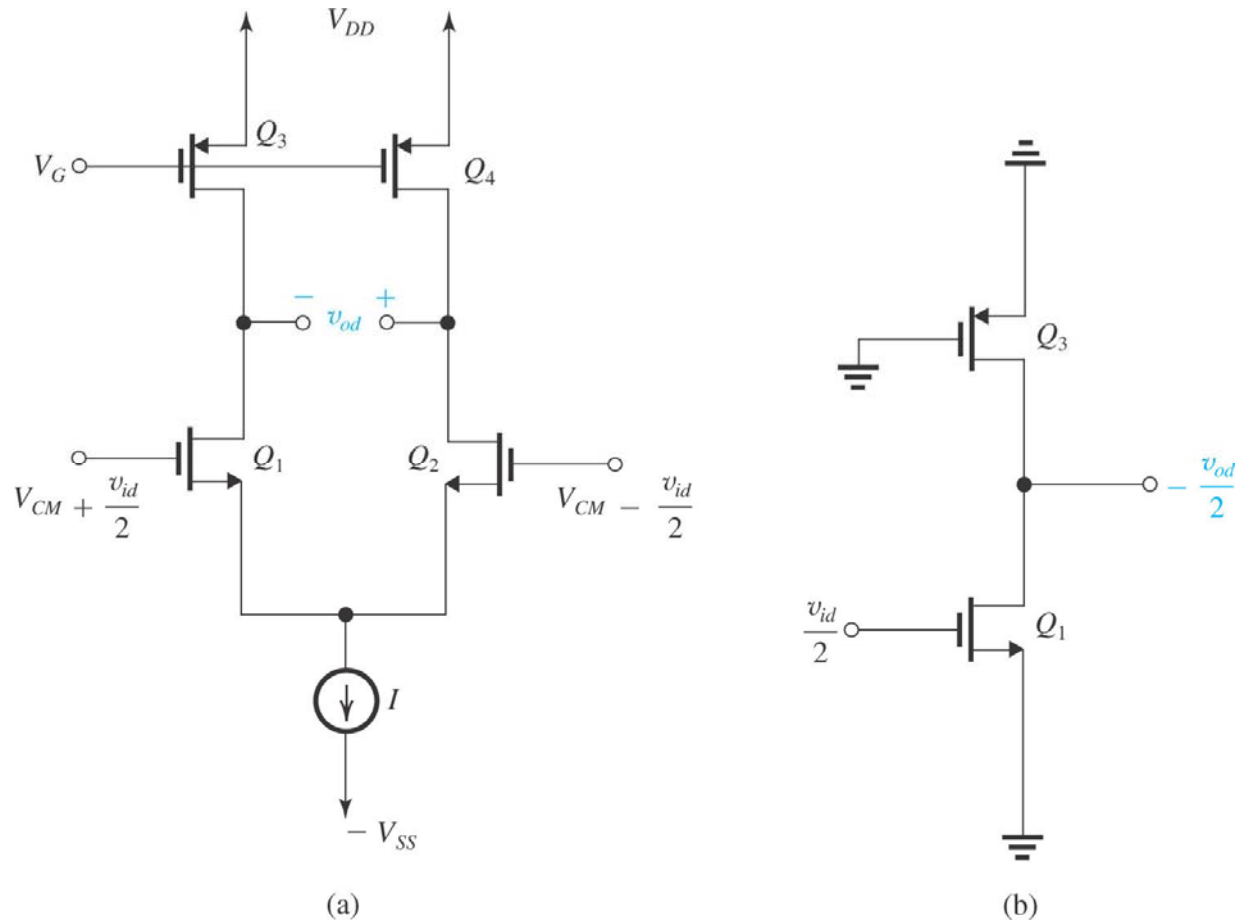


$$A_d = \frac{v_{od}}{v_{id}} = g_m (r_{o1} \parallel r_{o3})$$

Example: MOS Differential Amplifier

- 1) Let $K'_n=400\mu\text{A}/\text{V}^2$, $K'_p=100\mu\text{A}/\text{V}^2$, $|V_t|=0.5$, $|V'_A|=10\text{V}/\mu\text{m}$, $I=200\mu\text{A}$, $L=0.36\mu\text{m}$, $|V_{OV}|=0.2\text{V}$ find (W/L) and A_d .

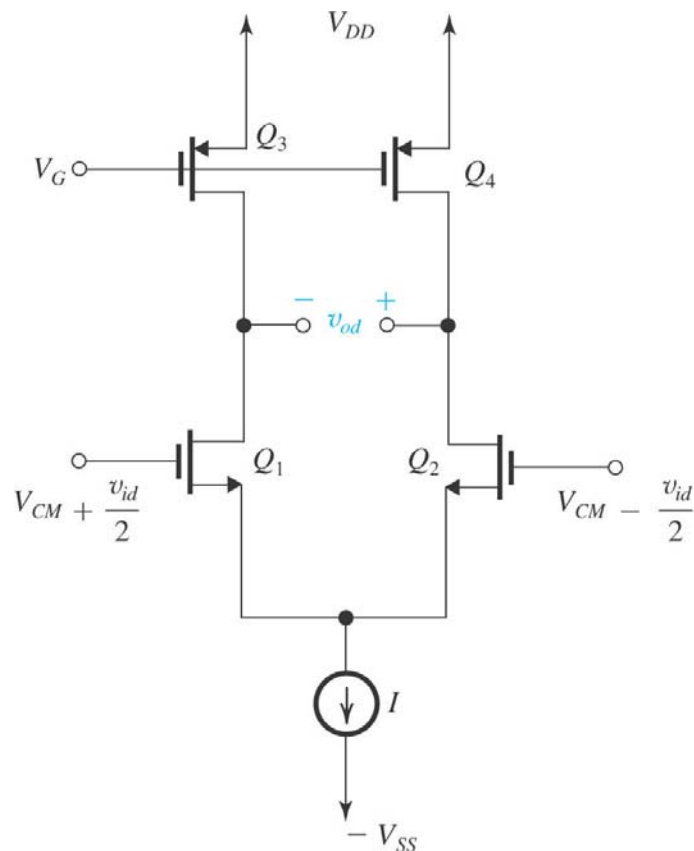


Cascode Differential Amplifier

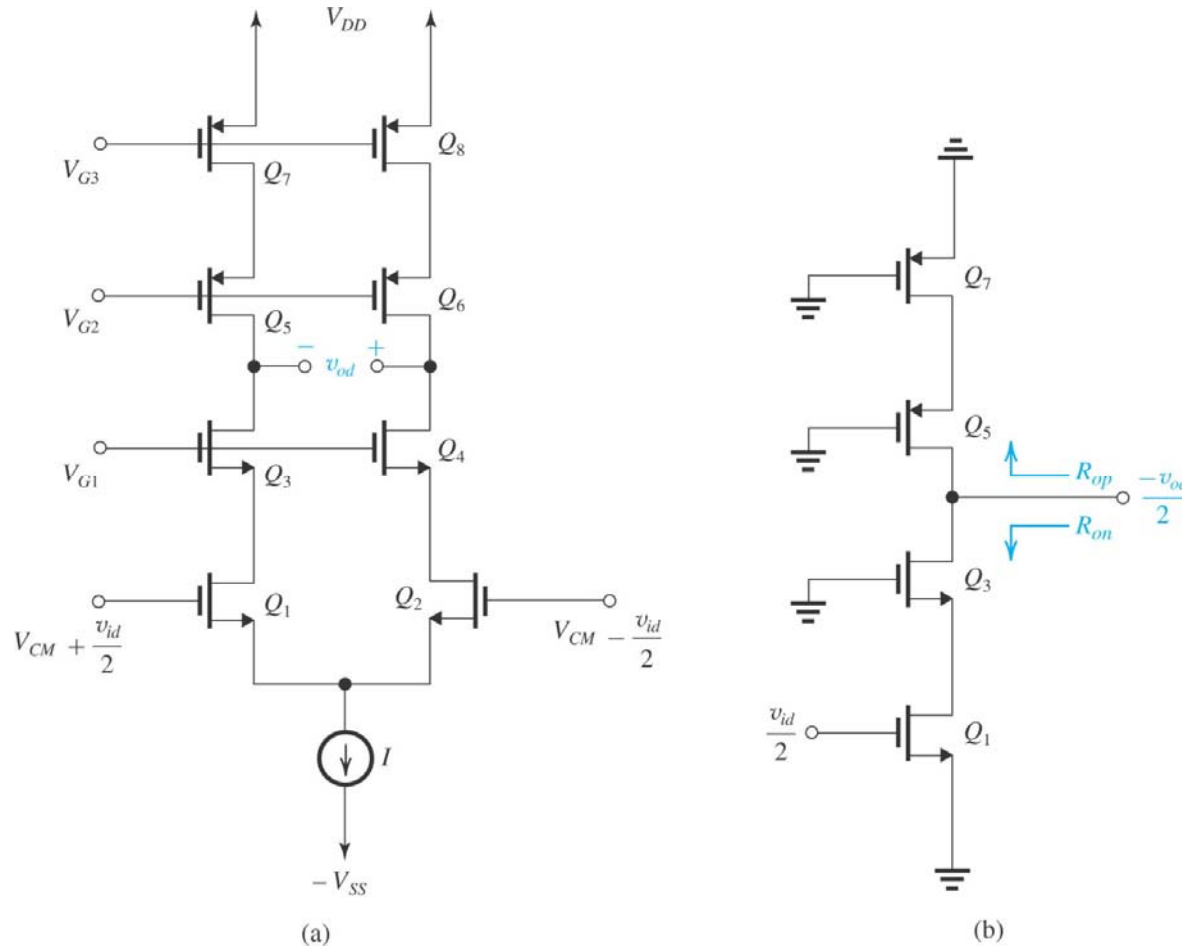



$$A_d = \frac{v_{od}}{v_{id}} = g_{m1} (R_{on} \parallel R_{op}) \quad R_{on} = (g_{m3} r_{o3}) r_{o1} \quad R_{op} = (g_{m5} r_{o5}) r_{o7}$$

Example: MOS Differential Amplifier

- 1) Let $K'_n=400\mu\text{A}/\text{V}^2$, $K'_p=100\mu\text{A}/\text{V}^2$, $|V_t|=0.5$, $|V'_A|=10\text{V}/\mu\text{m}$, $I=200\mu\text{A}$, $L=0.36\mu\text{m}$, $|V_{OV}|=0.2\text{V}$ find (W/L) and A_d .


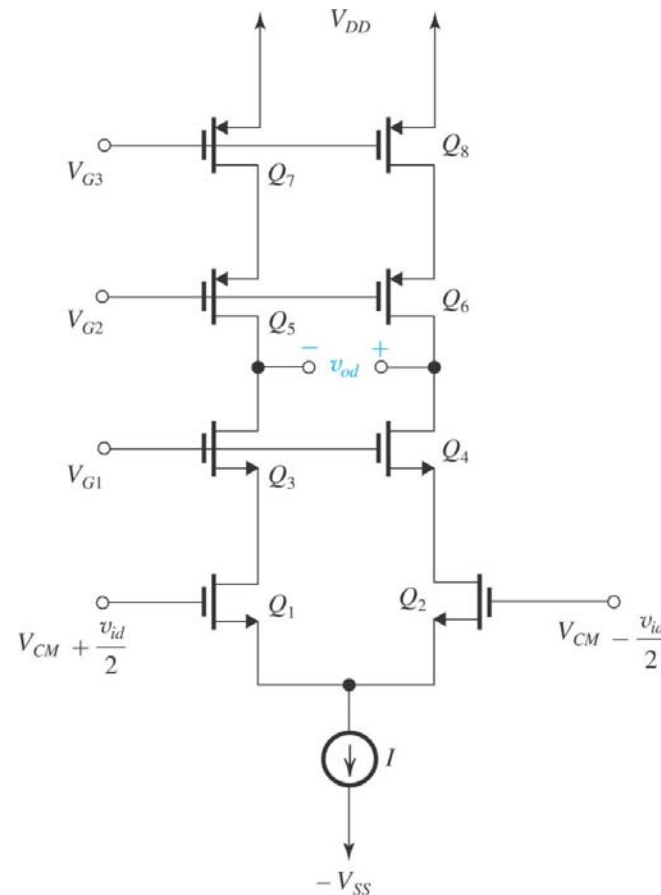


Common Mode Gain

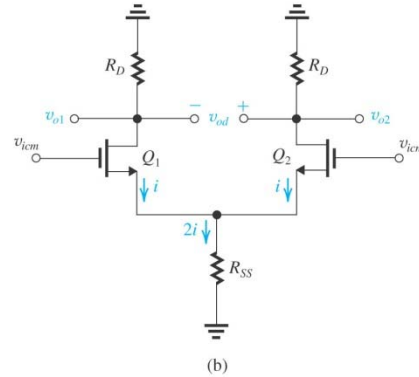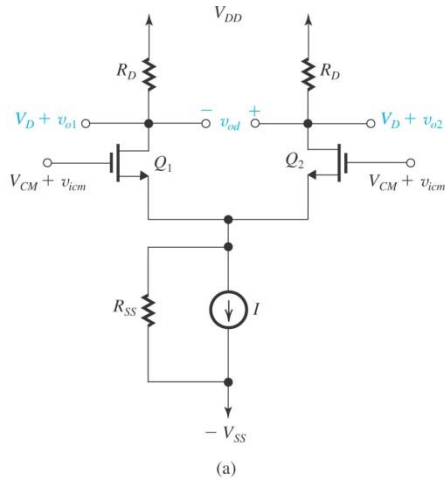

$$\frac{v_{o1}}{v_{icm}} = \frac{v_{o2}}{v_{icm}} = -\frac{R_D}{1/g_m + 2R_{SS}}$$

$$v_{od} = 0$$

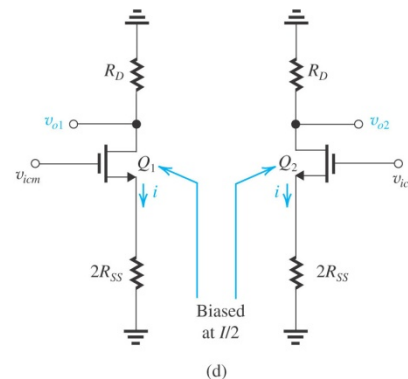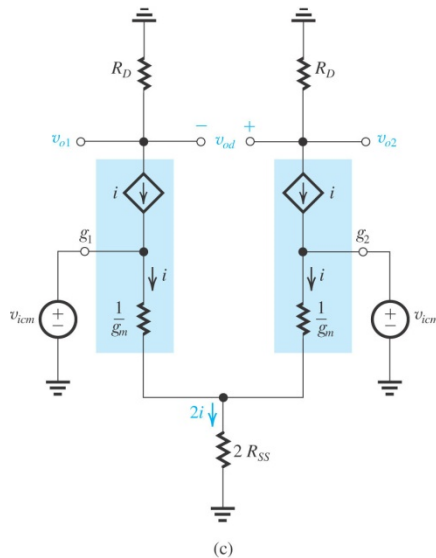

*** Assuming differential output**

R_D Mismatch and Common Mode Gain

$$\text{Ideal Case} \left\{ \begin{array}{l} \frac{V_{o1}}{V_{icm}} = \frac{V_{o2}}{V_{icm}} = -\frac{R_D}{1/g_m + 2R_{SS}} \\ V_{od} = 0 \end{array} \right.$$

$$\text{\textit{R}_D \text{ Mismatch Case}} \quad A_{cm} = \frac{V_{od}}{V_{icm}} = -\frac{R_D}{1/g_m + 2R_{SS}} \left(\frac{\Delta R_D}{R_D} \right)$$

*** Assuming differential output**

g_m Mismatch and Common Mode Gain

$$\text{Ideal Case} \left\{ \begin{array}{l} \frac{V_{o1}}{V_{icm}} = \frac{V_{o2}}{V_{icm}} = -\frac{R_D}{1/g_m + 2R_{SS}} \\ V_{od} = 0 \end{array} \right.$$

$$\text{\textit{\textbf{g}_m Mismatch Case}} \quad A_{cm} = \frac{V_{od}}{V_{icm}} = -\frac{R_D}{1/g_m + 2R_{SS}} \left(\frac{\Delta g_m}{g_m} \right)$$

*** Assuming differential output**

Common Mode Rejection Ratio

$$CMRR = \frac{|A_d|}{|A_{cm}|} \qquad CMRR(dB) = 20 \log \left(\frac{|A_d|}{|A_{cm}|} \right)$$

Examples:

**R_D Mismatch
Case**

$$CMRR = \frac{1 + 2g_m R_{SS}}{(\Delta R_D / R_D)}$$

**g_m Mismatch
Case**

$$CMRR = \frac{1 + 2g_m R_{SS}}{(\Delta g_m / g_m)}$$

*** Assuming differential output**