

ECE 523/421 – Analog Electronics

Lecture 15: Differential Amplifiers: With Active Loads

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ Offset in MOS Differential Amplifier
- ☐ Offset in BJT Differential Amplifier

Today's Lecture


- ☐ **Differential Gain of Active-Loaded MOS Pair**
- ☐ **Common Gain of Active-Loaded MOS Pair**
- ☐ **CMRR of Active-Loaded MOS Pair**
- ☐ **Differential Gain of Active-Loaded BJT Pair**
- ☐ **Common Gain of Active-Loaded BJT Pair**
- ☐ **CMRR of Active-Loaded BJT Pair**
- ☐ **Examples: Multistage Differential Amplifier**

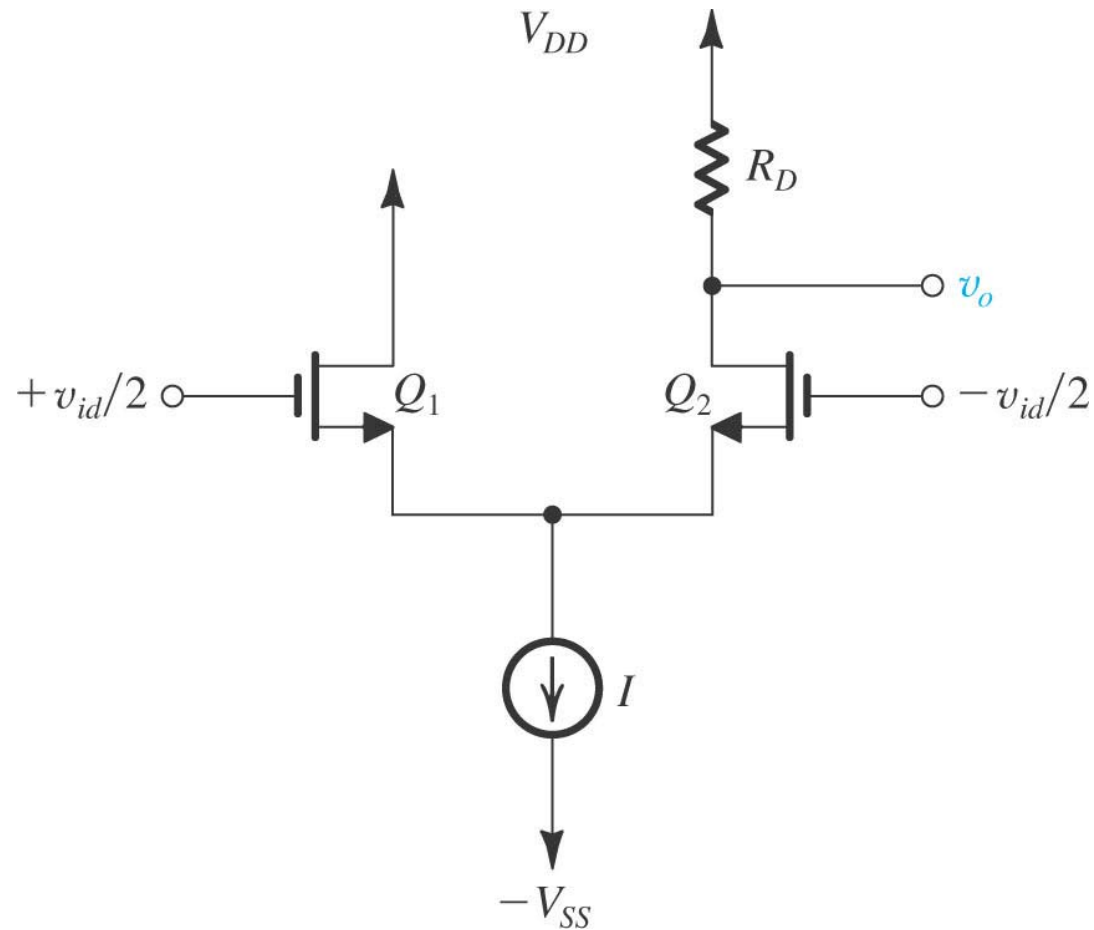Basic Differential to Single-Ended Conversion




Drain current signal on Q_1 is wasted!

Active-Loaded MOS Diff-Amp


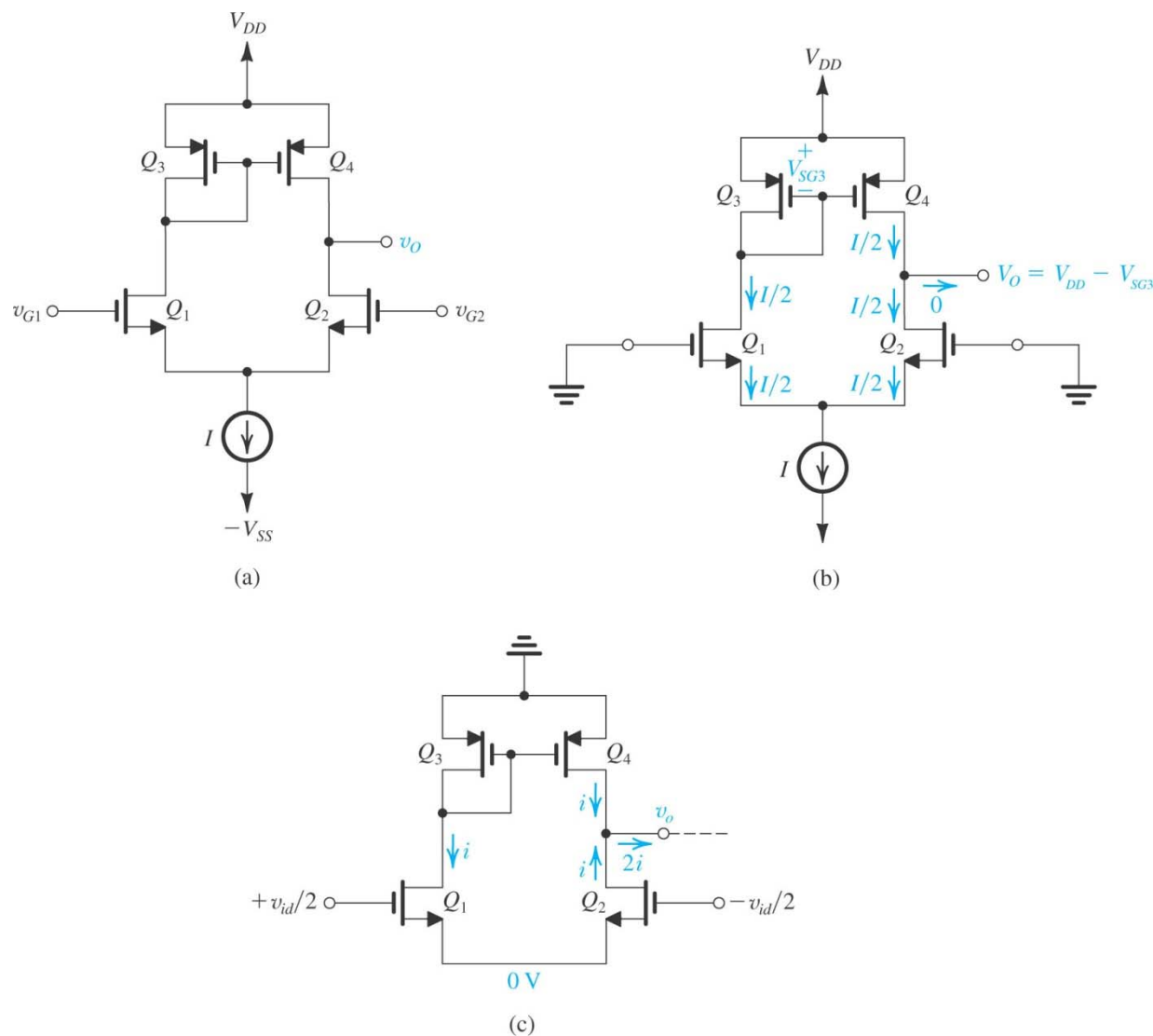


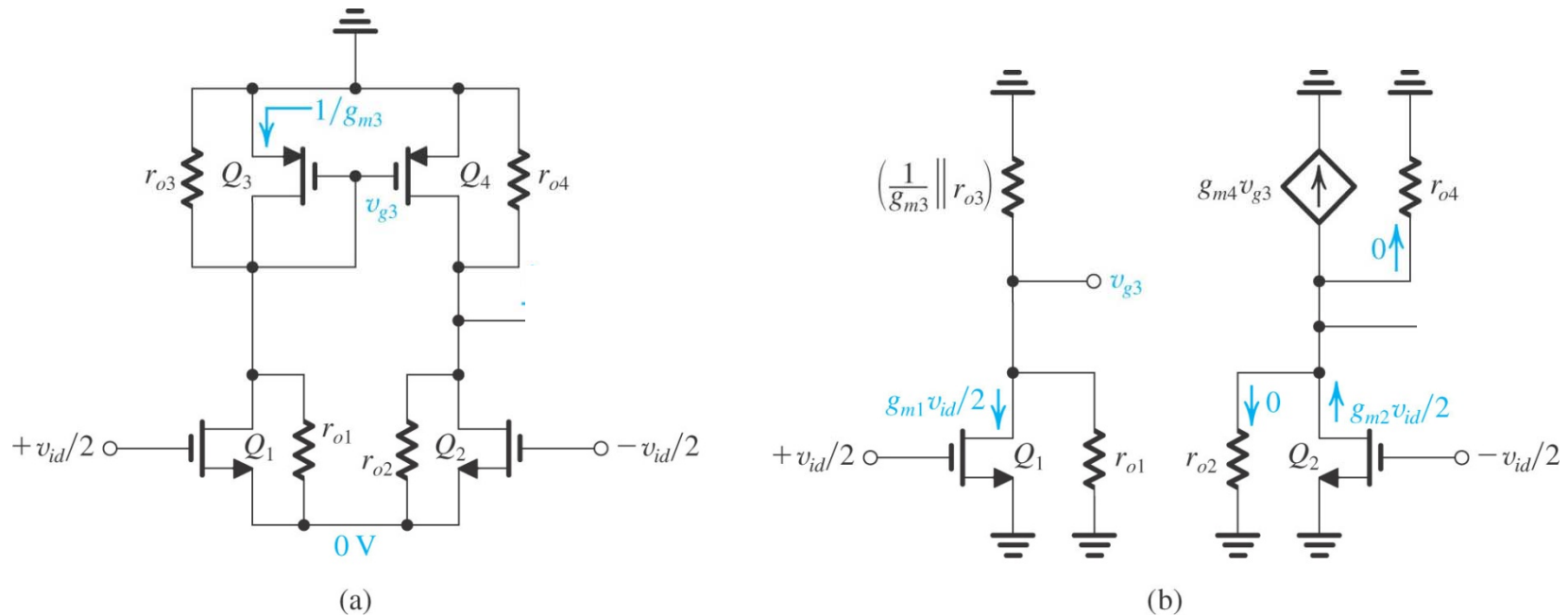Differential Gain of Active-Load MOS Pair




$$A_d = \frac{v_o}{v_{id}} \approx \left(\frac{g_{m2}}{2} + \frac{g_{m1}}{2} \frac{g_{m4}}{g_{m3}} \right) (r_{o2} \parallel r_{o4}) \approx g_m (r_{o2} \parallel r_{o4})$$

Common Gain of Active-Load MOS Pair

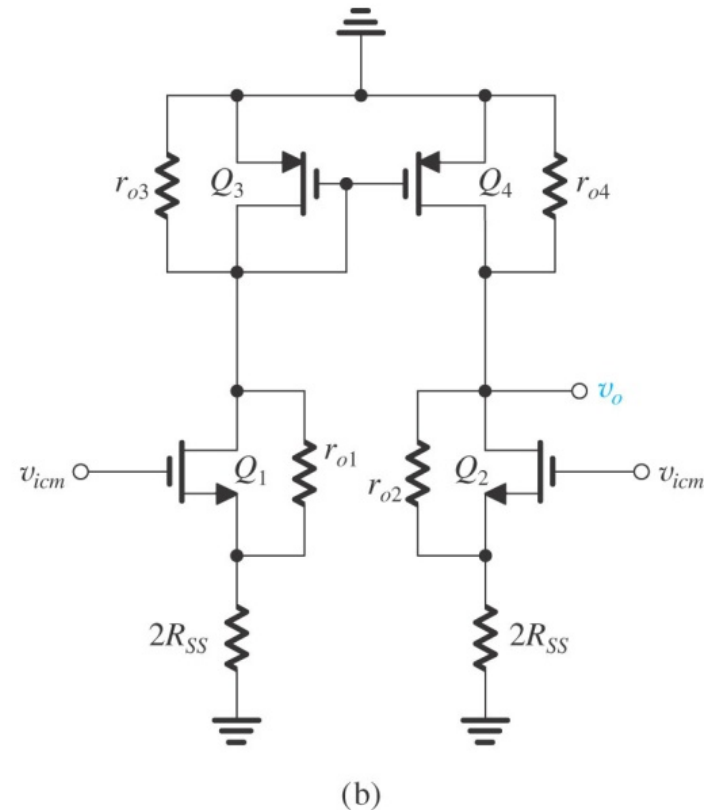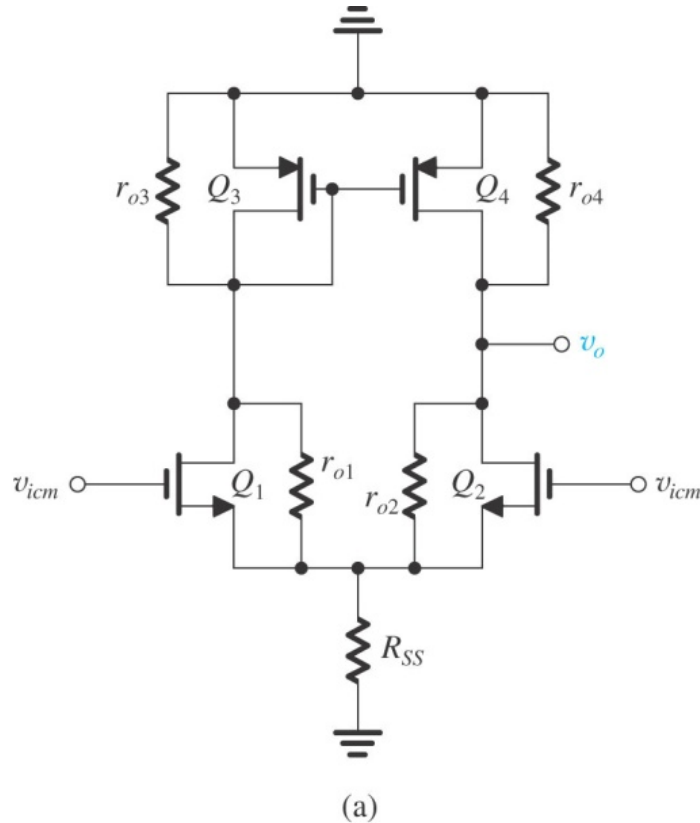


$$A_{cm} = \frac{v_o}{v_{icm}} \approx \left(\frac{1}{2R_{SS}} \left(\frac{1}{g_{m3}} \parallel r_{o3} \right) g_{m4} - \frac{1}{2R_{SS}} \right) r_{o4} \approx \frac{-1}{2g_{m3}R_{SS}}$$

CMRR of Active-Load MOS Pair

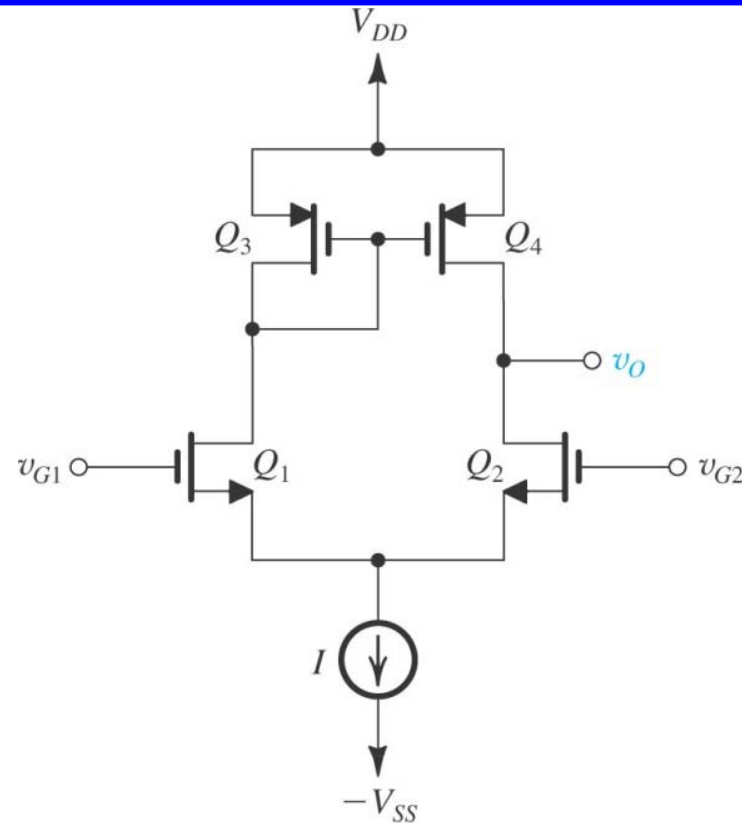

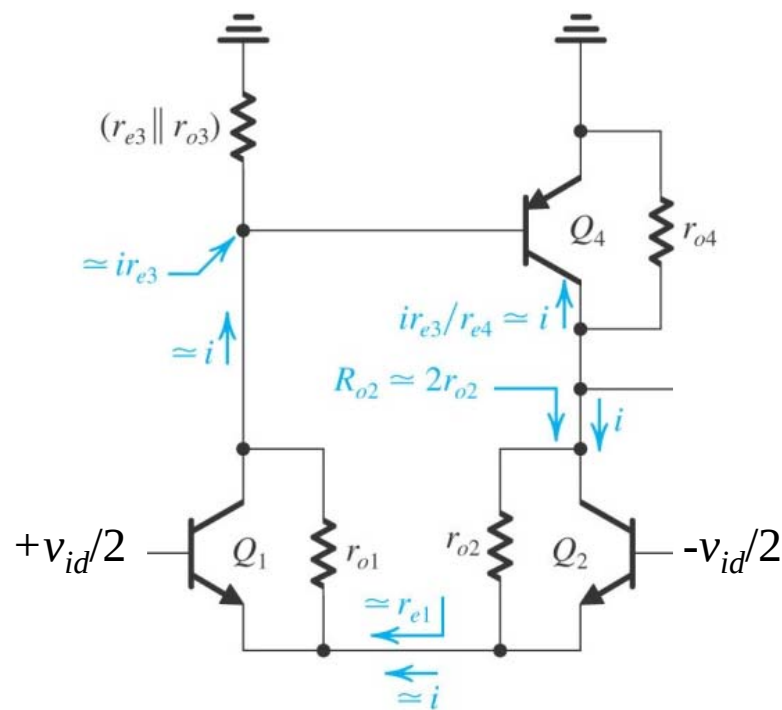
$$CMRR = \frac{A_d}{A_{cm}} \approx (g_m r_o)(g_m R_{SS})$$




$$A_d = \frac{v_o}{v_{id}} \approx \left(\frac{g_{m2}}{2} + \frac{g_{m1}}{2} \frac{g_{m4}}{g_{m3}} \right) (r_{o2} \| r_{o4}) \approx g_m (r_{o2} \| r_{o4})$$

Common Gain of Active-Load BJT Pair

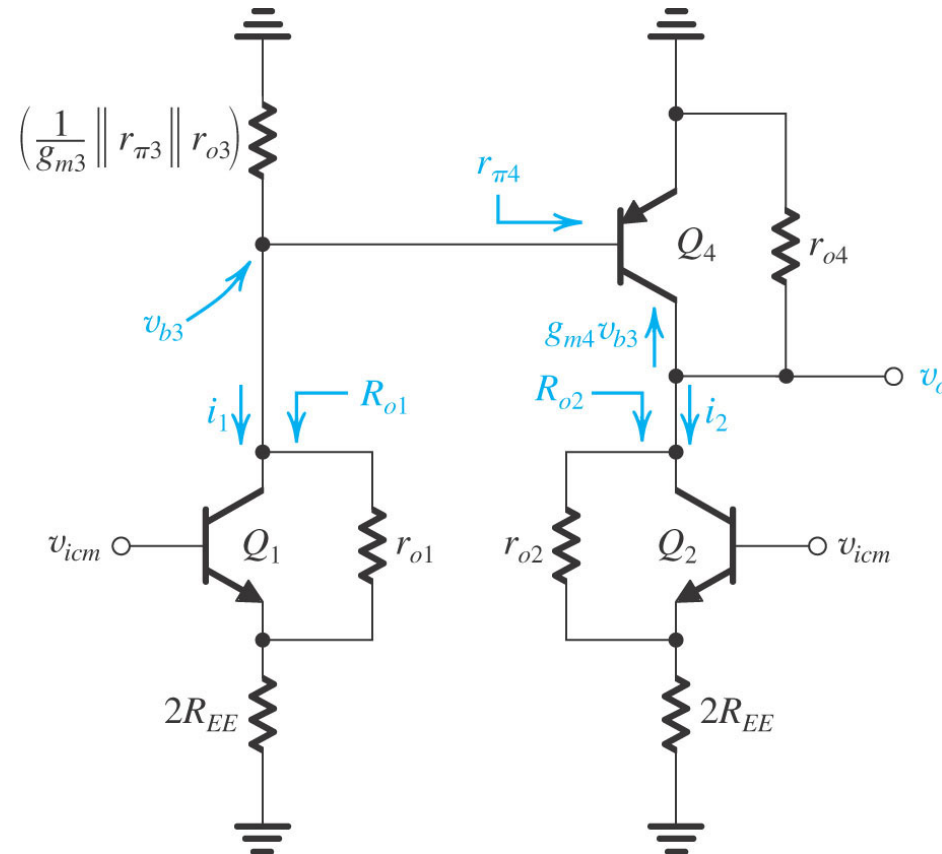


$$A_{cm} = \frac{v_o}{v_{icm}} \approx \left(\frac{1}{2R_{EE}} \left(\frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{\pi3} \parallel r_{\pi4} \right) g_{m4} - \frac{1}{2R_{EE}} \right) r_{o4} \approx \frac{-r_{o4}}{\beta_3 R_{EE}}$$

CMRR of Active-Load MOS Pair

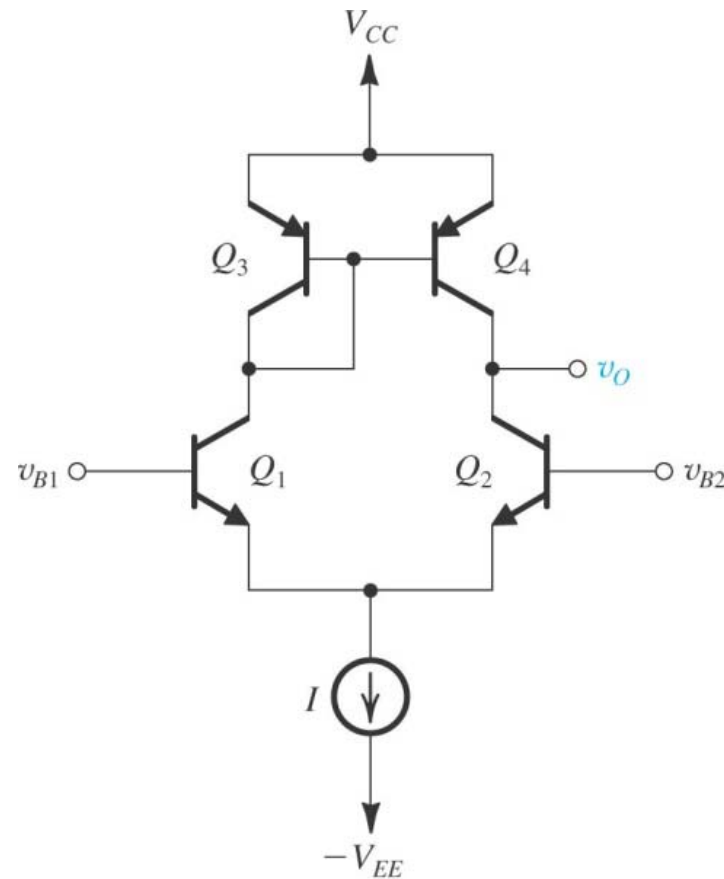


$$CMRR = \frac{A_d}{A_{cm}} \approx \frac{1}{2} \beta_3 (g_m R_{EE})$$

Example: Folded Cascode & Wilson Op Amp

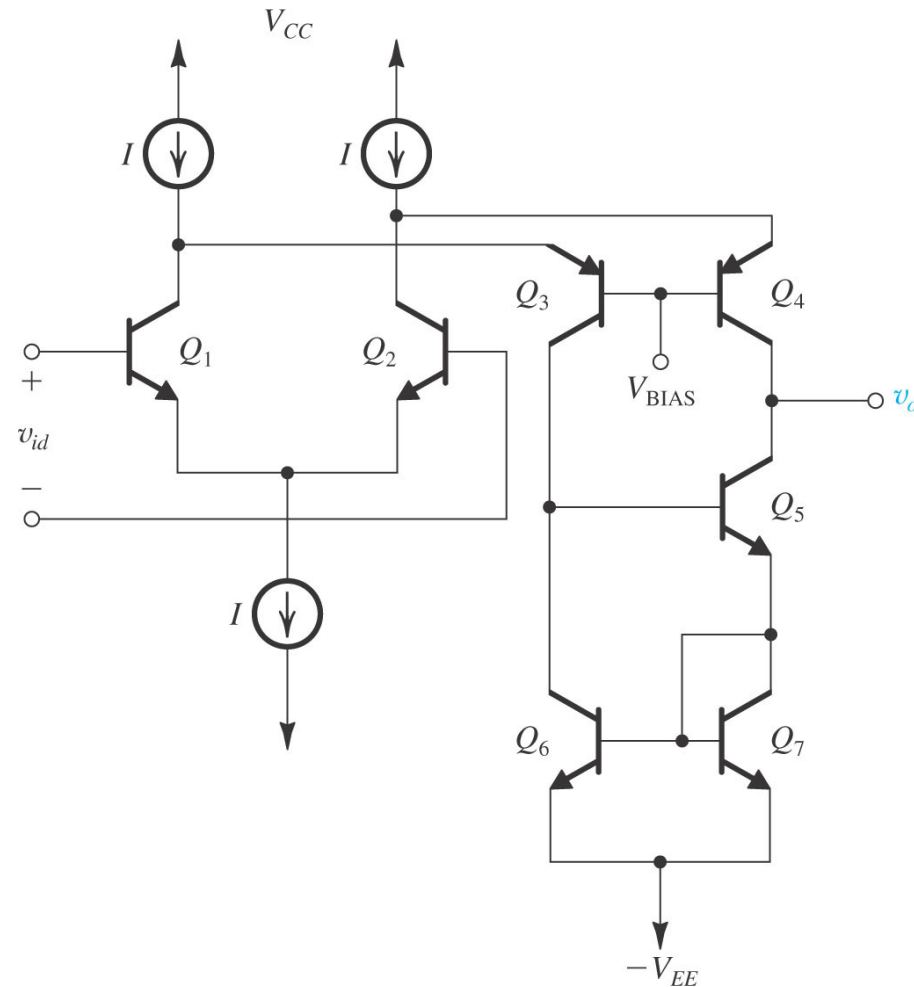


$$G = \frac{A_o}{A_{id}} \approx g_m \left(\beta_4 r_{o4} \parallel \beta_5 \frac{r_{o5}}{2} \right)$$

Example: 2-Stage CMOS Op Amp Gain

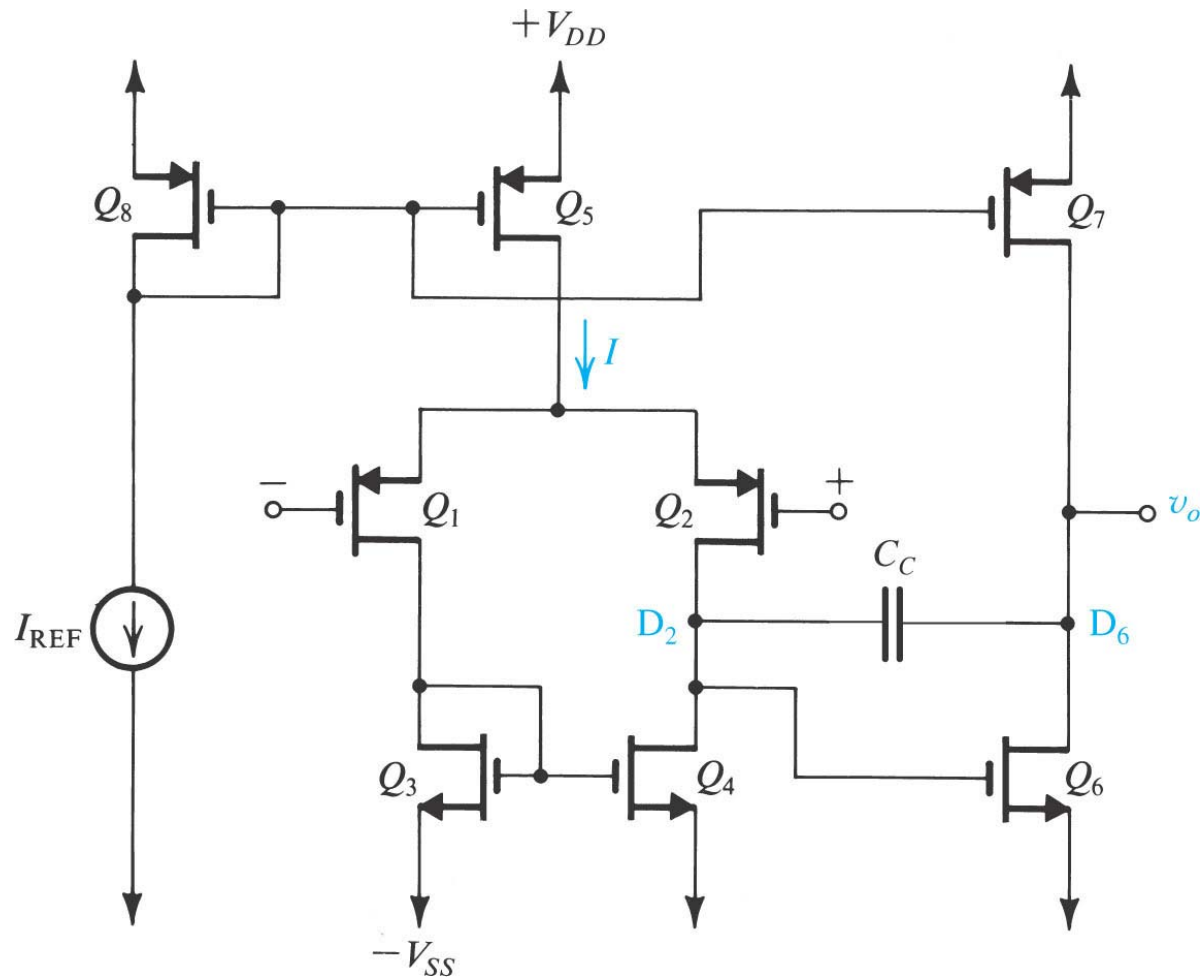


$$G = \frac{A_o}{A_{id}} \approx \left(-g_{m1} (r_{o2} \parallel r_{o4}) \right) \left(-g_{m6} (r_{o6} \parallel r_{o7}) \right)$$

Example: CMOS Op Amp Offset Cancellation

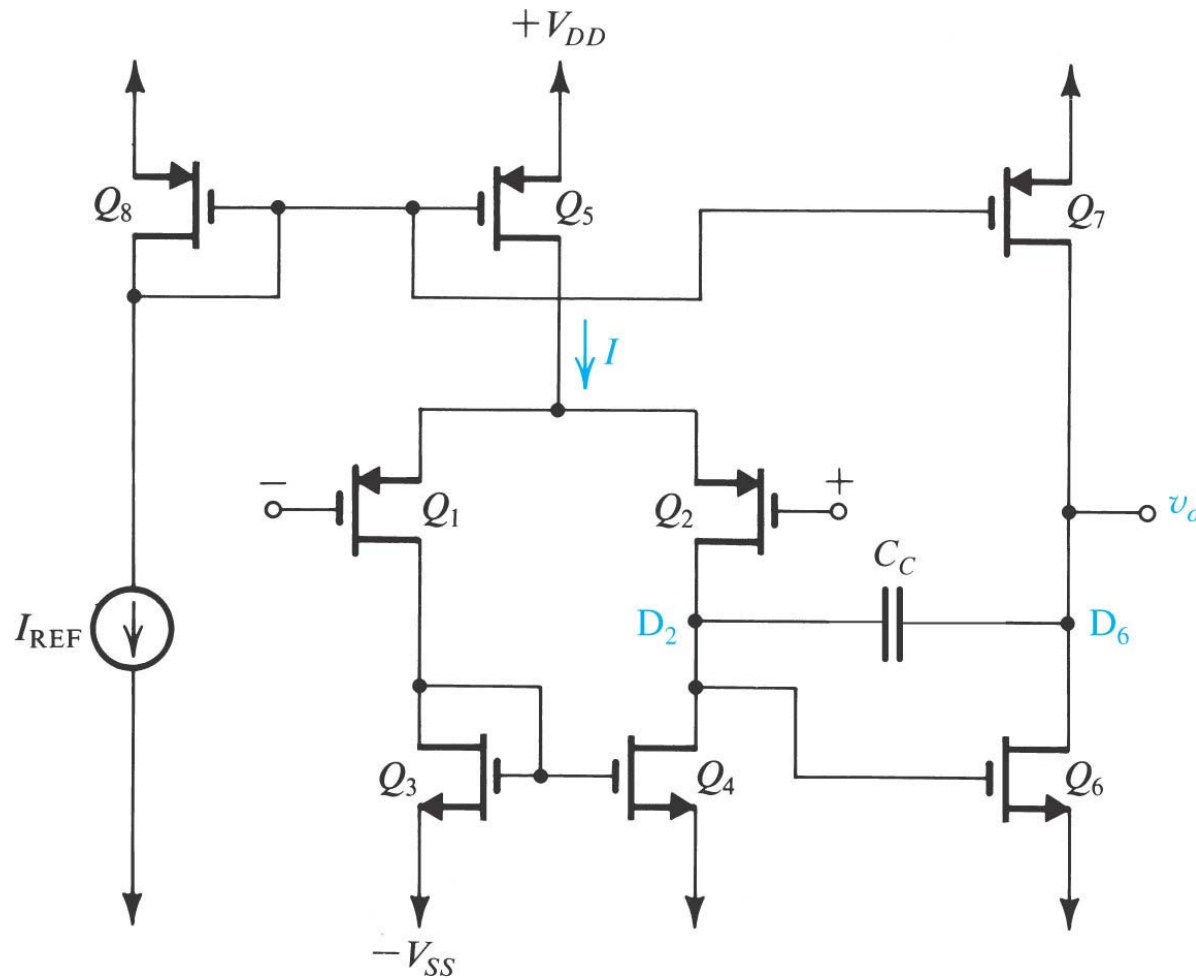


$$\frac{(W/L)_6}{(W/L)_4} = 2 \frac{(W/L)_7}{(W/L)_5}$$

Example: 4-Satge BJT Op Amp

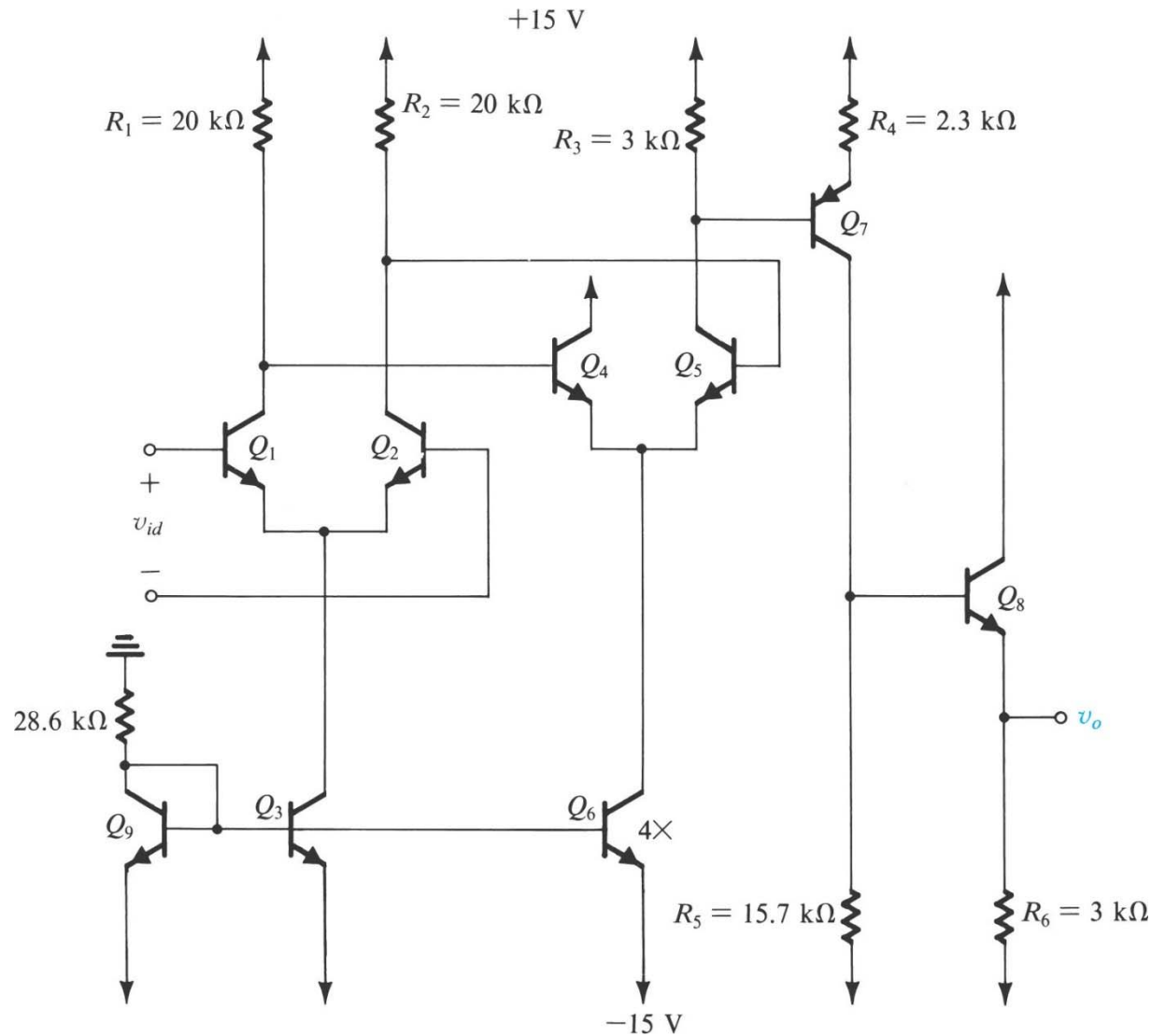

Example: 4-Satge BJT Op Amp DC Analysis

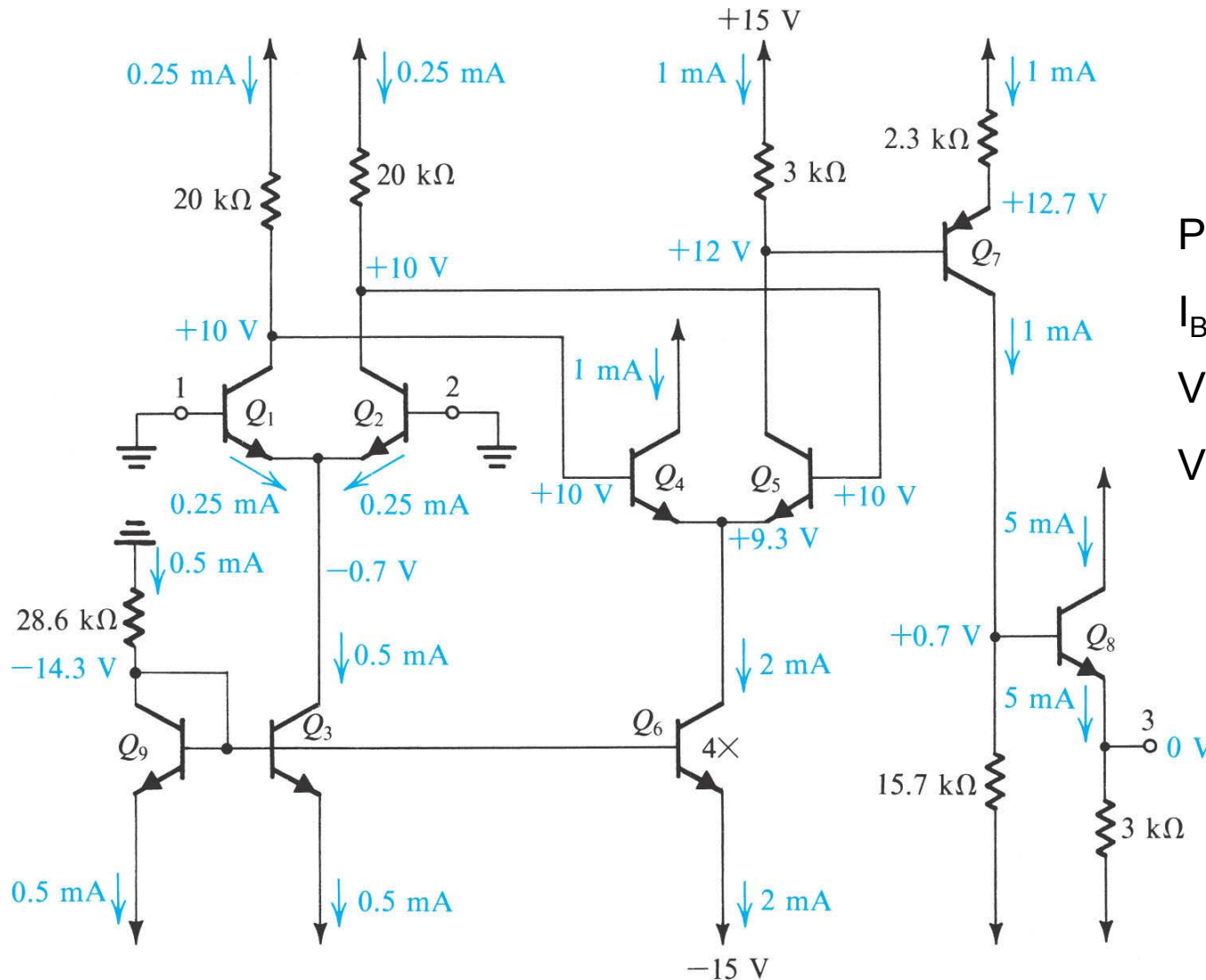


$$P_{DC} = 262.5\text{ mW}$$

$$I_B = 2.5\text{ uA}$$

$$V_{cm}(\text{max}) = +10.5\text{ V}$$

$$V_{cm}(\text{min}) = +14.1\text{ V}$$

Example: 4-Satge BJT Op Amp AC Analysis

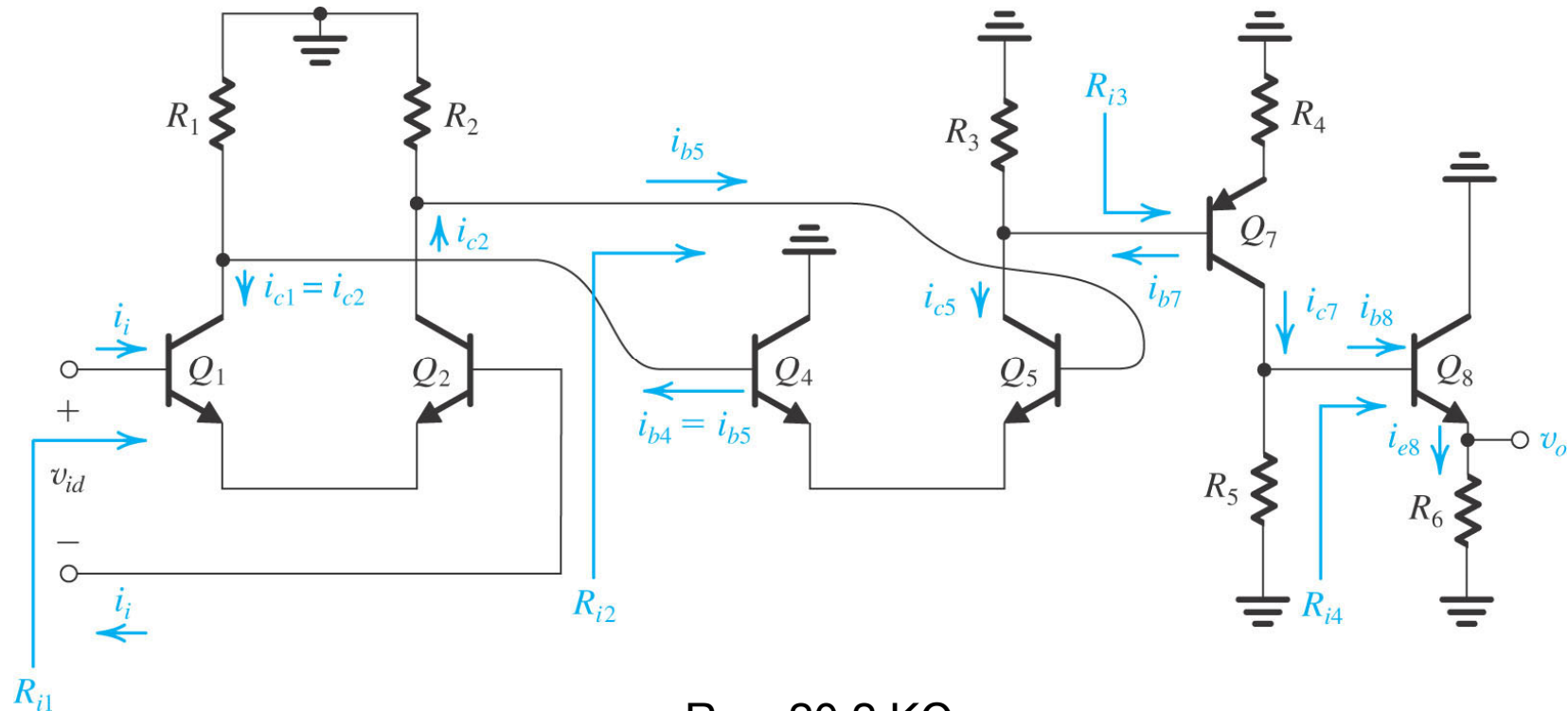

$$R_{in} = 20.2 \text{ K}\Omega$$

$$R_{out} = 152 \text{ }\Omega$$

$$A_V = 8256$$