

ECE 523/421 – Analog Electronics

Lecture 20: Frequency Response: Examples of HF Analysis (CG & Cascode)

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ Open-circuit time constants to approximate f_H
- ☐ Miller Theorem

Today's Lecture


- ☐ High frequency analysis of CG Circuit
- ☐ High frequency analysis of MOS Cascode Circuit
- ☐ High frequency analysis of BJT Cascode Circuit

High Frequency Analysis of CG Circuit

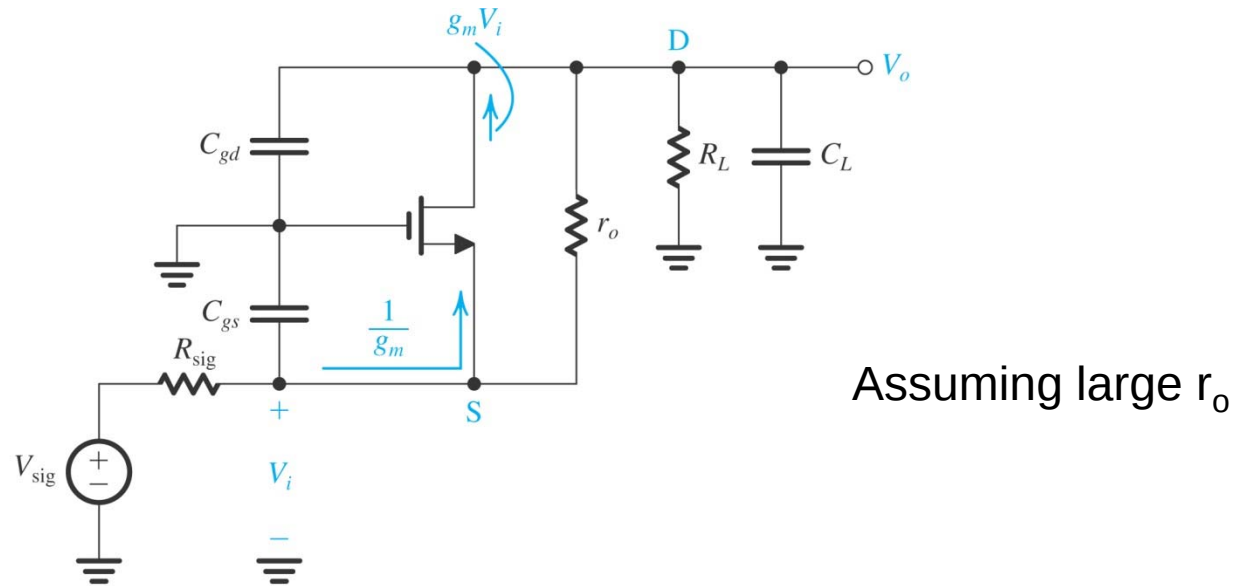

$$f_H \approx \frac{1}{2\pi} \frac{1}{\sum_i R_{i0} C_i} = \frac{1}{2\pi} \frac{1}{C_{gs} \left(R_{sig} \parallel \frac{1}{g_m} \right) + (C_{gd} + C_L)(R_L)}$$

High Frequency Analysis of MOS Cascode

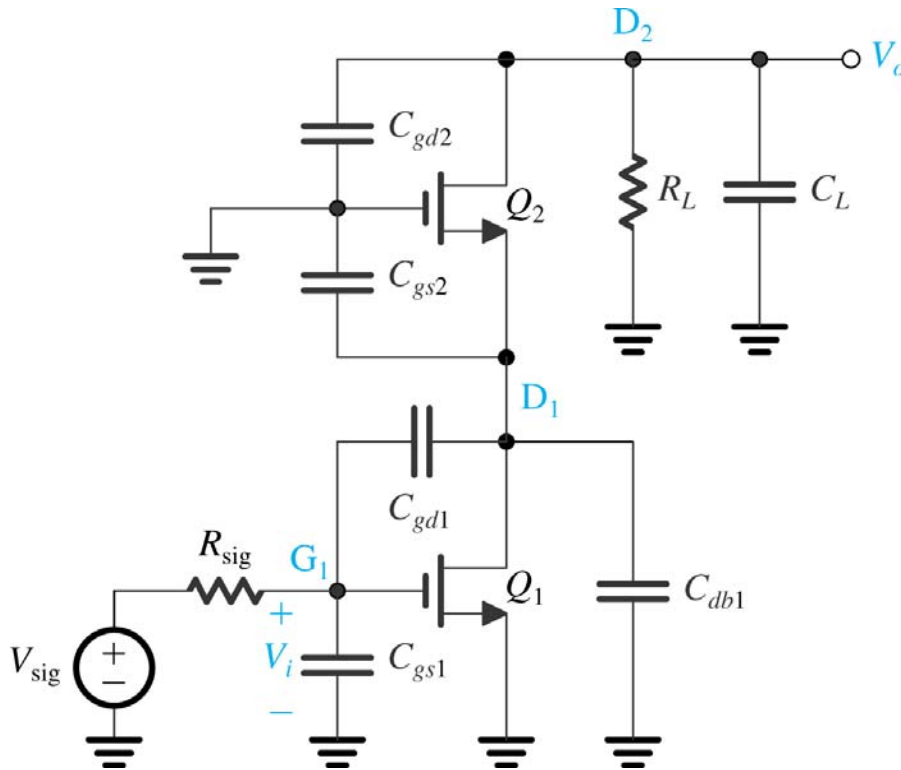


$$f_H \approx \frac{1}{2\pi\tau_H}$$

$$\begin{cases} R_o = r_{o1} + r_{o2} + (g_{m2}r_{o2})r_{o1} \approx (g_{m2}r_{o2})r_{o1} \\ R_{d1} = r_{o1} \parallel \frac{r_{o2} + R_L}{g_{m2}r_{o2}} \end{cases}$$

$$\tau_H \approx R_{sig} \left[C_{gs1} + C_{gd1} (1 + g_{m1}R_{d1}) \right] + R_{d1} (C_{gd1} + C_{db1} + C_{gs2}) + (R_L \parallel R_o) (C_L + C_{gd2})$$

High Frequency Analysis of BJT Cascode

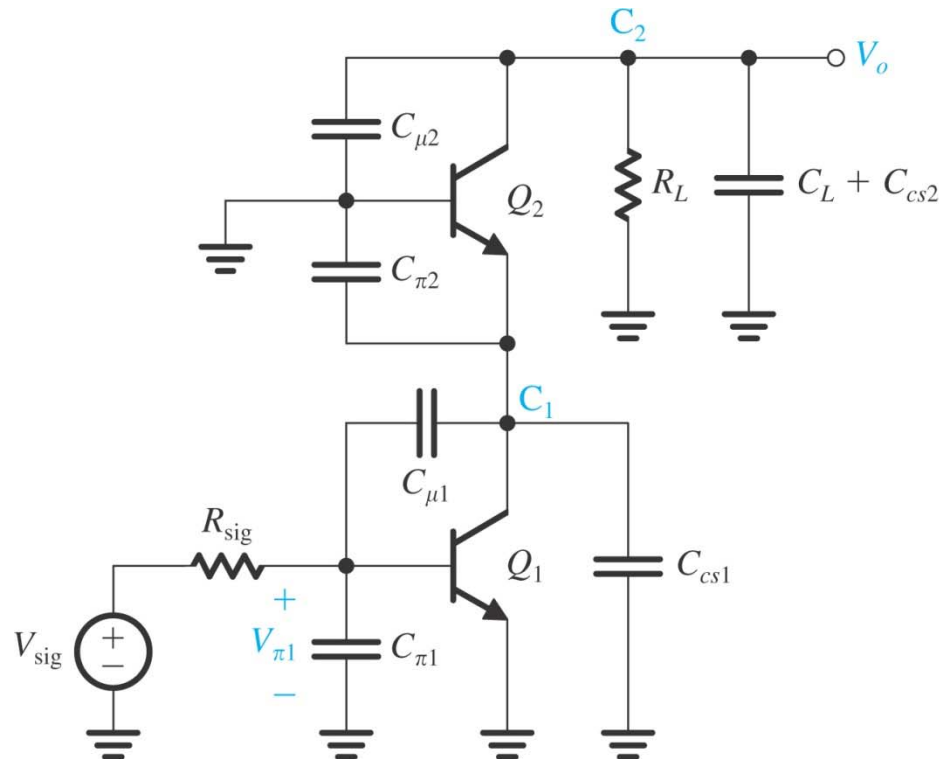

$$R'_{sig} = r_{\pi 1} \parallel (r_{x1} + R_{sig})$$

$$R_{\pi 1} = R'_{sig}$$

$$R_{\mu 1} = R'_{sig}(1 + g_{m1}R_{c1}) + R_{c1}$$

$$R_{c1} = r_{o1} \parallel \left[r_{e2} \left(\frac{r_{o2} + R_L}{r_{o2} + R_L/(\beta_2 + 1)} \right) \right]$$

$$\tau_H = C_{\pi 1}R_{\pi 1} + C_{\mu 1}R_{\mu 1} + (C_{cs1} + C_{\pi 2})R_{c1} + (C_L + C_{cs2} + C_{\mu 2})(R_L \parallel R_o)$$

$$R_o \approx \beta_2 r_{o2}$$

$$f_H \approx \frac{1}{2\pi\tau_H}$$

$$A_M = -\frac{r_{\pi}}{r_{\pi} + r_x + R_{sig}} g_m(\beta r_o \parallel R_L)$$