

ECE 523/421 – Analog Electronics

Lecture 22: Feedback: Introduction

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ Numerical example of low frequency analysis
- ☐ High frequency analysis of CC-CE wideband amplifier
- ☐ High frequency analysis of CMOS Op Amp

Today's Lecture

- ☐ **Feedback and Signal Flow Diagram**
- ☐ **Basic Properties of Negative Feedback**

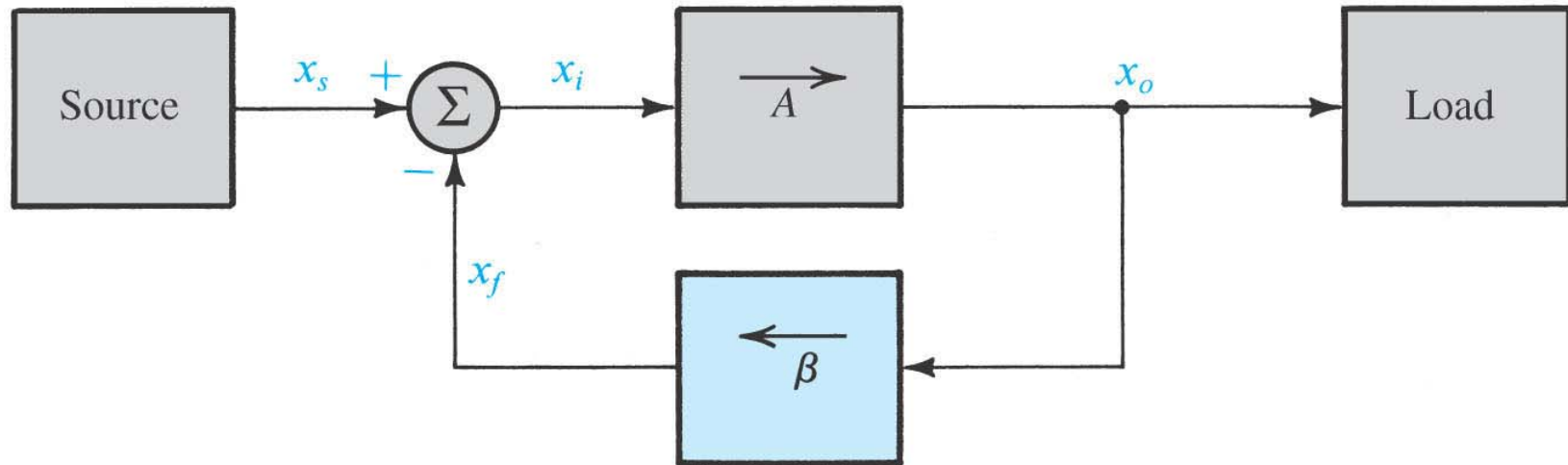
Signal Flow Diagram in Circuits with Feedback




$$A_f = \frac{A}{1 + A\beta}$$

$$A\beta = \text{Loop Gain}$$

A Feedback Example

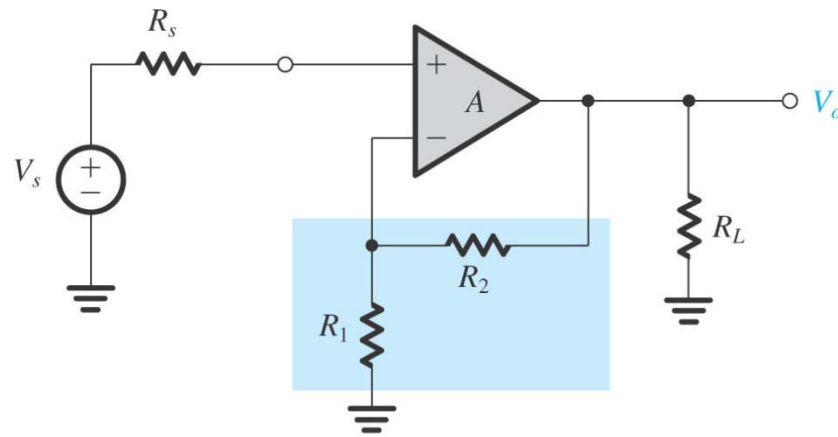

(a)

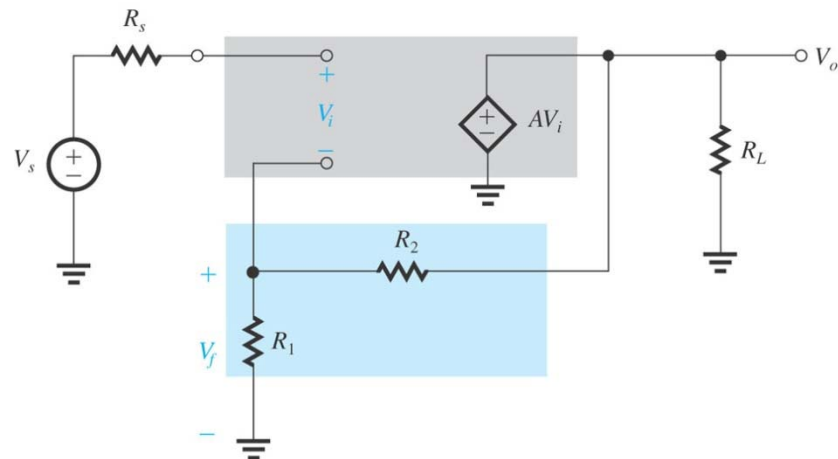

(b)

Some Properties of Negative Feedback

- ☐ Desensitize the gain
- ☐ Reduce nonlinear distortion
- ☐ Reduce the effect of noise
- ☐ Control R_{in} and R_{out}
- ☐ Extend the bandwidth