

ECE 523/421 – Analog Electronics

Lecture 27: Basic Analog Systems: ADC and DAC

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ **Review of Class A Power Amplifier**
- ☐ **Class B and Class AB Power Amplifiers**

Today's Lecture

- ☐ **Basic Digital to Analog Converters**
- ☐ **Basic Analog to Digital Converters**

Importance of Data Conversion

 

Courtesy of Prof. Philip Allen

Digital-to-Analog Converters

 



Fig. 10.1-01

Characteristics:

- Can be asynchronous or synchronous
- Primary active element is the op amp
- Conversion time can vary from fast (one clock period, T) to slow ($2^{\text{No. of bits}} \cdot T$)

Courtesy of Prof. Philip Allen

Analog-to-Digital Converters

 


Characteristics:

- Can only be synchronous (the analog signal must be sampled and held during conversion)
- Primary active element is the comparator
- Conversion time can vary from fast (one clock period, T) to slow ($2^{\text{No. of bits}} \cdot T$)

Courtesy of Prof. Philip Allen

Digital-to-Analog Block Diagram

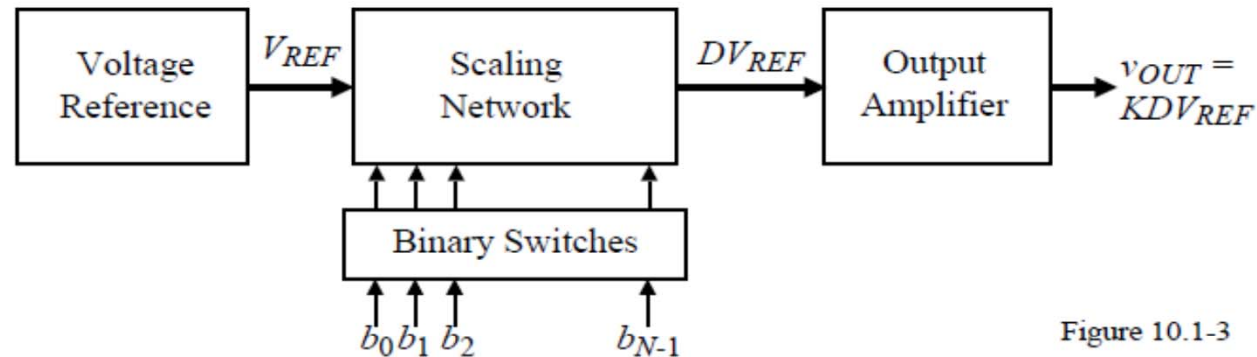

b_0 is the most significant bit (MSB)



The MSB is the bit that has the most (largest) influence on the analog output

b_{N-1} is the least significant bit (LSB)

The LSB is the bit that has the least (smallest) influence on the analog output



Courtesy of Prof. Philip Allen

Current Scaling DAC

  


Courtesy of Prof. Philip Allen


R-2R Ladder Implementation

  

Courtesy of Prof. Philip Allen

 


High Speed Current-Mode DAC

 

060926-01

Courtesy of Prof. Philip Allen

High-Speed, High-Accuracy DAC

 

Courtesy of Prof. Philip Allen

Voltage Scaling DAC

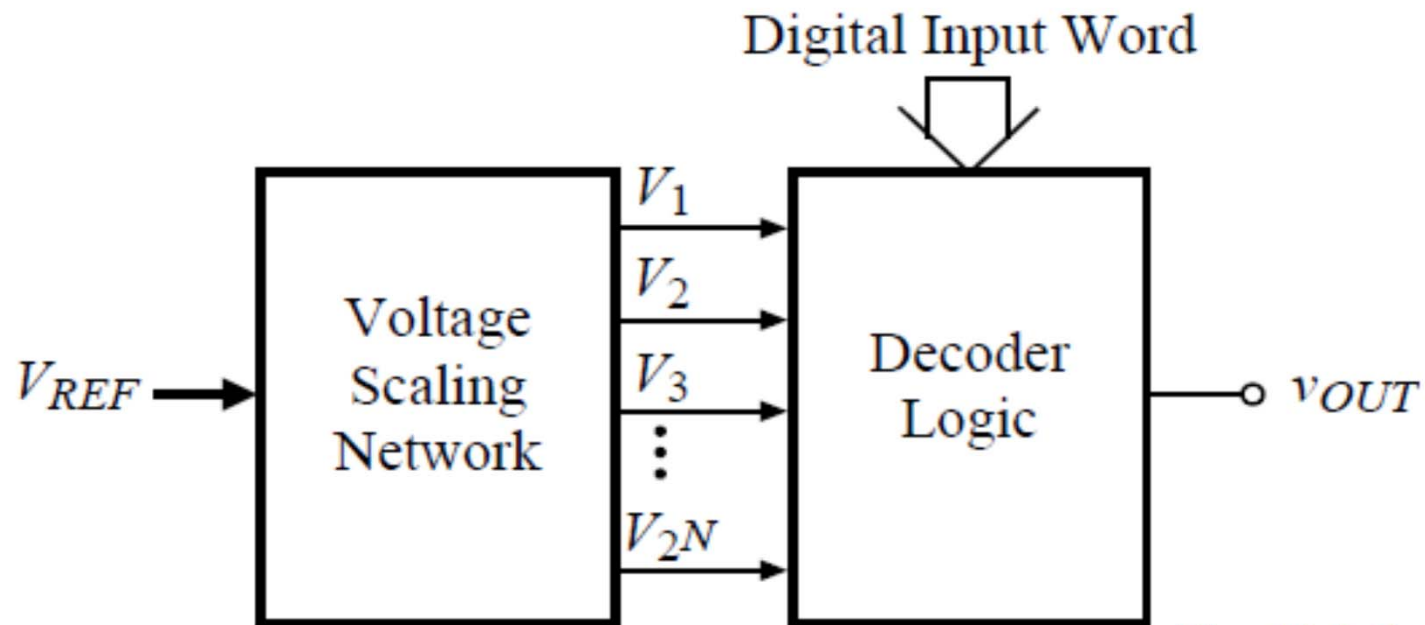


Fig. 10.2-6

Courtesy of Prof. Philip Allen



Slide: 14

Alternate Realization of the 3-bit DAC

 


Fig. 10.2-8

Courtesy of Prof. Philip Allen

DAC Input-Output Characteristics

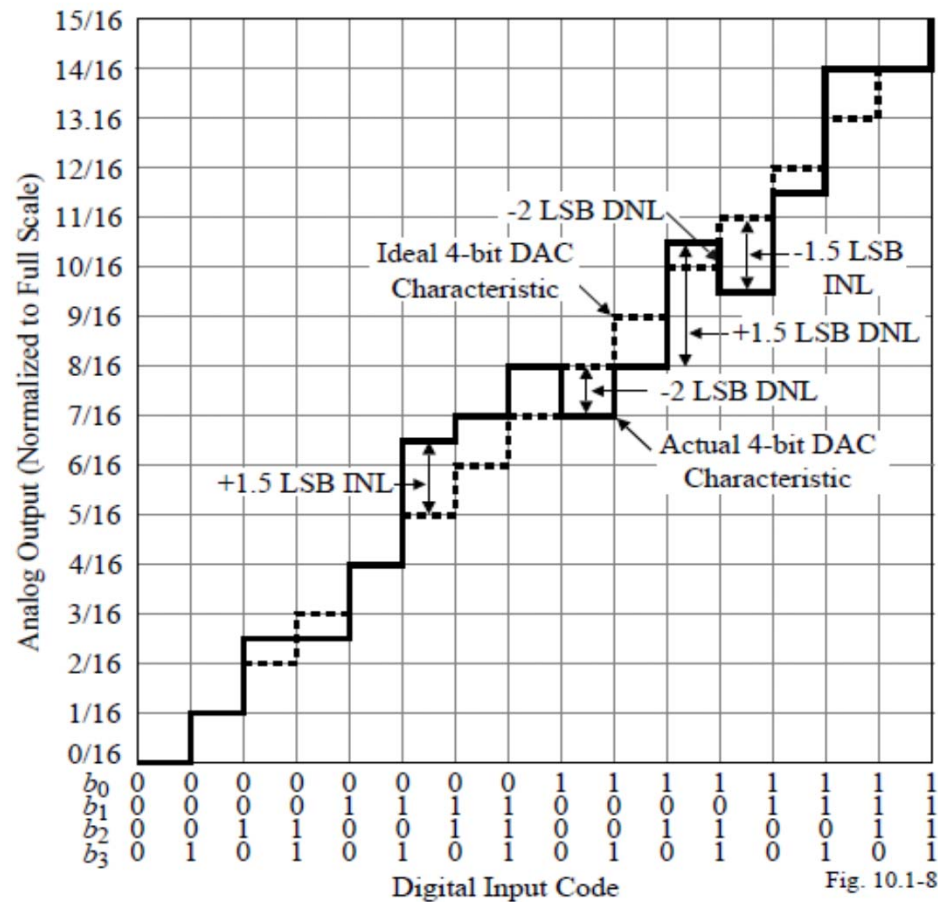


Fig. 10.1-8


Courtesy of Prof. Philip Allen

DAC Timing Requirements

To avoid errors in DACs (and ADCs), $v_{out}(t)$ must be within $\pm 0.5LSB$ of the final value by the end of the conversion time.


Multiple-pole response:

 Typically the response is underdamped like the following (see Appendix C of text).



Courtesy of Prof. Philip Allen



Basic Analog-to-Digital Converters (ADC)

 

- Prefilter - Avoids the aliasing of high frequency signals back into the baseband of the ADC
- Sample-and-hold - Maintains the input analog signal constant during conversion
- Quantizer - Finds the subrange that corresponds to the sampled analog input
- Encoder - Encoding of the digital bits corresponding to the subrange

Courtesy of Prof. Philip Allen

Sample and Hold Circuit (Settling Time)

  

Courtesy of Prof. Philip Allen

Serial ADC Circuit

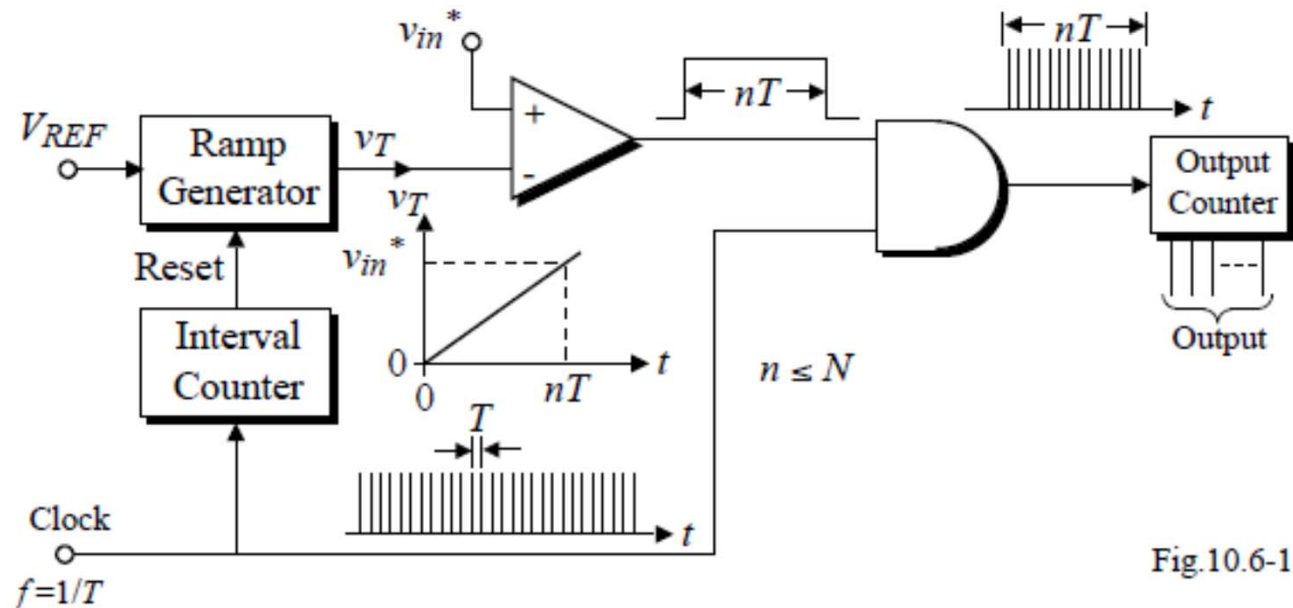


Fig.10.6-1

Attributes:


- Simplicity of operation
- Subject to error in the ramp generator
- Long conversion time $\leq 2^N T$

Courtesy of Prof. Philip Allen

Successive Approximation ADC



Successive Approximation Algorithm:

 - 1.) Start with the *MSB* bit and work toward the *LSB* bit.
- 2.) Guess the *MSB* bit as 1.
- 3.) Apply the digital word 10000.... to a DAC.
- 4.) Compare the DAC output with the sampled analog input voltage.
- 5.) If the DAC output is greater, keep the guess of 1. If the DAC output is less, change the guess to 0.
- 6.) Repeat for the next *MSB*.



Courtesy of Prof. Philip Allen

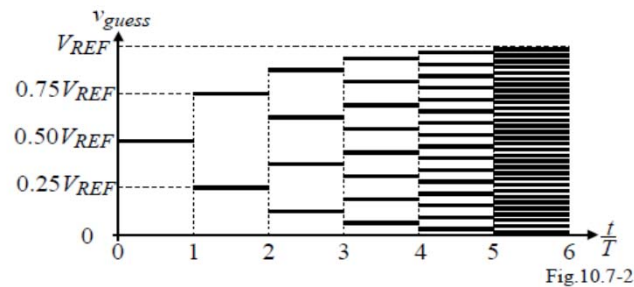 Implementation of Successive Approximation



Courtesy of Prof. Philip Allen

Parallel/Flash ADC Architecture

 


Fig.10.8-1

Courtesy of Prof. Philip Allen