

ECE 523/421 – Analog Electronics

Lecture 3: Basic MOSFET Amplifiers II

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu

Review of Last Lecture

- ☐ **MOSFET Biasing for Amplification**
- ☐ **MOSFET Small Signal (Π and T Models)**
- ☐ **Basic MOSFET Amplifier Configurations (CS, CG, CD)**
- ☐ **Examples**

Today's Lecture



☐ **Biasing in MOS Amplifier Circuits**

- **Fix V_{GS} Biasing**
- **Fix V_{GS} Biasing with Source Resistance**
- **Drain-to-Gate Feedback Resistor Biasing**
- **Constant Current Source Biasing**



☐ **Role of Body Effect in MOS Amplifiers**

☐ **Temperature Effect**

Problem of Fix V_{GS} Biasing

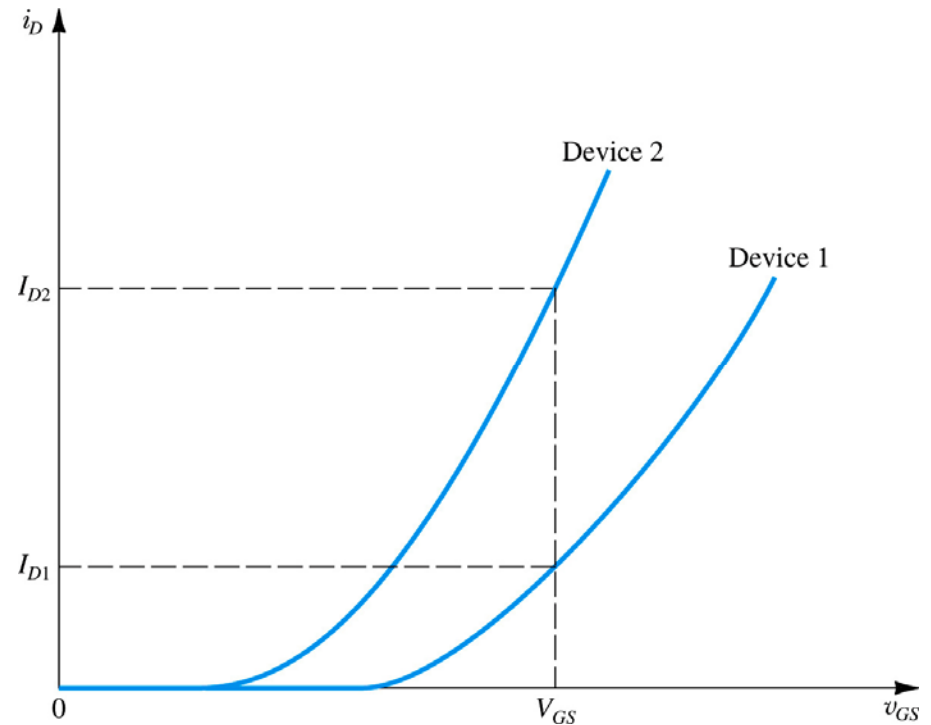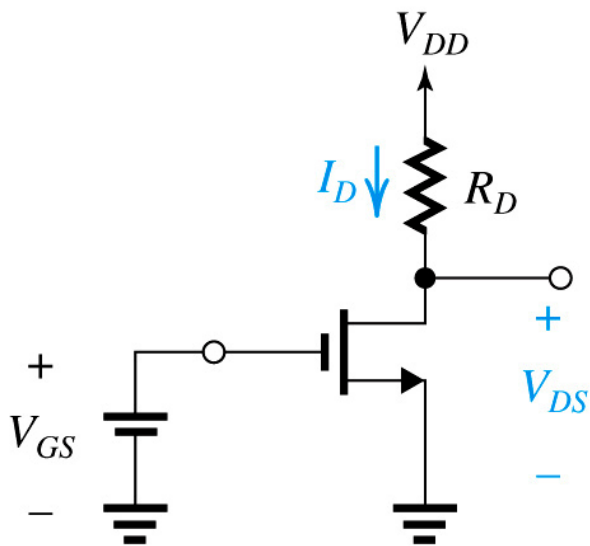


Advantage of R_S in Fix V_{GS} Biasing

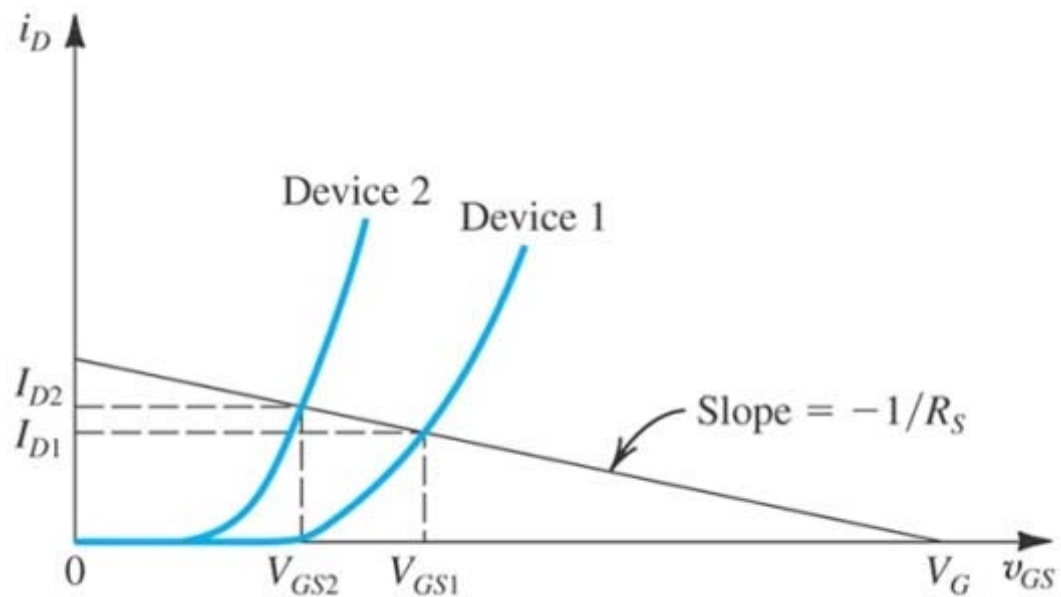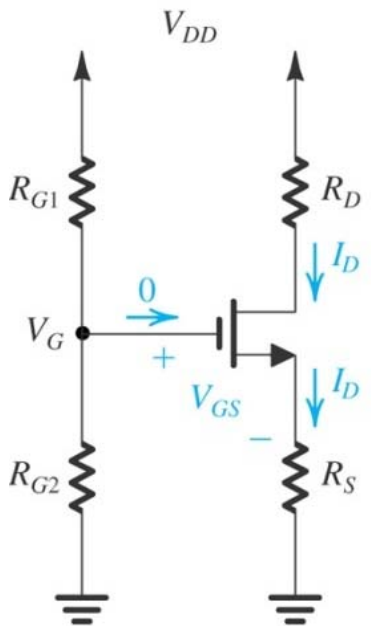


Example: Bias Circuit Design I

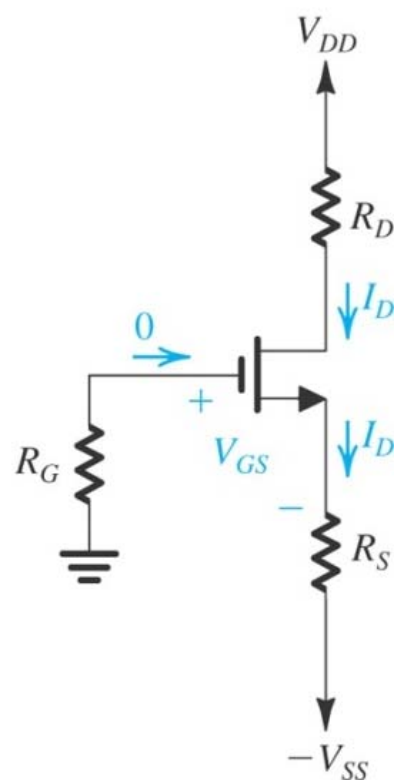
- 1) Design the following circuit to operate at a dc drain current of 0.5 mA and $V_D = +2$ V. Let $V_t = 1$ V, $K'_n W/L = 1$ mA/V², and $\lambda = 0$, $V_{DD} = V_{SS} = 5$ V. Use standard 5% resistor values and give the resulting values of I_D , V_D , and V_S .



Drain-to-Gate Feedback Biasing

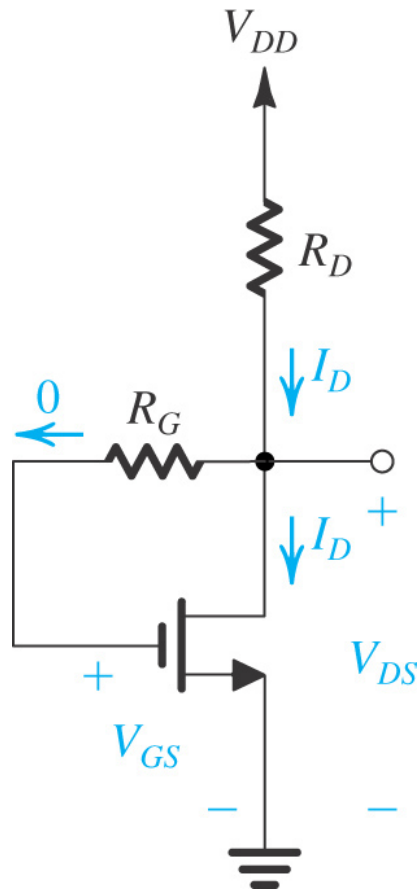


Constant Current Source Biasing


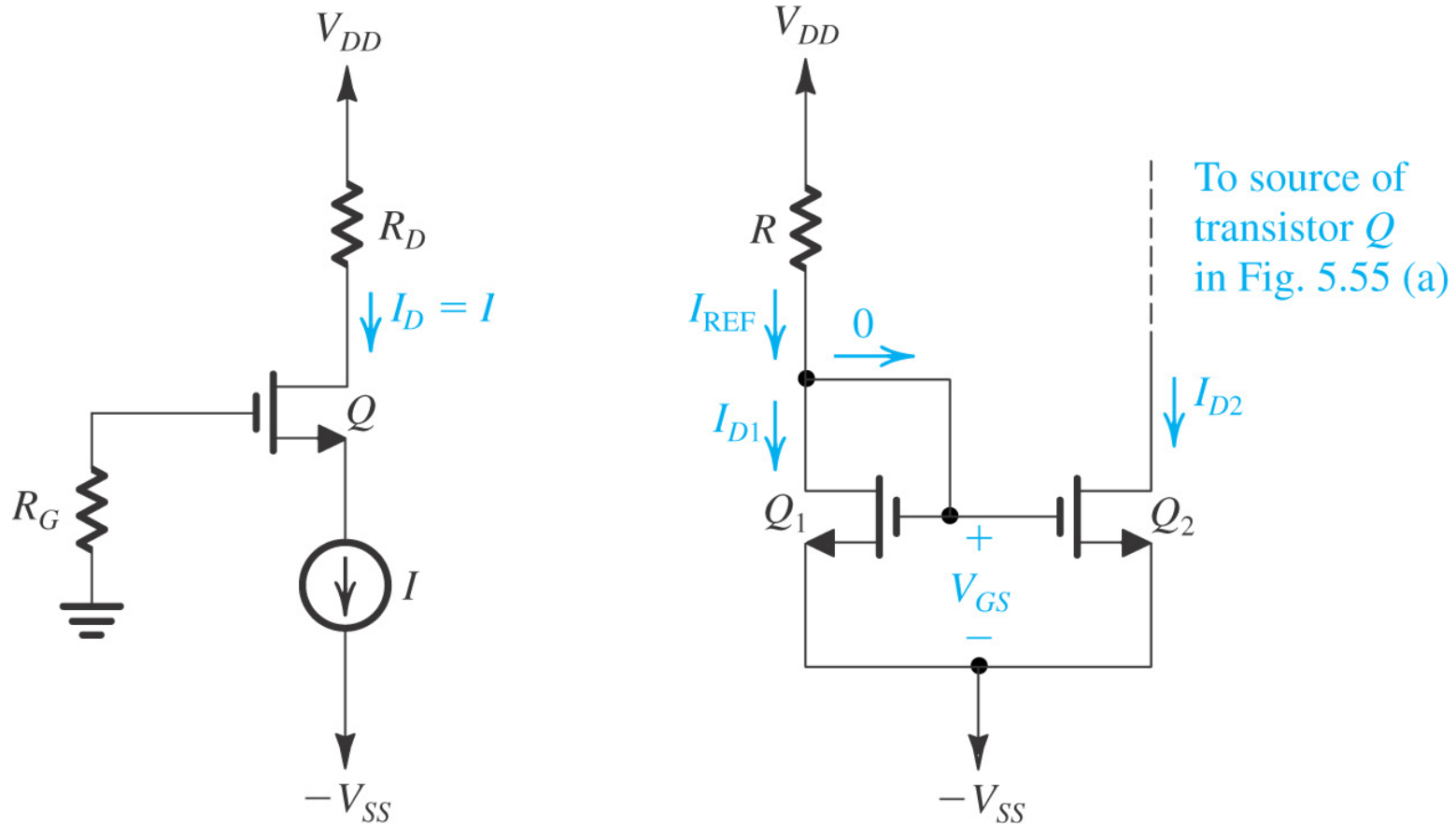


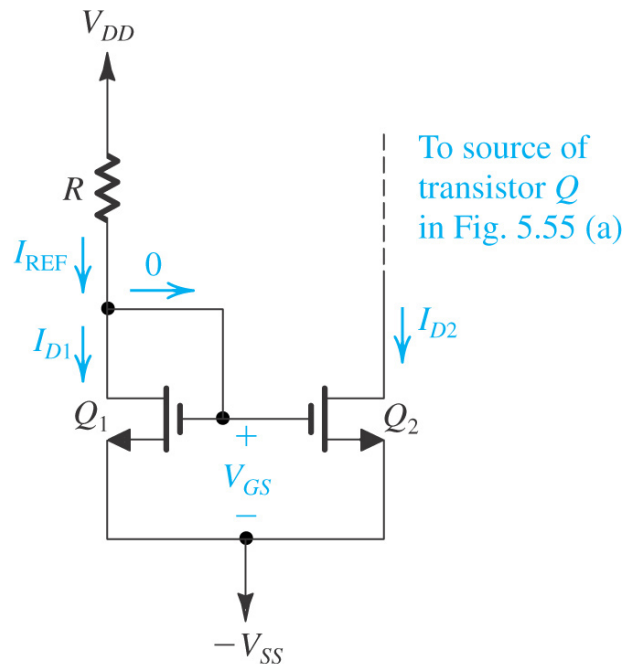Example: Bias Circuit Design II



Using two transistors Q_1 and Q_2 having equal lengths but widths related by $W_2/W_1=5$, design the current mirror circuit to obtain $I=0.5\text{mA}$. Let $V_{DD}=-V_{SS}=5\text{V}$, $K'_n(W/L)_1=0.8\text{mA/V}^2$, $V_t=1\text{V}$, and $\lambda=0$. Find the required value for R . What is the voltage at the gate of Q_1 and Q_2 ? What is the lowest voltage allowed at the drain of Q_2 while Q_2 remains in the saturation region?





Review of Common-Source Amplifier

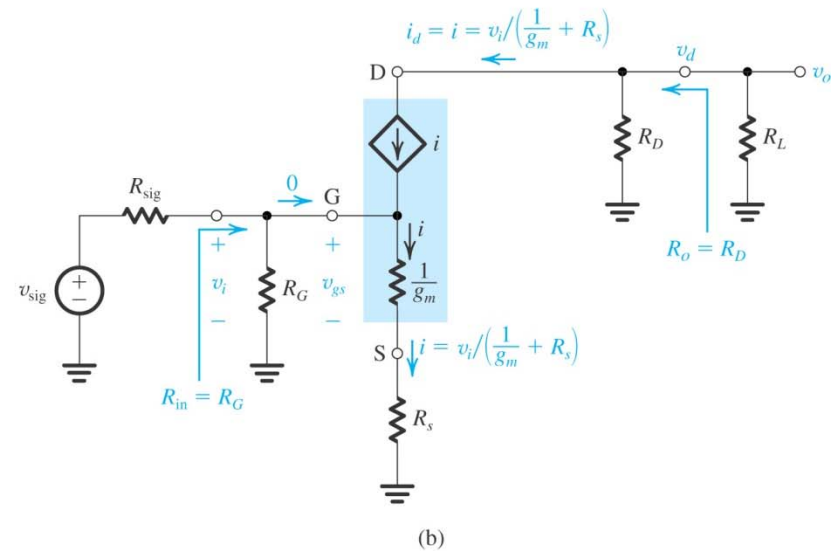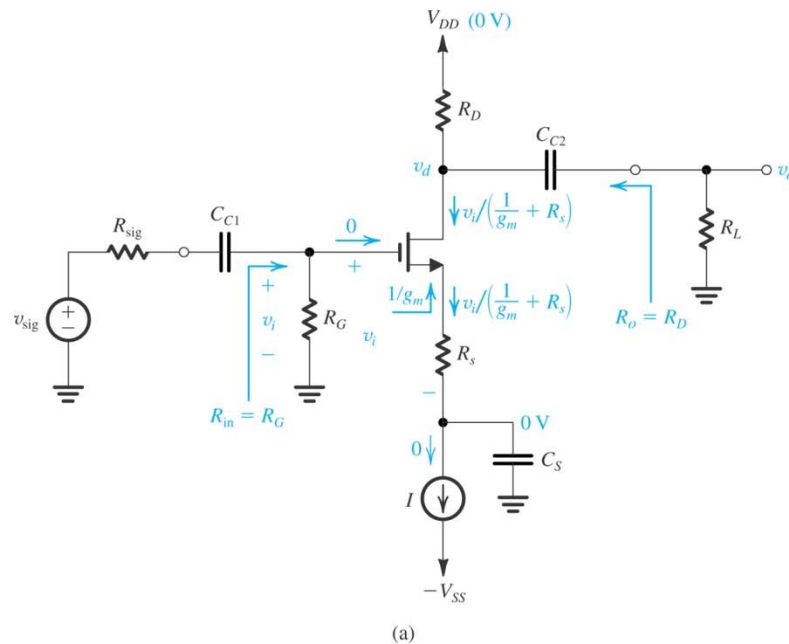


Review of Common-Gate Amplifier

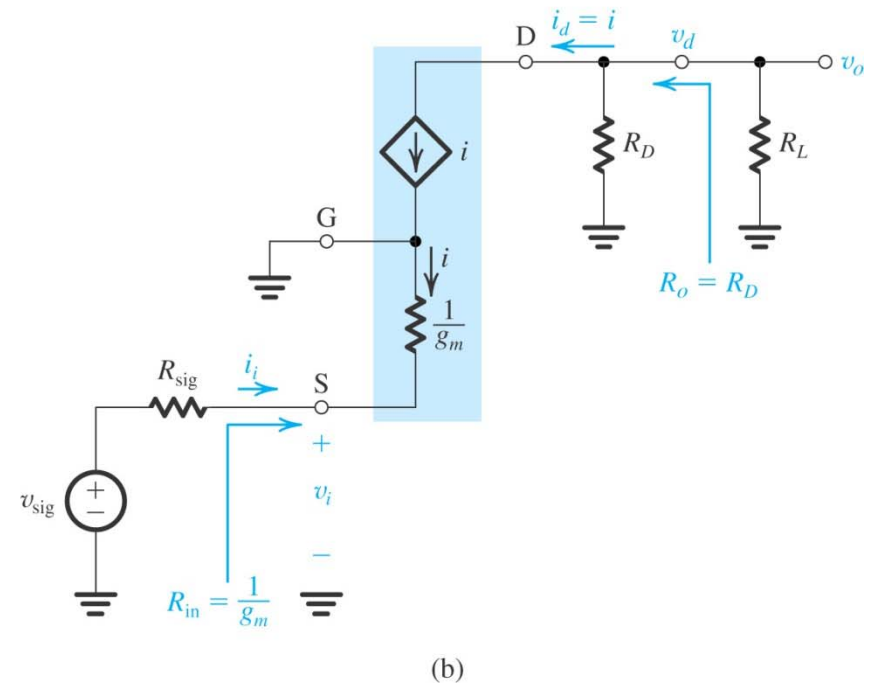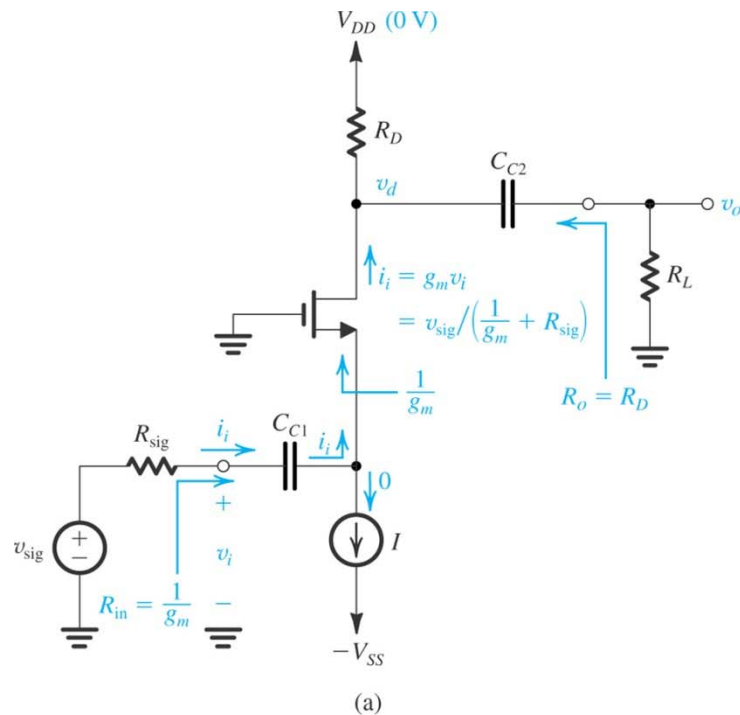


Review of Source Follower Circuit

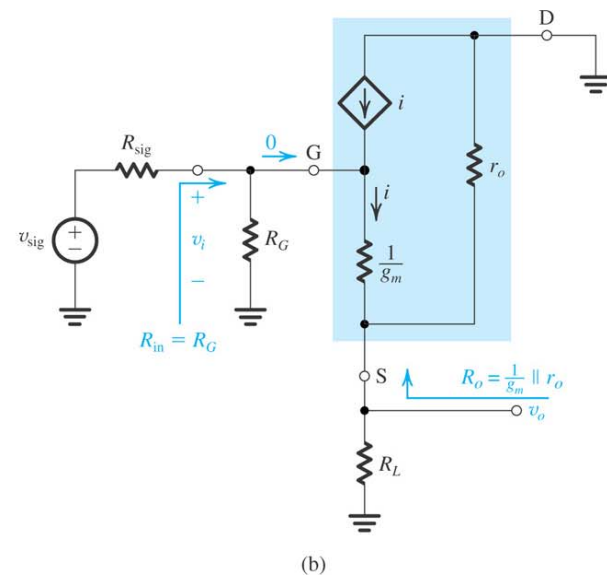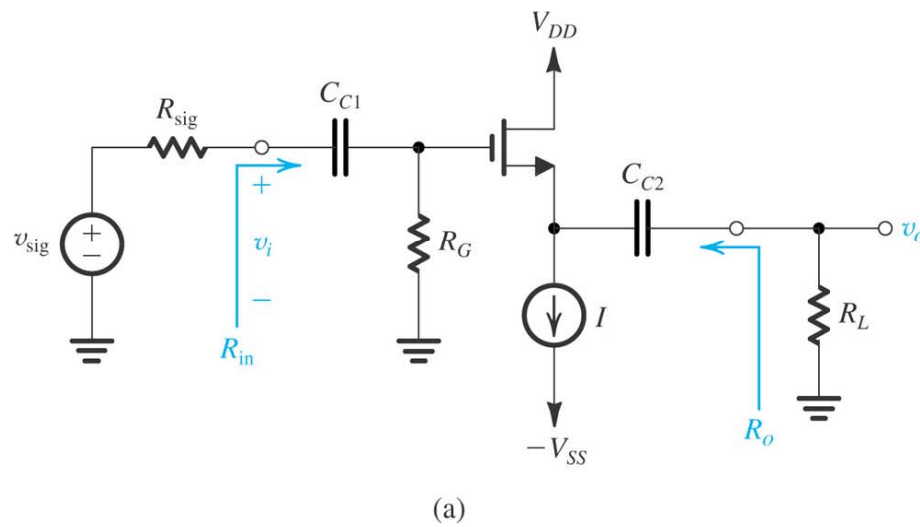

Quick Review of Frequency Response

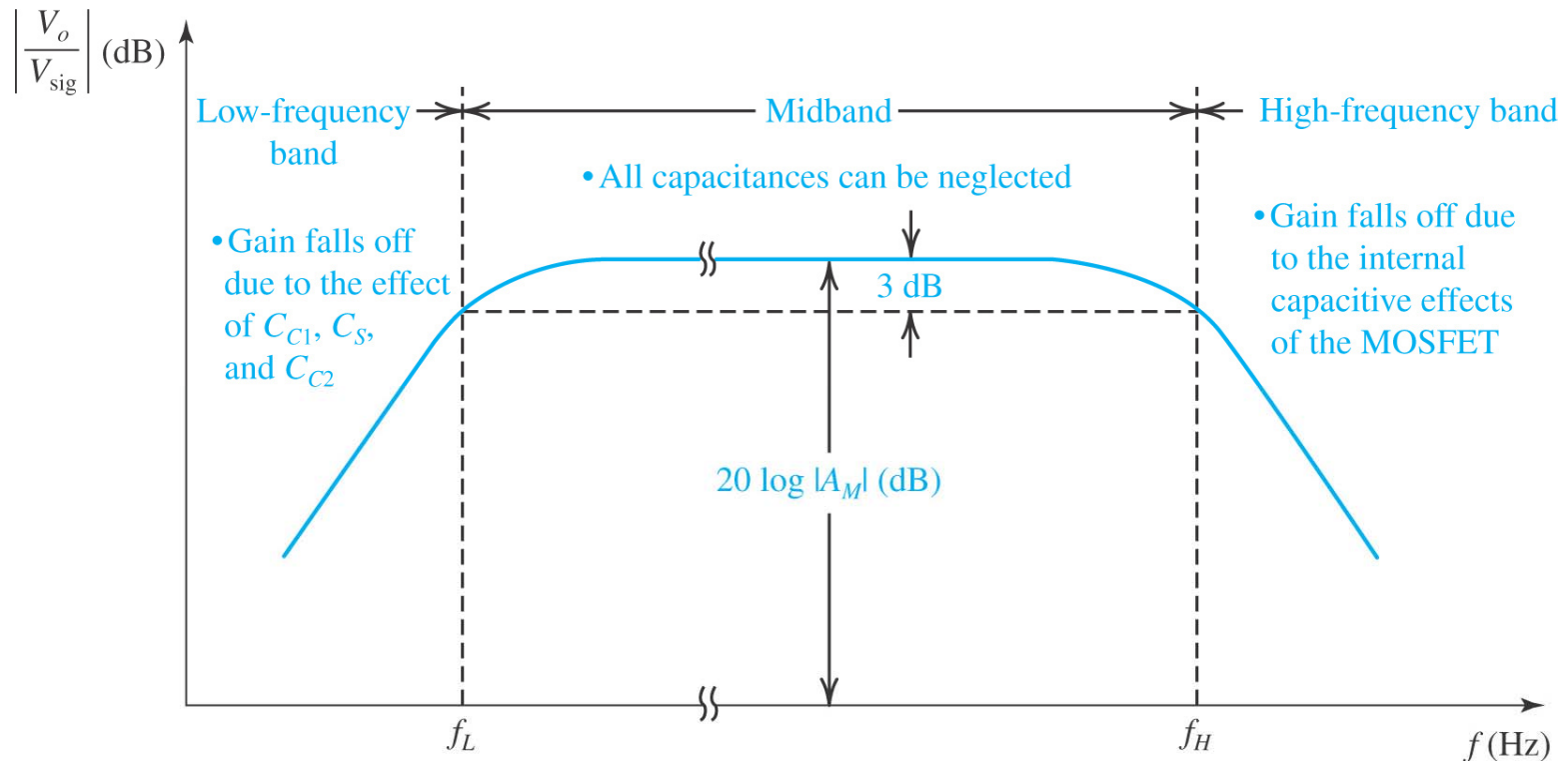

Modeling of Body Effect

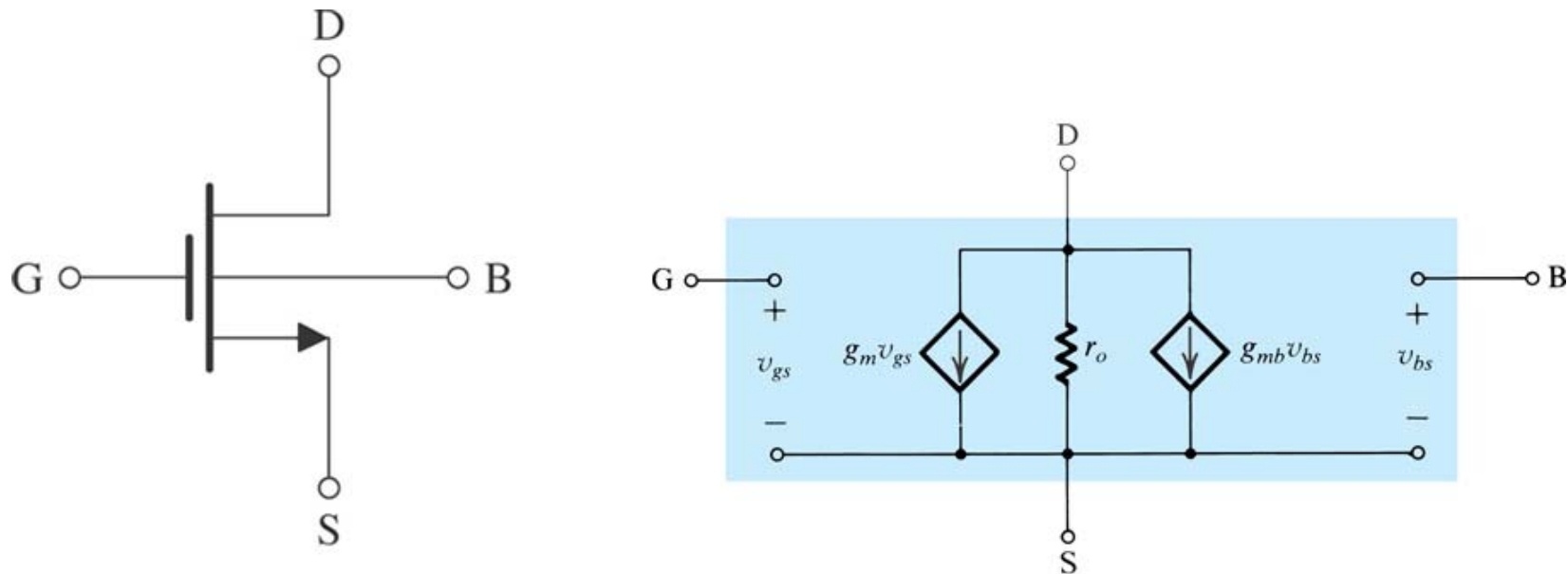

$$g_{mb} = \chi g_m$$

$$\chi = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}}$$

Temperature Effect

- ❑ V_t increases by about 2mV/°C by temperature increase
- ❑ K'_n decreases more by temperature increase
- ❑ Overall I_D decreases as temperature increase
- ❑ This is an advantage for MOSFET devices (No thermal runaway)