

ECE 523/421 – Analog Electronics

Lecture 5: Basic BJT Amplifiers II

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ **Basic BJT Characteristics**
- ☐ **DC analysis on BJT Circuits**

Today's Lecture



- ☐ AC analysis on BJT Circuits
- ☐ Basic BJT Amplifier Configurations
- ☐ Some Examples

Small Signal Bipolar Transistor Models

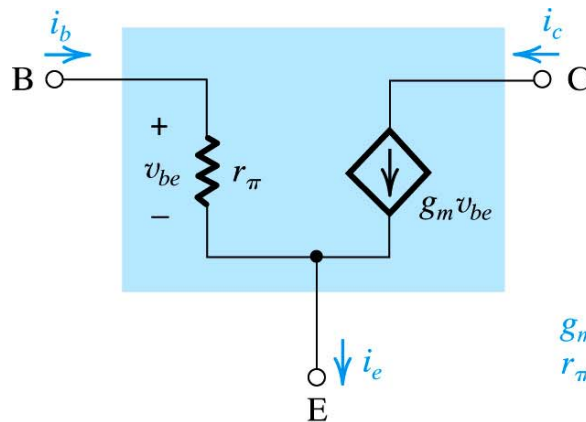


$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

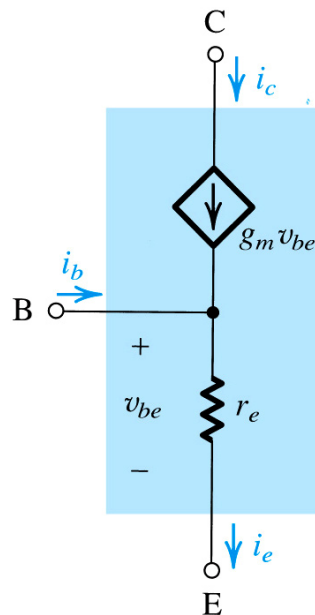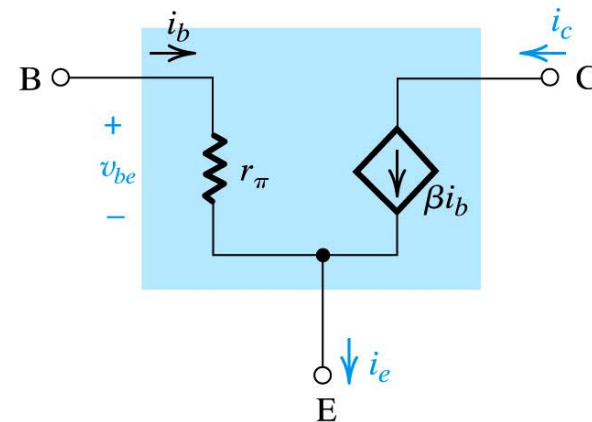


$$g_m = I_C / V_T$$
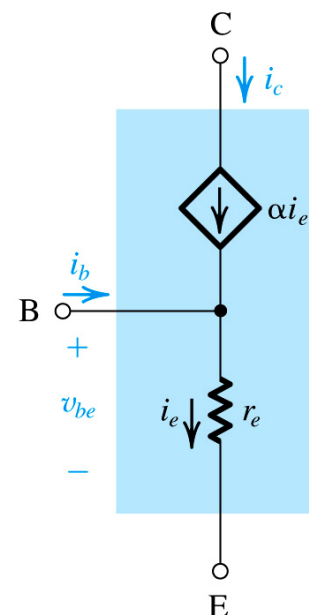
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$




Example: Common Base Design I

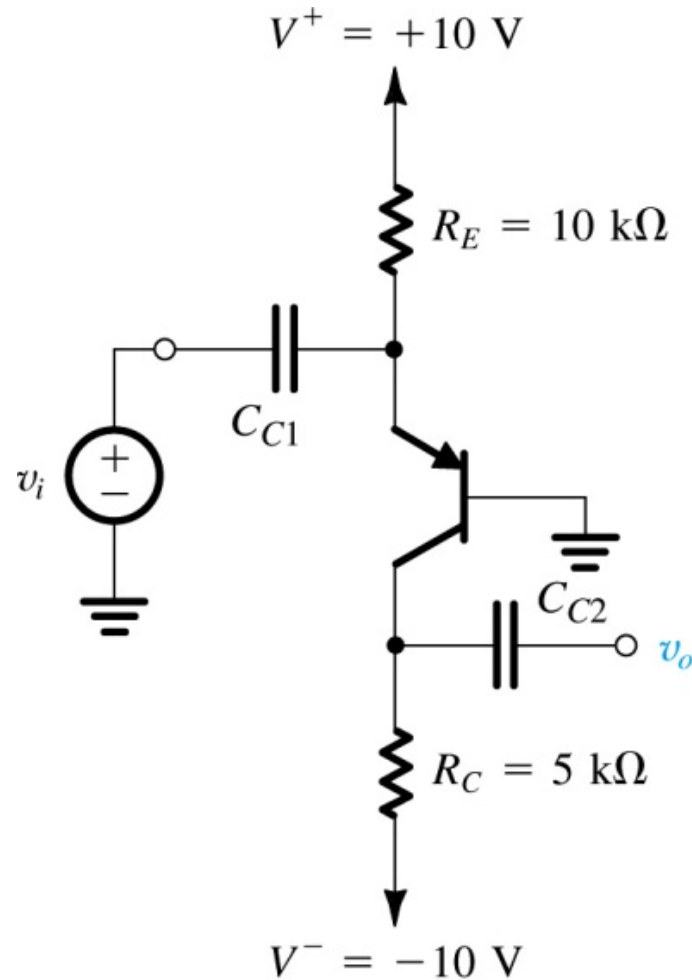- 1) Analyze the following circuit assuming that $\beta=100$.




Impact of Transistor Output Resistance

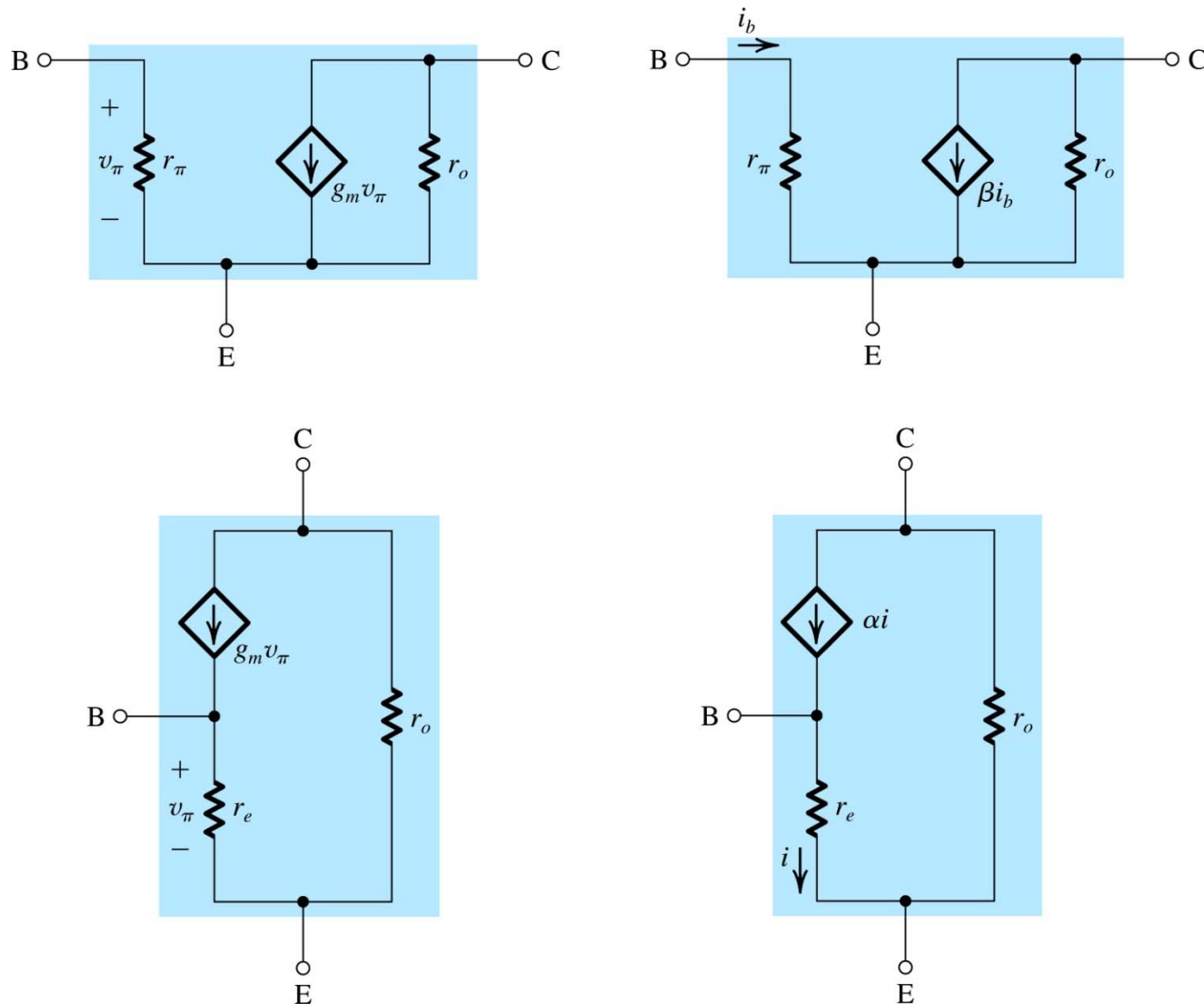


Example: Common Emitter Design I

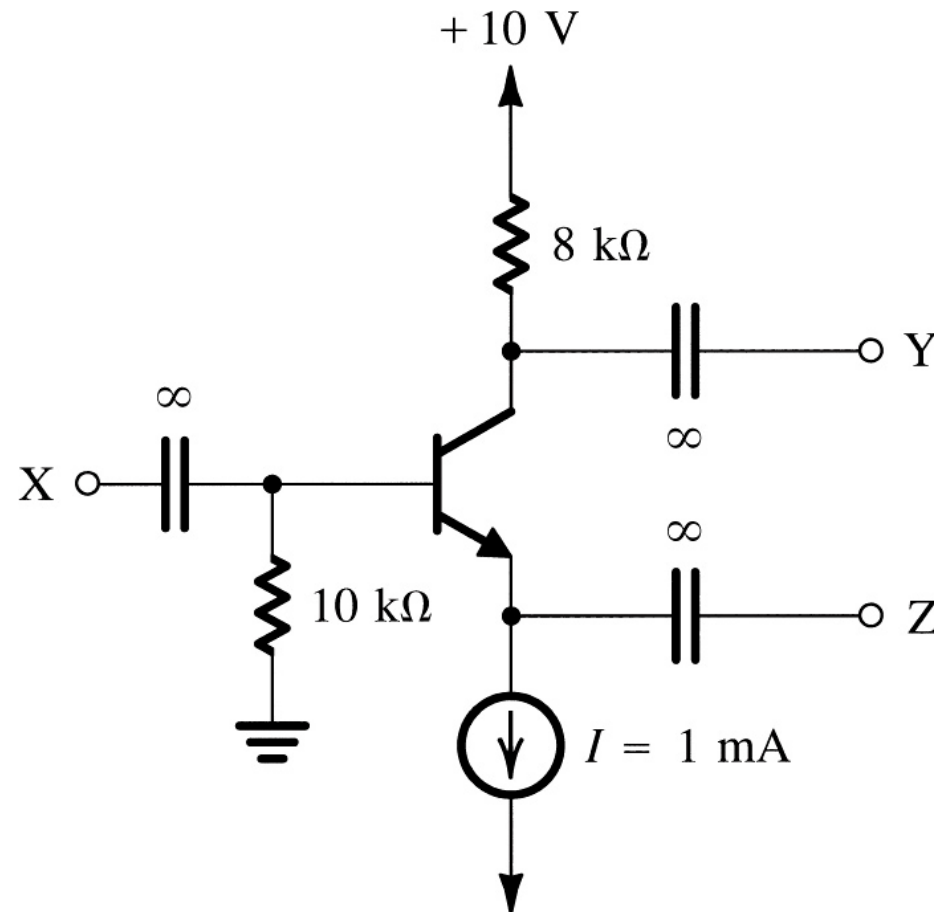
- 1) Analyze the following circuit assuming that $V_A = 100$ V and $\beta = 100$.




Summary of BJT Amplifier Configurations

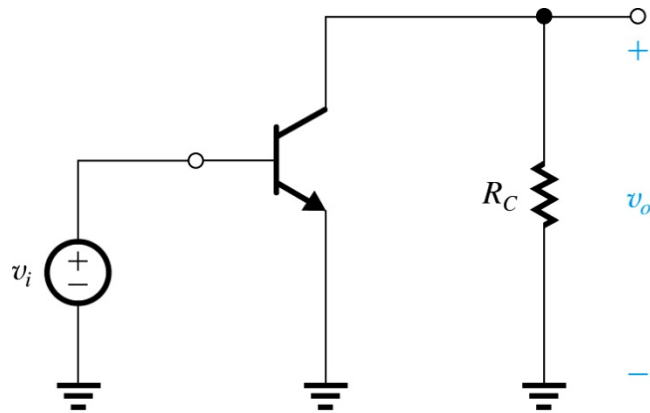

(a) Common-Emitter (CE)

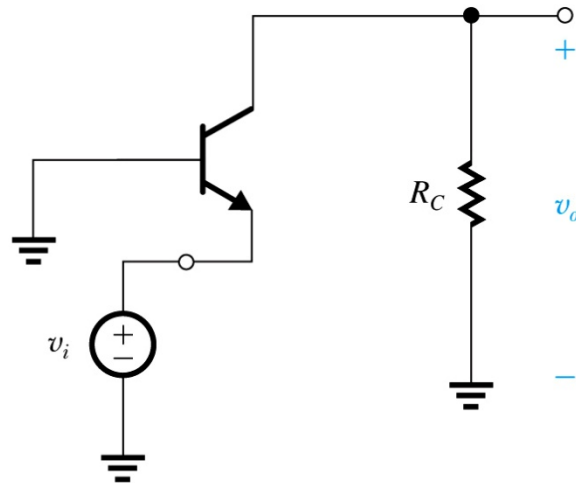


(b) Common-Base (CB)


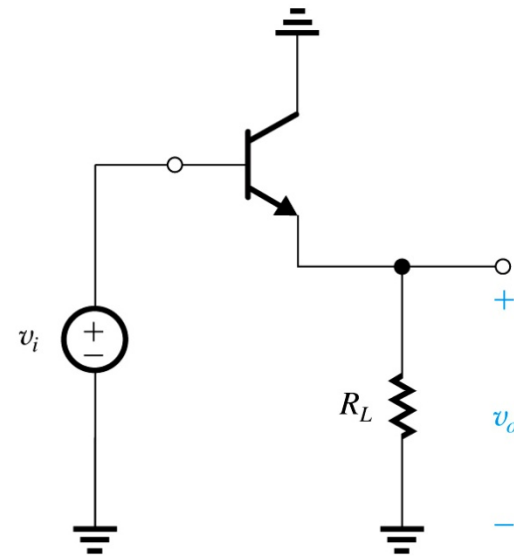


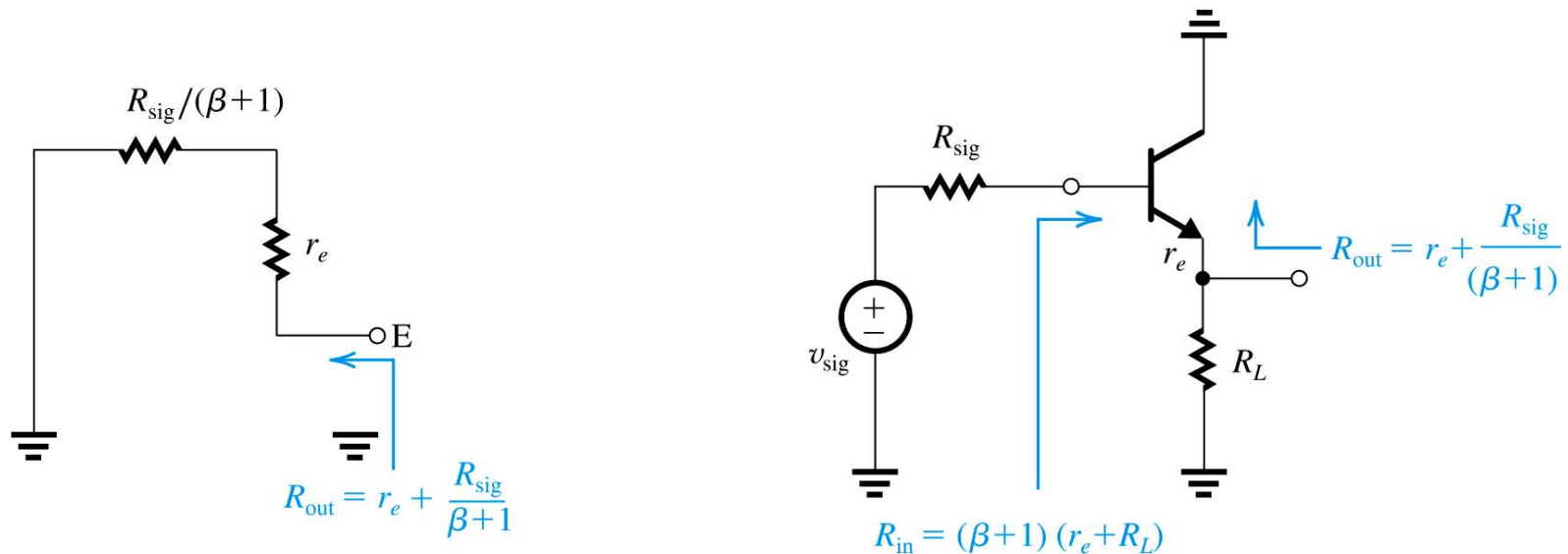(c) Common-Collector (CC)
or Emitter Follower

Helpful Point 1: Resistance Transformation




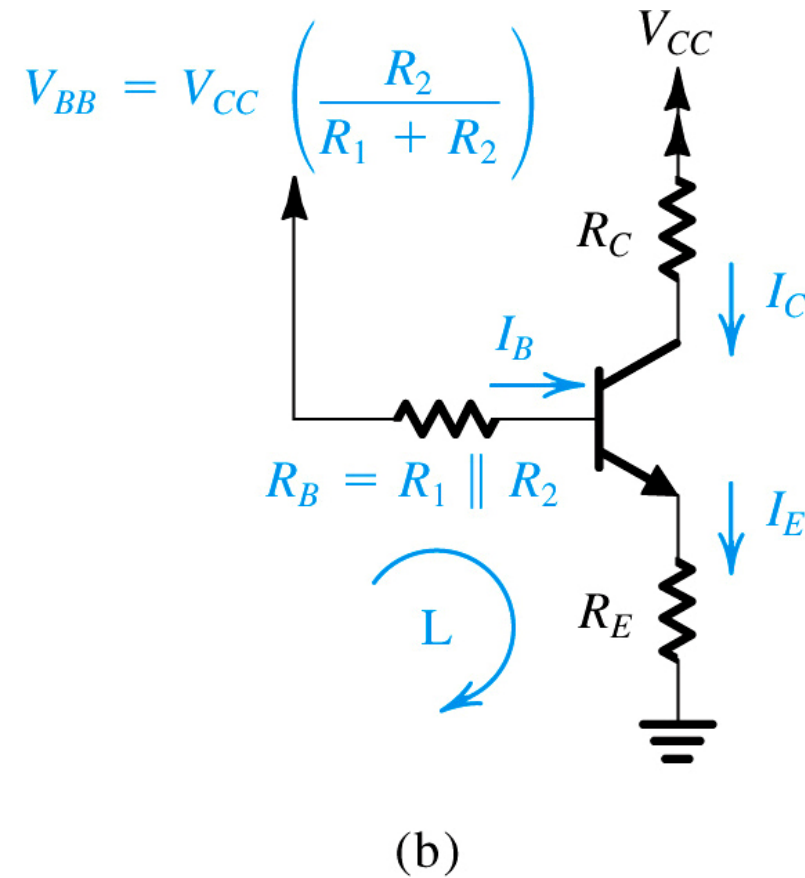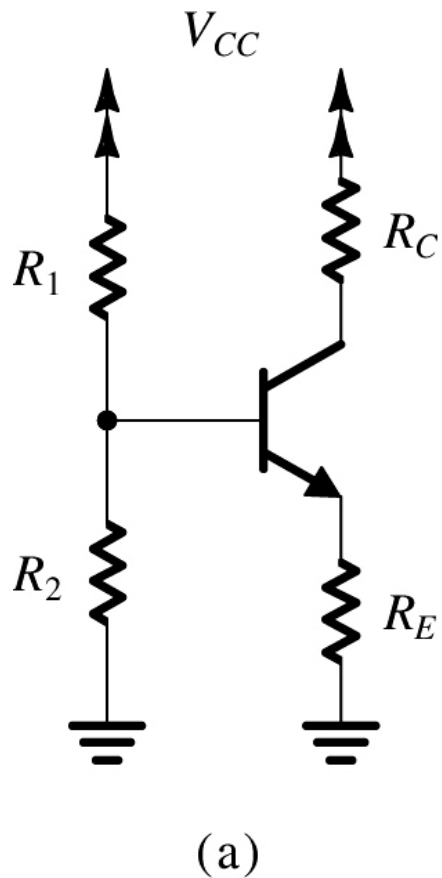Helpful Point 2: Thevenin of Bias Resistors




Example: BJT Current Mirror

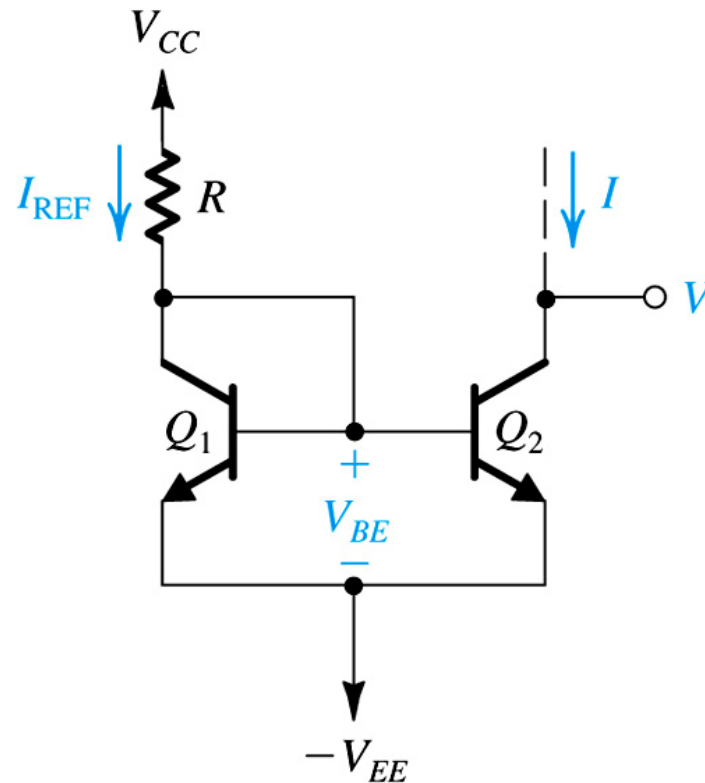- 1) Find R such that the output current become I_{REF} .



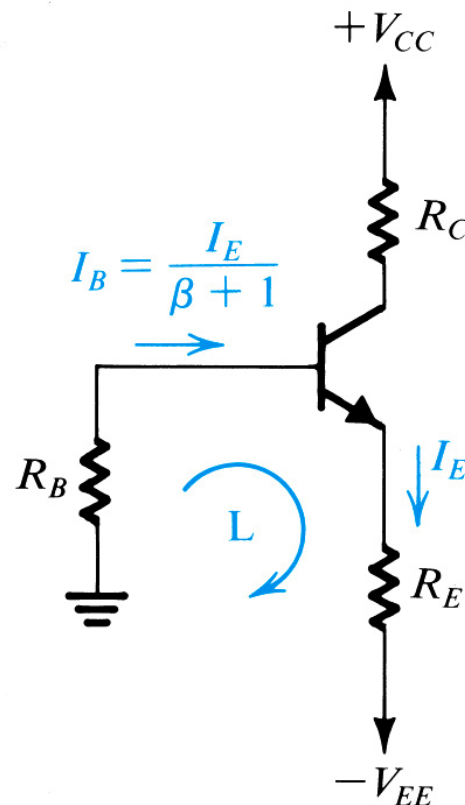
Example: Common Base Amplifier Design

The bias arrangement below is to be used for a common-base amplifier. Design the circuit to establish a dc emitter current of 1 mA and provide the highest possible voltage gain while allowing for a maximum signal swing at the collector of ± 2 V. Use +10 V and -5 V power supplies.



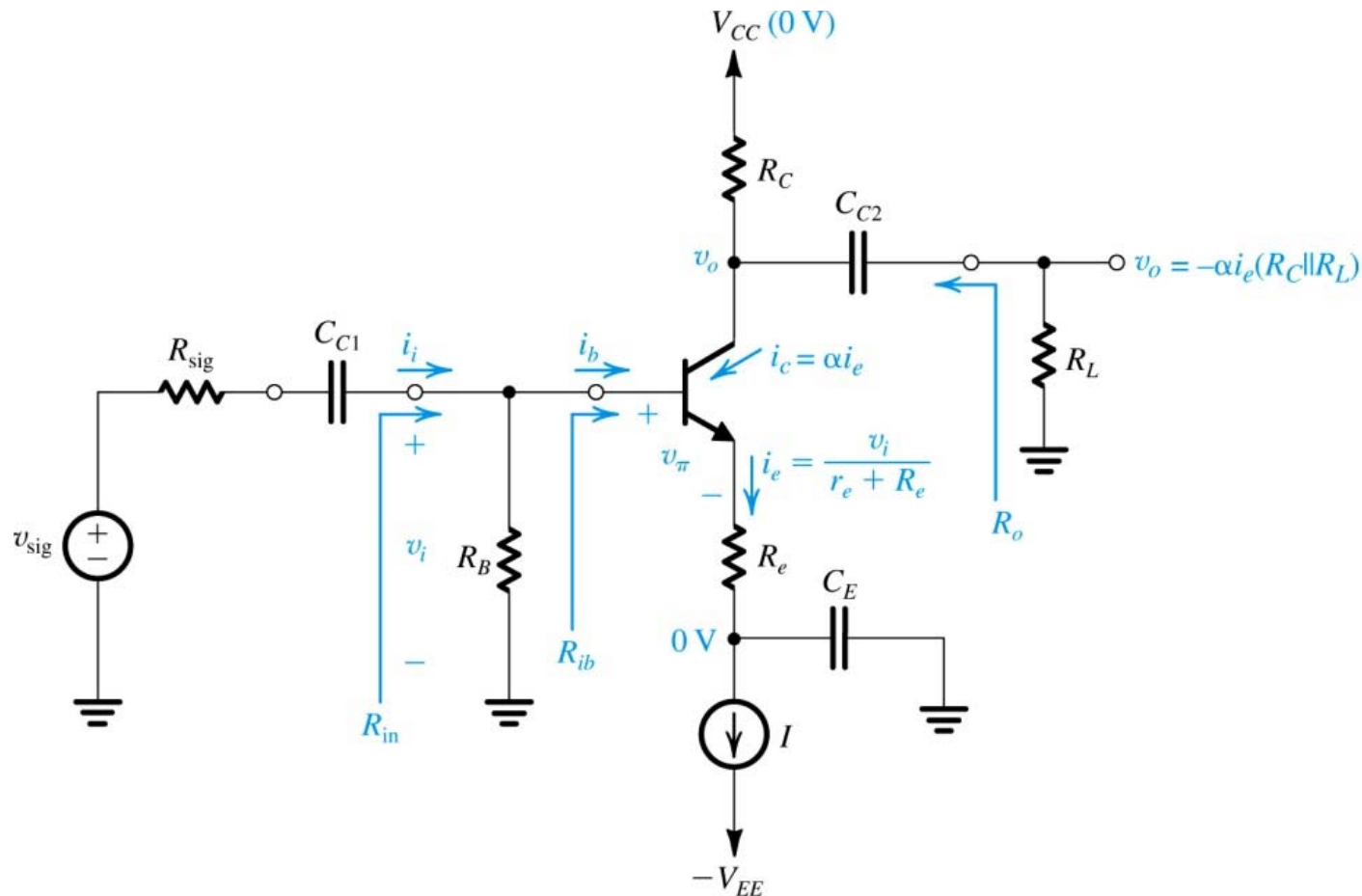Example: Common Source Amplifier

What is the overall gain, G_V , in the following circuit.



Example: Emitter Follower Design

The emitter follower below is used to connect a source with $R_{sig} = 10\text{ k}\Omega$ to a load $R_L = 1\text{ k}\Omega$. The transistor is biased at $I = 5\text{ mA}$, utilizes a resistance $R_B = 40\text{ k}\Omega$ and has $\beta = 100$. Find R_{ib} , R_{in} , G_v , G_{vo} , and R_{out} . If in order to limit nonlinear distortion, the base-emitter signal voltage is limited to 10 mV peak, what is the corresponding amplitude at the output? What Will the overall voltage gain become If R_L is changed to 2 k Ω ? To 500 Ω ?

