

ECE 523/421 – Analog Electronics

Lecture 9: Analog IC Building Blocks: Improved Current Mirror

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: pzarkesh@unm.edu


Review of Last Lecture

- ☐ **Current Mirror Circuits**
- ☐ **Current Sources**
- ☐ **Current Steering Circuits**

Today's Lecture

- ☐ **Cascode Current Mirror Circuits**
- ☐ **BJT Mirrors with Base Compensation Circuit**
- ☐ **Wilson Current Mirror**
- ☐ **Widlar Current Source**


Cascode Current Mirror

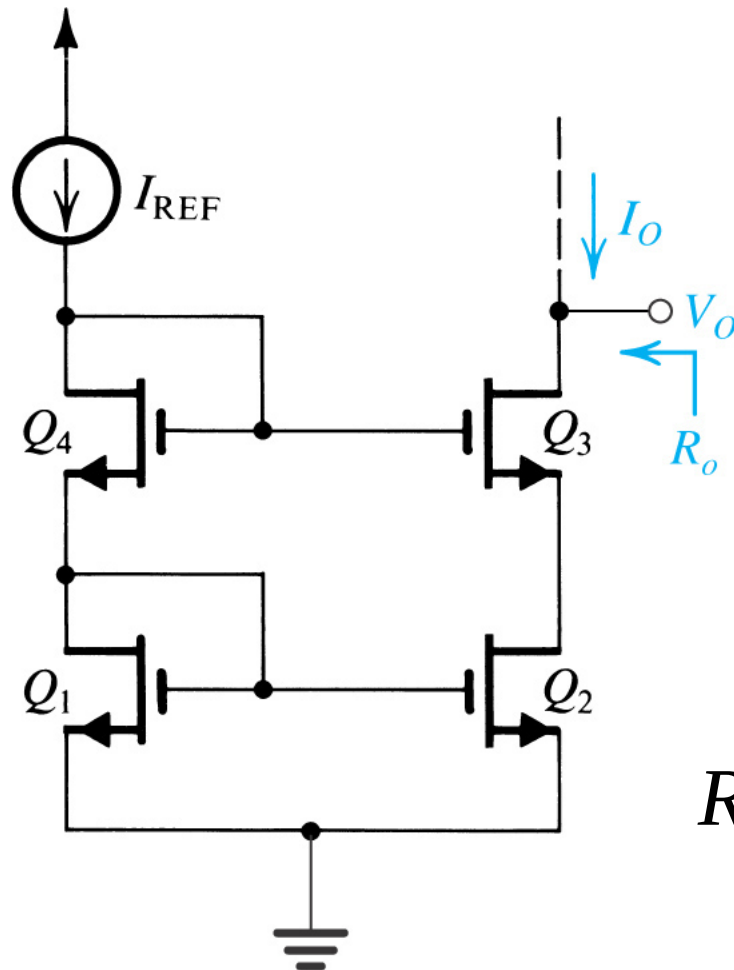


$$R_o \approx g_{m3} r_{o3} r_{o2}$$

Example: Cascode Current Source Design

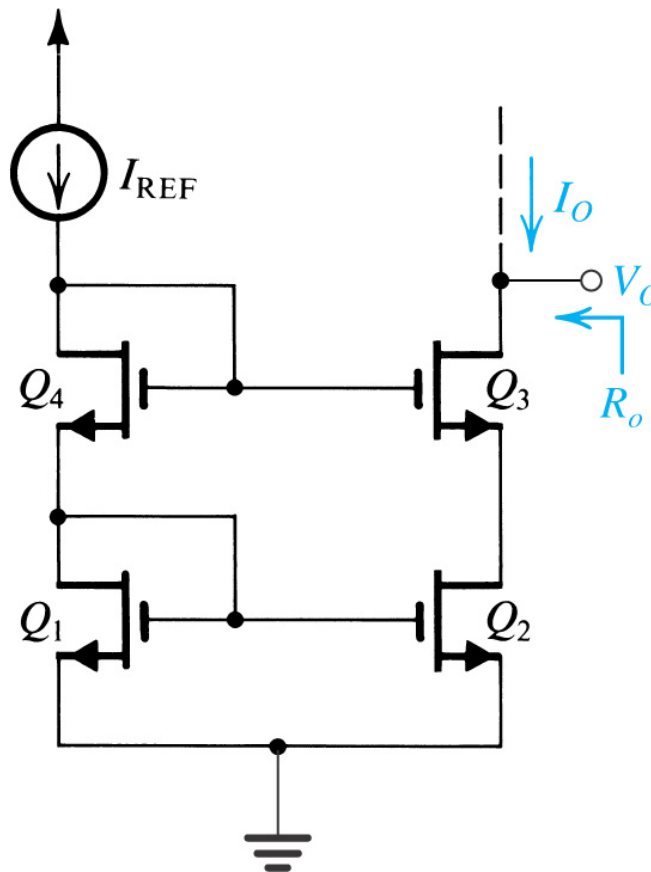- 1) Assume that $V_t = 0.5\text{V}$, $K'_n = 387\mu\text{A}/\text{V}^2$, $V'_A = 5\text{V}/\mu\text{m}$, $(W/L) = 3.6\mu\text{m}/0.36\mu\text{m}$, and $I_{\text{REF}} = 100\mu\text{A}$. Find R_{out} and V_{omin} .





Base-Current Compensation

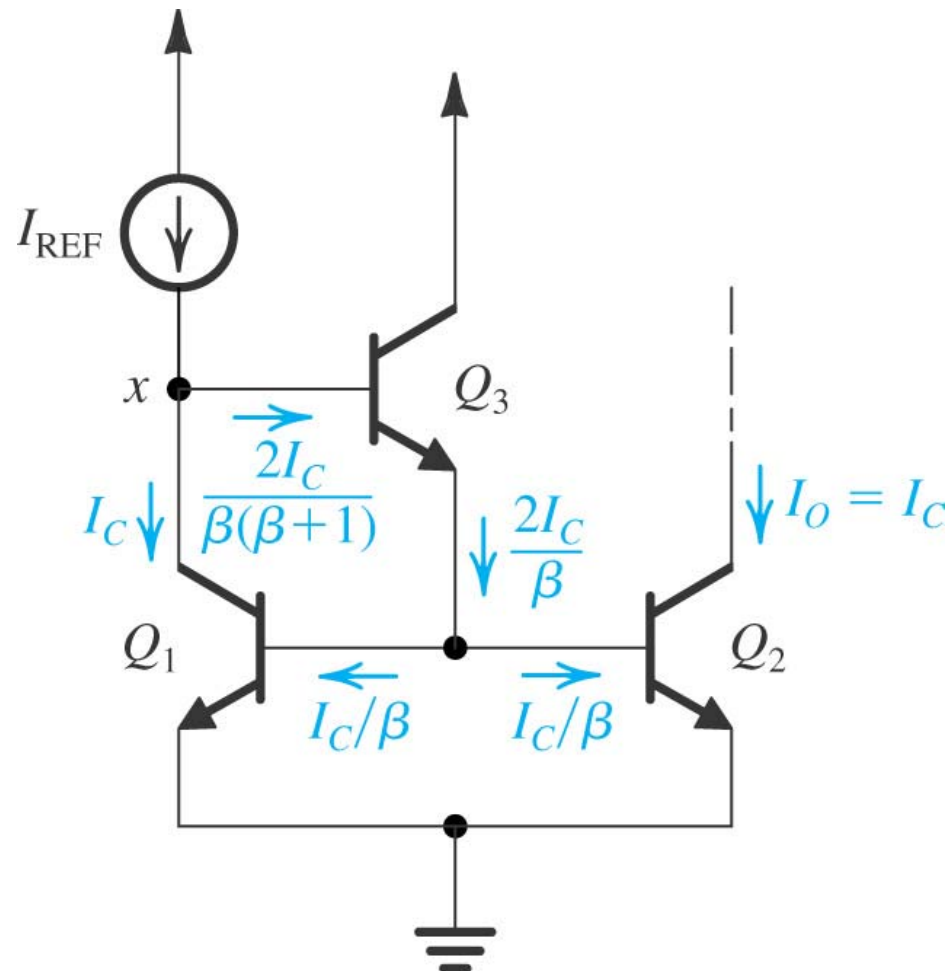

$$I_O = I_{REF} \left(\frac{1}{1 + \frac{2}{\beta^2}} \right)$$


$$R_O = r_{o2}$$

Wilson BJT Current Mirror

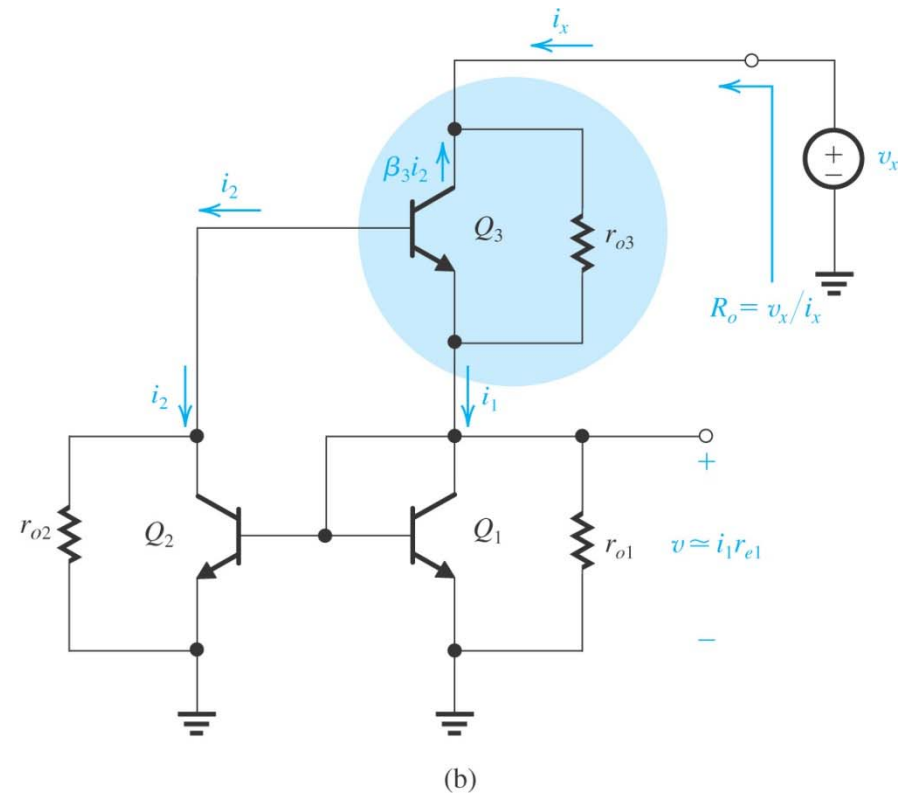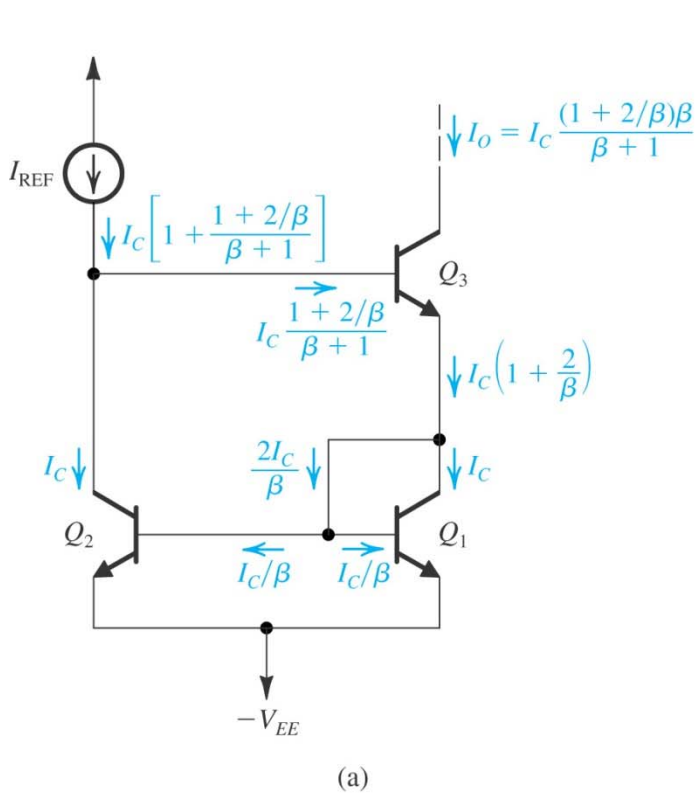



$$I_O \approx I_{REF} \left(\frac{1}{1 + \frac{2}{\beta^2}} \right)$$

$$R_O = \beta_3 r_{o3} / 2$$

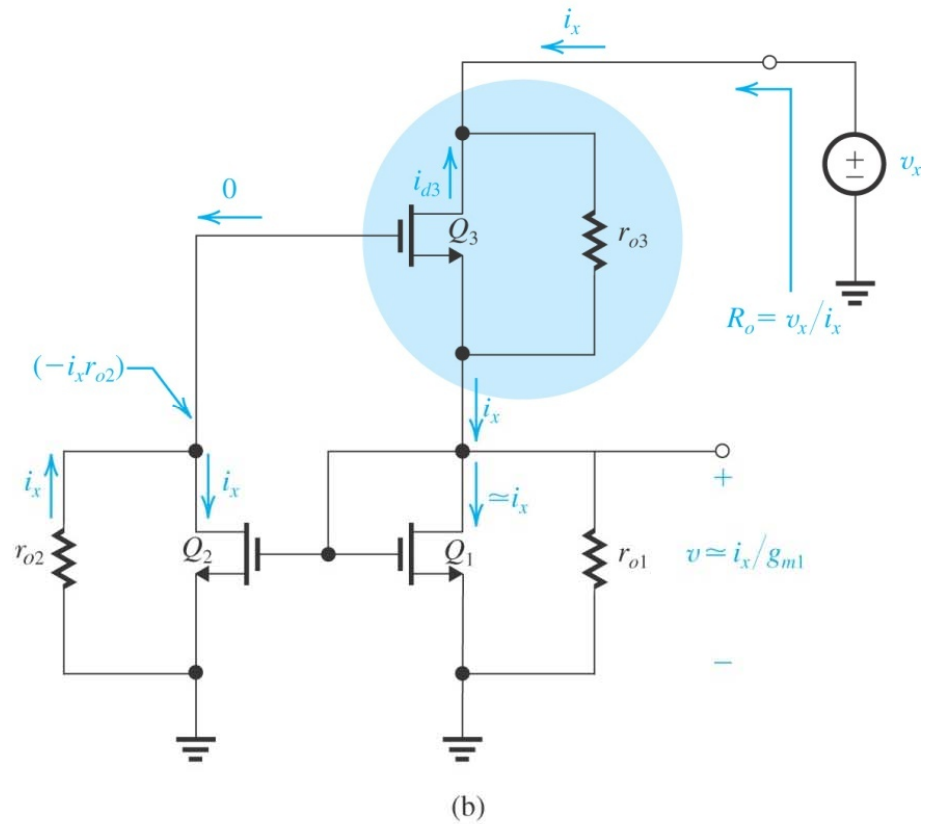


$$R_O = (g_{m3}r_{o3})r_{o2}$$

Modified Wilson MOS Current Mirror

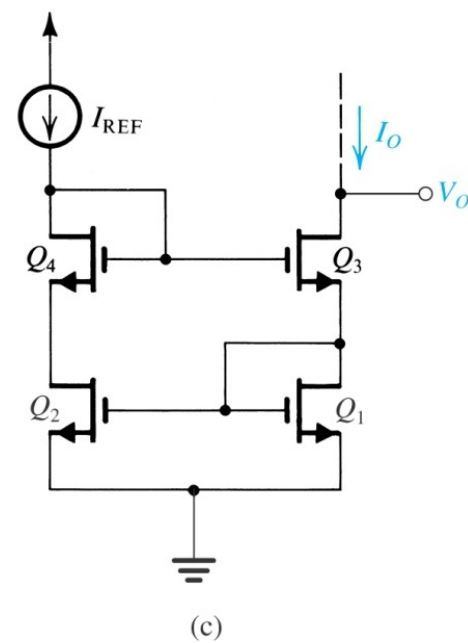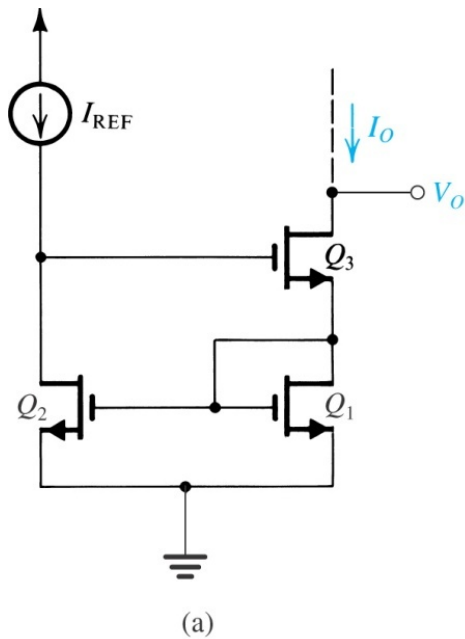

Widlar Current Compensation

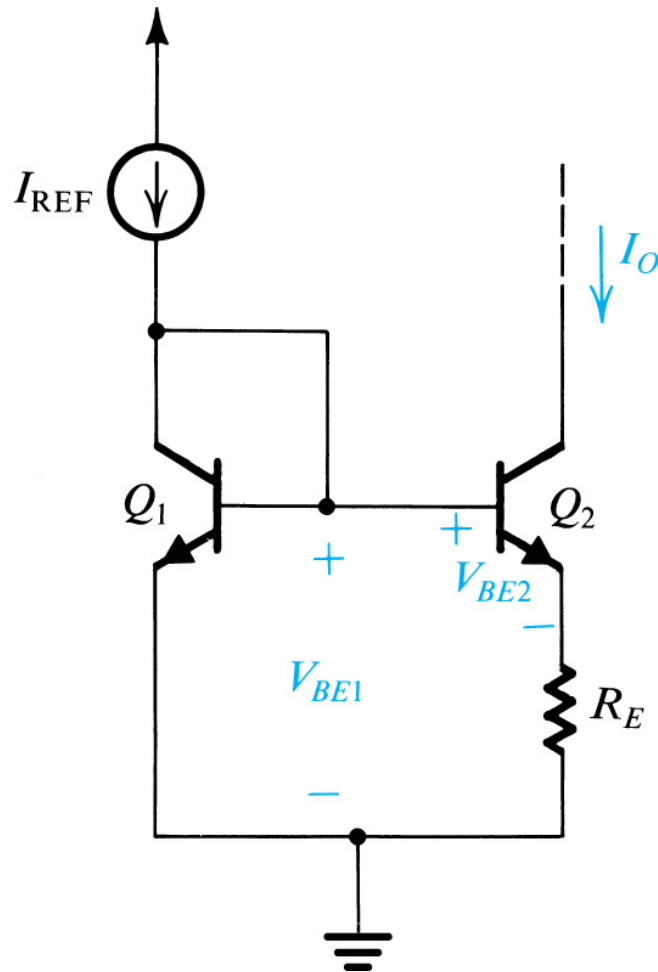


$$I_O R_E = V_T \ln \left(\frac{I_{REF}}{I_O} \right)$$


$$R_O \approx \left[1 + g_m (R_E \parallel r_\pi) \right] r_o$$

Example: Widlar Current Source Design

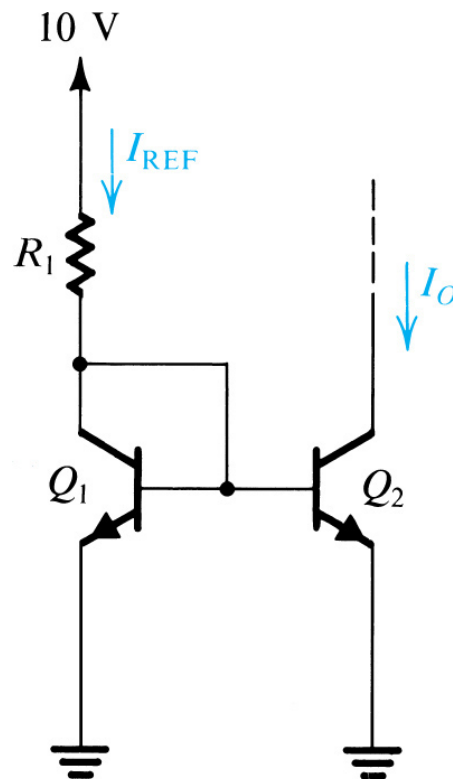- 1) Design the following circuits to get $I_O = 10\mu\text{A}$ with 10V supply. Assume that $V_{BE} = 0.7$ at 1mA and β is large.
- 2) If $V_A = 100\text{V}$ and $\beta = 100$, determine the R_{out} of the two circuits.



(a)

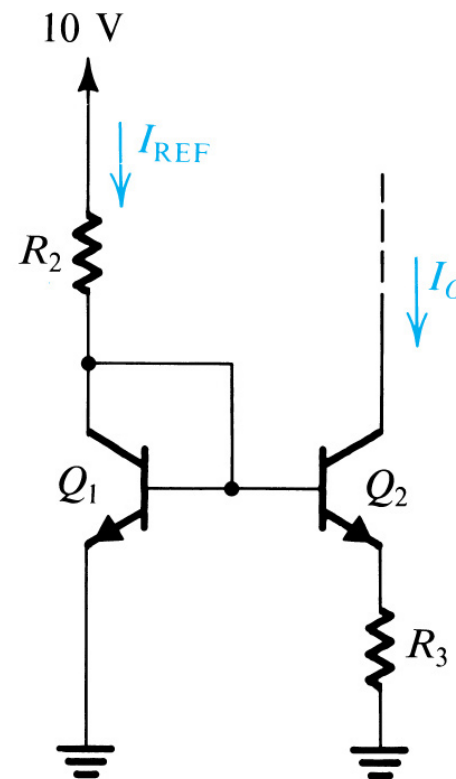

(b)